

# Single phase PWM inverter design

- Design requirement:

- Output voltage:  $U_o$  (V) ; Fundamental frequency  $f_1$  (Hz).
- Output power:  $S$  (kVA)

- Example:

$$U_{om} = 220\sqrt{2} = 311(V); f_1 = 50Hz; S = 1.25 \text{ kVA}$$

- Design step:

- 1. DC voltage calculation:  $V_{Bus}$  (V).

- Without over modulation, the modulation index  $\mu \leq 1$ , ex. choose  $\mu_{max} = 0,9$ .
- Then:  $V_{Bu} = U_{om}/0,9 = 311/0,9 = 346 \text{ V}$ .
- Normally, the drop voltage on the output filter can be chosen about 10% of the output voltage, then the minimum of required DC voltage can be calculated as following:  $V_{Bus\_min} = 1,1.346 = 380 \text{ V}$ .

Choose:  $V_{bus}=380V$

# Single phase PWM inverter design

- 2. Calculate the amplitude of the output current :  $I_{om}$  (A).
    - RMS value:  $I_o = S_o/U_o = 1250/220 = 5,68$  (A).
    - Amplitude value:  $I_{om} = I_o \cdot \sqrt{2} = 5,68 \cdot 1,4142 = 8$  (A).
  - 3. Choose switching frequency:  $f_s$  (Hz),
    - With low power inverter using IGBT, choose  $f_s = 20$  kHz, period:  $T_s = 0,5 \cdot 10^{-4}$  (s).
  - 4. IGBT and Diode calculation:
    - IGBT average current:
    - $I_V = 2,29$  A.
    - Diode average current:
    - $I_D = 0,26$  A.
- $$I_V = \frac{1}{2\pi} \int_{\varphi}^{\pi} I_{om} \sin(\theta - \varphi) d\theta = \frac{1 + \cos \varphi}{2\pi} I_{om}$$
- $$I_D = \frac{1}{2\pi} \int_0^{\varphi} I_{om} \sin(\theta - \varphi) d\theta = \frac{1 - \cos \varphi}{2\pi} I_{om}$$

IGBT and diode block voltage:  $V_{Bus}$

*Choose  $\cos \varphi = 0.8$  is the minimum load power factor*

# Single phase PWM inverter design

- 5. Inductor design

The voltage across the inductor is given as:

$$V = L_i \times \frac{di}{dt}$$

For the full-bridge inverter with an AC output, write the equation as:

$$\Rightarrow (V_{Bus} - V_O) = L_i \times \frac{\Delta i_{pp}}{D \times T_s} \Rightarrow \Delta i_{pp} = \frac{D \times T_s \times (V_{Bus} - V_O)}{L_i}$$

Where: D is duty circle


Replace duty circle  $D = \mu \cdot \sin(\omega t)$  and  $V_O = D \cdot V_{Bus}$ , then:

$$\Delta i_{pp} = \frac{V_{Bus} \times T_s \times m_a \times \sin(\omega t) \times (1 - m_a \sin(\omega t))}{L_i}$$

Maximum current ripple can be calculated as:

$$\Delta i_{pp}|_{max} = \frac{V_{Bus} \times T_s}{4 \times L_i}$$

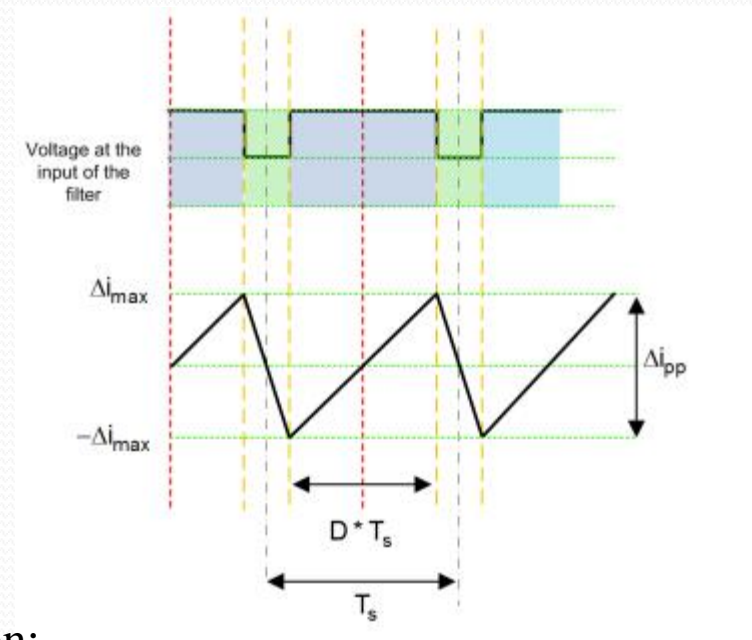When:  $\sin(\omega t) = \frac{1}{2 m_a}$



Current ripple calculation

# Single phase PWM inverter design

- 5. Inductor design

Normally, the current ripple  $\leq 30\%$  is tolerable by the inductor core, then the inductor can be calculated as following:

$$L_i = \frac{V_{Bus}}{4 \times F_{sw} \times \Delta i_{pp}|_{max}}$$

Example design: choose current ripple= 20%

$$L_i = \frac{380}{4.20000.0.2.5.68} = 4,18 (mH)$$

Check drop voltage condition (less than 10%)

$$\text{Drop voltage} = \omega_s L_i I_o = 2.3,14.50.4,18.10^{-3}.5,68 = 7,45V \approx 3.4\%$$

# Single phase PWM inverter design

- 6. Capacitance selection

- The output inductor and capacitor form a low pass filter that filters out the switching frequency. To get good switching frequency attenuation the cut off frequency is kept at  $f_{sw}/10$  or lower.
- Example design, choose  $\omega_{CL} = 0,1\omega_s \Rightarrow \omega_{CL} = 12,5664.10^3$  (rad/s)

Then:

$$C = \frac{1}{L} \frac{1}{\omega_{CL}^2} = \frac{1}{4.18.10^{-3}} \frac{1}{(12,5664.10^3)^2} = 1.51(\mu F)$$

## 5. Space vector modulation

### 5.1 Clark transformation (Alpha-beta transformation)

- Three phase voltage/current system  $X = (X_A, X_B, X_C)$ ,

if :  $X_a + X_b + X_c = 0$

By Clark transformation, it equal to a space vector:

$$\bar{u} = \frac{2}{3}(u_A + au_B + a^2u_C)$$

Where:  $a = e^{j\frac{2\pi}{3}} = -\frac{1}{2} + j\frac{\sqrt{3}}{2}$

- Express on Alpha-beta axis:

$\bar{u}$

$$\begin{cases} u_\alpha = \frac{1}{3}(2u_A - u_B - u_C) \\ u_\beta = \frac{1}{\sqrt{3}}(u_B - u_C) \end{cases}$$

- Express by transformation matrix:

$$\begin{bmatrix} u_\alpha \\ u_\beta \end{bmatrix} = \frac{2}{3} \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} [u_A u_B u_C]^T \\ = T_1 \cdot [u_A u_B u_C]^T$$

- If: 
$$\begin{cases} u_A = U^m \cos(\omega t) \\ u_B = U^m \cos\left(\omega t - \frac{2\pi}{3}\right) \\ u_C = U^m \cos\left(\omega t + \frac{2\pi}{3}\right) \end{cases}$$

- Then  $\bar{u}$  is rotating vector:

$$\bar{u} = U^m e^{j(\omega t)}$$

## 5. Space vector modulation

### 5.1 Clark transformation (Alpha-beta transformation)

- Three phase voltage/current system  $X = (X_A, X_B, X_C)$ ,

if :  $X_a + X_b + X_c = 0$

By Clark transformation, it equal to a space vector:

$$\bar{u} = \frac{2}{3}(u_A + au_B + a^2u_C)$$

Where:  $a = e^{j\frac{2\pi}{3}} = -\frac{1}{2} + j\frac{\sqrt{3}}{2}$

- Express on Alpha-beta axis:

$\bar{u}$

$$\begin{cases} u_\alpha = \frac{1}{3}(2u_A - u_B - u_C) \\ u_\beta = \frac{1}{\sqrt{3}}(u_B - u_C) \end{cases}$$

- Express by transformation matrix:

$$\begin{bmatrix} u_\alpha \\ u_\beta \end{bmatrix} = \frac{2}{3} \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} [u_A u_B u_C]^T \\ = T_1 \cdot [u_A u_B u_C]^T$$

- If: 
$$\begin{cases} u_A = U^m \cos(\omega t) \\ u_B = U^m \cos\left(\omega t - \frac{2\pi}{3}\right) \\ u_C = U^m \cos\left(\omega t + \frac{2\pi}{3}\right) \end{cases}$$

- Then  $\bar{u}$  is rotating vector:

$$\bar{u} = U^m e^{j(\omega t)}$$

# 5. Space vector modulation


## 5.2 Switching states and vectors

No	Van dẫn	$u_A$	$u_B$	$u_C$	$\bar{u}$
<b>U0</b>	V2, V4, V6	0	0	0	0
<b>U1</b>	V6, V1, V2	$\frac{2}{3}U_{DC}$	$-\frac{1}{3}U_{DC}$	$-\frac{1}{3}U_{DC}$	$\frac{2}{3}U_{DC}e^{-j0}$
<b>U2</b>	V1, V2, V3	$\frac{1}{3}U_{DC}$	$\frac{1}{3}U_{DC}$	$-\frac{2}{3}U_{DC}$	$\frac{2}{3}U_{DC}e^{j\frac{\pi}{3}}$
<b>U3</b>	V2, V3, V4	$-\frac{1}{3}U_{DC}$	$\frac{2}{3}U_{DC}$	$-\frac{1}{3}U_{DC}$	$\frac{2}{3}U_{DC}e^{j\frac{2\pi}{3}}$
<b>U4</b>	V3, V4, V5	$-\frac{2}{3}U_{DC}$	$\frac{1}{3}U_{DC}$	$\frac{1}{3}U_{DC}$	$\frac{2}{3}U_{DC}e^{-j\pi}$
<b>U5</b>	V4, V5, V6	$-\frac{1}{3}U_{DC}$	$-\frac{1}{3}U_{DC}$	$\frac{2}{3}U_{DC}$	$\frac{2}{3}U_{DC}e^{-j\frac{2\pi}{3}}$
<b>U6</b>	V5, V6, V1	$\frac{1}{3}U_{DC}$	$-\frac{2}{3}U_{DC}$	$\frac{1}{3}U_{DC}$	$\frac{2}{3}U_{DC}e^{-j\frac{\pi}{3}}$
<b>U7</b>	V1, V3, V5	0	0	0	0




# 5. Space vector modulation
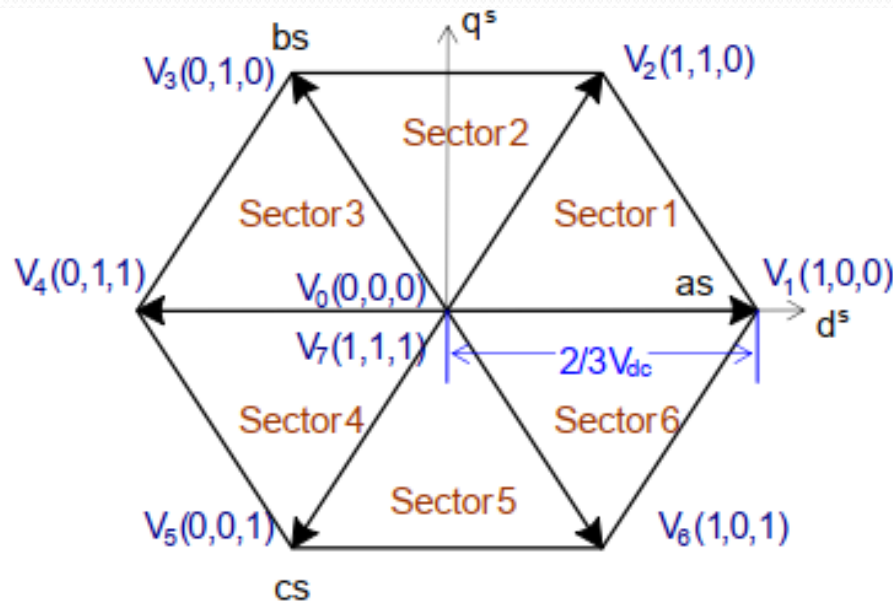
## 5.2 Switching states and space vectors





$V_1$	:	$(S_a, S_b, S_c) = (1, 0, 0);$
$V_2$	:	$(S_a, S_b, S_c) = (1, 1, 0);$
$V_3$	:	$(S_a, S_b, S_c) = (0, 1, 0);$
$V_4$	:	$(S_a, S_b, S_c) = (0, 1, 1);$
$V_5$	:	$(S_a, S_b, S_c) = (0, 0, 1);$
$V_6$	:	$(S_a, S_b, S_c) = (1, 0, 1);$
$V_7$	:	$(S_a, S_b, S_c) = (1, 1, 1);$
$V_0$	:	$(S_a, S_b, S_c) = (0, 0, 0).$

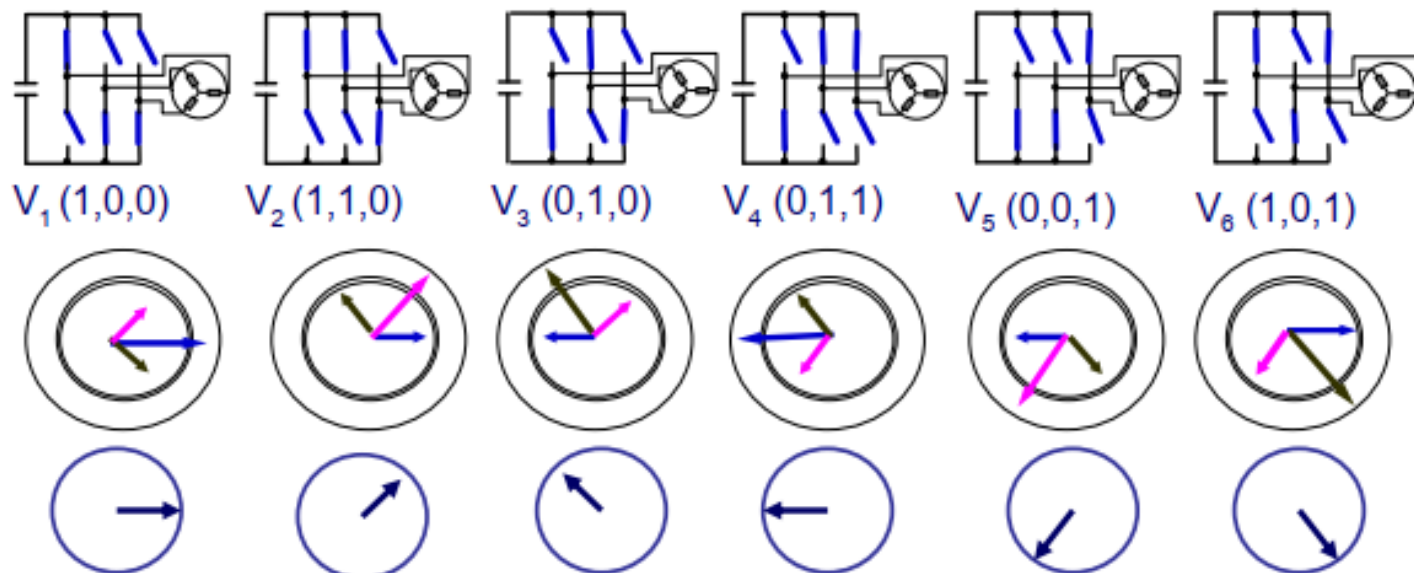


## 5. Space vector modulation

### 5.3 Modulation

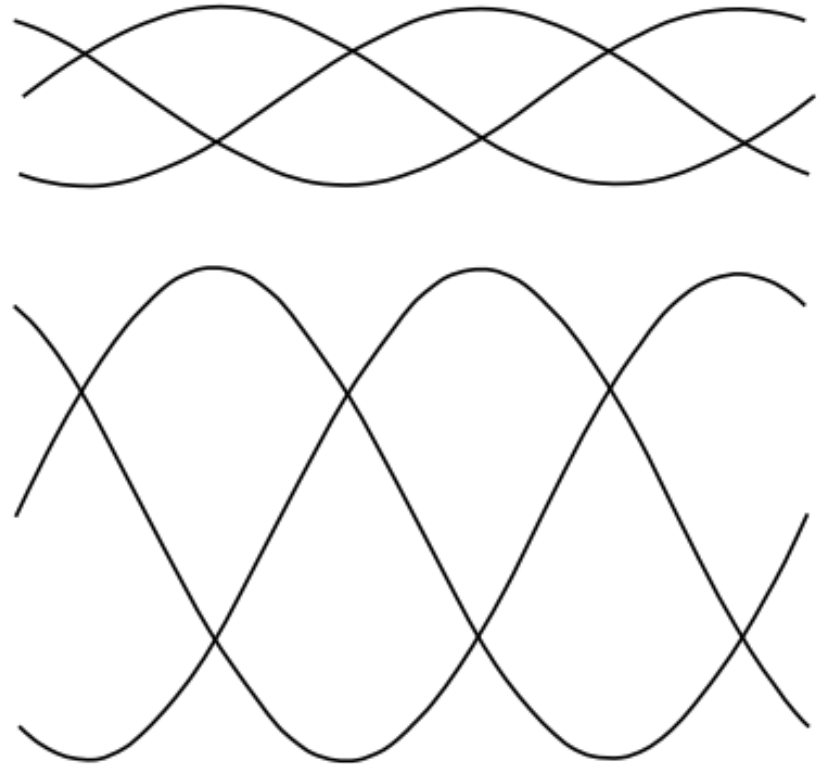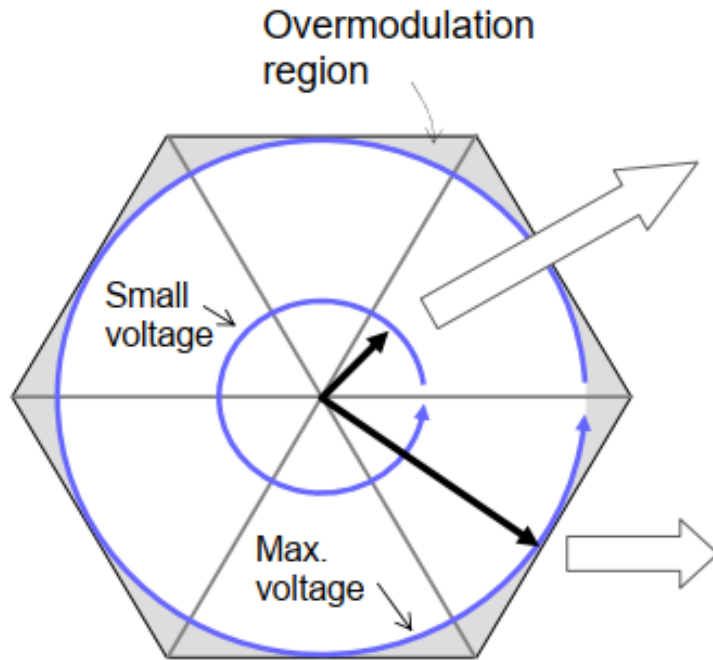

## 5. Space vector modulation

### 5.3 Modulation

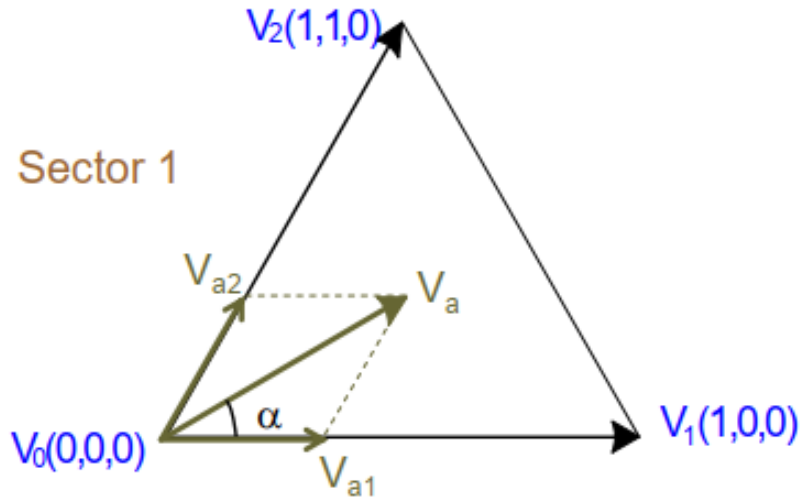

$$\frac{V_{a1}}{(2/3)V_{dc}} = \frac{T_1}{T_s},$$

$$\frac{V_{a2}}{(2/3)V_{dc}} = \frac{T_2}{T_s}.$$

$$\begin{aligned} \begin{bmatrix} v_d^s \\ v_q^s \end{bmatrix} &\equiv V_a \begin{bmatrix} \cos(\alpha) \\ \sin(\alpha) \end{bmatrix} = \frac{T_1 2}{T_s 3} V_{dc} \begin{bmatrix} 1 \\ 0 \end{bmatrix} + \frac{T_2 2}{T_s 3} V_{dc} \begin{bmatrix} \cos \frac{\pi}{3} \\ \sin \frac{\pi}{3} \end{bmatrix} \\ &= \frac{2 V_{dc}}{3 T_s} \begin{bmatrix} 1 & \cos \frac{\pi}{3} \\ 0 & \sin \frac{\pi}{3} \end{bmatrix} \begin{bmatrix} T_1 \\ T_2 \end{bmatrix}. \end{aligned}$$




$$\begin{bmatrix} T_1 \\ T_2 \end{bmatrix} = \frac{\sqrt{3} T_s}{V_{dc}} \begin{bmatrix} \sin \frac{\pi}{3} & -\cos \frac{\pi}{3} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} v_d^s \\ v_q^s \end{bmatrix}.$$

$$T_0 = T_s - T_1 - T_2$$

# 5. Space vector modulation


## 5.3 Modulation

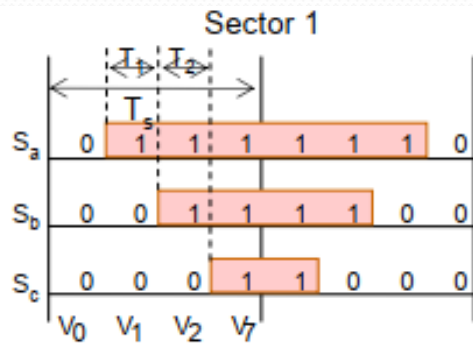

$$S_a = T_1 + T_2 + (T_s - T_1 - T_2)/2$$

$$S_b = T_2 + (T_s - T_1 - T_2)/2$$


$$S_c = (T_s - T_1 - T_2)/2$$

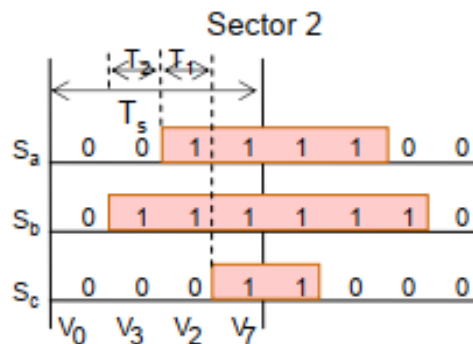

$$S_a = T_1 + (T_s - T_1 - T_2)/2$$

$$S_b = T_2 + T_1 + (T_s - T_1 - T_2)/2$$

$$S_c = (T_s - T_1 - T_2)/2$$

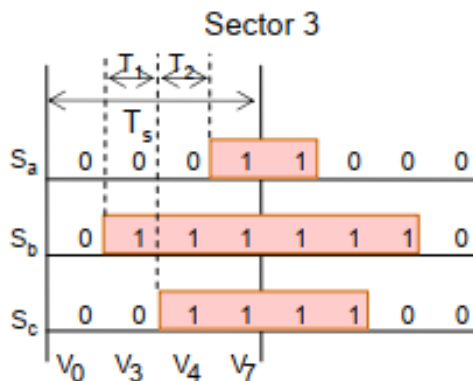


$$S_a = (T_s - T_1 - T_2)/2$$

$$S_b = T_1 + T_2 + (T_s - T_1 - T_2)/2$$

$$S_c = T_2 + (T_s - T_1 - T_2)/2$$

# 5. Space vector modulation


## 5.3 Modulation

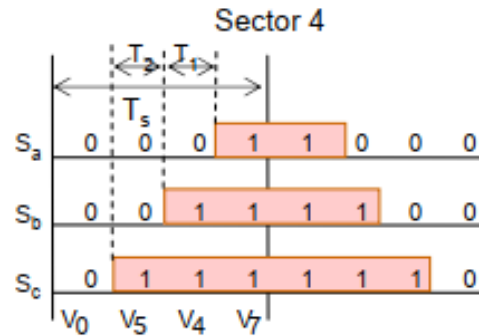

$$S_a = (T_s - T_1 - T_2)/2$$

$$S_b = T_1 + (T_s - T_1 - T_2)/2$$

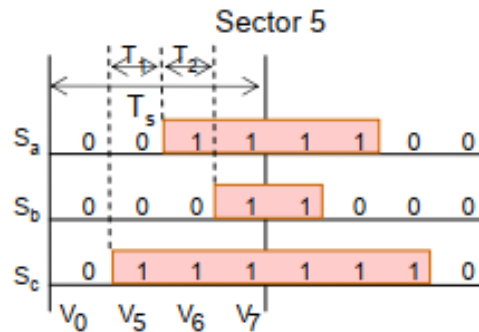
$$S_c = T_2 + T_1 + (T_s - T_1 - T_2)/2$$



$$S_a = T_2 + (T_s - T_1 - T_2)/2$$

$$S_b = (T_s - T_1 - T_2)/2$$
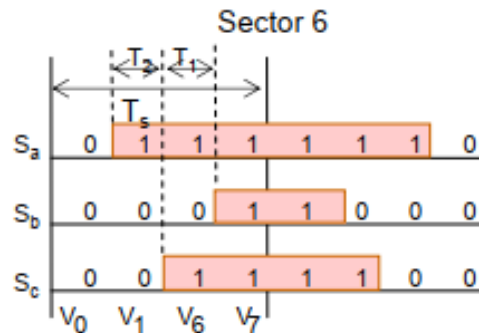
$$S_c = T_1 + T_2 + (T_s - T_1 - T_2)/2$$




$$S_a = T_2 + T_1 + (T_s - T_1 - T_2)/2$$

$$S_b = (T_s - T_1 - T_2)/2$$

$$S_c = T_1 + (T_s - T_1 - T_2)/2$$

## 5. Space vector modulation

### 5.4 Sector finding method

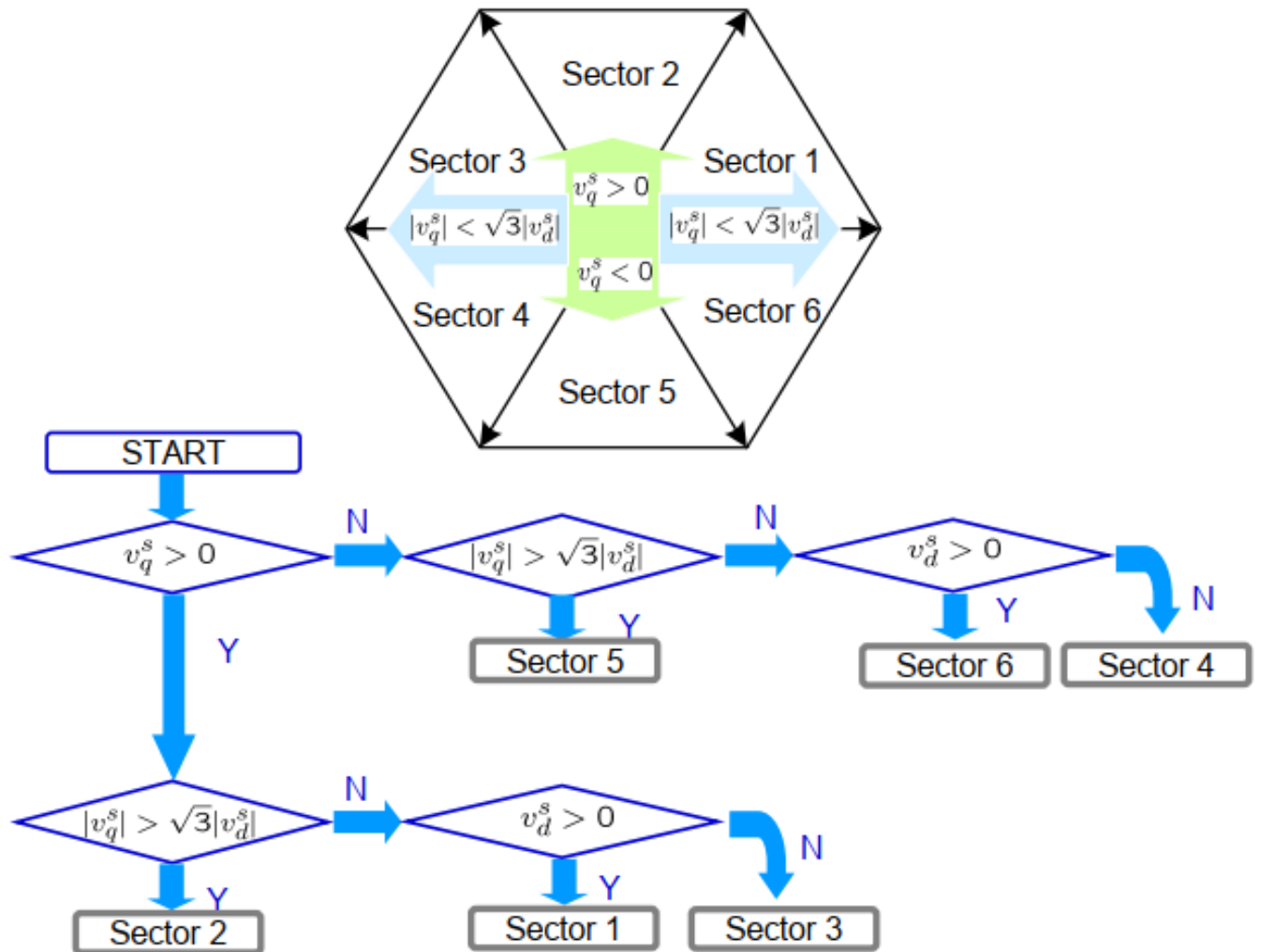


## 5. Space vector modulation

### 5.5 SPWM versus SVPWM

#### ▪ SPWM

$$V_{o,\max} = \frac{1}{2}V_{dc}$$

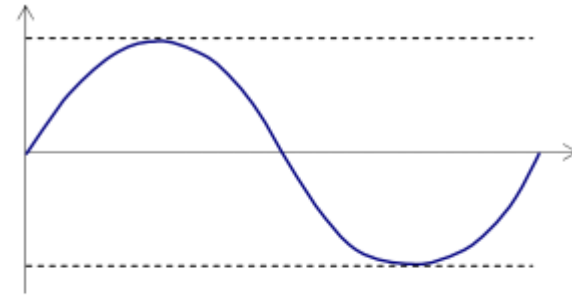

#### ▪ SVPWM

- Voltage Usage : 15.5% increase
- No of switching decreases.

$$V_{o,\max} = \frac{\sqrt{3}}{2} \frac{2}{3} V_{dc}$$

