

Fundamentals of Electric Circuits

DC Circuits

Chapter 5. Operational Amplifiers

- 5.1. Introduction
- 5.2. Operational amplifiers
- 5.3. Ideal Op Amp
- 5.4. Inverting – Non-inverting amplifier
- 5.5. Summing amplifier
- 5.6. Difference amplifier
- 5.7. Cascaded Op Amp circuits
- 5.8. Applications

Operational Amplifiers

5.1. Introduction

- + **Operational amplifier** (*op amp*) → an electronic unit that behaves like a **voltage-controlled voltage** source
- + **Op amp can**: **sum**, **amplify**, **integrate**, or **differentiate** a signal
- + **Op amp are popular** in practical circuit designs because they are **versatile**, **inexpensive**, **easy to use**,...
- + **In this chapter**:
 - **Ideal op amp** first and the **non-ideal op amp** later
 - **Op amp circuits**: the inverter, voltage follower, summer and difference amplifier
 - **Using nodal analysis** as a tool to analyze circuits

5

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Operational Amplifiers

5.2. Operational Amplifiers

+ **Op amp** → an **active circuit element** designed to **perform mathematical operations** of **addition, subtraction, multiplication, division, differentiation, and integration**


+ **Op amp** → an **electronic device** consisting of a **complex arrangement of resistor, transistor, capacitor, and diodes** → **treat them as a circuit building block, study what takes place at its terminals**

+ **Several important terminals** in an op amp:


- **inverting input**: pin 2 (-)
- **non-inverting input**: pin 3 (+)
- **output**: pin 6
- **positive power supply** V^+ : pin 7
- **negative power supply** V^- : pin 4



An op amp package

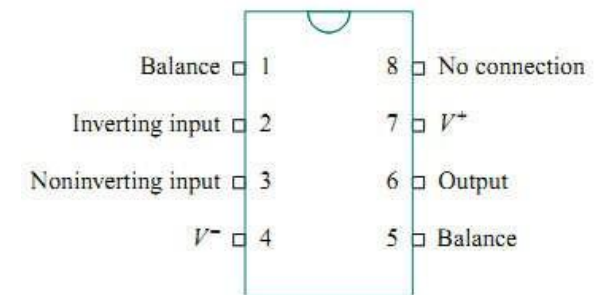

Dual in-line package of op amp

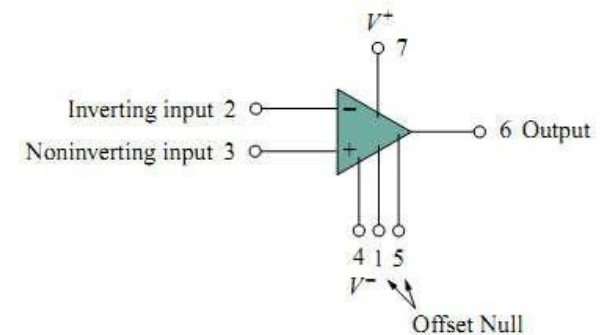


Operational Amplifiers

5.2. Operational Amplifiers

+ An op amp: → must be powered by a voltage supply:


- often ignored in op amp circuit diagram
- power supply currents must not be overlook

$$i_0 = i_1 + i_2 + i_+ + i_-$$

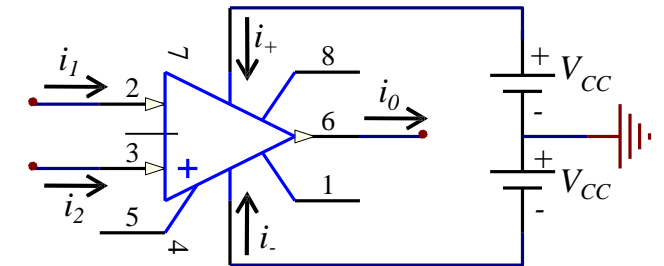

+ Equivalent circuit model of a non-ideal op amp:

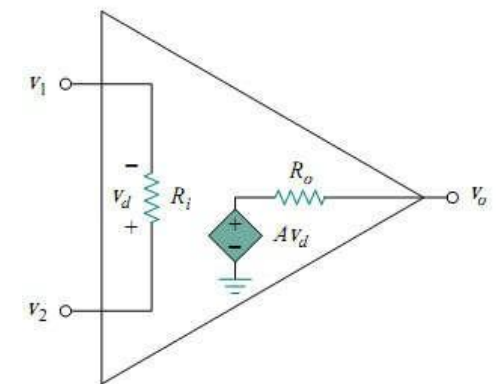- **Output section:** Voltage-controlled source $A.v_d$ in series with output resistance R_o
- R_i : Thevenin equivalent resistance seen at input terminals
- R_o : Thevenin equivalent resistance seen at the output
- Output voltage: $v_0 = A.v_d = A(v_2 - v_1)$



The equivalent circuit of the non-ideal op amp

A : **Open-loop voltage gain** (gain of the op amp without any external feedback from output to input)

5

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Operational Amplifiers


5.2. Operational Amplifiers

+ Typical parameter values of op am:

Parameter	Typical range	Ideal value
Open-loop gain, A	$10^5 - 10^8$	∞
Input resistance, R_i	$10^6 - 10^{13} \Omega$	$\infty \Omega$
Output resistance, R_o	$10 - 100 \Omega$	0Ω
Supply voltage, V_{cc}	$5 - 24 \text{ V}$	

+ Modes of operation: 3 (depending on the v_o)

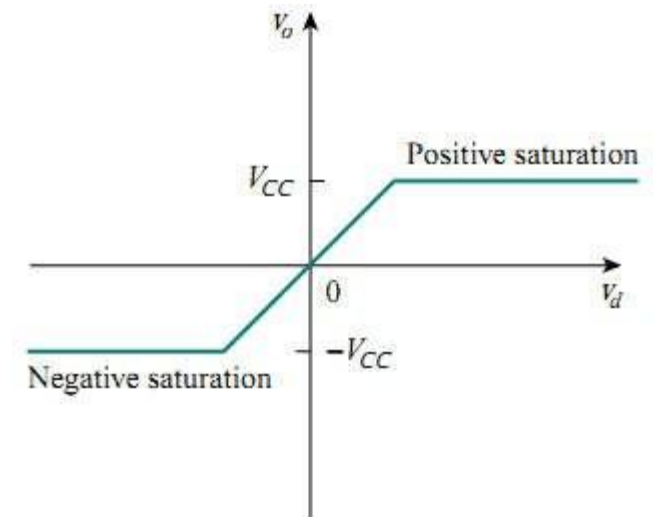- Positive saturation: $v_o = V_{cc}$
- Linear region: $-V_{cc} \leq v_o = A \cdot v_d \leq V_{cc}$
- Negative saturation: $v_o = -V_{cc}$



5

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Operational Amplifiers

5.2. Operational Amplifiers

+ **Example 1:** Find the closed-loop gain V_o / V_s . Determine current i when $V_s = 2V$

From op amp equivalent circuit → applying the nodal analysis:

At node 1:
$$\frac{V_s - V_1}{R_1} - \frac{V_1 - V_o}{R_2} - \frac{V_1}{R_i} = 0 \rightarrow V_1 = \frac{2V_s + V_o}{3}$$



At node 0:
$$\begin{cases} \frac{V_1 - V_o}{R_2} = \frac{V_o - AV_d}{R_o} \\ V_d = -V_1 \end{cases} \rightarrow V_1 - V_o = 400(V_o + 2.10^6 V_1)$$

So we have a set of equations:
$$\begin{cases} V_1 - \frac{V_o}{3} = \frac{2}{3} V_s \\ (1 - 800.10^6) V_1 - 401 V_o = 0 \end{cases}$$

When $V_s = 2V$:

$$\begin{cases} V_1 = 20.067 \mu V \\ i = \frac{V_1 - V_o}{R_2} = 0.2 mA \end{cases} \quad \frac{V_o}{V_s} = -1.9999$$

741 parameter	Value
Open-loop gain, A	2.10^5
Input resistance, R_i	$2 M \Omega$
Output resistance, R_o	50Ω

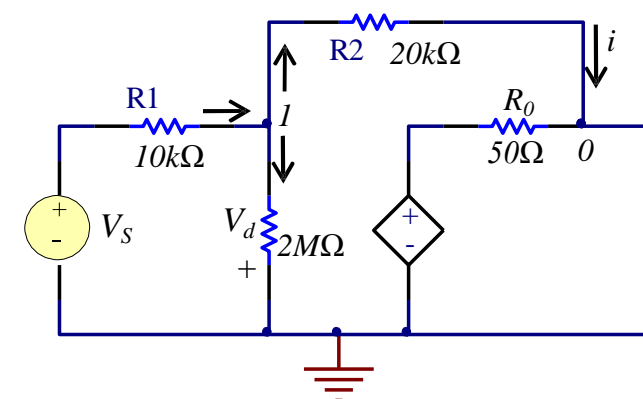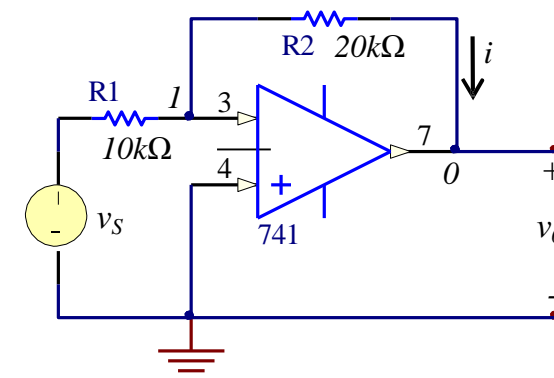

Operational Amplifiers

5.3. Ideal Operational Amplifier

+ **Ideal op amp** → an amplifier with **infinite open-loop gain** ($A = \infty$), **infinite input resistance** ($R_i = \infty$), and **zero output resistance** ($R_o = 0$).


+ **Important characteristics** of an ideal op amp:

- **Currents** into both input terminals are zero

$$i_1 = 0 \quad ; \quad i_2 = 0$$

- **Voltage** across the input terminals is small
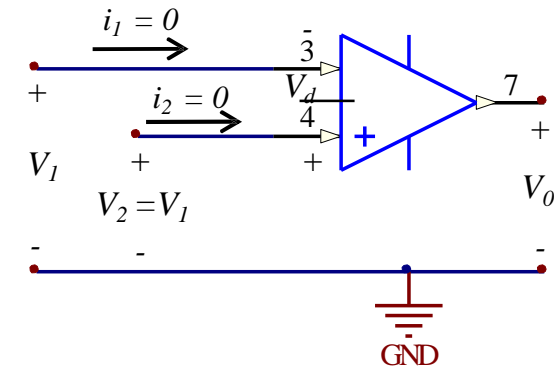
$$V_d = V_2 - V_1 = 0 \quad ; \quad V_1 = V_2$$



Operational Amplifiers

5.3. Ideal Operational Amplifier

+ **Example 2:** Considering 741 op amp as an ideal op amp. Calculate the V_o/V_s and find i_o when $v_s = 1V$

As an ideal op amp, we have: $V_2 = V_s$


Since $i_1 = 0 \rightarrow R_1$ and R_2 are in series

$$V_1 = \frac{V_o}{R_1 + R_2} R_1 = \frac{V_o}{9} \quad V_2 = V_1 \rightarrow V_s = \frac{V_o}{9}$$

$$\text{KCL at node 0: } i_o = \frac{V_o}{R_1 + R_2} + \frac{V_o}{20 \cdot 10^3} = \frac{9V_s}{R_1 + R_2} + \frac{9V_s}{20 \cdot 10^3}$$

So when $v_s = 1V$:
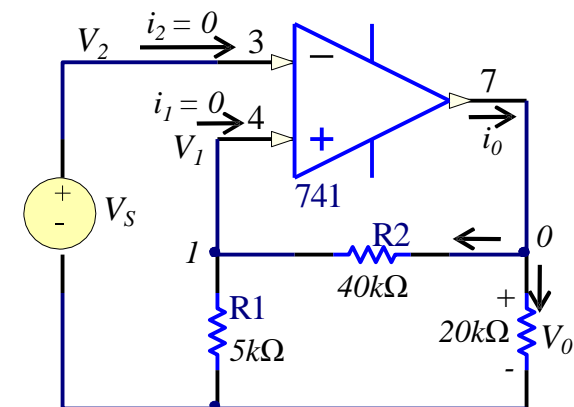
$$\begin{cases} \frac{V_o}{V_s} = 9 \\ i_o = 0.65mA \end{cases}$$



Operational Amplifiers

5.4. Inverting – Non-inverting Amplifier

5.4.1. Inverting Amplifier

+ Apply KCL at node 1



Ideal op amp

$$\left. \begin{aligned} i_1 = i_2 &\rightarrow \frac{V_i - V_1}{R_1} = \frac{V_1 - V_0}{R_2} \\ V_1 = V_2 &= 0 \end{aligned} \right\} \rightarrow V_0 = -\frac{R_2}{R_1} V_i$$

+ Note:

$$A_v = -\frac{R_2}{R_1} \rightarrow \text{voltage gain depends only on the external elements connected to the op amp}$$

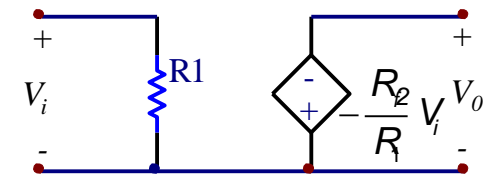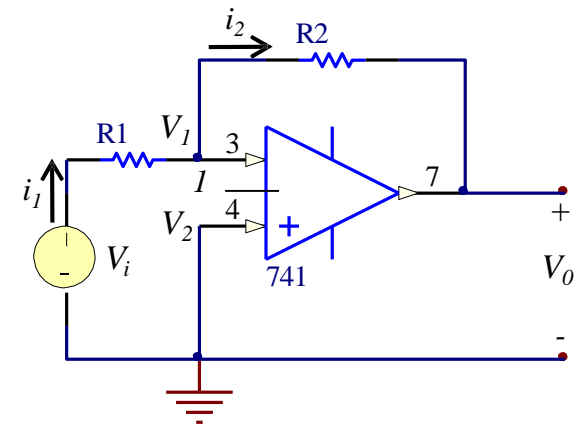- Both the input signal and the feedback are applied at the inverting terminal of the op amp
- Inverting amplifier is used in a current to voltage converter



Operational Amplifiers

5.4. Inverting – Non-inverting Amplifier


5.4.1. Inverting Amplifier

+ **Example 3:** Calculate the output voltage v_o and the current through R_1 and R_2 if $v_i = 0.5V$

For inverting amplifier:
$$V_o = -\frac{R_2}{R_1} V_i = -\frac{25}{10} \cdot 0.5 = -1.25V$$

The current through the R_1 :
$$i_{R1} = \frac{V_i - 0}{R_1} = \frac{0.5}{10^4} = 50\mu A$$

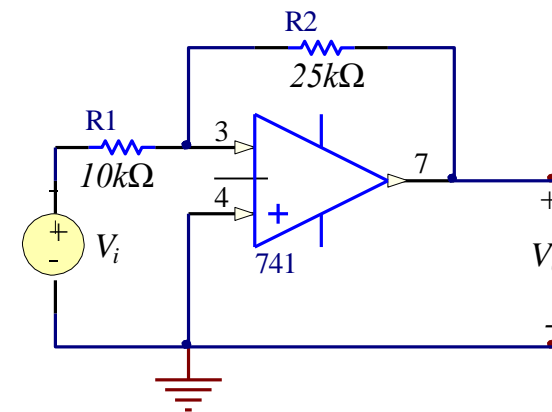The current through the R_2 :
$$i_{R2} = \frac{0 - V_o}{R_2} = \frac{1.25}{25 \cdot 10^3} = 50\mu A$$



Operational Amplifiers

5.4. Inverting – Non-inverting Amplifier


5.4.1. Inverting Amplifier

+ **Example 4:** Calculate the output voltage v_o of the given circuit

KCL at node 3:

$$\left. \begin{array}{l} \frac{6 - V_3}{R_1} = \frac{V_3 - V_o}{R_2} \\ V_3 = 4 \end{array} \right\} \rightarrow V_o = V_3 - R_2 \frac{6 - V_3}{R_1}$$
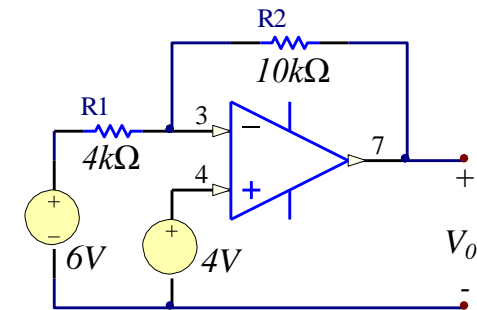
$$\rightarrow V_o = 4 - 10 \frac{6 - 4}{4} = -1V$$



Operational Amplifiers


5.4. Inverting – Non-inverting Amplifier

5.4.2. Non-Inverting Amplifier

+ *Non-inverting amplifier* → op amp circuit designed to provide a positive voltage gain

- Input voltage V_i is applied directly at the **non-inverting** input terminal
- R_1 is connected **between** the **ground** and the **inverting terminal**
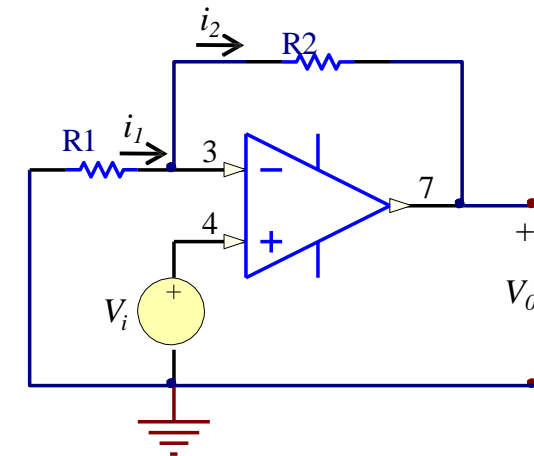
$$\left. \begin{array}{l} \frac{0 - V_3}{R_1} = \frac{V_3 - V_0}{R_2} \\ V_3 = V_i \end{array} \right\} \rightarrow \frac{V_0}{R_2} = \frac{V_i}{R_1} + \frac{V_i}{R_2} \rightarrow V_0 = \left(1 + \frac{R_2}{R_1} \right) V_i$$



Operational Amplifiers

5.4. Inverting – Non-inverting Amplifier



5.4.2. Non-Inverting Amplifier

+ Note:

If $R_2 = 0$ or $R_1 = \infty \rightarrow$ the voltage gain becomes 1
 \rightarrow the circuit is called a *voltage follower* (or *unity gain amplifier*)

+ Characteristic of voltage follower:

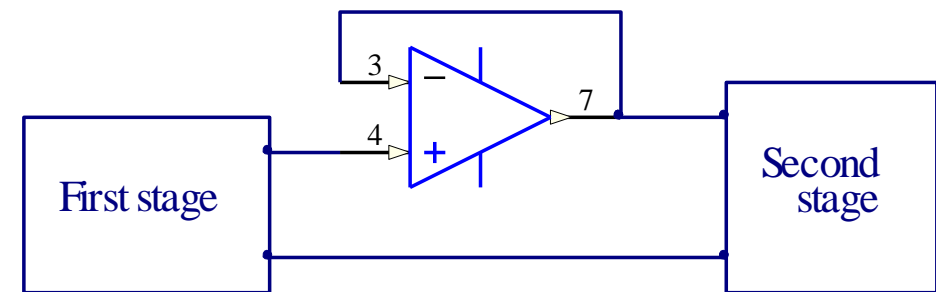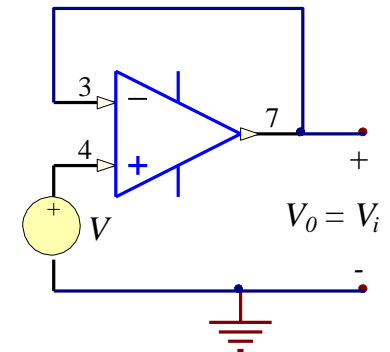- Very high input impedance
- Useful as an *intermediate – stage* (or *buffer*) amplifier to isolate one circuit from another
- Minimize *interaction* between the two stages and *eliminate inter-stage loading*




Voltage follower used to isolate two cascaded stages of a circuit

Operational Amplifiers

5.4. Inverting – Non-inverting Amplifier

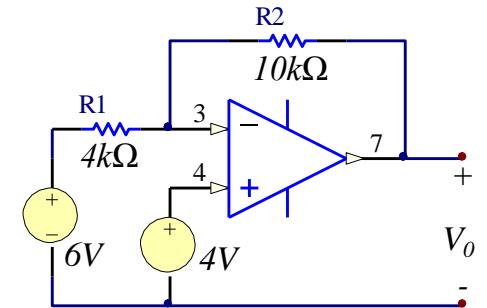5.4.2. Non-Inverting Amplifier

+ **Example 5:** Calculate the output voltage v_o of the given circuit



Using superposition: $V_o = V_{o1} + V_{o2}$

V_{o1} is due to the 6V voltage source V_{o2} is due to the 4V voltage source

Calculate V_{o1} : Set the 4V voltage source to zero, the circuit becomes an inverting amplifier

$$V_{o1} = -\frac{R_2}{R_1} V_{i1} = -\frac{10}{4} 6 = -15V$$

Calculate V_{o2} : Set the 6V voltage source to zero, the circuit becomes a non-inverting amplifier

$$V_{o2} = \left(1 + \frac{R_2}{R_1}\right) V_{i2} = \left(1 + \frac{10}{4}\right) 4 = 14V$$

So we obtain the output voltage: $V_o = V_{o1} + V_{o2} = -1V$

Operational Amplifiers

5.4. Inverting – Non-inverting Amplifier


5.4.2. Non-Inverting Amplifier

+ **Example 6:** Calculate the output voltage v_o of the given circuit

Apply KCL at node 3 and 4:

$$\left\{ \begin{array}{l} -\frac{V_P}{R_4} + \frac{V_i - V_P}{R_3} = 0 \\ -\frac{V_N}{R_1} + \frac{V_0 - V_N}{R_2} = 0 \\ V_N = V_P \end{array} \right. \rightarrow \left\{ \begin{array}{l} V_i = \frac{R_3 + R_4}{R_4} V_P \\ V_0 = \frac{R_1 + R_2}{R_1} V_P \end{array} \right.$$
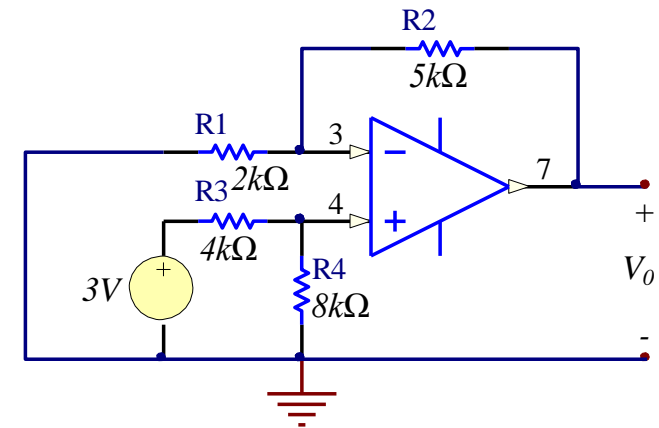
$$\rightarrow V_0 = \frac{R_1 + R_2}{R_1} \cdot \frac{R_4}{R_3 + R_4} V_i = \frac{2+5}{2} \cdot \frac{8}{4+8} \cdot 3 = 7V$$



Operational Amplifiers

5.5. Summing Amplifier

+ **Summing amplifier** → op amp circuit that combines several inputs and produces an output that is the weighted sum of the inputs


+ **Summing amplifier** → a variation of the inverting amplifier

+ **As an example**, for the given circuit, apply KCL at node a:

$$i = i_1 + i_2 + i_3 \rightarrow \frac{V_a - V_0}{R_f} = \frac{V_1 - V_a}{R_1} + \frac{V_2 - V_a}{R_2} + \frac{V_3 - V_a}{R_3}$$

Because of $V_a = V_4 = 0$:
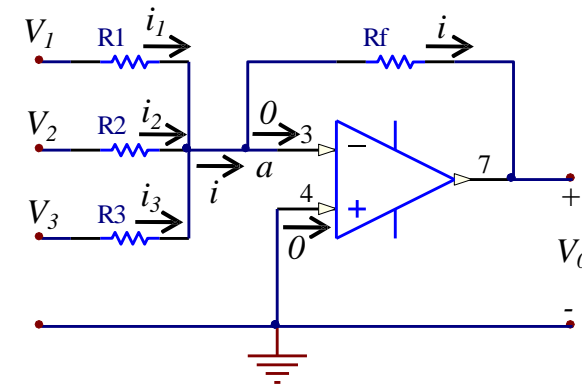
$$V_0 = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3\right)$$




Operational Amplifiers

5.5. Summing Amplifier

+ **Example 7:** Calculate the output voltage v_o and i_o of the given circuit

Apply the equation of summing amplifier to calculate V_o
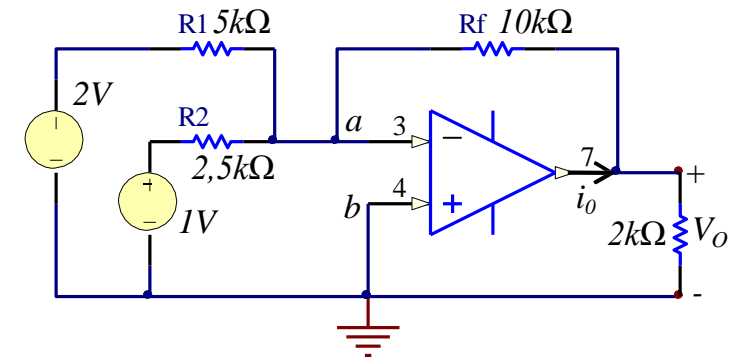
$$V_o = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2\right) = -\left(\frac{10}{5} \cdot 2 + \frac{10}{2,5} \cdot 1\right) = -8V$$



Calculate the current i_o

$$i_o + i_f = i_{load} \rightarrow i_o = i_{load} - i_f = \frac{V_o}{R_{load}} - \frac{0 - V_o}{R_f} = -\frac{8}{2 \cdot 10^3} - \frac{8}{10 \cdot 10^3} = -4.8mA$$


Operational Amplifiers

5.6. Difference Amplifier

+ **Difference (differential) amplifier** → circuit that **amplifies** the difference between two inputs but **rejects** any signals common to the two inputs

KCL at **node a**:
$$\frac{V_1 - V_a}{R_1} = \frac{V_a - V_0}{R_2} \rightarrow V_0 = \left(1 + \frac{R_2}{R_1}\right)V_a - \frac{R_2}{R_1}V_1$$

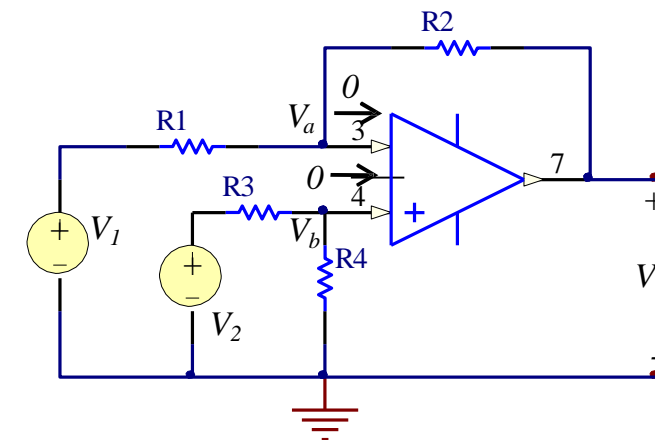KCL at **node b**:
$$\frac{V_2 - V_b}{R_3} = \frac{V_b}{R_4} \rightarrow V_b = \left(\frac{R_4}{R_3 + R_4}\right)V_2$$



Output voltage:

$$V_a = V_b \rightarrow V_0 = \left(\frac{R_1 + R_2}{R_1}\right)\left(\frac{R_4}{R_3 + R_4}\right)V_2 - \frac{R_2}{R_1}V_1 \rightarrow V_0 = \frac{R_2}{R_1} \frac{\left(1 + \frac{R_1}{R_2}\right)}{\left(1 + \frac{R_3}{R_4}\right)} V_2 - \frac{R_2}{R_1}V_1$$

Operational Amplifiers

5.6. Difference Amplifier

+ A **difference amplifier** must reject a signal common to the two inputs: $V_o = 0$ when $V_1 = V_2$

$$\rightarrow \frac{R_1}{R_2} = \frac{R_3}{R_4}$$


+ So the output voltage of a difference amplifier:

$$V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

+ If $R_2 = R_1$, and $R_3 = R_4 \rightarrow$ the difference amplifier becomes a subtractor: $V_o = V_2 - V_1$

+ Remarks

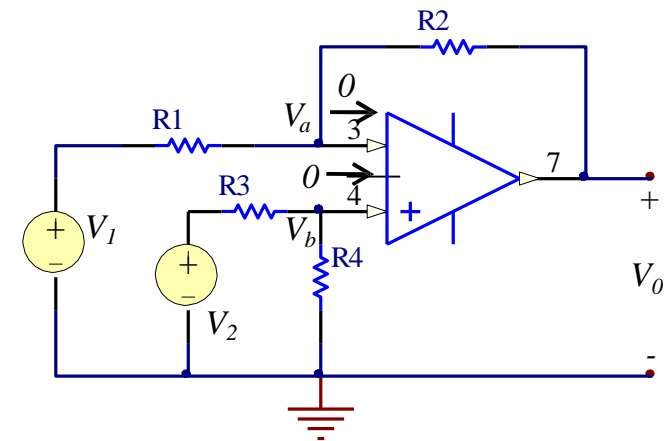- A difference amplifier \rightarrow also known as a **subtractor**
- Difference amplifier \rightarrow used in various applications (**instrumentation amplifier**)



Operational Amplifiers

5.6. Difference Amplifier

+ **Example 8:** Design an op amp circuit with inputs V_1 and V_2 such that $V_0 = -5V_1 + 3V_2$

Solution 1: Using only one op amp

Rewrite:
$$V_0 = 5\left(\frac{3}{5}V_2 - V_1\right)$$

From the output voltage equation of a difference amplifier:

$$V_0 = \frac{R_2}{R_1} \frac{\left(1 + \frac{R_1}{R_2}\right)}{\left(1 + \frac{R_3}{R_4}\right)} V_2 - \frac{R_2}{R_1} V_1 \rightarrow \begin{cases} \frac{R_2}{R_1} = 5 & (1) \\ \frac{\left(1 + \frac{1}{5}\right)}{1 + \frac{R_3}{R_4}} = \frac{3}{5} \end{cases}$$

and from:
$$\frac{\frac{6}{5}}{1 + \frac{R_3}{R_4}} = \frac{3}{5} \rightarrow 1 + \frac{R_3}{R_4} = 2 \rightarrow R_3 = R_4 \quad (2)$$

From (1) and (2), we can choose: $R_1 = 10k\Omega \rightarrow R_2 = 50k\Omega$

$$R_3 = 20k\Omega \rightarrow R_4 = 20k\Omega$$

Operational Amplifiers

5.6. Difference Amplifier

+ **Example 8:** Design an op amp circuit with inputs V_1 and V_2 such that $V_0 = -5V_1 + 3V_2$

Solution 2: Using 2 op amp \rightarrow one inverting amplifier and one 2-inputs inverting summer


Output voltage of the first stage:

$$V_a = -\frac{3R_1}{R_1} V_2 = -3V_2$$

Output voltage of the second stage:

$$V_0 = -\left(\frac{5R_1}{R_1} V_1 + \frac{5R_1}{5R_1} V_2\right) = -(5V_1 - 3V_2) = -5V_1 + 3V_2$$

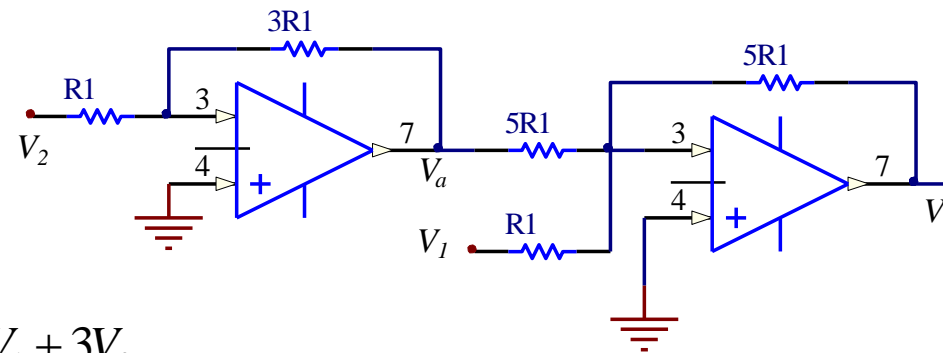In this case, we can choose: $R_1 = 10k\Omega$



Operational Amplifiers

5.6. Difference Amplifier

+ **Example 9:** Find the relationship between V_o and two inputs of an instrumentation amplifier

There are not current into A_1 , and A_2 , the current i flows through the 3 resistors


$$V_{01} - V_{02} = i(2R_3 + R_4)$$

$$i = \frac{V_a - V_b}{R_4} \quad V_a = V_1, V_b = V_2 \rightarrow i = \frac{V_1 - V_2}{R_4}$$

Therefore:
$$V_{01} - V_{02} = (V_1 - V_2) \left(1 + 2 \frac{R_3}{R_4} \right)$$

In this case, we have the output voltage of the difference amplifier:
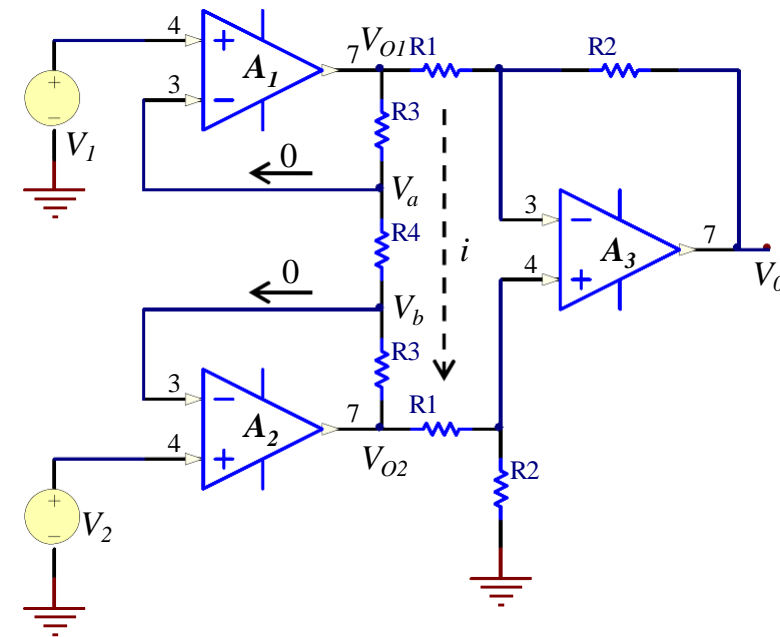
$$V_o = \frac{R_2}{R_1} (V_{02} - V_{01}) \rightarrow V_o = \frac{R_2}{R_1} \left(1 + 2 \frac{R_3}{R_4} \right) (V_2 - V_1)$$




Operational Amplifiers

5.6. Difference Amplifier

+ **Example 10:** Find the current i_o of the given instrumentation amplifier circuit

$$V_o = \frac{R_2}{R_1} (V_{i+} - V_{i-}) = \frac{40}{20} (8.01 - 8) = 0.02V$$
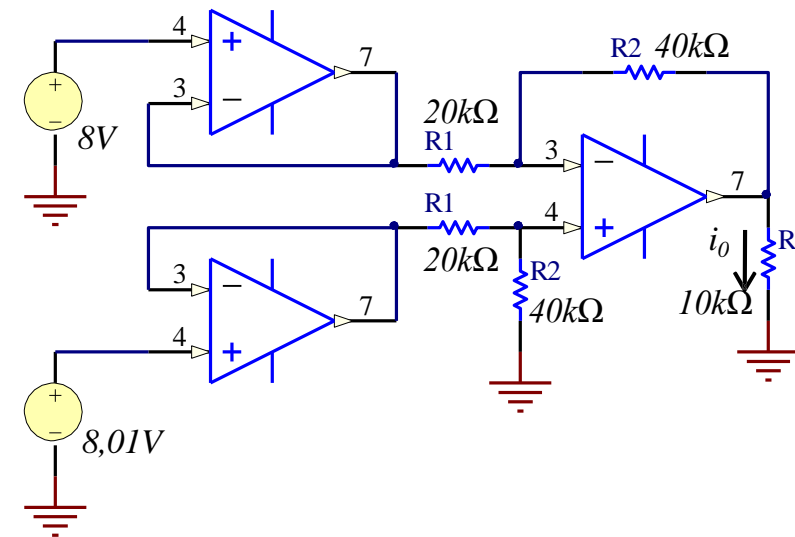
$$i_o = \frac{V_o}{R_3} = \frac{0.02}{10 \cdot 10^3} = 2\mu A$$



Operational Amplifiers

5.7. Cascaded op amp Circuit


+ **Cascade connection:** head-to-tail arrangement of two or more op amp circuits such that the output of one is the input of the next

→ Each op amp circuit in the string is called a *stage*

→ Op amp circuits can be cascaded without changing their input-output relationship because of:

- Infinite input resistance
- Zero output resistance

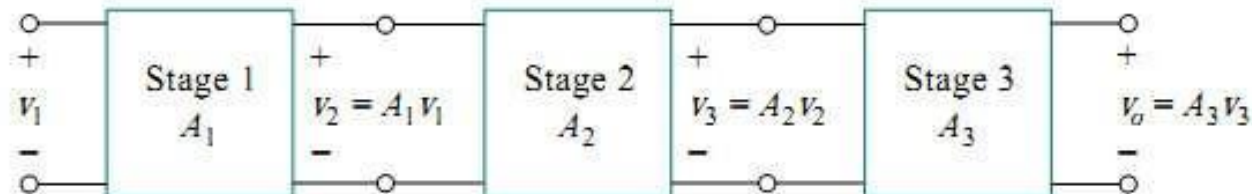+ **In cascaded connection:** The original input signal is increased by the gain of the individual stage



$$A = A_1 \cdot A_2 \cdot A_3$$

Operational Amplifiers

5.7. Cascaded op amp Circuit

+ Example 11: Find the voltage v_o and the current i_o of the given circuit

The cascaded circuit consists of two non-inverting amplifiers


Output of the first stage:

$$V_a = \left(1 + \frac{R_1}{R_2}\right) V_i = \left(1 + \frac{12}{3}\right) \cdot 20 = 100 \text{ mV}$$

Output of the second stage:

$$V_o = \left(1 + \frac{R_3}{R_4}\right) V_a = \left(1 + \frac{10}{4}\right) \cdot 100 = 350 \text{ mV}$$

The current i_o flows through the resistor R_3 :
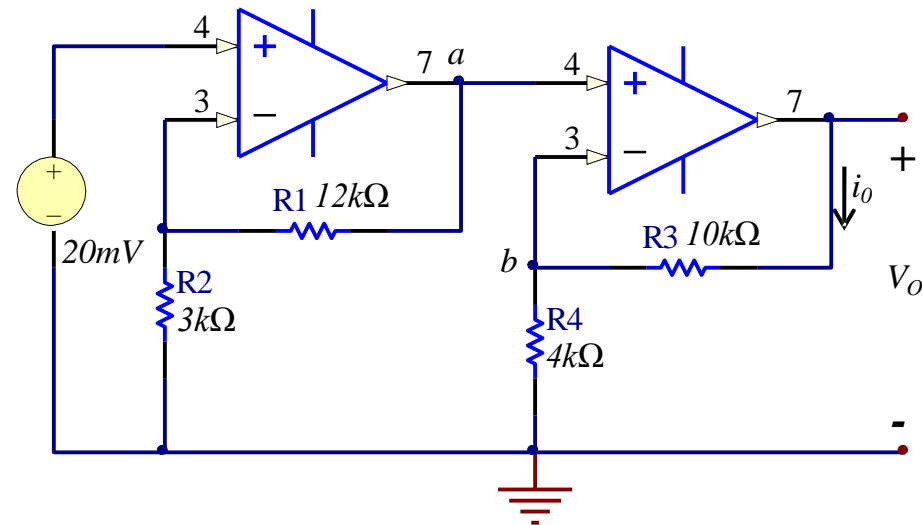
$$i_o = \frac{V_o - V_b}{R_3} = \frac{V_o - V_a}{R_3} = \frac{350 - 100}{10 \cdot 10^3} = 25 \mu\text{A}$$


Operational Amplifiers

5.7. Cascaded op amp Circuit

+ **Example 12:** Find the voltage v_o of the given circuit


Circuit consists of two inverters A and B and a summer C

$$V_a = -\frac{R_2}{R_1} V_1 = -\frac{6}{2} \cdot 1 = -3V$$

$$V_b = -\frac{R_4}{R_3} V_2 = -\frac{8}{4} \cdot 2 = -4V$$

Output of the given circuit:
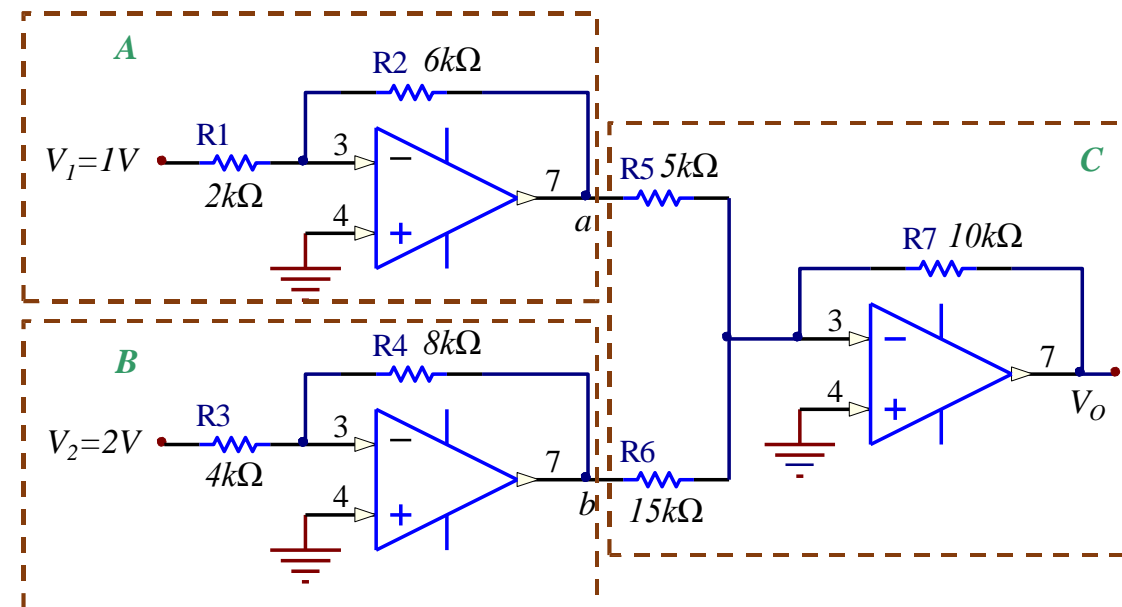
$$V_o = -\left(\frac{R_7}{R_5} V_a + \frac{R_7}{R_6} V_b\right) = \left(\frac{10}{5} 3 + \frac{10}{15} 4\right) = 8.66V$$



Operational Amplifiers


5.7. Cascaded op amp Circuit

+ **Example 13:** Find V_o if $V_1 = 2V$, $V_2 = 1.5V$

$$V_{21} = V_1 = 2V$$

$$V_{22} = -\frac{R_2}{R_3} V_2 = -\frac{50}{15} \cdot 1.5 = -5V$$
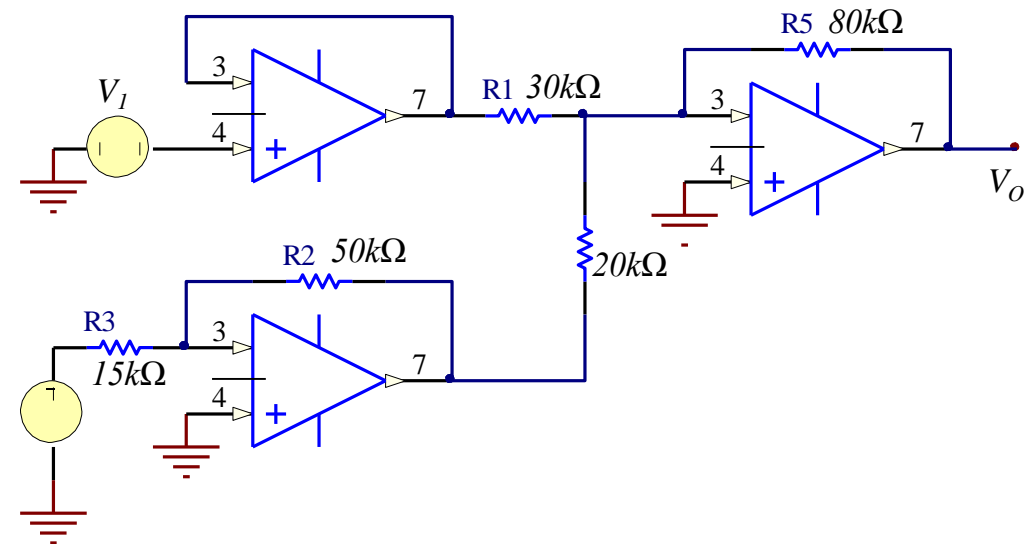
$$V_o = -\left(\frac{R_5}{R_1} V_{21} + \frac{R_5}{R_4} V_{22}\right) = -\left(\frac{80}{30} \cdot 2 - \frac{80}{20} \cdot 5\right) = 14.67V$$



Operational Amplifiers

5.8. Applications

+ **Practical applications** of op amp circuits:

- Inverters, summers, integrators, differentiators, subtractors, logarithmic amplifiers
- **Instrumentation amplifiers**, calibration circuits
- **DAC**, voltage-to-current converters, current-to-voltage converter
- Analog computers
- Filters, clippers, rectifier, regulators, level shifters
- Comparators, gyrators, oscillator

Operational Amplifiers

5.8. Applications


5.8.1. DAC – Digital to Analog Converter

+ Digital-to-analog converter (DAC):

- Transforms digital signals into analog form
- Can be realized by using the binary weighted ladder
 - The bits are weights according to the magnitude of their place value
 - Their weights decrease value of $R_f/R_n \rightarrow$ each lesser bit has half the weight of the next higher

$$V_0 = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3 + \frac{R_f}{R_4}V_4\right)$$

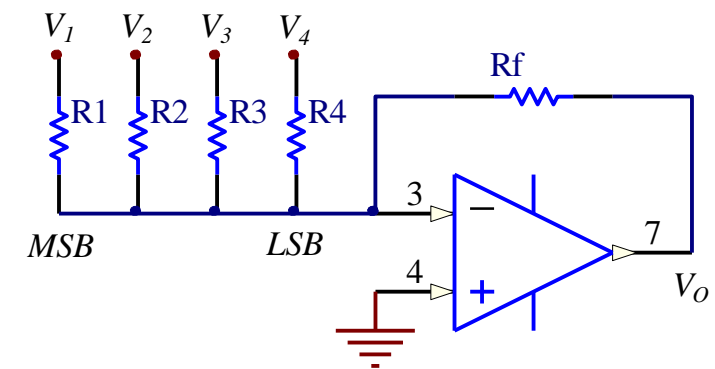- V_1, \dots, V_4 can assume only two voltage levels (0, 1) (binary code) \rightarrow DAC provides a single output that is proportional to the inputs



Binary weighted ladder type

Operational Amplifiers

5.8. Applications

5.8.1. DAC – Digital to Analog Converter


+ **Example 14:** Obtain the analog output for binary inputs [0000], [0001], [0010], ... [1111]

Inputs [B]	Value [D]	$-V_0$
0000	0	0
0001	1	0.125
0010	2	0.25
0011	3	0.375
0100	4	0.5
0101	5	0.625
0110	6	0.75
0111	7	0.875
1000	8	1.0
1001	9	1.125
...		
1111	15	1.875

$$V_0 = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3 + \frac{R_f}{R_4}V_4\right)$$

$$V_0 = -(V_1 + 0.5V_2 + 0.25V_3 + 0.125V_4)$$

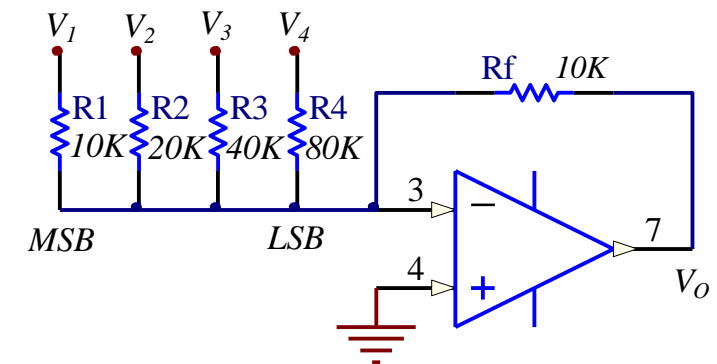Each bit has a value of 0.125V → cannot represent a voltage between 1V → 1.125V (*DAC resolution*)



Operational Amplifiers

5.8. Applications

5.8.2. Instrumentation Amplifier (IA)



+ **Typical applications of IAs:** isolation amplifiers, thermocouple amplifiers, data acquisition systems

+ **Output voltage of IAs:**

$$V_0 = \left(1 + \frac{2R}{R_G}\right)(V_2 - V_1)$$

Small differential signal voltages superimposed on larger common-mode voltages

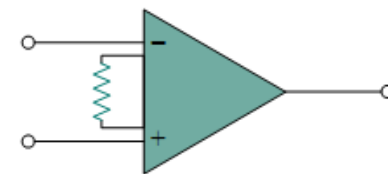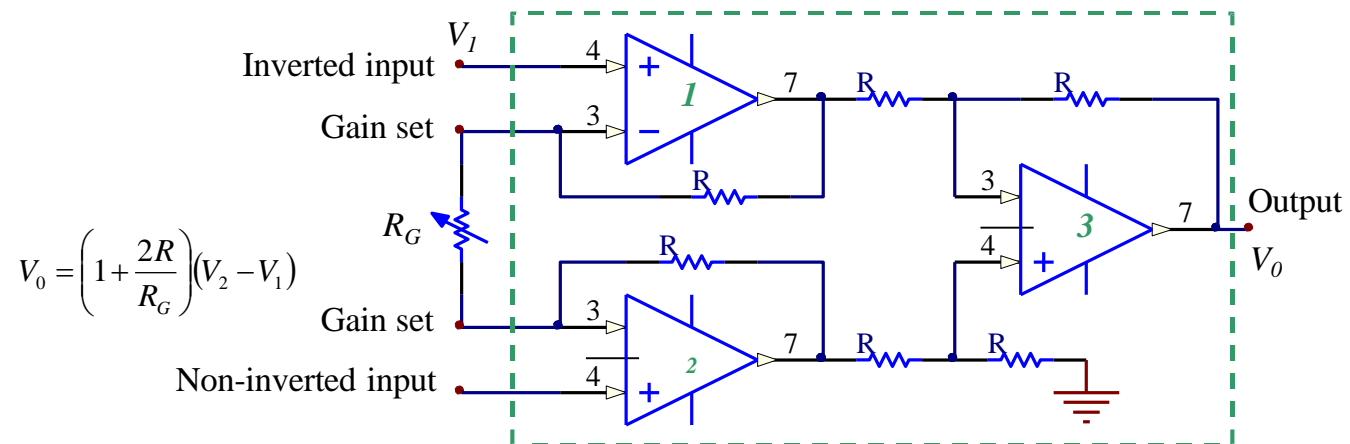Since the common-mode voltages are equal, they cancel each other




Schematic diagram


Operational Amplifiers

5.8. Applications


5.8.2. Instrumentation Amplifier

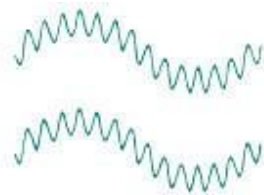

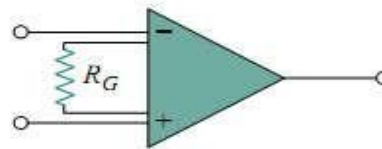Small differential signals riding on larger common-mode signals



Instrumentation amplifier

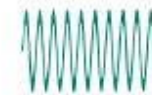

Amplified differential signal,
No common-mode signal

+ Three main characteristics:

- *Voltage gain is adjusted* by one external resistor R_G
- *Input impedance of both inputs is very high* and does *not vary* as the gain is adjusted
- *Output V_O depends on the difference* between the inputs V_1 and V_2 , not on the voltage common to them (common-mode voltage)

5

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Operational Amplifiers

5.8. Applications

5.8.2. Instrumentation Amplifier

+ Precision Intrumentation amplifier AD624

CMRR: *Common Mode Rejection Ratio*

PSRR: *Power Supply Rejection Ratio*

TC: *Temperature Change*

FEATURES

Low Noise: 0.2 μV p-p 0.1 Hz to 10 Hz

Low Gain TC: 5 ppm max ($G = 1$)

Low Nonlinearity: 0.001% max ($G = 1$ to 200)

High CMRR: 130 dB min ($G = 500$ to 1000)

Low Input Offset Voltage: 25 μV , max

Low Input Offset Voltage Drift: 0.25 $\mu\text{V}/^\circ\text{C}$ max

Gain Bandwidth Product: 25 MHz

Pin Programmable Gains of 1, 100, 200, 500, 1000

No External Components Required

Internally Compensated


Price (100 - 499)

Price (1000)

\$4.82

\$4.09

FUNCTIONAL BLOCK DIAGRAM

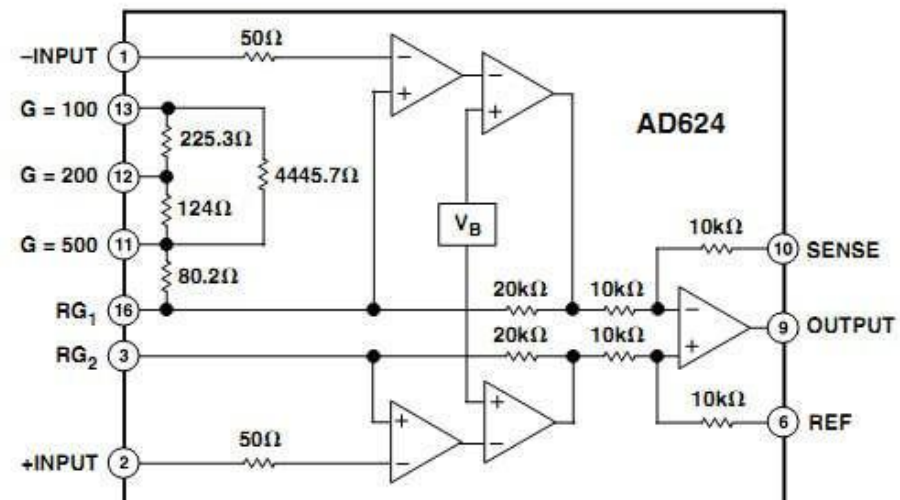

Datasheet:


http://www.analog.com/static/imported-files/data_sheets/AD620.pdf

Operational Amplifiers

5.8. Applications

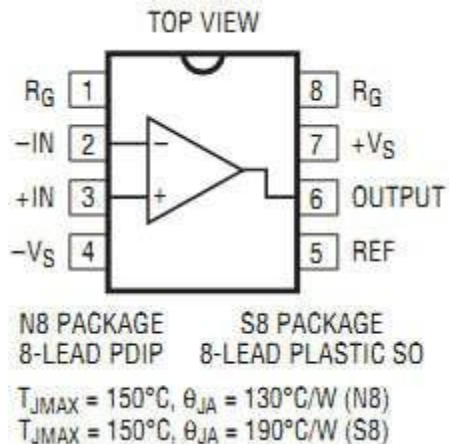5.8.2. Instrumentation Amplifier

+ LT167 – Single resistor gain, programmable, precision instrumentation amplifier



APPLICATIONS

- Bridge Amplifiers
- Strain Gauge Amplifiers
- Thermocouple Amplifiers
- Differential to Single-Ended Converters
- Medical Instrumentation

FEATURES

- Single Gain Set Resistor: $G = 1$ to 10,000
- Gain Error: $G = 10$, 0.08% Max
- Input Offset Voltage Drift: $0.3\mu\text{V}/^{\circ}\text{C}$ Max
- Meets IEC 1000-4-2 Level 4 ESD Tests with Two External 5k Resistors
- Gain Nonlinearity: $G = 10$, 10ppm Max
- Input Offset Voltage: $G = 10$, 60 μV Max
- Input Bias Current: 350pA Max
- PSRR at $G = 1$: 105dB Min
- CMRR at $G = 1$: 90dB Min
- Supply Current: 1.3mA Max
- Wide Supply Range: $\pm 2.3\text{V}$ to $\pm 18\text{V}$
- 1kHz Voltage Noise: $7.5\text{nV}/\sqrt{\text{Hz}}$
- 0.1Hz to 10Hz Noise: $0.28\mu\text{V}_{P-P}$
- Available in 8-Pin PDIP and SO Packages