

Subject: Power electronic (EE3410E) – Problems

1. Design converter with the parameters as following:

- Input : 48VDC \pm 15%
 - Output : 12V, 5A with the ripple of voltage is $\pm 2\%$
 - Switching frequency: 100 kHz
- a) Design the topology of converter, explain the operating principle of converter.
- b) Calculate the essential parameters, choose the MOSFET, diode, and other device on the circuit.

(Guide: When design the output inductor and capacitor should choose: $\Delta I = 30\% I_{out}$. And the $\Delta U = 1\% U_{out}$.)

2. Design a PWM single phase full-bridge inverter with the parameters as following:

- Output voltage: 220V RMS/ 50Hz;
 - Output power: 1000W, power factor: 0.85;
 - PWM frequency: 10 kHz
- a) Calculate the required input DC voltage.
- b) Calculate the output current.
- c) Calculate the essential parameters to choose IGBTs and diodes.
- d) Calculate the essential parameters of the output filter.
- e) Calculate the essential parameters to choose the DC capacitor to keep the DC voltage ripple less than 5%.

3. Design a three phase inverter control by SPWM method with the parameters as following:

- Output voltage: 3x380V/50Hz
 - Output power: 5kW, power factor: 0.85
 - PWM switching frequency: 10 kHz
- a) Calculate the required input DC voltage.
- b) Calculate the output current.
- c) Calculate the essential parameters to choose IGBTs and diodes.
- d) Calculate the essential parameters of the output filter.
- e) Calculate the essential parameters to choose the DC capacitor to keep the DC voltage ripple less than 5%.

4. The three phase inverter control by SVM method with the parameters as following:

- Input DC voltage: 450V
 - Load: $Z_a = Z_b = Z_c = 10 + 10j$, in Star Connection (Y).
 - Switching frequency: 10 kHz
 - Output voltage fundamental frequency: 50Hz
- a) Output voltage vector: $U_0 = 250e^{j\theta}$, $\theta = 2\pi * 50 * t$ (rad). Calculate the applied time for each vector when the $\theta = 30^\circ$. Sketch the control pulse waveform in this case.
- b) Output voltage $U_0 = [U_\alpha, U_\beta]^T = [150, 80]^T$. Calculate the applied time for each vector and sketch the control pulse waveform in this case.