



TRƯỜNG ĐẠI HỌC
BÁCH KHOA HÀ NỘI

Nguyễn Công Phương



Electric Circuit Theory

Two-port Networks

Contents

- I. Basic Elements Of Electrical Circuits
- II. Basic Laws
- III. Electrical Circuit Analysis
- IV. Circuit Theorems
- V. Active Circuits
- VI. Capacitor And Inductor
- VII. First Order Circuits
- VIII. Second Order Circuits
- IX. Sinusoidal Steady State Analysis
- X. AC Power Analysis
- XI. Three-phase Circuits
- XII. Magnetically Coupled Circuits
- XIII. Frequency Response
- XIV. The Laplace Transform
- XV. Two-port Networks**




Two-port Networks


1. Introduction
2. Parameters
3. Relationships between Parameters
4. Two-port Network Analysis
5. Interconnection of Networks
6. T & Π Networks
7. Equivalent Two-port Networks of Magnetically Coupled Circuits
8. Input Impedance
9. Transfer Function



Introduction

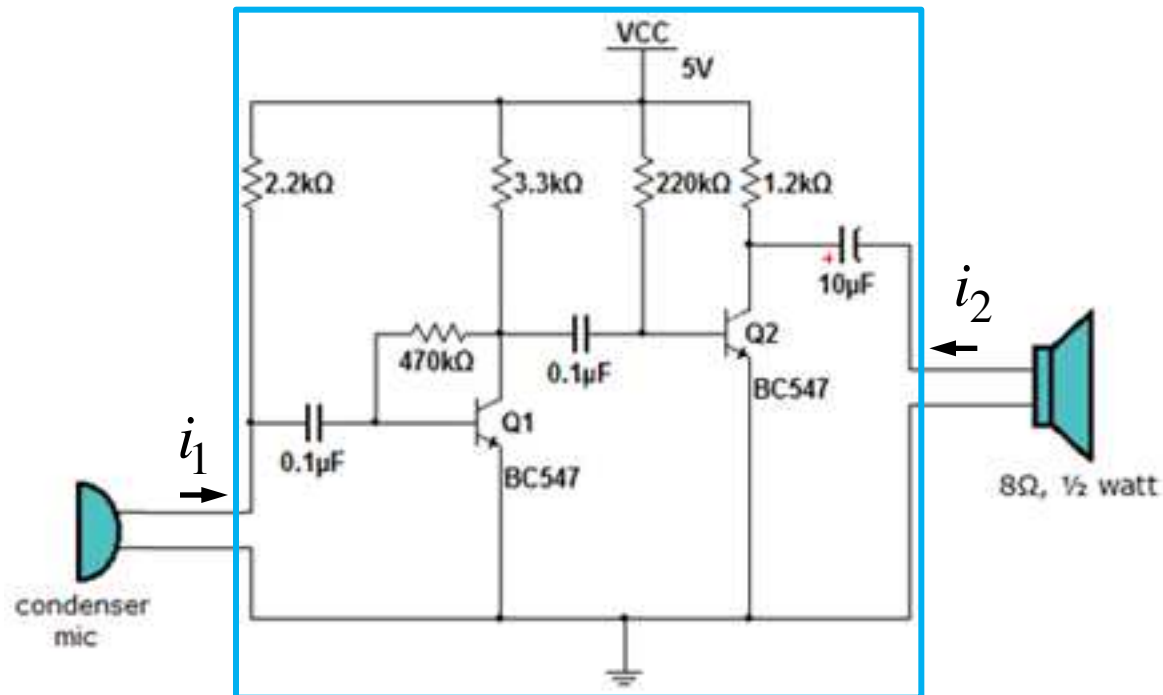
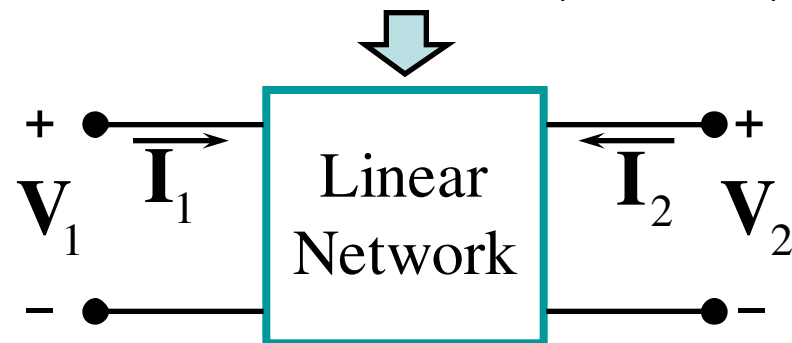
<https://www.efxkits.us/two-transistor-audio-amplifier-circuit-explanation/>



<https://sites.google.com/site/ncpdhbkhn/home>


Two-port Networks

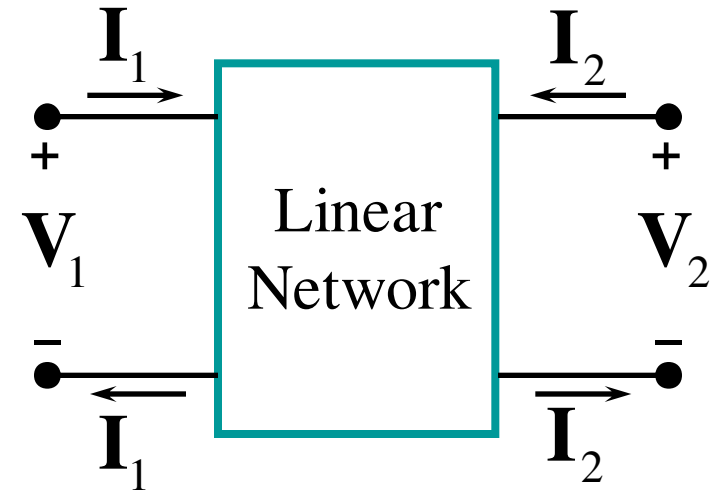1. Introduction
- 2. Parameters**
 - a) Impedance \mathbf{z}
 - b) Admittance \mathbf{y}
 - c) Hybrid \mathbf{h}
 - d) Inverse Hybrid \mathbf{g}
 - e) Transmission \mathbf{T}
 - f) Inverse Transmission \mathbf{t}
3. Relationships between Parameters
4. Two-port Network Analysis
5. Interconnection of Networks
6. T & Π Networks
7. Equivalent Two-port Networks of Magnetically Coupled Circuits
8. Input Impedance
9. Transfer Function



Impedance Parameters (1)

$$\begin{cases} \mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2 \\ \mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2 \end{cases}$$





$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = [\mathbf{z}] \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$

Impedance Parameters (2)

$$\left\{ \begin{array}{l} \mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2 \\ \mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2 \\ \mathbf{I}_2 = 0 \end{array} \right\}$$



$$\rightarrow \left\{ \begin{array}{l} \mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 \\ \mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 \end{array} \right. \rightarrow \left\{ \begin{array}{l} \mathbf{z}_{11} = \frac{\mathbf{V}_1}{\mathbf{I}_1} \Big|_{\mathbf{I}_2=0} \\ \mathbf{z}_{21} = \frac{\mathbf{V}_2}{\mathbf{I}_1} \Big|_{\mathbf{I}_2=0} \end{array} \right.$$

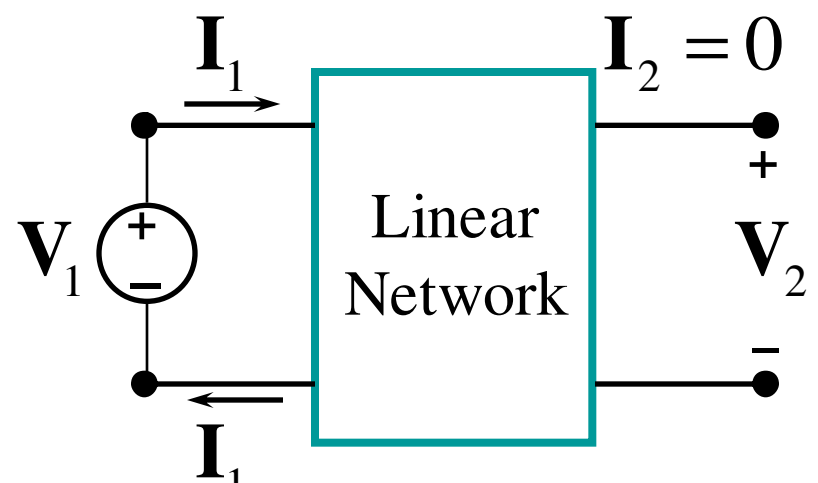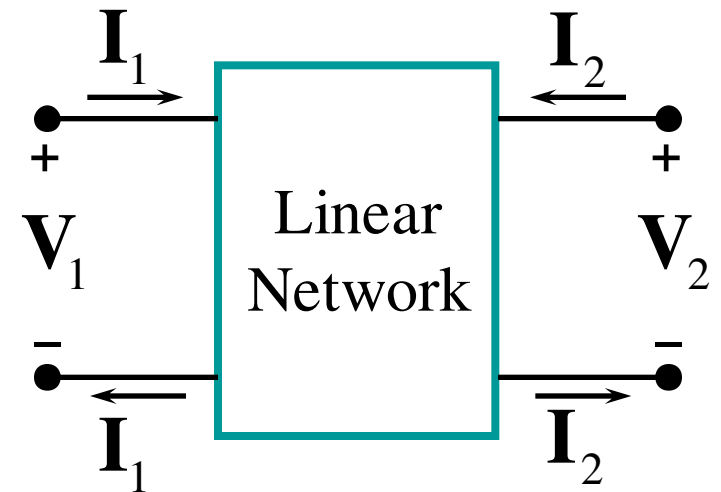

Impedance Parameters (3)


$$\left\{ \begin{array}{l} \mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2 \\ \mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2 \\ \mathbf{I}_1 = 0 \end{array} \right\}$$

$$\rightarrow \left\{ \begin{array}{l} \mathbf{V}_1 = \mathbf{z}_{12}\mathbf{I}_2 \\ \mathbf{V}_2 = \mathbf{z}_{22}\mathbf{I}_2 \end{array} \right\} \rightarrow \left\{ \begin{array}{l} \mathbf{z}_{12} = \frac{\mathbf{V}_1}{\mathbf{I}_2} \Big|_{\mathbf{I}_1=0} \\ \mathbf{z}_{22} = \frac{\mathbf{V}_2}{\mathbf{I}_2} \Big|_{\mathbf{I}_1=0} \end{array} \right.$$

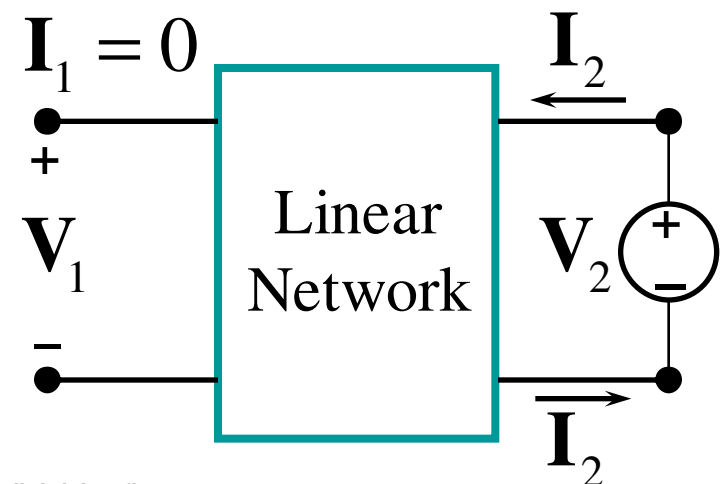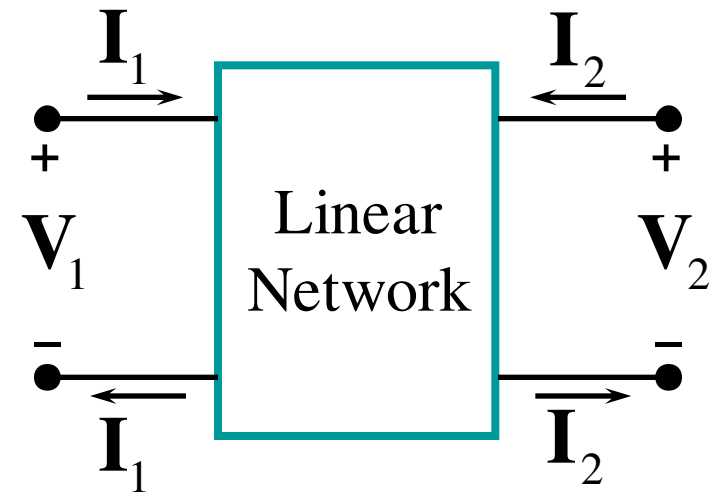

Impedance Parameters (4)
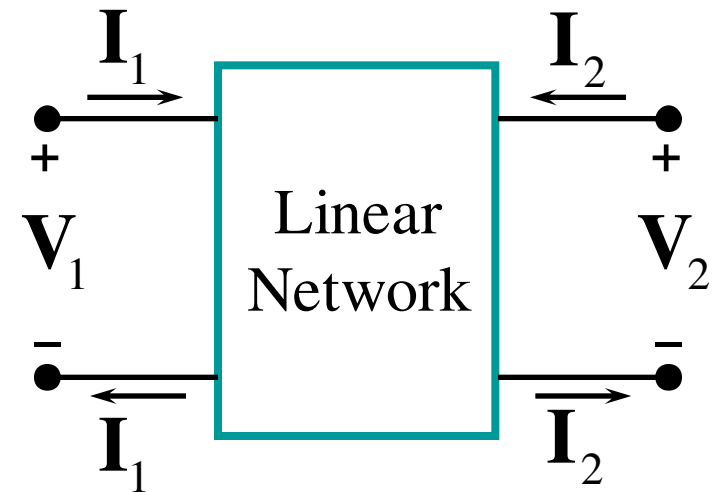
$$\begin{cases} \mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2 \\ \mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2 \end{cases}$$




$$\left[\begin{array}{cc} \mathbf{z}_{11} = \left. \frac{\mathbf{V}_1}{\mathbf{I}_1} \right|_{\mathbf{I}_2=0} & \mathbf{z}_{12} = \left. \frac{\mathbf{V}_1}{\mathbf{I}_2} \right|_{\mathbf{I}_1=0} \\ \mathbf{z}_{21} = \left. \frac{\mathbf{V}_2}{\mathbf{I}_1} \right|_{\mathbf{I}_2=0} & \mathbf{z}_{22} = \left. \frac{\mathbf{V}_2}{\mathbf{I}_2} \right|_{\mathbf{I}_1=0} \end{array} \right]$$

Ex.

Impedance Parameters (5)


Find $[z]$?

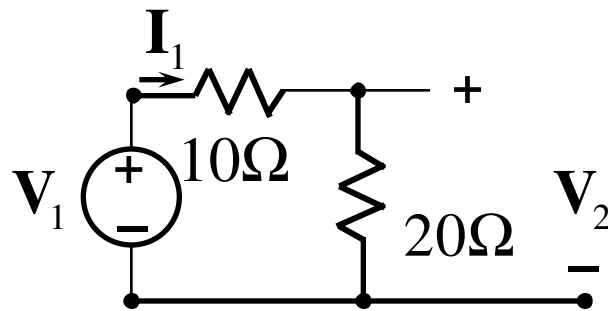

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$V_1 = (10 + 20)I_1 = 30I_1$$
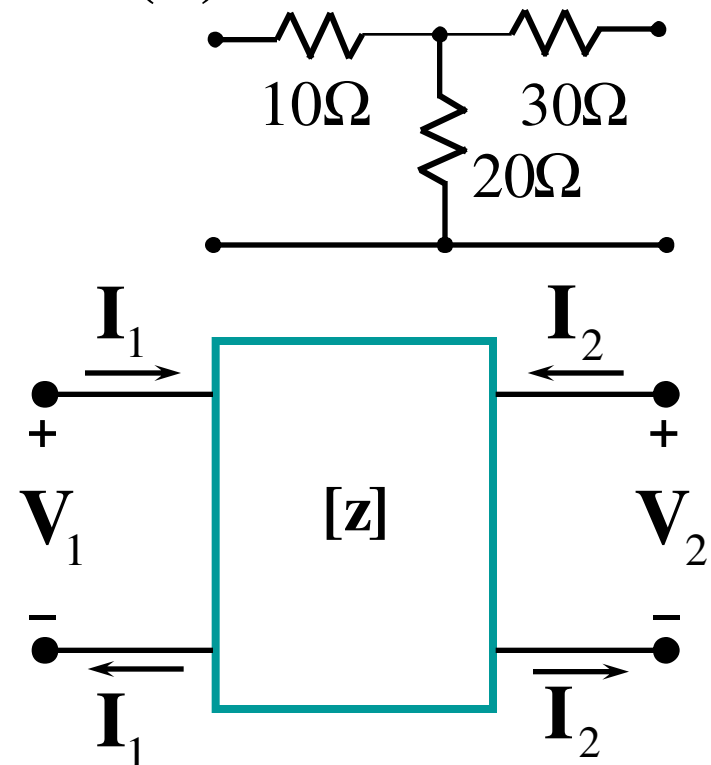
$$\rightarrow z_{11} = \frac{30I_1}{I_1} = \boxed{30\Omega}$$




$$\begin{cases} V_1 = z_{11}I_1 + z_{12}I_2 \\ V_2 = z_{21}I_1 + z_{22}I_2 \end{cases}$$

Ex. 1


Impedance Parameters (6)

Find $[z]$?

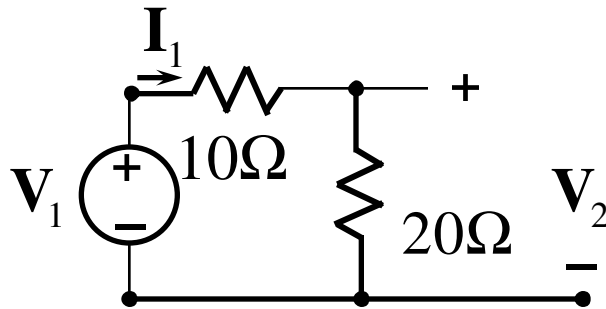

$$\left. \begin{aligned} z_{21} &= \frac{V_2}{I_1} \Big|_{I_2=0} \\ V_2 &= 20I_1 \end{aligned} \right\}$$

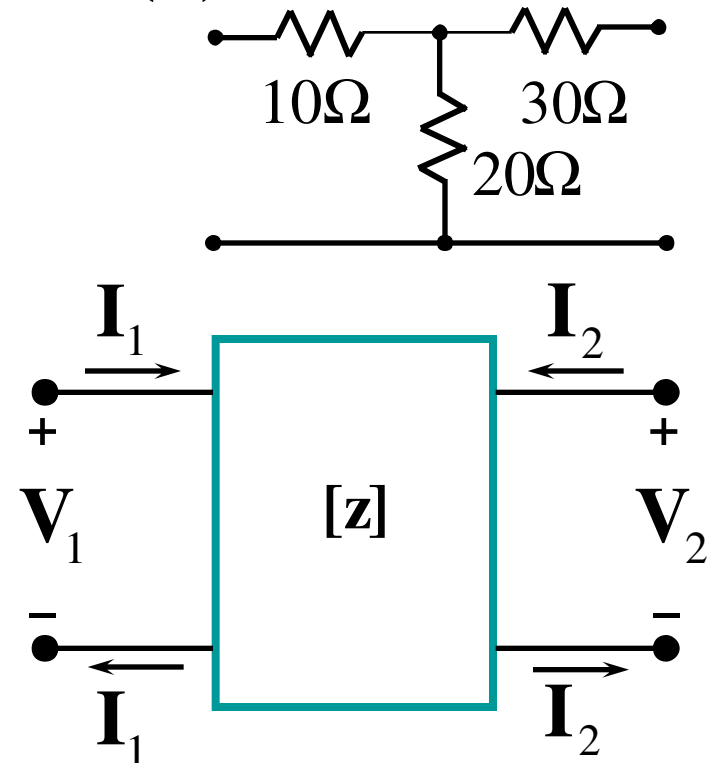
$$\rightarrow z_{21} = \frac{20I_1}{I_1} = \boxed{20\Omega}$$



$$\begin{cases} V_1 = z_{11}I_1 + z_{12}I_2 \\ V_2 = z_{21}I_1 + z_{22}I_2 \end{cases}$$


Ex. 1

Find $[z]$?

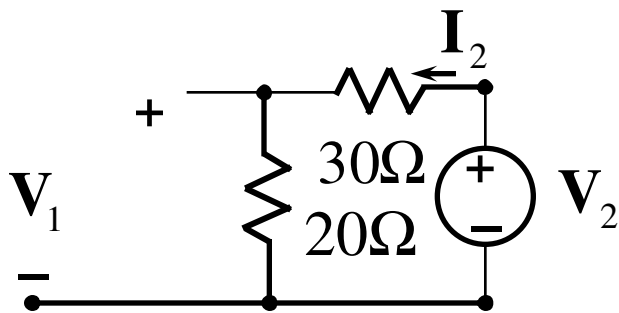

$$\left. \begin{aligned} z_{12} &= \frac{V_1}{I_2} \Big|_{I_1=0} \\ V_1 &= 20I_2 \end{aligned} \right\}$$

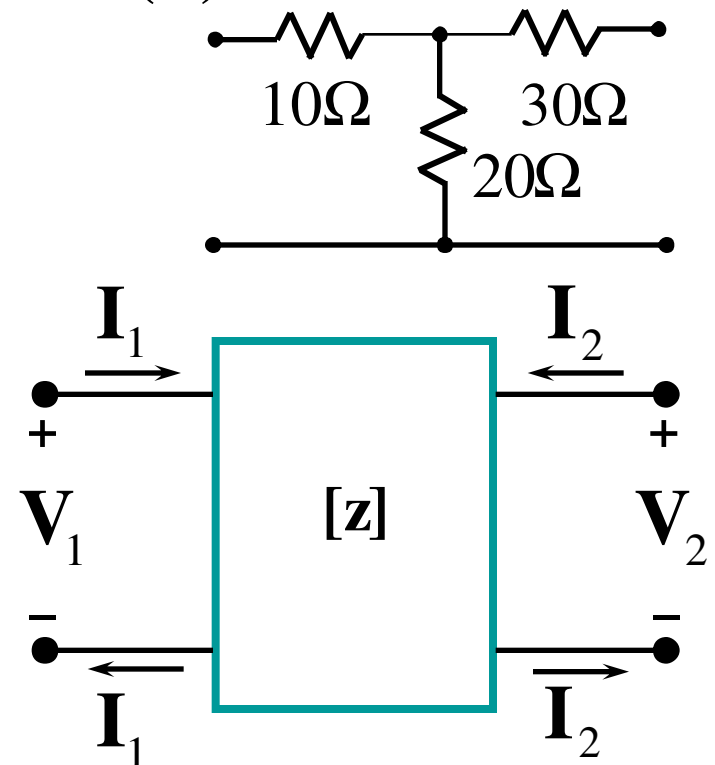
$$\rightarrow z_{12} = \frac{20I_2}{I_2} = \boxed{20\Omega}$$



$$\begin{cases} V_1 = z_{11}I_1 + z_{12}I_2 \\ V_2 = z_{21}I_1 + z_{22}I_2 \end{cases}$$


Ex. 1

Find $[z]$?

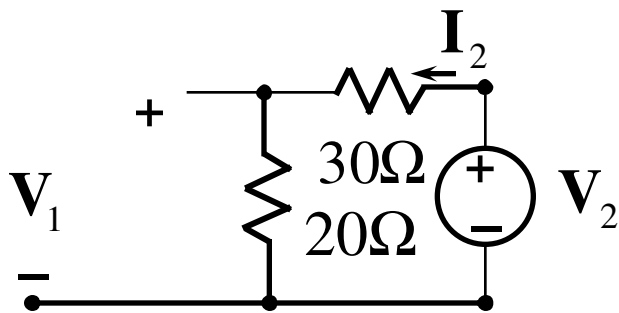

$$\left. \begin{aligned} z_{22} &= \frac{V_2}{I_2} \bigg|_{I_1=0} \\ V_2 &= (20 + 30)I_2 = 50I_2 \end{aligned} \right\}$$
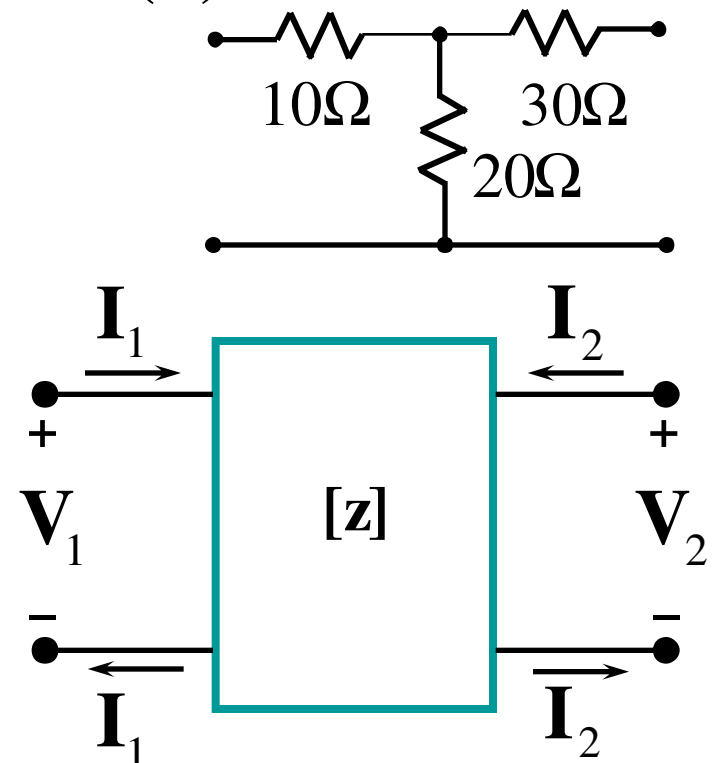
$$\rightarrow z_{22} = \frac{50I_2}{I_2} = \boxed{50\Omega}$$




$$\begin{cases} V_1 = z_{11}I_1 + z_{12}I_2 \\ V_2 = z_{21}I_1 + z_{22}I_2 \end{cases}$$

Ex. 1

Find $[z]$?

Impedance Parameters (9)


$$\mathbf{z} = \begin{bmatrix} 30 & 20 \\ 20 & 50 \end{bmatrix} \Omega$$

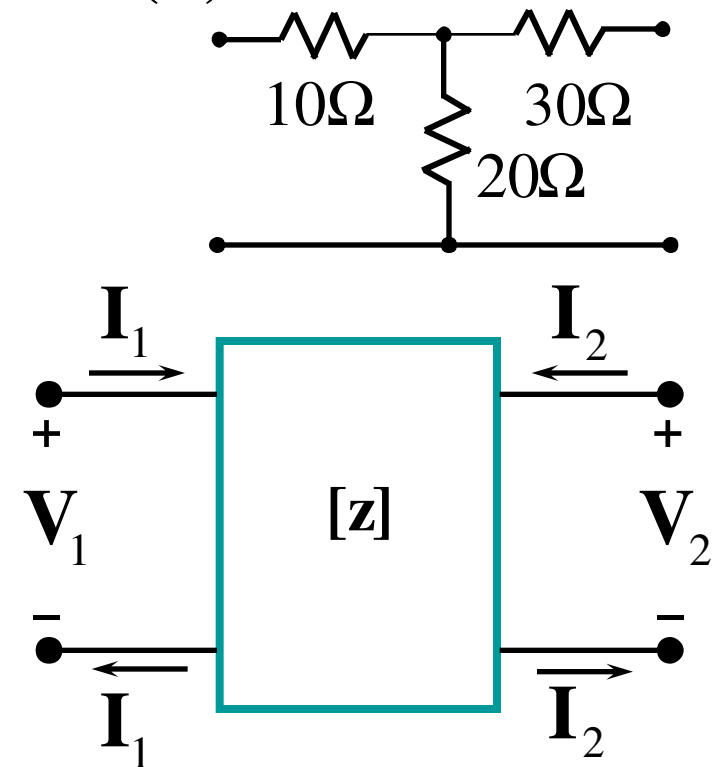



Ex. 1

Impedance Parameters (10)

Find $[z]$?

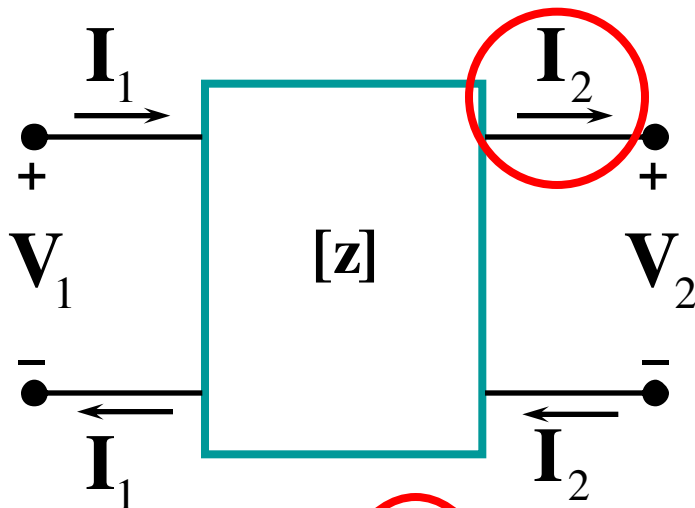
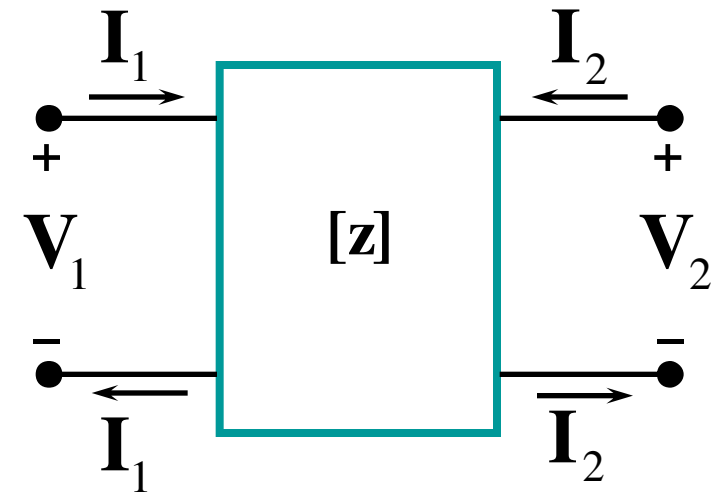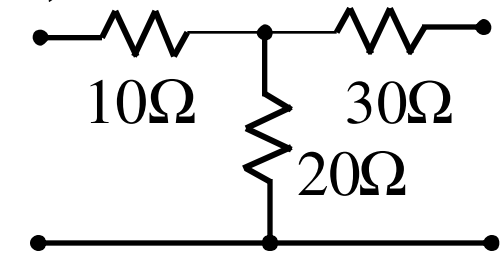
$$\mathbf{z} = \begin{bmatrix} 30 & -20 \\ 20 & -50 \end{bmatrix} \Omega$$




$$\mathbf{z} = \begin{bmatrix} 30 & 20 \\ 20 & 50 \end{bmatrix} \Omega$$

Ex. 1

Impedance Parameters (11)

Find $[z]$?

Method 2

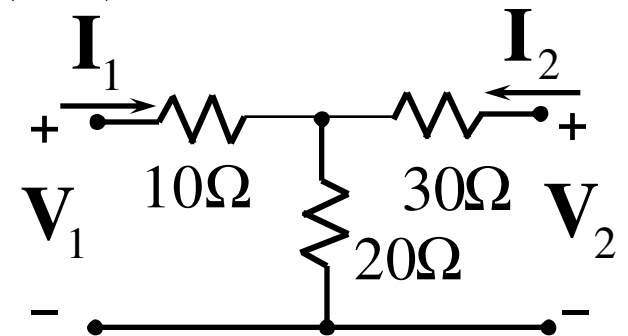

$$V_1 = V_{10} + V_{20} = 10I_1 + 20(I_1 + I_2) = (10 + 20)I_1 + 20I_2$$

$$V_2 = V_{30} + V_{20} = 30I_2 + 20(I_1 + I_2) = 20I_1 + (20 + 30)I_2$$

$$\rightarrow \begin{cases} V_1 = (10 + 20)I_1 + 20I_2 \\ V_2 = 20I_1 + (20 + 30)I_2 \end{cases} \rightarrow \begin{cases} z_{11} = 10 + 20 = 30\Omega \\ z_{12} = 20 = 20\Omega \\ z_{21} = 20 = 20\Omega \\ z_{22} = 20 + 30 = 50\Omega \end{cases}$$

Ex. 2


Impedance Parameters (12)

Find $[z]$?

$$\begin{cases} V_1 = R_1 I_1 + \frac{1}{C_s} I_1 \\ V_2 = R_2 I_2 + R_3 I_3 - R_4 I_4 \\ I_3 = -I_4 \\ \frac{1}{C_s} I_1 = -R_4 I_4 \end{cases}$$

$$\rightarrow \begin{cases} V_1 = \left(R_1 + \frac{1}{C_s} \right) I_1 \\ V_2 = \frac{R_3 + R_4}{R_4 C_s} I_1 + R_2 I_2 \end{cases}$$
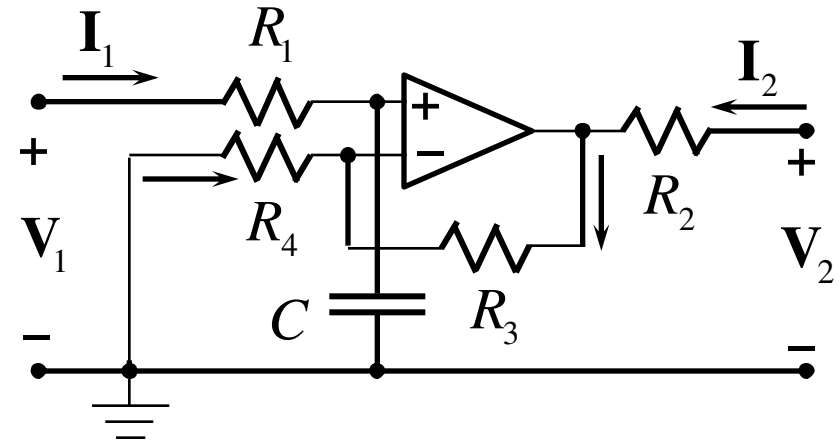
$$\rightarrow [z] = \begin{bmatrix} R_1 + \frac{1}{C_s} & 0 \\ \frac{R_3 + R_4}{R_4 C_s} & R_2 \end{bmatrix}$$



$$\begin{cases} V_1 = z_{11} I_1 + z_{12} I_2 \\ V_2 = z_{21} I_1 + z_{22} I_2 \end{cases}$$

Two-port Networks

1. Introduction

2. Parameters

- a) Impedance z
- b) Admittance y
- c) Hybrid h
- d) Inverse Hybrid g
- e) Transmission T
- f) Inverse Transmission t

3. Relationships between Parameters

4. Two-port Network Analysis

5. Interconnection of Networks

6. T & Π Networks

7. Equivalent Two-port Networks of Magnetically Coupled Circuits


8. Input Impedance

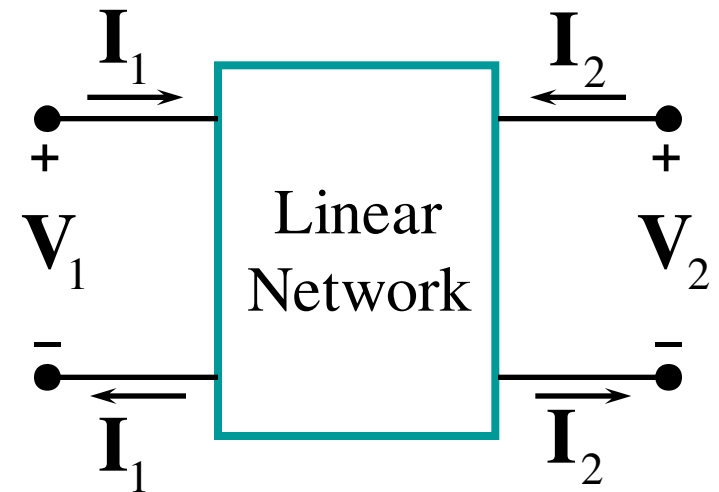9. Transfer Function



Admittance Parameters (1)

$$\begin{cases} \mathbf{I}_1 = \mathbf{y}_{11} \mathbf{V}_1 + \mathbf{y}_{12} \mathbf{V}_2 \\ \mathbf{I}_2 = \mathbf{y}_{21} \mathbf{V}_1 + \mathbf{y}_{22} \mathbf{V}_2 \end{cases}$$





$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{y}_{11} & \mathbf{y}_{12} \\ \mathbf{y}_{21} & \mathbf{y}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = [\mathbf{y}] \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix}$$

Admittance Parameters (2)

$$\left\{ \begin{array}{l} \mathbf{I}_1 = \mathbf{y}_{11} \mathbf{V}_1 + \mathbf{y}_{12} \mathbf{V}_2 \\ \mathbf{I}_2 = \mathbf{y}_{21} \mathbf{V}_1 + \mathbf{y}_{22} \mathbf{V}_2 \\ \mathbf{V}_2 = 0 \end{array} \right.$$



$$\rightarrow \left\{ \begin{array}{l} \mathbf{I}_1 = \mathbf{y}_{11} \mathbf{V}_1 \\ \mathbf{I}_2 = \mathbf{y}_{21} \mathbf{V}_1 \end{array} \right. \rightarrow \left\{ \begin{array}{l} \mathbf{y}_{11} = \frac{\mathbf{I}_1}{\mathbf{V}_1} \Big|_{\mathbf{V}_2=0} \\ \mathbf{y}_{21} = \frac{\mathbf{I}_2}{\mathbf{V}_1} \Big|_{\mathbf{V}_2=0} \end{array} \right.$$

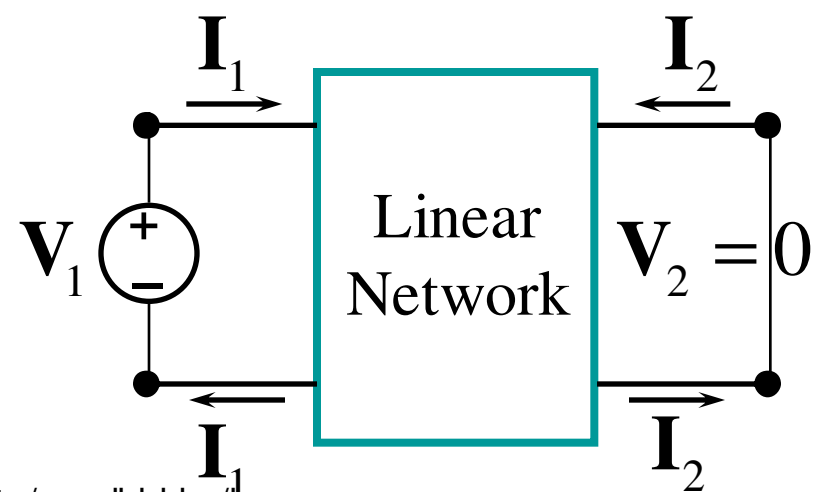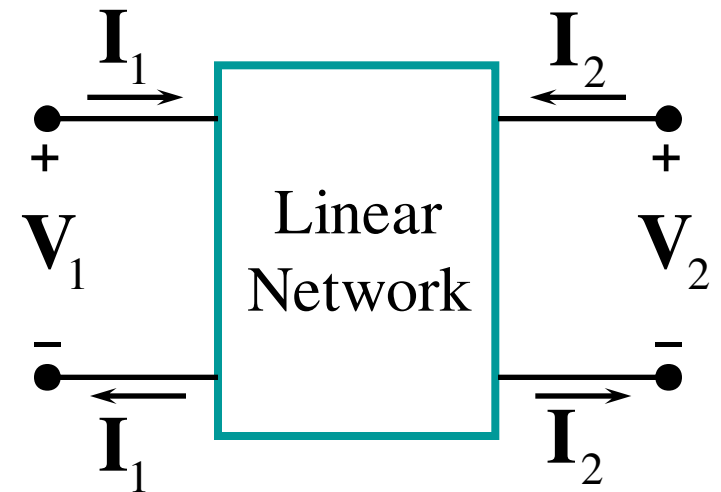

Admittance Parameters (3)

$$\left\{ \begin{array}{l} \mathbf{I}_1 = \mathbf{y}_{11} \mathbf{V}_1 + \mathbf{y}_{12} \mathbf{V}_2 \\ \mathbf{I}_2 = \mathbf{y}_{21} \mathbf{V}_1 + \mathbf{y}_{22} \mathbf{V}_2 \\ \mathbf{V}_1 = 0 \end{array} \right.$$


$$\rightarrow \left\{ \begin{array}{l} \mathbf{I}_1 = \mathbf{y}_{12} \mathbf{V}_2 \\ \mathbf{I}_2 = \mathbf{y}_{22} \mathbf{V}_2 \end{array} \right. \rightarrow \left\{ \begin{array}{l} \mathbf{y}_{12} = \frac{\mathbf{I}_1}{\mathbf{V}_2} \Big|_{\mathbf{V}_1=0} \\ \mathbf{y}_{22} = \frac{\mathbf{I}_2}{\mathbf{V}_2} \Big|_{\mathbf{V}_1=0} \end{array} \right.$$

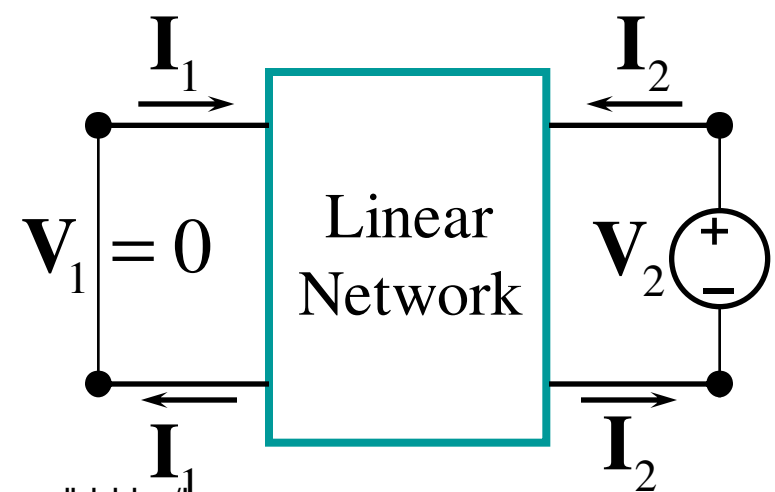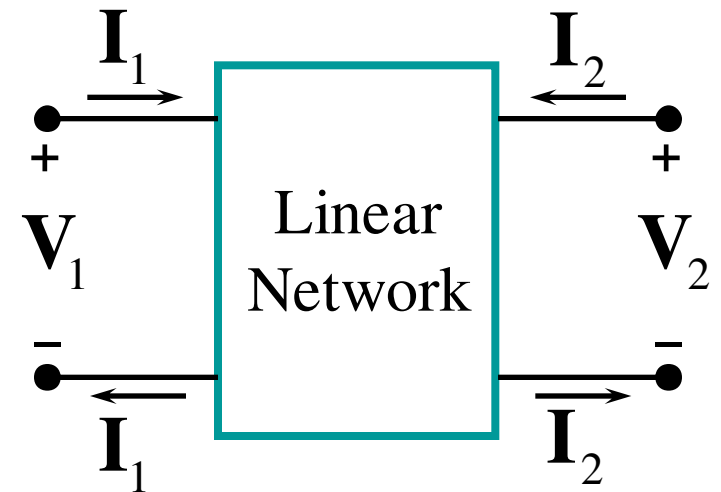

Admittance Parameters (4)

$$\begin{cases} \mathbf{I}_1 = \mathbf{y}_{11} \mathbf{V}_1 + \mathbf{y}_{12} \mathbf{V}_2 \\ \mathbf{I}_2 = \mathbf{y}_{21} \mathbf{V}_1 + \mathbf{y}_{22} \mathbf{V}_2 \end{cases}$$


$$\left[\begin{array}{ll} \mathbf{y}_{11} = \left. \frac{\mathbf{I}_1}{\mathbf{V}_1} \right|_{\mathbf{V}_2=0} & \mathbf{y}_{12} = \left. \frac{\mathbf{I}_1}{\mathbf{V}_2} \right|_{\mathbf{V}_1=0} \\ \mathbf{y}_{21} = \left. \frac{\mathbf{I}_2}{\mathbf{V}_1} \right|_{\mathbf{V}_2=0} & \mathbf{y}_{22} = \left. \frac{\mathbf{I}_2}{\mathbf{V}_2} \right|_{\mathbf{V}_1=0} \end{array} \right]$$

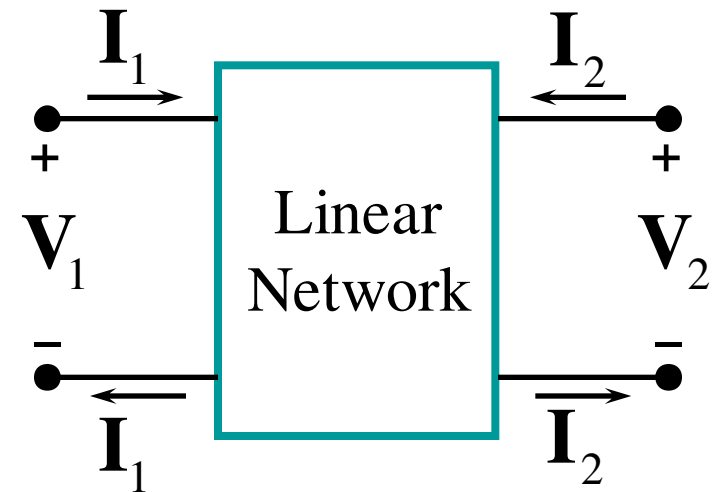

Ex.

Admittance Parameters (5)



Find $[y]$?

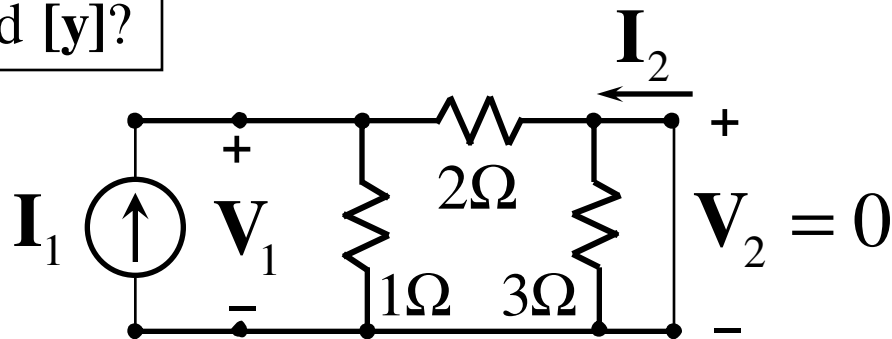

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$V_1 = (1 // 2) I_1 = \frac{1 \times 2}{1 + 2} I_1 = 0.67 I_1$$
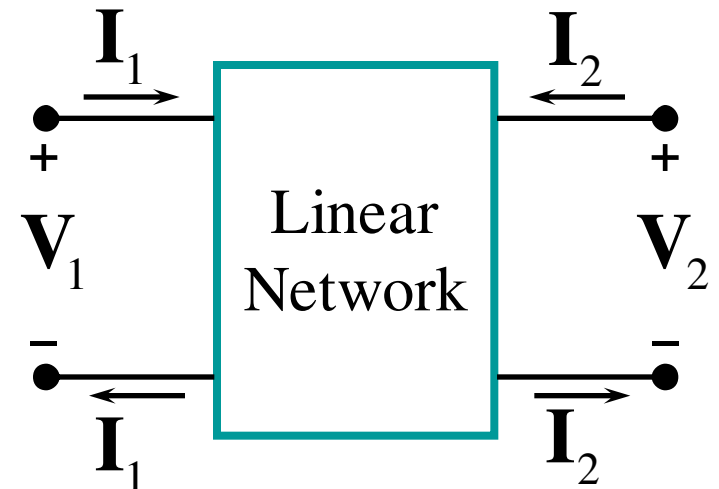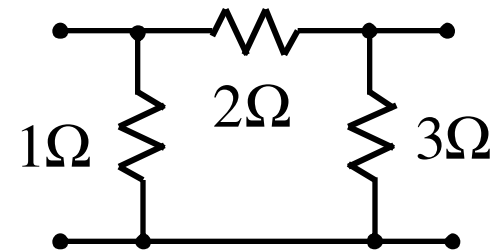
$$\rightarrow y_{11} = \frac{I_1}{0.67 I_1} = 1.5 \text{ S}$$




$$\begin{cases} I_1 = y_{11} V_1 + y_{12} V_2 \\ I_2 = y_{21} V_1 + y_{22} V_2 \end{cases}$$

Ex.

Admittance Parameters (6)



Find $[y]$?

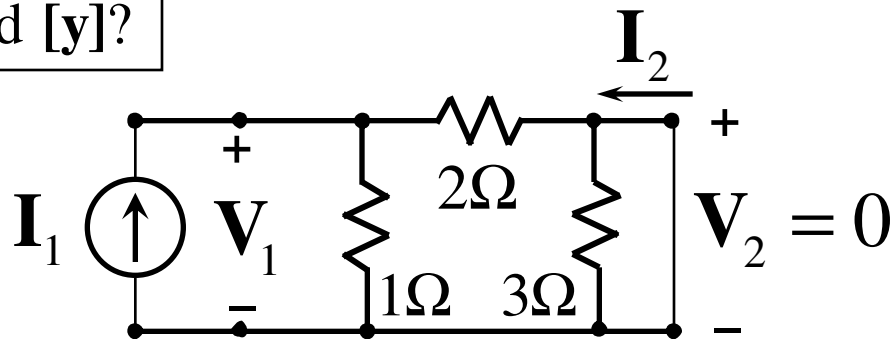

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$V_1 = V_{1\Omega} = V_{2\Omega} = -2I_2$$
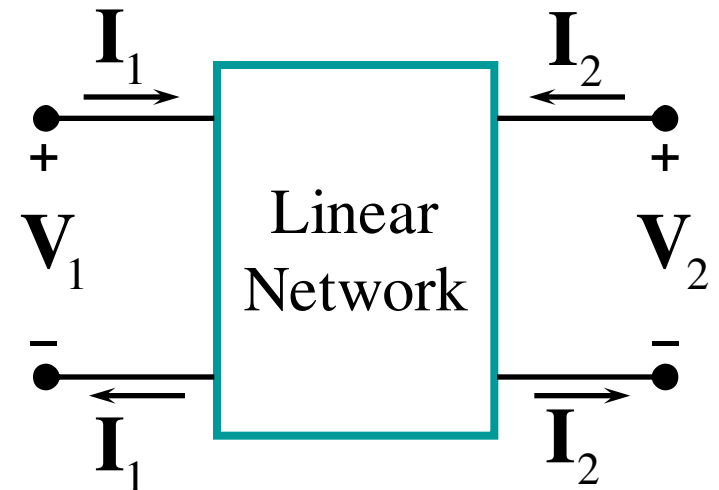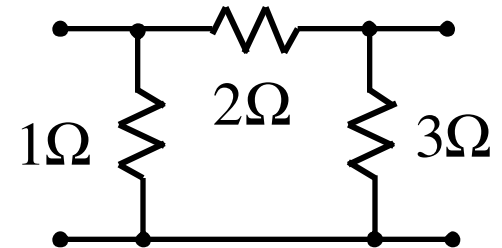
$$\rightarrow y_{21} = \frac{I_2}{-2I_2} = \boxed{-0.5S}$$




$$\begin{cases} I_1 = y_{11}V_1 + y_{12}V_2 \\ I_2 = y_{21}V_1 + y_{22}V_2 \end{cases}$$

Ex.

Find $[y]$?



Admittance Parameters (7)

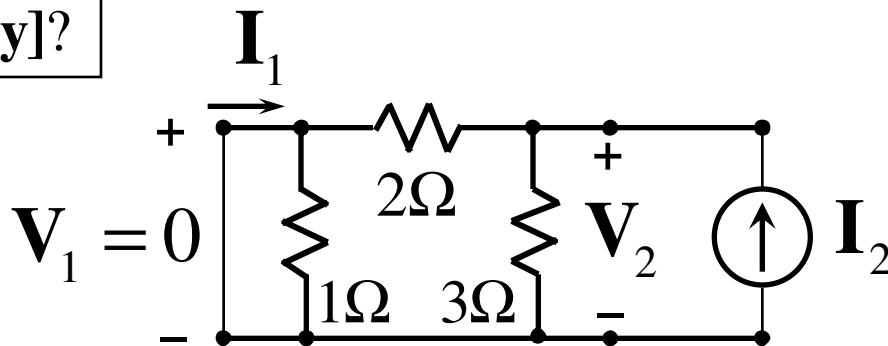

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$V_2 = V_{3\Omega} = V_{2\Omega} = -2I_1$$
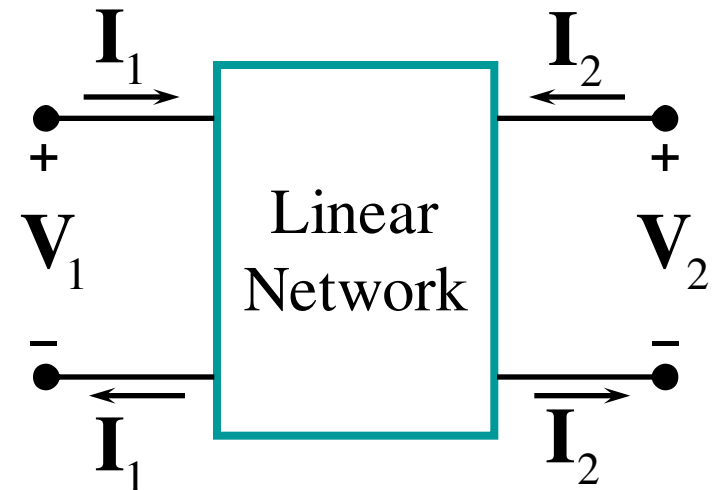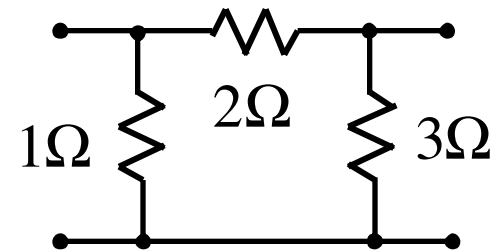
$$\rightarrow y_{12} = \frac{I_1}{-2I_1} = -0.5S$$






$$\begin{cases} I_1 = y_{11}V_1 + y_{12}V_2 \\ I_2 = y_{21}V_1 + y_{22}V_2 \end{cases}$$

Ex.

Admittance Parameters (8)

Find $[y]$?

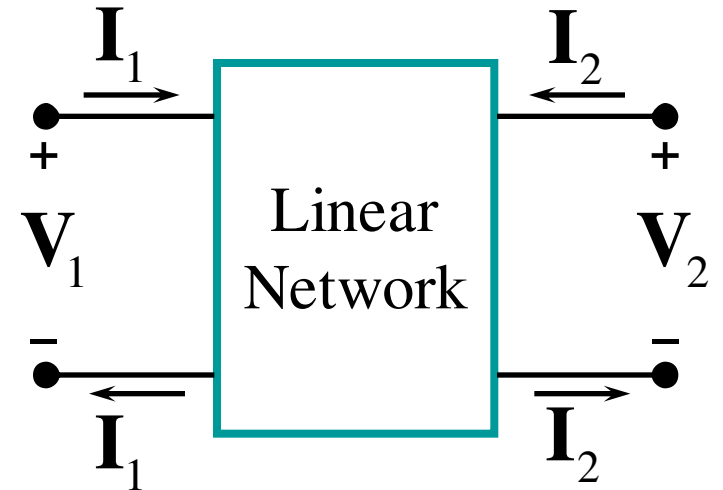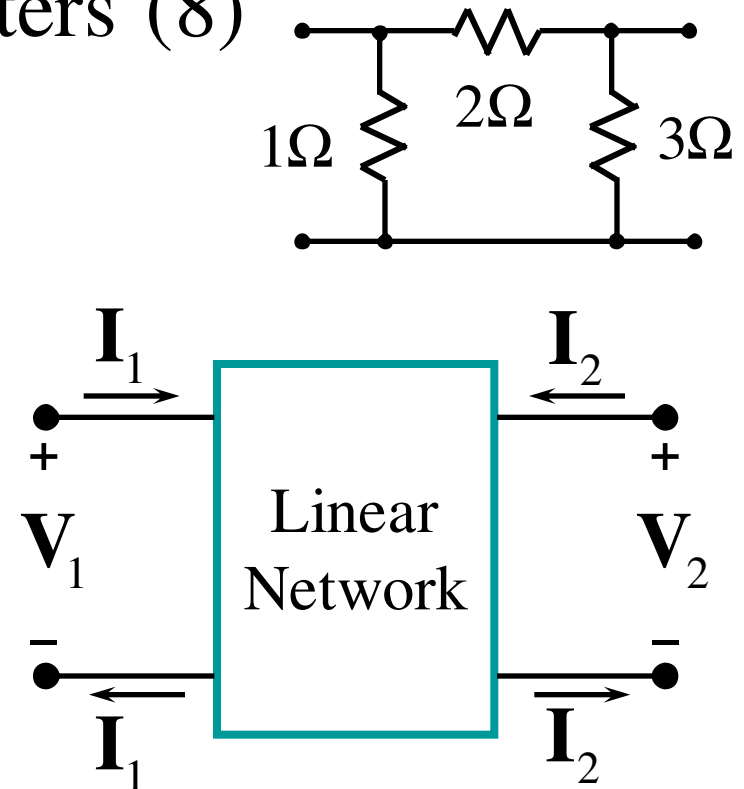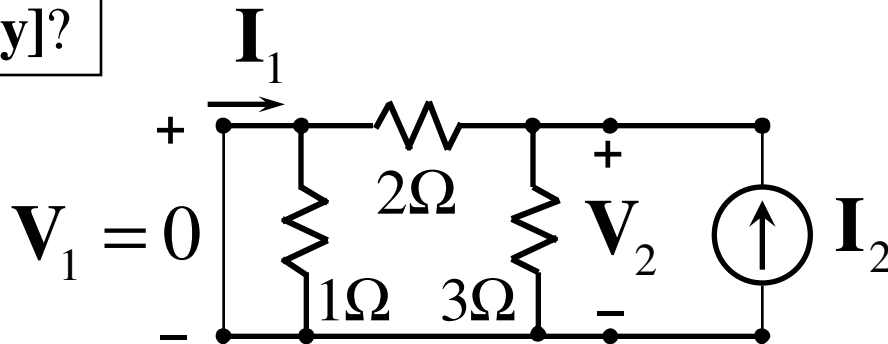

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

$$V_2 = (2 // 3)I_2 = \frac{2 \times 3}{2 + 3} V_2 = 1.2V_2$$


$$\rightarrow y_{22} = \frac{I_2}{1.2I_2} = \boxed{0.83S}$$

$$\begin{cases} I_1 = y_{11}V_1 + y_{12}V_2 \\ I_2 = y_{21}V_1 + y_{22}V_2 \end{cases}$$


Ex.

Find $[y]$?

Admittance Parameters (9)

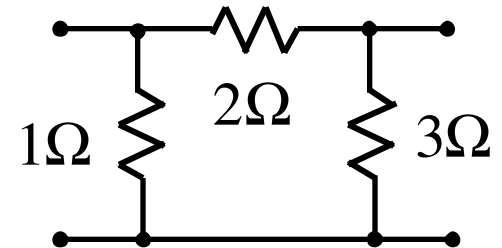
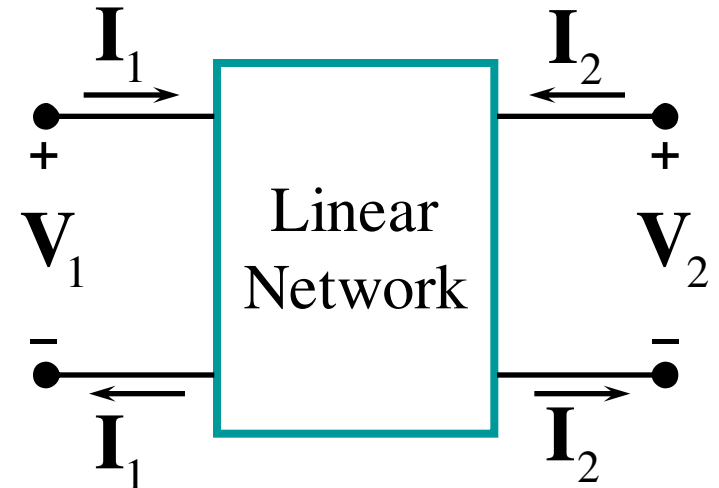
$$\mathbf{y} = \begin{bmatrix} 1.5 & -0.5 \\ -0.5 & 0.83 \end{bmatrix}$$



Two-port Networks


1. Introduction
- 2. Parameters**
 - a) Impedance z
 - b) Admittance y
 - c) Hybrid h
 - d) Inverse Hybrid g
 - e) Transmission T
 - f) Inverse Transmission t
3. Relationships between Parameters
4. Two-port Network Analysis
5. Interconnection of Networks
6. T & Π Networks
7. Equivalent Two-port Networks of Magnetically Coupled Circuits
8. Input Impedance
9. Transfer Function



Hybrid Parameters

$$\begin{cases} \mathbf{V}_1 = \mathbf{h}_{11}\mathbf{I}_1 + \mathbf{h}_{12}\mathbf{V}_2 \\ \mathbf{I}_2 = \mathbf{h}_{21}\mathbf{I}_1 + \mathbf{h}_{22}\mathbf{V}_2 \end{cases}$$
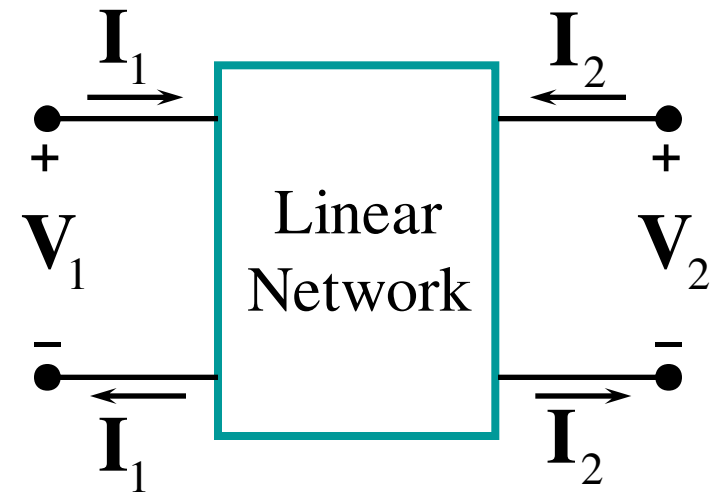
$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{h}_{11} & \mathbf{h}_{12} \\ \mathbf{h}_{21} & \mathbf{h}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{V}_2 \end{bmatrix} = [\mathbf{h}] \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{V}_2 \end{bmatrix}$$




$$\begin{bmatrix} \mathbf{h}_{11} = \left. \frac{\mathbf{V}_1}{\mathbf{I}_1} \right|_{\mathbf{V}_2=0} & \mathbf{h}_{12} = \left. \frac{\mathbf{V}_1}{\mathbf{V}_2} \right|_{\mathbf{I}_1=0} \\ \mathbf{h}_{21} = \left. \frac{\mathbf{I}_2}{\mathbf{I}_1} \right|_{\mathbf{V}_2=0} & \mathbf{h}_{22} = \left. \frac{\mathbf{I}_2}{\mathbf{V}_2} \right|_{\mathbf{I}_1=0} \end{bmatrix}$$

Inverse Hybrid Parameters

$$\begin{cases} \mathbf{I}_1 = \mathbf{g}_{11} \mathbf{V}_1 + \mathbf{g}_{12} \mathbf{I}_2 \\ \mathbf{V}_2 = \mathbf{g}_{21} \mathbf{V}_1 + \mathbf{g}_{22} \mathbf{I}_2 \end{cases}$$
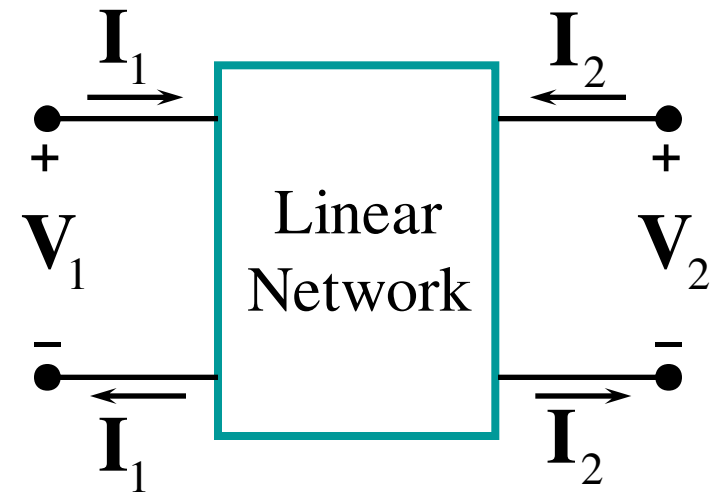
$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{g}_{11} & \mathbf{g}_{12} \\ \mathbf{g}_{21} & \mathbf{g}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix} = [\mathbf{g}] \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix}$$




$$\begin{bmatrix} \mathbf{g}_{11} = \left. \frac{\mathbf{I}_1}{\mathbf{V}_1} \right|_{\mathbf{I}_2=0} & \mathbf{g}_{12} = \left. \frac{\mathbf{I}_1}{\mathbf{I}_2} \right|_{\mathbf{V}_1=0} \\ \mathbf{g}_{21} = \left. \frac{\mathbf{V}_2}{\mathbf{V}_1} \right|_{\mathbf{I}_2=0} & \mathbf{g}_{22} = \left. \frac{\mathbf{V}_2}{\mathbf{I}_2} \right|_{\mathbf{V}_1=0} \end{bmatrix}$$

Transmission Parameters

$$\begin{cases} \mathbf{V}_1 = \mathbf{A}\mathbf{V}_2 - \mathbf{B}\mathbf{I}_2 \\ \mathbf{I}_1 = \mathbf{C}\mathbf{V}_2 - \mathbf{D}\mathbf{I}_2 \end{cases}$$
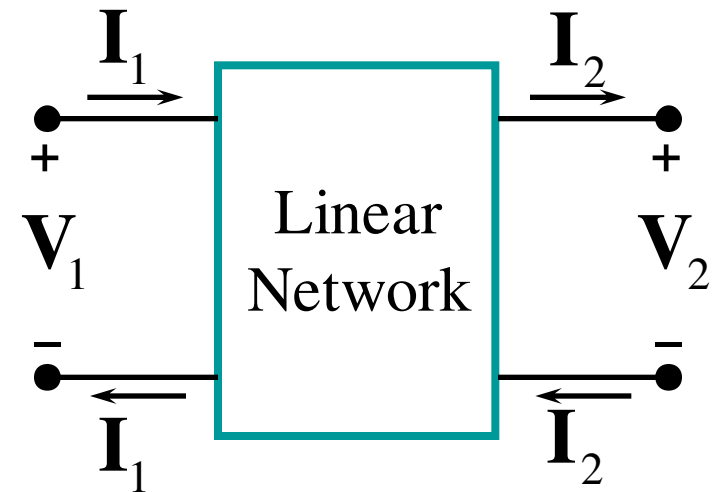
$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} \begin{bmatrix} \mathbf{V}_2 \\ -\mathbf{I}_2 \end{bmatrix} = [\mathbf{T}] \begin{bmatrix} \mathbf{V}_2 \\ -\mathbf{I}_2 \end{bmatrix}$$




$$\begin{bmatrix} \mathbf{A} = \left. \frac{\mathbf{V}_1}{\mathbf{V}_2} \right|_{\mathbf{I}_2=0} & \mathbf{B} = \left. \frac{\mathbf{V}_1}{\mathbf{I}_2} \right|_{\mathbf{V}_2=0} \\ \mathbf{C} = \left. \frac{\mathbf{I}_1}{\mathbf{V}_2} \right|_{\mathbf{I}_2=0} & \mathbf{D} = \left. \frac{\mathbf{I}_1}{\mathbf{I}_2} \right|_{\mathbf{V}_2=0} \end{bmatrix}$$

Inverse Transmission Parameters

$$\begin{cases} \mathbf{V}_2 = \mathbf{a}\mathbf{V}_1 - \mathbf{b}\mathbf{I}_1 \\ \mathbf{I}_2 = \mathbf{c}\mathbf{V}_1 - \mathbf{d}\mathbf{I}_1 \end{cases}$$
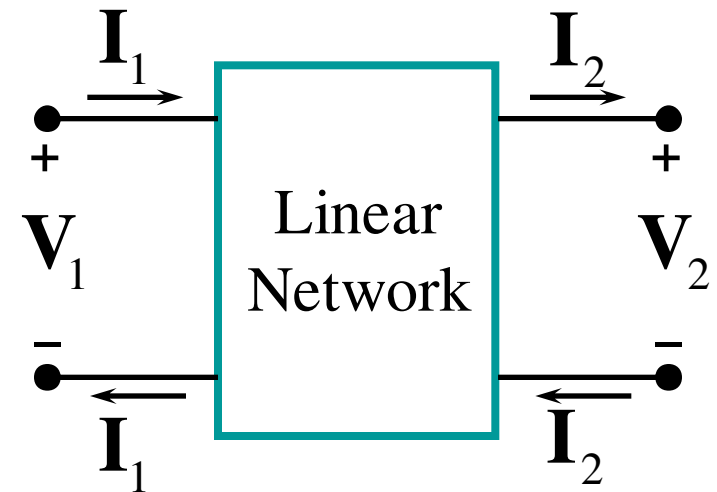
$$\begin{bmatrix} \mathbf{V}_2 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{a} & \mathbf{b} \\ \mathbf{c} & \mathbf{d} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ -\mathbf{I}_1 \end{bmatrix} = [\mathbf{t}] \begin{bmatrix} \mathbf{V}_1 \\ -\mathbf{I}_1 \end{bmatrix}$$



$$\begin{bmatrix} \mathbf{a} = \left. \frac{\mathbf{V}_2}{\mathbf{V}_1} \right|_{\mathbf{I}_1=0} & \mathbf{b} = \left. \frac{\mathbf{V}_2}{\mathbf{I}_1} \right|_{\mathbf{V}_1=0} \\ \mathbf{c} = \left. \frac{\mathbf{I}_2}{\mathbf{V}_1} \right|_{\mathbf{I}_1=0} & \mathbf{d} = \left. \frac{\mathbf{I}_2}{\mathbf{I}_1} \right|_{\mathbf{V}_1=0} \end{bmatrix}$$

Two-port Networks

$$\begin{cases} \mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2 \\ \mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2 \end{cases}$$

$$\begin{cases} \mathbf{V}_1 = \mathbf{h}_{11}\mathbf{I}_1 + \mathbf{h}_{12}\mathbf{V}_2 \\ \mathbf{I}_2 = \mathbf{h}_{21}\mathbf{I}_1 + \mathbf{h}_{22}\mathbf{V}_2 \end{cases}$$

$$\begin{cases} \mathbf{V}_1 = \mathbf{A}\mathbf{V}_2 - \mathbf{B}\mathbf{I}_2 \\ \mathbf{I}_1 = \mathbf{C}\mathbf{V}_2 - \mathbf{D}\mathbf{I}_2 \end{cases}$$

$$\begin{cases} \mathbf{I}_1 = \mathbf{y}_{11}\mathbf{V}_1 + \mathbf{y}_{12}\mathbf{V}_2 \\ \mathbf{I}_2 = \mathbf{y}_{21}\mathbf{V}_1 + \mathbf{y}_{22}\mathbf{V}_2 \end{cases}$$

$$\begin{cases} \mathbf{I}_1 = \mathbf{g}_{11}\mathbf{V}_1 + \mathbf{g}_{12}\mathbf{I}_2 \\ \mathbf{V}_2 = \mathbf{g}_{21}\mathbf{V}_1 + \mathbf{g}_{22}\mathbf{I}_2 \end{cases}$$

$$\begin{cases} \mathbf{V}_2 = \mathbf{a}\mathbf{V}_1 - \mathbf{b}\mathbf{I}_1 \\ \mathbf{I}_2 = \mathbf{c}\mathbf{V}_1 - \mathbf{d}\mathbf{I}_1 \end{cases}$$

Two-port Networks

1. Introduction
2. Parameters
- 3. Relationships between Parameters**
4. Two-port Network Analysis
5. Interconnection of Networks
6. T & Π Networks
7. Equivalent Two-port Networks of Magnetically Coupled Circuits
8. Input Impedance
9. Transfer Function



Relationships between Parameters (1)

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = [\mathbf{z}] \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$

$$\left. \begin{aligned} \rightarrow \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} &= [\mathbf{z}]^{-1} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} \\ \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} &= [\mathbf{y}] \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} \end{aligned} \right\} \rightarrow [\mathbf{y}] = [\mathbf{z}]^{-1}$$

Relationships between Parameters (2)

$$[\mathbf{y}] = [\mathbf{z}]^{-1}$$

$$[\mathbf{g}] = [\mathbf{h}]^{-1}$$

$$[\mathbf{t}] = [\mathbf{T}]^{-1}$$



Relationships between Parameters (3)

$$\left\{ \begin{array}{l} \mathbf{V}_1 = \mathbf{h}_{11}\mathbf{I}_1 + \mathbf{h}_{12}\mathbf{V}_2 \\ \mathbf{I}_2 = \mathbf{h}_{21}\mathbf{I}_1 + \mathbf{h}_{22}\mathbf{V}_2 \end{array} \right\} \rightarrow \mathbf{V}_2 = -\frac{\mathbf{h}_{12}}{\mathbf{h}_{22}}\mathbf{I}_1 + \frac{1}{\mathbf{h}_{22}}\mathbf{I}_2$$
$$\rightarrow \mathbf{V}_1 = \left(\mathbf{h}_{11} - \frac{\mathbf{h}_{12}\mathbf{h}_{21}}{\mathbf{h}_{22}} \right) \mathbf{I}_1 + \frac{\mathbf{h}_{12}}{\mathbf{h}_{22}} \mathbf{I}_2$$
$$\rightarrow \left\{ \begin{array}{l} \mathbf{V}_1 = \left(\mathbf{h}_{11} - \frac{\mathbf{h}_{12}\mathbf{h}_{21}}{\mathbf{h}_{22}} \right) \mathbf{I}_1 + \frac{\mathbf{h}_{12}}{\mathbf{h}_{22}} \mathbf{I}_2 \\ \mathbf{V}_2 = -\frac{\mathbf{h}_{12}}{\mathbf{h}_{22}} \mathbf{I}_1 + \frac{1}{\mathbf{h}_{22}} \mathbf{I}_2 \end{array} \right. \rightarrow \left[\begin{array}{ll} \mathbf{z}_{11} = \mathbf{h}_{11} - \frac{\mathbf{h}_{12}\mathbf{h}_{21}}{\mathbf{h}_{22}} & \mathbf{z}_{12} = \frac{\mathbf{h}_{12}}{\mathbf{h}_{22}} \\ \mathbf{z}_{21} = -\frac{\mathbf{h}_{12}}{\mathbf{h}_{22}} & \mathbf{z}_{22} = \frac{1}{\mathbf{h}_{22}} \end{array} \right]$$

Two-port Networks


1. Introduction
2. Parameters
3. Relationships between Parameters
- 4. Two-port Network Analysis**
5. Interconnection of Networks
6. T & Π Networks
7. Equivalent Two-port Networks of Magnetically Coupled Circuits
8. Input Impedance
9. Transfer Function



Ex. 1 Two-port Network Analysis (1)

$$\mathbf{E} = 220 \angle 0^\circ \text{ V}; \mathbf{Z}_L = j50 \Omega;$$
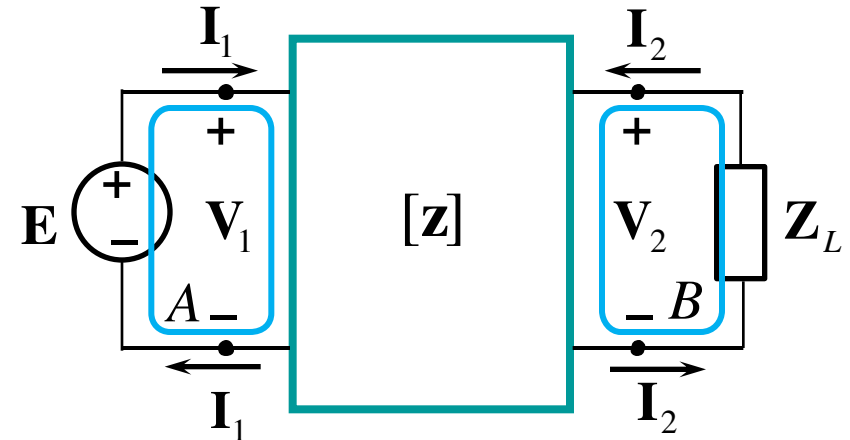
$$\mathbf{z} = \begin{bmatrix} 10 & j20 \\ j20 & 40 \end{bmatrix}; \text{find currents?}$$




$$\left\{ \begin{array}{l} \mathbf{V}_1 = 10\mathbf{I}_1 + j20\mathbf{I}_2 \\ \mathbf{V}_2 = j20\mathbf{I}_1 + 40\mathbf{I}_2 \\ \mathbf{V}_1 = \mathbf{E} = 220 \angle 0^\circ \text{ V} \\ \mathbf{V}_2 = -\mathbf{Z}_L \mathbf{I}_2 = -j50\mathbf{I}_2 \end{array} \right\} \rightarrow \left\{ \begin{array}{l} 220 \angle 0^\circ = 10\mathbf{I}_1 + j20\mathbf{I}_2 \\ -j50\mathbf{I}_2 = j20\mathbf{I}_1 + 40\mathbf{I}_2 \end{array} \right. \rightarrow \left\{ \begin{array}{l} \mathbf{I}_1 = 14.09 + j4.94 \text{ A} \\ \mathbf{I}_2 = -2.47 - j3.96 \text{ A} \end{array} \right.$$

Ex. 2 Two-port Network Analysis (2)

$$E = 220 \text{ V};$$
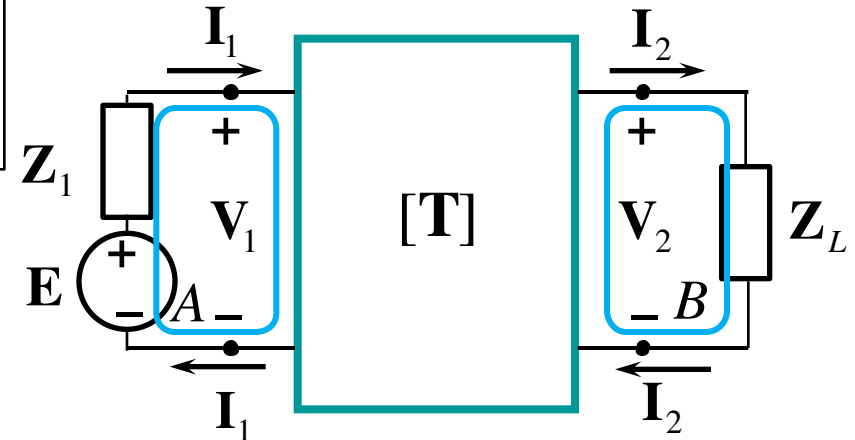
$$Z_1 = 20 \Omega; \quad Z_L = j50 \Omega; \quad T = \begin{bmatrix} 3 & -200 \\ 0.04 & -3 \end{bmatrix}.$$




$$\begin{cases} V_1 = 3V_2 + 200I_2 \\ I_1 = 0.04V_2 + 3I_2 \\ ZI_1 + V_1 = E \\ Z_L I_2 - V_2 = 0 \end{cases} \rightarrow \begin{cases} V_1 = 3V_2 + 200I_2 \\ I_1 = 0.04V_2 + 3I_2 \\ 20I_1 + V_1 = 220 \\ j50I_2 - V_2 = 0 \end{cases} \rightarrow \begin{cases} I_1 = 2.46 - j0.11 \text{ A} \\ I_2 = 0.55 - j0.40 \text{ A} \end{cases}$$

Ex. 3

Two-port Network Analysis (3)

$$\begin{aligned} E &= 200 \text{ V}; Z_n = 5 \, \Omega; \\ Z_f &= j10 \, \Omega; Z_L = -j20 \, \Omega; Y = \begin{bmatrix} 0.0455 & -0.0182 \\ -0.0182 & 0.0273 \end{bmatrix} \text{ S.} \end{aligned}$$

Method 1

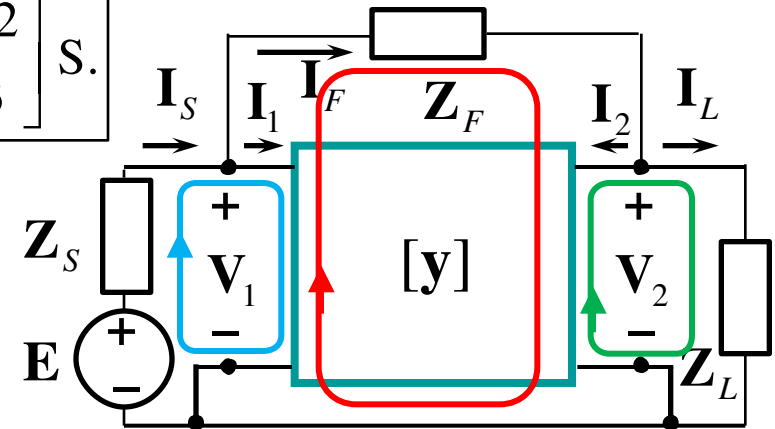


$$\begin{cases} I_1 = y_{11} V_1 + y_{12} V_2 \\ I_2 = y_{21} V_1 + y_{22} V_2 \\ I_S - I_1 - I_F = 0 \\ I_F - I_2 - I_L = 0 \\ Z_S I_S + V_1 = E \\ Z_F I_F - V_1 + V_2 = 0 \\ V_2 - Z_L I_L = 0 \end{cases}$$

$$\rightarrow \begin{cases} I_S = 12.80 + j7.99 \text{ A} \\ I_L = 7.20 + j10.40 \text{ A} \end{cases}$$

Ex. 3 Two-port Network Analysis (4)

$$\begin{aligned} E &= 200 \text{ V}; Z_n = 5 \, \Omega; \\ Z_f &= j10 \, \Omega; Z_L = -j20 \, \Omega; \mathbf{Y} = \begin{bmatrix} 0.0455 & -0.0182 \\ -0.0182 & 0.0273 \end{bmatrix} \text{ S.} \end{aligned}$$

Method 2

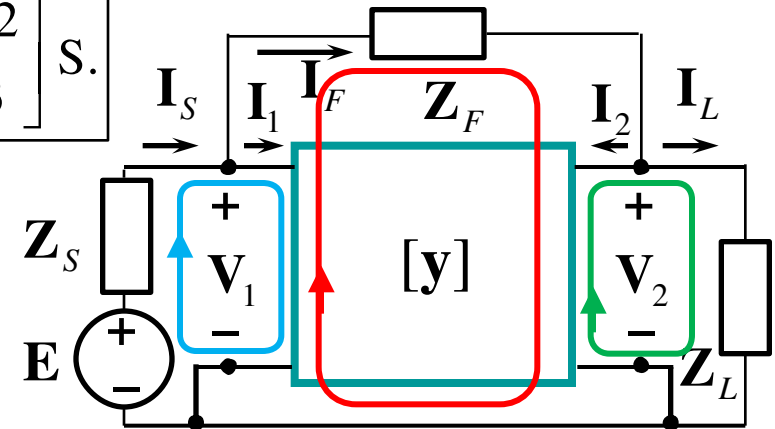


$$\begin{cases} \mathbf{I}_1 = \mathbf{y}_{11} \mathbf{V}_1 + \mathbf{y}_{12} \mathbf{V}_2 = \mathbf{I}_b - \mathbf{I}_r \\ \mathbf{I}_2 = \mathbf{y}_{21} \mathbf{V}_1 + \mathbf{y}_{22} \mathbf{V}_2 = \mathbf{I}_r - \mathbf{I}_g \\ \mathbf{Z}_S \mathbf{I}_b + \mathbf{V}_1 = \mathbf{E} \\ \mathbf{Z}_F \mathbf{I}_r - \mathbf{V}_1 + \mathbf{V}_2 = 0 \\ \mathbf{Z}_L \mathbf{I}_g - \mathbf{V}_2 = 0 \end{cases}$$

$$\rightarrow \begin{cases} \mathbf{I}_b = 12.80 + j7.99 \text{ A} = \mathbf{I}_S \\ \mathbf{I}_g = 7.20 + j10.40 \text{ A} = \mathbf{I}_L \end{cases}$$

Ex. 3 Two-port Network Analysis (5)

$$\begin{aligned} E &= 200 \text{ V}; Z_n = 5 \, \Omega; \\ Z_f &= j10 \, \Omega; Z_L = -j20 \, \Omega; Y = \begin{bmatrix} 0.0455 & -0.0182 \\ -0.0182 & 0.0273 \end{bmatrix} \text{ S.} \end{aligned}$$

Method 3

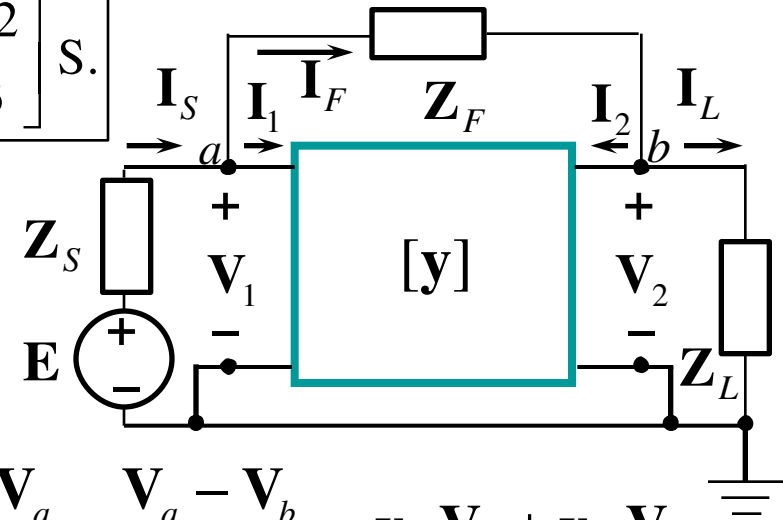


$$\left. \begin{aligned} I_S - I_1 - I_F &= 0 \\ I_F - I_2 - I_L &= 0 \\ I_1 &= y_{11} V_1 + y_{12} V_2 = y_{11} V_a + y_{12} V_b \\ I_2 &= y_{21} V_1 + y_{22} V_2 = y_{21} V_a + y_{22} V_b \\ I_S &= \frac{E - V_a}{Z_S} \\ I_L &= \frac{V_b}{Z_L} \\ I_F &= \frac{V_a - V_b}{Z_F} \end{aligned} \right\} \rightarrow \left\{ \begin{aligned} \frac{E - V_a}{Z_S} - \frac{V_a - V_b}{Z_F} &= y_{11} V_a + y_{12} V_b \\ \frac{V_a - V_b}{Z_F} - \frac{V_b}{Z_L} &= y_{21} V_a + y_{22} V_b \end{aligned} \right.$$

Ex. 3 Two-port Network Analysis (6)

$$\begin{aligned} E &= 200 \text{ V}; Z_n = 5 \Omega; \\ Z_f &= j10 \Omega; Z_L = -j20 \Omega; Y = \begin{bmatrix} 0.0455 & -0.0182 \\ -0.0182 & 0.0273 \end{bmatrix} \text{ S.} \end{aligned}$$

Method 3
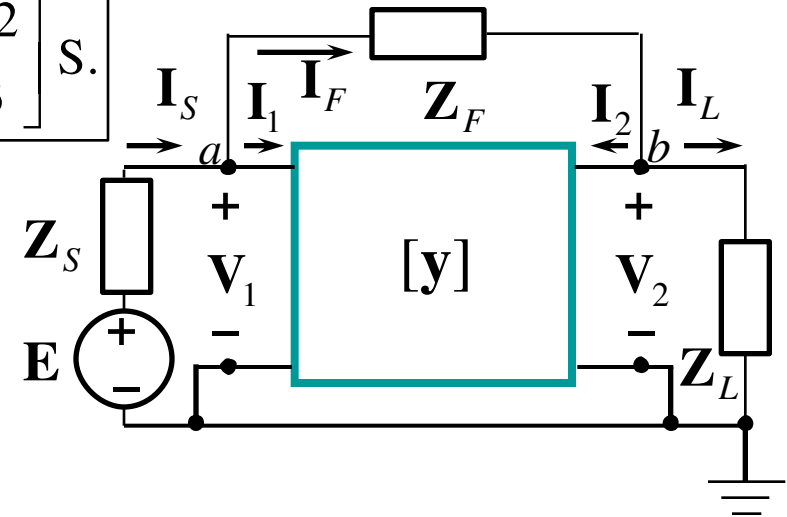
$$\begin{cases} \frac{E - V_a}{Z_S} - \frac{V_a - V_b}{Z_F} = y_{11} V_a + y_{12} V_b \\ \frac{V_a - V_b}{Z_F} - \frac{V_b}{Z_L} = y_{21} V_a + y_{22} V_b \end{cases}$$




$$\begin{aligned} \rightarrow \begin{cases} V_a = 135.99 - j39.97 \text{ V} \\ V_b = 207.92 - j143.97 \text{ V} \end{cases} &\rightarrow \begin{cases} I_S = \frac{E - V_a}{Z_S} = 12.80 + j7.99 \text{ A} \\ I_L = \frac{V_b}{Z_L} = 7.20 + j10.40 \text{ A} \end{cases} \end{aligned}$$

Ex. 4

Two-port Network Analysis (7)

Write equations?

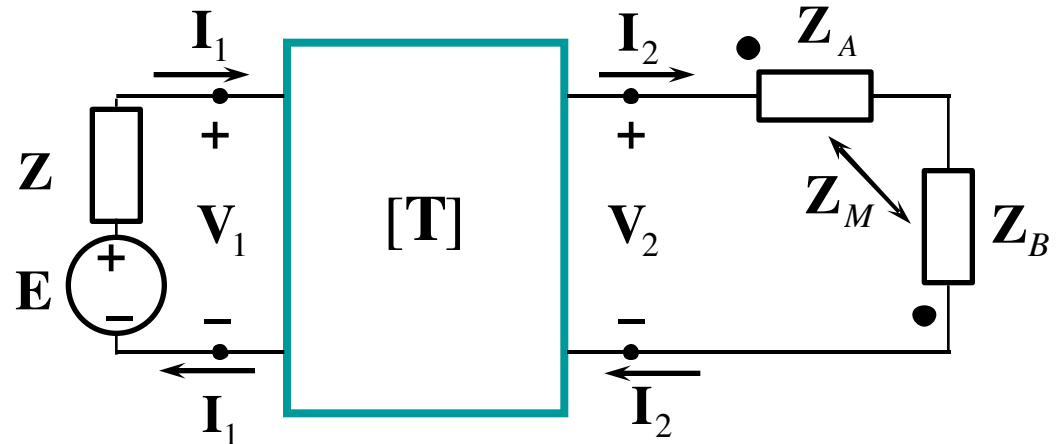


$$\begin{cases} \begin{cases} \mathbf{V}_1 = \mathbf{A}\mathbf{V}_2 - \mathbf{B}\mathbf{I}_2 \\ \mathbf{I}_1 = \mathbf{C}\mathbf{V}_2 - \mathbf{D}\mathbf{I}_2 \end{cases} \\ \mathbf{Z}\mathbf{I}_1 + \mathbf{V}_1 = \mathbf{E} \\ \mathbf{V}_2 = (\mathbf{Z}_A + \mathbf{Z}_B - 2\mathbf{Z}_M)\mathbf{I}_2 \end{cases}$$

Ex. 5 Two-port Network Analysis (8)


$e = 10 + 20\cos 5t$ V. Find i_1 ?
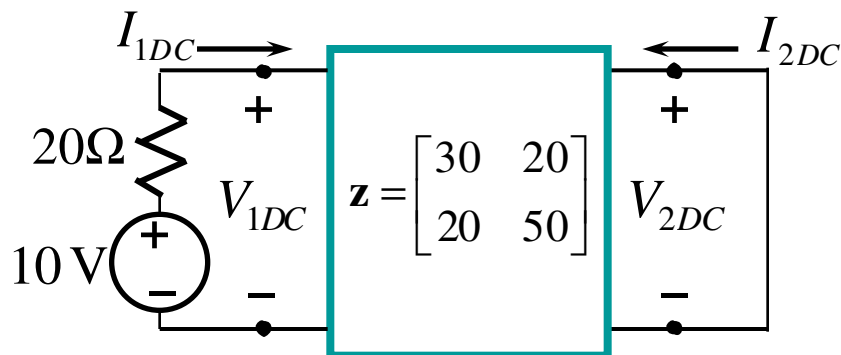
$$\rightarrow i_1(t) = 0.31 + 0.60 \cos(5t - 4.76^\circ) \text{ A}$$



$$\begin{cases} V_{1DC} = 30I_{1DC} + 20I_{2DC} \\ V_{2DC} = 20I_{1DC} + 50I_{2DC} \\ 10I_{1DC} + V_{1DC} = 10 \\ V_{2DC} = 0 \end{cases}$$

$$\rightarrow I_{1DC} = 0.31 \text{ A}$$

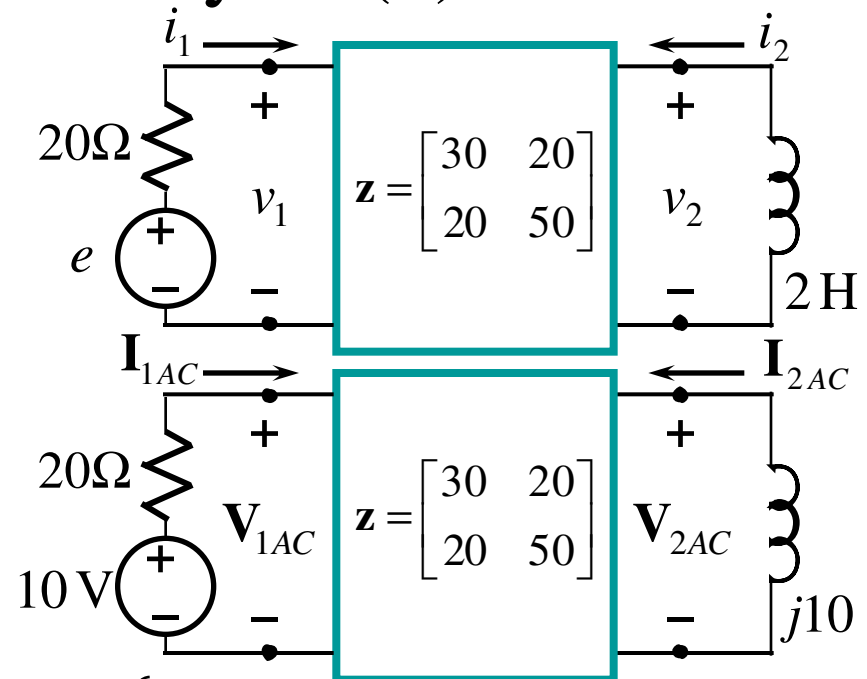

$$\begin{cases} \mathbf{V}_{1AC} = 30\mathbf{I}_{1AC} + 20\mathbf{I}_{2AC} \\ \mathbf{V}_{2AC} = 20\mathbf{I}_{1AC} + 50\mathbf{I}_{2AC} \\ 10\mathbf{I}_{1AC} + \mathbf{V}_{1AC} = 20 \\ \mathbf{V}_{2AC} + j20\mathbf{I}_{2AC} = 0 \end{cases}$$

$$\rightarrow \mathbf{I}_{1AC} = 0.60 \angle -4.76^\circ \text{ A}$$

Ex. 6

Two-port Network Analysis (9)

Find $i_1(t)$?



$$v_C(0) = 12 \text{ V}$$

$$\begin{cases} v_1(0) = 30i_1(0) + 20i_2(0) \\ v_2(0) = 20i_1(0) + 50i_2(0) \\ v_1(0) = 12 \\ v_2(0) = -10i_2(0) \end{cases}$$

$$\rightarrow i_1(0) = 0.5143 \text{ A} = i_L(0)$$

$$\begin{cases} V_1(s) = 30I_1(s) + 20I_2(s) \\ V_2(s) = 20I_1(s) + 50I_2(s) \\ \left(2s + \frac{200}{s}\right)I_1(s) + V_1(s) = 1.03 + \frac{12}{s} \\ V_2(s) = -10I_2(s) \end{cases}$$
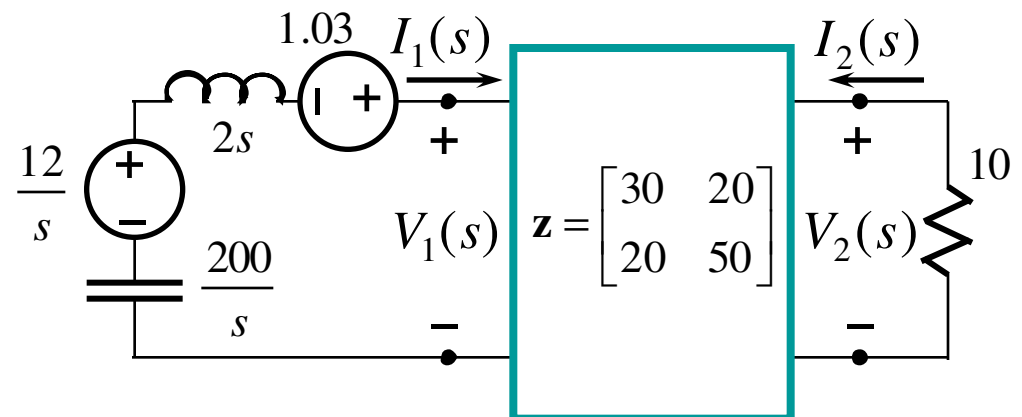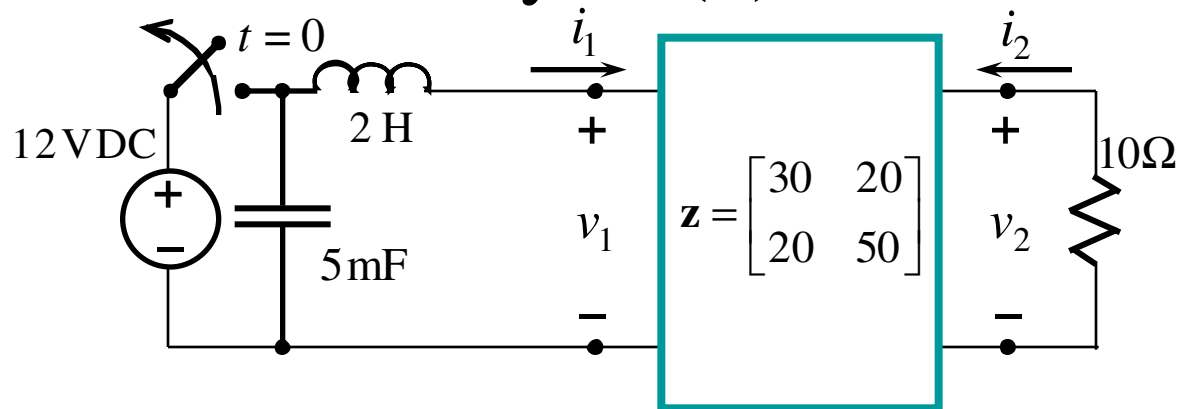
$$\rightarrow I_1(s) = \frac{0.515s + 6}{s^2 + 11.667s + 100} \text{ A} \quad \rightarrow \boxed{i_1(t) = 0.6334e^{-5.83t} \cos(8.12t - 35.6^\circ) \text{ A}}$$




Two-port Networks

1. Introduction
2. Parameters
3. Relationships between Parameters
4. Two-port Network Analysis
- 5. Interconnection of Networks**
6. T & Π Networks
7. Equivalent Two-port Networks of Magnetically Coupled Circuits
8. Input Impedance
9. Transfer Function




Interconnection of Networks (1)

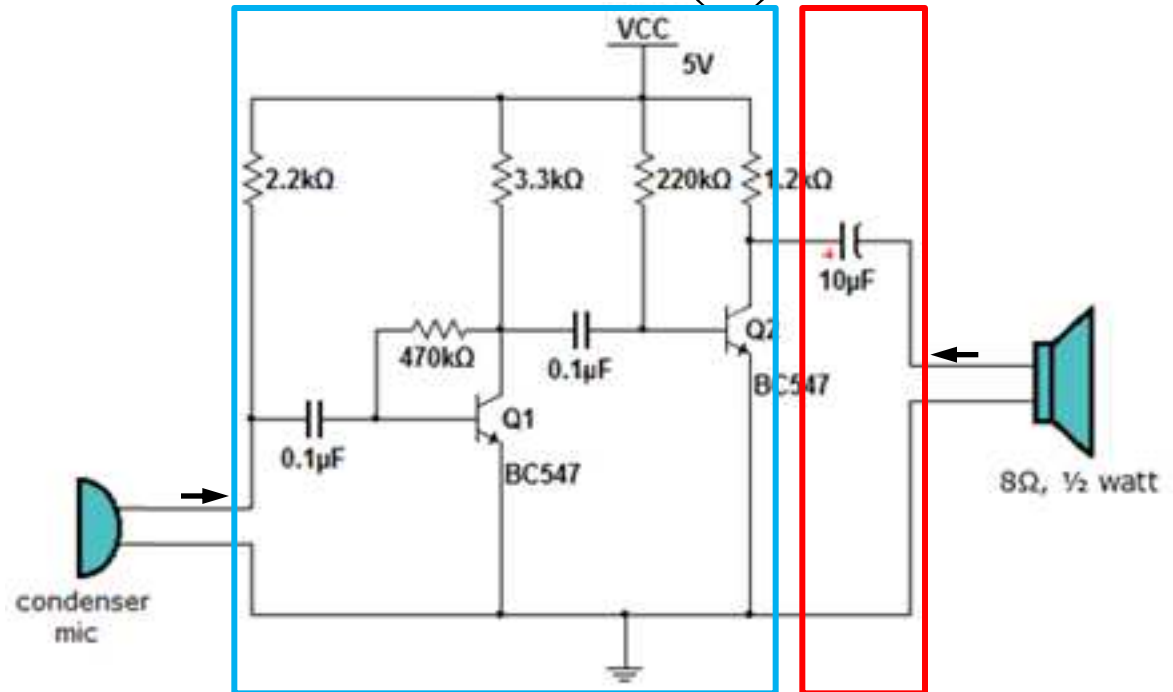1. Series
2. Parallel
3. Cascade
4. Hybrid 1
5. Hybrid 2



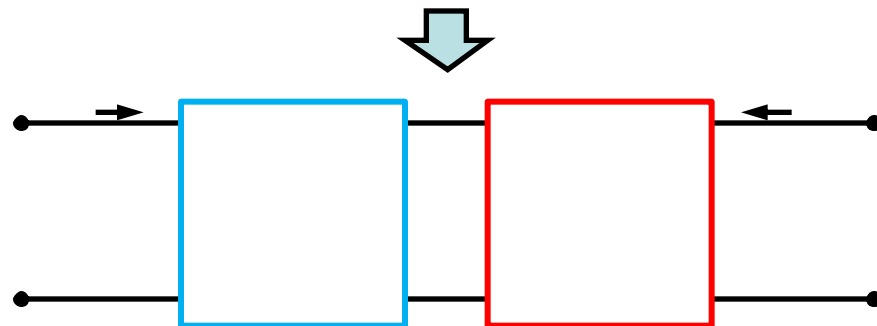
<https://www.efxkits.us/two-transistor-audio-amplifier-circuit-explanation/>




<https://sites.google.com/site/ncpdhbkhn/home>

Interconnection of Networks (2), Series

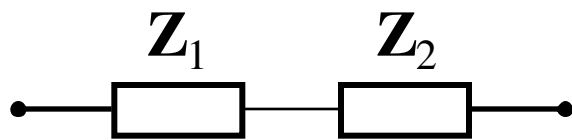

$$\begin{cases} \mathbf{I} = \mathbf{I}_1 = \mathbf{I}_2 \\ \mathbf{V} = \mathbf{V}_1 + \mathbf{V}_2 \end{cases}$$
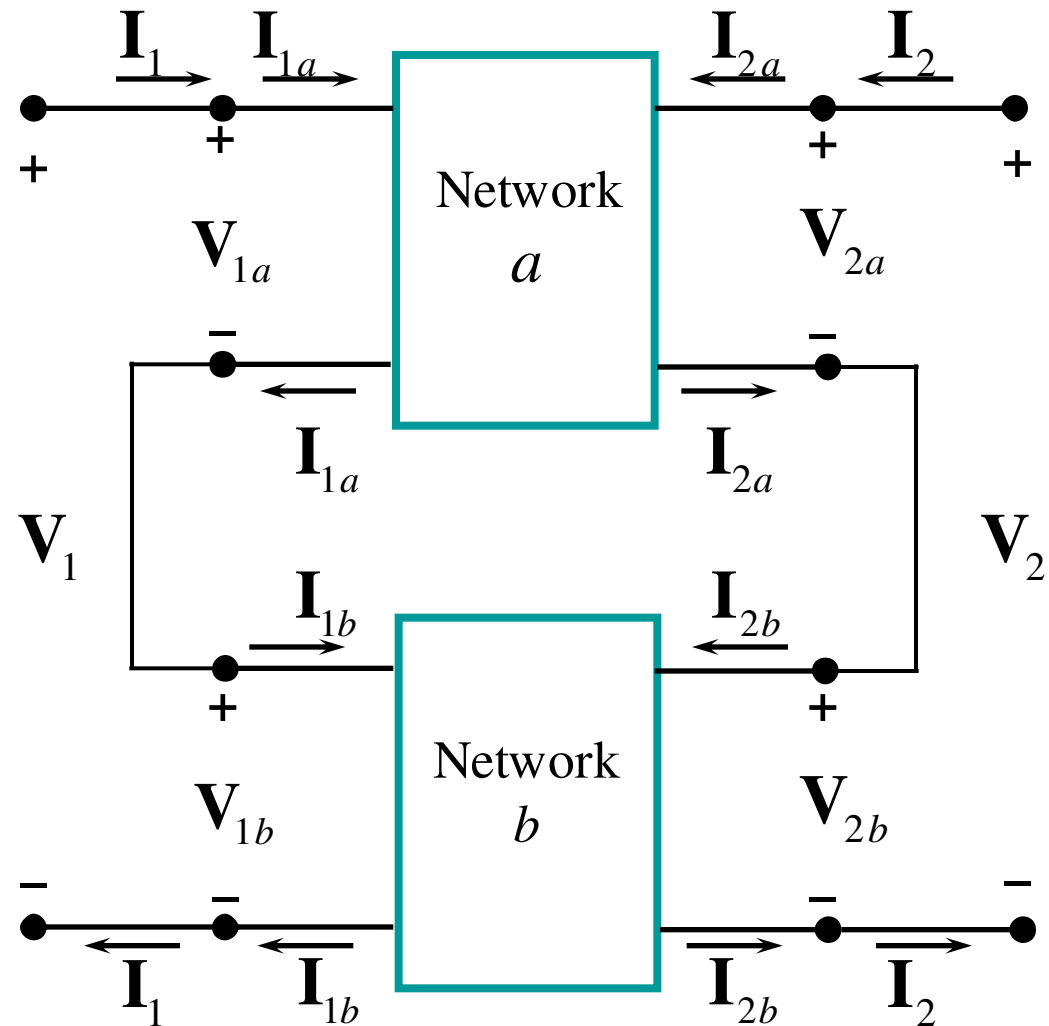
$$\begin{cases} \mathbf{I}_1 = \mathbf{I}_{1a} = \mathbf{I}_{1b} \\ \mathbf{V}_1 = \mathbf{V}_{1a} + \mathbf{V}_{1b} \\ \mathbf{I}_2 = \mathbf{I}_{2a} = \mathbf{I}_{2b} \\ \mathbf{V}_2 = \mathbf{V}_{2a} + \mathbf{V}_{2b} \end{cases}$$



Interconnection of Networks (3), Series

$$\left\{ \begin{array}{l} \mathbf{I}_1 = \mathbf{I}_{1a} = \mathbf{I}_{1b} \\ \mathbf{V}_1 = \mathbf{V}_{1a} + \mathbf{V}_{1b} \\ \mathbf{I}_2 = \mathbf{I}_{2a} = \mathbf{I}_{2b} \\ \mathbf{V}_2 = \mathbf{V}_{2a} + \mathbf{V}_{2b} \end{array} \right.$$

Network a :

$$\left\{ \begin{array}{l} \mathbf{V}_{1a} = \mathbf{z}_{11a} \mathbf{I}_{1a} + \mathbf{z}_{12a} \mathbf{I}_{2a} \\ \mathbf{V}_{2a} = \mathbf{z}_{21a} \mathbf{I}_{1a} + \mathbf{z}_{22a} \mathbf{I}_{2a} \end{array} \right.$$

Network b :

$$\left\{ \begin{array}{l} \mathbf{V}_{1b} = \mathbf{z}_{11b} \mathbf{I}_{1b} + \mathbf{z}_{12b} \mathbf{I}_{2b} \\ \mathbf{V}_{2b} = \mathbf{z}_{21b} \mathbf{I}_{1b} + \mathbf{z}_{22b} \mathbf{I}_{2b} \end{array} \right.$$

$$\mathbf{I}_1 = \mathbf{I}_{1a} = \mathbf{I}_{1b}$$

$$\mathbf{I}_2 = \mathbf{I}_{2a} = \mathbf{I}_{2b}$$

$$\rightarrow \left\{ \begin{array}{l} \left\{ \begin{array}{l} \mathbf{V}_{1a} = \mathbf{z}_{11a} \mathbf{I}_1 + \mathbf{z}_{12a} \mathbf{I}_2 \\ \mathbf{V}_{2a} = \mathbf{z}_{21a} \mathbf{I}_1 + \mathbf{z}_{22a} \mathbf{I}_2 \end{array} \right. \\ \left\{ \begin{array}{l} \mathbf{V}_{1b} = \mathbf{z}_{11b} \mathbf{I}_1 + \mathbf{z}_{12b} \mathbf{I}_2 \\ \mathbf{V}_{2b} = \mathbf{z}_{21b} \mathbf{I}_1 + \mathbf{z}_{22b} \mathbf{I}_2 \end{array} \right. \end{array} \right.$$

Interconnection of Networks (4), Series

$$\left\{ \begin{array}{l} \mathbf{I}_1 = \mathbf{I}_{1a} = \mathbf{I}_{1b} \\ \mathbf{V}_1 = \mathbf{V}_{1a} + \mathbf{V}_{1b} \\ \mathbf{I}_2 = \mathbf{I}_{2a} = \mathbf{I}_{2b} \\ \mathbf{V}_2 = \mathbf{V}_{2a} + \mathbf{V}_{2b} \end{array} \right. \left\{ \begin{array}{l} \text{Network } a: \left\{ \begin{array}{l} \mathbf{V}_{1a} = \mathbf{z}_{11a}\mathbf{I}_1 + \mathbf{z}_{12a}\mathbf{I}_2 \\ \mathbf{V}_{2a} = \mathbf{z}_{21a}\mathbf{I}_1 + \mathbf{z}_{22a}\mathbf{I}_2 \end{array} \right. \\ \text{Network } b: \left\{ \begin{array}{l} \mathbf{V}_{1b} = \mathbf{z}_{11b}\mathbf{I}_1 + \mathbf{z}_{12b}\mathbf{I}_2 \\ \mathbf{V}_{2b} = \mathbf{z}_{21b}\mathbf{I}_1 + \mathbf{z}_{22b}\mathbf{I}_2 \end{array} \right. \\ \mathbf{V}_1 = \mathbf{V}_{1a} + \mathbf{V}_{1b} \\ \mathbf{V}_2 = \mathbf{V}_{2a} + \mathbf{V}_{2b} \end{array} \right. \rightarrow$$

$$\rightarrow \left\{ \begin{array}{l} \mathbf{V}_1 = \mathbf{V}_{1a} + \mathbf{V}_{1b} = (\mathbf{z}_{11a} + \mathbf{z}_{11b})\mathbf{I}_1 + (\mathbf{z}_{12a} + \mathbf{z}_{12b})\mathbf{I}_2 \\ \mathbf{V}_2 = \mathbf{V}_{2a} + \mathbf{V}_{2b} = (\mathbf{z}_{21a} + \mathbf{z}_{21b})\mathbf{I}_1 + (\mathbf{z}_{22a} + \mathbf{z}_{22b})\mathbf{I}_2 \end{array} \right.$$

Interconnection of Networks (5), Series


$$\begin{cases} \mathbf{V}_1 = \mathbf{V}_{1a} + \mathbf{V}_{1b} = (\mathbf{z}_{11a} + \mathbf{z}_{11b})\mathbf{I}_1 + (\mathbf{z}_{12a} + \mathbf{z}_{12b})\mathbf{I}_2 \\ \mathbf{V}_2 = \mathbf{V}_{2a} + \mathbf{V}_{2b} = (\mathbf{z}_{21a} + \mathbf{z}_{21b})\mathbf{I}_1 + (\mathbf{z}_{22a} + \mathbf{z}_{22b})\mathbf{I}_2 \end{cases}$$

$$\Leftrightarrow \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{z}_{11a} + \mathbf{z}_{11b} & \mathbf{z}_{12a} + \mathbf{z}_{12b} \\ \mathbf{z}_{21a} + \mathbf{z}_{21b} & \mathbf{z}_{22a} + \mathbf{z}_{22b} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = [\mathbf{z}] \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$


$$[\mathbf{z}_a] = \begin{bmatrix} \mathbf{z}_{11a} & \mathbf{z}_{12a} \\ \mathbf{z}_{21a} & \mathbf{z}_{22a} \end{bmatrix}; [\mathbf{z}_b] = \begin{bmatrix} \mathbf{z}_{11b} & \mathbf{z}_{12b} \\ \mathbf{z}_{21b} & \mathbf{z}_{22b} \end{bmatrix}$$

$$\longrightarrow \boxed{[\mathbf{z}] = [\mathbf{z}_a] + [\mathbf{z}_b]}$$


Interconnection of Networks (6), Series

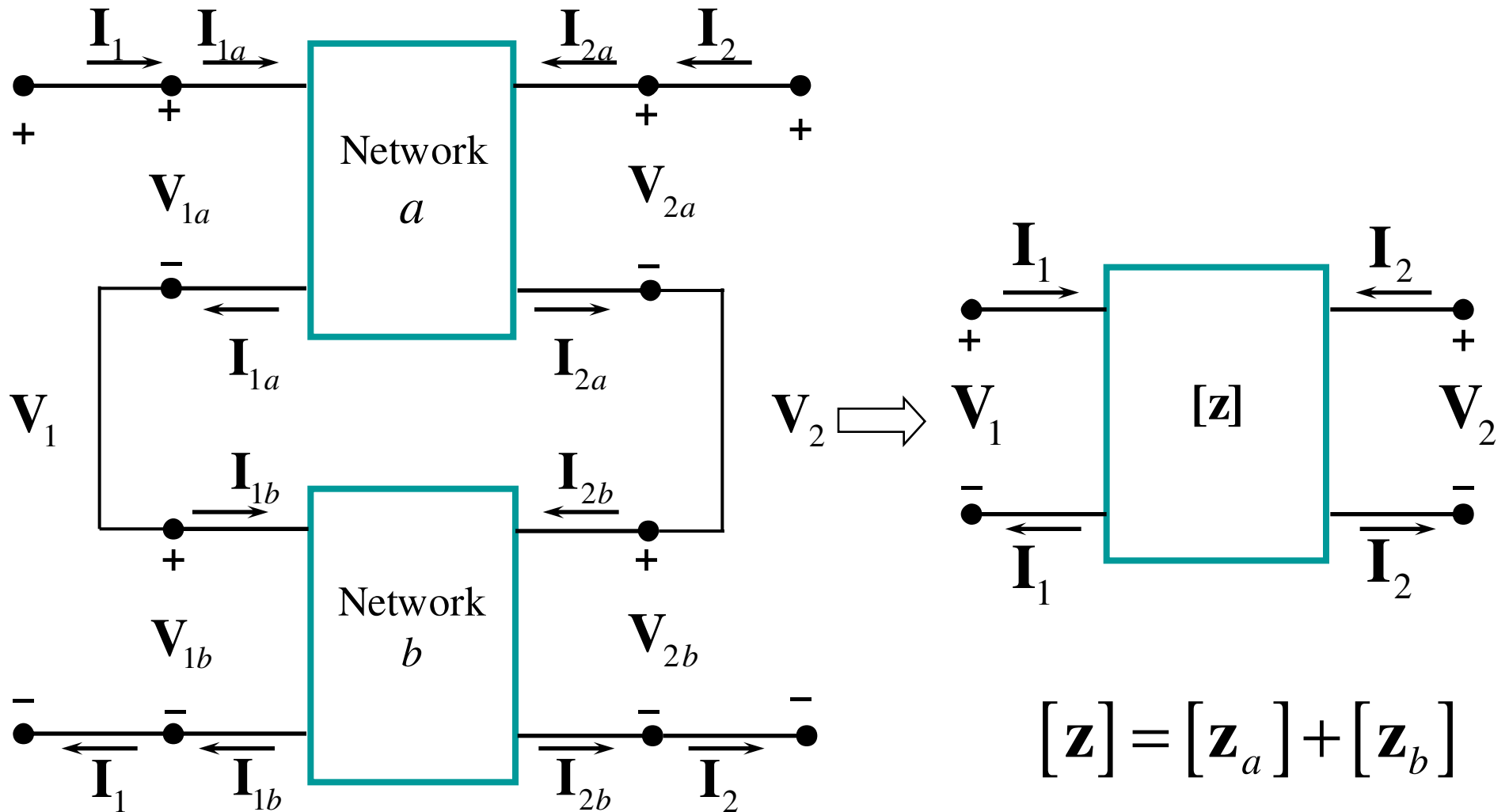

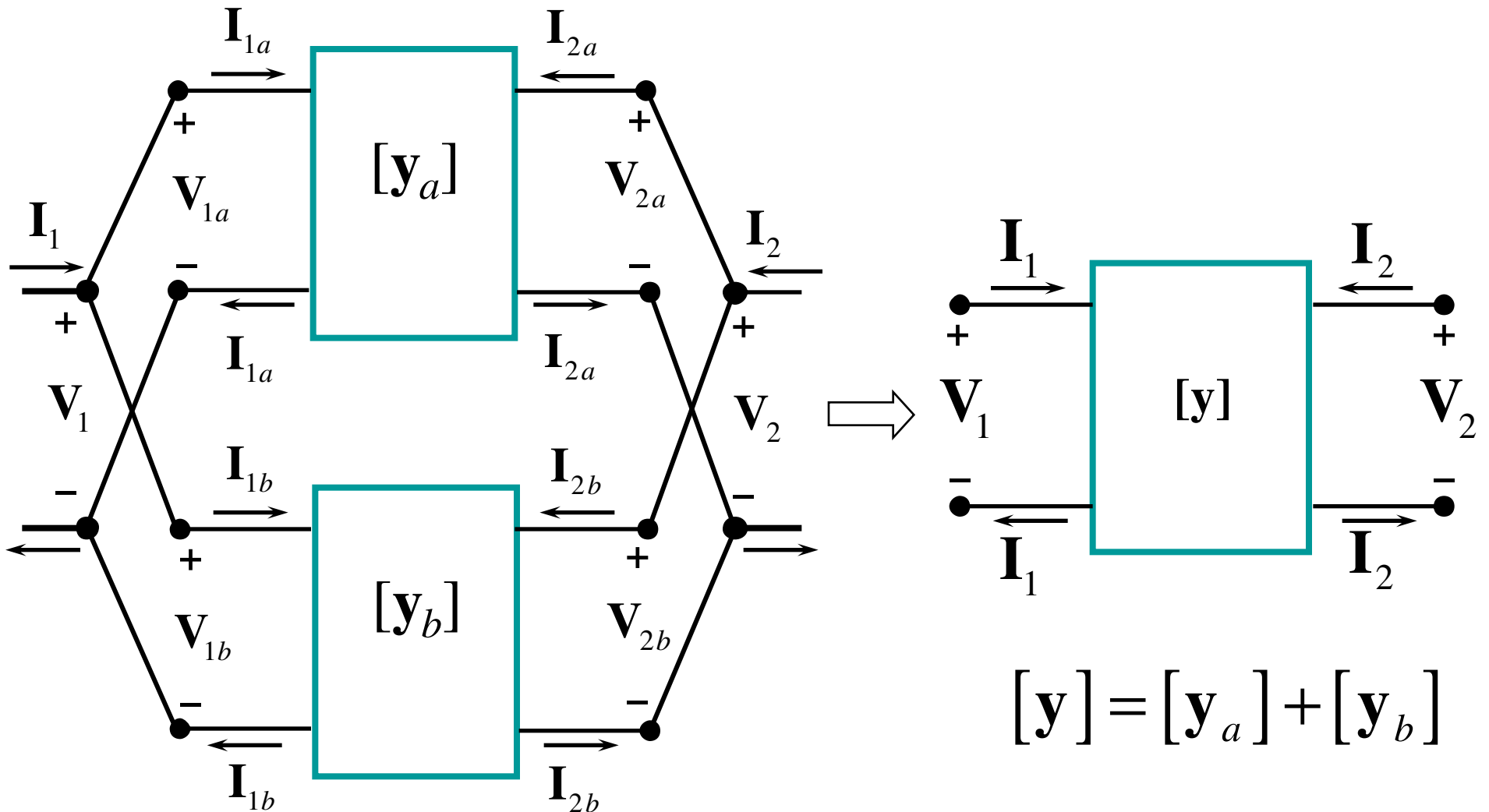Interconnection of Networks (7), Parallel




Interconnection of Networks (8), Cascade

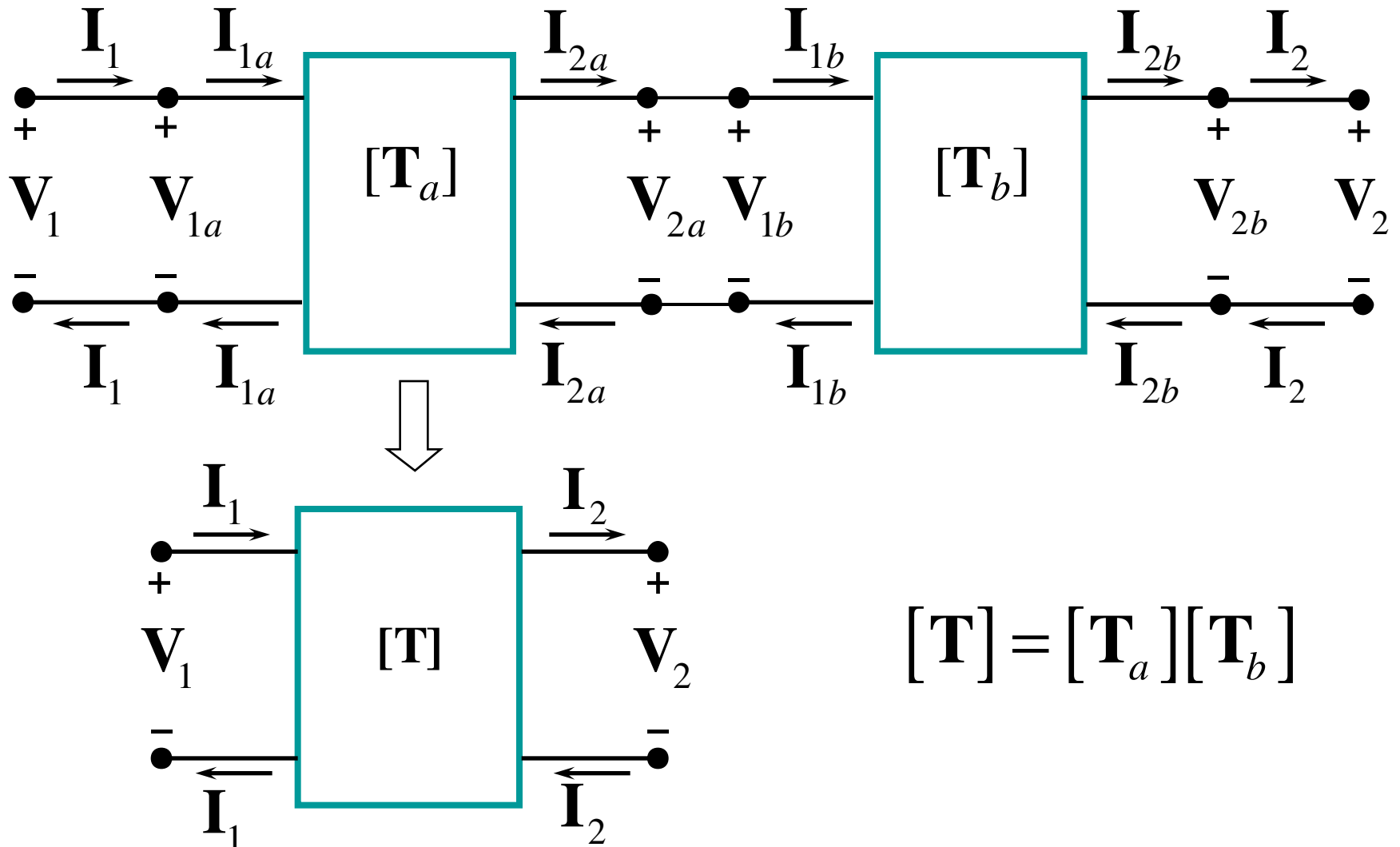


$$[T] = [T_a][T_b]$$

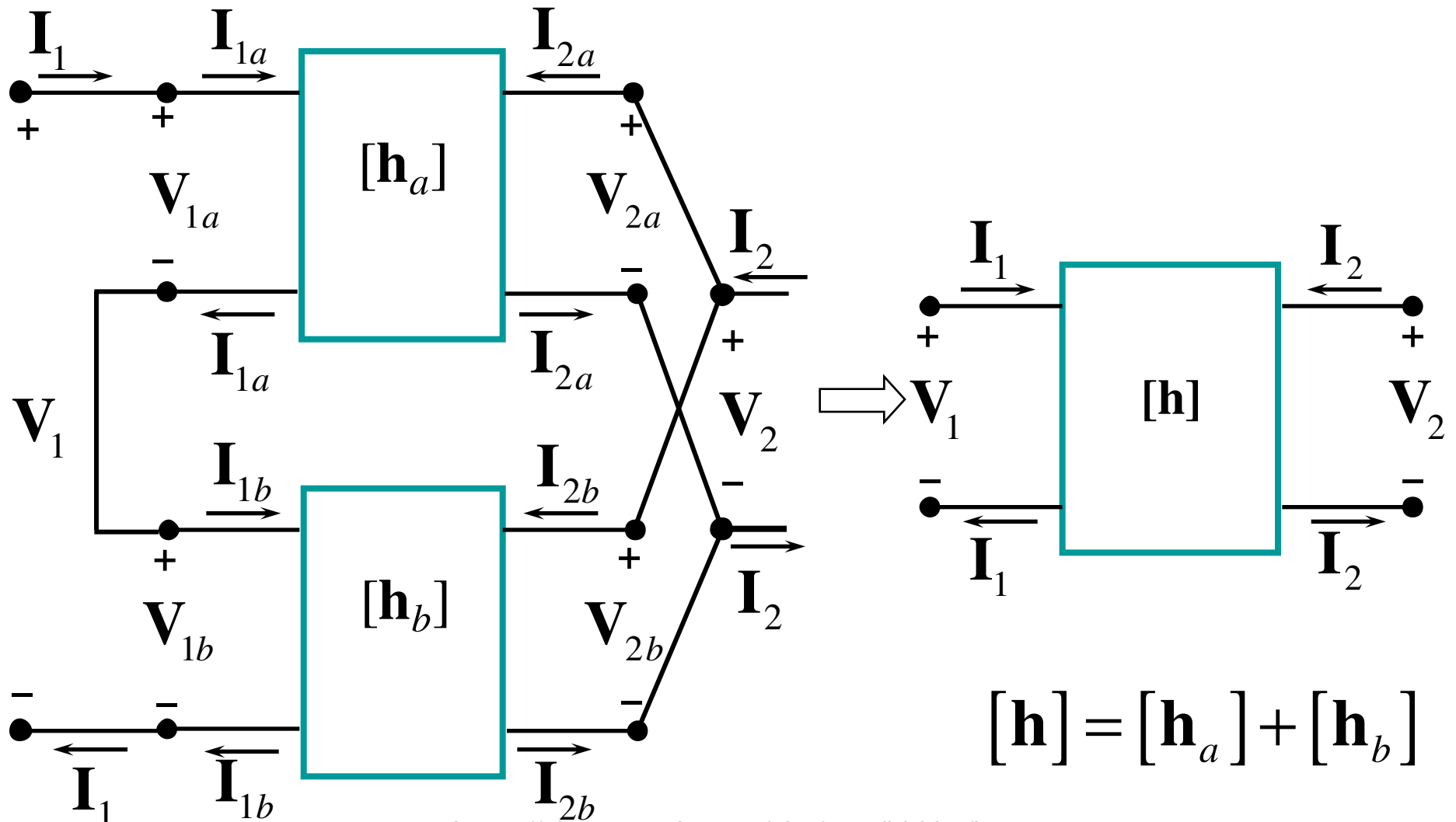Interconnection of Networks (9), Hybrid 1



Interconnection of Networks (10), Hybrid 2

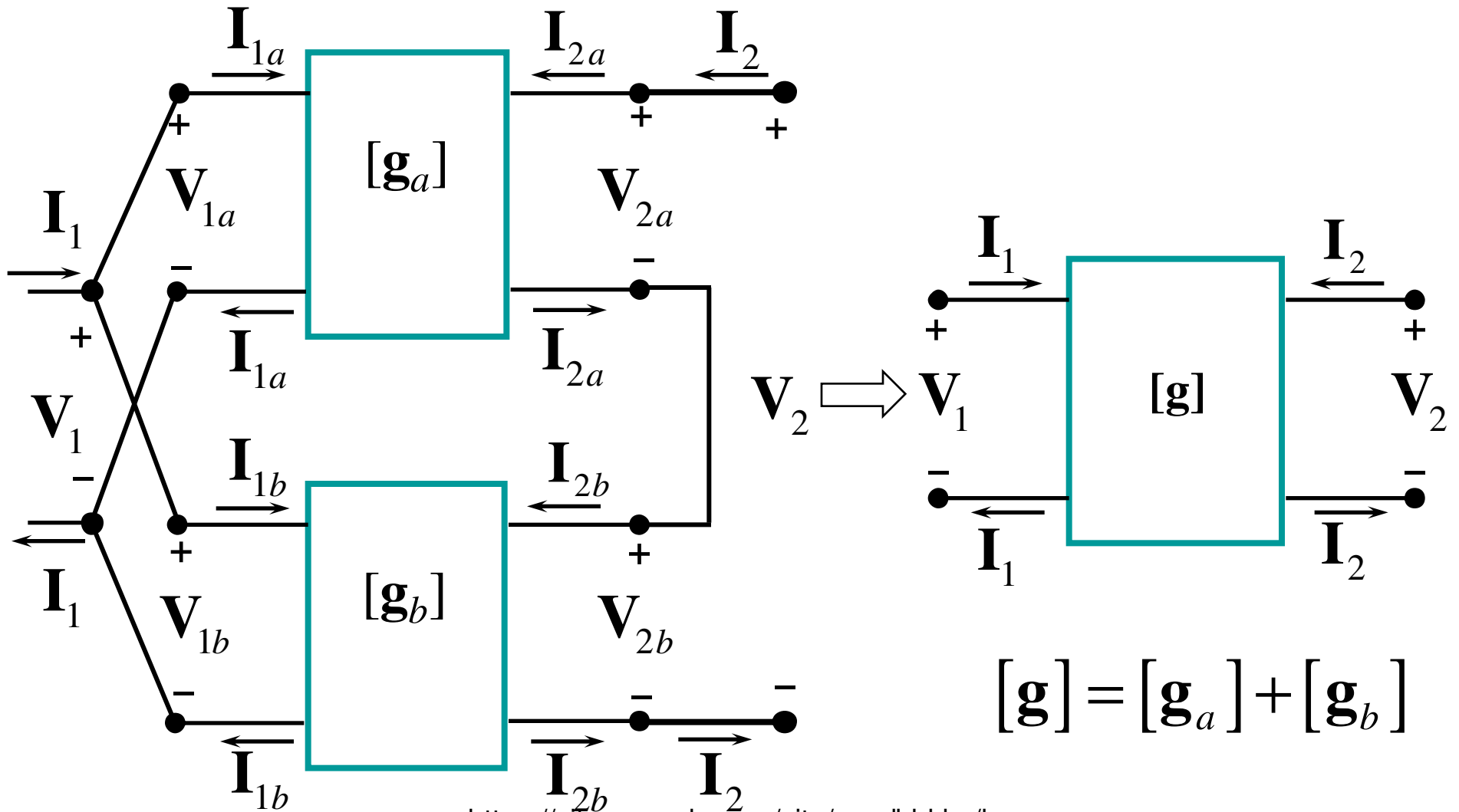

Ex. 1


Interconnection of Networks (11)

$$\begin{aligned} E &= 220\text{V}; Z_2 = j10\ \Omega; \\ Z_a &= j20\ \Omega; Z_b = -j40\ \Omega; Z_c = 5\ \Omega; \mathbf{z} = \begin{bmatrix} 30 & 20 \\ 20 & 50 \end{bmatrix} \Omega. \end{aligned}$$

Method 1

$$\begin{cases} V_1 = 30I_1 + 20I_2 \\ V_2 = 20I_1 + 50I_2 \\ b: I_1 + I_2 - I_c = 0 \\ A: V_1 + Z_a I_1 + Z_c I_c = E \\ B: Z_2 I_2 + V_2 + Z_b I_2 + Z_c I_c = 0 \end{cases}$$
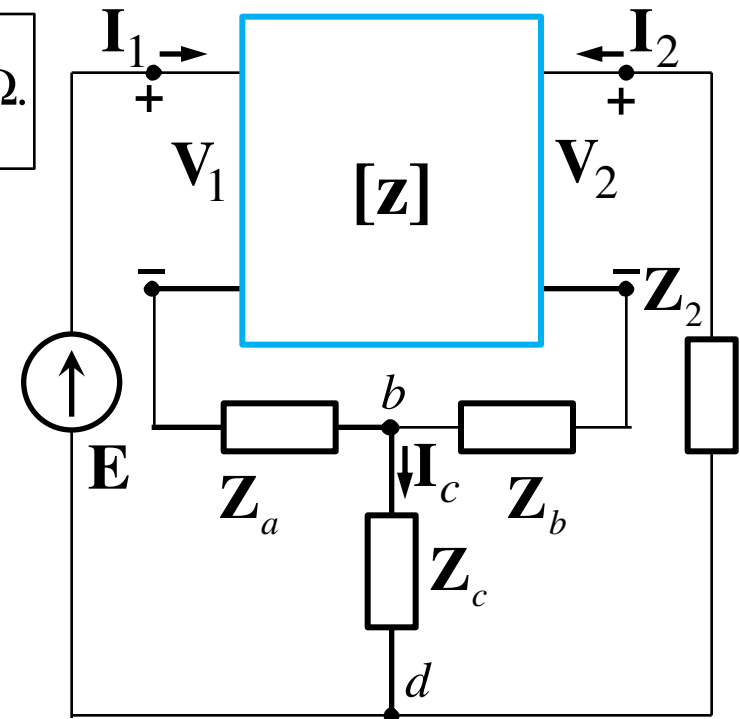
$$\rightarrow \begin{cases} I_1 = 6.27 - j3.64\text{ A} \\ I_2 = -2.89 + j0.076\text{ A} \\ I_c = 3.38 - j3.56\text{ A} \end{cases}$$



Ex. 1 Interconnection of Networks (12)

$$\begin{aligned} E &= 220\text{V}; Z_2 = j10\ \Omega; \\ Z_a &= j20\ \Omega; Z_b = -j40\ \Omega; Z_c = 5\ \Omega; \mathbf{z} = \begin{bmatrix} 30 & 20 \\ 20 & 50 \end{bmatrix} \Omega. \end{aligned}$$


Method 2

$$[\mathbf{z}'] = \begin{bmatrix} Z_a + Z_c & Z_c \\ Z_c & Z_b + Z_c \end{bmatrix} = \begin{bmatrix} 5 + j20 & 5 \\ 5 & 5 - j40 \end{bmatrix} \Omega$$

$$[\mathbf{z}] + [\mathbf{z}'] = \begin{bmatrix} 35 + j20 & 25 \\ 25 & 55 - j40 \end{bmatrix} \Omega$$

$$\begin{cases} \mathbf{V}'_1 = (35 + j20)\mathbf{I}_1 + 25\mathbf{I}_2 = 220 \\ \mathbf{V}'_2 = 25\mathbf{I}_1 + (55 - j40)\mathbf{I}_2 = -j10\mathbf{I}_2 \end{cases}$$
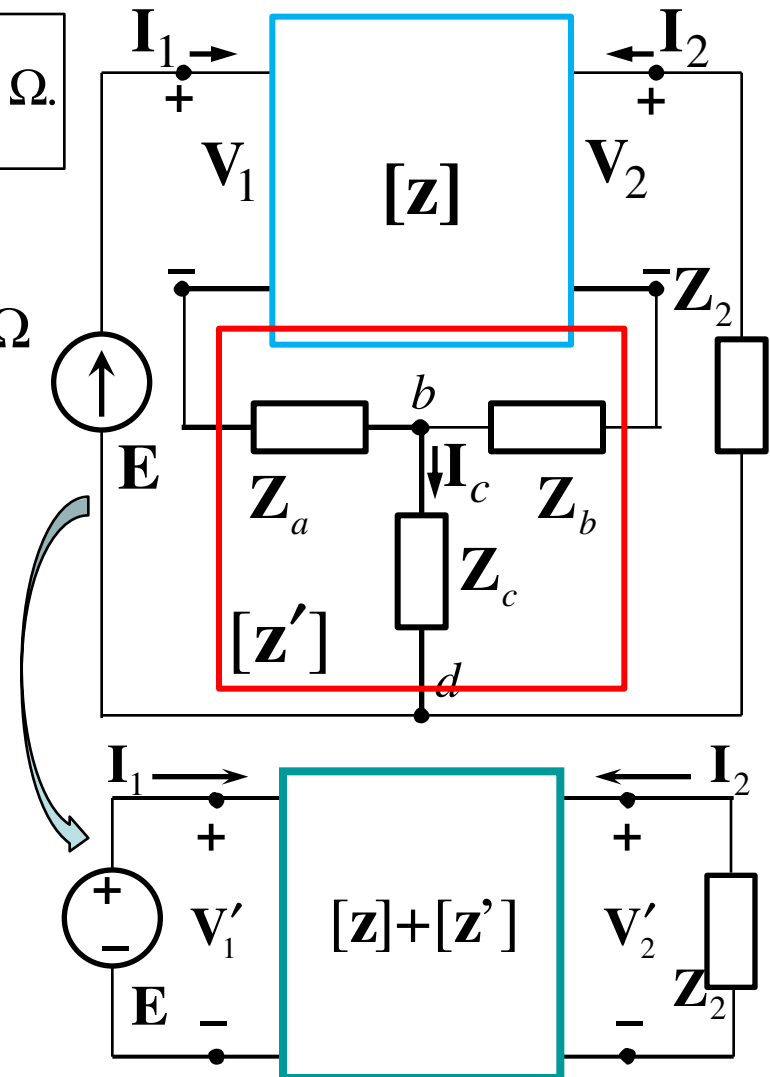
$$\rightarrow \begin{cases} \mathbf{I}_1 = 6.27 - j3.64\text{ A} \\ \mathbf{I}_2 = -2.89 + j0.076\text{ A} \end{cases}$$




Ex. 2 Interconnection of Networks (13)




$$E = 200\text{V}; Z_n = 5\ \Omega; \\ Z_f = j10\ \Omega; Z_L = -j20\ \Omega; Y = \begin{bmatrix} 0.0455 & -0.0182 \\ -0.0182 & 0.0273 \end{bmatrix} \text{S.}$$

$$\begin{cases} -V'_1 + Z_f I'_1 + V'_2 = 0 \\ -V'_1 - Z_f I'_2 + V'_2 = 0 \end{cases}$$
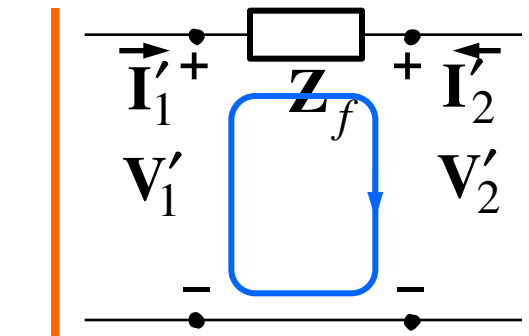
$$\rightarrow \begin{cases} I'_1 = \frac{V'_1}{Z_f} - \frac{V'_2}{Z_f} \\ I'_2 = -\frac{V'_1}{Z_f} + \frac{V'_2}{Z_f} \end{cases}$$



$$\rightarrow [y'] = \begin{bmatrix} -j0.10 & j0.10 \\ j0.10 & -j0.10 \end{bmatrix} \text{S}$$

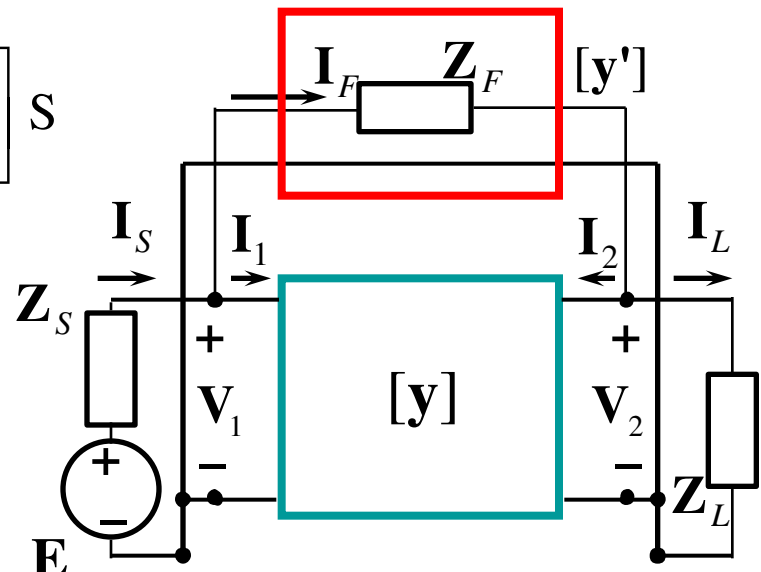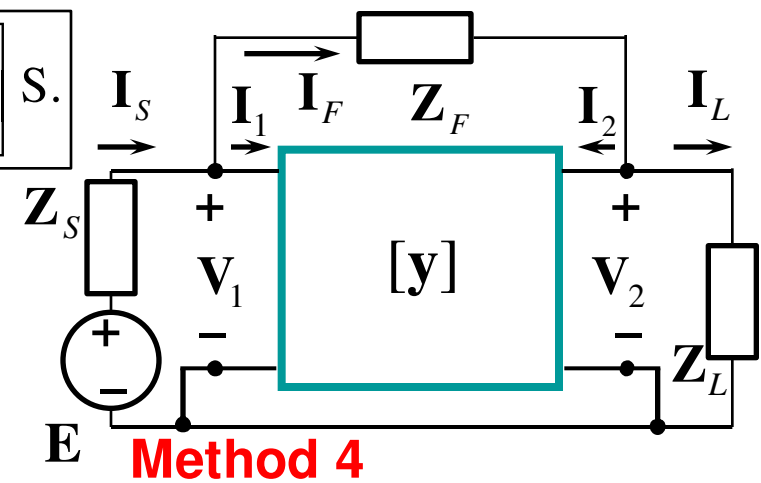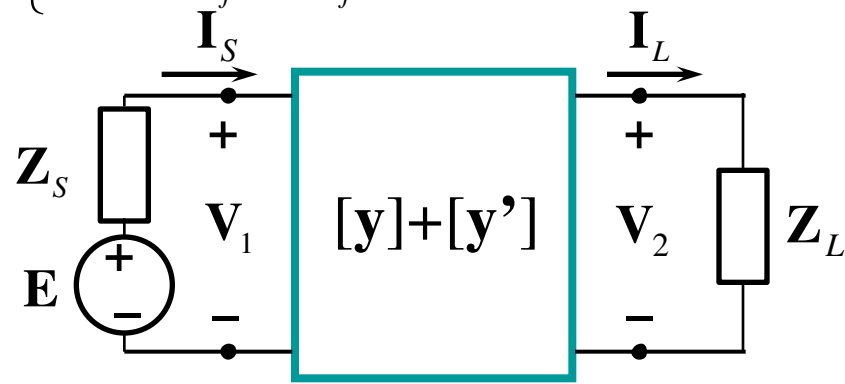

Ex. 2

Interconnection of Networks (14)

$$E = 200 \text{ V}; Z_n = 5 \Omega; Y = \begin{bmatrix} 0.0455 & -0.0182 \\ -0.0182 & 0.0273 \end{bmatrix} \text{ S.}$$



$$Z_f = j10 \Omega; Z_L = -j20 \Omega;$$

$$[y'] = \begin{bmatrix} -j0.10 & j0.10 \\ j0.10 & -j0.10 \end{bmatrix} \text{ S}$$

$$[y] + [y'] = \begin{bmatrix} 0.0455 - j0.10 & -0.0182 + j0.10 \\ -0.0182 + j0.10 & 0.0273 - j0.10 \end{bmatrix} \text{ S}$$

$$\begin{cases} I_S = (0.0455 - j0.10)V_1 - (0.0182 - j0.10)V_2 \\ -I_L = -(0.0182 - j0.10)V_1 + (0.0273 - j0.10)V_2 \\ 5I_S + V_1 = 200 \\ V_2 + j20I_L = 0 \end{cases}$$

$$\rightarrow \begin{cases} I_S = 12.76 + j8.02 \text{ A} \\ I_L = 7.22 + j10.41 \text{ A} \end{cases}$$

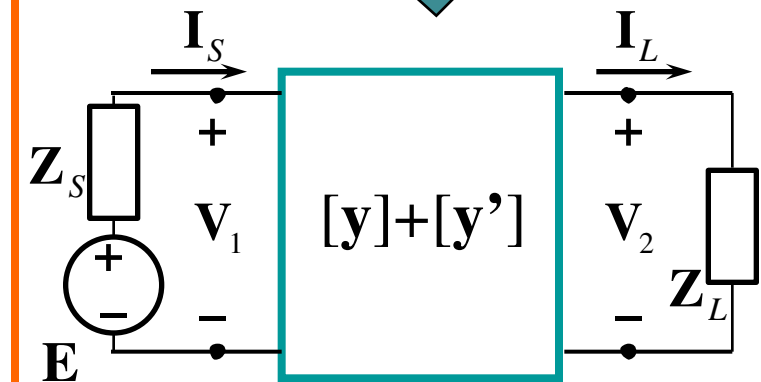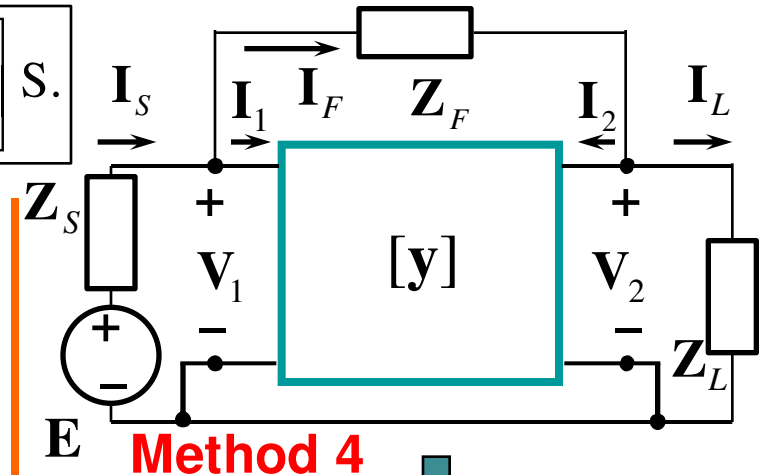




Ex. 2

Interconnection of Networks (15)

$$E = 200 \text{ V}; Z_n = 5 \Omega; Y = \begin{bmatrix} 0.0455 & -0.0182 \\ -0.0182 & 0.0273 \end{bmatrix} \text{ S.}$$

$$Z_f = j10 \Omega; Z_L = -j20 \Omega;$$

Method 5

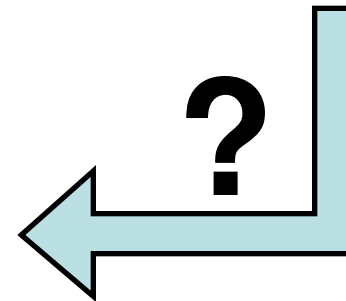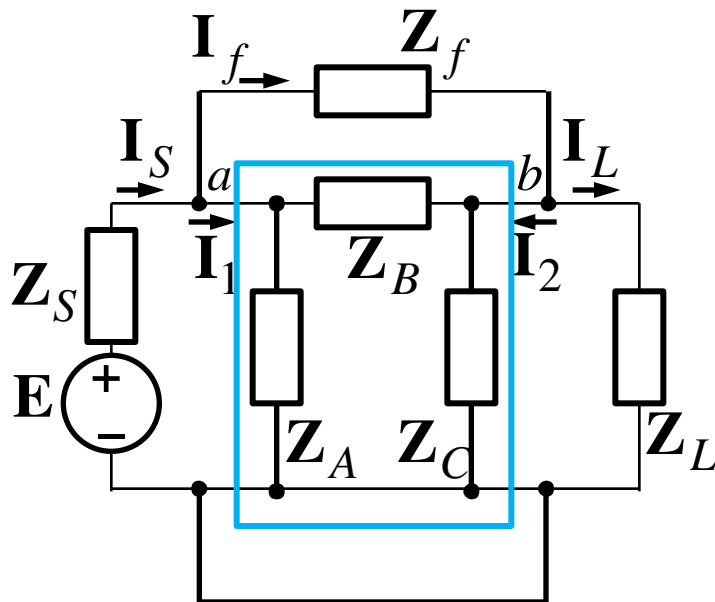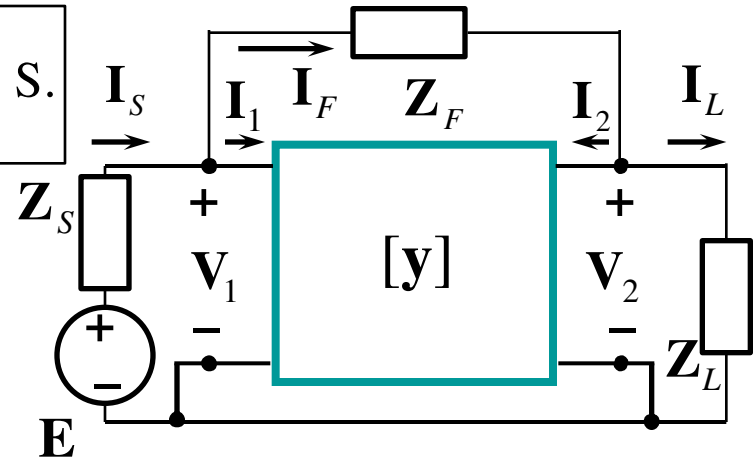


T & Π Networks

Two-port Networks



1. Introduction
2. Parameters
3. Relationships between Parameters
4. Two-port Network Analysis
5. Interconnection of Networks
- 6. T & Π Networks**
7. Equivalent Two-port Networks of Magnetically Coupled Circuits
8. Input Impedance
9. Transfer Function



T & Π Networks (1)

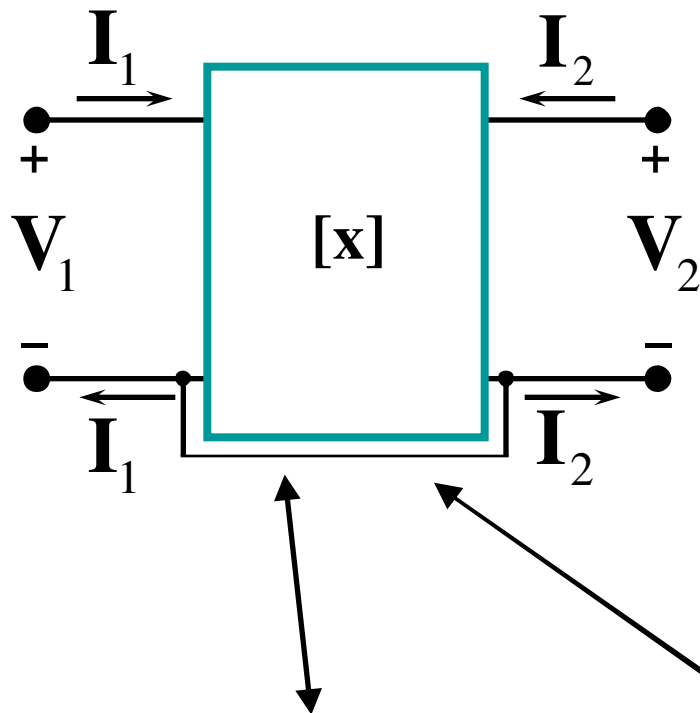

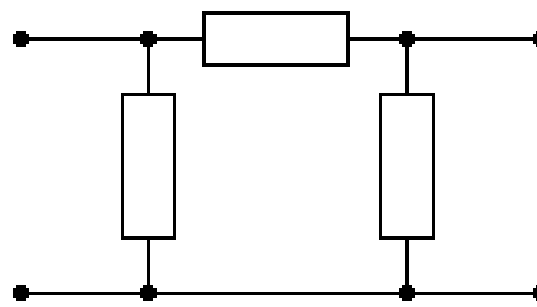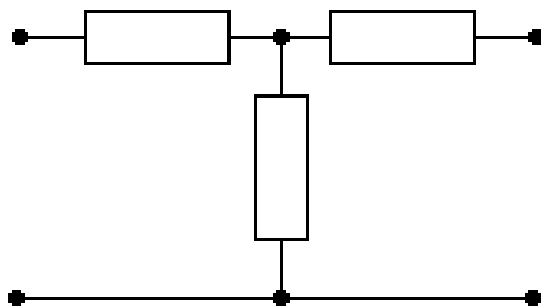1. Find the $[x']$ of the T (or Π) network,
2. Let $[x] = [x'] (\alpha)$,
3. Solve for (α) to find impedances of the T (or Π) network.





T & Π Networks (2)

$$\left. \begin{aligned} [\mathbf{z}'] &= \begin{bmatrix} \mathbf{Z}_A + \mathbf{Z}_B & \mathbf{Z}_B \\ \mathbf{Z}_B & \mathbf{Z}_B + \mathbf{Z}_C \end{bmatrix} \\ [\mathbf{z}] &= \begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} \\ [\mathbf{z}] &= [\mathbf{z}'] \end{aligned} \right\}$$

$$\rightarrow \begin{cases} \mathbf{Z}_A + \mathbf{Z}_B = \mathbf{z}_{11} \\ \mathbf{Z}_B = \mathbf{z}_{12} \\ \mathbf{Z}_B = \mathbf{z}_{21} \\ \mathbf{Z}_B + \mathbf{Z}_C = \mathbf{z}_{22} \end{cases}$$
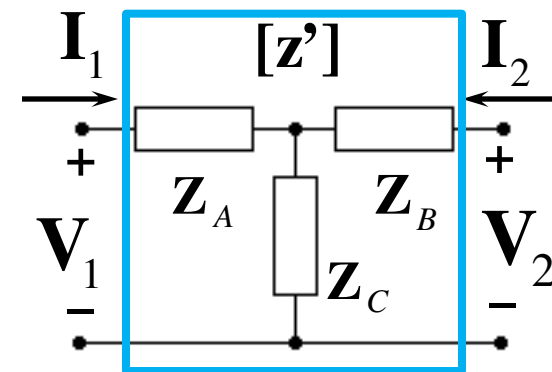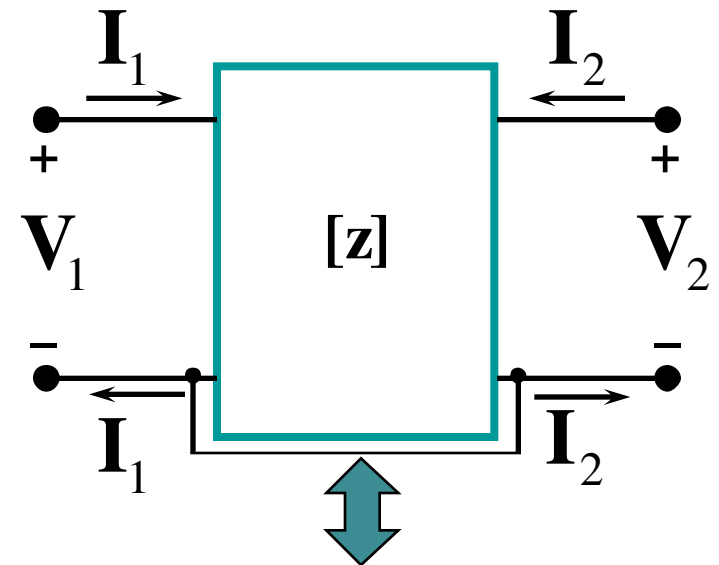
$$\rightarrow \begin{cases} \mathbf{Z}_A = \mathbf{z}_{11} - \mathbf{z}_{12} \\ \mathbf{Z}_B = \mathbf{z}_{12} \\ \mathbf{Z}_C = \mathbf{z}_{22} - \mathbf{z}_{12} \end{cases}$$




T & Π Networks (3)

$$[z'] = \begin{bmatrix} \frac{Z_A(Z_B + Z_C)}{Z_A + Z_B + Z_C} & \frac{Z_A Z_C}{Z_A + Z_B + Z_C} \\ \frac{Z_A Z_C}{Z_A + Z_B + Z_C} & \frac{Z_C(Z_A + Z_B)}{Z_A + Z_B + Z_C} \end{bmatrix}$$

$[z] = [z']$

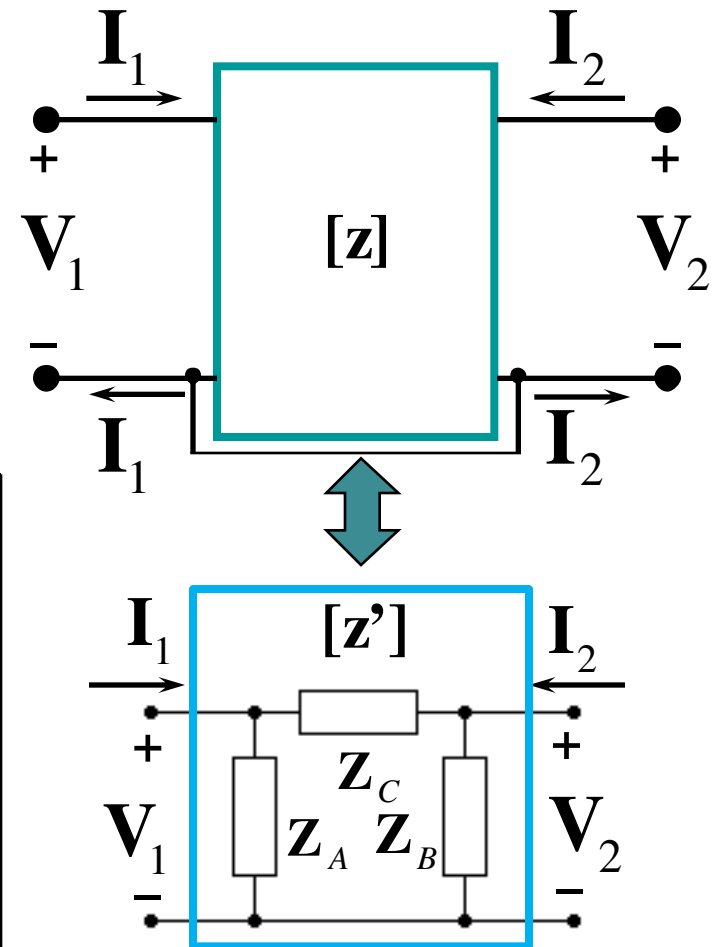
$$\rightarrow \begin{cases} Z_A = \frac{z_{11}z_{22} - z_{12}^2}{z_{22} - z_{12}} \\ Z_B = \frac{z_{11}z_{22} - z_{12}^2}{z_{12}} \\ Z_C = \frac{z_{11}z_{22} - z_{12}^2}{z_{11} - z_{12}} \end{cases}$$



T & Π Networks (4)

$$[\mathbf{T}'] = \begin{bmatrix} 1 + \frac{\mathbf{Z}_A}{\mathbf{Z}_B} & -\left(\mathbf{Z}_A + \mathbf{Z}_C + \frac{\mathbf{Z}_A \mathbf{Z}_C}{\mathbf{Z}_B}\right) \\ \frac{1}{\mathbf{Z}_B} & -\left(1 + \frac{\mathbf{Z}_C}{\mathbf{Z}_B}\right) \end{bmatrix}$$

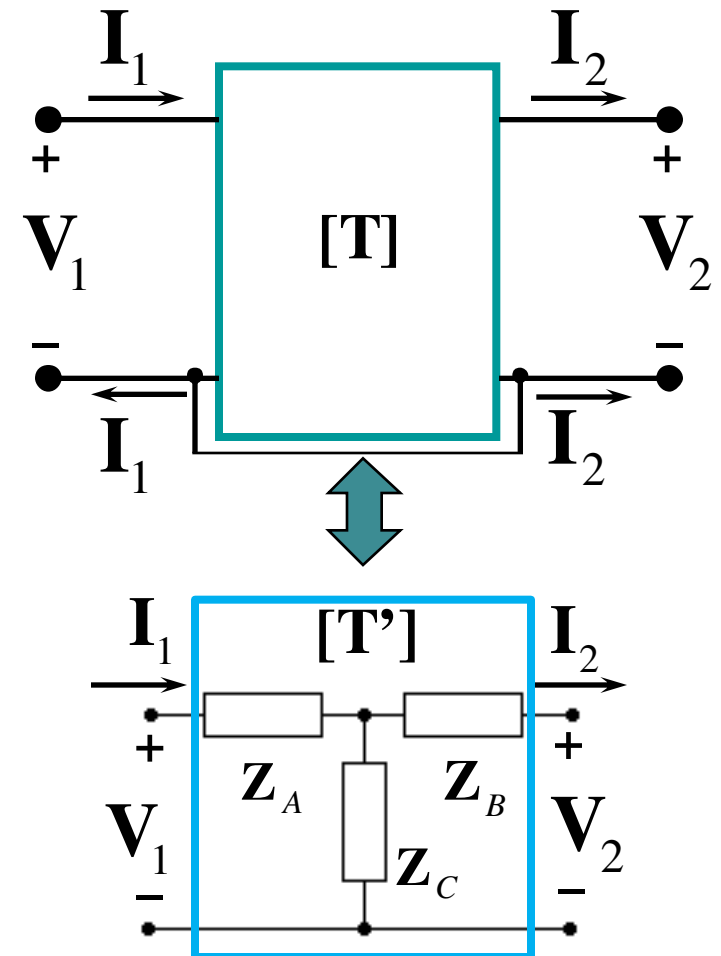
$$\begin{aligned} \mathbf{Z}_A &= \frac{\mathbf{A} - 1}{\mathbf{C}} \\ \mathbf{Z}_B &= \frac{1}{\mathbf{C}} \\ \mathbf{Z}_C &= \frac{-\mathbf{D} - 1}{\mathbf{C}} \end{aligned}$$



T & Π Networks (5)

$$[T'] = \begin{bmatrix} 1 + \frac{Z_B}{Z_C} & -Z_B \\ \frac{Z_A + Z_B + Z_C}{Z_A Z_C} & -\left(1 + \frac{Z_B}{Z_A}\right) \end{bmatrix}$$

$$\begin{aligned} Z_A &= -\frac{B}{D+1} \\ Z_B &= -B \\ Z_C &= \frac{-B}{A-1} \end{aligned}$$

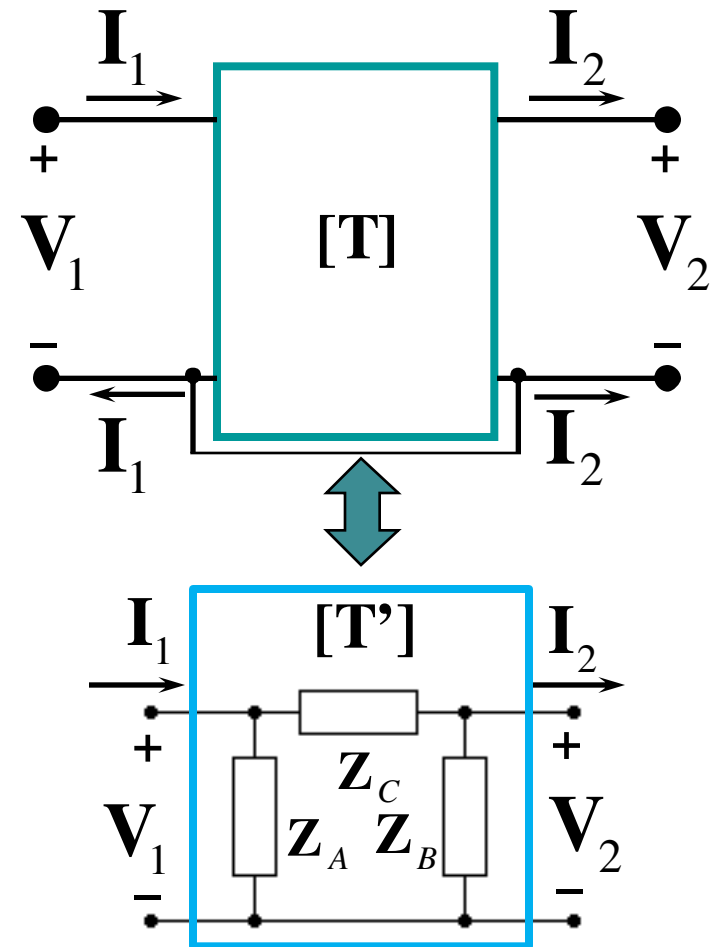


Ex. 1

T & Π Networks (6)

$$\mathbf{E} = 220 \text{ V}; \mathbf{Z}_L = j50 \Omega; \mathbf{Z} = \begin{bmatrix} 10 & j20 \\ j20 & 40 \end{bmatrix} \Omega.$$


$$\begin{cases} \mathbf{Z}_A = \mathbf{z}_{11} - \mathbf{z}_{12} = 10 - j20 \Omega \\ \mathbf{Z}_B = \mathbf{z}_{12} = j20 \Omega \\ \mathbf{Z}_C = \mathbf{z}_{22} - \mathbf{z}_{12} = 40 - j20 \Omega \end{cases}$$

Method 2

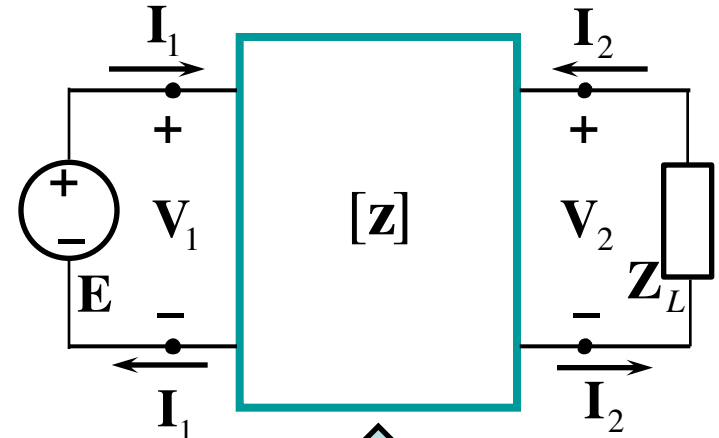

$$\mathbf{I}_1 = \frac{\mathbf{E}}{\mathbf{Z}_A + \mathbf{Z}_B // (\mathbf{Z}_C + \mathbf{Z}_L)} = \frac{220}{(10 - j20) + \frac{j20(40 - j20 + j50)}{j20 + 40 - j20 + j50}} = \boxed{14.09 + j4.94 \text{ A}}$$

$$\mathbf{I}_2 = \frac{-\mathbf{I}_1 \mathbf{Z}_B}{\mathbf{Z}_B + \mathbf{Z}_C + \mathbf{Z}_L} = \frac{-(14.09 + j4.94) j20}{j20 + 40 - j20 + j50} = \boxed{-2.47 - j3.96 \text{ A}}$$

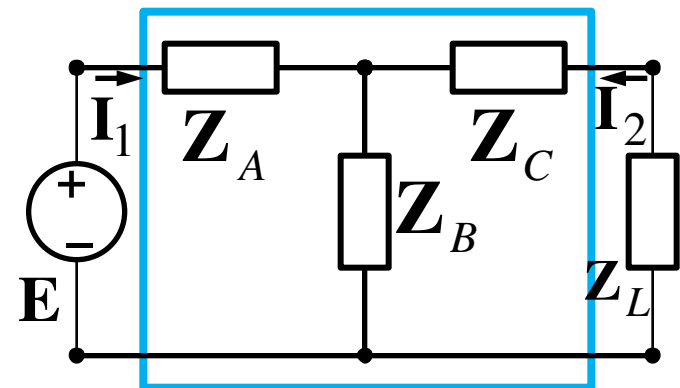

Ex. 1

T & Π Networks (7)



$$\mathbf{E} = 220 \text{ V}; \mathbf{Z}_L = j50 \Omega; \mathbf{Z} = \begin{bmatrix} 10 & j20 \\ j20 & 40 \end{bmatrix} \Omega.$$

$$\mathbf{Z}_A = \frac{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}^2}{\mathbf{z}_{22} - \mathbf{z}_{12}} = 16 + j8 \Omega$$

$$\mathbf{Z}_B = \frac{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}^2}{\mathbf{z}_{12}} = -j40 \Omega$$

$$\mathbf{Z}_C = \frac{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}^2}{\mathbf{z}_{11} - \mathbf{z}_{12}} = 16 + j32 \Omega$$

Method 3

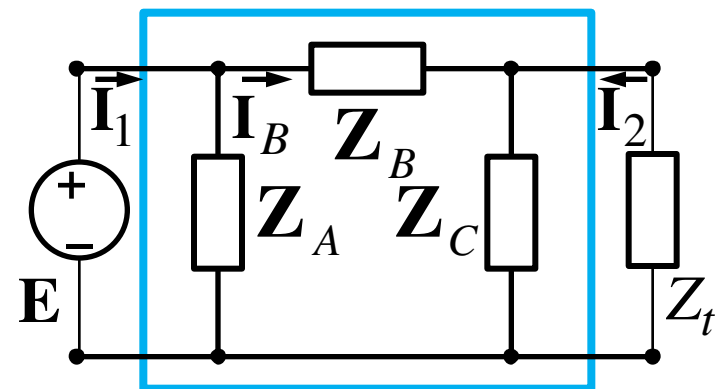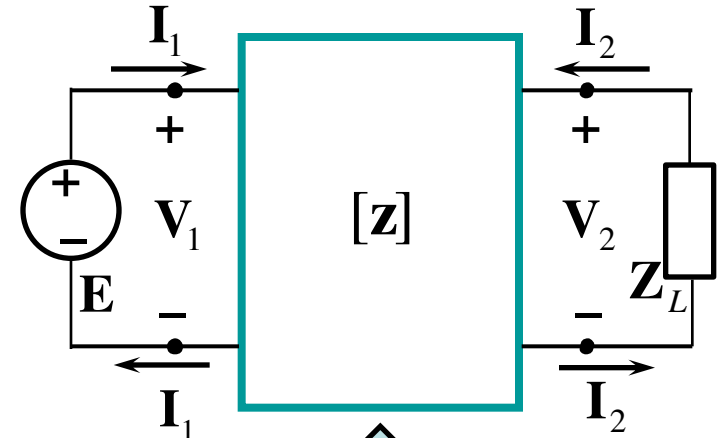

$$\mathbf{I}_1 = \frac{\mathbf{E}}{\mathbf{Z}_A // [\mathbf{Z}_B + (\mathbf{Z}_C // \mathbf{Z}_L)]} = 14.09 + j4.94 \text{ A}$$

$$\mathbf{I}_B = \frac{\mathbf{E}}{\mathbf{Z}_B + (\mathbf{Z}_C // \mathbf{Z}_L)} = 3.09 + j10.44 \text{ A}$$

$$\mathbf{I}_2 = \frac{-\mathbf{I}_B \mathbf{Z}_C}{\mathbf{Z}_C + \mathbf{Z}_L} = -2.47 - j3.96 \text{ A}$$

Ex. 2

T & Π Networks (8)



$$\begin{aligned} E &= 220 \text{ V}; \\ Z_1 &= 20 \Omega; \quad Z_L = j50 \Omega; \quad T = \begin{bmatrix} 3 & -200 \\ 0.04 & -3 \end{bmatrix}. \end{aligned}$$

Method 2

$$\begin{cases} Z_A = \frac{A-1}{C} = \frac{3-1}{0.04} = 50 \Omega \\ Z_B = \frac{1}{C} = \frac{1}{0.04} = 25 \Omega \\ Z_C = \frac{-D-1}{C} = \frac{3-1}{0.04} = 50 \Omega \end{cases}$$

$$I_1 = \frac{E}{Z_1 + Z_A + Z_B \parallel (Z_C + Z_L)} = \boxed{2.46 - j0.11 \text{ A}}$$

$$I_2 = \frac{I_1 Z_B}{Z_B + Z_C + Z_L} = \boxed{0.55 - j0.40 \text{ A}}$$

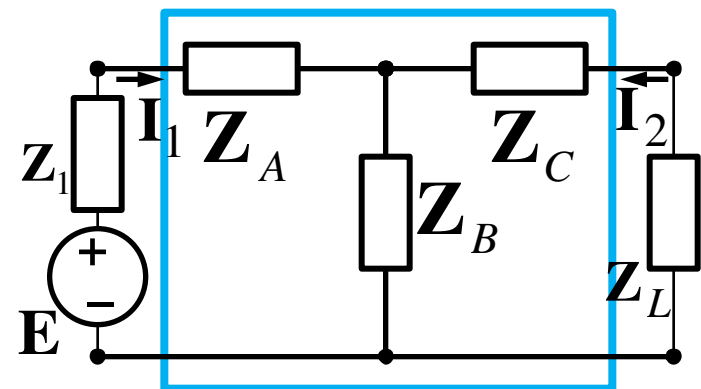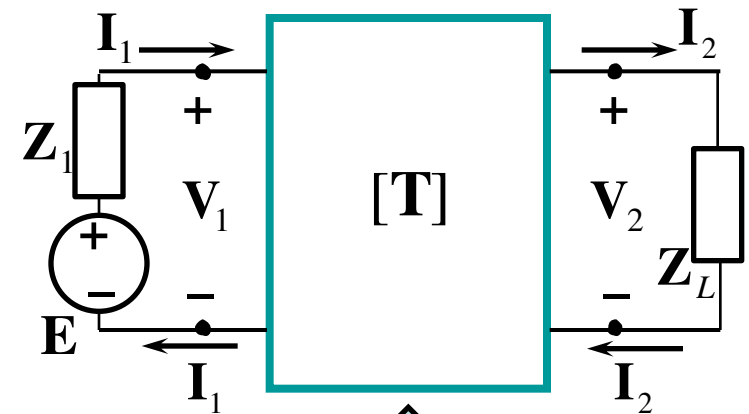

Ex. 3

T & Π Networks (9)



$$E = 200\text{ V}; Z_n = 5\ \Omega; Y = \begin{bmatrix} 0.0455 & -0.0182 \\ -0.0182 & 0.0273 \end{bmatrix} \text{ S.}$$

$$Z_f = j10\ \Omega; Z_L = -j20\ \Omega;$$

Method 5

$$[y] = [z]^{-1} = \begin{bmatrix} 0.0455 & -0.0182 \\ -0.0182 & 0.0273 \end{bmatrix}^{-1} = \begin{bmatrix} 30 & 20 \\ 20 & 50 \end{bmatrix} \Omega$$

$$\begin{cases} Z_A = \frac{z_{11}z_{22} - z_{12}^2}{z_{22} - z_{12}} = 36.67\ \Omega \\ Z_B = \frac{z_{11}z_{22} - z_{12}^2}{z_{12}} = 55.00\ \Omega \\ Z_C = \frac{z_{11}z_{22} - z_{12}^2}{z_{11} - z_{12}} = 110.00\ \Omega \end{cases}$$

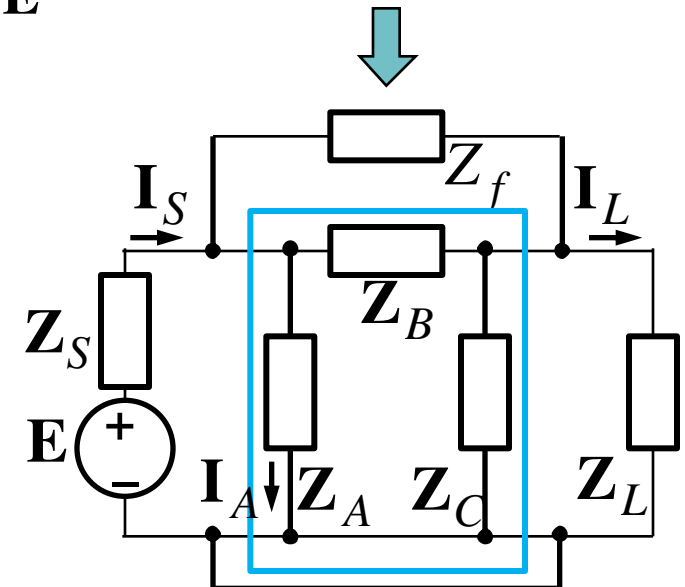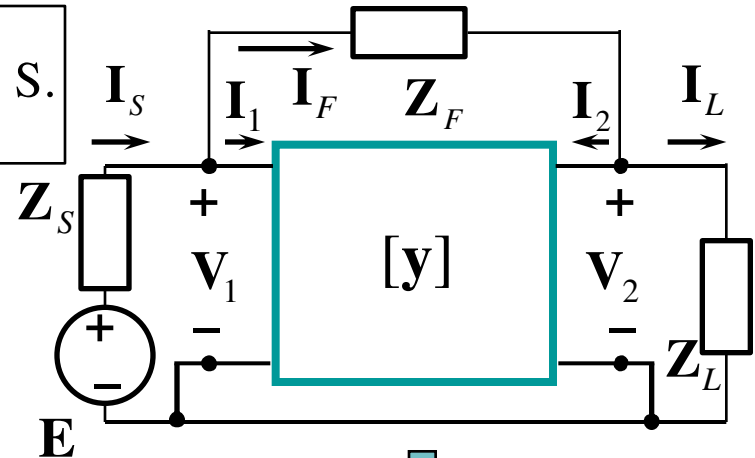

Ex. 3

T & Π Networks (10)

$$E = 200 \text{ V}; Z_n = 5 \Omega; Y = \begin{bmatrix} 0.0455 & -0.0182 \\ -0.0182 & 0.0273 \end{bmatrix} \text{ S.}$$

$$Z_f = j10 \Omega; Z_L = -j20 \Omega;$$

Method 5



$$Z_A = 36.67 \Omega; Z_B = 55.00 \Omega; Z_C = 110.00 \Omega$$

$$I_n = \frac{E}{Z_S + \{Z_A // [(Z_f // Z_B) + (Z_L // Z_C)]\}}$$

$$= \boxed{12.80 + j8.00 \text{ A}}$$

$$I_A = \frac{E - Z_S I_S}{Z_A} = 3.71 - j1.09 \text{ A}$$

$$I_L = \frac{(I_S - I_A)Z_C}{Z_C + Z_L} = \boxed{7.20 + j10.40 \text{ A}}$$

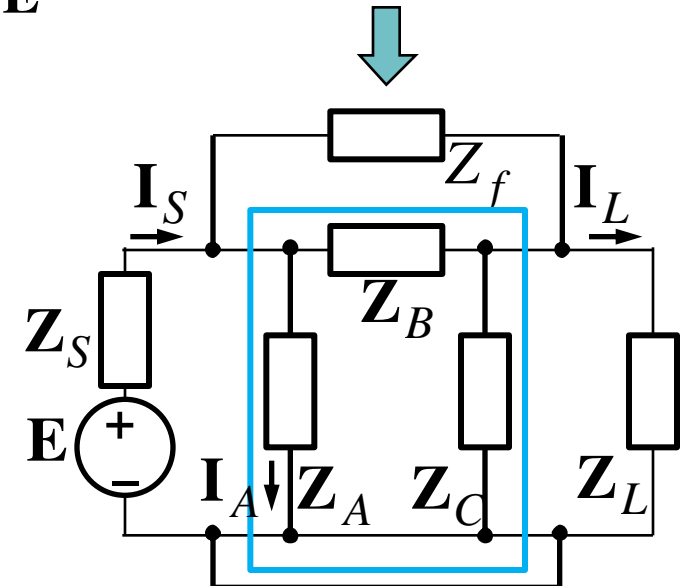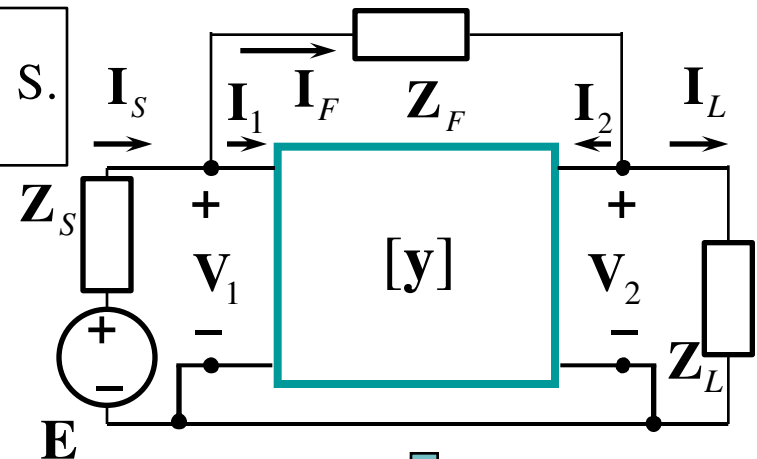

Ex. 4

T & Π Networks (11)

Find $i_1(t)$? **Method 1**



$$v_C(0) = 12 \text{ V}$$

$$\begin{cases} v_1(0) = 30i_1(0) + 20i_2(0) \\ v_2(0) = 20i_1(0) + 50i_2(0) \\ v_1(0) = 12 \\ v_2(0) = -10i_2(0) \end{cases}$$

$$\rightarrow i_1(0) = 0.5143 \text{ A} = i_L(0)$$

$$\begin{cases} V_1(s) = 30I_1(s) + 20I_2(s) \\ V_2(s) = 20I_1(s) + 50I_2(s) \\ \left(2s + \frac{200}{s}\right)I_1(s) + V_1(s) = 1.03 + \frac{12}{s} \\ V_2(s) = -10I_2(s) \end{cases}$$

$$\rightarrow I_1(s) = \frac{0.515s + 6}{s^2 + 11.667s + 100} \text{ A} \quad \rightarrow \boxed{i_1(t) = 0.6334e^{-5.83t} \cos(8.12t - 35.6^\circ) \text{ A}}$$

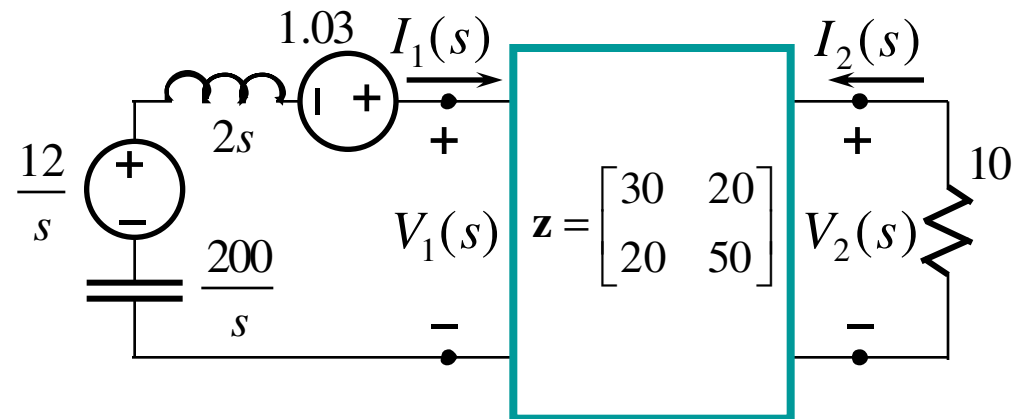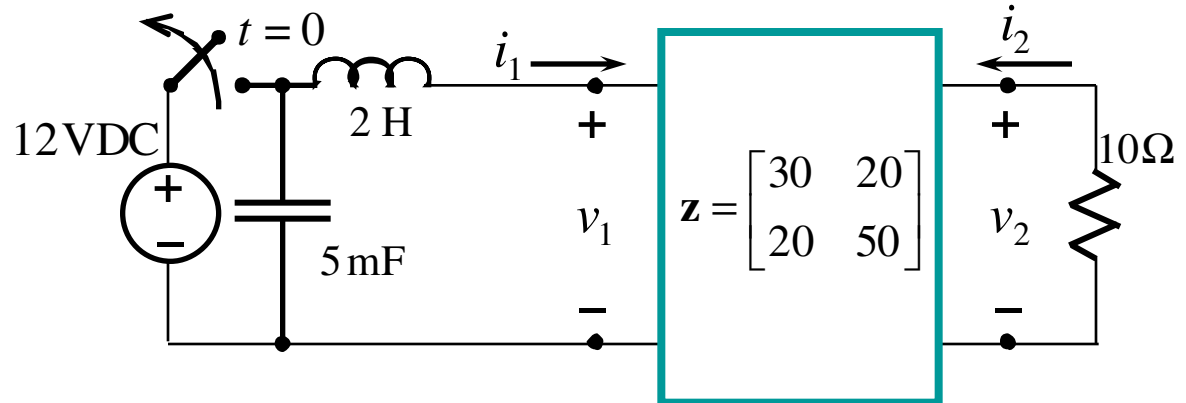

Ex. 4

T & Π Networks (12)

Find $i_1(t)$? **Method 2**

$$v_C(0) = 12 \text{ V}$$




$$R_{eq} = 10 + \frac{(30 + 10)20}{30 + 10 + 20} = 23.33 \Omega$$

$$i_1(0) = \frac{12}{23.33} = 0.5143 \text{ A} = i_L(0)$$

$$I_1(s) = \frac{1.03 + \frac{12}{s}}{\frac{200}{s} + 2s + 23.33}$$

$$= \frac{0.515s + 6}{s^2 + 11.667s + 100} \text{ A}$$
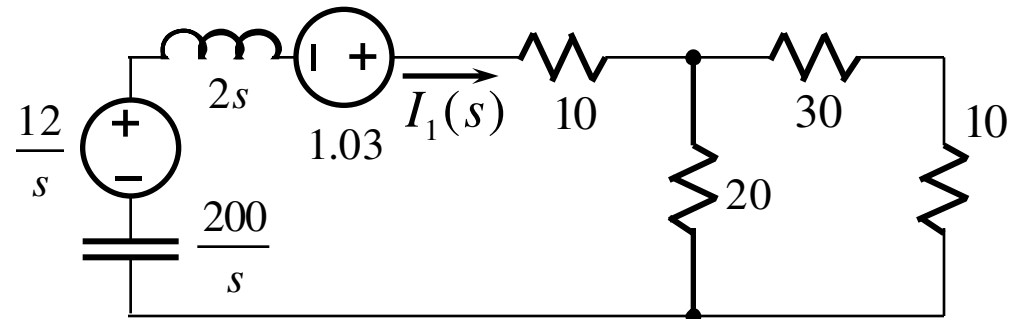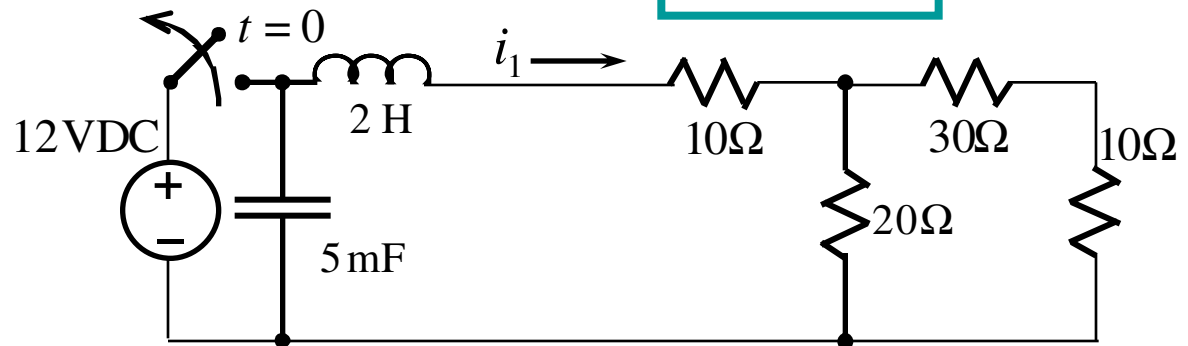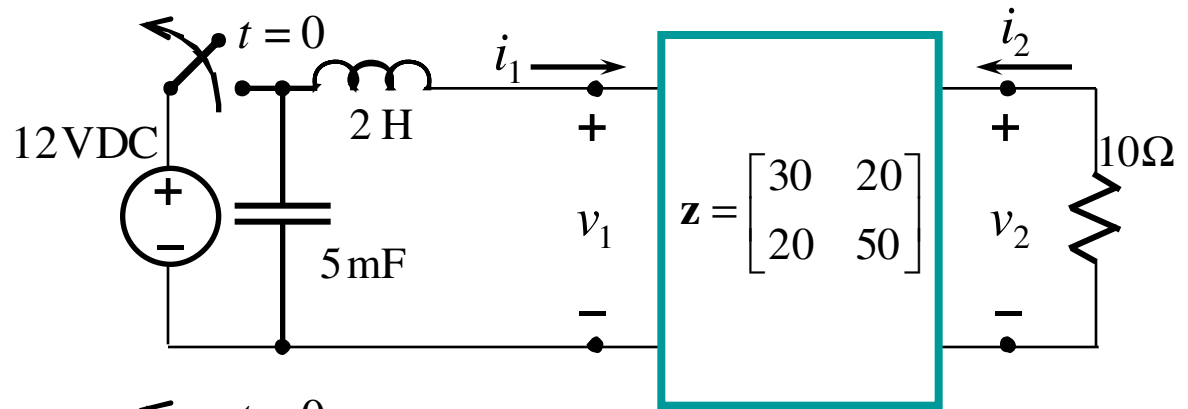
$$\rightarrow i_1(t) = 0.6334e^{-5.83t} \cos(8.12t - 35.6^\circ) \text{ A}$$




Two-port Networks

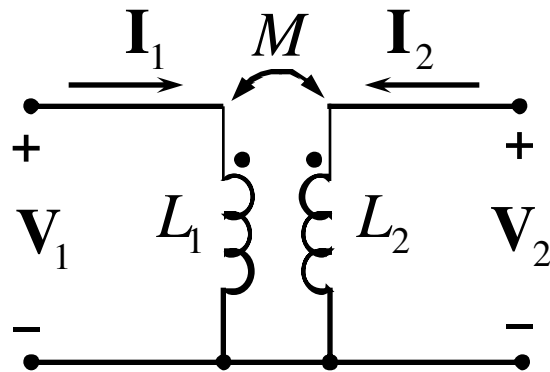
1. Introduction
2. Parameters
3. Relationships between Parameters
4. Two-port Network Analysis
5. Interconnection of Networks
6. T & Π Networks
- 7. Equivalent Two-port Networks of Magnetically Coupled Circuits**
8. Input Impedance
9. Transfer Function



Equivalent Two-port Networks of Magnetically Coupled Circuits (1)




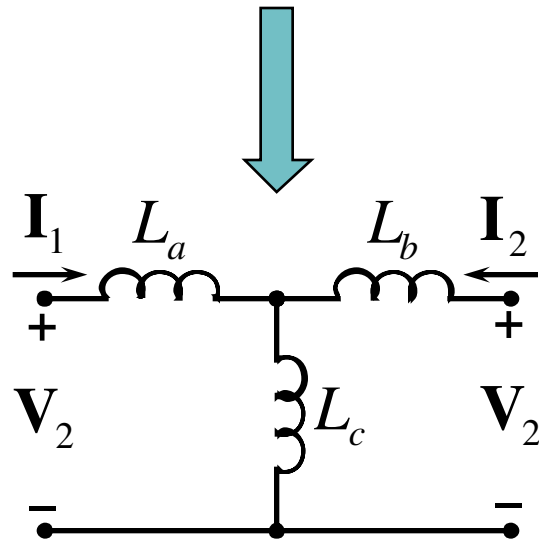
$$\rightarrow \begin{cases} \mathbf{V}_1 = j\omega L_1 \mathbf{I}_1 + j\omega M \mathbf{I}_2 \\ \mathbf{V}_2 = j\omega M \mathbf{I}_1 + j\omega L_2 \mathbf{I}_2 \end{cases}$$



$$\rightarrow \begin{cases} \mathbf{V}_1 = j\omega L_a \mathbf{I}_1 + j\omega L_c (\mathbf{I}_1 + \mathbf{I}_2) \\ \quad = j\omega (L_a + L_c) \mathbf{I}_1 + j\omega L_c \mathbf{I}_2 \\ \mathbf{V}_2 = j\omega L_c (\mathbf{I}_1 + \mathbf{I}_2) + j\omega L_b \mathbf{I}_2 \\ \quad = j\omega L_c \mathbf{I}_1 + j\omega (L_c + L_b) \mathbf{I}_2 \end{cases}$$

$$\rightarrow \begin{cases} L_a = L_1 - M \\ L_b = L_2 - M \\ L_c = M \end{cases}$$

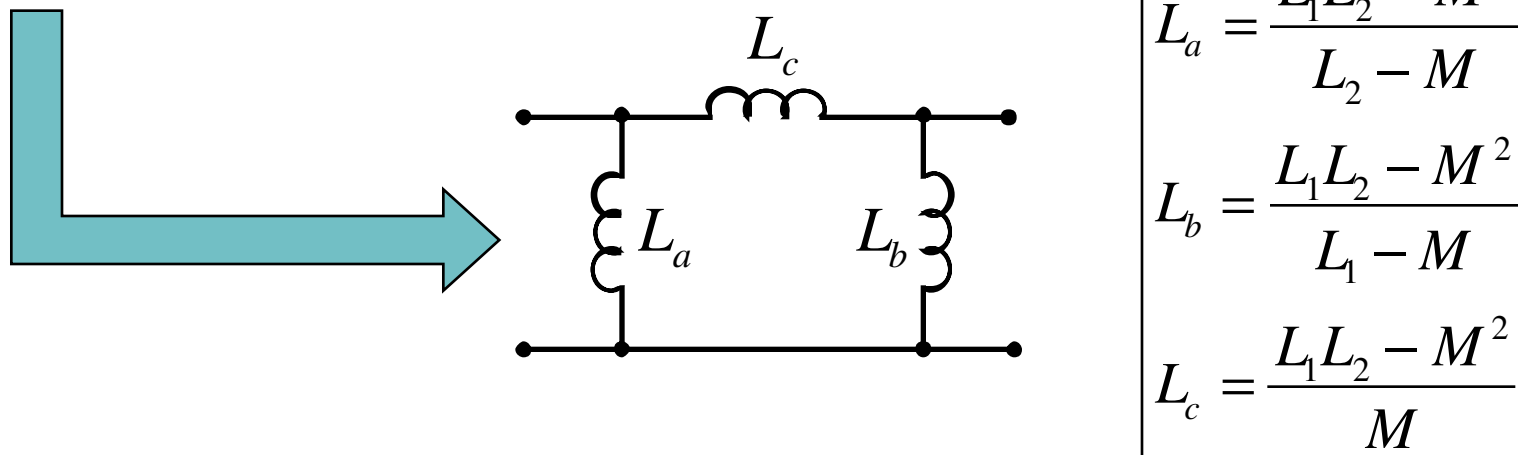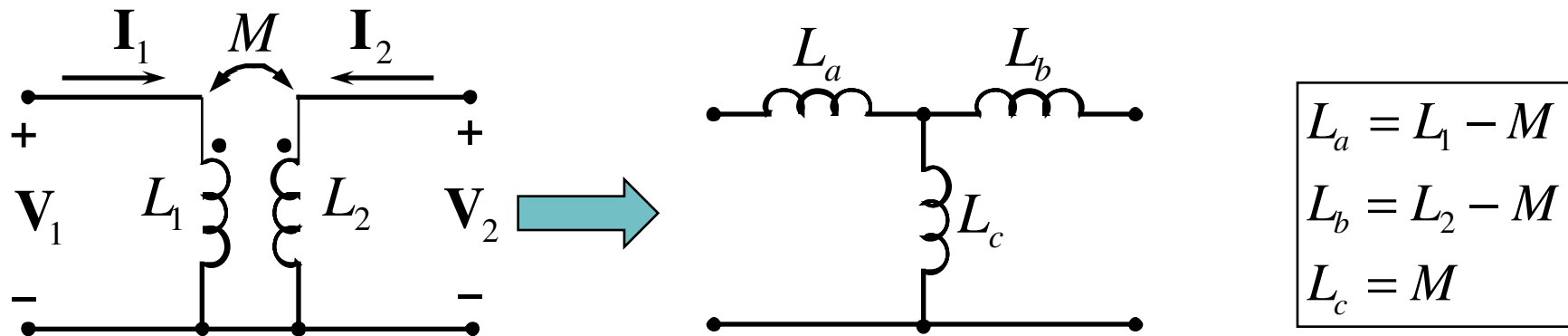Equivalent Two-port Networks of Magnetically Coupled Circuits (2)



Ex. 1 Equivalent Two-port Networks of Magnetically Coupled Circuits (3)


$\mathbf{Z}_{ab} = ?$ **Method 3**

$$\mathbf{Z}_A = j20 - j5 = j15\Omega$$

$$\mathbf{Z}_C = j50 - j5 = j45\Omega$$

$$\mathbf{Z}_B = j5\Omega$$
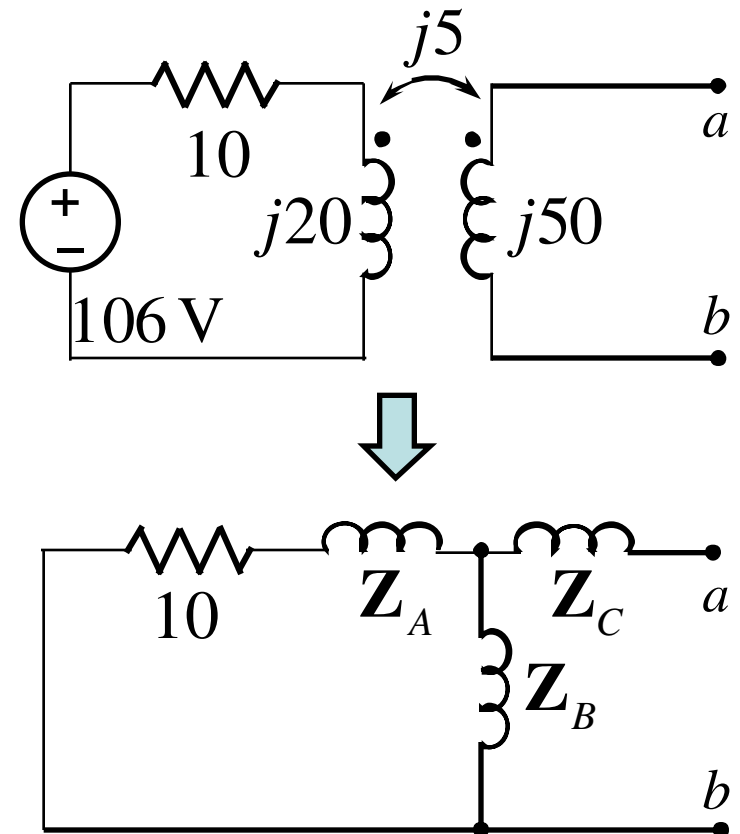
$$\begin{aligned}\mathbf{Z}_{ab} &= \frac{\mathbf{Z}_B (10 + \mathbf{Z}_A)}{\mathbf{Z}_B + 10 + \mathbf{Z}_A} + \mathbf{Z}_C \\ &= \boxed{0.50 + j49\Omega}\end{aligned}$$



Ex. 1 Equivalent Two-port Networks of Magnetically Coupled Circuits (4)


$Z_{ab} = ?$ Method 4

$$Z_A = \frac{j20 \times j50 - (j5)^2}{j50 - j5} = j21.67 \, \Omega$$

$$Z_B = \frac{j20 \times j50 - (j5)^2}{j5} = j195 \, \Omega$$

$$Z_C = \frac{j20 \times j50 - (j5)^2}{j20 - j5} = j65 \, \Omega$$

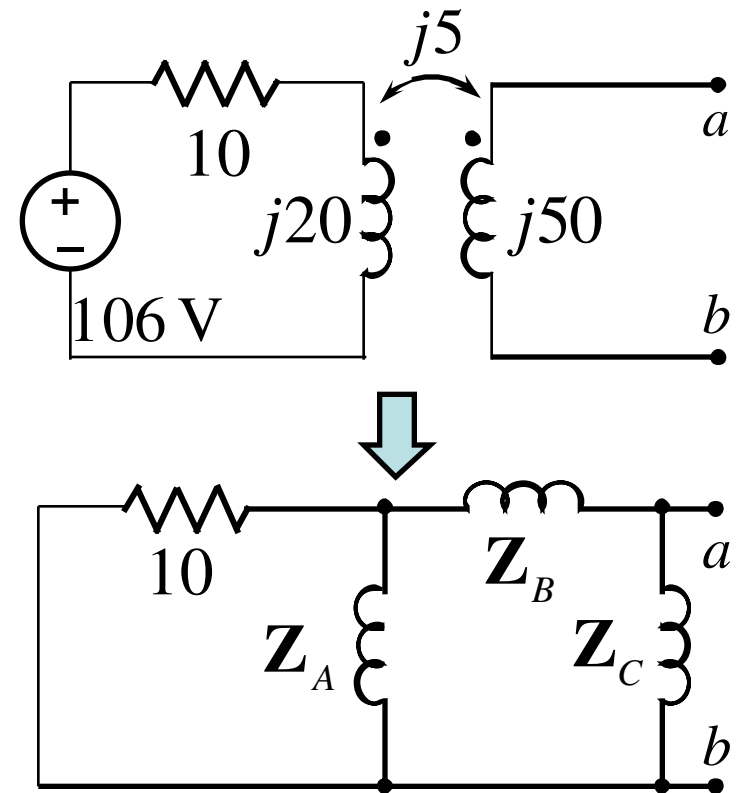
$$Z_{ab} = \frac{\left(\frac{10Z_A}{10 + Z_A} + Z_B \right) Z_C}{\frac{10Z_A}{10 + Z_A} + Z_B + Z_C} = \boxed{0.50 + j49 \, \Omega}$$



Ex. 2 Equivalent Two-port Networks of Magnetically Coupled Circuits (5)

$$\begin{aligned} E_1 &= 100 \angle 30^\circ \text{ V}; R_1 = 60 \Omega; R_2 = 40 \Omega; \\ Z_L &= 80 + j10 \Omega; Z_{L1} = j20 \Omega; Z_{L2} = j40 \Omega; \\ Z_M &= j5 \Omega. \text{ Find } I_1? \end{aligned}$$

Method 2

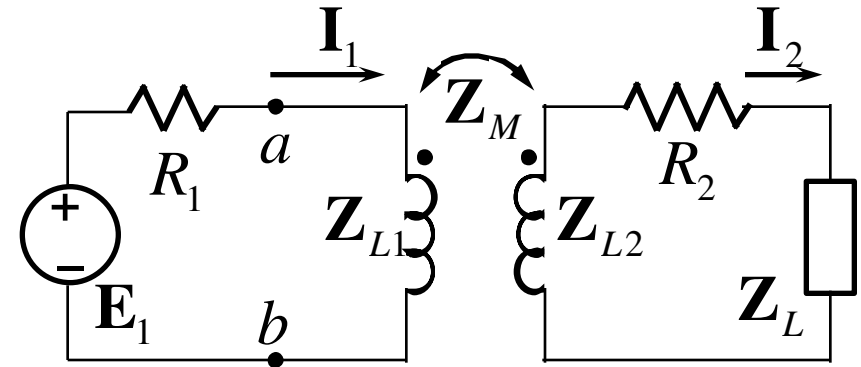


$$Z_A = j20 - j5 = j15 \Omega$$

$$Z_B = j5 \Omega$$


$$Z_C = j40 - j5 = j35 \Omega$$
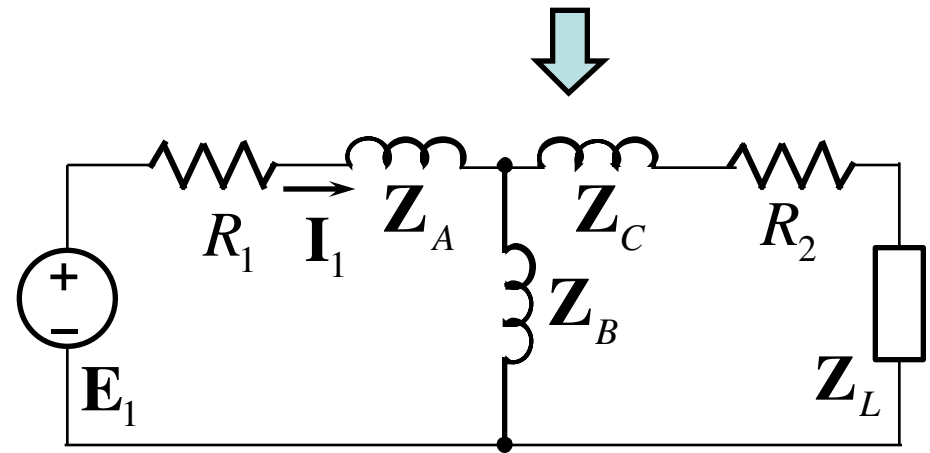
$$\begin{aligned} I_1 &= \frac{E_1}{R_1 + Z_A + \frac{Z_B(Z_C + R_2 + Z_L)}{Z_B + Z_C + R_2 + Z_L}} \\ &= \boxed{1.54 + j0.32 \text{ A}} \end{aligned}$$




Ex. 3 Equivalent Two-port Networks of Magnetically Coupled Circuits (6)
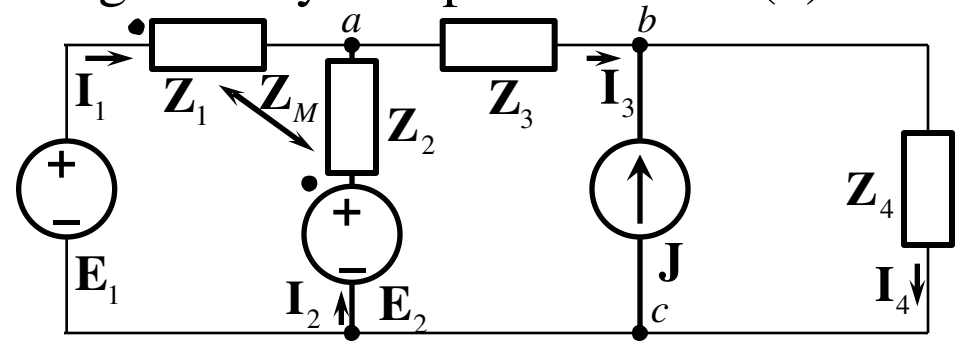
$$\begin{aligned} Z_1 &= 10 + j15\Omega; Z_2 = 20 + j10\Omega; Z_M = j2\Omega; \\ Z_3 &= -j20\Omega; Z_4 = 25\Omega; E_1 = 100\text{ V}; \\ E_2 &= 150\angle 30^\circ\text{ V}; J = 5\angle 45^\circ\text{ A}. \end{aligned}$$


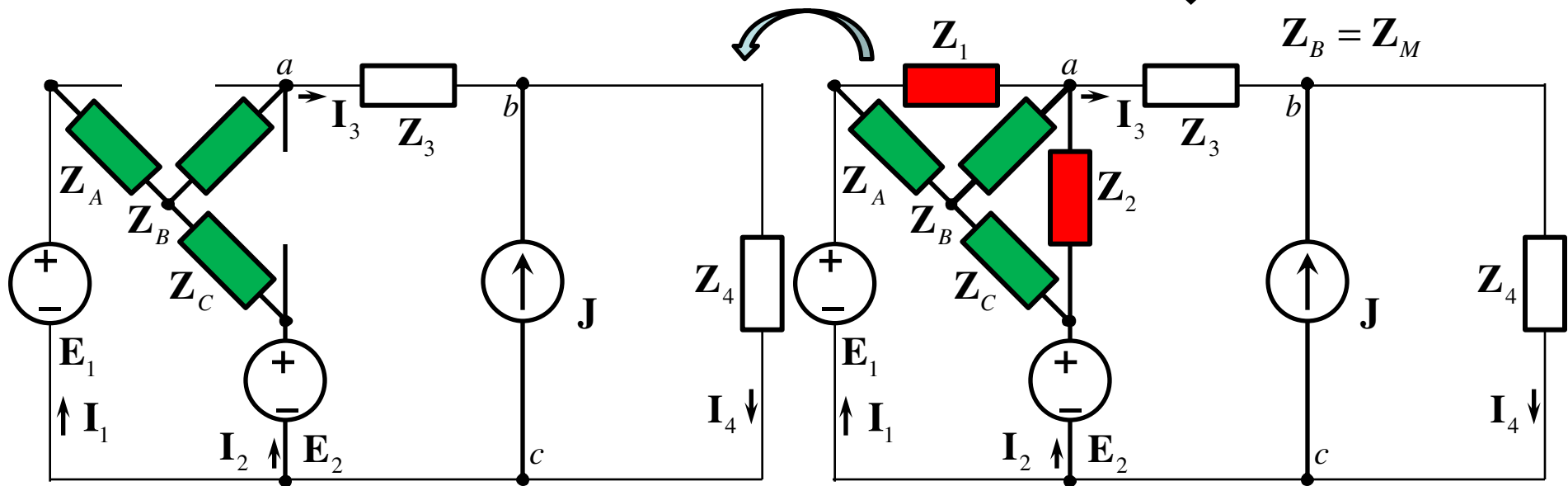
$$\begin{aligned} Z_A &= Z_1 - Z_M \\ Z_C &= Z_2 - Z_M \\ Z_B &= Z_M \end{aligned}$$




Ex. 3 Equivalent Two-port Networks of Magnetically Coupled Circuits (7)

$$\begin{aligned} Z_1 &= 10 + j15 \Omega; Z_2 = 20 + j10 \Omega; Z_M = j2 \Omega; \\ Z_3 &= -j20 \Omega; Z_4 = 25 \Omega; E_1 = 100 \text{ V}; \\ E_2 &= 150 \angle 30^\circ \text{ V}; J = 5 \angle 45^\circ \text{ A}. \end{aligned}$$


$$\begin{cases} \left(\frac{1}{Z_A} + \frac{1}{Z_C} + \frac{1}{Z_3 + Z_B} \right) V_d - \frac{1}{Z_3 + Z_B} V_b = \frac{E_1}{Z_A} + \frac{E_2}{Z_C} \\ -\frac{1}{Z_3 + Z_B} V_d + \left(\frac{1}{Z_3 + Z_B} + \frac{1}{Z_4} \right) V_b = J \end{cases}$$

$$\rightarrow \begin{cases} V_d = 88.11 + j40.06 \text{ V} \\ V_b = 111.12 + j56.43 \text{ V} \end{cases}$$
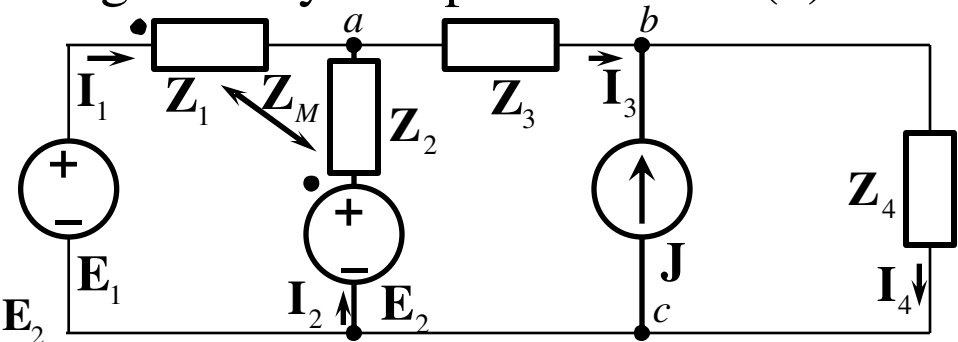
$$\rightarrow \begin{cases} I_1 = (E_1 - V_d) / Z_A = -1.49 - j2.06 \text{ A} \\ I_2 = (E_2 - V_d) / Z_C = 2.40 + j0.79 \text{ A} \\ I_3 = (V_d - V_b) / (Z_B + Z_3) = 0.91 - j1.28 \text{ A} \\ I_4 = V_b / Z_4 = 4.44 + j2.26 \text{ A} \end{cases}$$


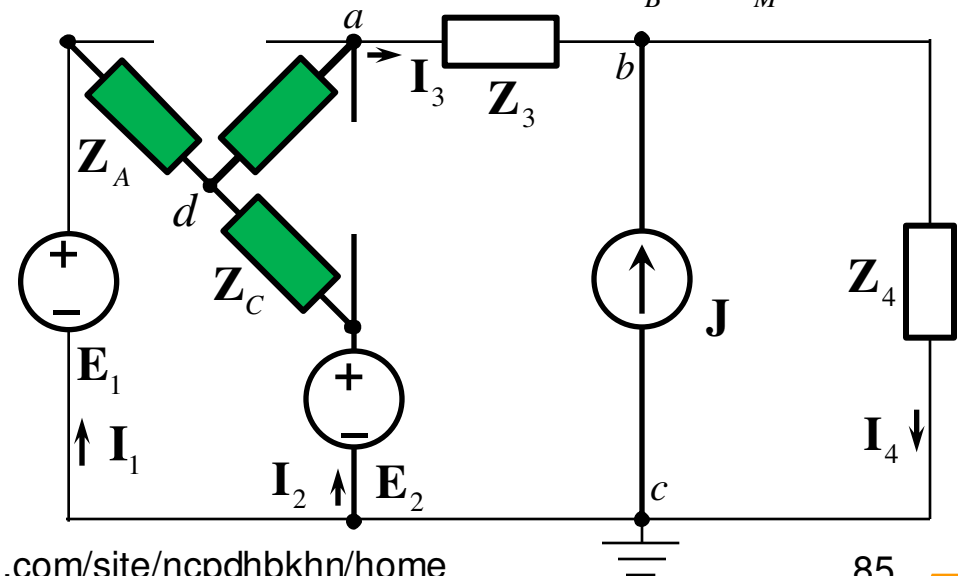
$$\begin{aligned} Z_A &= Z_1 - Z_M \\ Z_C &= Z_2 - Z_M \\ Z_B &= Z_M \end{aligned}$$



Ex. 4 Equivalent Two-port Networks of Magnetically Coupled Circuits (8)




Find the current $i_2(t)$? **Method 2**

$$i_1(0) = i_3(0) = \frac{60}{12} = 5\text{A}; i_2(0) = 0$$

$$V_b(s) = 0 \rightarrow V_a(s) = \frac{\frac{10}{2s+3} - \frac{10}{2s}}{\frac{1}{2s+3} + \frac{1}{2s} + \frac{1}{6s+12}}$$

$$I_2(s) = \frac{-V_a(s)}{6s+12} = \frac{15}{2(7s^2 + 18s + 9)} \text{ A}$$
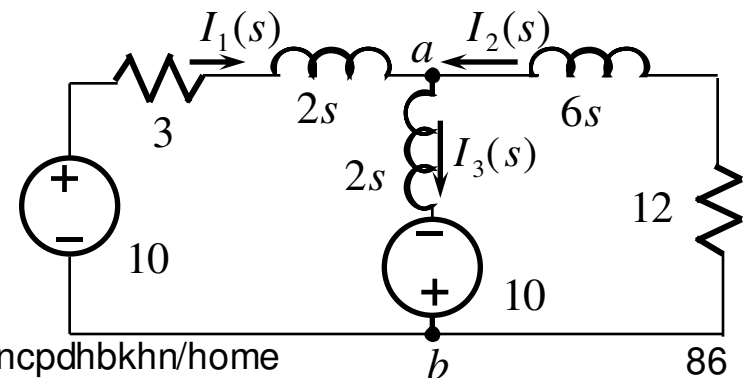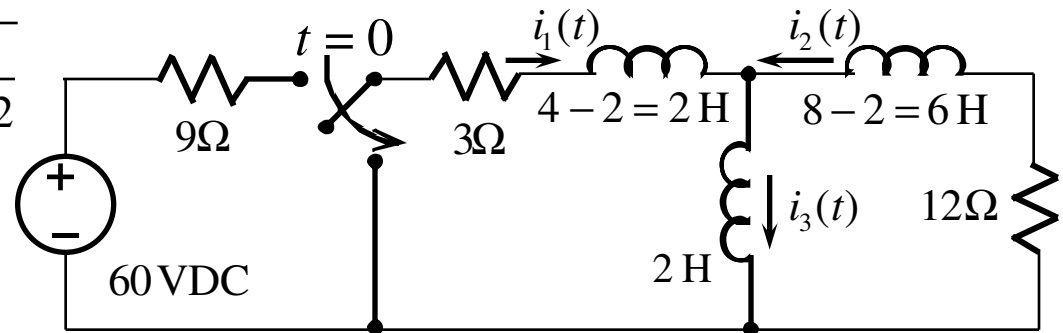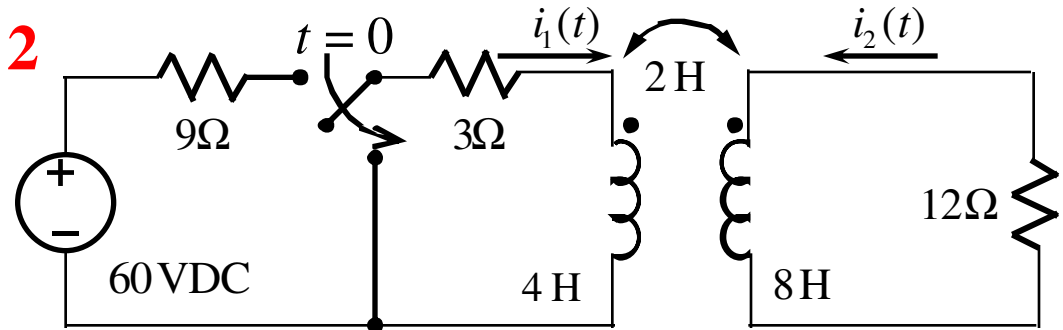
$$\rightarrow i_2(t) = 0.8838(e^{-0.6796t} - e^{-1.8918t}) \text{ A}$$





Two-port Networks

1. Introduction
2. Parameters
3. Relationships between Parameters
4. Two-port Network Analysis
5. Interconnection of Networks
6. T & Π Networks
7. Equivalent Two-port Networks of Magnetically Coupled Circuits
- 8. Input Impedance**
9. Transfer Function







Input Impedance (1)

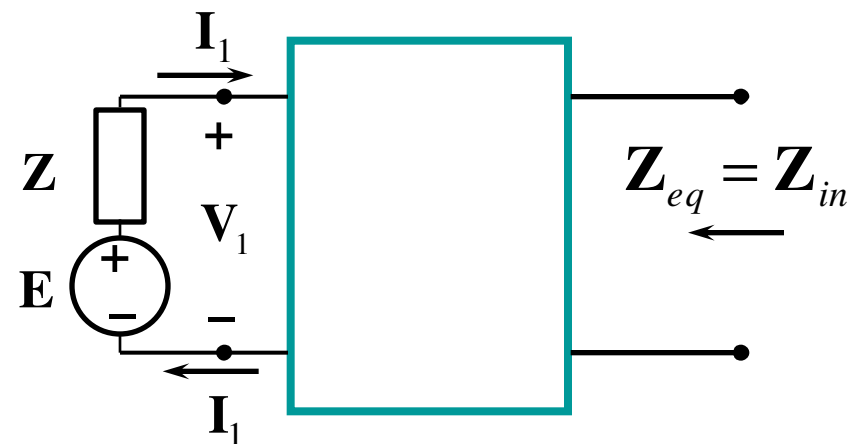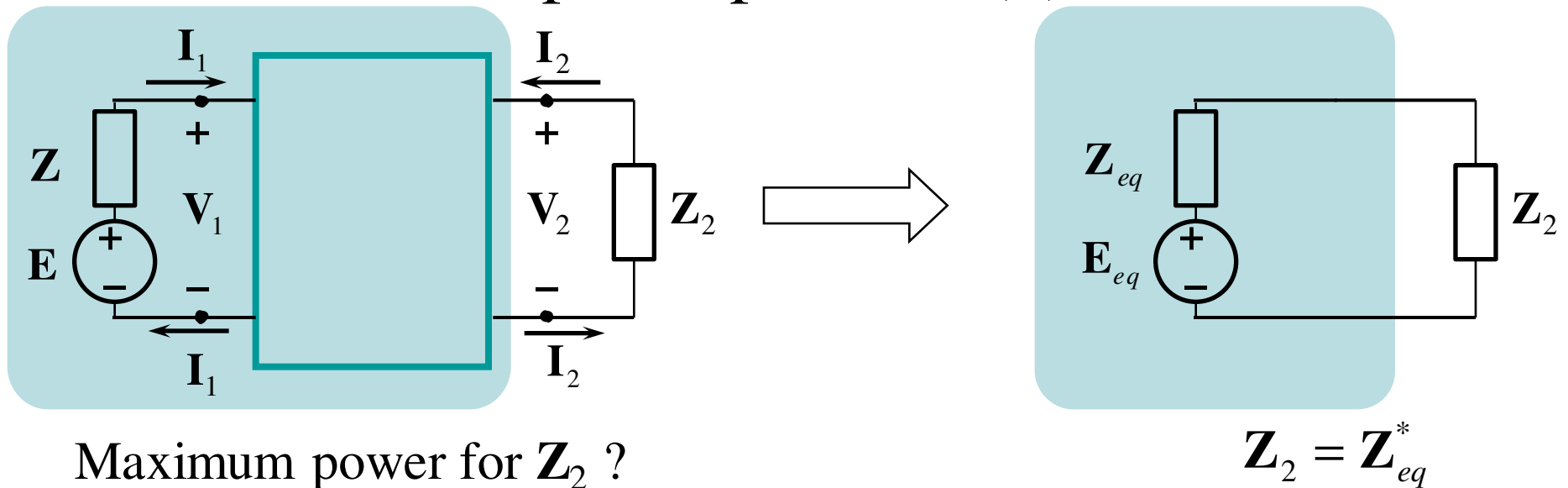





Input Impedance (2)

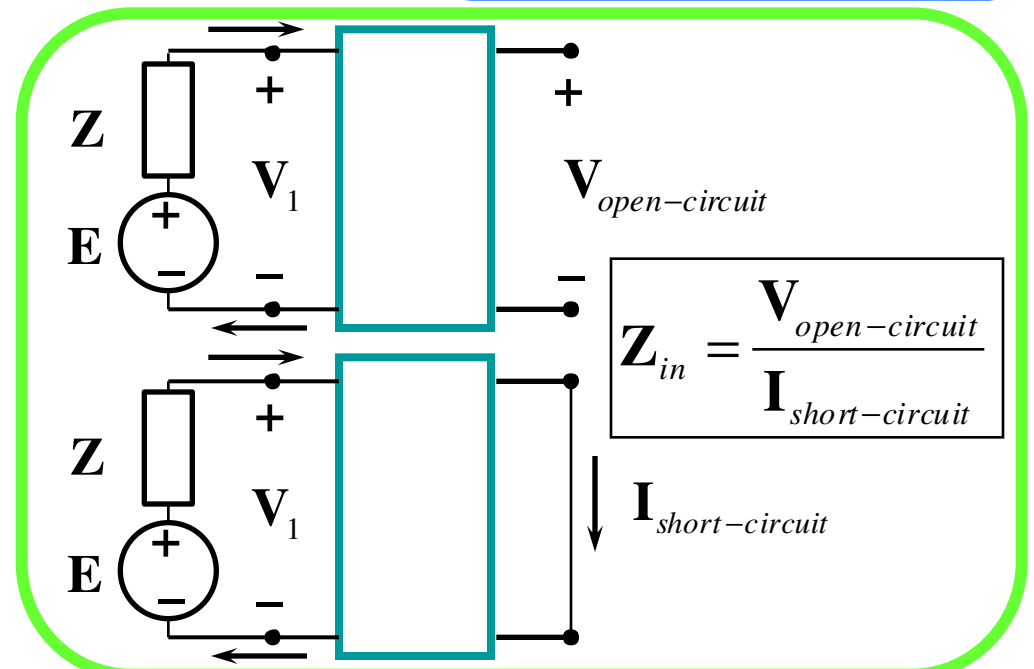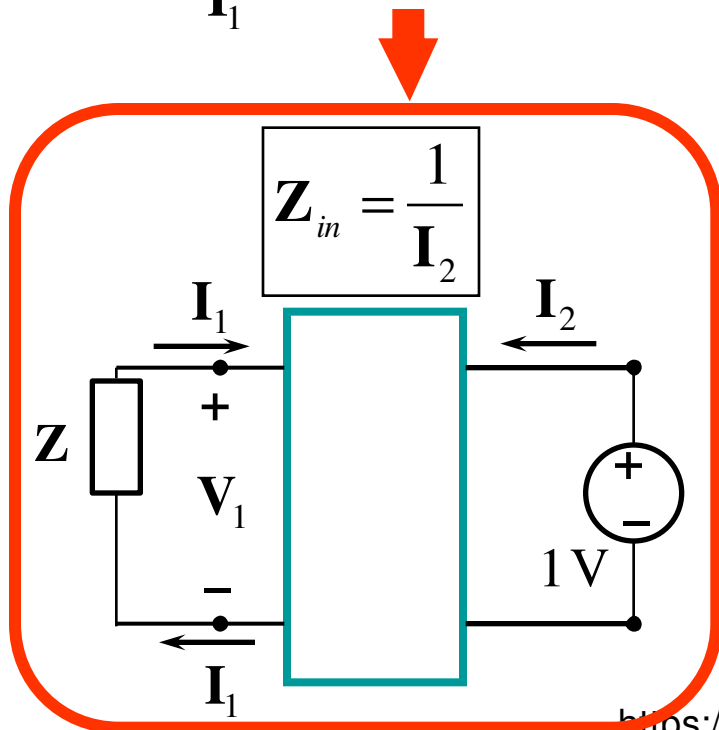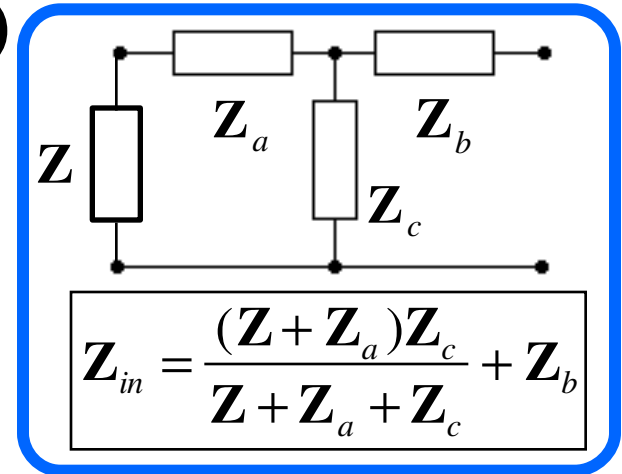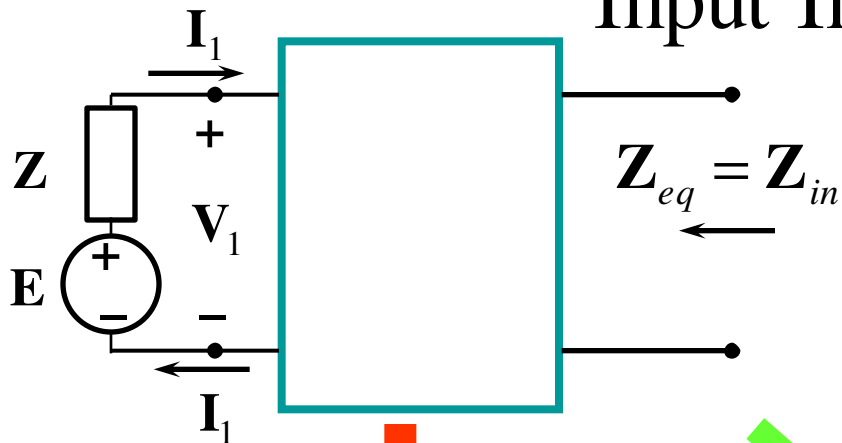

Input Impedance (3)

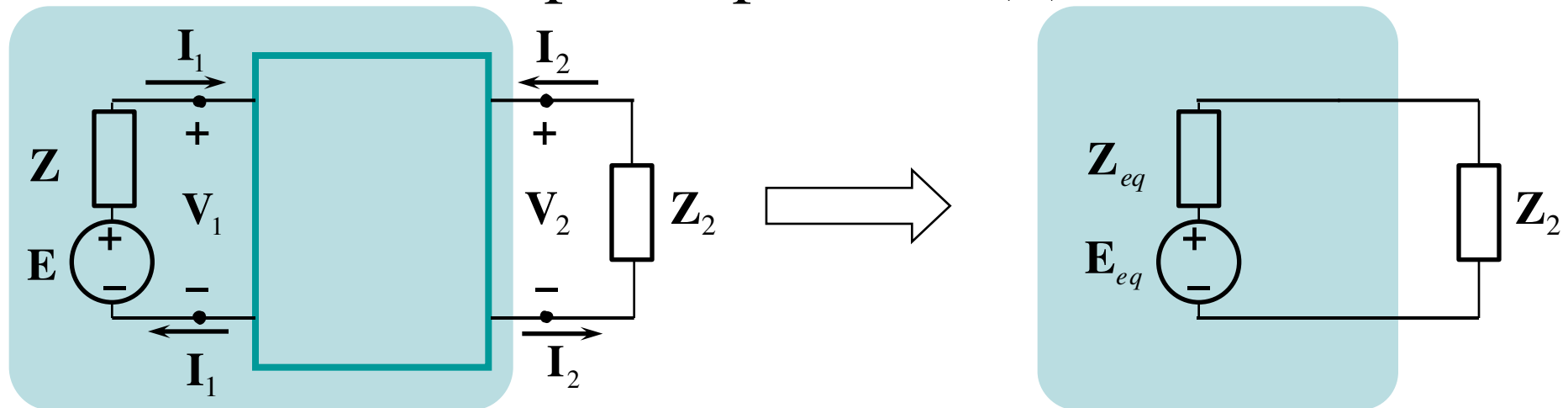

Maximum power for Z_2 ?

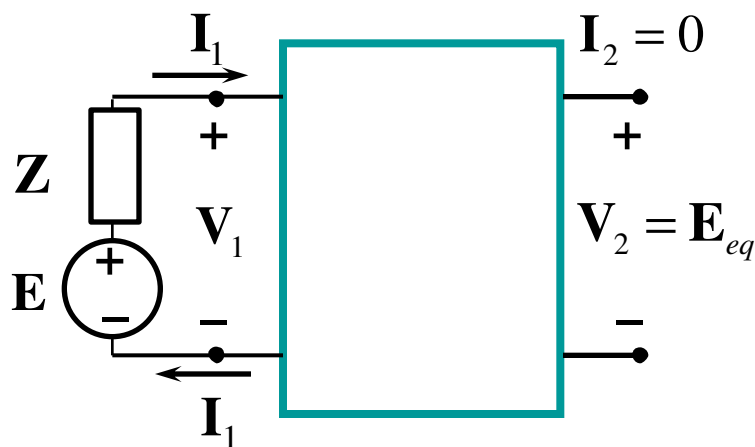

$$\left\{ \begin{array}{l} \mathbf{Z}_1 \mathbf{I}_1 + \mathbf{V}_1 = \mathbf{E} \\ \mathbf{I}_2 = 0 \end{array} \right. \rightarrow \mathbf{V}_2$$

$$\left\{ \begin{array}{l} \mathbf{V}_1 = \mathbf{z}_{11} \mathbf{I}_1 + \mathbf{z}_{12} \mathbf{I}_2 \\ \mathbf{V}_2 = \mathbf{z}_{21} \mathbf{I}_1 + \mathbf{z}_{22} \mathbf{I}_2 \end{array} \right.$$

$$\mathbf{Z}_2 = \mathbf{Z}_{eq}^*$$

Ex. 1

Input Impedance (4)

$$\mathbf{Z} = \begin{bmatrix} 30 & 20 \\ 20 & 50 \end{bmatrix}; \quad \mathbf{E} = 220\text{V}$$

$$\mathbf{Z} = 15 + j25\Omega$$

What \mathbf{Z}_2 will absorb maximum power from the circuit?

$$\mathbf{Z}_2 = \mathbf{Z}_{eq}^*$$

Method 1 $\mathbf{Z}_{eq} = \frac{1}{\mathbf{I}_2}$




$$(15 + j25)\mathbf{I}_1 + \mathbf{V}_1 = 0$$

$$\mathbf{V}_2 = 1$$

$$\begin{cases} \mathbf{V}_1 = 30\mathbf{I}_1 + 20\mathbf{I}_2 \\ \mathbf{V}_2 = 20\mathbf{I}_1 + 50\mathbf{I}_2 \end{cases}$$

$$\rightarrow \mathbf{I}_2 = 0.023 - j0.002 \text{ A}$$

$$\rightarrow \mathbf{Z}_{eq} = 43.15 + j3.75\Omega \rightarrow \mathbf{Z}_2 = 43.15 - j3.75\Omega$$

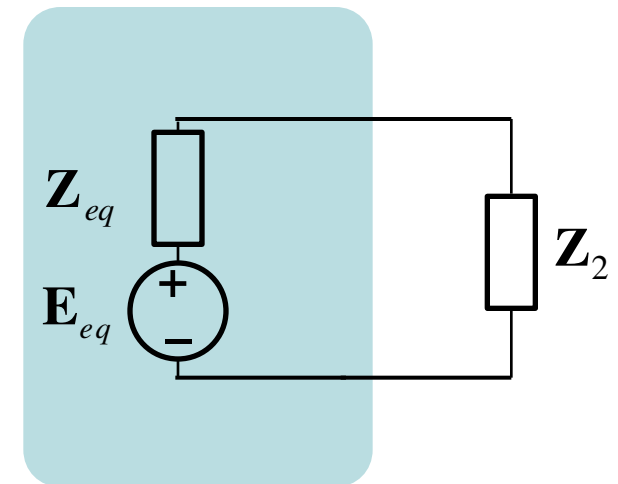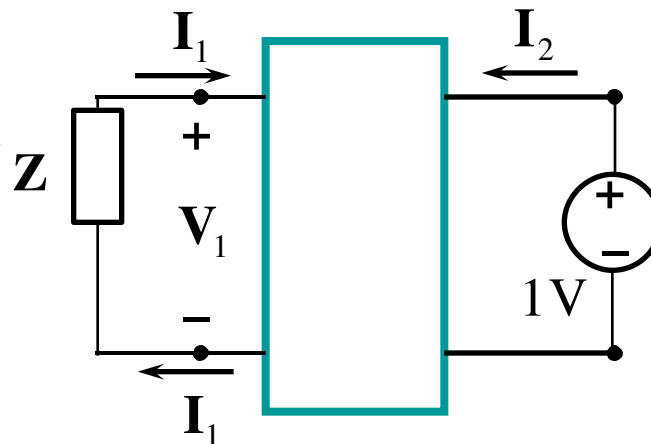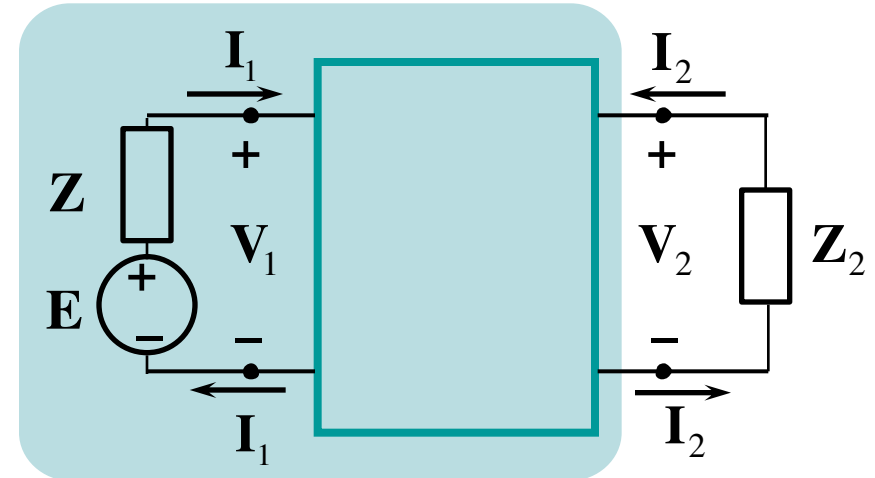



Ex. 1

Input Impedance (5)

$$\mathbf{Z} = \begin{bmatrix} 30 & 20 \\ 20 & 50 \end{bmatrix}; \quad \mathbf{E} = 220 \text{ V}$$

$$\mathbf{Z} = 15 + j25 \Omega$$

What \mathbf{Z}_2 will absorb maximum power from the circuit?

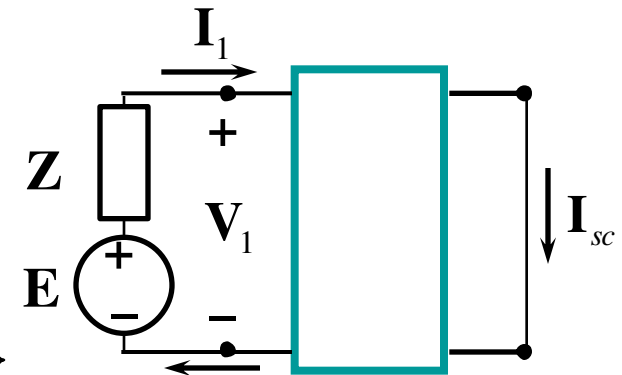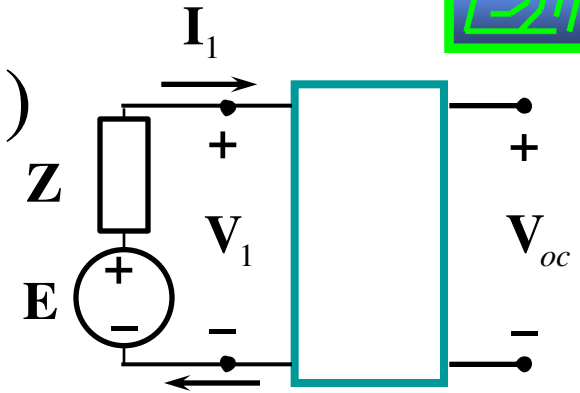

Method 2

$$\mathbf{Z}_2 = \mathbf{Z}_{eq}^*$$

$$\mathbf{Z}_{eq} = \frac{\mathbf{V}_{oc}}{\mathbf{I}_{sc}}$$

$$\left. \begin{aligned} (15 + j25)\mathbf{I}_1 + \mathbf{V}_1 &= 220 \\ \mathbf{I}_2 &= 0 \\ \begin{cases} \mathbf{V}_1 = 30\mathbf{I}_1 + 20\mathbf{I}_2 \\ \mathbf{V}_2 = 20\mathbf{I}_1 + 50\mathbf{I}_2 \end{cases} \end{aligned} \right\}$$

$$\rightarrow \mathbf{V}_2 = 74.72 - j41.51 \text{ V} = \mathbf{V}_{oc}$$

$$\left. \begin{aligned} (15 + j25)\mathbf{I}_1 + \mathbf{V}_1 &= 220 \\ \mathbf{V}_2 &= 0 \\ \begin{cases} \mathbf{V}_1 = 30\mathbf{I}_1 + 20\mathbf{I}_2 \\ \mathbf{V}_2 = 20\mathbf{I}_1 + 50\mathbf{I}_2 \end{cases} \end{aligned} \right\}$$

$$\rightarrow \mathbf{I}_2 = -1.63 + j1.10 \text{ A} = -\mathbf{I}_{sc}$$

$$\rightarrow \mathbf{Z}_{eq} = \frac{74.72 - j41.51}{1.63 - j1.10} = 43.31 + j3.77 \Omega \rightarrow \boxed{\mathbf{Z}_2 = 43.31 - j3.77 \Omega}$$

Ex. 1

Input Impedance (5)

$$\mathbf{Z} = \begin{bmatrix} 30 & 20 \\ 20 & 50 \end{bmatrix}; \quad \mathbf{E} = 220\text{V}$$

$$\mathbf{Z} = 15 + j25\Omega$$

What \mathbf{Z}_2 will absorb maximum power from the circuit?



$$\mathbf{Z}_2 = \mathbf{Z}_{eq}^*$$

Method 3
$$\mathbf{Z}_{eq} = \frac{(\mathbf{Z} + \mathbf{Z}_a)\mathbf{Z}_c}{\mathbf{Z} + \mathbf{Z}_a + \mathbf{Z}_c} + \mathbf{Z}_b$$

$$\mathbf{Z}_a = 10\Omega$$

$$\mathbf{Z}_c = 20\Omega$$

$$\mathbf{Z}_b = 30\Omega$$

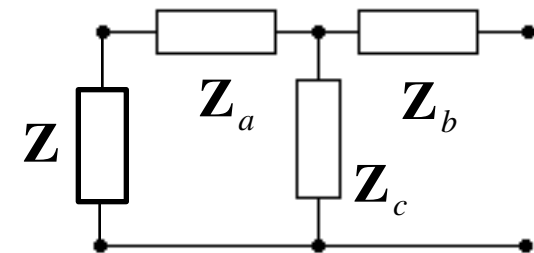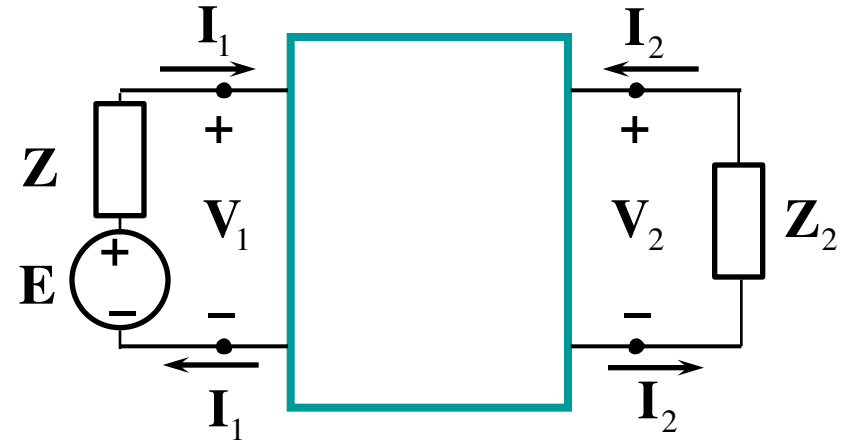

$$\rightarrow \mathbf{Z}_{eq} = \frac{(15 + j25 + 10)20}{15 + j25 + 10 + 20} + 30 = 43.21 + j3.77\Omega \rightarrow \boxed{\mathbf{Z}_2 = 43.21 - j3.77\Omega}$$

Input Impedance (6)



$$\begin{cases} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{cases}$$

$$\left. \begin{aligned} Z_{1in} &= \frac{V_1}{I_1} = \frac{AV_2 - BI_2}{CV_2 - DI_2} \\ V_2 &= Z_2 I_2 \end{aligned} \right\}$$

$$\rightarrow Z_{1in} = \frac{AZ_2 - B}{CZ_2 - D}$$

$$\left. \begin{aligned} Z_{2in} &= \frac{V_2}{-I_2} = \frac{DV_1 - BI_1}{-CV_1 + AI_1} \\ V_1 &= -Z_1 I_1 \end{aligned} \right\}$$
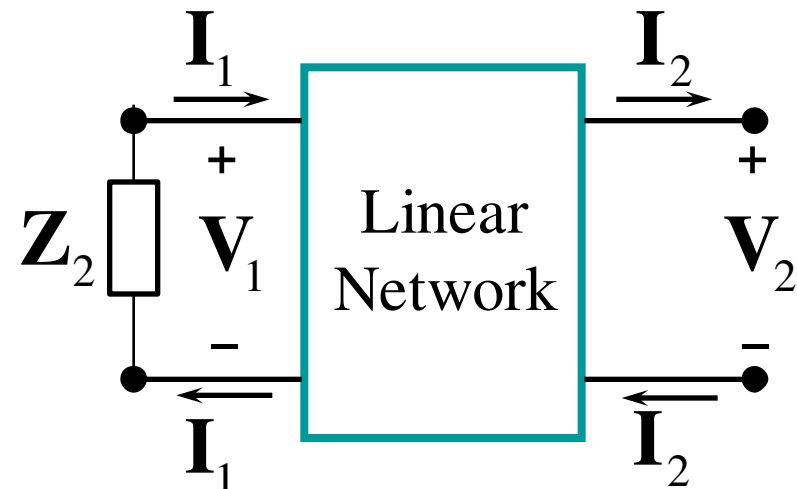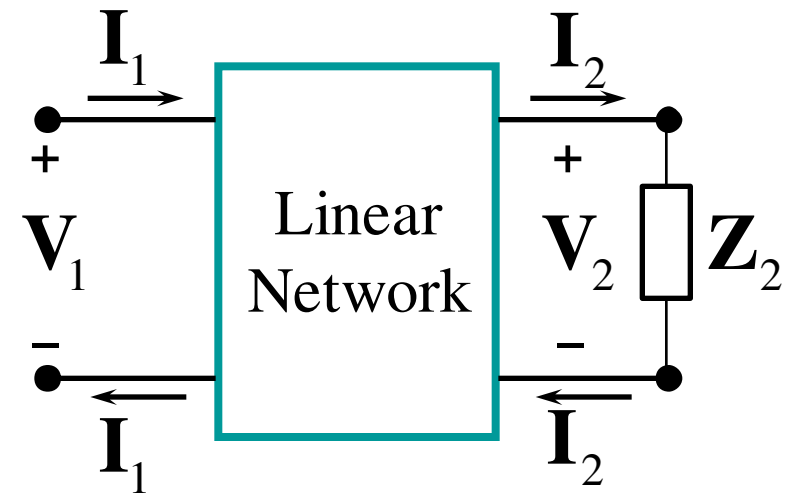
$$\rightarrow Z_{2in} = \frac{-DZ_1 - B}{CZ_1 + A}$$



Input Impedance (7)

$$\left. \begin{array}{l} Z_{1in} = \frac{AZ_2 - B}{CZ_2 - D} \\ Z_2 = 0 \text{ (short-circuit)} \end{array} \right\} \rightarrow \boxed{Z_{1sc} = \frac{B}{D}}$$

$$\left. \begin{array}{l} Z_{1in} = \frac{AZ_2 - B}{CZ_2 - D} \\ Z_2 \rightarrow \infty \text{ (open-circuit)} \end{array} \right\} \rightarrow \boxed{Z_{1oc} = \frac{A}{C}}$$

$$\left. \begin{array}{l} Z_{2in} = \frac{-DZ_1 - B}{CZ_1 + A} \\ Z_1 = 0 \text{ (short-circuit)} \end{array} \right\} \rightarrow \boxed{Z_{2sc} = \frac{-B}{A}}$$

$$\left. \begin{array}{l} Z_{2in} = \frac{-DZ_1 - B}{CZ_1 + A} \\ Z_1 \rightarrow \infty \text{ (open-circuit)} \end{array} \right\} \rightarrow \boxed{Z_{2oc} = \frac{-D}{C}}$$

Input Impedance (8)

$$\left. \begin{aligned} Z_{1sc} &= \frac{B}{D} \\ Z_{1oc} &= \frac{A}{C} \\ Z_{2sc} &= \frac{-B}{A} \\ Z_{2oc} &= \frac{-D}{C} \end{aligned} \right\} \rightarrow \left\{ \begin{aligned} A &= \sqrt{\frac{Z_{1sc} Z_{1oc}}{Z_{2sc} (Z_{1oc} - Z_{1sc})}} \\ B &= -A Z_{2sc} \\ C &= \frac{A}{Z_{1oc}} \\ D &= -\frac{B}{Z_{1sc}} \end{aligned} \right.$$

Input Impedance (9)

Ex. 2 Find **T**?


$$\mathbf{A} = \left. \frac{\mathbf{V}_1}{\mathbf{V}_2} \right|_{\mathbf{I}_2=0}$$

$$\mathbf{A} = \sqrt{\frac{\mathbf{Z}_{1sc} \mathbf{Z}_{1oc}}{\mathbf{Z}_{2sc} (\mathbf{Z}_{1oc} - \mathbf{Z}_{1sc})}}$$

$$\mathbf{B} = -\mathbf{A} \mathbf{Z}_{2sc}$$

$$\mathbf{C} = \frac{\mathbf{A}}{\mathbf{Z}_{1oc}}$$
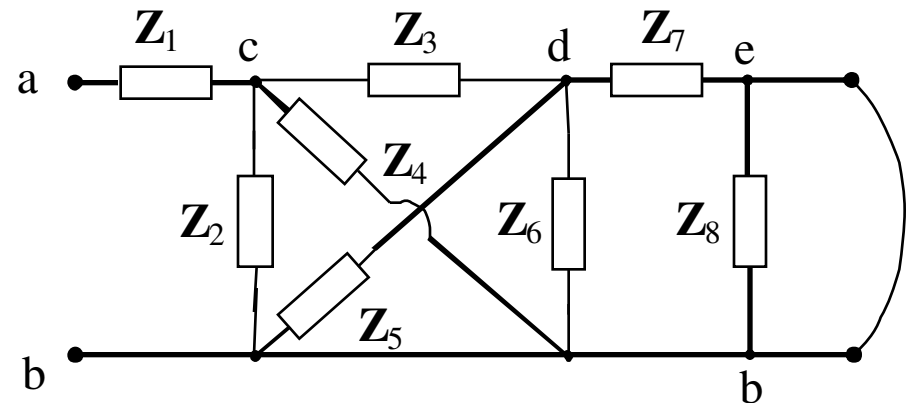
$$\mathbf{D} = -\frac{\mathbf{B}}{\mathbf{Z}_{1sc}}$$




$$\mathbf{Z}_{1sc} = ?$$

$$\mathbf{Z}_{1sc} = \mathbf{Z}_{ab} = \{ [(\mathbf{Z}_7 // \mathbf{Z}_6 // \mathbf{Z}_5) + \mathbf{Z}_3] // \mathbf{Z}_4 // \mathbf{Z}_2 \} + \mathbf{Z}_1$$

Input Impedance (10)

Ex. 2 Find **T**?

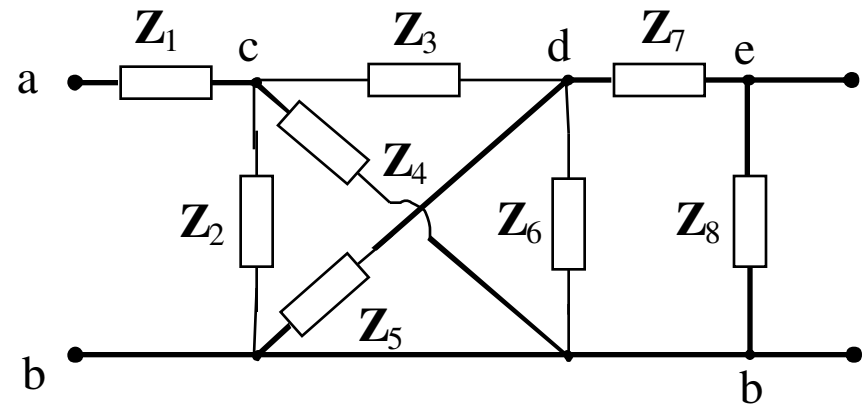

$Z_{1oc} = ?$

$$A = \sqrt{\frac{Z_{1sc} Z_{1oc}}{Z_{2sc} (Z_{1oc} - Z_{1sc})}}$$

$$B = -AZ_{2sc}$$


$$C = \frac{A}{Z_{1oc}}$$

$$D = -\frac{B}{Z_{1sc}}$$

$$Z_{1oc} = Z_{ab} = \left[\left\{ [(Z_7 + Z_8) // Z_6 // Z_5] + Z_3 \right\} // Z_4 // Z_2 \right] + Z_1$$

Input Impedance (11)

Ex. 2 Find **T**?

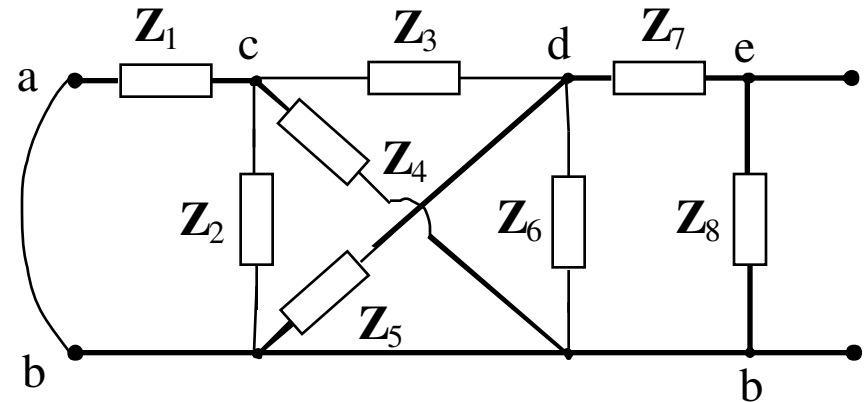

$$Z_{2sc} = ?$$

$$A = \sqrt{\frac{Z_{1sc} Z_{1oc}}{Z_{2sc} (Z_{1oc} - Z_{1sc})}}$$

$$B = -AZ_{2sc}$$

$$C = \frac{A}{Z_{1oc}}$$


$$D = -\frac{B}{Z_{1sc}}$$

$$Z_{2sc} = Z_{eb} = \left[\{ [(Z_1 // Z_2 // Z_4) + Z_3] // Z_5 // Z_6 \} + Z_7 \right] // Z_8$$


Input Impedance (12)

Ex. 2 Find **T**?
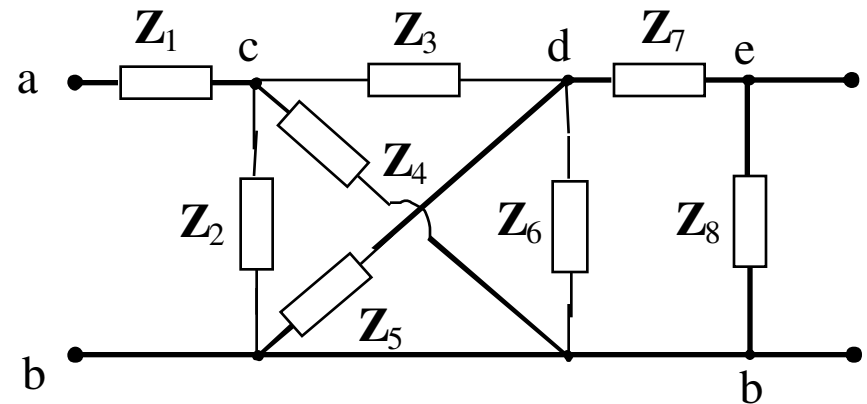
$$\left. \begin{array}{l} Z_{1sc} \\ Z_{1oc} \\ Z_{2sc} \end{array} \right\} \rightarrow \left\{ \begin{array}{l} \mathbf{A} = \sqrt{\frac{Z_{1sc} Z_{1oc}}{Z_{2sc} (Z_{1oc} - Z_{1sc})}} \\ \mathbf{B} = -\mathbf{A} Z_{2sc} \\ \mathbf{C} = \frac{\mathbf{A}}{Z_{1oc}} \\ \mathbf{D} = -\frac{\mathbf{B}}{Z_{1sc}} \end{array} \right.$$





Input Impedance (13)

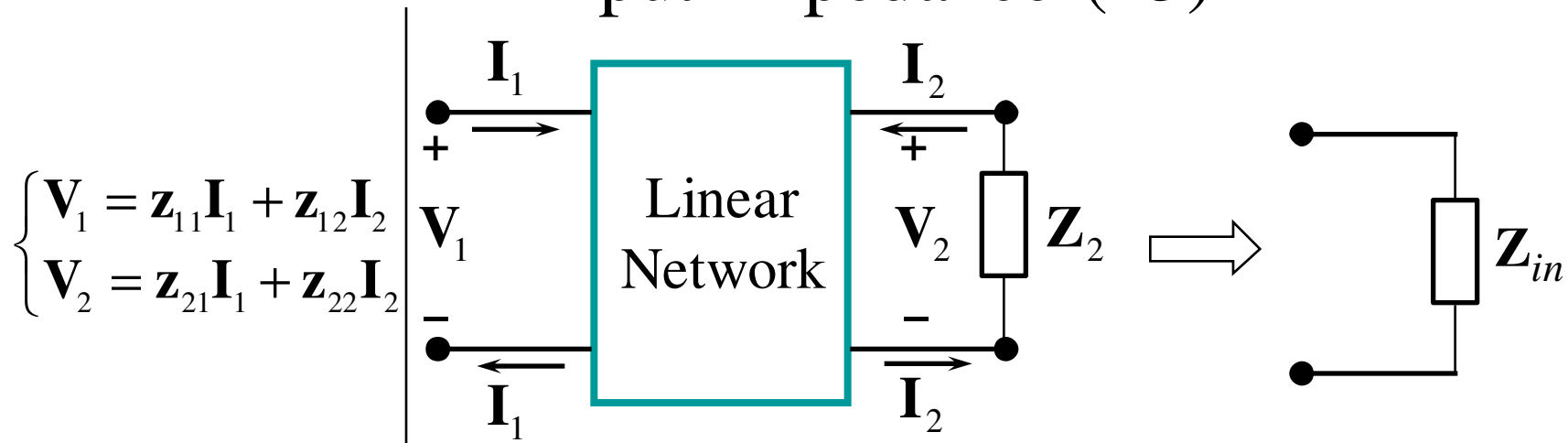

$$\rightarrow \mathbf{I}_1 = \frac{\mathbf{V}_2 - \mathbf{z}_{22}\mathbf{I}_2}{\mathbf{z}_{21}}$$

$$\rightarrow \mathbf{Z}_{in} = \frac{\mathbf{V}_1}{\mathbf{I}_1} = \frac{\mathbf{z}_{11} \frac{\mathbf{V}_2 - \mathbf{z}_{22}\mathbf{I}_2}{\mathbf{z}_{21}} + \mathbf{z}_{12}\mathbf{I}_2}{\frac{\mathbf{V}_2 - \mathbf{z}_{22}\mathbf{I}_2}{\mathbf{z}_{21}}} \quad \left. \begin{array}{l} \\ \mathbf{V}_2 = -\mathbf{Z}_2\mathbf{I}_2 \end{array} \right\} \rightarrow \mathbf{Z}_{in} = \frac{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21} + \mathbf{z}_{11}\mathbf{Z}_2}{\mathbf{z}_{22} + \mathbf{Z}_2}$$

Input Impedance (14)

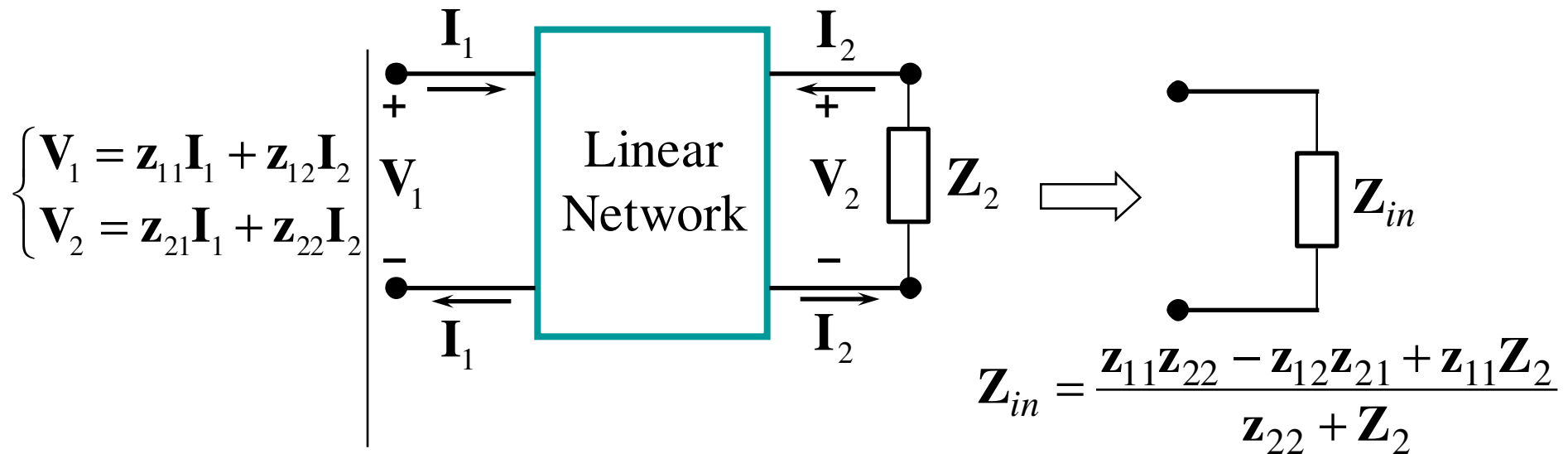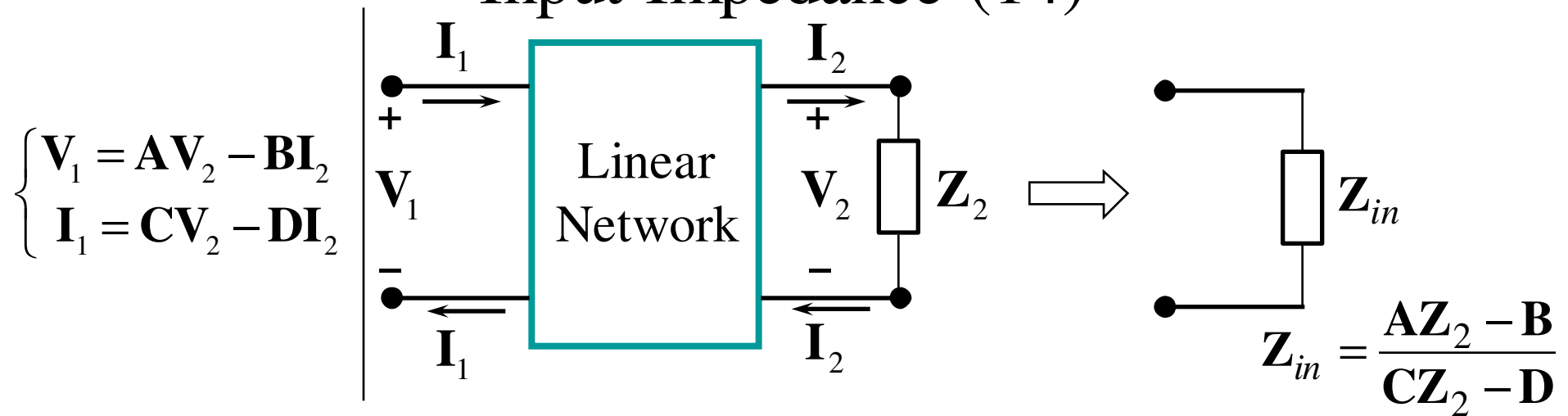

Ex. 3

Input Impedance (15)

$$E = 220 \text{ V}; Z_1 = 20\Omega; Z_2 = j50\Omega; \mathbf{T} = \begin{bmatrix} 3 & -4 \\ 2 & -3 \end{bmatrix}.$$

Solve for \mathbf{I}_1 ?



$$\left\{ \begin{array}{l} V_1 = 3V_2 + 4I_2 \\ I_1 = 2V_2 + 3I_2 \\ 20I_1 + V_1 = 220 \\ V_2 = j50I_2 \end{array} \right\} \rightarrow \mathbf{I}_1 = 10.23 - j0.0024 \text{ A}$$

Method 1

$$Z_{in} = \frac{AZ_2 - B}{CZ_2 - D} = \frac{3(j50) + 4}{2(j50) + 3} = 1.50 + j0.0050\Omega$$

Method 2

$$\mathbf{I}_1 = \frac{E}{Z_1 + Z_{in}} = \frac{220}{20 + 1.50 + j0.0050} = 10.23 - j0.0024 \text{ A}$$

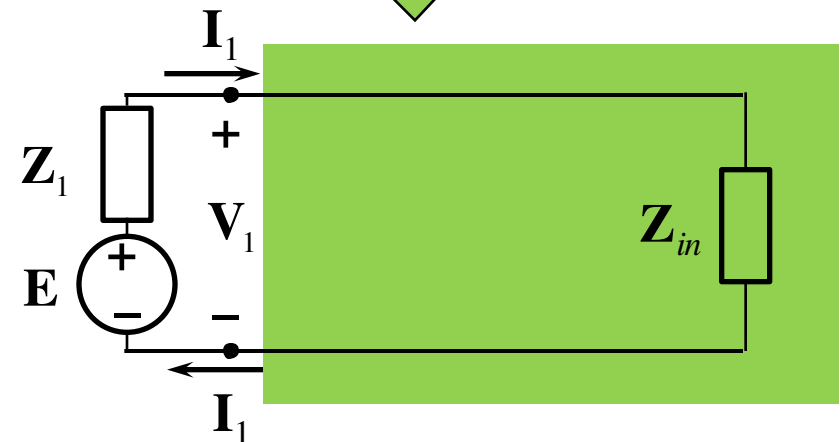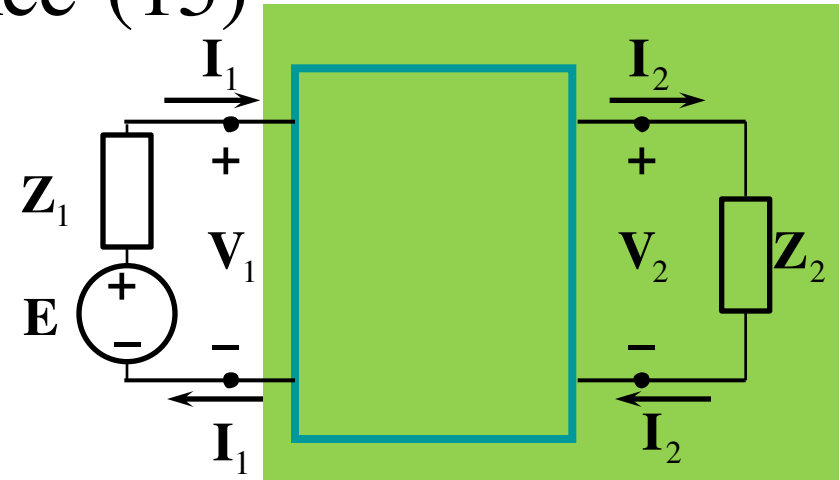

Ex. 4

Find $i_1(t)$? **Method 1**

$$v_C(0) = 12 \text{ V}$$



$$\begin{cases} v_1(0) = 30i_1(0) + 20i_2(0) \\ v_2(0) = 20i_1(0) + 50i_2(0) \\ v_1(0) = 12 \\ v_2(0) = -10i_2(0) \end{cases}$$

$$\rightarrow i_1(0) = 0.5143 \text{ A} = i_L(0)$$

$$\begin{cases} V_1(s) = 30I_1(s) + 20I_2(s) \\ V_2(s) = 20I_1(s) + 50I_2(s) \\ \left(2s + \frac{200}{s}\right)I_1(s) + V_1(s) = 1.10 + \frac{12}{s} \\ V_2(s) = -10I_2(s) \end{cases}$$

$$\rightarrow I_1(s) = \frac{0.515s + 6}{s^2 + 11.667s + 100} \text{ A} \rightarrow i_1(t) = 0.6334e^{-5.83t} \cos(8.12t - 35.6^\circ) \text{ A}$$

Input Impedance (16)

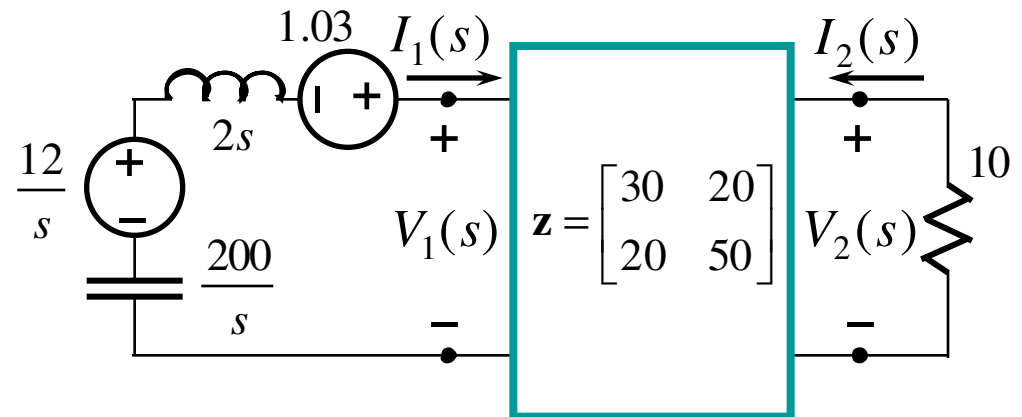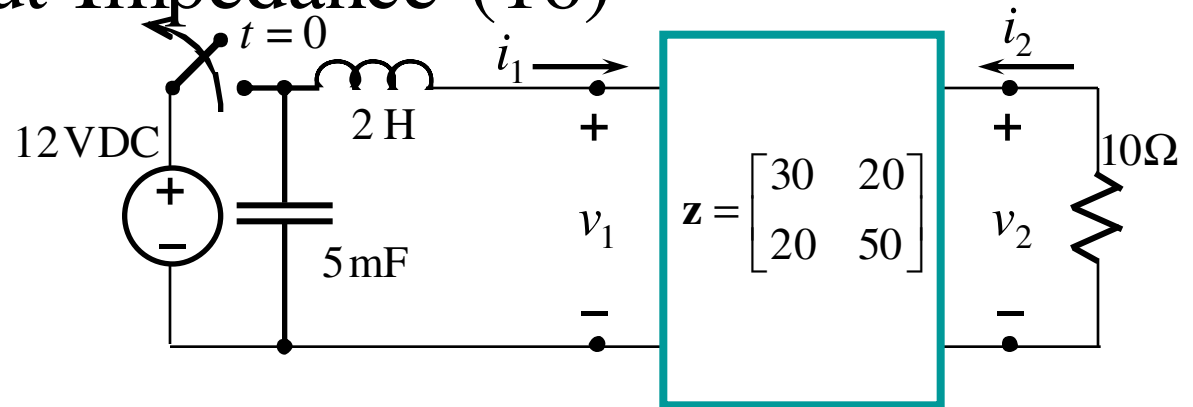

Ex. 4

Input Impedance (17)

Find $i_1(t)$? Method 3

$$v_C(0) = 12 \text{ V}$$




$$\mathbf{z}_{in} = \frac{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21} + \mathbf{z}_{11}\mathbf{Z}_2}{\mathbf{z}_{22} + \mathbf{Z}_2} = 23.33\Omega$$

$$i_1(0) = \frac{12}{23.33} = 0.5143 \text{ A} = i_L(0)$$

$$I_1(s) = \frac{1.03 + \frac{12}{s}}{\frac{200}{s} + 2s + 23.33}$$

$$= \frac{0.515s + 6}{s^2 + 11.667s + 100} \text{ A}$$
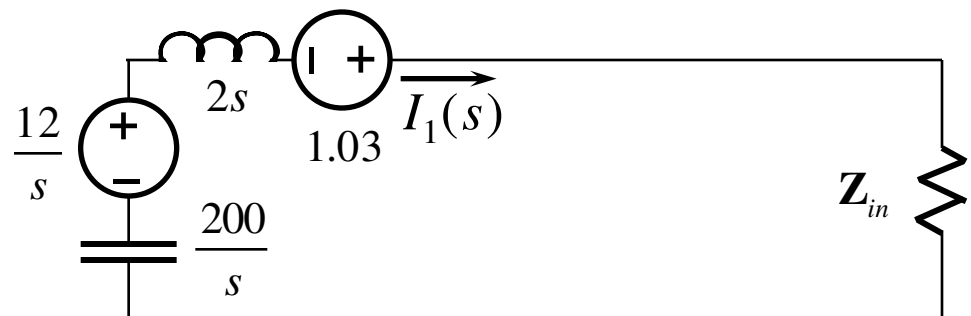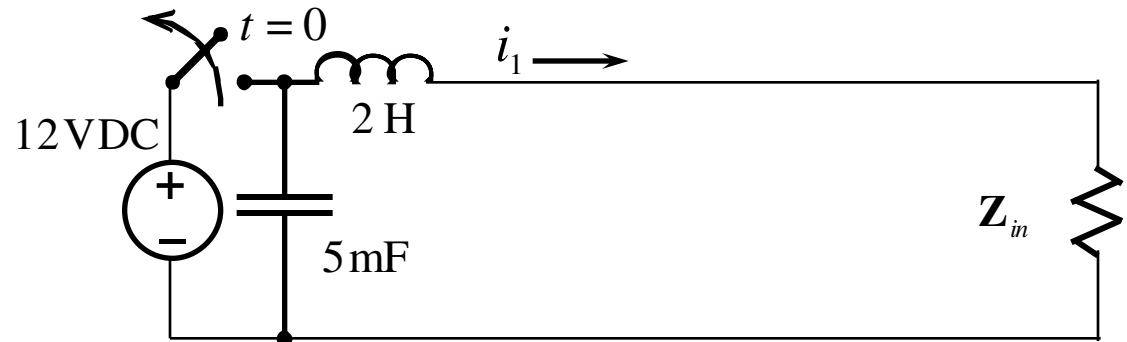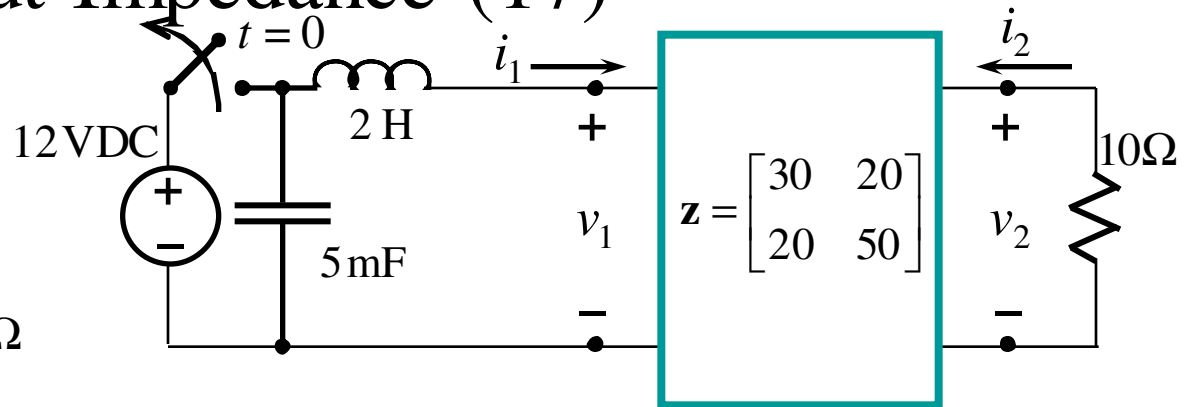
$$\rightarrow i_1(t) = 0.6334e^{-5.83t} \cos(8.12t - 35.6^\circ) \text{ A}$$



Two-port Networks

1. Introduction
2. Parameters
3. Relationships between Parameters
4. Two-port Network Analysis
5. Interconnection of Networks
6. T & Π Networks
7. Equivalent Two-port Networks of Magnetically Coupled Circuits
8. Input Impedance
- 9. Transfer Function**



Transfer Function (1)

- Voltage transfer function: $\mathbf{K}_v = \frac{\mathbf{V}_2}{\mathbf{V}_1}$
- Current transfer function: $\mathbf{K}_i = \frac{\mathbf{I}_2}{\mathbf{I}_1}$
- Voltage – current transfer function: $\mathbf{K}_{vi} = \frac{\mathbf{V}_2}{\mathbf{I}_1}$


Ex. 1

Transfer Function (2)

$$\mathbf{z} = \begin{bmatrix} 30 & 20 \\ 20 & 50 \end{bmatrix}; \mathbf{E} = 220 \text{ V}$$

$$\mathbf{Z}_L = 15 + j25 \Omega$$

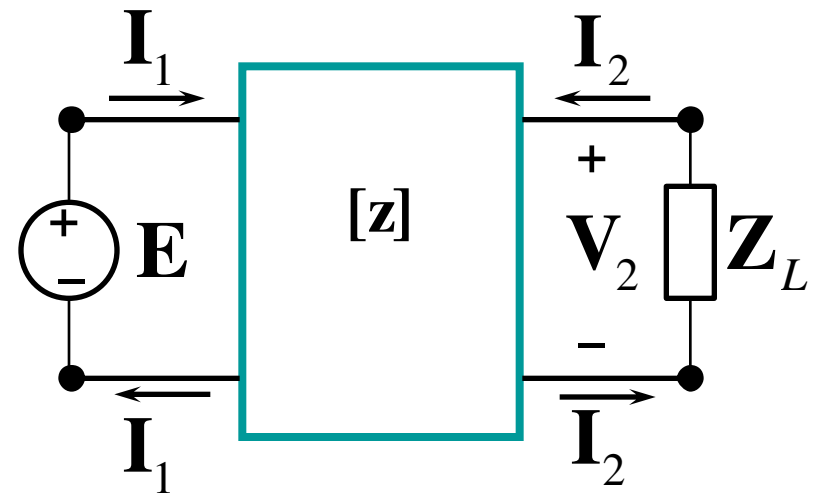Find \mathbf{K}_v , \mathbf{K}_i , \mathbf{K}_{vi} ?



$$\left\{ \begin{array}{l} \mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2 \\ \mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2 \end{array} \right.$$

$$\left. \begin{array}{l} \mathbf{V}_1 = \mathbf{E} \\ \mathbf{V}_2 = -\mathbf{Z}_L\mathbf{I}_2 \end{array} \right\}$$

$$\rightarrow \left\{ \begin{array}{l} \mathbf{E} = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2 \\ -\mathbf{Z}_L\mathbf{I}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2 \end{array} \right. \rightarrow \left\{ \begin{array}{l} \mathbf{I}_1 = \frac{\mathbf{z}_{22} + \mathbf{Z}_L}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21} + \mathbf{z}_{11}\mathbf{Z}_L} \mathbf{E} \\ \mathbf{I}_2 = \frac{-\mathbf{z}_{21}}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21} + \mathbf{z}_{11}\mathbf{Z}_L} \mathbf{E} \end{array} \right.$$


Ex. 1

Transfer Function (3)

$$\mathbf{z} = \begin{bmatrix} 30 & 20 \\ 20 & 50 \end{bmatrix}; \mathbf{E} = 220 \text{ V}$$

$$\mathbf{Z}_L = 15 + j25 \Omega$$

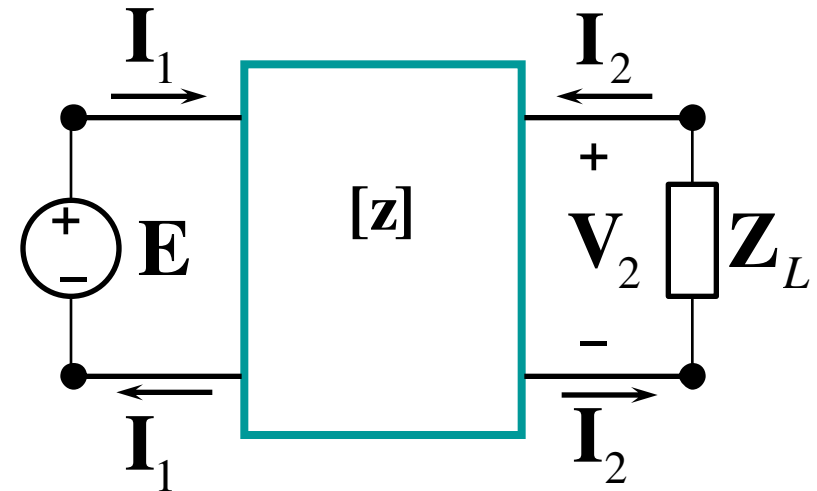Find \mathbf{K}_v , \mathbf{K}_i , \mathbf{K}_{vi} ?



$$\mathbf{I}_1 = \frac{\mathbf{z}_{22} + \mathbf{Z}_L}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21} + \mathbf{z}_{11}\mathbf{Z}_L} \mathbf{E}$$

$$\mathbf{I}_2 = \frac{-\mathbf{z}_{21}}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21} + \mathbf{z}_{11}\mathbf{Z}_L} \mathbf{E}$$

$$\left. \begin{array}{l} \mathbf{V}_2 = -\mathbf{Z}_L \mathbf{I}_2 \end{array} \right\} \rightarrow \mathbf{V}_2 = \frac{\mathbf{z}_{21}\mathbf{Z}_L}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21} + \mathbf{z}_{11}\mathbf{Z}_L} \mathbf{E}$$

$$\rightarrow \mathbf{K}_v = \frac{\mathbf{V}_2}{\mathbf{V}_1} = \frac{\mathbf{z}_{21}\mathbf{Z}_L}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21} + \mathbf{z}_{11}\mathbf{Z}_L} = \boxed{0.28 + j0.19}$$


Ex. 1

Transfer Function (4)

$$\mathbf{z} = \begin{bmatrix} 30 & 20 \\ 20 & 50 \end{bmatrix}; \mathbf{E} = 220 \text{ V}$$

$$\mathbf{Z}_L = 15 + j25 \Omega$$

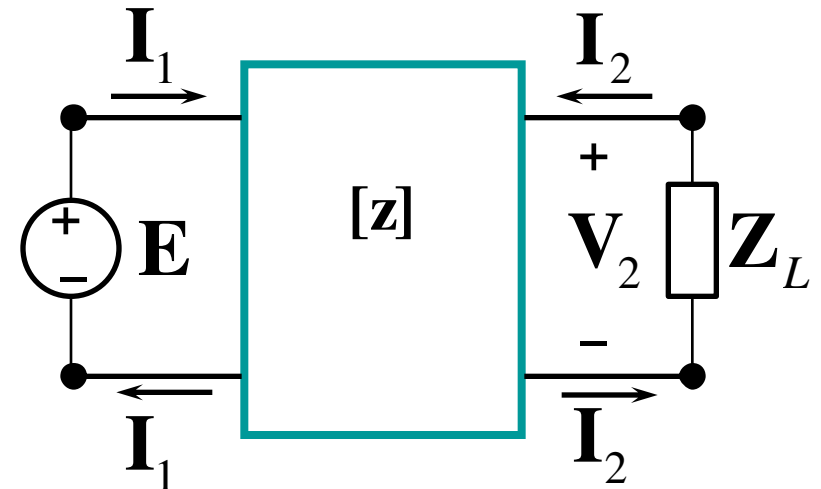Find \mathbf{K}_v , \mathbf{K}_i , \mathbf{K}_{vi} ?



$$\left. \begin{aligned} \mathbf{I}_1 &= \frac{\mathbf{z}_{22} + \mathbf{Z}_L}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21} + \mathbf{z}_{11}\mathbf{Z}_L} \mathbf{E} \\ \mathbf{I}_2 &= \frac{-\mathbf{z}_{21}}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21} + \mathbf{z}_{11}\mathbf{Z}_L} \mathbf{E} \\ \mathbf{K}_i &= \frac{\mathbf{I}_2}{\mathbf{I}_1} \end{aligned} \right\} \rightarrow \mathbf{K}_i = \frac{-\mathbf{z}_{21}}{\mathbf{z}_{22} + \mathbf{Z}_L} = \boxed{-0.27 + j0.10}$$


Ex. 1

Transfer Function (5)

$$\mathbf{z} = \begin{bmatrix} 30 & 20 \\ 20 & 50 \end{bmatrix}; \mathbf{E} = 220 \text{ V}$$

$$\mathbf{Z}_L = 15 + j25 \Omega$$

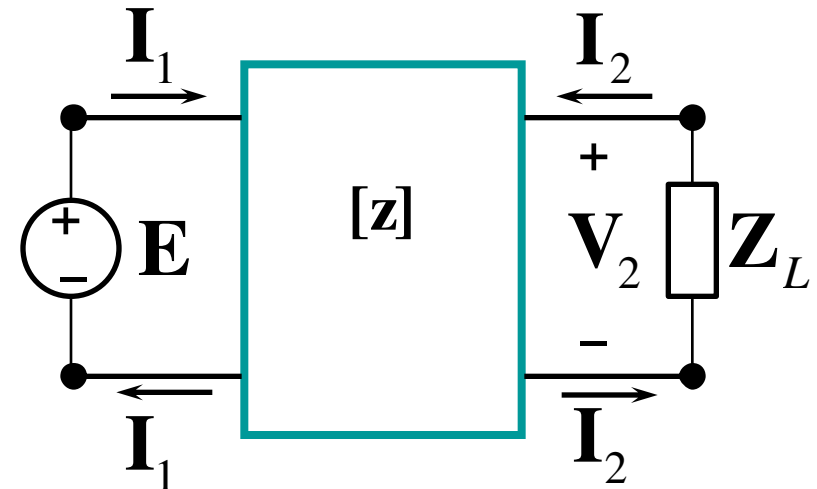Find \mathbf{K}_v , \mathbf{K}_i , \mathbf{K}_{vi} ?



$$\mathbf{I}_1 = \frac{\mathbf{z}_{22} + \mathbf{Z}_L}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21} + \mathbf{z}_{11}\mathbf{Z}_L} \mathbf{E}$$

$$\mathbf{V}_2 = \frac{\mathbf{z}_{21}\mathbf{Z}_L}{\mathbf{z}_{11}\mathbf{z}_{22} - \mathbf{z}_{12}\mathbf{z}_{21} + \mathbf{z}_{11}\mathbf{Z}_L} \mathbf{E}$$


$$\mathbf{K}_{vi} = \frac{\mathbf{V}_2}{\mathbf{I}_1} \rightarrow \mathbf{K}_{vi} = \frac{\mathbf{z}_{21}\mathbf{Z}_L}{\mathbf{z}_{22} + \mathbf{Z}_L}$$

$$= \boxed{6.60 + j5.15 \Omega}$$

Ex. 2

Transfer Function (6)

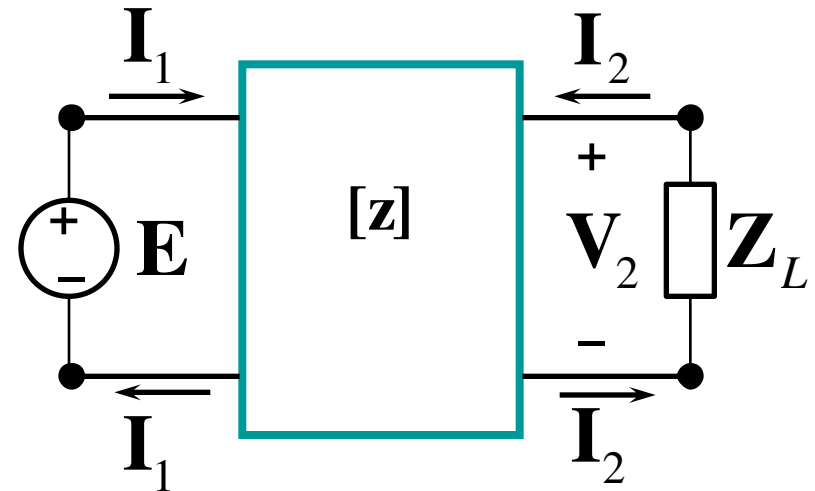$E = 380 \text{ V}; Z_L = 15 + j25 \Omega;$
 $K_v = 0.28 + j0.19;$ Find V_2 ?



$$\left. \begin{array}{l} K_v = \frac{V_2}{V_1} \\ V_1 = E \end{array} \right\} \rightarrow V_2 = K_v E = (0.28 + j0.19) \times 380$$

$$= 107.7 + j70.5 \text{ V}$$

$$\rightarrow \boxed{V_2 = 128.7 \text{ V}}$$