

Fundamentals of Electric Circuits

DC Circuits

Chapter 6. Capacitors and Inductors

- 6.1. Introduction
- 6.2. Capacitors
- 6.3. Series and parallel capacitors
- 6.4. Inductors
- 6.5. Series and parallel inductors
- 6.6. Applications

Capacitors and Inductors

6.1. Introduction

- + In this chapter → introduce two new and important passive linear circuit elements: capacitor and inductor
- + Capacitors and inductors → *not dissipate but store energy* which can be retrieved at a later time → be called *storage elements*
- + Introduction of capacitors and inductors: → able to analyze more important and practical circuits
- + Applications: Capacitors can be combined with op amps to form *integrators, differentiators, and analog computers*

6

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Capacitors and Inductors

6.2. Capacitors


+ **Capacitor** → a passive element designed to store energy in its electric field

+ **Capacitor** → two conducting plates separated by an insulator (or dielectric): *air, ceramic, paper, mica,...*


+ When a voltage v is connected:

→ Positive charge q on one plate

→ Negative charge $-q$ on another one

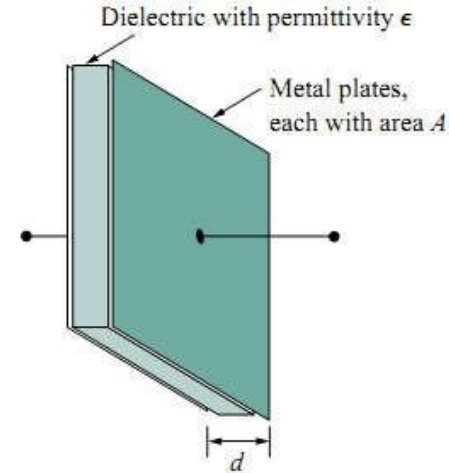

A typical capacitor

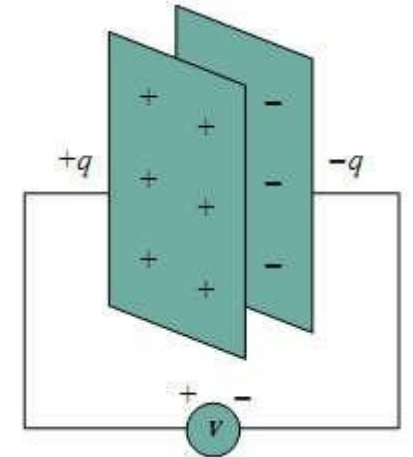

A capacitor with applied voltage v

+ **Capacitance**: → the ratio of the charge on one plate of a capacitor to the voltage difference between the two plates, measured in farads

$$C = \frac{q}{V}$$

$$1F = \frac{1C}{1V}$$

6

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Capacitors and Inductors

6.2. Capacitors

+ **Capacitance C**: depend on capacitor **physical dimension** (not q and V)


For parallel plate capacitors

$$C = \frac{\epsilon A}{d}$$

A : **surface area** of each plate


d : **distance** between the plates

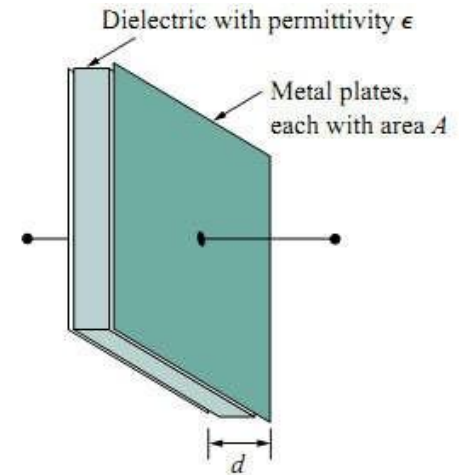ϵ : **permittivity** of the dielectric material between the plates



A typical capacitor

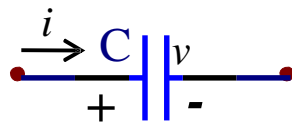
+ **Typically**, **capacitance** have values in the pF to μF



Fix, un-polarized capacitor




Ceramic capacitor

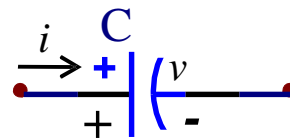

Fix, polarized capacitor



Electrolytic capacitor

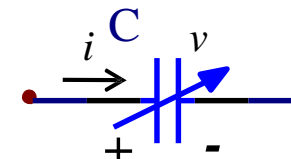

Variable capacitor



Trimmer capacitor

6

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits


Capacitors and Inductors

6.2. Capacitors

+ **Capacitors** → used to block DC, pass AC, shift phase, store energy, start motors, suppress noise,...

$$i = \frac{dq}{dt} = \frac{\partial q}{\partial v} \cdot \frac{dv}{dt} = C \frac{dv}{dt}$$
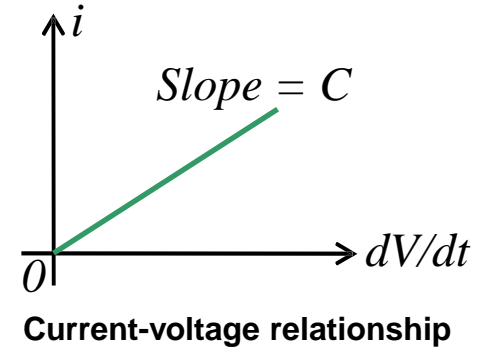
$$v = \frac{1}{C} \int_{-\infty}^t i dt = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$$



+ **Instantaneous power:**

$$p = vi = Cv \frac{dv}{dt}$$

+ **Energy:**

$$w = \int_{-\infty}^t p dt = \int_{-\infty}^t Cv \frac{dv}{dt} dt = \frac{1}{2} Cv^2$$

$$w = \frac{1}{2} Cv^2 = \frac{q^2}{2C}$$

+ **Classification:**

Linear capacitor


Nonlinear capacitor

Capacitors and Inductors

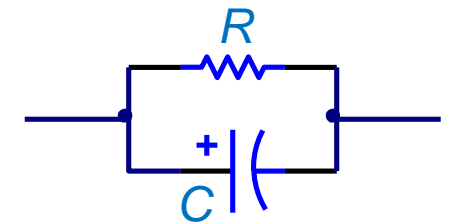6.2. Capacitors

+ Properties of a capacitor:

- A capacitor is an *open circuit to DC*
- The voltage on a capacitor *cannot change abruptly*: A discontinuous change in voltage requires an infinite current
- The ideal capacitor does *not dissipate energy*: It takes power from the circuit when storing energy in its field and returns previously stored energy when delivering power to the circuit
- A *non-ideal capacitor* has a parallel-model leakage resistance (~100MΩ) → the leakage resistance may be neglected for most practical applications



Circuit model of a non-ideal capacitor

6

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Capacitors and Inductors

6.2. Capacitors



+ **Example 1:** Determine the current through a $200\mu\text{F}$ capacitor whose voltage is

$$v(t) = \begin{cases} 50tV & 0 < t < 1 \\ 100 - 50tV & 1 < t < 3 \\ -200 + 50tV & 3 < t < 4 \\ 0V & \text{otherwise} \end{cases}$$

The current through a capacitor: $i = C \frac{dv}{dt}$

So we have:
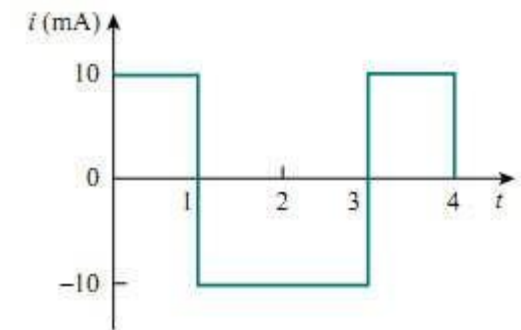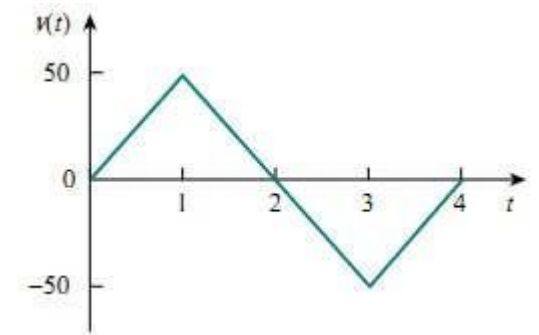
$$i(t) = 200 \cdot 10^{-6} \cdot \begin{cases} 50A & 0 < t < 1 \\ -50A & 1 < t < 3 \\ 50A & 3 < t < 4 \\ 0A & \text{otherwise} \end{cases} = \begin{cases} 10mA & 0 < t < 1 \\ -10mA & 1 < t < 3 \\ 10mA & 3 < t < 4 \\ 0mA & \text{otherwise} \end{cases}$$



6

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Capacitors and Inductors

6.2. Capacitors

+ **Example 2:** Obtain the energy stored in each capacitor in the given circuit under DC condition

Under DC conditions, each capacitor is an open circuit

The current through R1, R2 and R4 is:


$$i = \frac{jR_1}{R_1 + R_2 + R_4} = \frac{6 \cdot 10^{-3} \cdot 3}{3 + 2 + 4} = 2mA$$

The voltages across C_1 and C_2 are:

$$v_1 = R_2 i = 2 \cdot 10^3 \cdot 2 \cdot 10^{-3} = 4V \quad v_2 = R_4 i = 4 \cdot 10^3 \cdot 2 \cdot 10^{-3} = 8V$$

So energies stored in C_1 , C_2 are:
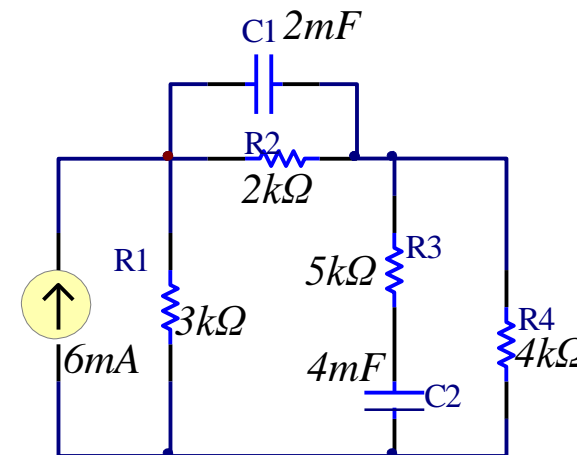
$$w_1 = \frac{1}{2} C_1 v_1^2 = 16mJ \quad w_2 = \frac{1}{2} C_2 v_2^2 = 128mJ$$



Capacitors and Inductors

6.3. Series and Parallel Capacitors

+ Equivalent capacitance C_{eq} of N capacitor in parallel:



Apply KCL:

$$i = i_1 + i_2 + \dots + i_N \rightarrow i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt}$$

$$\rightarrow i = \left(\sum_{k=1}^N C_k \right) \frac{dv}{dt} = C_{eq} \frac{dv}{dt}$$

$$C_{eq} = C_1 + C_2 + \dots + C_N$$

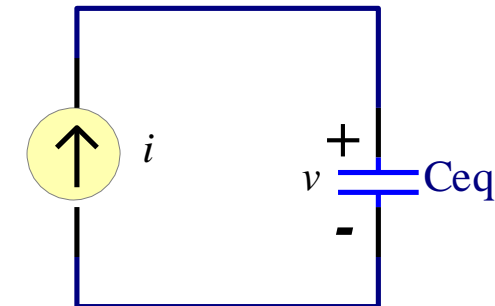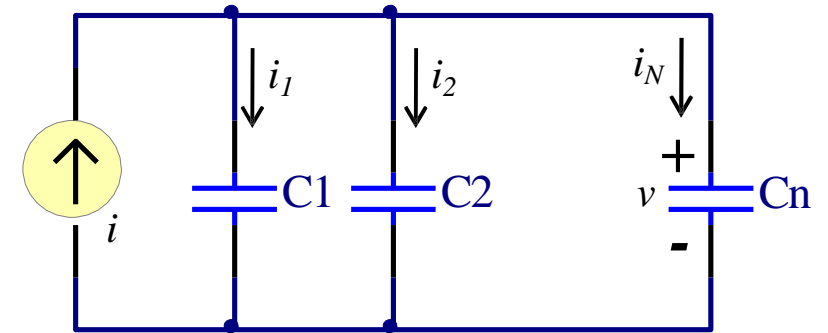+ Equivalent capacitance of N parallel-connected capacitors \rightarrow the sum of the individual capacitances



6

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Capacitors and Inductors

6.3. Series and Parallel Capacitors


+ Equivalent capacitance C_{eq} of N capacitor in series:

KVL to the loop:

$$v = v_1 + v_2 + \dots + v_N$$

$$\rightarrow v = \frac{1}{C_1} \int_{t_0}^t i dt + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i dt + v_2(t_0) + \dots + \frac{1}{C_N} \int_{t_0}^t i dt + v_N(t_0)$$
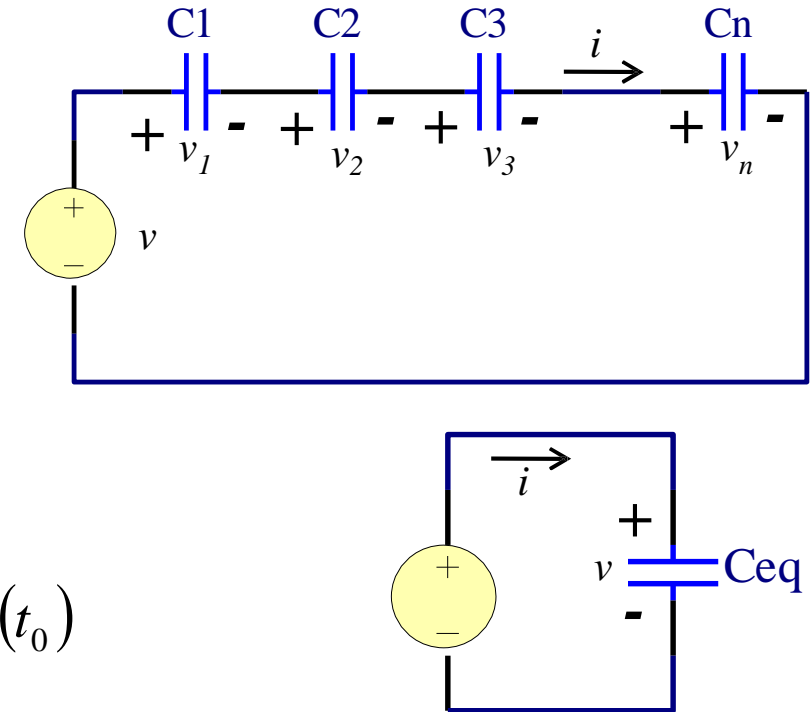
$$\rightarrow v = \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int_{t_0}^t i dt + v_1(t_0) + \dots + v_N(t_0) = \frac{1}{C_{eq}} \int_{t_0}^t i dt + v(t_0)$$



+ Equivalent capacitance of series-connected capacitors: \rightarrow the reciprocal of the sum of the reciprocals of the individual capacitances

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$

6

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Capacitors and Inductors

6.3. Series and Parallel Capacitors

+ **Example 3:** Find the voltage across each capacitor


C_3 and C_4 can be combined to get: $C_{34} = C_3 + C_4 = 60mF$

C_{34} is in series with C_1 and C_2 :
$$C_{eq} = \frac{1}{\frac{1}{C_{34}} + \frac{1}{C_1} + \frac{1}{C_2}} = 10mF$$

Total charge : $q = C_{eq}v = 10 \cdot 10^{-3} \cdot 30 = 0.3C$

$$v_1 = \frac{q}{C_1} = \frac{0.3}{20 \cdot 10^{-3}} = 15V \quad v_2 = \frac{q}{C_2} = \frac{0.3}{30 \cdot 10^{-3}} = 10V \quad v_3 = 30 - (v_1 + v_2) = 5V$$

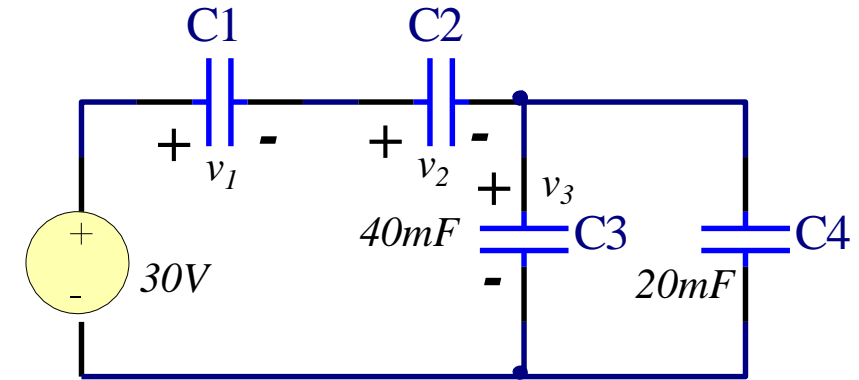or :
$$v_3 = \frac{q}{C_{34}} = \frac{0.3}{60 \cdot 10^{-3}} = 5V$$



6

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Capacitors and Inductors

6.3. Series and Parallel Capacitors

+ **Example 4:** Find the voltage across each capacitor

$$C_{34} = \frac{1}{\frac{1}{C_3} + \frac{1}{C_4}} = 20\mu F$$

$$C_{234} = C_2 + C_{34} = 40\mu F$$

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_{234}}} = 20\mu F$$

$$\rightarrow q = 60.C_{eq} = 1200\mu C$$


$$\rightarrow v_1 = \frac{q}{C_1} = \frac{1200}{40} = 30V$$

$$\rightarrow v_2 = v_{34} = \frac{q}{C_{234}} = 60 - v_1 = 30V$$

$$\rightarrow q_{34} = C_{34}v_{34} = 20.30 = 600\mu C$$

$$\rightarrow v_3 = \frac{q_{34}}{C_3} = 10V$$
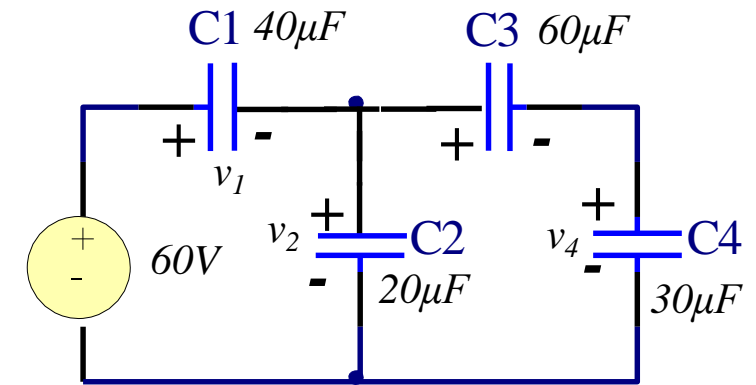
$$\rightarrow v_4 = \frac{q_{34}}{C_4} = v_{34} - v_3 = 20V$$



6

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Capacitors and Inductors

6.4. Inductors


+ An inductor:

- a passive element designed to store energy in its magnetic field
- consists of a coil of conducting wire


+ If current is allowed to pass through an inductor → the voltage across the inductor is directly proportional to the time rate of change of the current

$$v = L \frac{di}{dt} \leftrightarrow i = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$$


L : inductance of the inductor [H]

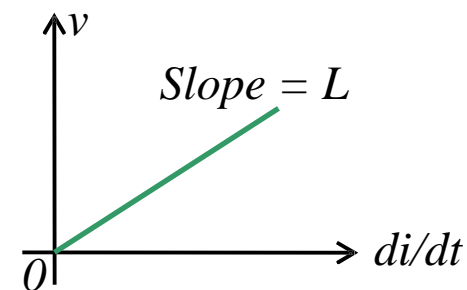

Voltage-current relationship

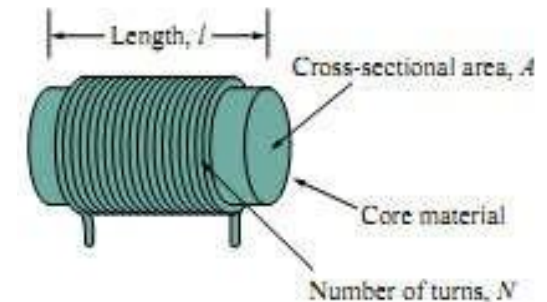

Typical form of an inductor

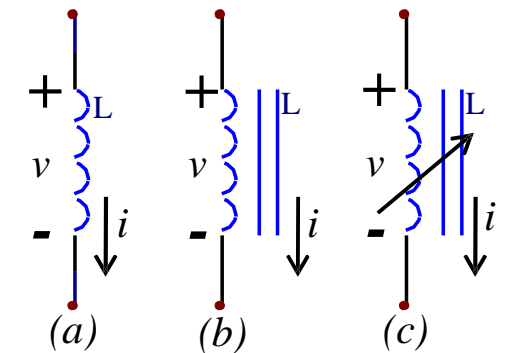

Circuit symbols for inductors: (a) air-core, (b) iron-core, (c) variable iron-core

Capacitors and Inductors

6.4. Inductors

+ Inductance:

→ **property of an inductor** by which a change in current through it induces an electromotive force in the conductor

→ depends on **physical dimension** and **construction** of inductor

$$L = \frac{N^2 \mu A}{l}$$

N : number of turns

l : length of coil

A : cross-section area

μ : permeability of the core



Toroidal inductor



Solenoidal
wound inductor



Inductor

+ Inductor classification:

→ Fixed – Variable inductance

→ Linear – Non-linear inductors

→ Core material: iron, plastic, air,...

Capacitors and Inductors


6.4. Inductors

+ Power: $p = vi = \left(L \frac{di}{dt} \right) i$

+ Energy: $w = \int_{-\infty}^t p dt = \int_{-\infty}^t \left(L \frac{di}{dt} \right) i dt \rightarrow w = \frac{1}{2} Li^2$

+ Note:

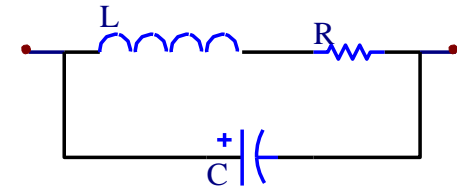- inductor acts like a *short circuit to DC*
- current through an inductor *cannot change instantaneously*
- ideal inductor does *not dissipate energy*
- Non-ideal inductor:
 - very small winding resistance
 - very small winding capacitance, except at high frequencies



Circuit model for
a practical inductor

Capacitors and Inductors

6.4. Inductors

+ **Example 5:** Find the current through a 5H inductor and the energy stored within $0 < t < 5\text{s}$, if its voltage is:

$$v(t) = \begin{cases} 30t^2 & t > 0 \\ 0 & t \leq 0 \end{cases}$$

The current through the inductor

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0) = \frac{1}{5} \int_0^t 30t^2 dt + 0 = 2t^3 \text{ A}$$

The power delivered to the inductor:

$$p = vi = 60t^5 \text{ W}$$

The energy stored in the inductor:

$$w = \int_0^t p dt = \int_0^5 60t^5 dt = 60 \left. \frac{t^6}{6} \right|_0^5 = 156.25 \text{ kJ}$$

Or it could be calculated by using equation:

$$w = \frac{1}{2} Li^2 = \frac{1}{2} 5 (2.5^3)^2 = 156.25 \text{ kJ}$$

6

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Capacitors and Inductors

6.4. Inductors

+ **Example 6:** Find i , v_C , i_L , energy stored in the capacitor and inductor under DC condition

Under DC source: capacitor \rightarrow open circuit, inductor \rightarrow short circuit


$$i = i_L = \frac{12}{R_1 + R_3} = \frac{12}{1+5} = 2A \rightarrow v_C = R_3 i = 10V$$

Energy stored in the capacitor:

$$w_C = \frac{1}{2} C v_C^2 = \frac{1}{2} \cdot 1 \cdot 10^2 = 50J$$

Energy stored in the inductor:
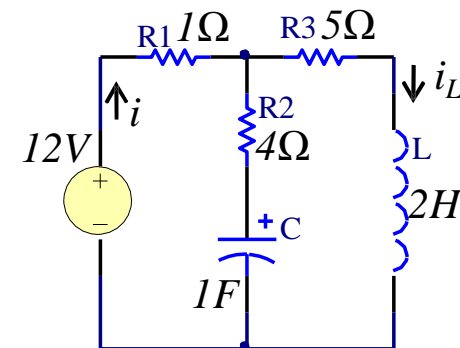
$$w_L = \frac{1}{2} L i_L^2 = \frac{1}{2} \cdot 2 \cdot 2^2 = 4J$$



Capacitors and Inductors



6.5. Series and Parallel Inductors

+ N inductors connected in series:

$$v = v_1 + v_2 + \dots + v_N$$

$$\rightarrow v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_N \frac{di}{dt} = \left(\sum_{k=1}^N L_k \right) \frac{di}{dt} = L_{eq} \frac{di}{dt}$$

$$L_{eq} = L_1 + L_2 + \dots + L_N$$

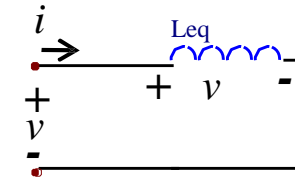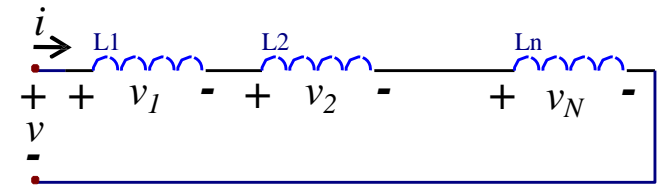

+ Equivalent inductance of series-connected inductors: sum of the individual inductances

6

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Capacitors and Inductors


6.5. Series and Parallel Inductors

+ N inductors connected in parallel:

$$i = i_1 + i_2 + \dots + i_N$$

$$\rightarrow i = \frac{1}{L_1} \int_{t_0}^t v dt + i_1(t_0) + \dots + \frac{1}{L_N} \int_{t_0}^t v dt + i_N(t_0) = \left(\sum_{k=1}^N \frac{1}{L_k} \right) \int_{t_0}^t v dt + \sum_{k=1}^N i_k(t_0)$$
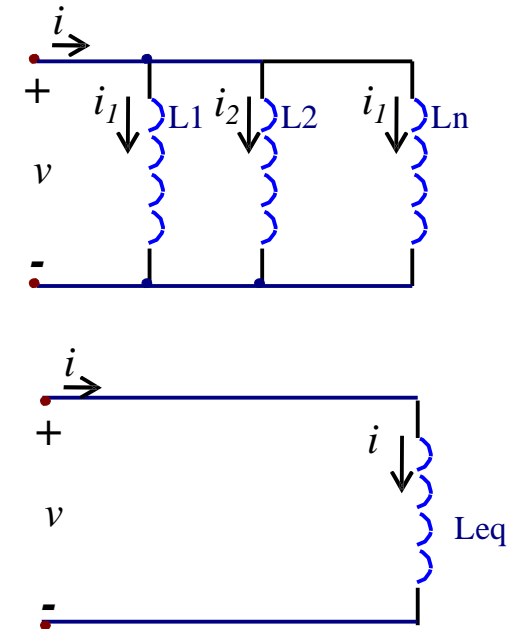
$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}}$$



+ Equivalent inductance of parallel-connected inductors: reciprocal of the sum of the reciprocals of the individual inductances

Capacitors and Inductors

6.5. Series and Parallel Inductors

+ Example 7: Find $i_2(0)$, $v(t)$, $v_1(t)$, $v_2(t)$, $i_2(t)$, $i_n(t)$ if $i_1(t) = 4.(2 - e^{-10t})$ mA and $i_n(0) = -1$ mA

Equivalent inductance is:
$$L_{eq} = L_1 + \frac{L_2 \cdot L_N}{L_2 + L_N} = 2 + \frac{4 \cdot 12}{4 + 12} = 5H$$


So:
$$v(t) = L_{eq} \frac{di_1}{dt} = 5.(-4)(-10)e^{-10t} = 200e^{-10t}V$$

From:
$$i_1(t) = 4(2 - e^{-10t})mA \rightarrow i_1(0) = 4mA$$

$$i_1 = i_2 + i_N \rightarrow i_2(0) = i_1(0) - i_N(0) = 4 - (-1) = 5mA$$

$$v_1(t) = L_1 \frac{di_1}{dt} = 2.(-4).(-10e^{-10t}) = 80e^{-10t}mV$$
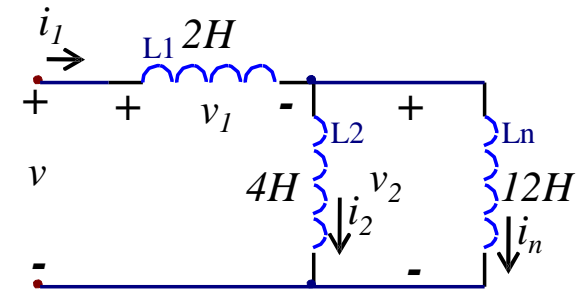
$$v_2(t) = v(t) - v_1(t) = 200e^{-10t} - 80e^{-10t} = 120e^{-10t}mV$$



Capacitors and Inductors

6.5. Series and Parallel Inductors

+ Example 7: Find $i_2(0)$, $v(t)$, $v_1(t)$, $v_2(t)$, $i_2(t)$, $i_n(t)$ if $i_1(t) = 4.(2 - e^{-10t})$ mA and $i_n(0) = -1$ mA

Current through L_2 is:


$$i_2(t) = \frac{1}{L_2} \int_0^t v_2 dt + i_2(0) = \frac{1}{4} \int_0^t 120e^{-10t} dt + 5 = 8 - 3e^{-10t} \text{ mA}$$

Current through L_N is:

$$i_N(t) = \frac{1}{L_N} \int_0^t v_2 dt + i_N(0) = \frac{1}{12} \int_0^t 120e^{-10t} dt - 1 = -e^{-10t} \text{ mA}$$

Or by applying the KCL we obtain the same result:
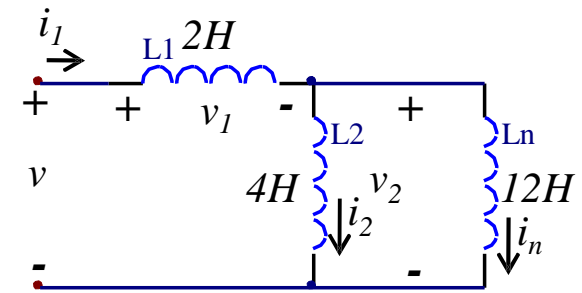
$$i_N(t) = i_1(t) - i_2(t) = -e^{-10t} \text{ mA}$$



Capacitors and Inductors

6.5. Series and Parallel Inductors

+ **Example 8:** Find $i_2(0)$, $i_2(t)$, $i(t)$, $v(t)$, $v_1(t)$, $v_2(t)$ if $i_1(t) = 0.6.e^{-2t}$

and $i(0) = 1.4A$


$$i = i_1 + i_2 \rightarrow i(0) = i_1(0) + i_2(0) \rightarrow i_2(0) = i(0) - i_1(0) = 1.4 - 0.6 = 0.8A$$

$$v_1(t) = L_1 \frac{di_1}{dt} = -4.8e^{-2t}V = v_2(t)$$

$$\rightarrow i_2(t) = \frac{1}{L_2} \int_0^t v_2 dt + i_2(0) = \frac{1}{4} \int_0^t (-4.8)e^{-2t} dt + 0.8 = 0.6e^{-2t} + 0.2 \quad \rightarrow i(t) = i_1(t) + i_2(t) = 1.2e^{-2t} + 0.2A$$

$$\rightarrow v_2(t) = L_n \frac{di}{dt} = 12 \cdot 1.2 \cdot (-2)e^{-2t} = -28.8e^{-2t}V$$
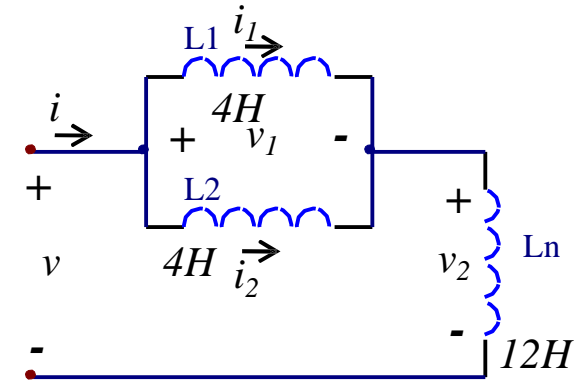
$$\rightarrow v(t) = v_1(t) + v_2(t) = -33.6e^{-2t}V$$



Capacitors and Inductors

6.6. Applications

+ Circuit elements (R, C) are available in either discrete form or integrated circuit (IC) form, but inductance are difficult to produce on IC substrates

+ Inductor are used in applications:

- Telephone circuits, radio, TV receivers
- Power supplies, electric motors, microphones, loudspeakers
- Relays, delays, sensing devices

+ Capacitors and inductors possess 03 special properties:

- Useful for generating a current or voltage in short period of time (DC circuit)
- Useful for suppression and converting pulsating DC voltage into relatively smooth DC voltage (DC circuit)
- Useful for frequency discrimination (AC circuit)

+ Capacitors + Op amp: → Integrator and Differentiator

Capacitors and Inductors

6.6. Applications

6.6.1. Integrator


+ **Integrator** : an op amp circuit whose output is proportional to the integral of the input signal

$$i_R = i_C \rightarrow \frac{v_i}{R} = -C \frac{dv_0}{dt} \rightarrow dv_0 = -\frac{1}{RC} v_i dt$$

$$\rightarrow v_0(t) = -\frac{1}{RC} \int_0^t v_i(t) dt$$

+ **In practice**, note that:

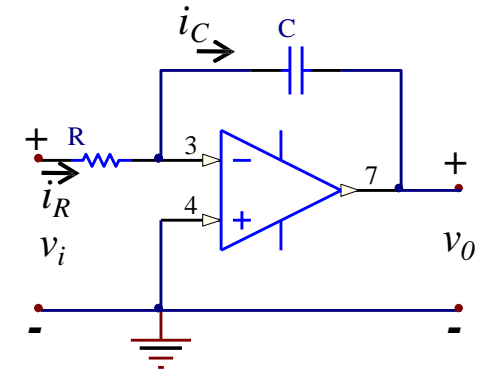- Op amp integrator \rightarrow requires a *feedback resistor to reduce DC gain and prevent saturation*
- Op amp integrator operates within the *linear range* \rightarrow does not saturate



6

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Capacitors and Inductors

6.6. Applications

6.6.1. Integrator


+ **Example 9:** Find v_o in the op amp circuit if $v_1 = 10.\cos 2t$ (mV) and $v_2 = 0.5t$ (mV)

We have a summing integrator:

$$v_o = -\frac{1}{R_1 C} \int V_1 dt - \frac{1}{R_2 C} \int V_2 dt$$

$$v_o = -\frac{1}{3 \cdot 10^6 \cdot 2 \cdot 10^{-6}} \int_0^t 10 \cos 2t dt - \frac{1}{100 \cdot 10^3 \cdot 2 \cdot 10^{-6}} \int_0^t 0.5t dt$$
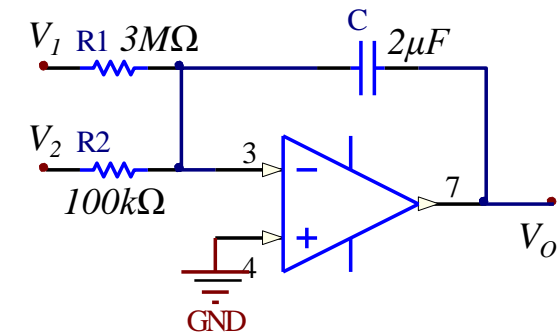
$$v_o = -\frac{10}{6.2} \sin 2t - \frac{1}{0.2 \times 2} 0.5t^2 = -0.833 \sin 2t - 1.25t^2 \text{ mV}$$



6

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Capacitors and Inductors


6.6. Applications

6.6.2. Differentiator

+ **Differentiator**: an op amp circuit whose output is proportional to the rate of change of the inputs signal

$$i_C = i_R \rightarrow C \frac{dv_i}{dt} = -\frac{v_o}{R}$$

$$v_o(t) = -RC \frac{dv_i}{dt}$$

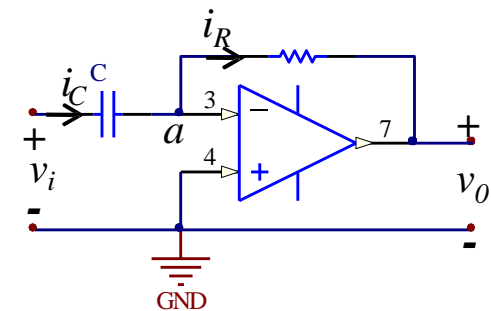

+ **Note that:**

- Differentiator circuits → *electronically unstable* because any electrical noise within the circuit is exaggerated by the differentiator
- Differentiator circuits → **not** as useful and popular as integrators

Capacitors and Inductors

6.6. Applications

6.6.2. Differentiator

+ **Example 10:** Find the output voltage with the given input. Take $v_0 = 0$ at $t = 0$

For $0 < t < 4\text{ms}$ or $4 < t < 8\text{ms}$, the input voltage is:

$$v_i = \begin{cases} 2t & 0 < t < 2\text{ms} & 4 < t < 6\text{ms} \\ 8 - 2t & 2 < t < 4\text{ms} & 6 < t < 8\text{ms} \end{cases}$$

This is a differentiator with $RC = 5 \times 10^3 \times 0.2 \times 10^{-6} = 10^{-3}$

$$v_0 = -RC \frac{dv_i}{dt} = \begin{cases} -2\text{mV} & 0 < t < 2\text{ms} & 4 < t < 6\text{ms} \\ 2\text{mV} & 2 < t < 4\text{ms} & 6 < t < 8\text{ms} \end{cases}$$

