

# Fundamentals of Electric Circuits

## DC Circuits

### Chapter 4. Circuit Theorems

- 4.1. Introduction
- 4.2. Linearity property
- 4.3. Superposition
- 4.4. Source transformation
- 4.5. Thevenin's Theorem
- 4.6. Norton's theorem
- 4.7. Maximum power transfer

# Circuit Theorems

## 4.1. Introduction

+ To reduce the number of equations:

→ The first way: Circuit variable transformations (node voltage and mesh current methods)

→ The second way: Circuit topology transformations (Thevenin's theorem, Norton's theorem,...)

+ In this chapter:

- Concept of circuit linearity
- Circuit theorems
- Concept of superposition, source transformation, maximum power transfer

# Circuit Theorems

## 4.2. Linearity property

+ **Linearity** → property of an element describing a linear relationship between cause (input, excitation) and effect (output, response)

+ Linearity property combines:

*Homogeneity (scaling) property:*  $v = iR \rightarrow kiR = kv$

*Additivity property:*

$$\begin{aligned} v_1 &= i_1 R \\ v_2 &= i_2 R \end{aligned} \rightarrow v = (i_1 + i_2)R = i_1 R + i_2 R = v_1 + v_2$$

+ A **linear circuit**: its output is linearly related (or directly proportional) to its input

+ A linear circuit consists of only linear elements, linear dependent sources, and independent sources

## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems

## 4.2. Linearity property

+ **Example 1:** find  $i_0$  when  $v_s = 12V$  and  $v_s = 24V$

Apply the mesh current method:


$$v_x = R_2 i_1 = 2i_1$$

$$\begin{cases} (R_1 + R_2 + R_3)i_1 - R_3 i_2 + v_s = 0 \\ -R_3 i_1 + (R_3 + R_4 + R_5)i_2 - v_s - 3v_x = 0 \end{cases} \rightarrow \begin{cases} 12i_1 - 4i_2 + v_s = 0 \\ -10i_1 + 16i_2 - v_s = 0 \end{cases} \rightarrow \begin{cases} i_1 = -6i_2 \\ i_2 = \frac{v_s}{76} \end{cases}$$

When  $v_s = 12V$ :  $i_0 = i_2 = \frac{12}{76} = 0.158A$

When  $v_s = 24V$ :  $i_0 = i_2 = \frac{24}{76} = 0.316A = 2 \times 0.158A$

Prove the linearity of this circuit

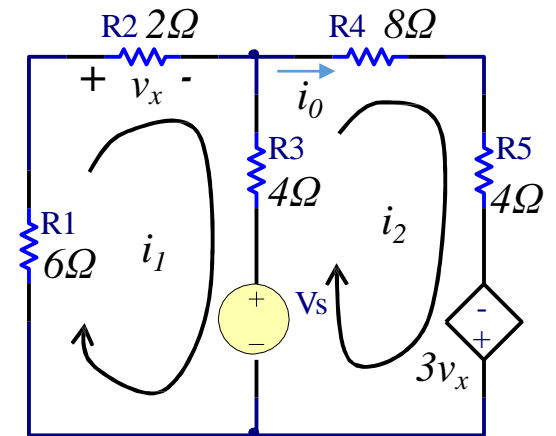

# Circuit Theorems

## 4.3. Superposition

+ Linear circuits → satisfy superposition principle

The **superposition** principle states that the voltage across (or current through) an element *in a linear circuit* is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone

+ So: if circuit has two or more independent sources → several possible ways to determine the value of a specific variable (voltage, current)

- **Direct approach:** let all sources acting simultaneously → applying nodal or mesh analysis to analyze the given circuit
- **Superposition approach:** determine the contribution of each independent source to the variable, and then add them up (applying NA or MA for each sub-problem)

+ Superposition: applicable in any linear system

# Circuit Theorems

## 4.3. Superposition

+ To apply superposition principle

- Turn off all **independent sources** except one source (*dependent sources are left intact*):
  - Replace **voltage source** by **short circuit**
  - Replace **current source** by **open circuit**
- Find the output (voltage or/and current) due to that active source (using nodal or mesh analysis)
- Repeat two above steps for each of the other independent sources
- Find the total contribution by adding algebraically all the contributions due to the independent sources

## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems

## 4.3. Superposition

+ **Example 2:** Using the superposition theorem, find  $v_0$

Let:  $v_0 = v_{01} + v_{02}$

To obtain  $v_{01}$ , set the current source to zero

Apply KVL to the obtained loop, we have

$$(3+5+2)i = 20 \rightarrow i = 2A \rightarrow v_{01} = 2 \cdot 2 = 4V$$

To obtain  $v_{02}$ , set the voltage source to zero




Apply KCL to node A, we have

$$\frac{v_A}{R_1 + R_2} + \frac{v_A}{R_3} = 8 \rightarrow \frac{2}{5}v_A = 8 \rightarrow v_A = 20V \quad v_{02} = R_1 i = R_1 \frac{v_A}{R_1 + R_2} = 8V$$

Or applying current division:  $i_{R_1} = \frac{8}{2+3+5} \cdot 5 = 4A \rightarrow v_{02} = R_1 i_{R_1} = 2 \cdot 4 = 8V$

Finally, calculate  $v_0$ :

$$v_0 = v_{01} + v_{02} = 4 + 8 = 12V$$

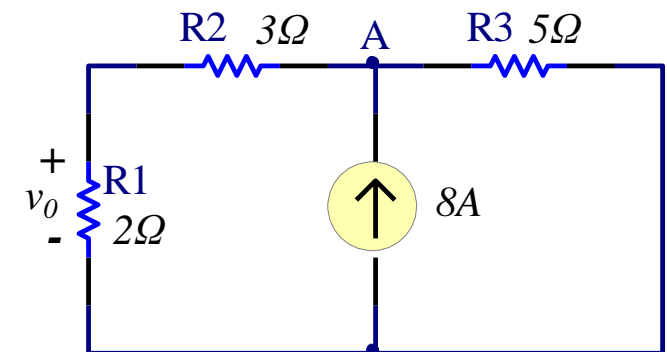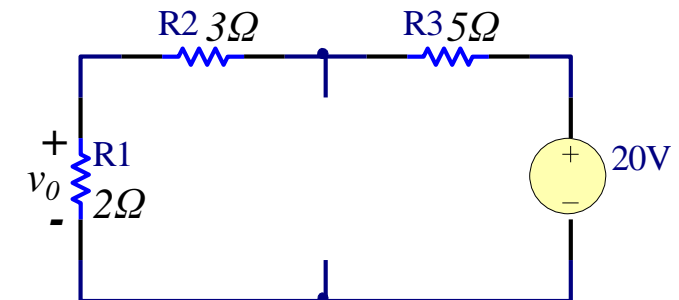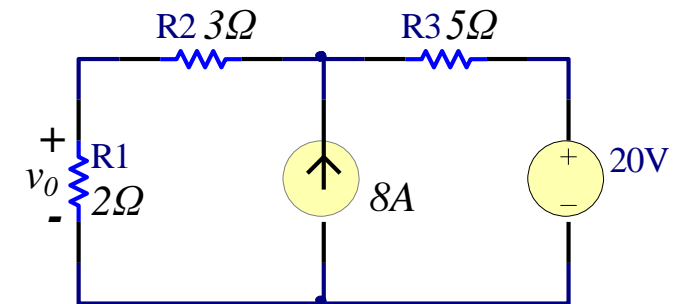

# 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

### Circuit Theorems

#### 4.3. Superposition

+ **Example 3:** Using the superposition theorem, find  $i_0$

There is a dependent source, so we left intact



Let:  $i_0 = i_{01} + i_{02}$

To obtain  $i_{01}$ , set the voltage source 20V to zero

Apply mesh current method:

$$\left\{ \begin{array}{ll} i_1 = 4A & \leftarrow \text{Loop 1} \\ -R_1 i_1 + (R_1 + R_2 + R_3) i_2 - R_3 i_3 - 5i_{01} = 0 & \leftarrow \text{Loop 2} \\ -R_2 i_1 - R_3 i_2 + (R_2 + R_3 + R_5) i_3 + 5i_{01} = 0 & \leftarrow \text{Loop 3} \\ i_3 = i_1 - i_{01} & \leftarrow \text{KCL at node 0} \end{array} \right.$$

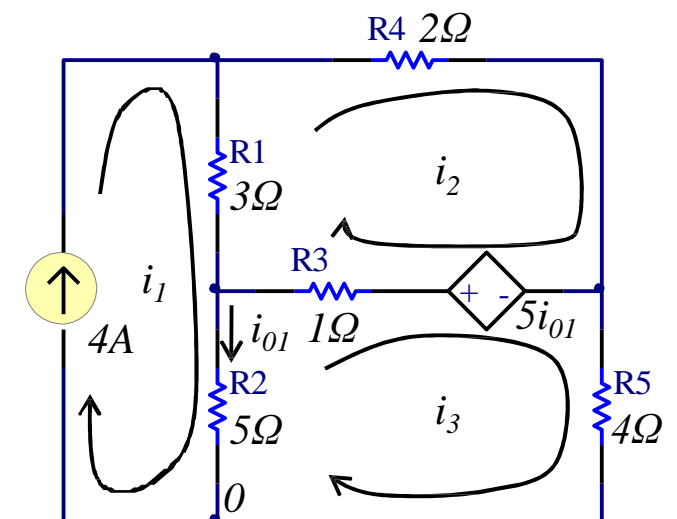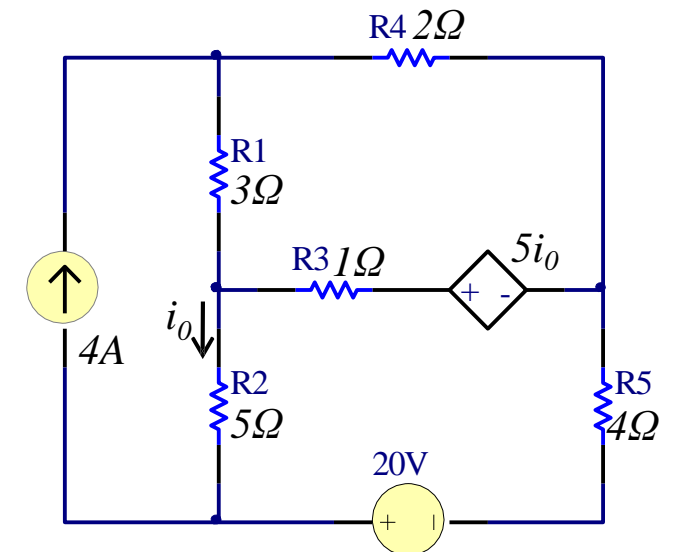Solve this equation system:  $i_{01} = 3.06A$





## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems

## 4.3. Superposition

+ **Example 3:** Using the superposition theorem, find  $i_0$

There is a dependent source, so we left intact

Let:  $i_0 = i_{01} + i_{02}$


To obtain  $i_{02}$ , set the current source 4A to zero

Apply mesh current method:

$$\begin{cases} (R_1 + R_3 + R_4)i_4 - R_3i_5 = 5i_{02} \\ -R_3i_4 + (R_2 + R_3 + R_5)i_5 = 20 - 5i_{02} \end{cases} \rightarrow \begin{cases} 6i_4 - i_5 = -5i_{02} \\ -i_4 + 10i_5 = 20 + 5i_{02} \end{cases}$$

Solve this equation system:  $i_{02} = -i_5 = -3.53A$

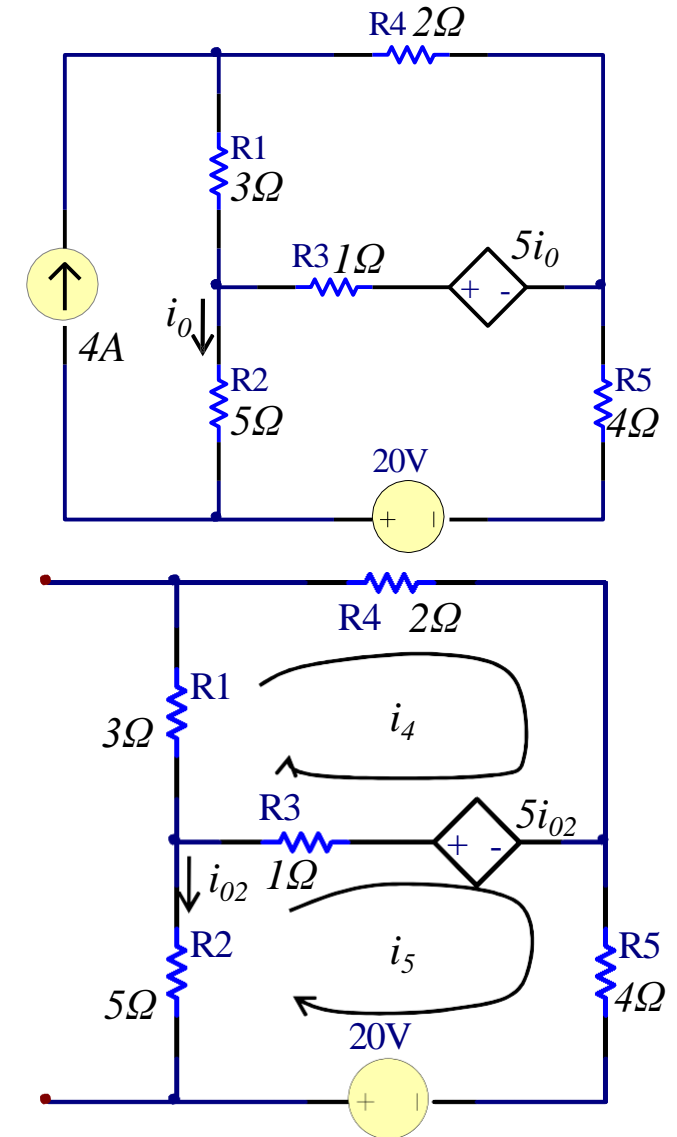Finally, calculate  $i_0$ :  $i_0 = i_{01} + i_{02} = 3.06 - 3.53 = -0.47A$



# 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

### Circuit Theorems

#### 4.3. Superposition

+ **Example 4:** Using the superposition theorem, find  $i$

Let:  $i = i_1 + i_2 + i_3$




Turn off 3A source, 24V source to calculate  $i_1$  :

$$i_1 = \frac{12}{[R_1 // (R_2 + R_4)] + R_3} = \frac{12}{6} = 2A$$

Turn off 3A source, 12V source to calculate  $i_2$  :

$$i_{R4} = \frac{24}{(R_1 // R_3) + R_2 + R_4} = \frac{24}{42} = 1.75A$$
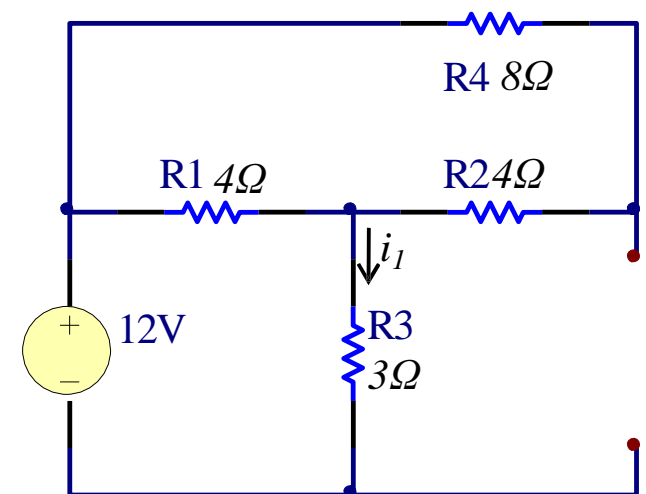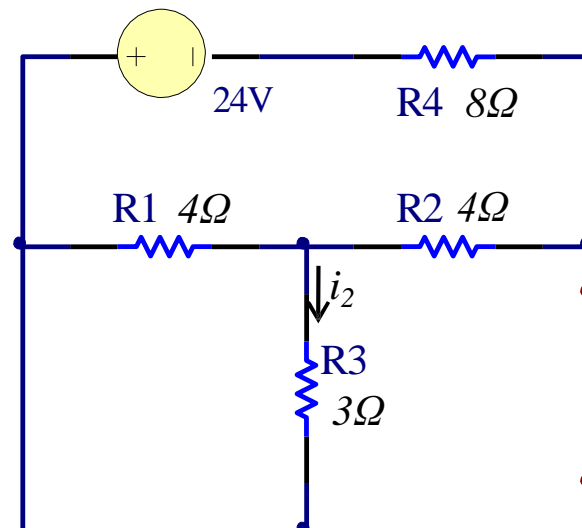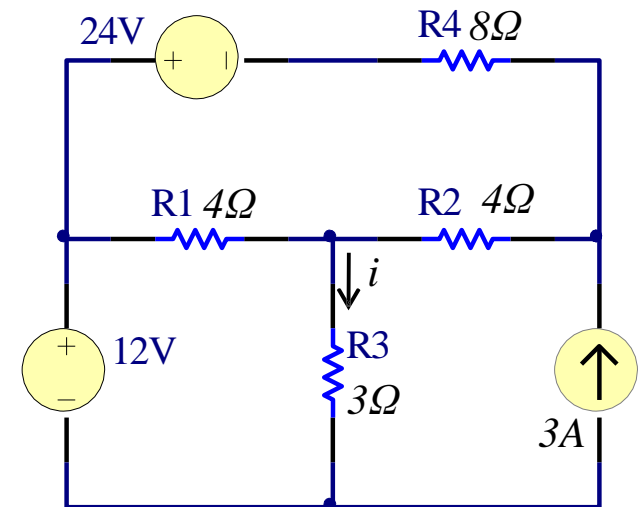
$$i_2 = i_{R4} \cdot \frac{-R_1}{R_1 + R_3} = -1A$$



## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems

## 4.3. Superposition

+ **Example 4:** Using the superposition theorem, find  $i$

Let:  $i = i_1 + i_2 + i_3$

Turn off 12V source, 24V source to calculate  $i_3$  :



Apply node voltage method, we have

$$\begin{cases} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) v_1 - \frac{1}{R_2} v_2 = 0 \\ -\frac{1}{R_2} v_1 + \left( \frac{1}{R_2} + \frac{1}{R_4} \right) v_2 = 3 \end{cases} \rightarrow \begin{cases} 3.33v_1 - v_2 = 0 \\ -2v_1 + 3v_2 = 24 \end{cases}$$

Solving this set of equations gives:

$$v_1 = 3V \rightarrow i_3 = 1A$$

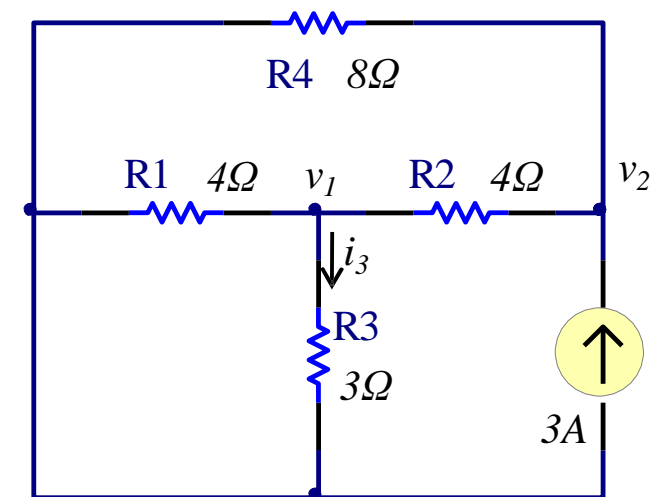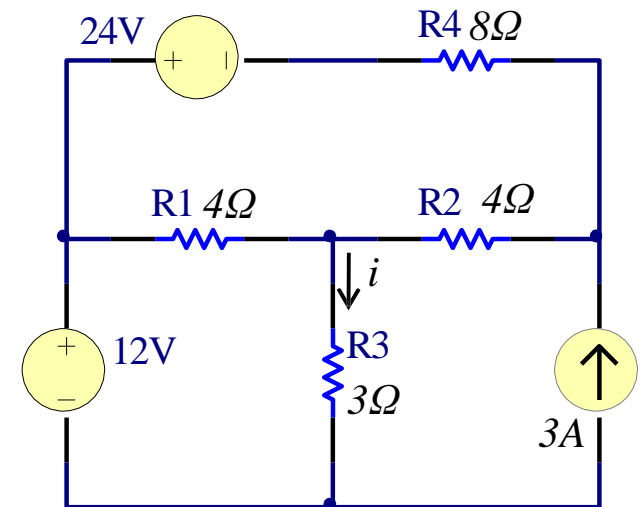Thus:  $i = i_1 + i_2 + i_3 = 2 - 1 + 1 = 2A$



## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems

## 4.3. Superposition

+ **Example 5:** Using the superposition theorem, find  $i$

Let:  $i = i_1 + i_2 + i_3$

Turn off 4A source, 12V source to calculate  $i_1$  :

$$i_1 = \frac{16}{R_1 + R_2 + R_3} = 1A$$




Turn off 16V source, 12V source to calculate  $i_2$  :

$$i_2 = \frac{4}{R_1 + R_2 + R_3} R_2 = 0.5A$$

Turn off 16V source, 4A source to calculate  $i_3$  :

$$i_3 = \frac{-12}{R_1 + R_2 + R_3} = -0.75A$$

Thus:  $i = 1 + 0.5 - 0.75 = 0.75A$

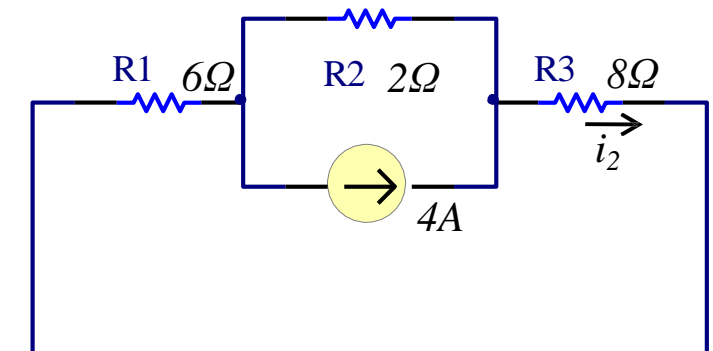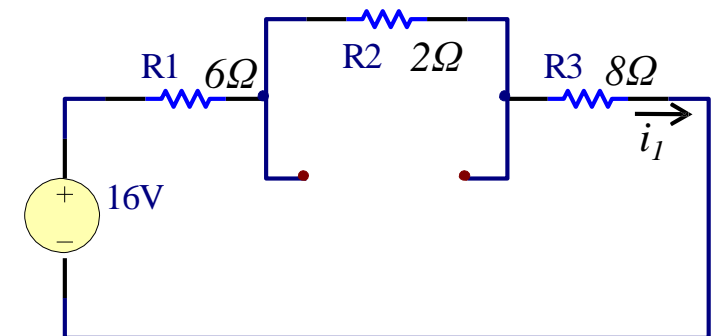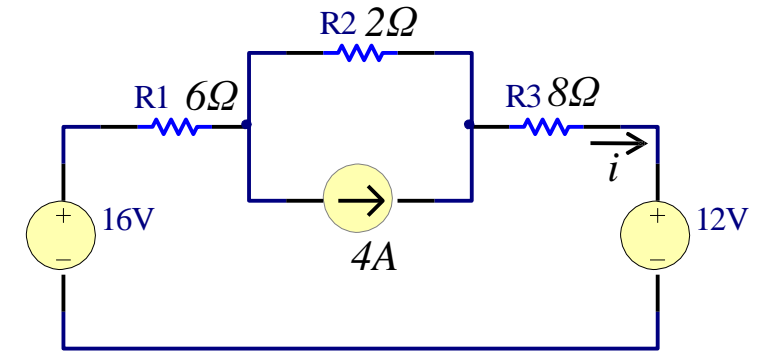

# Circuit Theorems

## 4.4. Source transformation

+ **Source transformation** → process of replacing a voltage source  $v_s$  in series with a resistor  $R$  by a current source  $i_s$  in parallel with a resistor  $R$ , or vice versa

+ **Source transformation** → to simplify circuits that bases on the *concept of equivalence*

**Note:** similar to series-parallel combination and wye-delta transformation → circuit structure equivalent transformation


+ **Equivalent circuit** →  $v - i$  characteristics are identical with the original circuit

## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems

## 4.4. Source transformation

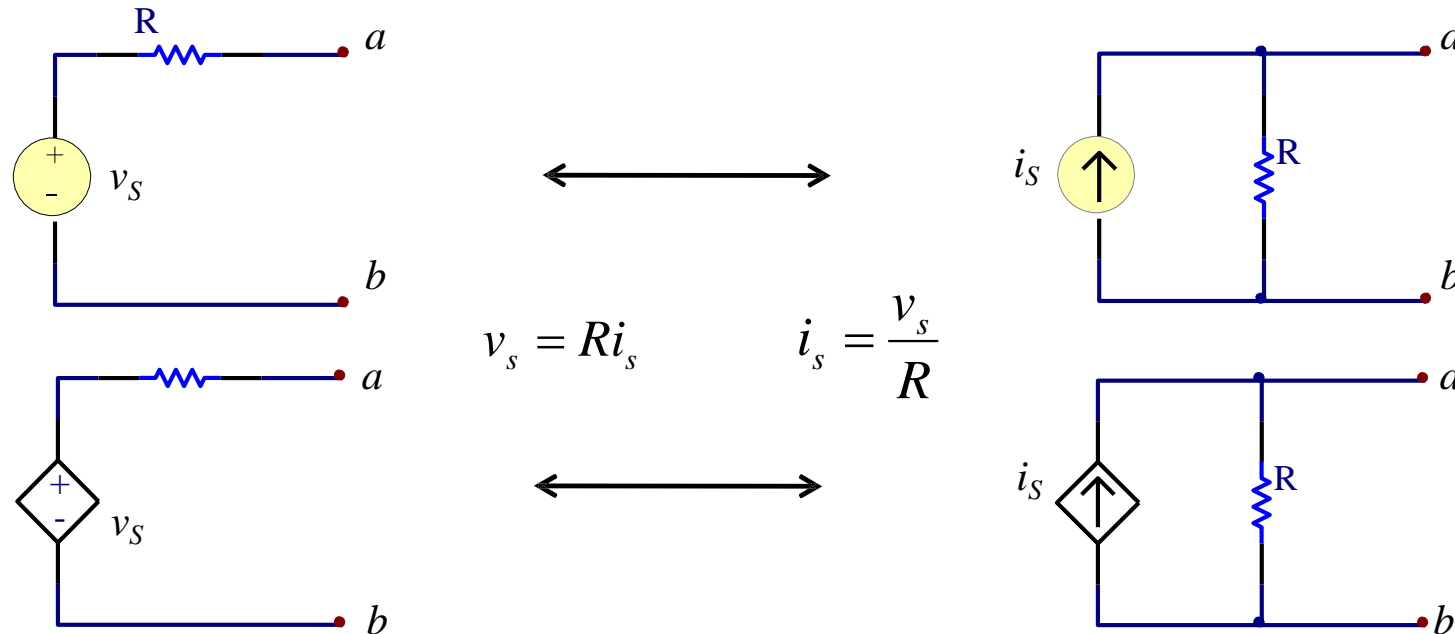**Note:**

- arrow of the current source is directed toward the positive terminal of the voltage source
- source transformation is **not possible** when  $R = 0$  (ideal voltage source) or  $R = \infty$  (ideal current source)
- One port network transformation


## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits


## Circuit Theorems
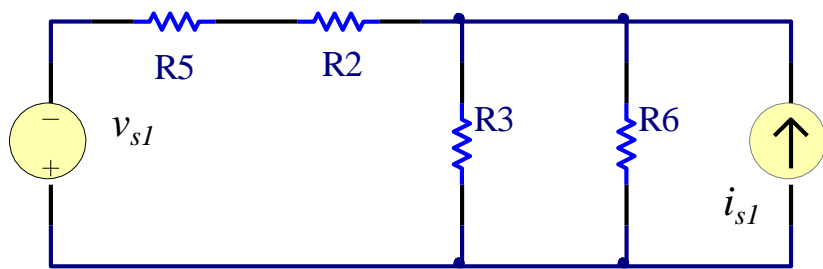
## 4.4. Source transformation


+ **Example 6:** Use source transformation to find  $v_0$



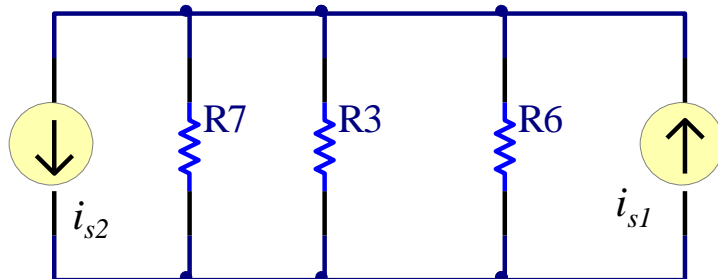
$$\begin{cases} i_{s2} = \frac{v_{s1}}{R_5 + R_2} = \frac{12}{6} = 2A \\ R_7 = R_5 + R_2 = 6\Omega \end{cases}$$


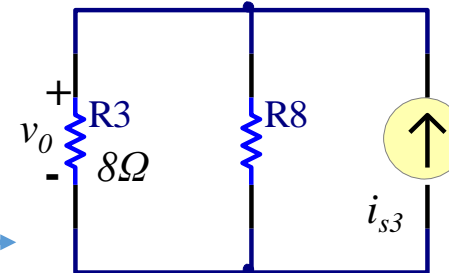
$$\begin{cases} i_{s3} = i_{s1} - i_{s2} = 2A \\ R_8 = R_6 // R_7 = 2\Omega \end{cases}$$


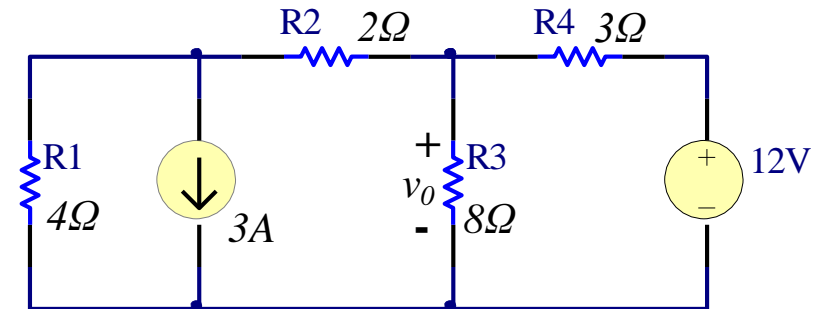
$$\begin{cases} v_{s1} = i_{s1} R_1 = 3.4 = 12V \\ R_5 = R_1 = 4\Omega \\ i_{s1} = \frac{v_s}{R_4} = \frac{12}{3} = 4A \\ R_6 = R_4 = 3\Omega \end{cases}$$



$$v_0 = i_{s3} \frac{R_3 R_8}{R_3 + R_8} = 2 \frac{8.2}{8 + 2} = 3.2V$$


# 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

### Circuit Theorems
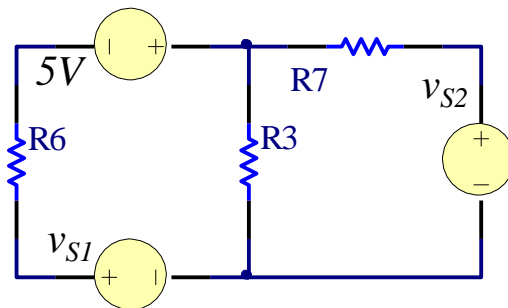
#### 4.4. Source transformation


+ **Example 7:** Use source transformation to find  $i_0$




$$\begin{cases} R_6 = R_1 // R_2 = 2\Omega \\ v_{s1} = 5R_6 = 10V \end{cases}$$

$$\begin{cases} R_7 = R_4 + R_5 = 5\Omega \\ v_{s2} = 3R_7 = 15V \end{cases}$$

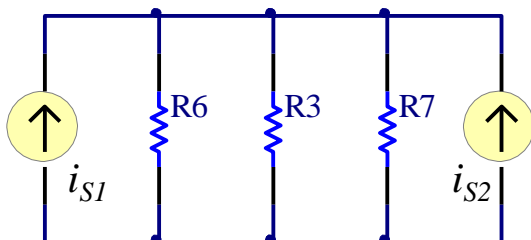
$$\begin{cases} i_{s1} = \frac{5 + v_{s1}}{R_6} = 7.5A \\ i_{s2} = v_{s2} / R_7 = 3A \end{cases}$$


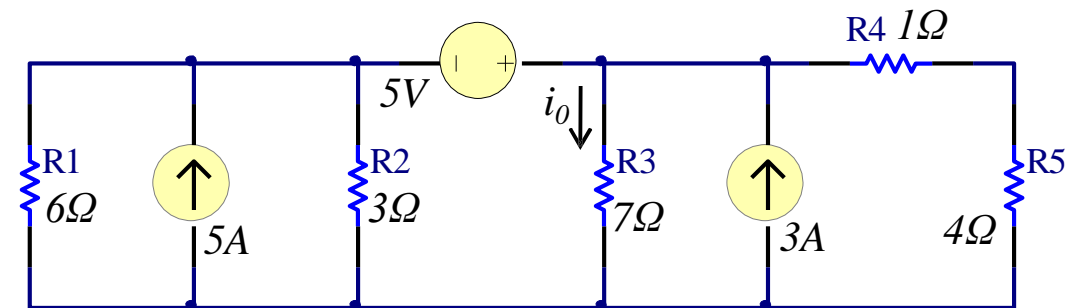
$$\begin{cases} i_{s3} = i_{s1} + i_{s2} = 10.5A \\ R_8 = R_6 // R_7 = 1.43\Omega \end{cases}$$


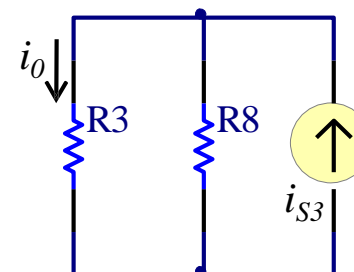
$$i_0 = i_{s3} \frac{R_8}{R_3 + R_8} = 1.78A$$






## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits


## Circuit Theorems
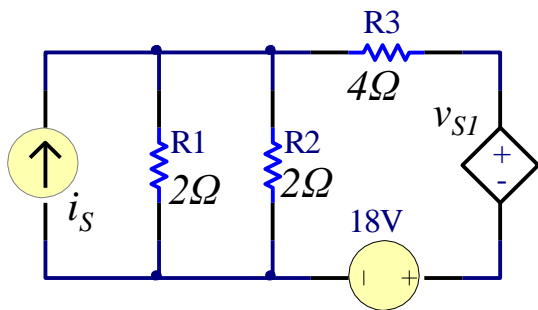
## 4.4. Source transformation

+ **Example 8:** Use source transformation to find  $v_x$



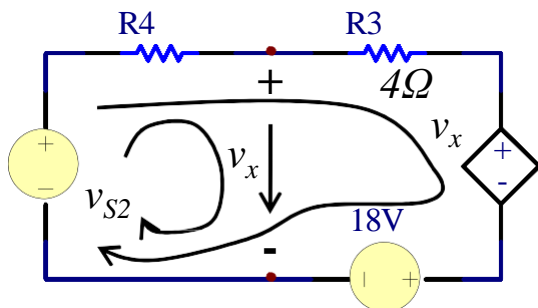
$$\begin{cases} R_4 = R_1 // R_2 = 1\Omega \\ v_{s2} = i_{s2} R_4 = 3V \end{cases}$$



Finally, apply KVL to calculate  $v_x$

$$\begin{cases} (R_3 + R_4)i + v_x + 18 - v_{s2} = 0 \\ R_4 i + v_x = v_{s2} \end{cases} \rightarrow \begin{cases} 5i + v_x = -15 \\ i + v_x = 3 \end{cases}$$
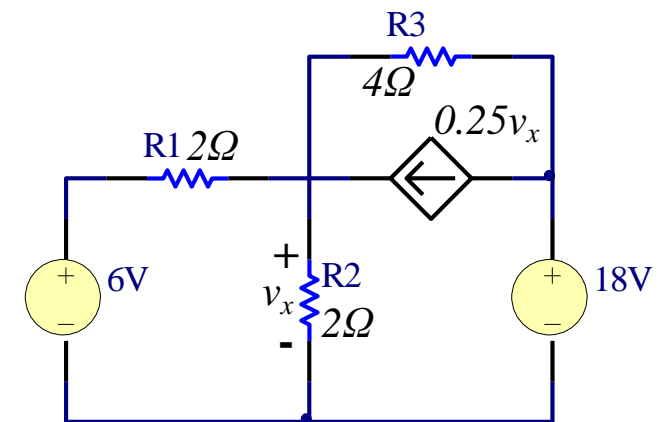
$$\begin{cases} i = -4.5A \\ v_x = 7.5V \end{cases}$$




## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems
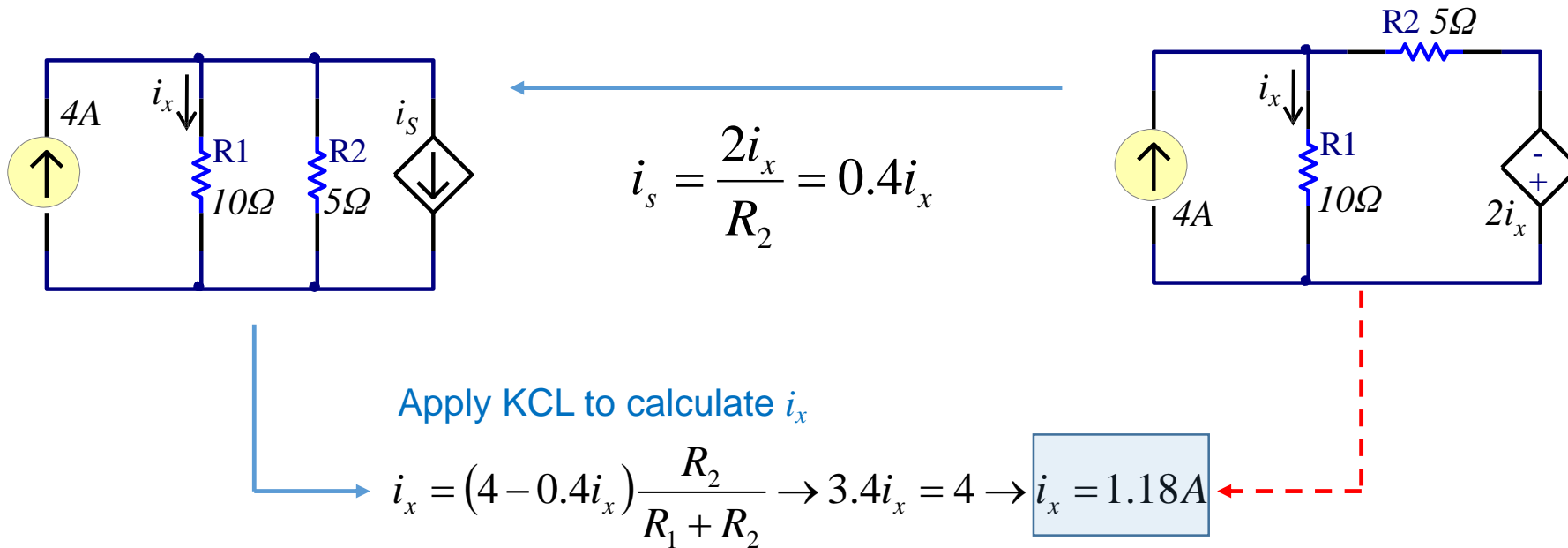
## 4.4. Source transformation

+ **Example 9:** Use source transformation to find  $i_x$




## Circuit Theorems
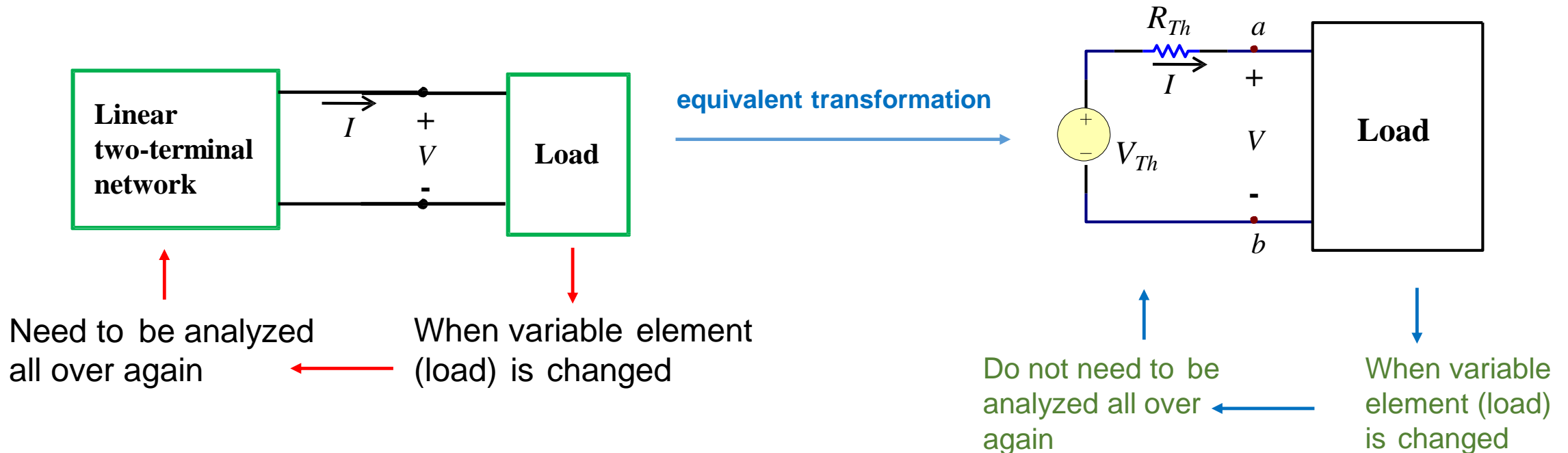
## 4.5. Thevenin's theorem

+ **Thevenin's theorem:** A linear **two terminal network** can be replaced by an **equivalent network** consisting of a voltage source  $V_{Th}$  in series with a resistor  $R_{Th}$  where

- $V_{Th}$  is the *open-circuit voltage* at the terminals
- $R_{Th}$  is the *input or equivalent resistance* at the terminals when all independent sources are turned off




## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems
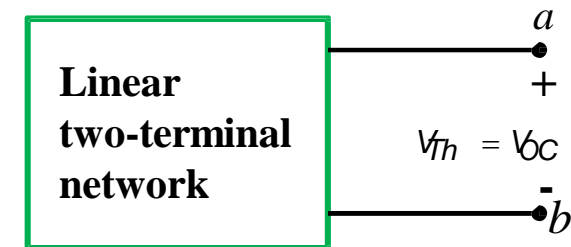
## 4.5. Thevenin's theorem

+ Find  $V_{Th}$ :  $V_{Th}$  is the **open-circuit voltage** across the terminals




+ Find  $R_{Th}$ :


- Network has no dependent sources:

Turn off all independent sources in network

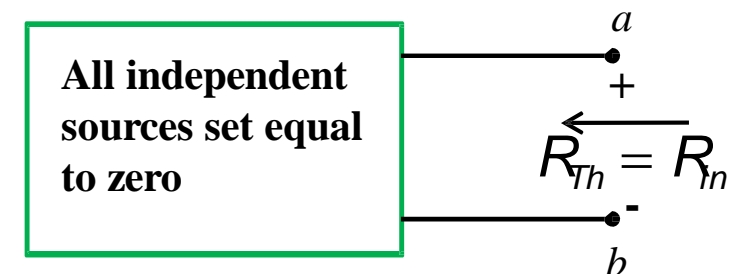$R_{Th} \rightarrow$  input resistance of the network



- Network has dependent sources

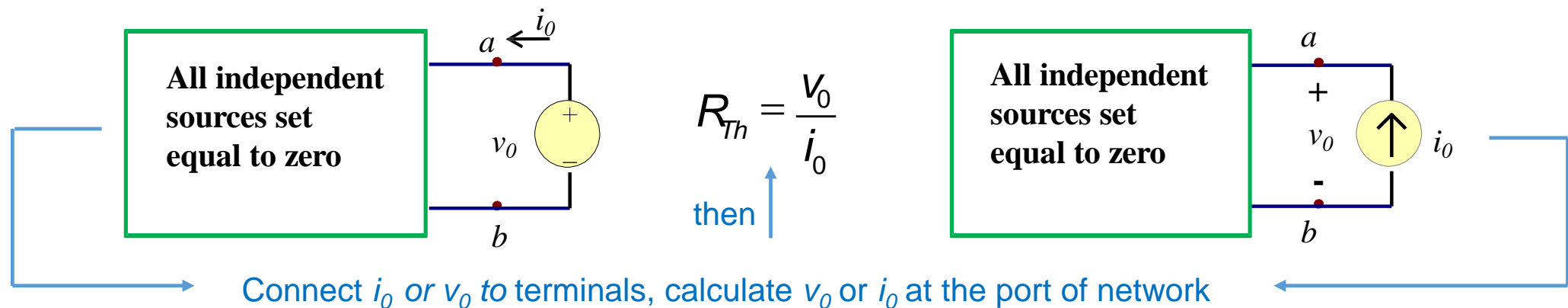


# Circuit Theorems

## 4.5. Thevenin's theorem
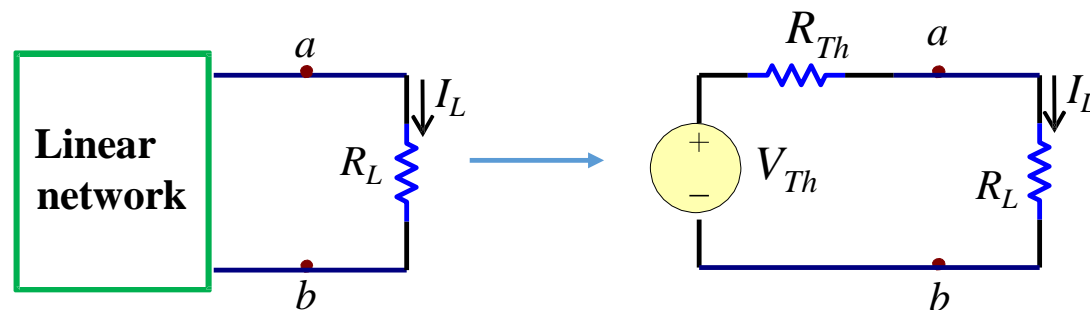
### + Advantages of Thevenin's theorem in circuit analysis

- **Simplify a circuit:** Replace a large circuit by a single independent voltage source and a single resistor
- **Easily to determine** the current and voltage on the load



$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$V_L = R_L I_L = \frac{R_L}{R_{Th} + R_L} V_{Th}$$

## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems

## 4.5. Thevenin's theorem

+ **Example 10:** Find the **Thevenin equivalent network** of the circuit. Find the **current through  $R_L = 6, 16, 36\Omega$**

Calculating  $R_{th}$

$$R_{th} = R_3 + \frac{R_1 R_2}{R_1 + R_2} = 4\Omega$$

Calculating  $V_{th}$

$$\frac{32 - V_{th}}{R_1} - \frac{V_{th}}{R_2} + 2 = 0 \rightarrow V_{th} = 30V$$


Current through  $R_L$

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{30}{4 + R_L}$$

$$R_L = 6\Omega \rightarrow I_L = \frac{30}{4 + 6} = 3A$$

$$R_L = 16\Omega \rightarrow I_L = \frac{30}{4 + 16} = 1.5A$$
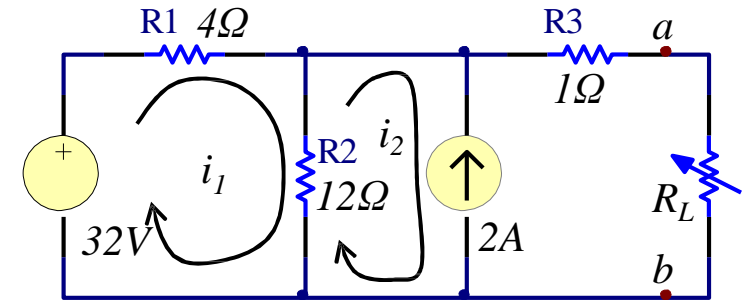
$$R_L = 36\Omega \rightarrow I_L = \frac{30}{4 + 36} = 0.75A$$



## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems

## 4.5. Thevenin's theorem

+ **Example 11**: Find  $i$  using Thevenin theorem

Calculating  $R_{th}$  :


$$R_{th} = \frac{R_3(R_1 + R_2)}{R_1 + R_2 + R_3} = 3\Omega$$

Calculating  $V_{th}$  :

$$\frac{12 - V}{R_1} - \frac{V}{R_2 + R_3} + 2 = 0 \rightarrow V = 15V \rightarrow V_{th} = \frac{V}{R_2 + R_3} R_3 = 6V$$

Current through  $R_4$  :
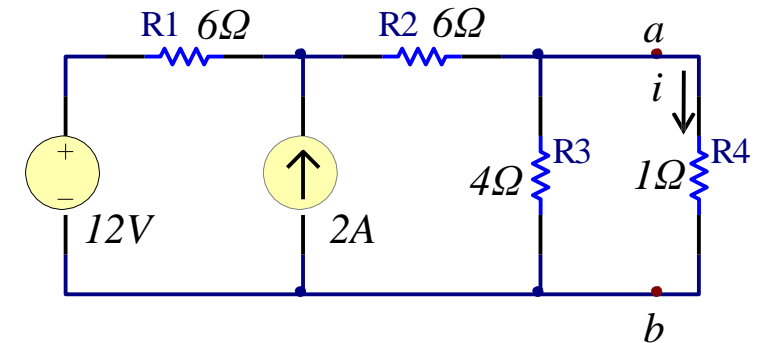
$$i = \frac{V_{th}}{R_{th} + R_4} = \frac{6}{3 + 1} = 1.5A$$



## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems

## 4.5. Thevenin's theorem



+ **Example 12:** Find the **Thevenin equivalent resistor** of the given circuit

Find  $R_{Th}$ :

- **set** the independent source equal to zero
- **leave** the dependent source intact
- **connect** to the terminal a voltage source  $v_0 = 1V$ , and find  $i_0$  through the terminal
- **apply** mesh current method

$$\begin{cases} -2v_x + R_2 i_1 - R_2 i_2 = 0 \\ (R_2 + R_3) i_2 - v_x - R_2 i_1 - R_3 i_3 = 0 \\ (R_3 + R_4) i_3 - R_3 i_2 + v_0 = 0 \end{cases} \xrightarrow{v_x = -4i_2} i_0 = -i_3 = \frac{1}{6} A$$

$$R_{th} = \frac{v_0}{i_0} = 6\Omega$$

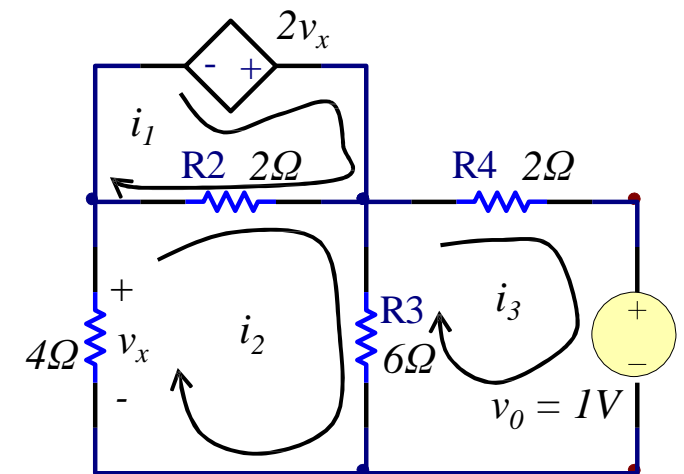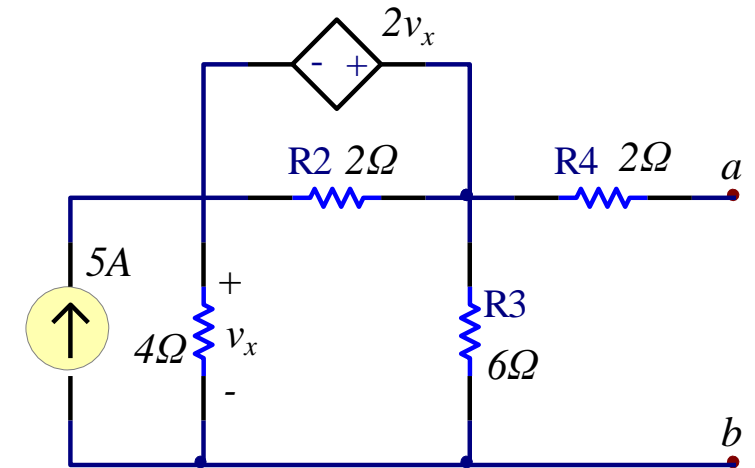



## Circuit Theorems

## 4.5. Thevenin's theorem

+ **Example 13:** Find the Thevenin equivalent resistor of the given circuit

Since the circuit has no independent sources  $\rightarrow V_{Th} = 0$



To find  $R_{th}$ , connect a current source  $i_0$  to terminals

Apply KCL, we have:

$$\begin{cases} i_0 + i_x = 2i_x + \frac{v_0}{R_1} \\ i_x = -\frac{v_0}{R_2} \end{cases} \rightarrow i_0 = \frac{v_0}{R_1} - \frac{v_0}{R_2} = -\frac{v_0}{4} \quad R_{th} = \frac{v_0}{i_0} = -4\Omega$$

+ **Note:**

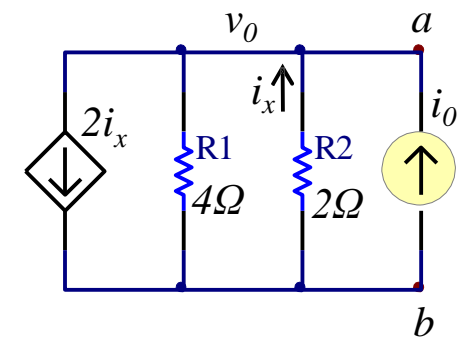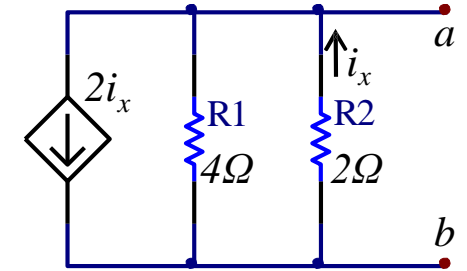- The negative value of  $R_{Th}$   $\rightarrow$  the circuit is supplying power by the dependent source
- This example shows how a dependent source and resistors could be used to simulated negative resistance



## Circuit Theorems

## 4.6. Norton's theorem

**+ Norton's theorem:** A linear two terminal network can be replaced by an equivalent network consisting of a current source  $I_N$  in parallel with a resistor  $R_N$ , where:




- $I_N$  is the short circuit current through the terminals
- $R_N$  is the input or equivalent resistance at the terminals when all independent sources are turned off

$$\begin{aligned} R_N &= R_{Th} \\ I_N &= i_{sc} \end{aligned}$$

**+ Relationship** between Norton's and Thevenin's theorems:

$$I_N = \frac{V_{Th}}{R_{Th}}$$

(Source transformation)

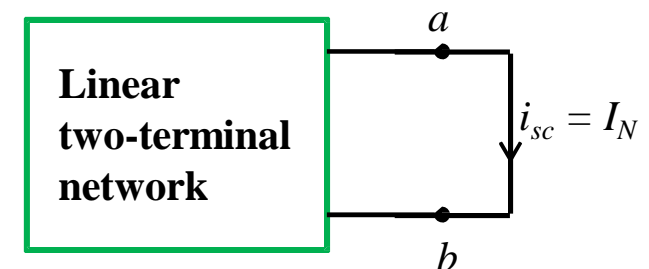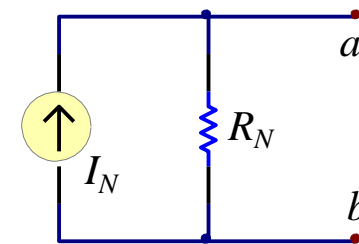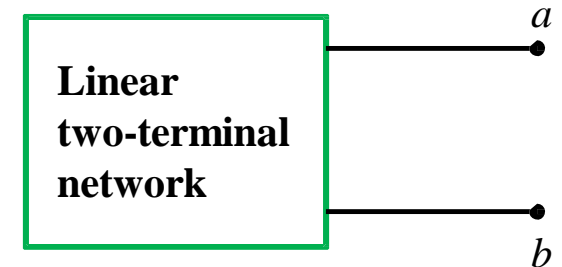

# Circuit Theorems

## 4.6. Norton's theorem

+ **To determine** the Thevenin or Norton equivalent circuit, we need to find

- open-circuit voltage  $v_{oc}$  across terminals  $a$  and  $b$
- short-circuit current  $i_{sc}$  at terminals  $a$  and  $b$
- input or equivalent resistance  $R_{in}$  at terminals  $a$  and  $b$  when all independent sources are turned off

$$V_{Th} = v_{oc} \quad ; \quad I_N = i_{sc} \quad ; \quad R_{Th} = \frac{v_{oc}}{i_{sc}} = R_N$$

# 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

### Circuit Theorems

#### 4.6. Norton's theorem

+ **Example 14:** Find the Norton equivalent circuit for the given circuit

Find  $R_N$  in the same way  $R_{Th}$   $R_N = R_4 // (R_1 + R_2 + R_3) = \frac{5(4+8+8)}{5+4+8+8} = 4\Omega$




Find  $I_N$  by shortening circuit terminals  $a$  and  $b$

$$\begin{cases} i_1 = 2 \\ (R_1 + R_2 + R_3)i_2 - R_1 i_1 = 12 \end{cases} \rightarrow \begin{cases} i_1 = 2 \\ -4i_1 + 20i_2 = 12 \end{cases} \rightarrow i_2 = i_{sc} = I_N = 1A$$

Another way, we can find  $I_N$  by the source transform equation

$$\begin{cases} i_3 = 2 \\ (R_1 + R_2 + R_3 + R_4)i_4 - R_1 i_3 = 12 \end{cases} \rightarrow \begin{cases} i_3 = 2 \\ -4i_3 + 25i_4 = 12 \end{cases}$$
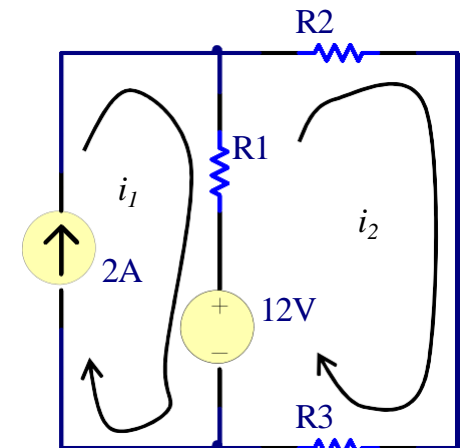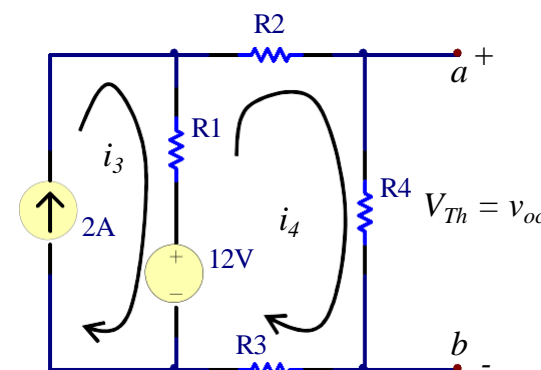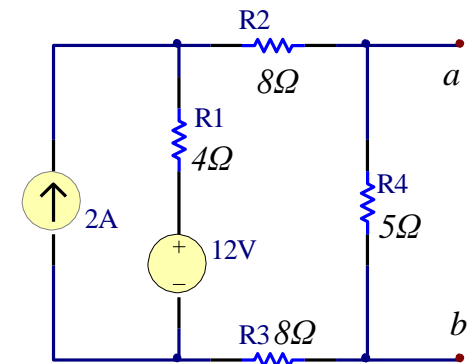
$$V_{Th} = v_{os} = R_4 i_4 = 5 \times 0.8 = 4V \quad I_N = \frac{V_{Th}}{R_{Th}} = 1A$$



## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems



## 4.6. Norton's theorem

+ **Example 15:** Find the Norton equivalent circuit for the given circuit

Find  $R_N$  in the same way  $R_{Th}$   $R_N = R_{Th} = R_3 // (R_1 + R_2) = \frac{6(3+3)}{6+3+3} = 3\Omega$

Find  $I_N$  by shortening circuit terminals  $a$  and  $b$
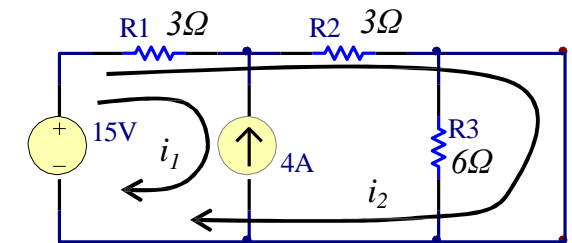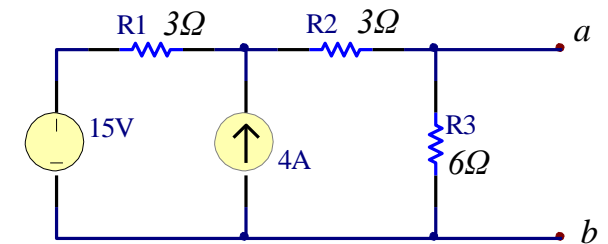
$$\begin{cases} i_1 = -4A \\ (R_1 + R_2)i_2 + R_1i_1 = 15 \end{cases} \rightarrow \begin{cases} i_1 = -4 \\ 3i_1 + 6i_2 = 15 \end{cases} \rightarrow i_2 = i_{sc} = I_N = 4.5A$$



## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems

## 4.6. Norton's theorem




+ **Example 16:** Using Norton theorem find  $R_N$  and  $I_N$  at terminals  $a-b$

**Find  $R_N$ :** set the independent voltage source equal to zero and connect a voltage source of  $v_0 = 1V$  to  $a-b$

$$\begin{cases} i_0 + i_x + 2i_x = 0 \\ R_2 i_x = -v_0 = -1 \end{cases} \rightarrow \begin{cases} i_x = -\frac{v_0}{5} = -0.2A \\ i_0 = -3i_x = 0.6A \end{cases} \rightarrow R_N = \frac{v_0}{i_0} = \frac{1}{0.6} = 1.67\Omega$$

**Find  $I_N$**  by shortening circuit terminals  $a$  and  $b$
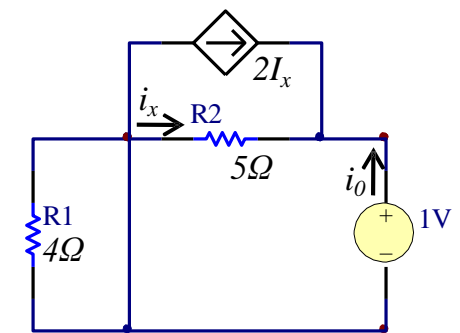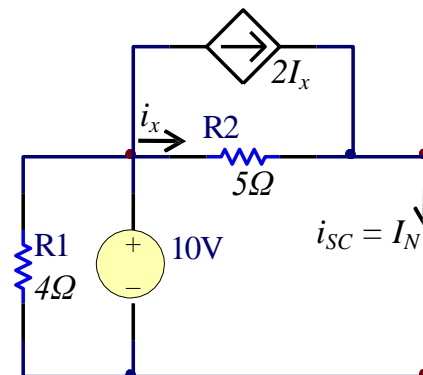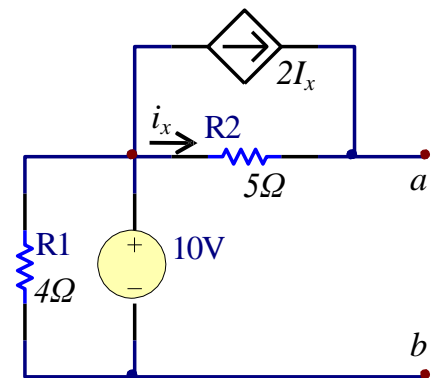
$$\begin{cases} R_2 i_x = 10 \\ I_N = i_{sc} = 3i_x \end{cases} \rightarrow \begin{cases} i_x = 2A \\ I_N = 6A \end{cases}$$



## 4

# FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems

### 4.7. Maximum power transfer

+ In many practical situations, a circuit is designed to provide power to a load

- Electric utilities: Minimizing power losses in the process of distribution
- Communications: Maximize the power delivered to a load

+ **Problem:** Delivering  $p_{\max}$  to a load when given a system with known internal losses




→ Assuming that the load resistance  $R_L$  can be adjusted

→ Replacing entire circuit by Thevenin equivalent circuit

$$p = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L \rightarrow p = p_{\max} \Leftrightarrow R_L = R_{Th}$$

+ **Maximum power** is transferred to the load when the load resistance equals the Thevenin resistance as seen from the load ( $R_L = R_{Th}$ )

$$p_{\max} = \frac{V_{Th}^2}{4R_{Th}}$$

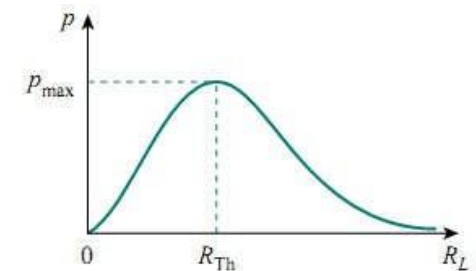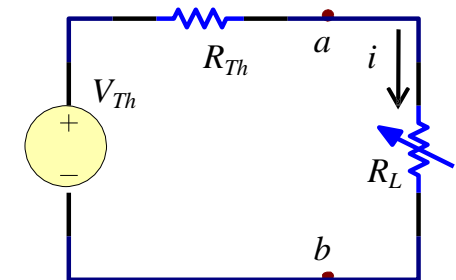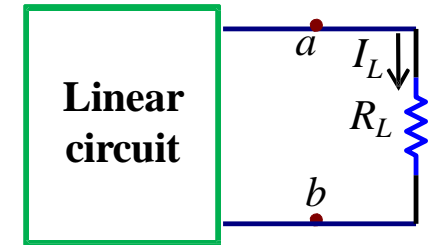

## 4

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Circuit Theorems

## 4.7. Maximum power transfer

+ **Example 17**: Find the value of  $R_L$  for maximum power transfer then find the maximum power

Find  $R_{Th}$  
$$R_{Th} = R_4 + R_3 + \frac{R_1 R_2}{R_1 + R_2} = 9\Omega$$


Find  $V_{Th}$  
$$\begin{cases} R_1 i_1 + R_2 (i_1 - i_2) = 12 \\ i_2 = -2 \end{cases} \rightarrow \begin{cases} i_1 = -\frac{2}{3} A \\ i_2 = -2 A \end{cases}$$

Apply KVL for the outer loop (open circuit) to get  $V_{Th}$

$$R_1 i_1 + R_3 i_2 + V_{Th} = 12 \rightarrow V_{Th} = 22V$$

For maximum power transfer:  $R_L = R_{Th} = 9\Omega$

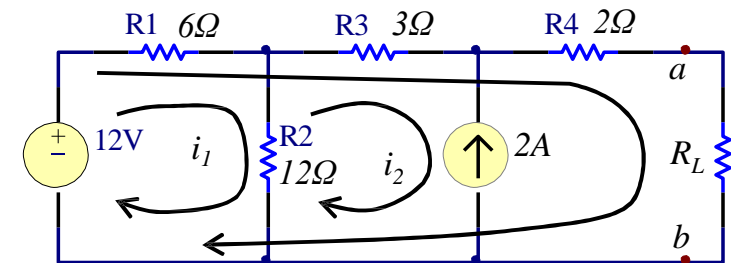Maximum power: 
$$P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{22^2}{4 \times 9} = 13.44W$$



Another way to calculate  $V_{Th}$

$$V_{Th} = R_2 (i_1 - i_2) + R_3 I_s \rightarrow V_{Th} = 22V$$



# 4


## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

### Circuit Theorems

#### 4.7. Maximum power transfer

+ **Example 18:** Find the value of  $R_L$  for maximum power transfer then find the maximum power

Find  $R_{Th}$ :

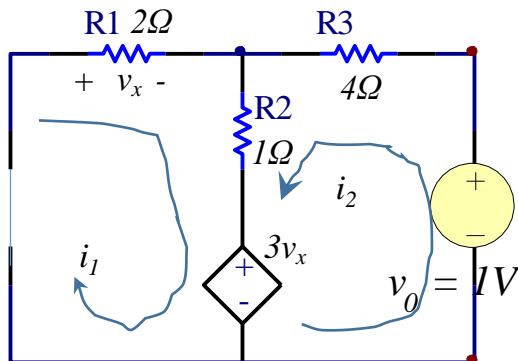


1st approach:

$$\begin{cases} (R_1 + R_2)i_1 + R_2i_2 + 3R_1i_1 = 0 \\ R_2i_1 + (R_2 + R_3)i_2 + 3R_1i_1 = 1 \end{cases} \rightarrow \begin{cases} 9i_1 + i_2 = 0 \\ 7i_1 + 5i_2 = 1 \end{cases} \rightarrow \begin{cases} i_1 = -\frac{1}{38} \\ i_2 = \frac{9}{38} \end{cases}$$

$$i_0 = i_2 = \frac{9}{38} A \rightarrow R_{Th} = \frac{v_0}{i_0} = \frac{38}{9} \approx 4.22\Omega$$

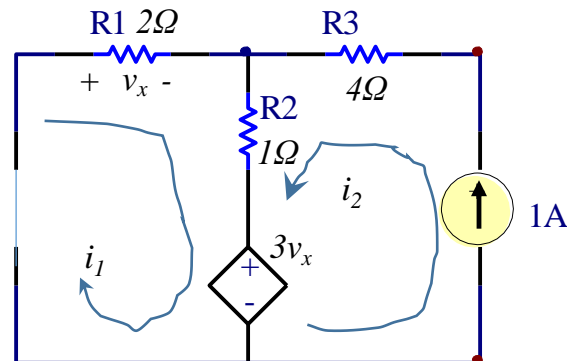
Find  $V_{Th}$ :  $(R_1 + R_2)i + 3R_1i = 9 \rightarrow i = 1A \rightarrow V_{Th} = R_2i + 3R_1i = 7V$



2nd approach:

$$\begin{cases} i_2 = 1A \\ R_1i_1 + R_2(i_1 + i_2) + 3R_1i_1 = 0 \end{cases} \rightarrow \begin{cases} i_1 = -\frac{1}{9} A \\ i_2 = 1A \end{cases}$$
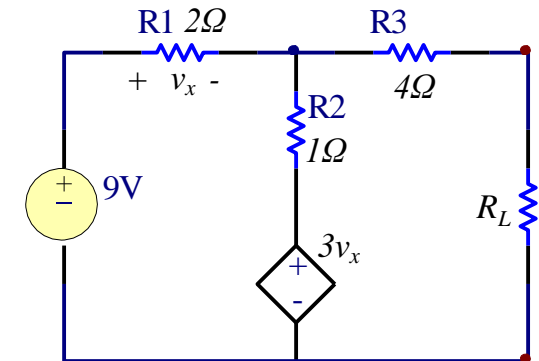
$$-v_0 + R_3i_2 - v_x = 0 \rightarrow v_0 = 4.1 + 2\frac{1}{9} = \frac{38}{9} V \rightarrow R_{Th} = \frac{v_0}{i_0} \approx 4.22\Omega$$



$$R_L = 4.22\Omega \quad P_{\max} = \frac{7^2}{4 \times 4.22} = 2.9W$$