

# Fundamentals of Electric Circuits

## DC Circuits


## Chapter 8. Second Order Circuits

- 8.1. Introduction
- 8.2. Finding initial and final values
- 8.3. The source-free series / parallel RLC circuit
- 8.4. Step response of a series / parallel RLC circuit
- 8.5. General second-order circuits
- 8.6. Applications

# Second Order Circuits
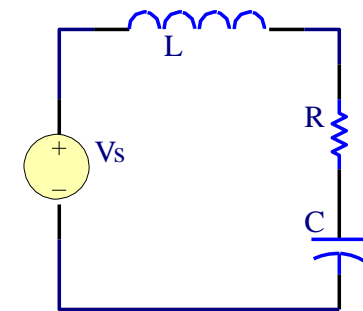
## 8.1. Introduction

- + **Previous chapter:** considered circuits with a single storage element (C or L) → first-order circuits
- + **In this chapter:** consider circuits containing two (independent) storage elements → *second-order circuits*
- + **A second-order circuit:**
  - characterized by a second-order differential equation
  - consists of resistors and the equivalence of 02 energy storage elements
- + **Second-order circuit classification:**
  - Two storage elements of different type: *L* and *C*
  - Two storage elements of one type: *L* or *C*
  - An op amp circuit with 02 storage elements



*Series RLC circuit*

# 8


## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

### Second Order Circuits

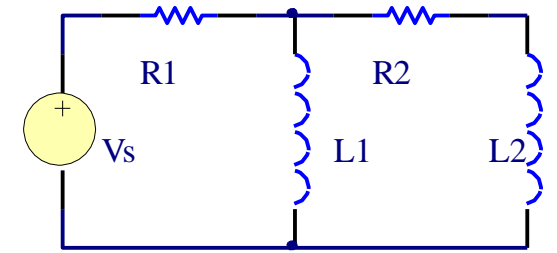
#### 8.1. Introduction

+ Analysis of second-order circuit:


- **First**, consider circuits that are excited by the initial conditions of the storage elements → source free circuits give natural responses
- **Second**, with independent sources, circuits will give both the nature response and the forced response



*RL circuit*

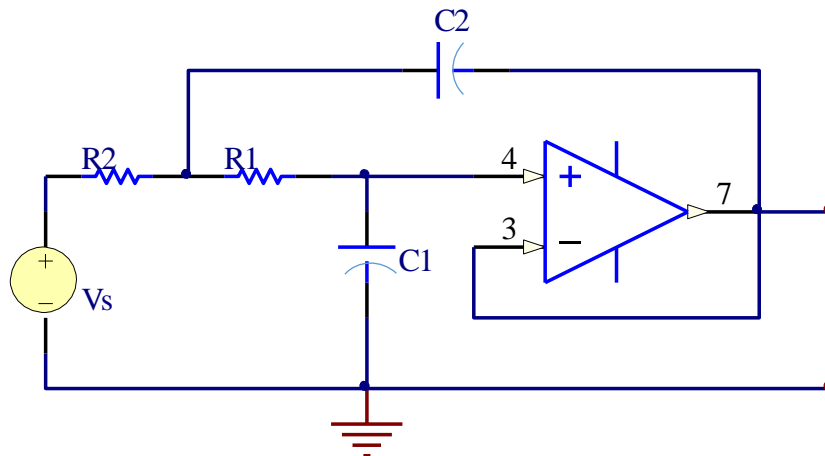

*Op amp with 2 storage element*

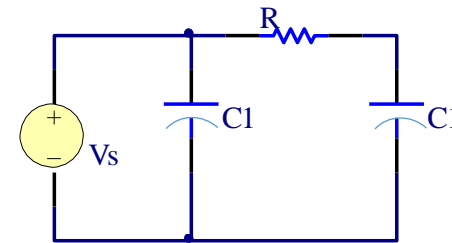

*RC circuit*

## Second Order Circuits

### 8.2. Finding initial and final values

+ The major problem: finding the initial and final conditions on circuits variables

→ Easy to get the initial and final values of  $v$  and  $i$

→ Difficult to find the initial values of their derivatives:  $dv/dt$ ,  $di/dt$

+ Key points in determining the initial conditions:

- First, carefully handle the *polarity of voltage*  $v_C(t)$ , and the *directions* of  $i_L(t)$
- Second, keep in mind that  $v_C(t)$ ,  $i_L(t)$  *are always continuous*

$$v_c(+0) = v_c(-0), i_L(+0) = i_L(-0)$$

$t = 0$ : the time that the switching event takes place

$t = -0$ : the time just before a switching event

$t = +0$ : the time just after a switching event

## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.2. Finding initial and final values



+ **Example 1**: The switch has been closed for a long time, and opens at  $t = 0$ . Find  $i(+0)$ ,  $v(+0)$ ,  $di(+0)/dt$ ,  $dv(+0)/dt$ ,  $i(\infty)$ ,  $v(\infty)$

For  $t = -0$ : The circuit has reached DC steady state  $\rightarrow$  L acts like a short circuit, C acts like an open circuit

$$i_L(-0) = \frac{E}{R_1 + R_2} = 2A \quad v_c(-0) = R_2 i_L(-0) = 2 \cdot 2 = 4V$$

As  $v_C(t)$  and  $i_L(t)$  cannot change abruptly, we have:
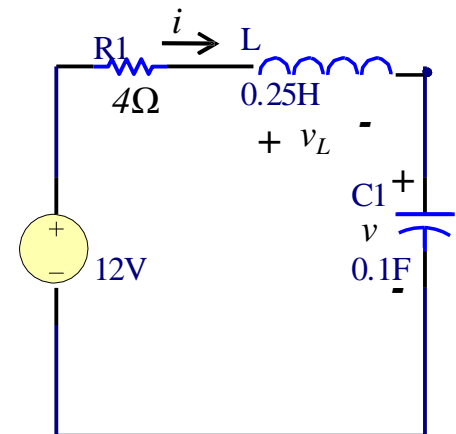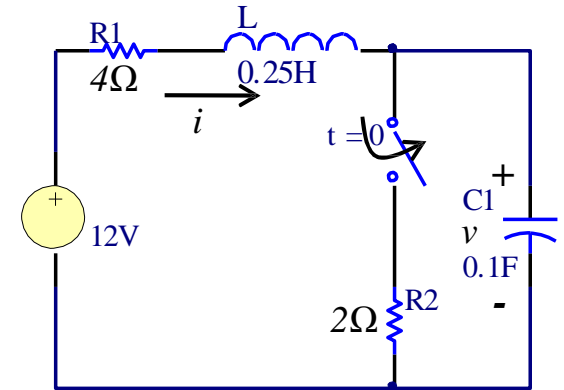
$$v_c(+0) = v_c(-0) = 4V \quad i_L(+0) = i_L(-0) = 2A$$



## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.2. Finding initial and final values

+ **Example 1**: The switch has been closed for a long time, and opens at  $t = 0$ . Find  $i(+0)$ ,  $v(+0)$ ,  $di(+0)/dt$ ,  $dv(+0)/dt$ ,  $i(\infty)$ ,  $v(\infty)$

For  $t = +0$ :

$$i_c = C \frac{dv_c}{dt} \rightarrow \frac{dv_c(+0)}{dt} = \frac{i_c(+0)}{C} = \frac{2}{0.1} = 20V/s$$



For  $t > 0$ :

$$R_1 i + L \frac{di}{dt} + v_c = E \rightarrow R_1 i_L(+0) + L \frac{di_L(+0)}{dt} + v_c(+0) = E$$

$$L \frac{di_L(+0)}{dt} = E - R_1 i_L(+0) - v_c(+0) = 12 - 4.2 - 4 = 0V \rightarrow \frac{di_L(+0)}{dt} = 0A/s$$

For  $t \rightarrow \infty$ : new DC steady state
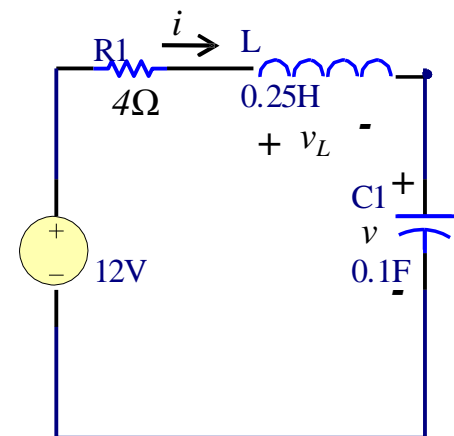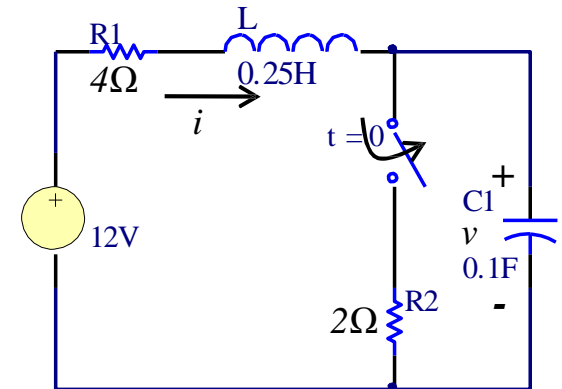
$$i(\infty) = 0A \quad v_c(\infty) = E = 12V$$



## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.2. Finding initial and final values

**+ Example 2:** Find  $i_L(+0)$ ,  $v_C(+0)$ ,  $v_R(+0)$ ,  $di_L(+0)/dt$ ,  $dv_C(+0)/dt$ ,  $i_L(\infty)$ ,  $v_C(\infty)$ ,  $v_R(\infty)$

For  $t < 0$ :  $3u(t) = 0$

At  $t = -0$  (old DC steady state):  $i_L(-0) = 0$ ,  $v_R(-0) = 0$ ,  $v_C(-0) = -E = -20V$

For  $t > 0$  (new DC steady state):


$$3u(t) = 3 \quad i_L(+0) = i_L(-0) = 0A, v_C(+0) = v_C(-0) = -20V$$

$$\text{KCL at node } a: I = \frac{v_R(+0)}{R_1} + \frac{v_0(+0)}{R_2}$$

$$\text{KVL to the middle mesh: } -v_R(+0) + v_0(+0) + v_c(+0) + E = 0 \rightarrow v_R(+0) = v_0(+0)$$

$$v_R(+0) = v_0(+0) = 4V$$
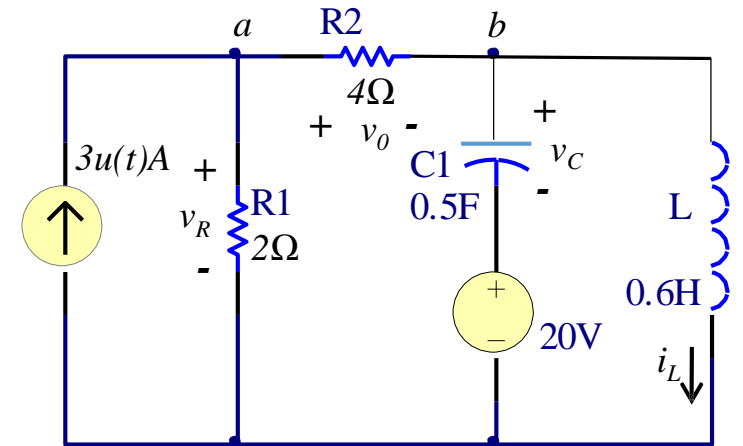
$$\text{Applying KVL to the right mesh: } v_L(+0) = v_c(+0) + E = -20 + 20 = 0V \rightarrow \frac{di_L(+0)}{dt} = 0A/s$$



## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.2. Finding initial and final values

+ **Example 2:** Find  $i_L(+0)$ ,  $v_C(+0)$ ,  $v_R(+0)$ ,  $di_L(+0)/dt$ ,  $dv_C(+0)/dt$ ,  $i_L(\infty)$ ,  $v_C(\infty)$ ,  $v_R(\infty)$

KCL at node  $b$ :

$$\frac{v_0(+0)}{R_2} = i_c(+0) + i_L(+0) \rightarrow i_c(+0) = \frac{v_0(+0)}{R_2} - i_L(+0) = \frac{4}{4} - 0 = 1A$$


$$\rightarrow \frac{dv_c(+0)}{dt} = \frac{i_c(+0)}{C} = \frac{1}{0.5} = 2V/s$$

For new steady state:  $I = \frac{v_a(\infty)}{R_1} + \frac{v_a(\infty)}{R_2} \rightarrow v_a(\infty) = \frac{R_1 R_2}{R_1 + R_2} I = \frac{2.4}{2 + 4} 3 = 4V$

$$\rightarrow v_R(\infty) = v_a(\infty) = 4V$$

$$i_L(\infty) = \frac{v_a(\infty)}{R_2} = \frac{4}{4} = 1A$$

$$v_c(\infty) = -E = -20V$$

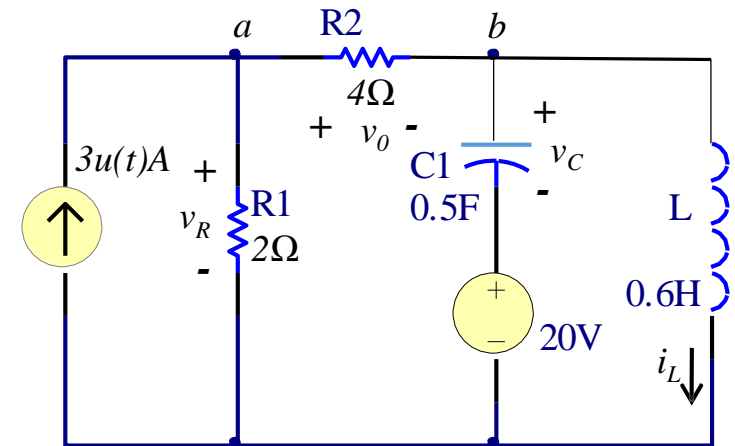



## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.3. The source-free series / parallel RLC circuit


## 8.3.1. The source-free series RLC circuit

+ Understanding of the **natural response** of the series RLC circuit: → necessary background for future studies in *filter design* and *communications network*

+ **Consider case**: The series RLC circuit that is excited by the energy initially stored  $V_0$ , and  $I_0$

$$\text{At } t = 0: \quad v_c(0) = \frac{1}{C} \int_{-\infty}^0 i(t) dt = V_0 \quad i(0) = I_0$$
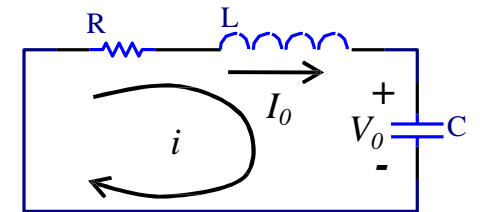
$$\text{For } t \geq 0, \text{ applying KVL to the loop: } Ri + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^0 i dt = 0 \rightarrow \boxed{\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0}$$



+ To solve a second-order differential equation → it requires 2 initial conditions

→  $i(+0)$  and  $i'(+0)$ , or

→  $i(+0)$  and  $v(+0)$

## Second Order Circuits

### 8.3. The source-free series / parallel RLC circuit

#### 8.3.1. The source-free series RLC circuit

+ Find  $i'(+0)$ :  $Ri(0) + L \frac{di(0)}{dt} + V_0 = 0 \rightarrow \frac{di(0)}{dt} = i'(0) = -\frac{1}{L}(RI_0 + V_0)$

+ Solution of the second-order equation:  $i(t) = Ae^{st}$


+ Substituting the solution into the equation, we have:

$$As^2e^{st} + \frac{AR}{L}se^{st} + \frac{A}{LC}e^{st} = 0 \rightarrow Ae^{st} \left( s^2 + \frac{R}{L}s + \frac{1}{LC} \right) = 0$$

$$\begin{cases} s_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} = -\alpha + \sqrt{\alpha^2 - \omega_0^2} & \alpha = \frac{R}{2L} \\ s_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} = -\alpha - \sqrt{\alpha^2 - \omega_0^2} & \omega_0 = \frac{1}{\sqrt{LC}} \end{cases}$$

$s_1$  and  $s_2$  are called *natural frequencies* [Np/s]

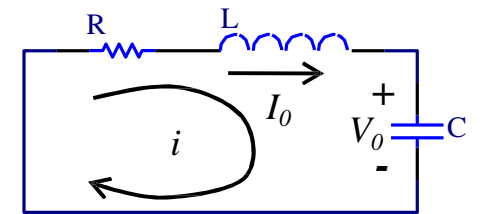$\omega_0$  *resonant frequency* (un-damped natural frequency, or damping factor)



## 8


## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.3. The source-free series / parallel RLC circuit
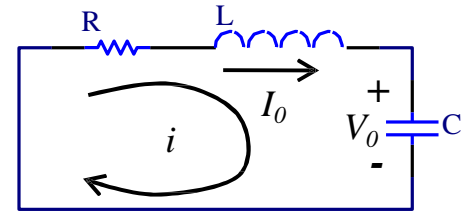
## 8.3.1. The source-free series RLC circuit

$$\begin{cases} s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} & \alpha = \frac{R}{2L} \\ s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} & \omega_0 = \frac{1}{\sqrt{LC}} \end{cases}$$



+ There are three types of solutions:

If  $\alpha > \omega_0$ : over damped case

If  $\alpha = \omega_0$ : critically damped case

If  $\alpha < \omega_0$ : under damped case

+ 2 values of  $s$ :  $\rightarrow$  2 possible solutions for  $i$ :  $i_1 = A_1 e^{s_1 t}, i_2 = A_2 e^{s_2 t} \rightarrow i = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

$A_1, A_2 \rightarrow$  determined from the initial values  $i(0)$  and  $di(0)/dt$

## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.3. The source-free series / parallel RLC circuit

## 8.3.1. The source-free series RLC circuit

+ **Over damped** case  $\alpha > \omega_0 \rightarrow s_1$  and  $s_2$  are *negative and real*



$$i = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

→ Response *decays* and *approaches* zero as  $t$  increases

+ **Critically damped** case  $\alpha = \omega_0$

$$i = A_1 t e^{\alpha t} + A_2 e^{\alpha t} = (A_1 t + A_2) e^{\alpha t}$$

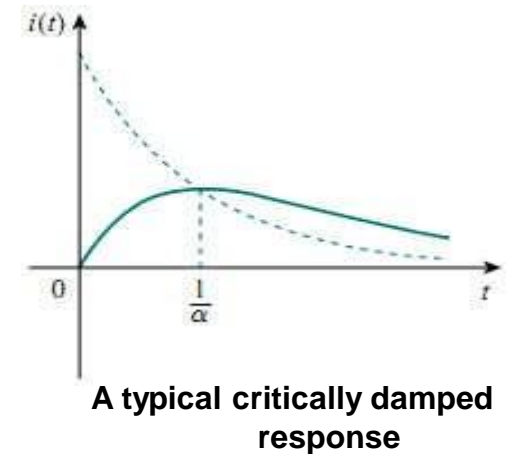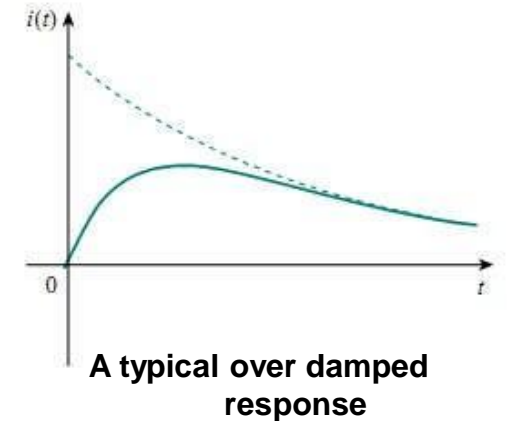→ Response reaches a maximum value at  $t = 1/\alpha$ , and then *decays* all the way to zero



## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits


## 8.3. The source-free series / parallel RLC circuit

## 8.3.1. The source-free series RLC circuit

+ **Under damped** case  $\alpha < \omega_0$

$$\begin{cases} s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -\alpha + j\omega_d & \omega_d: \text{damped natural frequency} \\ s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -\alpha - j\omega_d & \omega_0: \text{un-damped natural frequency} \end{cases}$$
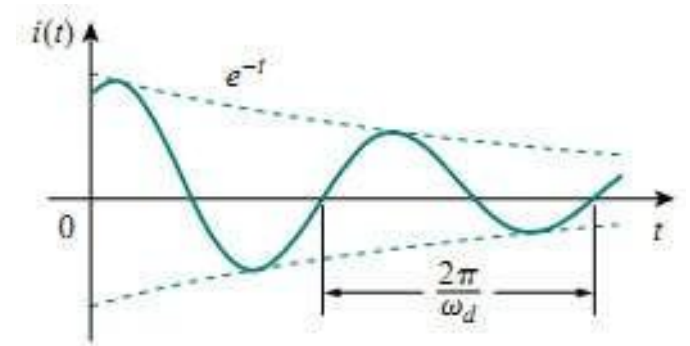
$$i = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$



A typical under damped response

→ The natural response is **exponentially damped** and **oscillatory** in nature

→ The response has a **time constant** of  $1/\alpha$  and a period of  $T = 2\pi/\omega_d$

## Second Order Circuits

### 8.3. The source-free series / parallel RLC circuit

#### 8.3.1. The source-free series RLC circuit

+ Notes:

- *Damping effect* → due to the presence of R
- *Damping factor  $\alpha$*  → the rate at which the response is damped
  - $\alpha = 0$ : having LC circuit with  $1/LC$  as the un-damped natural frequency
  - $\alpha < \omega_0$ : response is not only damped but also oscillatory
- *By adjusting R*, → response may be made un-damped: over damped, critically damped, or under damped
- *Oscillatory response* → possible due to the presence of L, C: They allows the flow of energy back and forth
- *Critically damped* case → the *borderline* between the under damped and over damped cases

## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.3. The source-free series / parallel RLC circuit

## 8.3.1. The source-free series RLC circuit

+ **Example 3:** Find  $i(t)$  in the circuit. Assume that the circuit has reached steady state at  $t = -0$


For  $t < 0$ :  $i(0) = \frac{E}{R_1 + R_3} = 1A$        $v(0) = R_3 i(0) = 6V$

For  $t > 0$ : Source – free series RLC circuit

$$\alpha = \frac{R_{eq}}{2L} = \frac{R_2 + R_3}{2L} = 9 \quad \omega_0 = \frac{1}{\sqrt{LC}} = 10 \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -9 \pm j4.359$$

Response is under-damped:
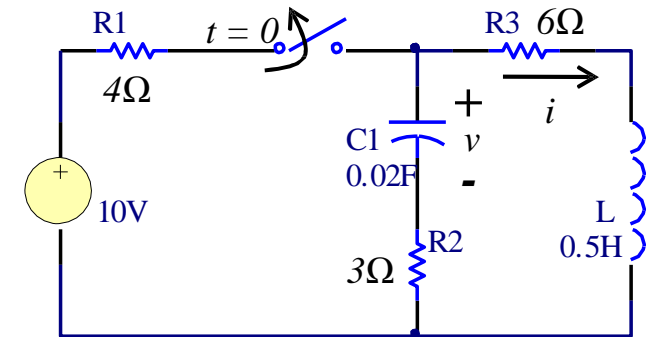
$$i(t) = e^{-9t} (A_1 \cos 4.359t + A_2 \sin 4.359t)$$



## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.3. The source-free series / parallel RLC circuit

## 8.3.2. The source-free parallel RLC circuit

Apply node voltage method:

$$\frac{v}{R} + \frac{1}{L} \int_{-\infty}^t v dt + C \frac{dv}{dt} = 0 \rightarrow \frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

Characteristic equation:  $\rightarrow s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Over damped ( $\alpha > \omega_0$ ):  $v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$


Critically damped ( $\alpha = \omega_0$ ):  $v(t) = (A_1 + A_2 t) e^{-\alpha t}$

Under damped ( $\alpha < \omega_0$ ):  $v(t) = e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$

$$s_{1,2} = -\alpha \pm j\omega_d, \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$A_i$  determined from the initial conditions:

$v(0), dv(0)/dt$

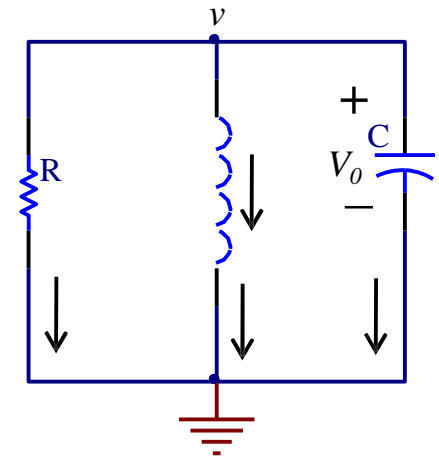



## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.3. The source-free series / parallel RLC circuit

## 8.3.2. The source-free parallel RLC circuit


+ **Example 4:** Find  $v(t)$  for  $t > 0$  in the RLC circuit

When  $t < 0$ : The switch is opened

$$v(0) = \frac{R_2}{R_1 + R_2} E = \frac{50}{30 + 50} 40 = 25V \quad i(0) = -\frac{E}{R_1 + R_2} = \frac{40}{30 + 50} = -0,5A$$

At  $t = 0$ , applying the KCL to the parallel RLC circuit:
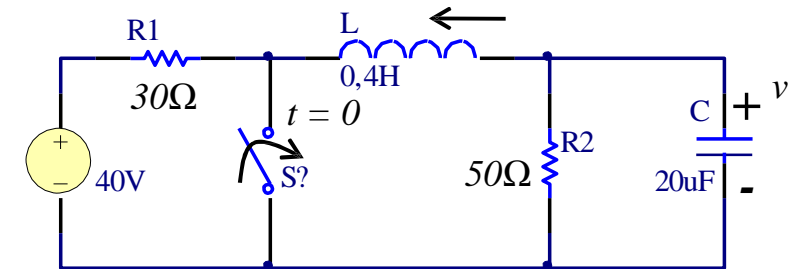
$$\begin{aligned} \frac{v(0)}{R_2} + \frac{1}{L} \int_{-\infty}^0 v dt + C \frac{dv(0)}{dt} &= 0 \rightarrow \frac{v(0)}{R_2} + i(0) + C \frac{dv(0)}{dt} = 0 \\ \rightarrow \frac{dv(0)}{dt} &= -\frac{v(0) + R_2 i(0)}{R_2 C} = -\frac{25 - 50 \times 0.5}{50 \times 20 \cdot 10^{-6}} = 0V/s \end{aligned}$$



## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.3. The source-free series / parallel RLC circuit

## 8.3.2. The source-free parallel RLC circuit

+ **Example 4:** Find  $v(t)$  for  $t > 0$  in the RLC circuit


When  $t > 0$ : The switch is closed

$$\alpha = \frac{1}{2R_2C} = 500 \quad \omega_0 = \frac{1}{\sqrt{LC}} = 354$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -854 \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -146 \quad \rightarrow v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{At } t = 0: \begin{cases} v(0) = A_1 + A_2 = 25 \\ \frac{dv(0)}{dt} = -854A_1 - 146A_2 = 0 \end{cases} \rightarrow \begin{cases} A_1 = -5.16 \\ A_2 = 30.16 \end{cases}$$
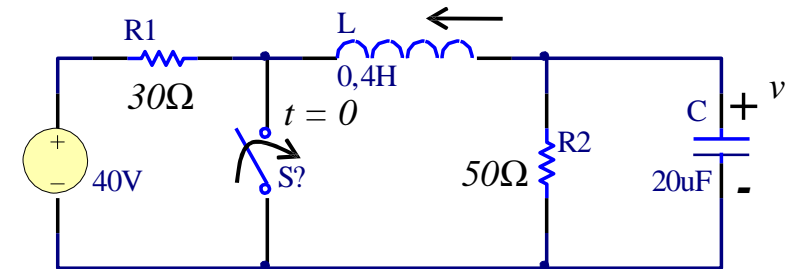
$$\text{The complete solution: } v(t) = -5.16e^{-854t} + 30.16e^{-146t}$$



## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.4. Step response of a series / parallel RLC circuit

## 8.4.1. Step response of a series RLC circuit

+ For  $t > 0$ : Applying KVL around the loop

$$\begin{cases} L \frac{di}{dt} + Ri + v = V_s \\ i = C \frac{dv}{dt} \end{cases} \rightarrow \frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{V_s}{LC} \rightarrow v(t) = v_n(t) + v_f(t)$$

$v_n(t)$ : natural response ,  $v_f(t)$ : forced response

Over damped:

$$v(t) = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


Critically damped:

$$v(t) = V_s + (A_1 + A_2 t) e^{-\alpha t}$$

Under damped:

$$v(t) = V_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t}$$

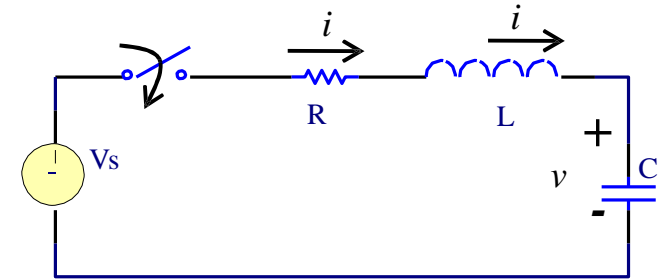$A_1, A_2 \rightarrow$  determined from the initial values  $v(0)$  and  $dv(0)/dt$




## Second Order Circuits

### 8.4. Step response of a series / parallel RLC circuit

#### 8.4.1. Step response of a series RLC circuit

+ **Example 5:** Find  $v(t)$  and  $i(t)$  for  $t > 0$  in the case of the different values of  $R_1 = 5\Omega, 4\Omega, 1\Omega$

○  $R_1 = 5\Omega$

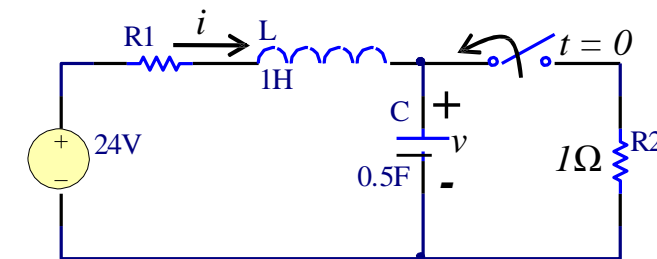

$$\text{For } t < 0: i(0) = \frac{E}{R_1 + R_2} = \frac{24}{5+1} = 4A \quad v(0) = R_2 i(0) = 4V \quad \alpha = \frac{R_1}{2L} = 2.5 \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2$$

$$\rightarrow s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -1 \quad \rightarrow s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -4$$

$$\text{For } t > 0: v(t) = E + A_1 e^{s_1 t} + A_2 e^{s_2 t} = 24 + A_1 e^{-t} + A_2 e^{-4t}$$

$$\text{At } t = 0: v(0) = 24 + A_1 + A_2 = 4 \rightarrow A_1 + A_2 = -20$$

$$i(t) = C \frac{dv}{dt} = C(-A_1 e^{-t} - 4A_2 e^{-4t}) \rightarrow i(0) = C(-A_1 - 4A_2) = 4$$

$$\rightarrow v(t) = 24 + \frac{4}{3}(-16e^{-t} + e^{-4t})V \quad \rightarrow i(t) = C \frac{dv}{dt} = 0.5 \frac{4}{3}(16e^{-t} - 4e^{-4t}) = \frac{8}{3}(4e^{-t} - e^{-4t})A$$

## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits


## Second Order Circuits

## 8.4. Step response of a series / parallel RLC circuit

## 8.4.1. Step response of a series RLC circuit

+ **Example 5:** Find  $v(t)$  and  $i(t)$  for  $t > 0$  in the case of the different values of  $R_1 = 5\Omega, 4\Omega, 1\Omega$

○  $R_1 = 4\Omega$

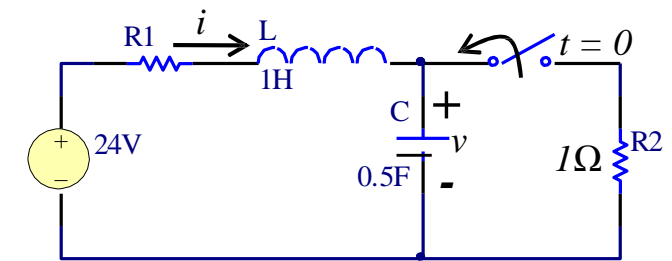

$$\text{For } t < 0: i(0) = \frac{E}{R_1 + R_2} = \frac{24}{4+1} = 4.5A \quad v(0) = R_2 i(0) = 4.5V \quad \alpha = \frac{R_1}{2L} = 2 \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2$$

$$\rightarrow s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -2 \quad \rightarrow s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -2$$

$$\text{For } t > 0: v(t) = E + (A_1 + A_2 t)e^{\alpha t} = 24 + (A_1 + A_2 t)e^{-2t}$$

$$\text{At } t = 0: v(0) = 24 + A_1 = 4.5 \rightarrow A_1 = -19.5$$

$$i(t) = C \frac{dv}{dt} = C(-2A_1 - 2tA_2 + A_2)e^{-2t} \rightarrow i(0) = C(-2A_1 + A_2) = 4.5 \rightarrow A_2 = 57$$

$$\rightarrow v(t) = 24 + (-19.5 + 57t)e^{-2t}V \quad \rightarrow i(t) = C \frac{dv}{dt} = 0.5 \times 2 \left( 19.5 - 57t + \frac{57}{2} \right) e^{-2t} = (48 - 57t)e^{-2t}A$$


## Second Order Circuits

### 8.4. Step response of a series / parallel RLC circuit

#### 8.4.1. Step response of a series RLC circuit

+ **Example 5:** Find  $v(t)$  and  $i(t)$  for  $t > 0$  in the case of the different values of  $R_1 = 5\Omega, 4\Omega, 1\Omega$

○  $R_1 = 1\Omega$

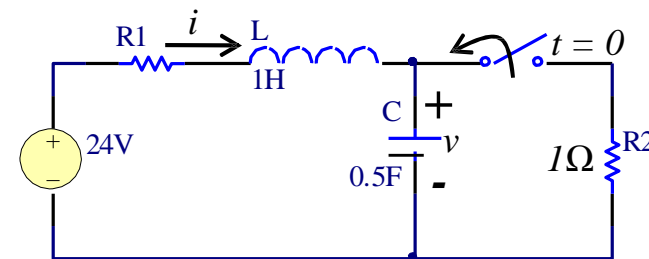

$$\text{For } t < 0: i(0) = \frac{E}{R_1 + R_2} = \frac{24}{1+1} = 12\text{A} \quad v(0) = R_2 i(0) = 12\text{V} \quad \alpha = \frac{R_1}{2L} = 0.5 \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2$$

$$\rightarrow s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -0.5 \pm j1.936$$

$$\text{For } t > 0: v(t) = 24 + (A_1 \cos 1.936t + A_2 \sin 1.936t)e^{-0.5t}\text{V}$$

$$\text{At } t = 0: v(0) = 24 + A_1 = 12 \rightarrow \boxed{A_1 = -12}$$

$$\frac{dv}{dt} = (-1.936A_1 \sin 1.936t + 1.936A_2 \cos 1.936t)e^{-0.5t} - 0.5e^{-0.5t}(A_1 \cos 1.936t + A_2 \sin 1.936t)$$

$$\rightarrow \frac{dv(0)}{dt} = 1.936A_2 - 0.5A_1 = \frac{i(0)}{C} = 24 \rightarrow \boxed{A_2 = 9.3} \quad v(t) = 24 + (-12 \cos 1.936t + 9.3 \sin 1.936t)e^{-0.5t}\text{V}$$

$$\rightarrow i(t) = C \frac{dv}{dt} = (9.291 \sin 1.936t + 12.002 \cos 1.936t)e^{-0.5t}\text{A}$$

## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits


## 8.4. Step response of a series / parallel RLC circuit

## 8.4.2. Step response of a parallel RLC circuit

+ Applying KCL at the top node for  $t > 0$ :

$$\left. \begin{aligned} \frac{v}{R} + i + C \frac{dv}{dt} &= I_s \\ v &= L \frac{di}{dt} \end{aligned} \right\} \rightarrow \frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = \frac{I_s}{LC}$$
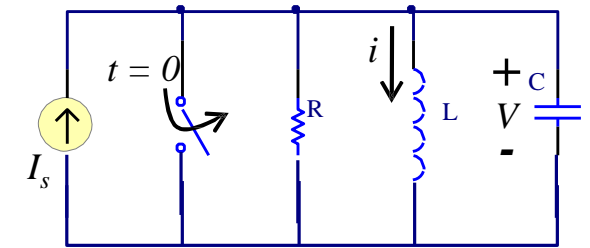
$$\rightarrow i(t) = i_n(t) + i_f(t) \quad i_n(t) - \text{Natural response} \quad i_f(t) - \text{Forced response}$$



Over damped:

$$i(t) = I_s + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Critically damped:

$$i(t) = I_s + (A_1 + A_2 t) e^{-\alpha t}$$

Under damped:

$$i(t) = I_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t}$$

$A_1, A_2 \rightarrow$  determined from the initial values  $i(0)$  and  $di(0)/dt$

## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.4. Step response of a series / parallel RLC circuit

## 8.4.2. Step response of a parallel RLC circuit

+ **Example 6:** Find  $i(t)$ ,  $i_R(t)$  for  $t > 0$

For  $t < 0$ :


$$i(0) = 4A$$

$$v(0) = \frac{E}{R_1 + R_2} R_1 = \frac{30}{40} 20 = 15V$$

At  $t = 0$ :

$$v(0) = L \frac{di(0)}{dt} \rightarrow \frac{di(0)}{dt} = \frac{v(0)}{L} = \frac{15}{20} = 0.75A/s$$

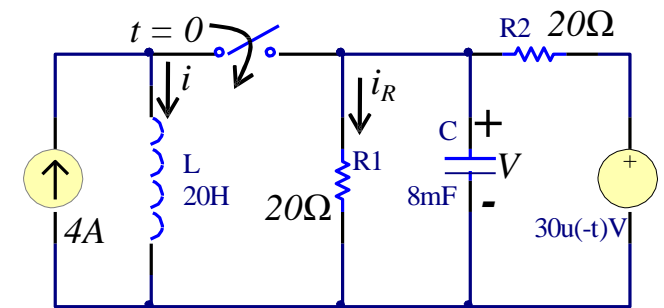For  $t > 0$ : parallel RLC circuit with current source



$$R = \frac{R_1 R_2}{R_1 + R_2} = 10\Omega \quad \alpha = \frac{1}{2RC} = 6.25 \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2.5 \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \rightarrow s_1 = -11.978, s_2 = -0.522$$

$$i(t) = I_f + A_1 e^{-11.978t} + A_2 e^{-0.522t} \quad \text{At } t = 0: \begin{cases} i(0) = 4 \\ \frac{di(0)}{dt} = 0.75 \end{cases} \rightarrow \begin{cases} A_1 + A_2 + 4 = 4 \\ -11.978A_1 - 0.522A_2 = 0.75 \end{cases} \rightarrow \begin{cases} A_1 = -0.0655 \\ A_2 = 0.0655 \end{cases}$$

$$\rightarrow i(t) = 4 - 0.0655e^{-11.978t} + 0.0655e^{-0.522t} A \quad i_R(t) = \frac{u_L}{R_1} = \frac{1}{R_1} L \frac{di}{dt} = 0.785e^{-11.978t} - 0.0342e^{-0.522t} A$$



## Second Order Circuits

### 8.5. General second order circuits

+ Give a second order circuit: → the step response  $x(t)$  (current or voltage) can be determined by taking the following 5 steps

- Determine the initial conditions  $x(0)$  and  $dx(0)/dt$  and the final value  $x(\infty)$
- Find the natural response  $x_n(t)$  (with 2 unknown constants) by turning off independent sources and applying KCL and KVL
- Obtain the forced response as:  $x_f(t) = x(\infty)$
- Obtain the total response: sum of the natural response and forced response

$$x(t) = x_n(t) + x_f(t)$$

- Determine 2 unknown constants by imposing the initial conditions  $x(0)$  and  $dx(0)/dt$

## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.5. General second order circuits

+ **Example 7:** Find the complete response  $v$  and  $i$  for  $t > 0$

Initial and final values


$$\begin{cases} v(0) = 12V & v(\infty) = 4V \\ i(0) = 0A & i(\infty) = 2A \end{cases}$$

Natural response:  $t > 0$ , turn off independent sources

$$\begin{cases} i = \frac{v}{R_2} + C \frac{dv}{dt} \\ R_1 i + L \frac{di}{dt} + v = 0 \end{cases} \rightarrow \frac{d^2 v}{dt^2} + 5 \frac{dv}{dt} + 6v = 0 \rightarrow v_n(t) = A_1 e^{-2t} + B e^{-3t}$$

Complete response:
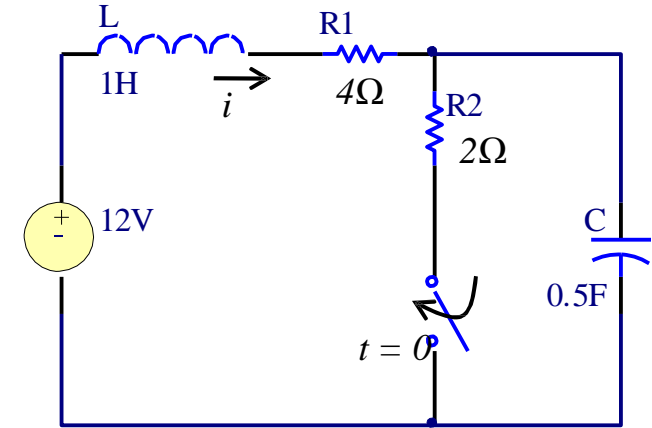
$$v(t) = v_n(t) + v_f(t) = 4 + A_1 e^{-2t} + A_2 e^{-3t} V$$



## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits


## 8.5. General second order circuits

+ **Example 7:** Find the complete response  $v$  and  $i$  for  $t > 0$

Imposing the initial condition:

$$\begin{cases} A_1 + A_2 = 8 \\ \frac{dv(0)}{dt} = -2A_1 - 2A_2 = -12 \end{cases} \rightarrow \begin{cases} A_1 = 12 \\ A_2 = -4 \end{cases} \rightarrow v(t) = 4 + 12e^{-2t} - 4e^{-3t} V$$
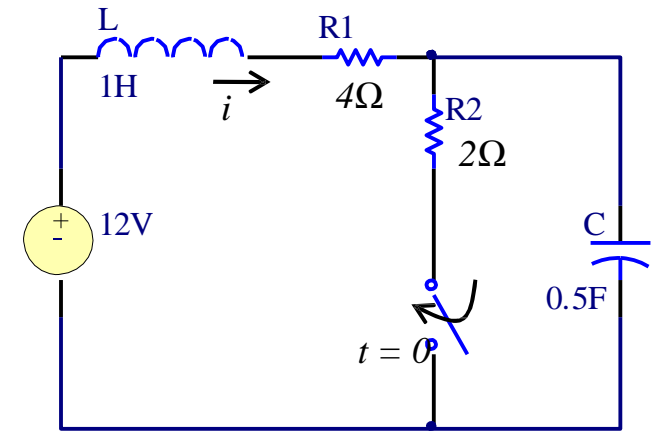
$$i = \frac{v}{R_2} + C \frac{dv}{dt} = 2 + 6e^{-2t} - 2e^{-3t} - 12e^{-2t} + 6e^{-3t} = 2 - 6e^{-2t} + 4e^{-3t} A$$



## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits


## Second Order Circuits

## 8.5. General second order circuits

+ **Example 8:** Find  $v_o(t)$  for  $t > 0$

Initial and final values
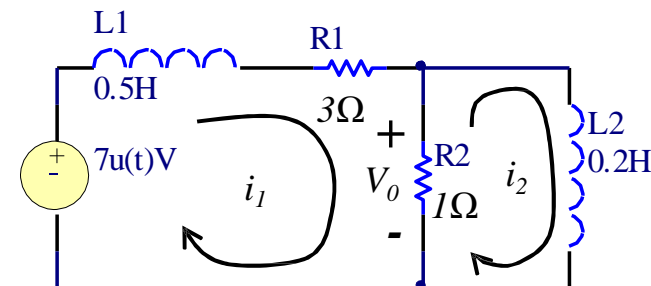
$$\begin{cases} i_1(0) = 0A \\ i_2(0) = 0A \\ v_o(t) = 0V \end{cases}$$



Natural response:  $t > 0$ , turn off independent source

$$\begin{cases} (R_1 + R_2)i_1 - R_2i_2 + L_1 \frac{di_1}{dt} = 0 \\ R_2(i_2 - i_1) + L_2 \frac{di_2}{dt} = 0 \end{cases} \rightarrow \frac{d^2i_1}{dt^2} + 13\frac{di_1}{dt} + 30i_1 = 0 \rightarrow i_{1n} = Ae^{-3t} + Be^{-10t} A$$

Force response:

$$i_{L1}(\infty) = i_{L2}(\infty) = \frac{E}{R_1} = \frac{7}{3} = 2.33A \quad v_o(\infty) = 0V$$

## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.5. General second order circuits

+ **Example 8:** Find  $v_o(t)$  for  $t > 0$

Complete response:

$$i_1(t) = i_{1f} + i_{1n} = 2.33 + Ae^{-3t} + Be^{-10t} \text{ A}$$


Imposing the initial condition

$$\begin{cases} A + B + 2.33 = 0 \\ -3A - 10B = 14 \end{cases} \rightarrow \begin{cases} A = -1.33 \\ B = -1 \end{cases} \rightarrow i_1(t) = 2.33 - 1.33e^{-3t} - e^{-10t} \text{ A}$$

To find  $v_o(t)$

$$L_1 \frac{di_1}{dt} + (R_1 + R_2)i_1 - R_2i_2 = E \rightarrow i_2(t) = 2.33 - 3.33e^{-3t} + e^{-10t} \text{ A}$$
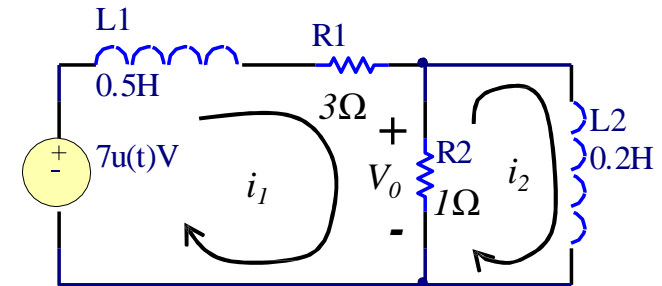
$$v_o(t) = R_2[i_1(t) - i_2(t)] = 2(e^{-3t} - e^{-10t}) \text{ V}$$



## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.5. General second order circuits

+ **Example 9:** Find  $v_o(t)$  for  $t > 0$


$$\text{At node 1: } \frac{v_s - v_1}{R_1} = C_2 \frac{dv_2}{dt} + \frac{v_1 - v_o}{R_2}$$

$$\text{At node 2: } \frac{v_1 - v_o}{R_2} = C_1 \frac{dv_o}{dt} \rightarrow v_1 = v_o + R_2 C_1 \frac{dv_o}{dt}$$

$$\rightarrow \frac{v_s - v_o}{R_1} = C_2 \frac{dv_2}{dt} + C_1 \frac{dv_o}{dt}$$

$$\rightarrow \frac{v_s - v_o}{R_1} = C_2 \frac{dv_2}{dt} + C_1 \frac{dv_o}{dt}$$
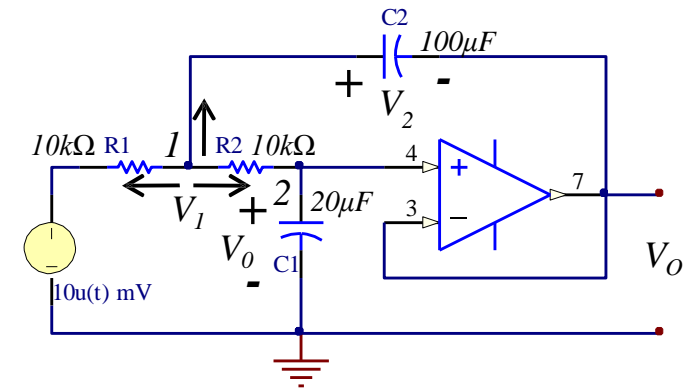
$$\rightarrow \frac{d^2 v_o}{dt^2} + \left( \frac{1}{R_1 C_2} + \frac{1}{R_2 C_2} \right) \frac{dv_o}{dt} + \frac{v_o}{R_1 R_2 C_1 C_2} = \frac{v_s}{R_1 R_2 C_1 C_2} \rightarrow \frac{d^2 v_o}{dt^2} + 2 \frac{dv_o}{dt} + 5v_o = 5v_s$$



## 8

## FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

## Second Order Circuits

## 8.5. General second order circuits

+ **Example 9:** Find  $v_o(t)$  for  $t > 0$

Natural response: turn off the source

$$s^2 + 2s + 5 = 0 \rightarrow s_{1,2} = -1 \pm j2 \rightarrow v_{on}(t) = e^{-t}(A \cos 2t + B \sin 2t)$$


Force response:  $v_o(\infty) = v_1(\infty) = v_s \rightarrow v_{of} = v_o(\infty) = 10mV$

Complete response:  $v_o(t) = 10 + e^{-t}(A \cos 2t + B \sin 2t)$

Initial conditions:  $v_o(+0) = 0V$   $\frac{dv_o(+0)}{dt} = \frac{v_1 - v_o}{R_2 C_1} = 0V$  (Eq. at node 2)

$$\rightarrow \begin{cases} v_o(+0) = 10 + A = 0 \rightarrow A = -10 \\ \frac{dv_o(+0)}{dt} = -A + 2B = 0 \rightarrow B = -5 \end{cases}$$
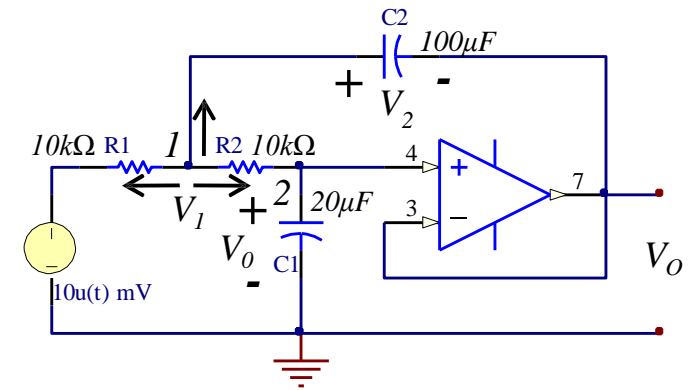
$$\rightarrow v(t) = 10 - e^{-t}(10 \cos 2t + 5 \sin 2t) mV$$



## Second Order Circuits

### 8.6. Applications

+ Practical applications of  $RLC$  circuits are found in control and communications circuits:

Ringling circuits

Peaking circuits

Resonant circuits

Filters

*Smoothing circuit*

*Automobile ignition*

→ Most of the circuits cannot be covered until we treat AC sources