

(Documents are allowed to use. Return the question sheet)

Student's name: ..... Student's Code: .....

### Question 1 (3 pts)

Given a circuit as in the figure 1.

Write the system of equations for the given circuit by the mesh current method? Express branch currents in terms of chosen mesh currents?

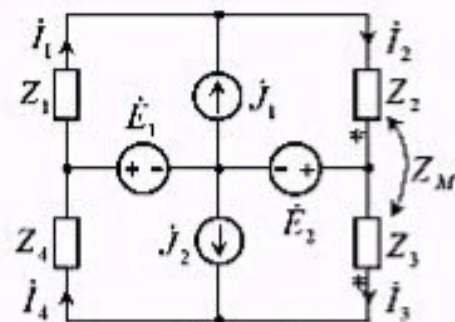


Figure 1

### Question 2 (3 pts)

Given a circuit as in the figure 2, where:  $R_1 = 20\Omega$ ,

$R_2 = 80\Omega$ ,  $C_2 = 5 \cdot 10^{-4} F$ ,  $L = 0.5 H$ ,  $V_s = 60V$  (DC).

Using the Laplace transformation, find the step response  $v_c(t)$  when the switch S is opened at the time  $t = 0$ ? (Note that, for  $t < 0$ , the given circuit was being in steady state)

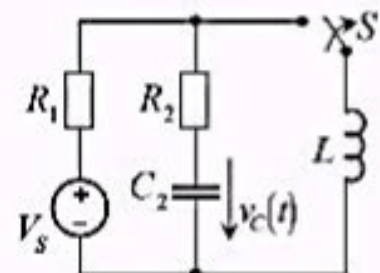


Figure 2

### Question 3 (3 pts)

Given a circuit as in the figure 3, where:

$Z_2 = 20 + j20\Omega$ ,  $Z_3 = 40 + j60\Omega$ ,

$Z_4 = 40 + j10\Omega$ ,  $J_3 = 2A$  (RMS),  $J_2 = \alpha I_3 A$ ,

$J_5 = \beta I_3 A$ ,  $\alpha = 0.5$ ,  $\beta = 2$ .

a) – Choose C as reference node, calculate the value of  $I_2$  and  $I_4$  by the nodal voltage method?

b) – Applying appropriate transformation technique to calculate the value of  $I_2$  and  $I_4$  from one KVL equation?

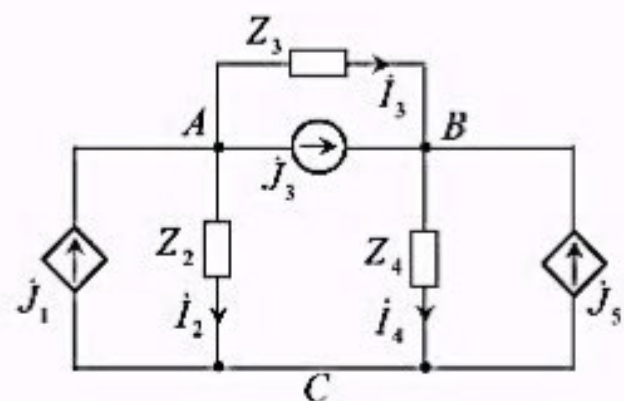


Figure 3

Note:

Good presentation: 1 pt