

I, OVERVIEW:

Design of a controlled rectifier power supply for a plating bath

Technology requirements


- Small output voltage, large load current
- Current must be stable, accurate
- High
- The voltage to be adjusted is low in startup process
- Large flow requires cooling valve

Designed parameters:

Rated voltage: 24V

Rated current: 3600A

Power supply 3x380V, 50Hz

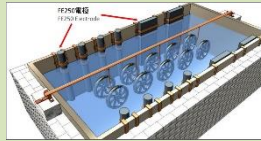

II, DESIGNED OPTION

1, Rectifier selection

- With large current and relatively low voltage ($U_d=24V$, $I_d=3600A$)
- Using a ray diagram is the most suitable option
- Large required power and current over 1000A
- Using a 6-phase beam diagram with a balanced reactor.

2, Advantage and Disadvantage


Advantage:

- ✓ Medium flow through small valve equal to 1/6 of rated current.
- ✓ Output voltage and current stable.
- ✓ Is a suitable rectifier circuit for circuits with low voltage high current.


Disadvantage:

- ✓ Complex transformer design more complex than other schemes.
- ✓ Number of valves used and equipment valve protection so much cost high production

IV, SIMULATION

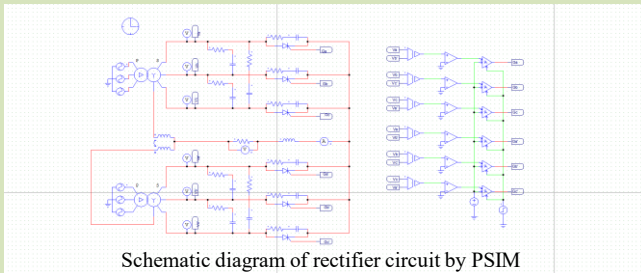

2. Kết quả mô phỏng

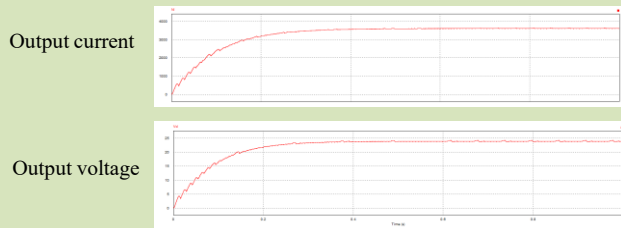

Comment:

- The output follows the desire value, ensure the current and voltage deviation is less than 10%.
- The graph form is relative similar in theory.
- Satisfying the pulse rate requirement $K_p < 20\%$.
- It takes about 3,2s to reach the set value due to the filter coil, reactor.

III, DESIGNED RECTIFIER CIRCUIT:

Requirements:

Output rated voltage: $U_d = 24V$

Output rated current: $I_d = 3600A$

Input voltage source: $3 \times 380V$, $50Hz \pm 10\%$

Choose: $e_r = 3\%$, $e_x = 9\%$ ($e_{nm} = 9,5\%$), $\alpha = 10^\circ$

1. Calculate transformer parameters

- No-load rectifier voltage:

$$U_{d,kt} = U_d + \Delta U_v + \Delta U_R + \Delta U_X$$

Where: $2\Delta U_v = 1,5(V)$, $U_{do} = \frac{U_d}{\cos \alpha} = 24,37(V)$

$$\Delta U_R = 2R_\alpha I_d = \frac{I_d e_r 3U^2}{S_{ba}} = 3,48 e_r U_{d,kt}$$

$$\Delta U_X = 6 \frac{X_\alpha I_d}{2\pi} = \frac{3}{\pi} \frac{3U^2}{S_{ba}} e_x I_d = 1,66 e_x U_{d,kt}$$

$$\rightarrow U_{d,kt} = \frac{U_{do} + 2\Delta U_v}{1 - (3,48 e_r + 1,66 e_x)} = 35,17(V)$$

$$\rightarrow U_2 = \frac{U_{d,kt}}{1,17} = 30,1(V)$$

$$U_1 = 380V$$

- Apparent power: $S_{ba} = 1,26 P_d = 1,26 \cdot 3600 \cdot 35,17 = 160(KVA)$

- Power factor (Voltage source drop 10%)

$$k_{ba} = \frac{U_1(1 - 0,1)}{U_2} = \frac{380(1 - 0,1)}{30,1} = 11,36$$

- Other parameters:

$$I_2 = 0,29 \cdot I_d = 0,29 \cdot 3600 = 1044(A)$$

$$I_1 = \frac{I_2}{k_{ba}} = \frac{1044}{11,36} = 91,9(A)$$

2. Value selection

- Average current through valve:

$$I_v = \frac{I_d}{6} = 600(A)$$

- Maximum reversed voltage:

$$U_{ng,max} = 1,1\sqrt{6} U_2 = 80,1(V)$$

- Assuming natural cooling condition, the value mounts on the heatsink. Choose value has $I_v = 600(A)$ and $U_{max} = 100(V)$

- Choose thyristor **T370N** with the following parameters:

- $I_v = 650V$, $V_{DRM} = 1800V$, $V_{RRM} = 1800$

$$- \frac{di}{dt} = 200A/\mu s, \frac{du}{dt} = 1000V/\mu s$$

3. Value protection

- RC circuit connected parallel with thyristor to protects current rate and voltage rate:

$$L_a = \frac{\sqrt{6} U_2}{2 \left(\frac{du}{dt} \right)} = 0,184(\mu H)$$

$$C > \frac{8L_a}{R} = 0,59(\mu F)$$

$$R = \frac{L_a}{\sqrt{6} U_2} \left(\frac{du}{dt} \right) = 2,5(\Omega)$$



- $R_f C_f$ to protect input secondary rectifier

$$C_f = \frac{mI_o}{\omega a^2 U_2 (K^2 - 1)} = 4(\mu F)$$

$$R_f = 2 \sqrt{\frac{2L_a}{C_f}} = 12,5(\Omega)$$

- Fuses CC protects short circuit in valve circuit

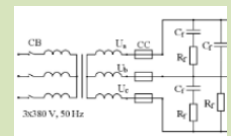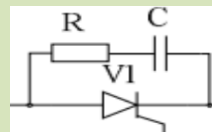- Aptomats CB protect schematic valve short circuit and transformer short circuit.



4. Calculate balanced reactor

$$L_{cb} \geq \frac{U_2}{6\omega 0,1 I_d} = 4,43 \cdot 10^{-5}(H)$$

Choose $L_{cb} = 0,45 \cdot 10^{-6}(H)$

5. Filter coil

The filter coil can be added at the output to make the signal output flatter. Choose $L_{filter} = 1(mH)$