

(Documents are allowed to use. Return the question sheet)

Student's name: ..... Student Code: .....

**Question 1** (3 pts)

A given circuit in figure 1: All sources have the same frequency.

- Write a set of equation by using mesh analysis (the direction of the mesh currents is given)?
- Express the branch currents with given direction in term of the mesh currents.

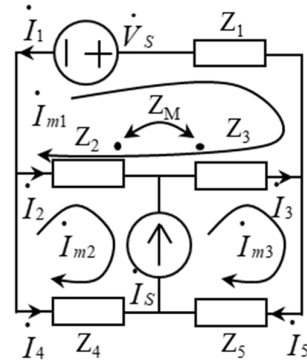


Figure 1

**Question 2** (3 pts)

A given circuit in figure 2, where:  $R = 50\Omega$ ,  $R_L = 25\Omega$ ,  $L = 0,5H$ ,  $C = 2 \cdot 10^{-4}F$ ,  $i_s(t) = 2\sqrt{2} \sin(100t) A$ ,  $V_s = 60V(DC)$ , the parameter  $Z = \begin{bmatrix} 20 & 10 \\ 10 & 30 \end{bmatrix} \Omega$ .

- Find the RMS value of  $i_L(t)$
- Find the average power supplied by each source and the average power delivered to the  $Z$  parameter.

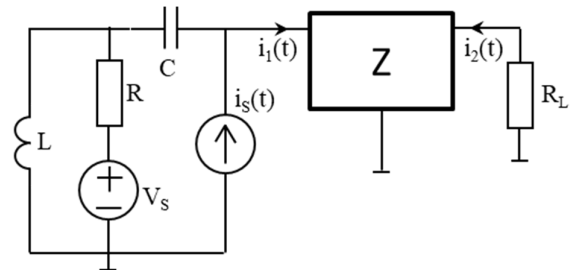


Figure 2

**Question 3** (3 pts)

A given circuit in figure 3, where:  $R_1 = 30\Omega$ ,  $R_2 = 20\Omega$ ,  $R_3 = 40\Omega$ ,  $L_1 = 12H$ ,  $L_2 = 6H$ ,  $M = 8H$ ,  $V_{S1} = 10V(DC)$ ,  $V_{S2} = 20V(DC)$ .

Find the step response  $i_2(t)$  when the switch  $K$  is opened at the time  $t = 0$ ?

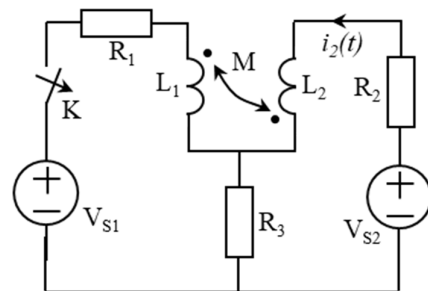


Figure 3

**Note:** Good representation: 1 pt