




Thứ . . . ngày . . .

Name : Lê Hoàng Thịnh

MSSV : 20181928

class code : 123153

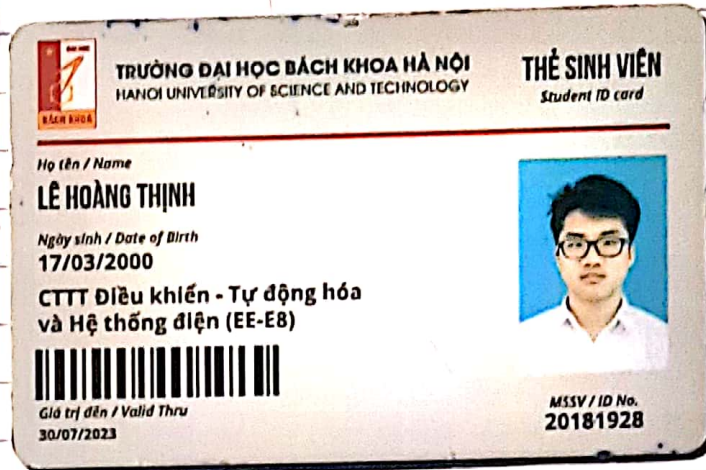

Đề 1

Question 1:

High power frequency switching preferred in modern converter because it allows the use of a smaller inductor (and input and output filter capacitor). This is because the inductor size is primarily determined by the amount of ripple current allowed in a given switching regulator's specification. For a given inductor, the ripple current decreases as the switching frequency increases and this will help reduce the size and the cost of power supply.


To reduce the loss switching loss, we can use zero voltage switching or zero current switching

Question 2:

ⓐ Topology (choose $K_I = 3$; $K_u = 2$)



Thư ngáy

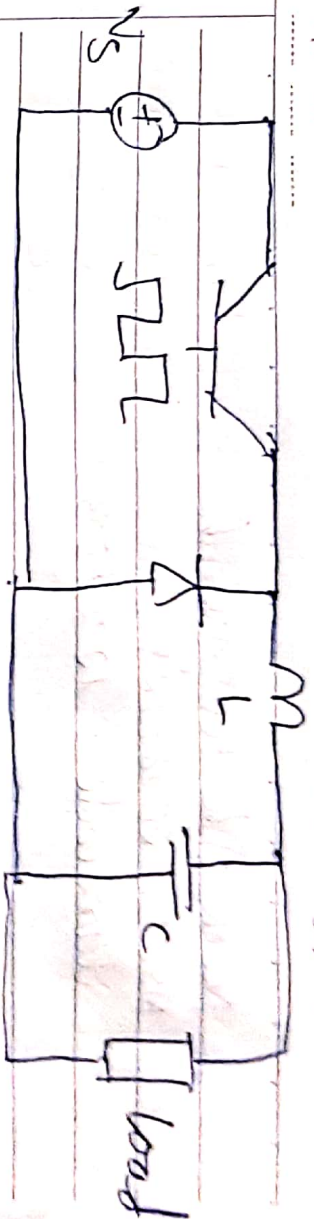

$$D = \frac{V_{out}}{V_{in, max}} = \frac{12}{48.15} = 0.22$$

$\Delta I = 30\%$ calculate inductor. (choose $\Delta I\% = 30\%$)

$$\Delta I = \frac{(V_{in, max} - V_{out}) D}{f_s \cdot L}$$

$$\Rightarrow L = \frac{(V_{in, max} - V_{out}) D}{f_s \cdot \Delta I} = \frac{(48.15 - 12) \cdot 0.22}{100 \cdot 10^3 \cdot 0.3} = 48.88 \mu H \approx 0.08 \text{ mH}$$

I_{avg} of inductor is $I_{out} = 4 \text{ (A)}$

\Rightarrow peak of inductor is

So we choose inductor $L = 0.08 \text{ mH}$

\oplus choose capacitor

$$C_{out, min} = \frac{\Delta I}{8 f_s \Delta V_{out}} = \frac{3.125}{8 \cdot 100 \cdot 10^3 \cdot 25} = 1.56 \mu F$$

V_C reverse = $48.12 \cdot 1.04 = 12.48 \text{ (V)}$

choose capacitor $C = 3.5 \mu F$

$K_V \cdot 12.5 = 25 \text{ V}$

\oplus MOSFET:

$$I_{avg} = I_{load} \cdot D = 4 \cdot 0.22 = 0.88 \text{ (A)}$$

$$I_{peak} = I_{load} + \frac{1}{2} \Delta I = 4.6 \text{ (A)}$$

$$V_{peak} = V_{in \max} = 48,15 = 55,2 (V)$$

$$\Rightarrow \text{choose MOSFET} \begin{cases} V_{peak} = 111 V \\ I_{avg} = 3 A \\ I_{peak} = 4,6 A \end{cases}$$

⊕ Diode.

$$I_{avg} = I_{load} (1-D) = 3,12 (A)$$


$$I_{peak} = I_{load} + \frac{1}{2} \Delta I = 4,6 (A)$$

$$V_{peak} = V_{in \max} \frac{2}{2} = 55,2 (V)$$

$$\Rightarrow \text{choose Diode} \begin{cases} V_{peak} = 111 V \\ I_{avg} = 10 A \\ I_{peak} = 4,6 A \end{cases}$$

Questions:

$$K_I = 3; K_V = 2$$

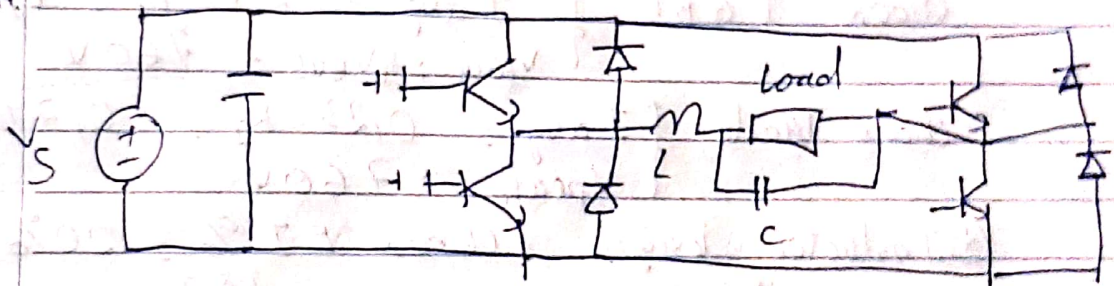

⊕ DC voltage calculation:

Choose $M_{max} = 0,9$ and drop voltage on the output filter ΔV be about 10% of output voltage

$$\Rightarrow V_{BUS} = \frac{U_{OM}}{0,9} \cdot 1,1 = \frac{220 \sqrt{3}}{0,9} \cdot 1,1$$

$$= 346 \approx 380 V$$

⊕ calculate the amplitude of the output current

$I_{OM} (A)$

$$\text{RMS value: } I_o = \frac{S_o}{U_o} = \frac{1100}{220} = 5 (A)$$

$$\text{Amplitude: } I_{OM} = 5 \cdot \sqrt{2} = 7,07 (A)$$



Thứ ngày . . .

④ IGBT and Diode calculation. (Choose $\cos \phi = 0,8$)

IGBT average current:

$$I_v = \frac{1}{2\pi} \cdot (1 + \cos \phi) \cdot \frac{1}{2\pi} \int_{\phi}^{\pi} I_{OM} \sin(\theta - \phi) d\theta$$
$$= \frac{1 + \cos \phi}{2\pi} I_{OM}$$

$$= 2,03 \text{ (A)}$$

Diode average current:

$$I_D = \frac{1}{2\pi} \int_0^{\phi} I_{OM} \sin(\theta - \phi) d\theta$$
$$= \frac{1 - \cos \phi}{2\pi} I_{OM} = 0,23 \text{ (A)}$$

$$\text{Choose IGBT } \begin{cases} I_{avg} = 2,03 \cdot K_I = 6,09 \text{ (A)} \\ V_{peak} = K_V V_{BUS} = 760 \text{ V} \end{cases}$$

$$\text{Choose Diode } \begin{cases} I_{avg} = 0,23 \cdot K_I = 0,7 \text{ (A)} \\ V_{peak} = 760 \text{ V} \end{cases}$$

④ Inductor Design (Choose $\Delta I \% = 20\%$)

$$L_i = \frac{V_{BUS}}{4 f_{SW} \cdot \Delta I_{pp}/max} = \frac{380}{4 \cdot 10^4 \cdot 7,07 \cdot 0,2}$$
$$= 6,72 \text{ (mH)}$$

Check drop voltage (less than 10 %)

$$\text{Drop voltage} = W_s \cdot L_i \cdot I_o$$
$$= 100 \mu\text{s} \cdot 6,72 \cdot 10^{-3} \cdot 5$$
$$= 10,56 \text{ (} \sim 4,8 \% V_{out} \text{)}$$

$$I_{avg} = I_o = 5 \text{ (A)}$$

$$\text{Choose inductor } \begin{cases} L = 6,72 \text{ mH} \\ I_{avg} = 5 \cdot K_I = 15 \text{ (A)} \end{cases}$$

④ Capacitor:

$$\text{Choose } W_{CL} = 0,1 W_{SW} = 2000 \mu\text{J}$$
$$C = \frac{1}{L \cdot W_{CL}^2} = 3,77 \text{ (} \mu\text{F)}$$

④

HONGHA



$$V_{peak} = V_{out peak} = 310 \text{ V}$$

$$\Rightarrow \text{choose capacitor } \begin{cases} C = 3,177 \text{ MF} \\ V_{peak} = K_u \cdot 310 = 620 \text{ V} \end{cases}$$

⊕ DC capacitor: ~~Worst~~ worst case = 0,5, ripple = 5%

$$\Delta U_C = \frac{0,5 T_{SW}}{C} \cdot I_C$$

$$\Rightarrow C = \frac{0,5 T_{SW}}{\Delta U_C} \cdot I_{out max} = 18,6 \text{ MF}$$

$$V_{peak} = V_{in p} = 380 \text{ V}$$

$$\Rightarrow \text{choose } \begin{cases} C = 18,6 \text{ MF} \\ V_{peak} = K_u \cdot 380 = 760 \text{ (V)} \end{cases}$$

Question 5: ⊕ DC voltage calculation. V_{BUS}

$$V_{BUS} = \text{choose } m = 0,8$$

$$U_0 = 150 \text{ e } 308 \text{ f}$$

$$U_0 = 150 \text{ e } 50$$

$$\Rightarrow U_0 = 129,9 + 75 \text{ J}$$

$$\Rightarrow \begin{cases} U_A = 129,9 \text{ V} \\ U_B = 75,25 \text{ V} \end{cases} \Rightarrow \text{Sector 1}$$

$$T_1 = \frac{T_S}{2V_{DC}} \cdot (3V_A - \sqrt{3}V_B)$$

$$= \frac{1}{10^4 \cdot 2 \cdot 540} \cdot (3 \cdot 129,9 - \sqrt{3} \cdot 75,25)$$

$$= 2,14 \cdot 10^{-5}$$

$$T_2 = \frac{T_S}{V_{DC}} \cdot (\sqrt{3}V_B)$$

$$= \frac{1}{10^4 \cdot 540} \cdot \sqrt{3} \cdot 75,25 = 2,14 \cdot 10^{-5}$$

$$10^4 \cdot 540$$



Thứ ngày . . .

$$T_0 = T_s - T_1 - T_2 = \frac{5,2}{2,4} \cdot 10^{-5} (s)$$

Pulse waveform

T_0	T_1	T_2	T_0	T_0	T_2	T_1	T_0
4	2	2	4	4	2	2	4

~~V1~~
V1


V4

V3

V6


V5

V2

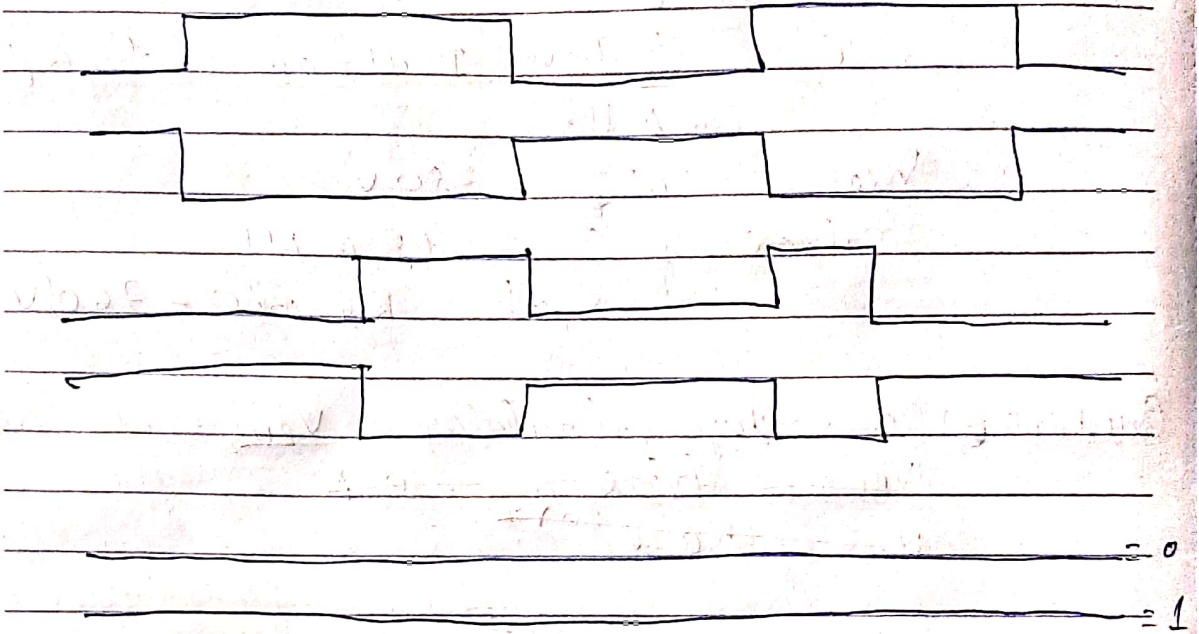

Question:
 ① Definition: Solid-state (Semiconductor relay) is a semiconductor device that can be used in place of a mechanical relay to switch electricity to a load in many applications. It is typical feature electrical isolation to several thousand volts between the control and load sites sides. It is quite common component nowadays but they are still quite expensive compared to their complexity.
 ② Topology:

Control voltage

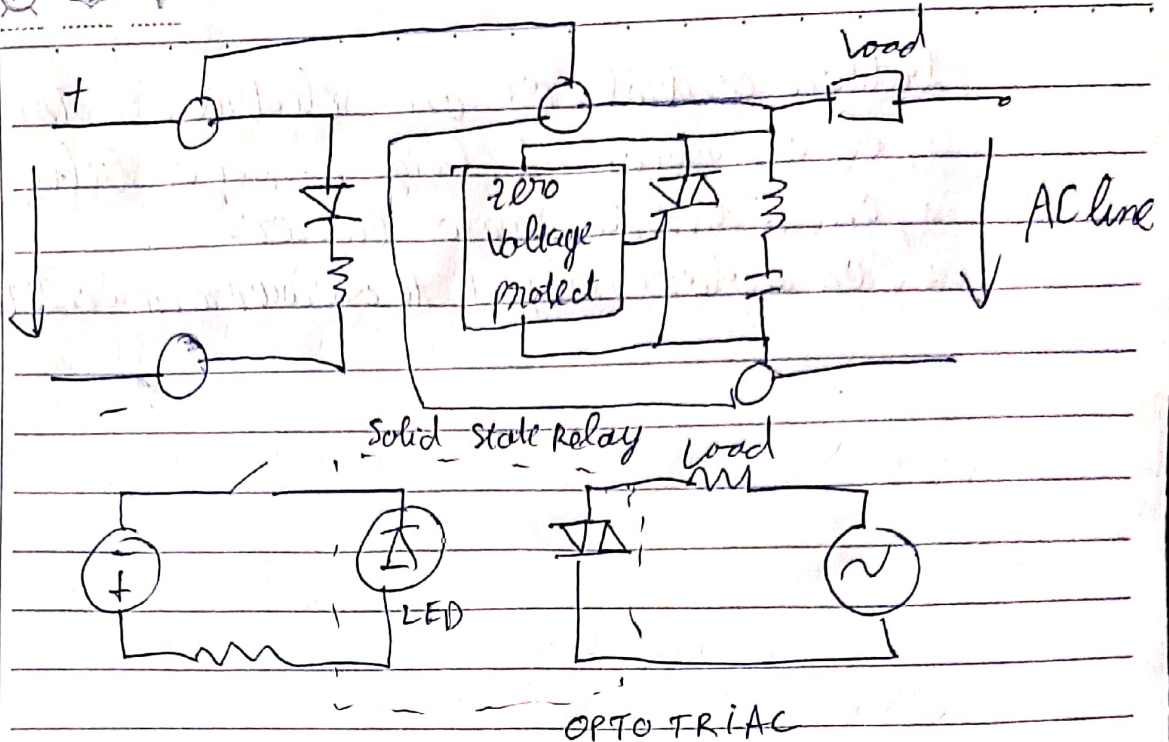

⊕ Basic operation principle: It has the characteristics of being turned on when the voltage crosses zero and being turned off when the load current crosses zero. When opto-coupler OPT is turned off, ~~It~~ turned on

⊕ Advantage:

- + No mechanical moving parts
- + High switching speed
- + High reliability
- + Long operating life
- + High input output isolation

⊕ Disadvantage:

- + output gets damaged quite easily by overvoltages
- + More expensive than normal relays
- + More sensitive to voltage transients

⊕ Application:

~~It can be used~~

It can be used as with classic push



Thứ ngày

button control or on electric-motor such as:
+, on the motor of large conveyor belts
+, on industrial motor blowers
+, on motors subject to overcurrent conditions

