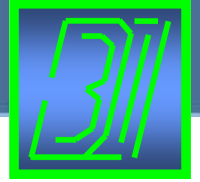




TRƯỜNG ĐẠI HỌC
BÁCH KHOA HÀ NỘI

Nguyễn Công Phương



Electric Circuit Theory

Three-phase Circuits

Contents

- I. Basic Elements Of Electrical Circuits
- II. Basic Laws
- III. Electrical Circuit Analysis
- IV. Circuit Theorems
- V. Active Circuits
- VI. Capacitor And Inductor
- VII. First Order Circuits
- VIII. Second Order Circuits
- IX. Sinusoidal Steady State Analysis
- X. AC Power Analysis
- XI. Three-phase Circuits**
- XII. Magnetically Coupled Circuits
- XIII. Frequency Response
- XIV. The Laplace Transform
- XV. Two-port Networks



Three-phase Circuits

1. Introduction
2. Three-phase Source
3. Three-phase Load
4. Three-phase Circuit Analysis
5. Power in Three-phase Circuits





Introduction (1)

- Polyphase:
 - Phase: branch, circuit or winding
 - Poly: many
- Three-phase: three phases
- Advantages:
 - Machine: less space & less cost
 - Transmission & distribution: less conducting material
 - Power delivered to a three-phase load is always constant
 - Single phase source from three-phase source



Three-phase Source (1)

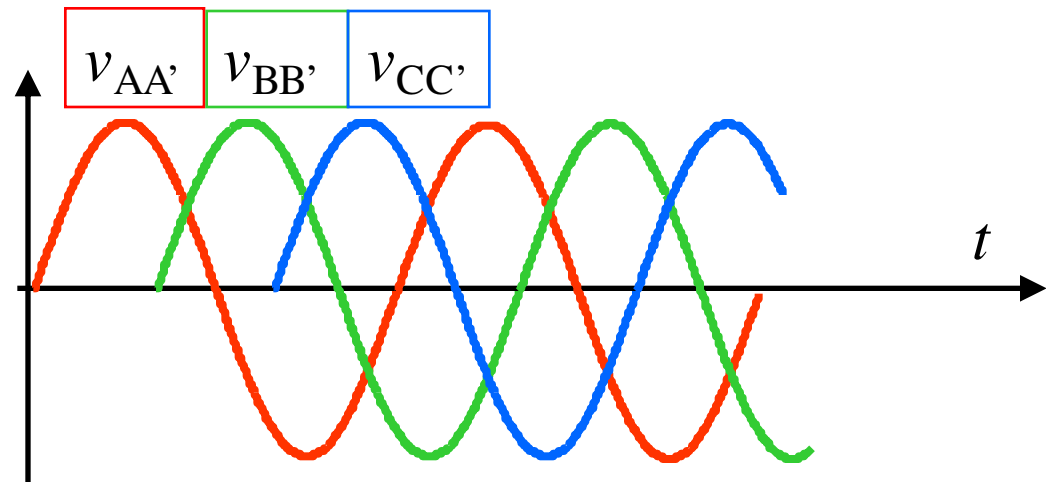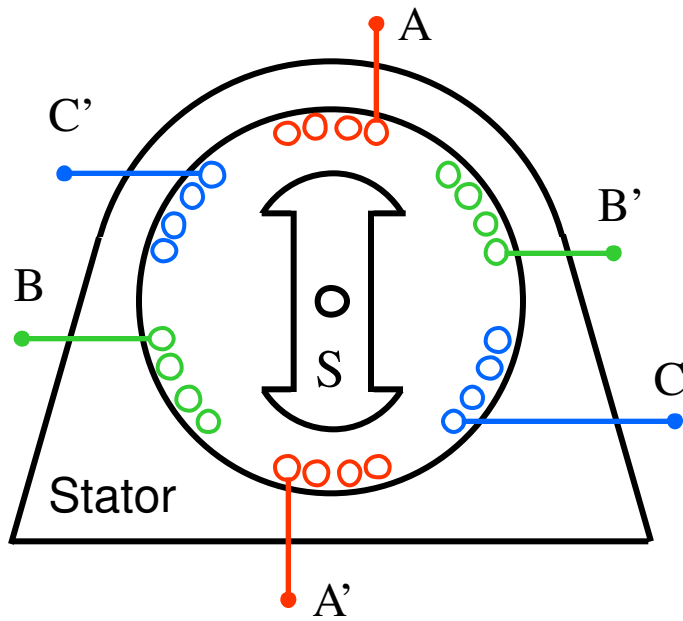

$$v_{AA'} = V_m \sin \omega t$$

$$v_{BB'} = V_m \sin(\omega t - 120^\circ)$$


$$v_{CC'} = V_m \sin(\omega t + 120^\circ)$$

Three-phase Source (2)

$$v_{AA'} = V_m \sin \omega t$$

$$v_{BB'} = V_m \sin(\omega t - 120^\circ)$$
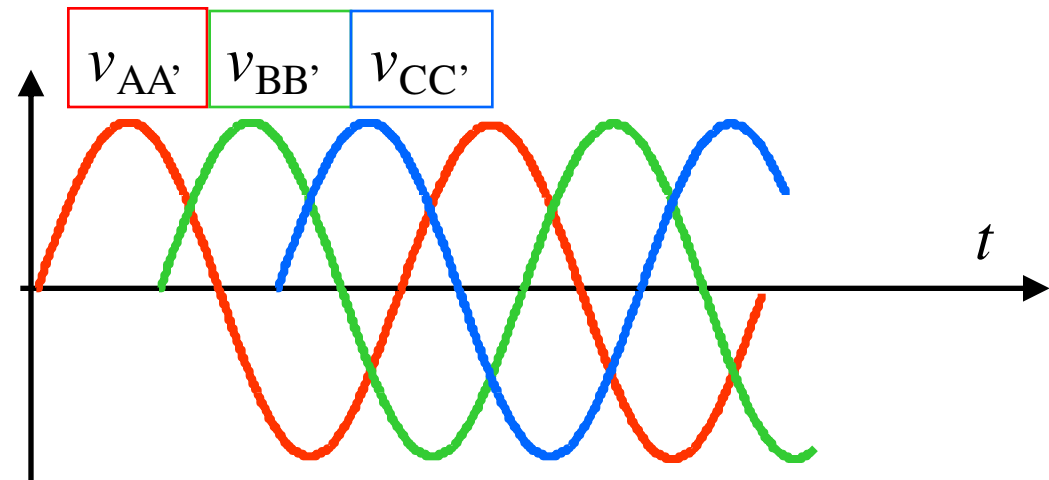
$$v_{CC'} = V_m \sin(\omega t + 120^\circ)$$




$$v_{AA'} + v_{BB'} + v_{CC'} =$$

$$= V_m (\sin \omega t + \sin \omega t \cos 120^\circ - \cos \omega t \sin 120^\circ + \sin \omega t \cos 120^\circ + \cos \omega t \sin 120^\circ)$$

$$= V_m (\sin \omega t + 2 \sin \omega t \cos 120^\circ)$$

$$= V_m \left[\sin \omega t + 2 \sin \omega t \left(\frac{-1}{2} \right) \right] = 0$$

$$v_{AA'} + v_{BB'} + v_{CC'} = 0$$

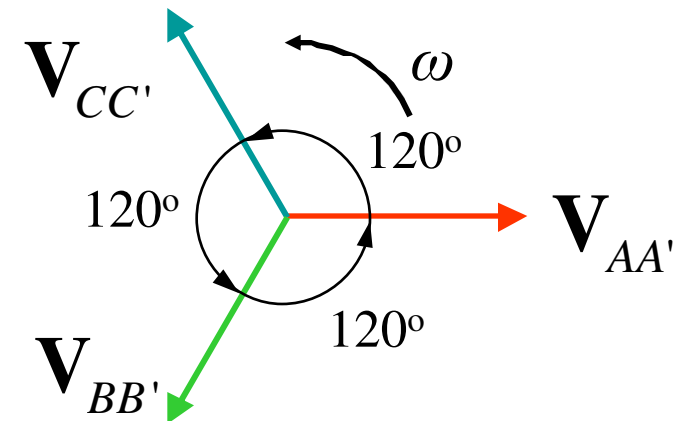



Three-phase Source (3)

$$v_{AA'} = V_m \sin \omega t$$

$$v_{BB'} = V_m \sin(\omega t - 120^\circ)$$

$$v_{CC'} = V_m \sin(\omega t + 120^\circ)$$




$$v_{AA'} + v_{BB'} + v_{CC'} = 0$$

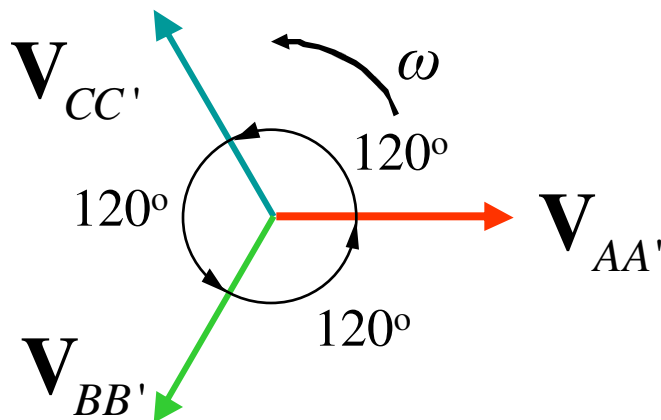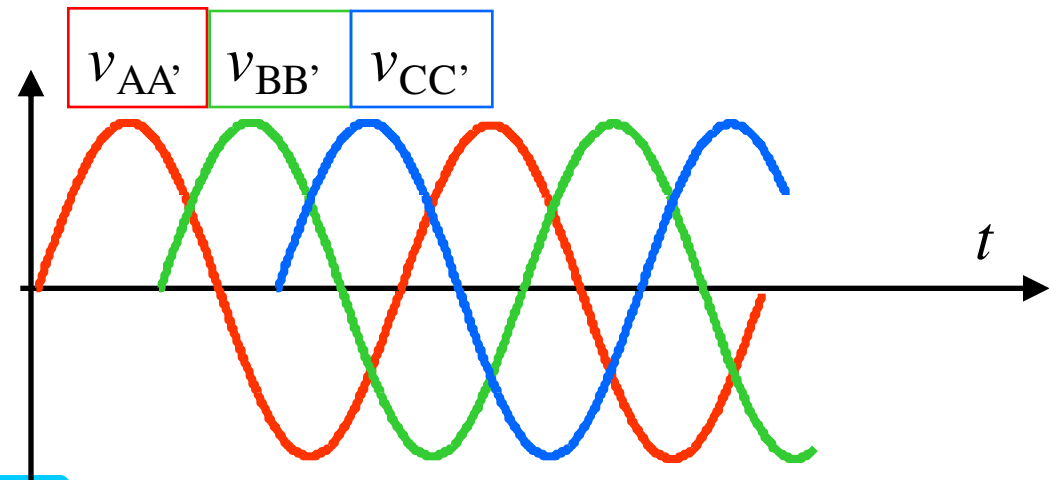





Symmetrical (balanced) Three-phase Source:

- Same magnitude
- Same frequency
- Displaced from each other by 120°


Three-phase Source (4)

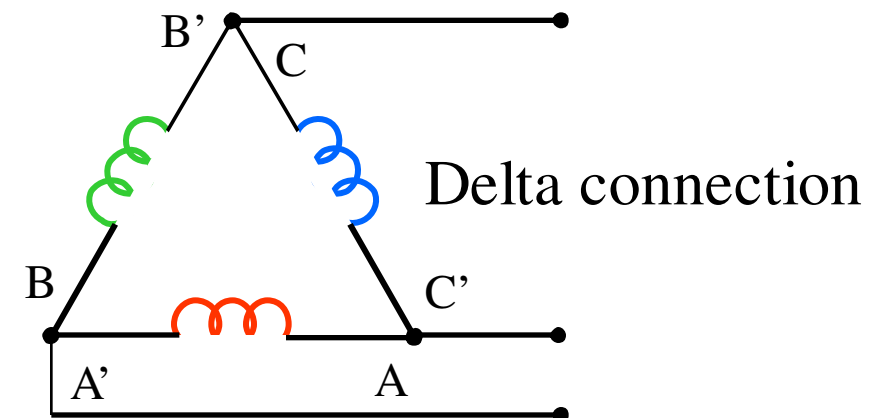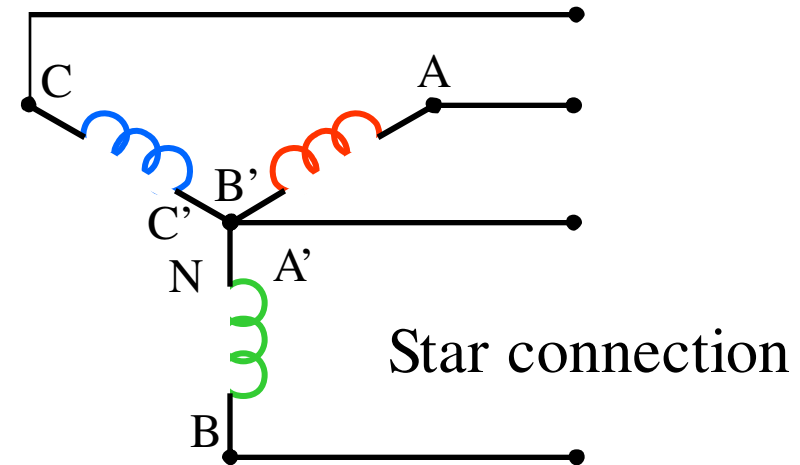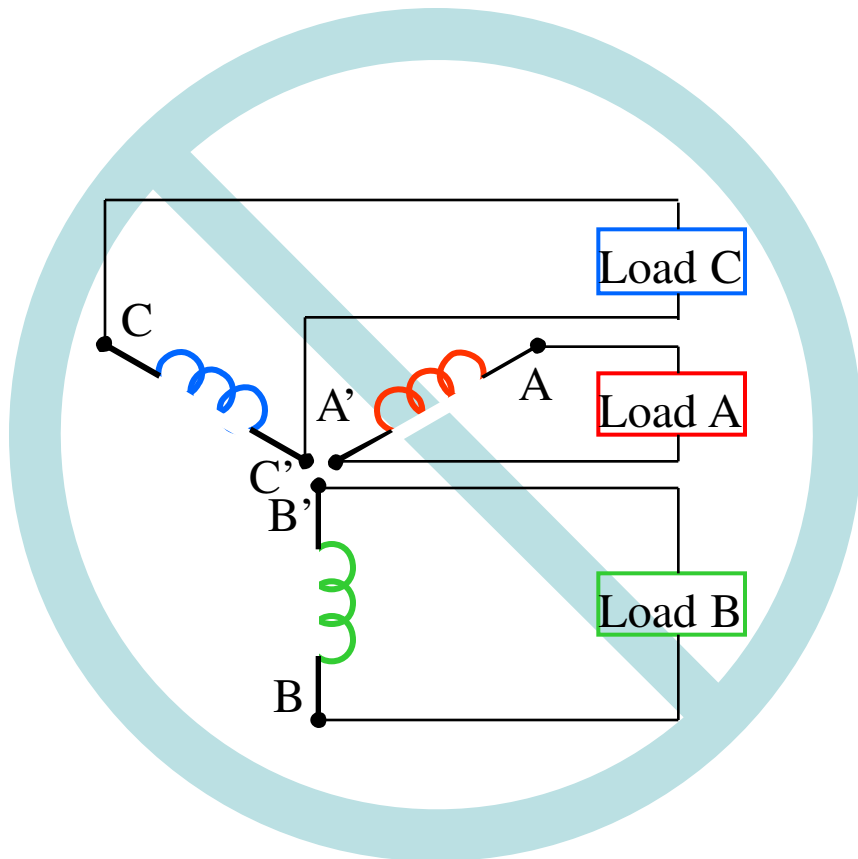

Three-phase Source (5)

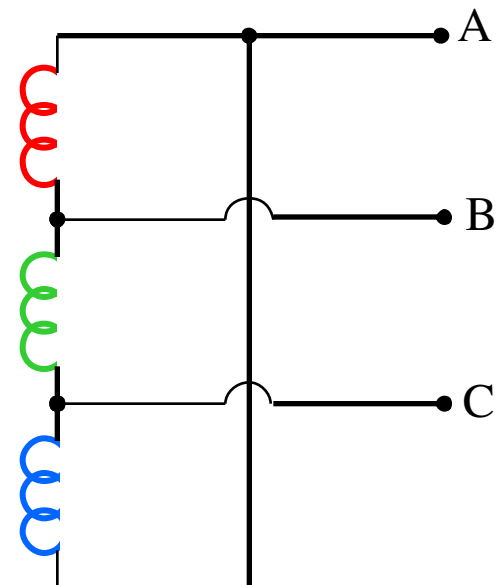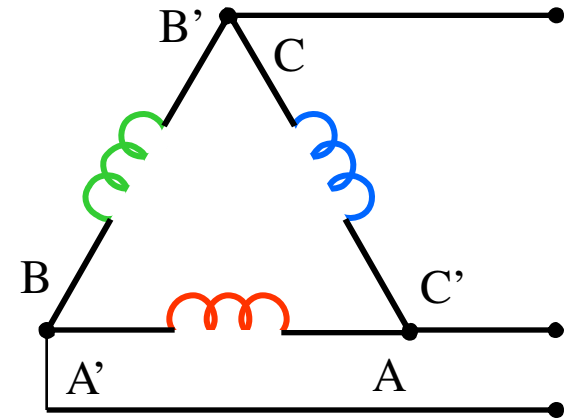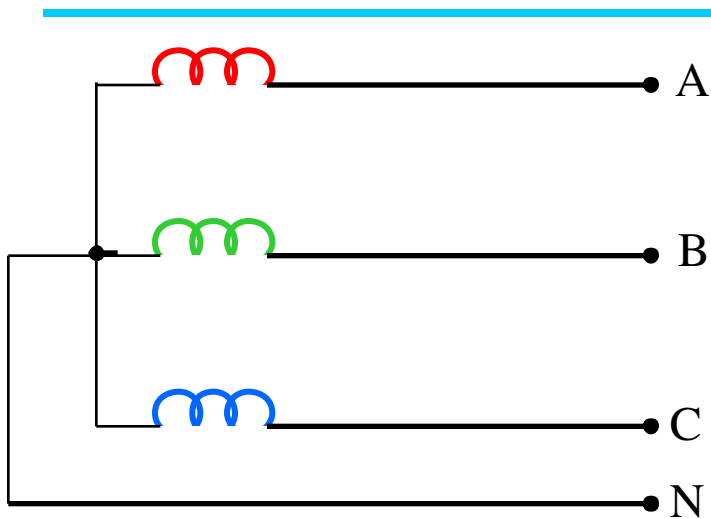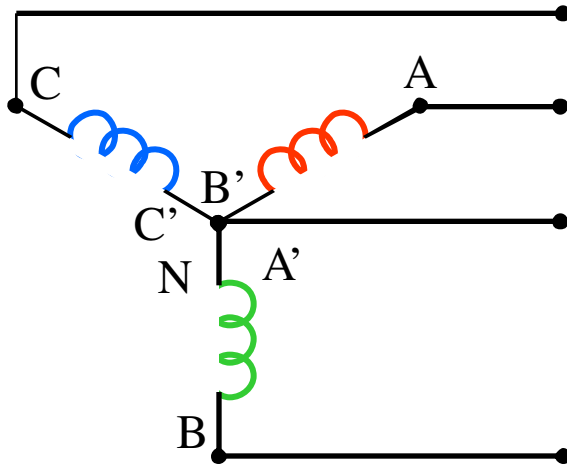


Three-phase Source (6)

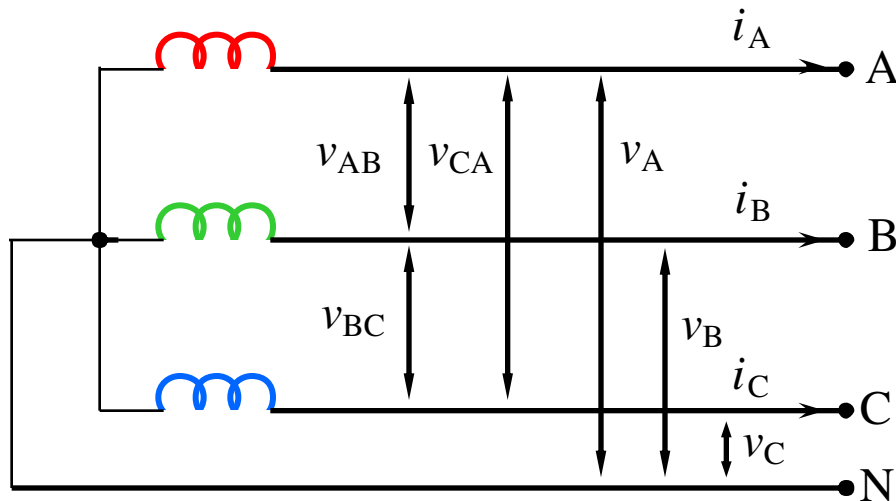

v_{AB} , v_{BC} , v_{CA} : line voltages

v_A , v_B , v_C : phase voltages

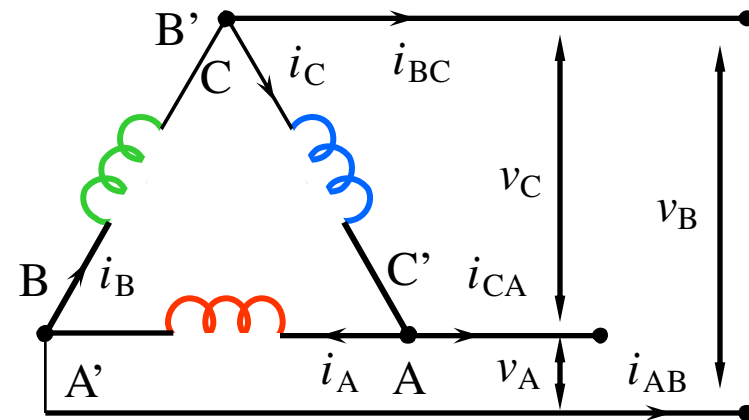i_A , i_B , i_C : line currents/phase currents



v_A , v_B , v_C : line voltages/phase voltages

i_{AB} , i_{BC} , i_{CA} : line currents

i_A , i_B , i_C : phase currents

Three-phase Source (7)

$$\mathbf{V}_A = V \angle 0^\circ$$


$$\mathbf{V}_B = V \angle -120^\circ$$

$$\mathbf{V}_C = V \angle 120^\circ$$

$$\begin{aligned} \mathbf{V}_{AB} &= \mathbf{V}_{AN} + \mathbf{V}_{NB} = \mathbf{V}_{AN} - \mathbf{V}_{BN} \\ &= V \angle 0^\circ - V \angle -120^\circ = V \left(1 + \frac{1}{2} + j\frac{\sqrt{3}}{2} \right) = \sqrt{3}V \angle 30^\circ \end{aligned}$$

$$\mathbf{V}_{BC} = \sqrt{3}V \angle -90^\circ$$
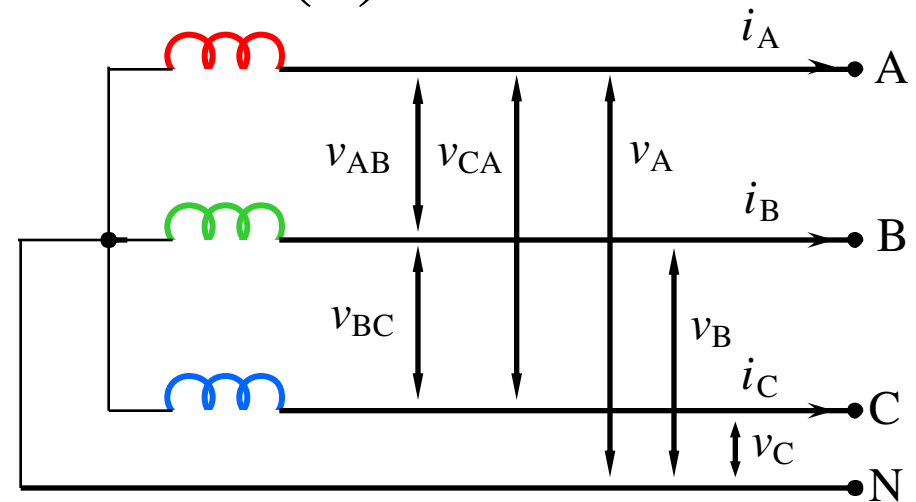
$$\mathbf{V}_{CA} = \sqrt{3}V \angle -210^\circ$$





$$\mathbf{V}_{line} = \mathbf{V}_{phase} \sqrt{3} \angle 30^\circ$$

Three-phase Source (8)

$$\mathbf{V}_A = V \angle 0^\circ$$

$$\mathbf{V}_{BN} = V \angle -120^\circ$$

$$\mathbf{V}_{CN} = V \angle 120^\circ$$

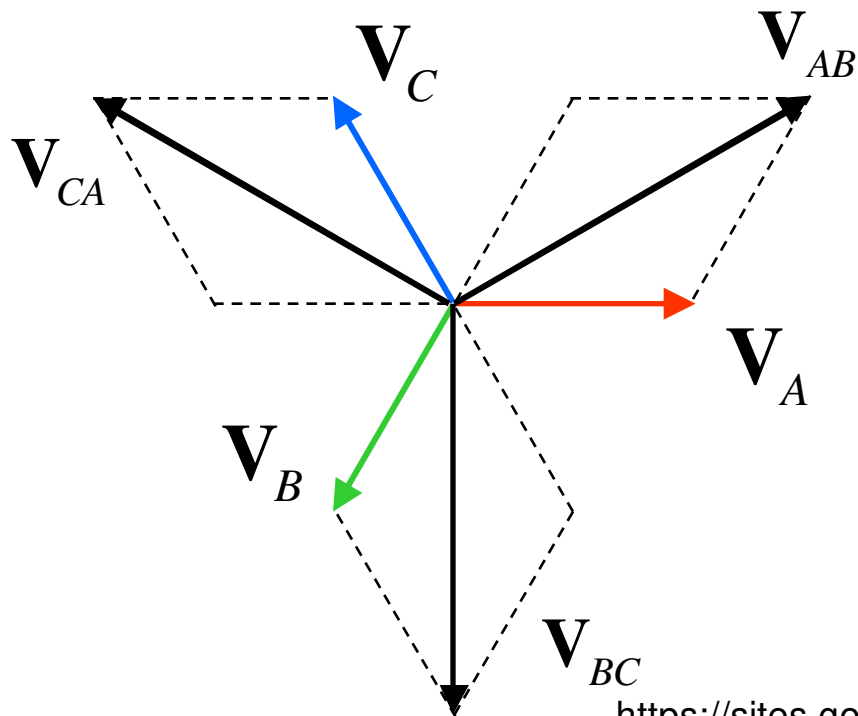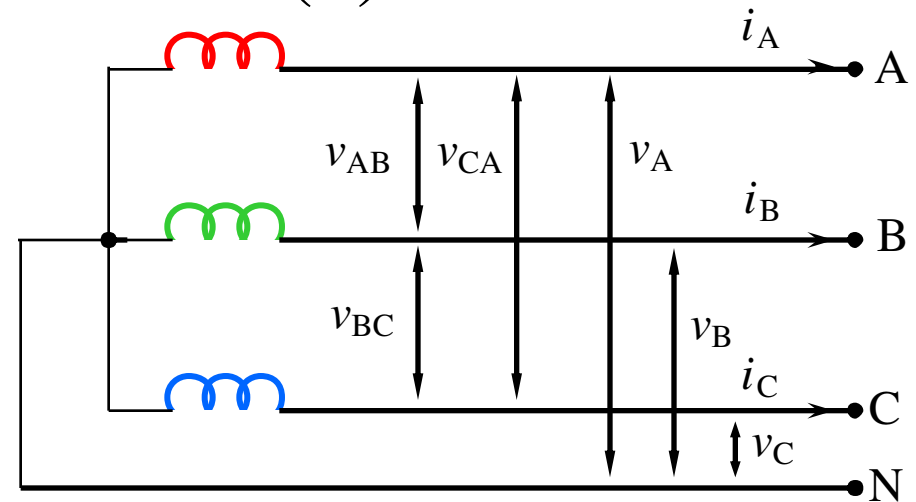

$$\mathbf{V}_{AB} = \sqrt{3}V \angle 30^\circ$$

$$\mathbf{V}_{BC} = \sqrt{3}V \angle -90^\circ$$



$$\mathbf{V}_{CA} = \sqrt{3}V \angle -210^\circ$$

Three-phase Circuits

1. Introduction
2. Three-phase Source
- 3. Three-phase Load**
4. Three-phase Circuit Analysis
5. Power in Three-phase Circuits



Three-phase Load

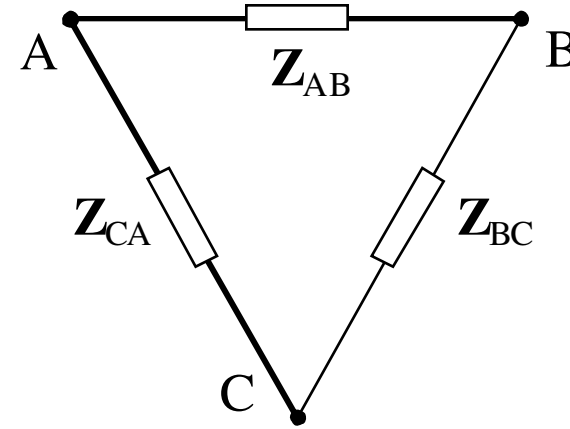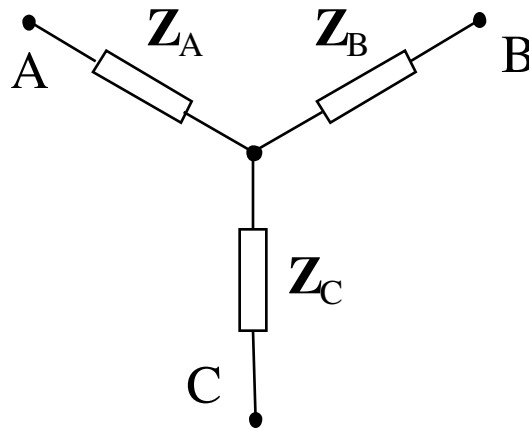

$$Z_A = \frac{Z_{CA} Z_{AB}}{Z_{AB} + Z_{BC} + Z_{CA}}$$

$$Z_B = \frac{Z_{AB} Z_{BC}}{Z_{AB} + Z_{BC} + Z_{CA}}$$

$$Z_C = \frac{Z_{BC} Z_{CA}}{Z_{AB} + Z_{BC} + Z_{CA}}$$

$$Z_{AB} = \frac{Z_A Z_B + Z_B Z_C + Z_C Z_A}{Z_C}$$

$$Z_{BC} = \frac{Z_A Z_B + Z_B Z_C + Z_C Z_A}{Z_A}$$


$$Z_{CA} = \frac{Z_A Z_B + Z_B Z_C + Z_C Z_A}{Z_B}$$

Three-phase Circuits


1. Introduction
2. Three-phase Source
3. Three-phase Load
- 4. Three-phase Circuit Analysis**
5. Power in Three-phase Circuits




Three-phase Circuit Analysis (1)

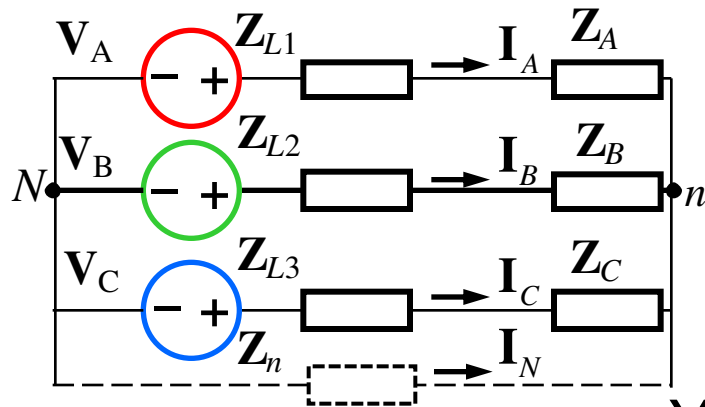


Y-Y

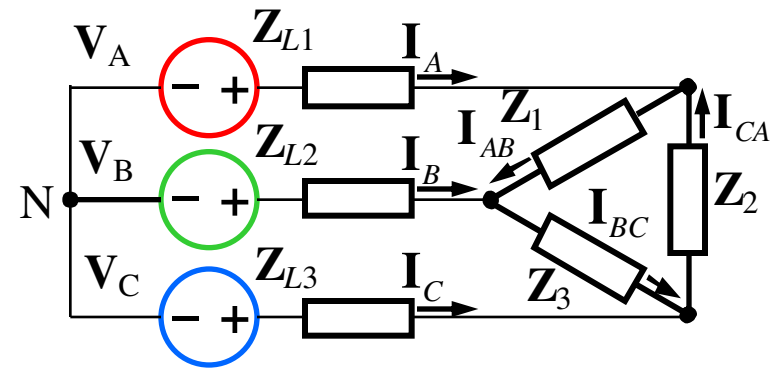

Y-Δ

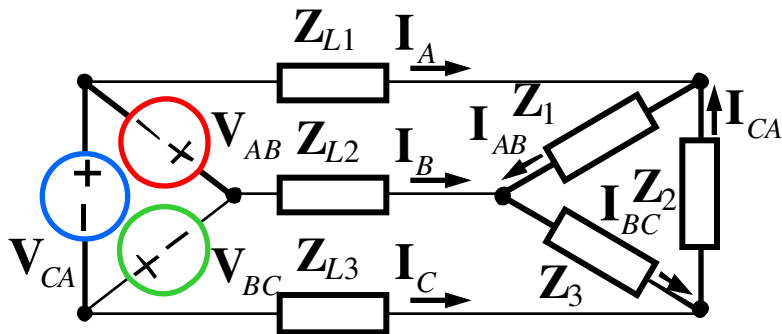

Δ-Δ

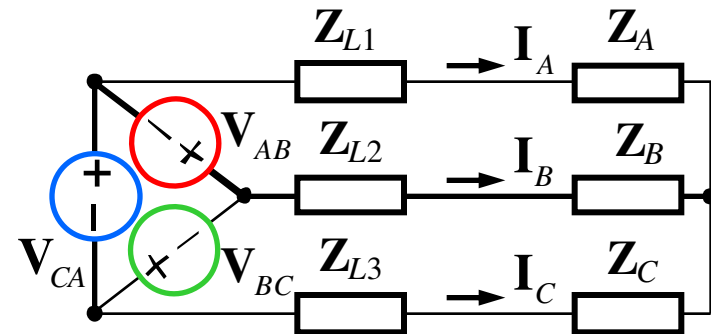

Δ-Y

Three-phase Circuit Analysis (2)

- Y-Y, Y- Δ , Δ - Δ , Δ -Y
- 2 kinds of three-phase circuit: balanced & unbalanced
- Balanced three-phase circuit:
 - Balanced three-phase source and balanced three-phase load
 - **Balanced three-phase source**: same magnitude, same frequency, displaced from each other by 120°
 - **Balanced three-phase load**: three identical loads
- Unbalanced three-phase circuit:
 - Unbalanced three-phase source and/or unbalanced three-phase load
- To solve a balanced one:
 - Exploit the symmetry of a balanced three-phase circuit, or
 - Treat it like a normal three-source circuit
- To solve an unbalanced one:
 - Treat it like a normal three-source circuit



Three-phase Circuit Analysis (3), Y–Y

Suppose $V_N = 0$


$$\left\{ \begin{aligned} \left(\frac{1}{Z_Y} + \frac{1}{Z_Y} + \frac{1}{Z_Y} + \frac{1}{Z_N} \right) V_n &= \frac{V_A}{Z_Y} + \frac{V_B}{Z_Y} + \frac{V_C}{Z_Y} \\ V_A + V_B + V_C &= 0 \end{aligned} \right.$$

$$\rightarrow V_n = 0 \rightarrow \boxed{V_{Nn} = 0}$$

$$\rightarrow I_A = \frac{V_A - V_n}{Z_Y} = \frac{V / 0^\circ - 0}{Z_Y} = \frac{V / 0^\circ}{Z_Y}$$

$$I_B = \frac{V_B}{Z_Y} = \frac{V_A \times 1 / -120^\circ}{Z_Y} = I_A \times 1 / -120^\circ$$
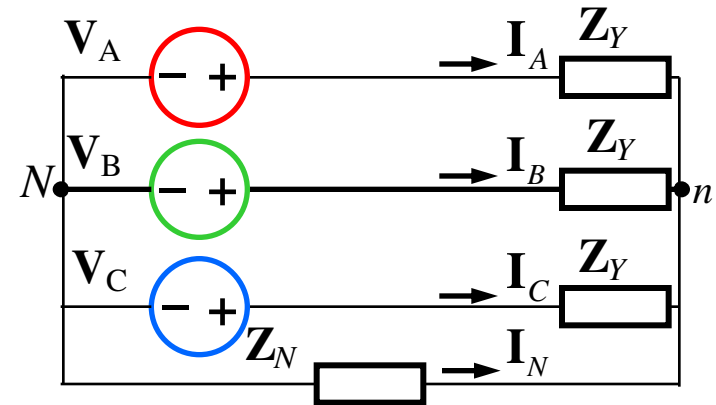
$$I_C = \frac{V_C}{Z_Y} = \frac{V_A \times 1 / 120^\circ}{Z_Y} = I_A \times 1 / 120^\circ$$



$$I_A + I_B + I_C = 0$$


$$I_N = 0$$

Three-phase Circuit Analysis (4), Y–Y

$$\mathbf{I}_A = \frac{\mathbf{V}_A}{\mathbf{Z}_Y} = \frac{V / 0^\circ}{\mathbf{Z}_Y}$$


$$\mathbf{I}_B = \mathbf{I}_A \times 1 / -120^\circ$$
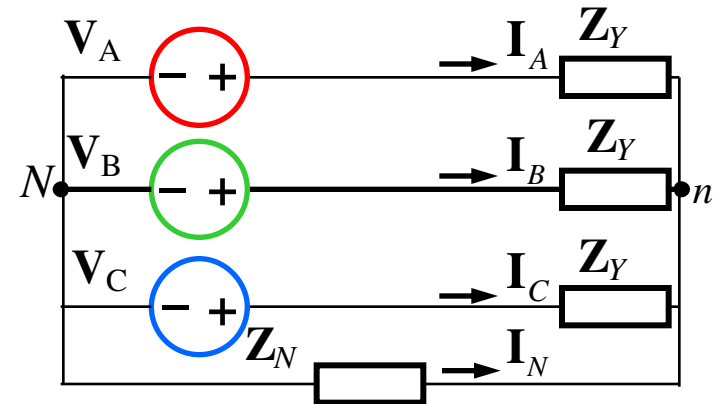
$$\mathbf{I}_C = \mathbf{I}_A \times 1 / 120^\circ$$



For a balanced Y–Y system:

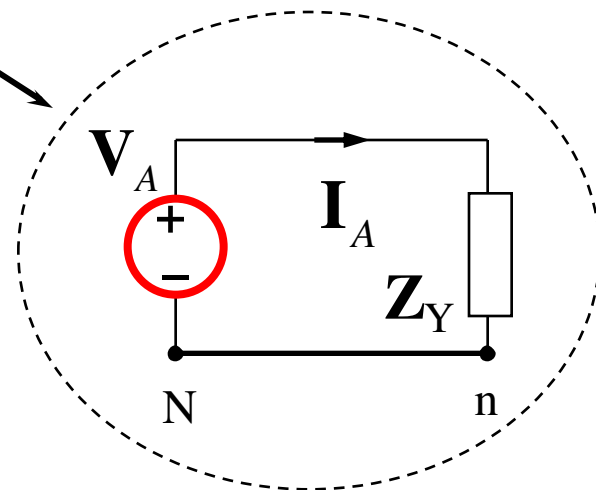1. Draw a single-phase equivalent circuit (A-phase)
2. Find the current in the A-phase
3. Write down the currents in the two other phases



Ex. 1 Three-phase Circuit Analysis (5), Y–Y

$Z_Y = 30 + j40 \Omega$; find phase currents?



For a balanced Y–Y system:

1. ✓ Draw a single-phase equivalent circuit (A-phase)
2. ✓ Find the current in the A-phase
3. ✓ Write down the currents in the two other phases

$$I_A = \frac{220 \angle 0^\circ}{Z_Y} = \frac{220 \angle 0^\circ}{30 + j40} = 4.4 \angle -53.1^\circ \text{ A}$$

$$I_B = I_A \times 1 \angle -120^\circ = 4.4 \angle -53.1^\circ - 120^\circ = 4.4 \angle -173.1^\circ \text{ A}$$
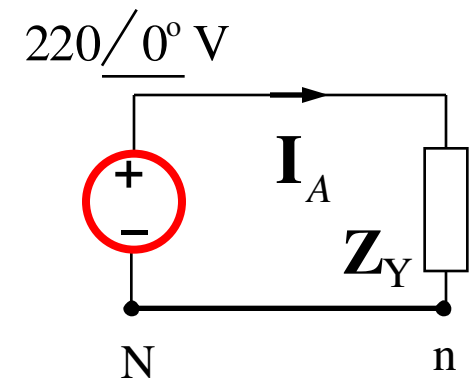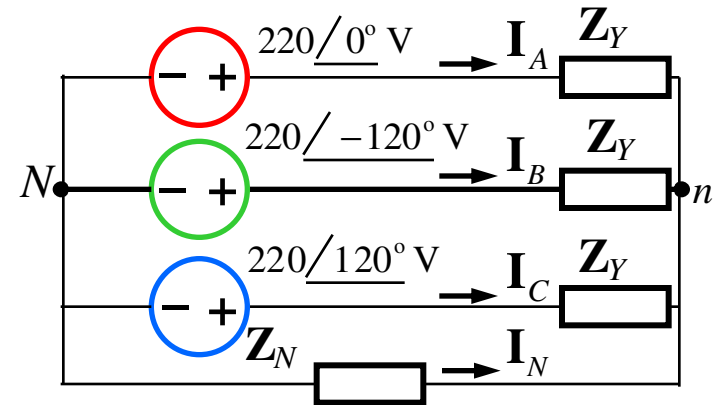
$$I_C = I_A \times 1 \angle 120^\circ = 4.4 \angle -53.1^\circ + 120^\circ = 4.4 \angle 66.9^\circ \text{ A}$$



Three-phase Circuit Analysis

- Y-Y, **Y-Δ**, Δ-Δ, Δ-Y
- 2 kinds of three-phase circuit: balanced & unbalanced
- **Balanced three-phase circuit:**
 - Balanced three-phase source and balanced three-phase load
 - *Balanced three-phase source*: same magnitude, same frequency, displaced from each other by 120°
 - *Balanced three-phase load*: three identical loads
- Unbalanced three-phase circuit:
 - Unbalanced three-phase source and/or unbalanced three-phase load
- To solve a balanced one:
 - Exploit the symmetry of a balanced three-phase circuit, or
 - Treat it like a normal three-source circuit
- To solve an unbalanced one:
 - Treat it like a normal three-source circuit




Three-phase Circuit Analysis (6), Y- Δ

$$\mathbf{V}_A = V \angle 0^\circ$$

$$\mathbf{V}_B = V \angle -120^\circ$$

$$\mathbf{V}_C = V \angle 120^\circ$$

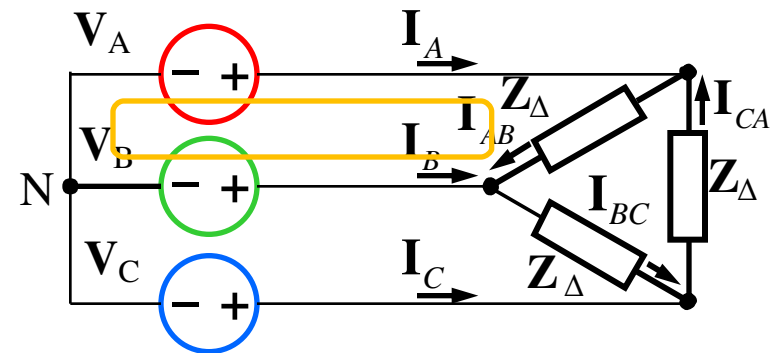

$$\mathbf{Z}_\Delta \mathbf{I}_{AB} = \mathbf{V}_A - \mathbf{V}_B$$

$$\rightarrow \mathbf{I}_{AB} = \frac{\mathbf{V}_A - \mathbf{V}_B}{\mathbf{Z}_\Delta} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_\Delta}$$

Line currents:

- Same magnitude
- Same frequency
- Displaced from each other by 120°

$$\mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{\mathbf{Z}_\Delta} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_\Delta} \times 1 \angle -120^\circ = \mathbf{I}_{AB} \times 1 \angle -120^\circ$$

$$\mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{\mathbf{Z}_\Delta} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_\Delta} \times 1 \angle 120^\circ = \mathbf{I}_{AB} \times 1 \angle 120^\circ$$

Three-phase Circuit Analysis (7), Y- Δ

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{Z_{\Delta}} = \mathbf{I}_{AB} \times 1 / 0^{\circ}$$

$$\mathbf{I}_{BC} = \mathbf{I}_{AB} \times 1 / -120^{\circ}$$

$$\mathbf{I}_{CA} = \mathbf{I}_{AB} \times 1 / 120^{\circ}$$

$$\text{KCL for a: } \mathbf{I}_A = \mathbf{I}_{AB} - \mathbf{I}_{CA}$$

$$\rightarrow \mathbf{I}_A = \mathbf{I}_{AB} (1 / 0^{\circ} - 1 / 120^{\circ})$$

$$= \mathbf{I}_{AB} (1 + 0,5 - j0,866)$$


$$= \mathbf{I}_{AB} \sqrt{3} / -30^{\circ}$$

$$\mathbf{I}_B = \mathbf{I}_{AB} \sqrt{3} / -150^{\circ}$$


$$\mathbf{I}_C = \mathbf{I}_{AB} \sqrt{3} / 90^{\circ}$$

Phase currents:

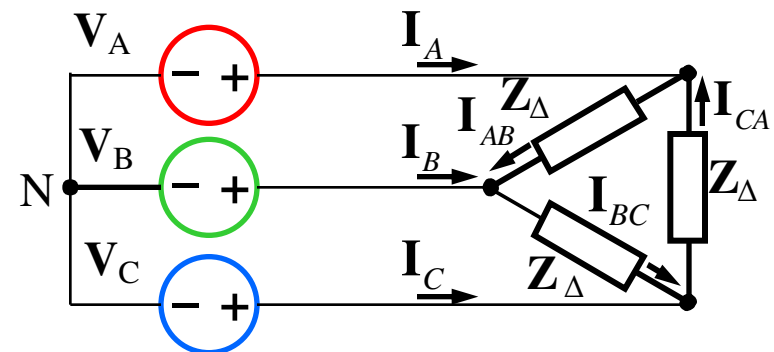- Same magnitude
- Same frequency
- Displaced from each other by 120°


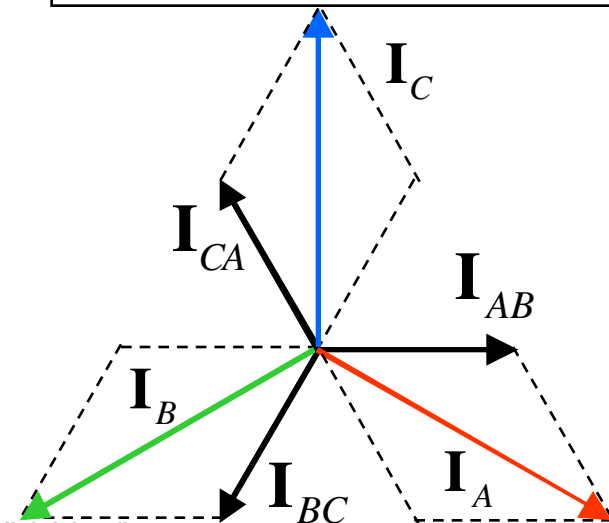
$$\mathbf{I}_{phase} = \mathbf{I}_{line} \sqrt{3} / -30^{\circ}$$



Ex. 2 Three-phase Circuit Analysis (8), Y- Δ

$Z_{\Delta} = 30 + j40 \Omega$; $V_A = 220/\underline{15^\circ}$ V . Find currents?

Method 1

$$V_{line} = V_{phase} \sqrt{3} / \underline{30^\circ}$$

$$\begin{aligned} V_{AB} &= \sqrt{3} V_A \times \underline{1/30^\circ} \\ &= \sqrt{3} \times 220 / \underline{15^\circ + 30^\circ} = 381 / \underline{45^\circ} \text{ V} \end{aligned}$$

$$I_{AB} = \frac{V_{ab}}{Z_{\Delta}} = \frac{V_{AB}}{Z_{\Delta}} = \frac{381 / \underline{45^\circ}}{30 + j40} = 7.62 / \underline{-8.1^\circ} \text{ A} \quad I_{phase} = I_{line} \sqrt{3} / \underline{-30^\circ}$$


$$I_{BC} = 7.62 / \underline{-8.1^\circ - 120^\circ} = 7.62 / \underline{-128.1^\circ} \text{ A}$$

$$I_{CA} = 7.62 / \underline{-8.1^\circ + 120^\circ} = 7.62 / \underline{111.9^\circ} \text{ A}$$

$$I_A = I_{AB} \sqrt{3} / \underline{-30^\circ} = 7.62 / \underline{-8.1^\circ} \times \sqrt{3} / \underline{-30^\circ} = 13.20 / \underline{-38.1^\circ} \text{ A}$$

$$I_B = I_A / \underline{-120^\circ} = 13.2 / \underline{-38.1^\circ - 120^\circ} = 13.20 / \underline{-158.1^\circ} \text{ A}$$
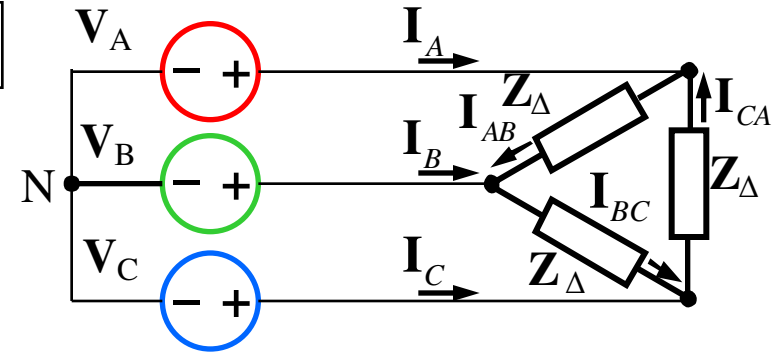
$$I_C = I_A / \underline{120^\circ} = 13.2 / \underline{-38.1^\circ + 120^\circ} = 13.20 / \underline{81.9^\circ} \text{ A}$$



Ex. 2 Three-phase Circuit Analysis (9), Y- Δ


$Z_{\Delta} = 30 + j40 \Omega$; $V_A = 220/\underline{15^\circ}$ V . Find currents?

Method 2

$$Z_A = \frac{Z_{CA} Z_{AB}}{Z_{AB} + Z_{BC} + Z_{CA}}$$

$$= \frac{Z_{\Delta}}{3} = \frac{30 + j40}{3} = 10 + j13.33 \Omega$$
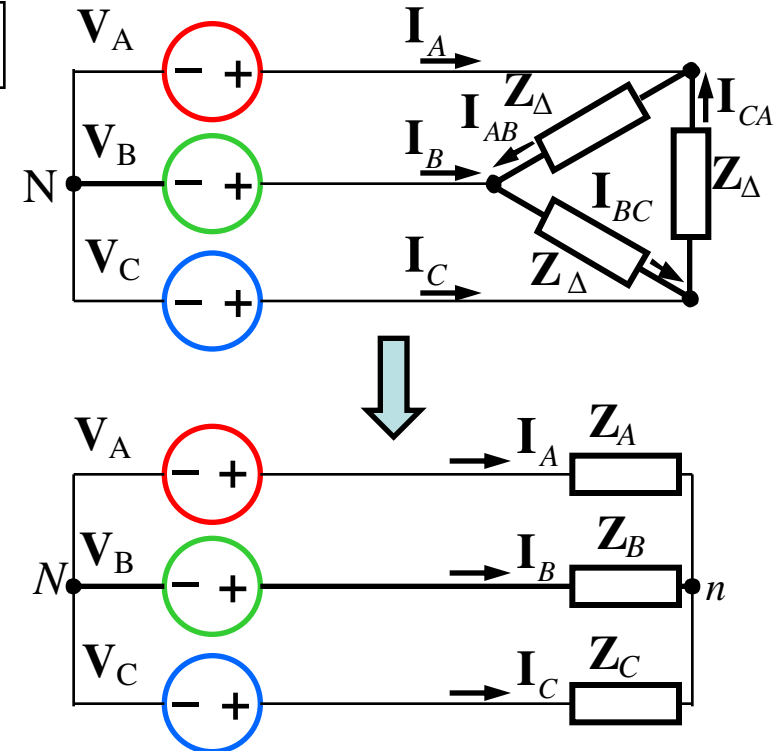
$$I_A = \frac{V_A}{Z_A} = \frac{220/\underline{15^\circ}}{10 + j13.33} = 13.20/\underline{-38.1^\circ} \text{ A}$$



Three-phase Circuit Analysis


- Y-Y, Y- Δ , Δ - Δ , Δ -Y
- 2 kinds of three-phase circuit: balanced & unbalanced
- **Balanced three-phase circuit:**
 - Balanced three-phase source and balanced three-phase load
 - *Balanced three-phase source*: same magnitude, same frequency, displaced from each other by 120°
 - *Balanced three-phase load*: three identical loads
- Unbalanced three-phase circuit:
 - Unbalanced three-phase source and/or unbalanced three-phase load
- To solve a balanced one:
 - Exploit the symmetry of a balanced three-phase circuit, or
 - Treat it like a normal three-source circuit
- To solve an unbalanced one:
 - Treat it like a normal three-source circuit

Three-phase Circuit Analysis (10), Δ - Δ

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_{\Delta}}$$

$$\mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{\mathbf{Z}_{\Delta}} = \mathbf{I}_{AB} \times 1 \angle -120^\circ$$
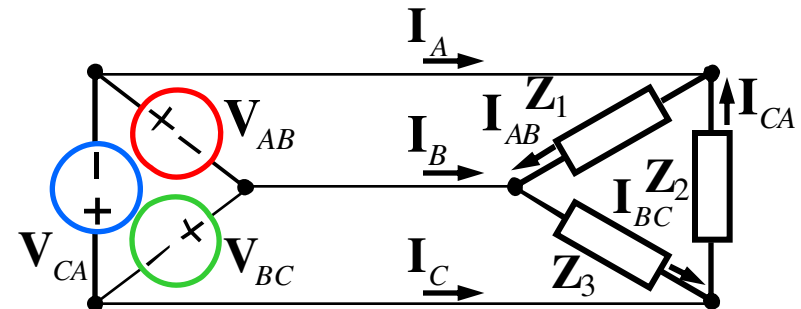
$$\left. \begin{aligned} \mathbf{I}_{CA} &= \frac{\mathbf{V}_{CA}}{\mathbf{Z}_{\Delta}} = \mathbf{I}_{AB} \times 1 \angle 120^\circ \\ \mathbf{I}_A &= \mathbf{I}_{AB} - \mathbf{I}_{CA} \end{aligned} \right\} \rightarrow$$



$$\rightarrow \mathbf{I}_A = \mathbf{I}_{AB} (1 \angle 0^\circ - 1 \angle 120^\circ) = \mathbf{I}_{ab} (1 + 0.50 - j0.87) = \mathbf{I}_{ab} \sqrt{3} \angle -30^\circ$$

$$\mathbf{I}_B = \mathbf{I}_{AB} \sqrt{3} \angle -150^\circ$$

$$\mathbf{I}_C = \mathbf{I}_{AB} \sqrt{3} \angle 90^\circ$$

Three-phase Circuit Analysis

- Y-Y, Y- Δ , Δ - Δ , Δ -Y
- 2 kinds of three-phase circuit: balanced & unbalanced
- **Balanced three-phase circuit:**
 - Balanced three-phase source and balanced three-phase load
 - *Balanced three-phase source*: same magnitude, same frequency, displaced from each other by 120°
 - *Balanced three-phase load*: three identical loads
- Unbalanced three-phase circuit:
 - Unbalanced three-phase source and/or unbalanced three-phase load
- To solve a balanced one:
 - Exploit the symmetry of a balanced three-phase circuit, or
 - Treat it like a normal three-source circuit
- To solve an unbalanced one:
 - Treat it like a normal three-source circuit




Three-phase Circuit Analysis (11), Δ -Y

$$\mathbf{V}_{AB} = V \angle 0^\circ$$

$$\mathbf{V}_{BC} = V \angle -120^\circ$$

$$\mathbf{V}_{CA} = V \angle 120^\circ$$

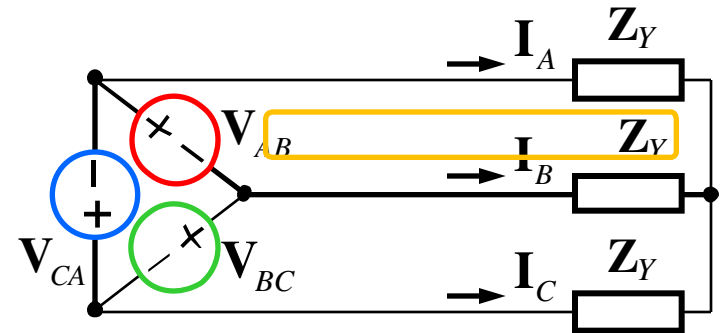

$$\left. \begin{aligned} Z_Y \mathbf{I}_A - Z_Y \mathbf{I}_B &= \mathbf{V}_{AB} \rightarrow \mathbf{I}_A - \mathbf{I}_B = \frac{\mathbf{V}_{AB}}{Z_Y} = \frac{V \angle 0^\circ}{Z_Y} \\ \mathbf{I}_B &= \mathbf{I}_A \times 1 \angle -120^\circ \rightarrow \mathbf{I}_A - \mathbf{I}_B = \mathbf{I}_A (1 - 1 \angle -120^\circ) = \mathbf{I}_A \sqrt{3} \angle 30^\circ \end{aligned} \right\}$$

$$\rightarrow \mathbf{I}_A = \frac{V}{\sqrt{3}Z_Y} \angle -30^\circ$$

$$\begin{aligned} \mathbf{I}_B &= \frac{V}{\sqrt{3}Z_Y} \angle -150^\circ \\ &= \mathbf{I}_A \times 1 \angle -120^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{I}_C &= \frac{V}{\sqrt{3}Z_Y} \angle 90^\circ \\ &= \mathbf{I}_A \times 1 \angle 120^\circ \end{aligned}$$

Ex. 3 Three-phase Circuit Analysis (12), Δ -Y

$Z_Y = 30 + j40 \, \Omega$; $V_{AB} = 220 \, \text{V}$. Find currents?

Method 1

$$\boxed{Z_Y \mathbf{I}_A - Z_Y \mathbf{I}_B = \mathbf{V}_{AB}} \rightarrow \mathbf{I}_A - \mathbf{I}_B = \frac{\mathbf{V}_{AB}}{Z_Y}$$


$$\mathbf{I}_B = \mathbf{I}_A \times 1 \angle -120^\circ$$

$$\rightarrow \mathbf{I}_A - \mathbf{I}_B = \mathbf{I}_A (1 - 1 \angle -120^\circ) = \mathbf{I}_A \sqrt{3} \angle 30^\circ$$

$$\rightarrow \mathbf{I}_A = \frac{\mathbf{V}_{AB}}{\sqrt{3} \angle 30^\circ Z_Y} = \frac{220}{\sqrt{3} \angle 30^\circ (30 + j40)} = 2.54 \angle -83.13^\circ \, \text{A}$$

$$\mathbf{I}_B = \mathbf{I}_A \times 1 \angle -120^\circ = 2.54 \angle -203.13^\circ \, \text{A}$$
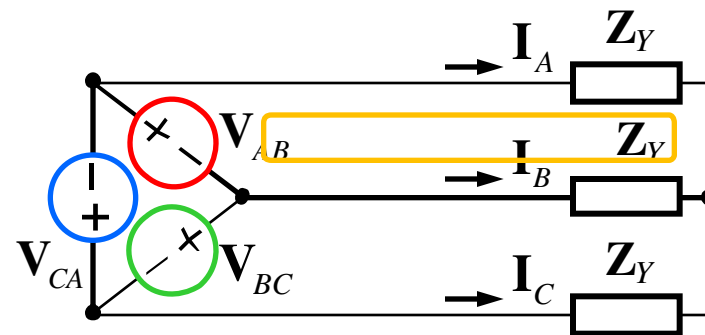
$$\mathbf{I}_C = \mathbf{I}_A \times 1 \angle 120^\circ = 2.54 \angle 36.87^\circ \, \text{A}$$



Ex. 3 Three-phase Circuit Analysis (13), Δ -Y

$Z_Y = 30 + j40 \Omega$; $V_{AB} = 220$ V. Find currents?

Method 2

$$Z_1 = \frac{Z_A Z_B + Z_B Z_C + Z_C Z_A}{Z_C}$$


$$= 3Z_Y = 3(30 + j40) = 90 + j120 \Omega$$

$$I_{AB} = \frac{V_{AB}}{Z_1} = \frac{220}{90 + j120} = 0.88 - j1.17 \text{ A}$$

$$I_{CA} = \frac{V_{CA}}{Z_1} = \frac{220 \angle 120^\circ}{90 + j120} = 0.58 + j1.35 \text{ A}$$

$$I_A + I_{CA} - I_{AB} = 0 \rightarrow I_A = I_{AB} - I_{CA} = (0.88 - j1.17) - (0.58 + j1.35)$$
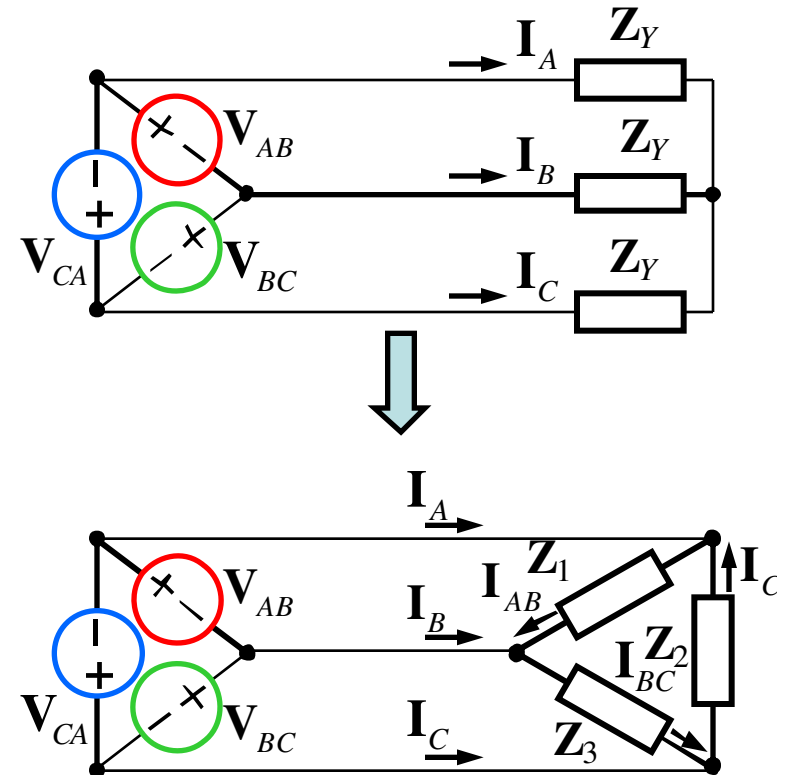
$$= \underline{2.54 \angle -83.13^\circ \text{ A}}$$



Three-phase Circuit Analysis

- Y–Y, Y– Δ , Δ – Δ , Δ –Y
- 2 kinds of three-phase circuit: balanced & unbalanced
- Balanced three-phase circuit:
 - Balanced three-phase source and balanced three-phase load
 - ***Balanced three-phase source***: same magnitude, same frequency, displaced from each other by 120°
 - ***Balanced three-phase load***: three identical loads
- Unbalanced three-phase circuit:
 - Unbalanced three-phase source and/or unbalanced three-phase load
- **To solve a balanced one:**
 - **Exploit the symmetry of a balanced three-phase circuit, or**
 - **Treat it like a normal three-source circuit**
- To solve an unbalanced one:
 - Treat it like a normal three-source circuit

Three-phase Circuit Analysis

- Y-Y, Y- Δ , Δ - Δ , Δ -Y
- 2 kinds of three-phase circuit: balanced & unbalanced
- Balanced three-phase circuit:
 - Balanced three-phase source and balanced three-phase load
 - **Balanced three-phase source**: same magnitude, same frequency, displaced from each other by 120°
 - **Balanced three-phase load**: three identical loads
- **Unbalanced three-phase circuit**:
 - Unbalanced three-phase source and/or unbalanced three-phase load
- To solve a balanced one:
 - Exploit the symmetry of a balanced three-phase circuit, or
 - Treat it like a normal three-source circuit
- **To solve an unbalanced one**:
 - **Treat it like a normal three-source circuit**



Ex. 4 Three-phase Circuit Analysis (14)

$$\begin{aligned} Z_A &= 20 \, \Omega; Z_B = j10 \, \Omega; Z_C = -j10 \, \Omega; V_A = 220 \, \text{V}; \\ V_B &= 220 \angle -120^\circ \, \text{V}; V_C = 220 \angle 120^\circ \, \text{V}; Z_n = 1 + j2 \, \Omega. \end{aligned}$$


$$\begin{aligned} V_N = 0 \rightarrow V_n &= \frac{V_A / Z_A + V_B / Z_B + V_C / Z_C}{1 / Z_A + 1 / Z_B + 1 / Z_C + 1 / Z_n} \\ &= 57.46 \angle -122^\circ \, \text{V} \end{aligned}$$

$$\rightarrow I_{Aa} = \frac{220 \angle 0^\circ - V_n}{20} = \frac{220 \angle 0^\circ - 57.46 \angle -122^\circ}{20} = \boxed{12.76 \angle 11^\circ \, \text{A}}$$

$$I_{Bb} = \frac{220 \angle -120^\circ - V_n}{j10} = \frac{220 \angle -120^\circ - 57.46 \angle -122^\circ}{j10} = \boxed{16.26 \angle 150.7^\circ \, \text{A}}$$

$$I_{Cc} = \frac{220 \angle 120^\circ - V_n}{-j10} = \frac{220 \angle 120^\circ - 57.46 \angle -122^\circ}{-j10} = \boxed{25.21 \angle -161.6^\circ \, \text{A}}$$
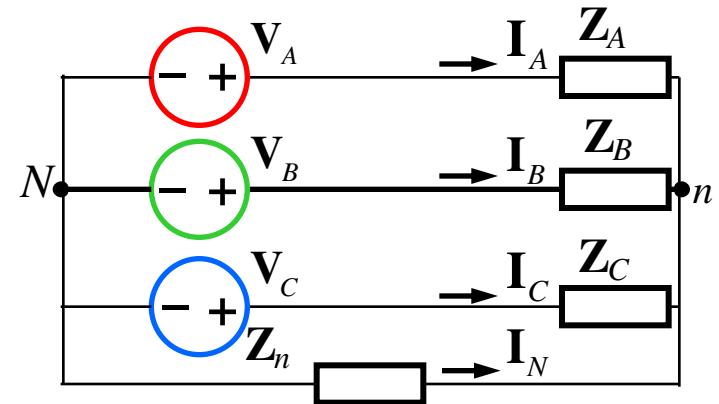
$$I_{nN} = \frac{V_n}{1 + j2} = \frac{57.46 \angle -122^\circ}{1 + j2} = \boxed{25.70 \angle 174.6^\circ \, \text{A}}$$




Ex. 5 Three-phase Circuit Analysis (15)

$$\begin{aligned} Z_A &= 20 \, \Omega; Z_B = j10 \, \Omega; Z_C = -j5 \, \Omega; V_A = 220 \, \text{V}; \\ V_B &= 220 \angle -120^\circ \, \text{V}; V_C = 220 \angle 120^\circ \, \text{V}. \end{aligned}$$

$$\begin{cases} Z_A \mathbf{I}_g + Z_B (\mathbf{I}_g - \mathbf{I}_y) = V_A - V_B \\ Z_B (\mathbf{I}_y - \mathbf{I}_g) + Z_C \mathbf{I}_y = V_B - V_C \end{cases}$$

$$\rightarrow \begin{cases} \mathbf{I}_g = 24.63 - j16.26 \, \text{A} \\ \mathbf{I}_y = -26.95 - j32.53 \, \text{A} \end{cases}$$
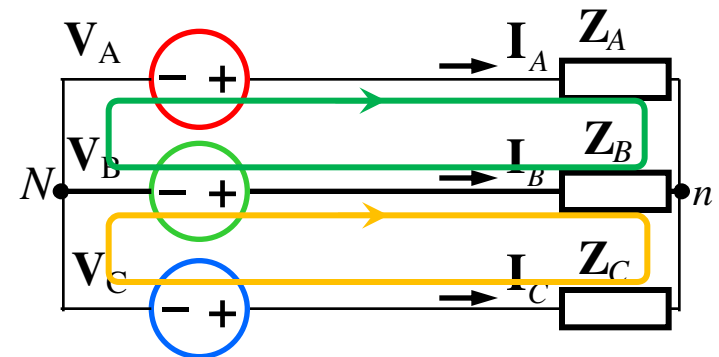
$$\rightarrow \begin{cases} \mathbf{I}_A = \mathbf{I}_g = 24.63 - j16.26 \, \text{A} \\ \mathbf{I}_B = \mathbf{I}_y - \mathbf{I}_g = -51.58 - j16.26 \, \text{A} \\ \mathbf{I}_C = -\mathbf{I}_y = 26.95 + j32.53 \, \text{A} \end{cases}$$




Three-phase Circuit Analysis (16)

Ex. 6

$$\begin{aligned} V_A &= 220/\underline{0^\circ} \text{ V}; V_B = 220/\underline{-120^\circ} \text{ V}; V_C = 220/\underline{120^\circ} \text{ V} \\ Z_L &= 5\Omega; Z_1 = 10\Omega; Z_2 = j20\Omega; Z_3 = -j30\Omega. \end{aligned}$$

$$\begin{cases} (2Z_L + Z_1)I_{red} - Z_1 I_{green} - Z_L I_{blue} = V_A - V_B \\ -Z_1 I_{red} + (Z_1 + Z_2 + Z_3)I_{green} - Z_3 I_{blue} = 0 \\ -Z_L I_{red} - Z_3 I_{green} + (2Z_L + Z_3)I_{blue} = V_B - V_C \end{cases}$$

Method 1

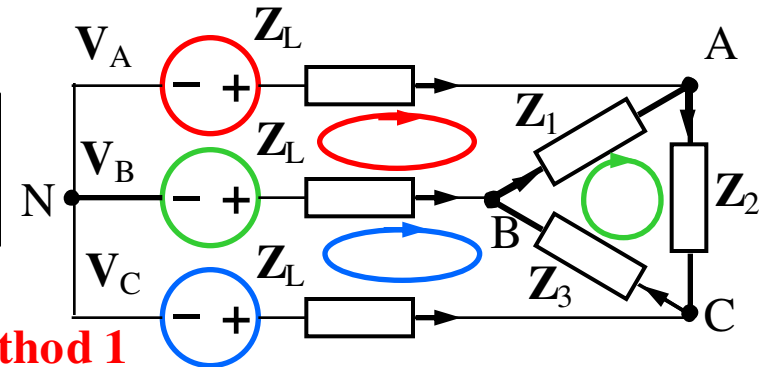


$$\rightarrow \begin{cases} I_{red} = 13.57 + j0.48 \text{ A} \\ I_{green} = -6.89 - j12.59 \text{ A} \\ I_{blue} = 2.06 - j11.02 \text{ A} \end{cases} \rightarrow \begin{cases} I_A = I_r = 13.36 + j0.15 \text{ A} \\ I_B = I_b - I_r = -11.39 - j11.21 \text{ A} \\ I_C = -I_b = -1.98 + j11.06 \text{ A} \\ I_{ab} = I_g - I_r = -20.38 - j12.94 \text{ A} \\ I_{bc} = I_g = -7.02 - j12.79 \text{ A} \\ I_{ca} = I_g - I_b = -8.99 - j1.74 \text{ A} \end{cases}$$



Three-phase Circuit Analysis (17)

Ex. 6

$$\begin{aligned} V_A &= 220/\underline{0^\circ} \text{ V}; V_B = 220/\underline{-120^\circ} \text{ V}; V_C = 220/\underline{120^\circ} \text{ V} \\ Z_L &= 5\Omega; Z_1 = 10\Omega; Z_2 = j20\Omega; Z_3 = -j30\Omega. \end{aligned}$$

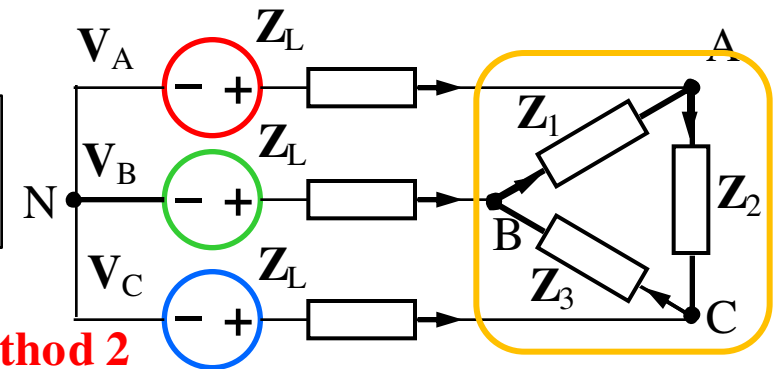


Method 2

$$Z_A = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3} = \frac{10(j20)}{10 + j20 - j30} = -10 + j10 \Omega$$

$$Z_B = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3} = \frac{10(-j30)}{10 + j20 - j30} = 15 - j15 \Omega$$

$$Z_C = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3} = \frac{j20(-j30)}{10 + j20 - j30} = 30 + j30 \Omega$$
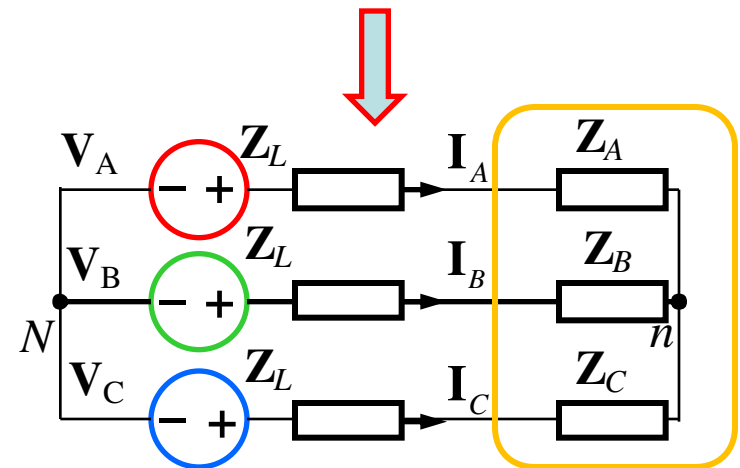
$$V_N = 0 \rightarrow V_n = \frac{\frac{V_A}{Z_L + Z_A} + \frac{V_B}{Z_L + Z_B} + \frac{V_C}{Z_L + Z_C}}{\frac{1}{Z_L + Z_A} + \frac{1}{Z_L + Z_B} + \frac{1}{Z_L + Z_C}} = 288.3 - j132.9 \text{ V}$$



Three-phase Circuit Analysis (18)

Ex. 6

$$\begin{aligned} V_A &= 220/\underline{0^\circ} \text{ V}; V_B = 220/\underline{-120^\circ} \text{ V}; V_C = 220/\underline{120^\circ} \text{ V} \\ Z_L &= 5\Omega; Z_1 = 10\Omega; Z_2 = j20\Omega; Z_3 = -j30\Omega. \end{aligned}$$

$$V_n = 288,3 - j132,9 \text{ V}$$

$$I_A = (V_A - V_n) / (Z_L + Z_A) = 13.36 + j0.15 \text{ A}$$

$$I_B = (V_B - V_n) / (Z_L + Z_B) = -11.39 - j11.21 \text{ A}$$



$$I_C = (V_C - V_n) / (Z_L + Z_C) = -1.98 + j11.06 \text{ A}$$

$$Z_L I_A - Z_1 I_{ab} - Z_L I_B = V_A - V_B$$

$$\rightarrow I_{ab} = \frac{V_B - V_A + Z_L (I_A - I_B)}{Z_1} = -20.38 - j12.94 \text{ A}$$

$$I_{bc} = I_A + I_{ab} = 13.36 + j0.15 - 20.38 - j12.94 = -7.02 - j12.79 \text{ A}$$
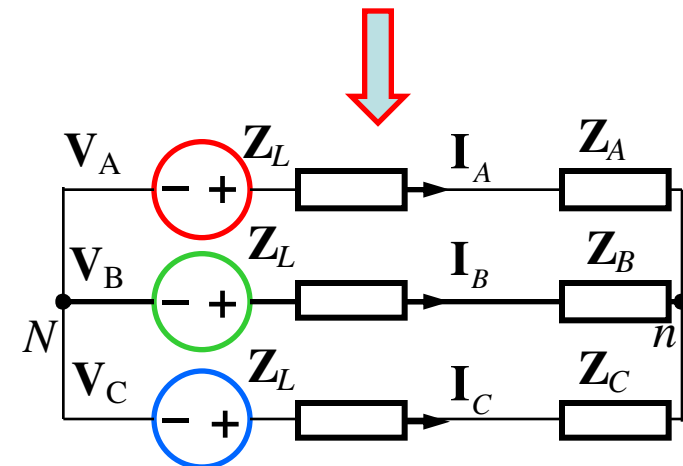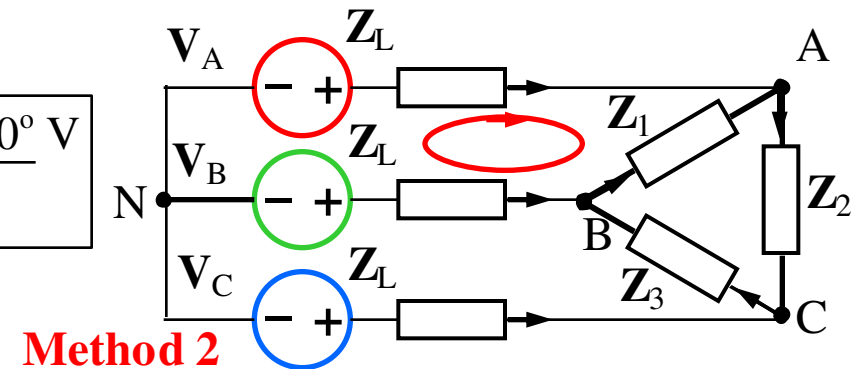
$$I_{ca} = I_C + I_{bc} = -1.98 + j11.06 - 7.02 - j12.79 = 9.00 - j1.73 \text{ A}$$



Three-phase Circuit Analysis (19)


Ex. 7

$$\begin{aligned}
 &V_{AB} = 220 \angle 0^\circ \text{ V}; \quad V_{BC} = 215 \angle -120^\circ \text{ V}; \\
 &Z_1 = 10\Omega; \quad Z_2 = j20\Omega; \quad Z_3 = -j30\Omega.
 \end{aligned}$$

$$\begin{cases}
 (Z_1 + Z_2)I_b - Z_2I_g = -V_{BC} \\
 -Z_2I_b + (Z_2 + Z_3)I_g = V_{AB} + V_{BC}
 \end{cases}$$

$$\rightarrow \begin{cases}
 I_g = 1.14 + j4.42 \text{ A} \\
 I_b = 8.74 + j3.42 \text{ A}
 \end{cases}$$
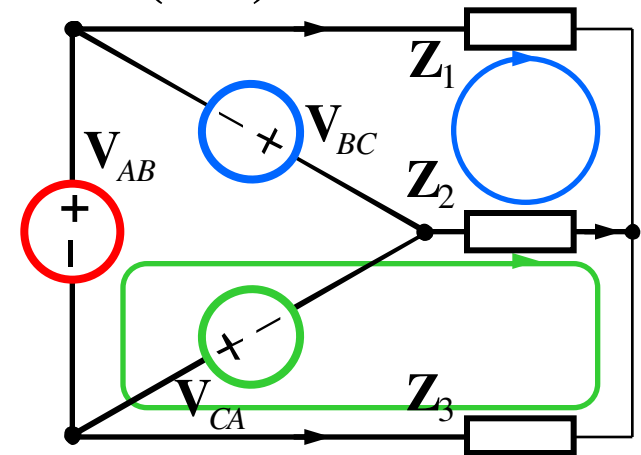
$$\rightarrow \begin{cases}
 I_1 = I_b = 8.74 + j3.42 \text{ A} \\
 I_2 = I_g - I_b = -7.60 + j1.01 \text{ A} \\
 I_3 = -I_g = -1.14 - j4.42 \text{ A}
 \end{cases}$$



Three-phase Circuit Analysis (20)

Ex. 8

$$\begin{aligned} \mathbf{V}_{AB} &= 220 \angle 0^\circ \text{ V}; \mathbf{V}_{BC} = 215 \angle -120^\circ \text{ V}; \\ \mathbf{Z}_1 &= 10\Omega; \mathbf{Z}_2 = j20\Omega; \mathbf{Z}_3 = -j30\Omega. \end{aligned}$$

$$\mathbf{I}_{BA} = \frac{\mathbf{V}_A}{\mathbf{Z}_1} = \frac{220}{10} = 22 \text{ A}$$


$$\mathbf{Z}_2 \mathbf{I}_{AC} = -\mathbf{V}_{AB} - \mathbf{V}_{BC} \rightarrow \mathbf{I}_{AC} = \frac{-\mathbf{V}_{AB} - \mathbf{V}_{BC}}{\mathbf{Z}_2} = \frac{-220 - 215 \angle -120^\circ}{j20} = 9.31 + j5.63 \text{ A}$$

$$\mathbf{I}_{CB} = \frac{\mathbf{V}_B}{\mathbf{Z}_3} = \frac{215 \angle -120^\circ}{-j30} = 6.21 - j3.58 \text{ A}$$

$$\mathbf{I}_A = \mathbf{I}_{AC} - \mathbf{I}_{BA} = 9.31 + j5.63 - 22 = -12.69 + j5.63 \text{ A}$$

$$\mathbf{I}_B = \mathbf{I}_{BA} - \mathbf{I}_{CB} = 22 - (6.21 - j3.58) = 15.79 + j3.58 \text{ A}$$
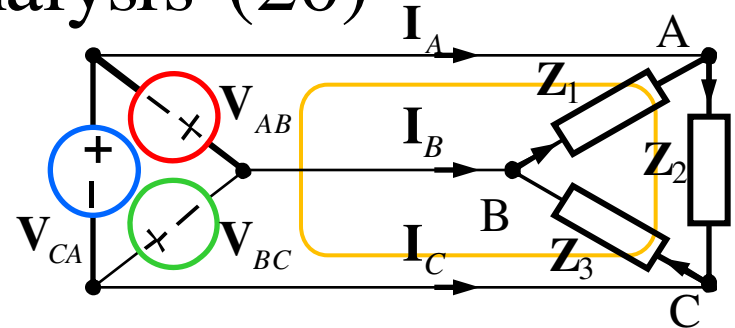
$$\mathbf{I}_C = \mathbf{I}_{CB} - \mathbf{I}_{AC} = 6.21 - j3.58 - (9.14 + j5.63) = -3.10 - j9.21 \text{ A}$$






Three-phase Circuit Analysis (21)

Ex. 9

$$\begin{aligned} V_A &= 220 \angle 0^\circ \text{ V}; V_B = 220 \angle -120^\circ \text{ V}; V_C = 220 \angle 120^\circ \text{ V} \\ Z_L &= 5\Omega; Z_1 = 10\Omega; Z_2 = j20\Omega; Z_3 = -j30\Omega. \end{aligned}$$

$$\begin{cases} (2Z_L + Z_1)I_{red} - Z_1 I_{green} - Z_L I_{blue} = V_A \\ -Z_1 I_{red} + (Z_1 + Z_2 + Z_3)I_{green} - Z_3 I_{blue} = 0 \\ -Z_L I_{red} - Z_3 I_{green} + (2Z_L + Z_3)I_{blue} = V_B \end{cases}$$

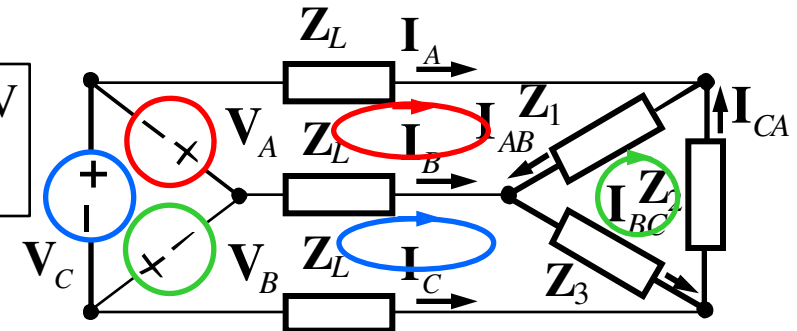

Method 1

$$\rightarrow \begin{cases} I_{red} = 6.92 - j3.68 \text{ A} \\ I_{green} = -7.08 - j4.31 \text{ A} \\ I_{blue} = -2.15 - j6.10 \text{ A} \end{cases} \rightarrow \begin{cases} I_A = I_r = 6.92 - j3.68 \text{ A} \\ I_B = I_b - I_r = -9.07 - j2.42 \text{ A} \\ I_C = -I_b = 2.15 + j6.10 \text{ A} \\ I_{ab} = I_r - I_g = 14.00 + j0.63 \text{ A} \\ I_{bc} = I_b - I_g = 4.93 - j1.80 \text{ A} \\ I_{ca} = -I_g = 7.08 - j4.31 \text{ A} \end{cases}$$

Three-phase Circuit Analysis (22)

Ex. 9

$$\begin{aligned} \mathbf{V}_A &= 220 \angle 0^\circ \text{ V}; \mathbf{V}_B = 220 \angle -120^\circ \text{ V}; \mathbf{V}_C = 220 \angle 120^\circ \text{ V} \\ \mathbf{Z}_L &= 5\Omega; \mathbf{Z}_1 = 10\Omega; \mathbf{Z}_2 = j20\Omega; \mathbf{Z}_3 = -j30\Omega. \end{aligned}$$


$$\mathbf{Z}_A = \frac{\mathbf{Z}_1 \mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3} = \frac{10(j20)}{10 + j20 - j30} = -10 + j10 \Omega$$

$$\mathbf{Z}_B = \frac{\mathbf{Z}_1 \mathbf{Z}_3}{\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3} = \frac{10(-j30)}{10 + j20 - j30} = 15 - j15 \Omega$$

$$\mathbf{Z}_C = \frac{\mathbf{Z}_2 \mathbf{Z}_3}{\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3} = \frac{j20(-j30)}{10 + j20 - j30} = 30 + j30 \Omega$$

$$\begin{cases} (2\mathbf{Z}_L + \mathbf{Z}_A + \mathbf{Z}_B)\mathbf{I}_r - (\mathbf{Z}_L + \mathbf{Z}_B)\mathbf{I}_g = \mathbf{V}_A \\ -(\mathbf{Z}_L + \mathbf{Z}_B)\mathbf{I}_r + (2\mathbf{Z}_L + \mathbf{Z}_B + \mathbf{Z}_C)\mathbf{I}_g = \mathbf{V}_B \end{cases}$$
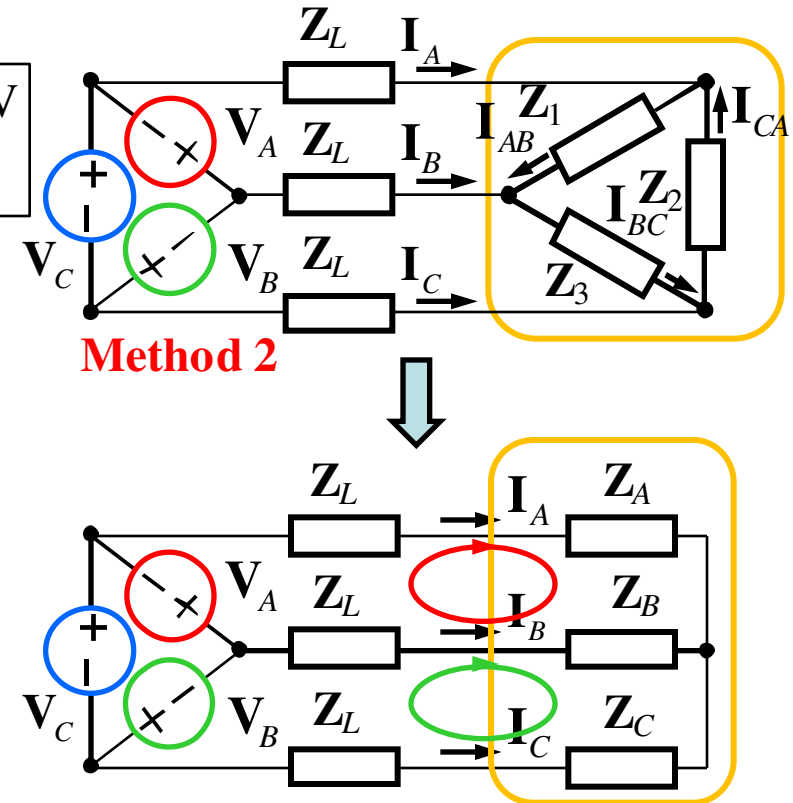
$$\rightarrow \begin{cases} \mathbf{I}_r = 6.92 - j3.68 \text{ A} \\ \mathbf{I}_g = -2.15 - j6.10 \text{ A} \end{cases}$$



Three-phase Circuits

1. Introduction
2. Three-phase Source
3. Three-phase Load
4. Three-phase Circuit Analysis
- 5. Power in Three-phase Circuits**
 - a) Balanced Three-phase Circuits**
 - b) Unbalanced Three-phase Circuits**

Balanced Three-phase Circuits (1)

$$\mathbf{Z}_Y = \mathbf{Z} / \underline{\phi}$$

$$v_{AN} = V\sqrt{2} \sin \omega t$$



$$i_A = I\sqrt{2} \sin(\omega t - \phi)$$

$$v_{BN} = V\sqrt{2} \sin(\omega t - 120^\circ)$$

$$i_B = I\sqrt{2} \sin(\omega t - \phi - 120^\circ)$$

$$v_{CN} = V\sqrt{2} \sin(\omega t + 120^\circ)$$
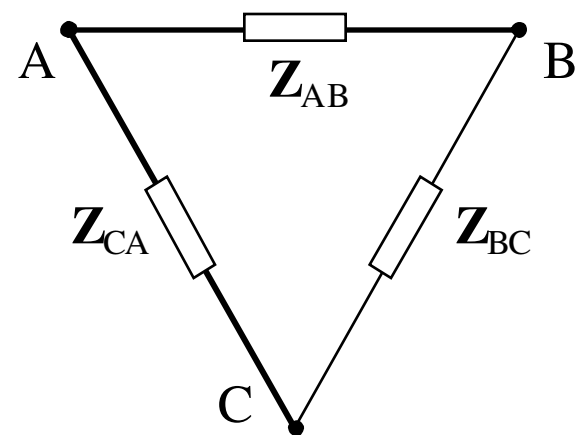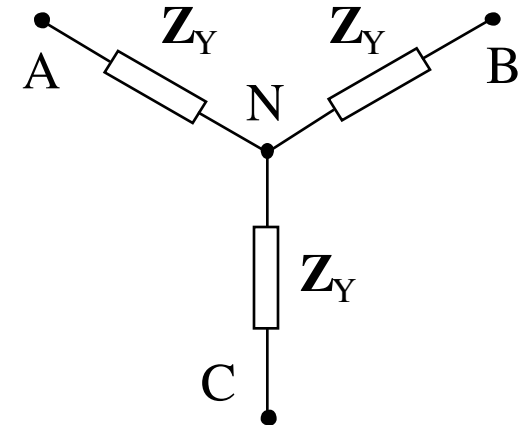
$$i_C = I\sqrt{2} \sin(\omega t - \phi + 120^\circ)$$



$$\left\{ \begin{aligned} p_{total} &= p_a + p_b + p_c = v_{AN}i_A + v_{BN}i_B + v_{CN}i_C \\ &= 2VI [\sin \omega t \sin(\omega t - \phi) + \sin(\omega t - 120^\circ) \sin(\omega t - \phi - 120^\circ) + \\ &\quad + \sin(\omega t + 120^\circ) \sin(\omega t - \phi + 120^\circ)] \\ \sin A \sin B &= \frac{1}{2} [\cos(A - B) - \cos(A + B)] \end{aligned} \right.$$

$$\rightarrow \boxed{p_{total} = 3VI \cos \phi}$$

Balanced Three-phase Circuits (2)

$$p_{total} = 3VI \cos \phi$$

$$P_p = VI \cos \phi$$

$$S_p = VI$$

$$Q_p = VI \sin \phi$$

$$\mathbb{S}_p = P_p + jQ_p = \mathbf{V}\hat{\mathbf{I}}$$



Balanced Three-phase Circuits (3)

Ex. 1

A three-phase balanced Y–Y system has a phase voltage of 220 V. The total real power absorbed by the load is 2400 W, the power factor angle of the load is 20° . Find the line current?

$$P_p = \frac{P_{total}}{3} = \frac{2400}{3} = 800 \text{ W} = V_p I_p \cos 20^\circ = 220 I_p \times 0.94$$

$$\rightarrow I_p = \frac{800}{0.94 \times 220} = 3.87 \text{ A}$$

$$\rightarrow I_L = I_p = \boxed{3.87 \text{ A}}$$

Balanced Three-phase Circuits (4)

Ex. 2

$Z_Y = 30 + j40 \, \Omega$; find phase currents?


$$\begin{cases} I_A = 4.4 \angle -53.13^\circ \text{ A} \\ I_B = 4.4 \angle -173.13^\circ \text{ A} \\ I_C = 4.4 \angle 66.87^\circ \text{ A} \end{cases}$$

$$\cos \varphi = \frac{R}{|Z|} = \frac{30}{\sqrt{30^2 + 40^2}} = 0.6$$

$$p_\Sigma = 3UI \cos \varphi = 3 \times 220 \times 4.4 \times 0.6 = 1742.4 \text{ W}$$

$$\rightarrow P_A = \frac{p_\Sigma}{3} = \frac{1742.4}{3} = \boxed{580.8 \text{ W}}$$
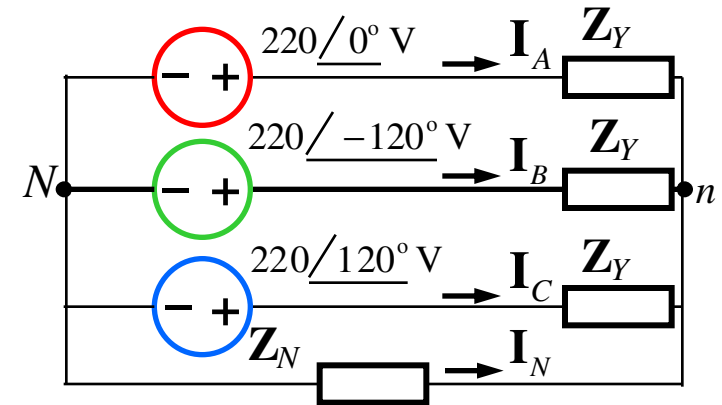
$$P_A = RI_A^2 = 30(4.4)^2 = \boxed{580.8 \text{ W}}$$



Balanced Three-phase Circuits (5)


Ex. 3

$$\begin{aligned} \mathbf{V}_A &= 220/\underline{15^\circ} \text{ V}; \mathbf{V}_B = 220/\underline{-105^\circ} \text{ V}; \\ \mathbf{V}_C &= 220/\underline{135^\circ} \text{ V}; Z_\Delta = 30 + j40 \, \Omega. \end{aligned}$$

$$\begin{cases} \mathbf{I}_{AB} = 7.62/\underline{-8.1^\circ} \text{ A} \\ \mathbf{I}_{BC} = 7.62/\underline{-128.1^\circ} \text{ A} \\ \mathbf{I}_{CA} = 7.62/\underline{111.9^\circ} \text{ A} \end{cases}$$

$$\begin{cases} \mathbf{V}_{AB} = \mathbf{Z}\mathbf{I}_{AB} = 381/\underline{45.0^\circ} \text{ V} \\ \mathbf{V}_{BC} = \mathbf{Z}\mathbf{I}_{BC} = 381/\underline{-75.0^\circ} \text{ V} \\ \mathbf{V}_{CA} = \mathbf{Z}\mathbf{I}_{CA} = 381/\underline{165^\circ} \text{ V} \end{cases}$$

$$\cos \varphi = \frac{R}{|Z|} = \frac{30}{\sqrt{30^2 + 40^2}} = 0,6$$

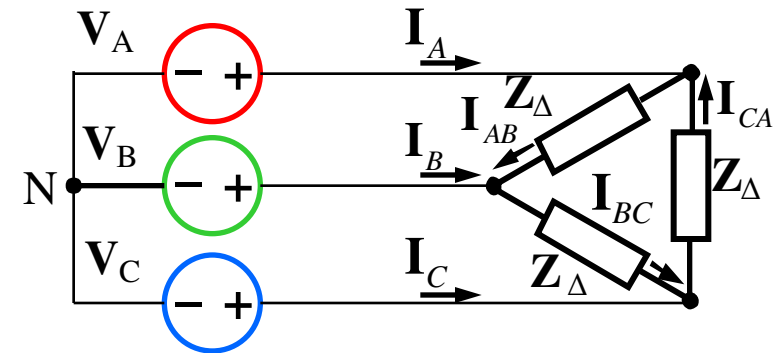

$$\begin{aligned} p_\Sigma &= 3UI \cos \varphi = 3 \times 381 \times 7.62 \times 0.6 \\ &= 5225.8 \text{ W} \end{aligned}$$

$$\rightarrow P_A = \frac{p_\Sigma}{3} = \frac{5225.8}{3} = \boxed{1741.9 \text{ W}}$$

$$P_A = RI_A^2 = 30(7.62)^2 = \boxed{1741.9 \text{ W}}$$

Three-phase Circuits

1. Introduction
2. Three-phase Source
3. Three-phase Load
4. Three-phase Circuit Analysis
- 5. Power in Three-phase Circuits**
 - a) Balanced Three-phase Circuits
 - b) Unbalanced Three-phase Circuits**




Unbalanced Three-phase Circuits (1)

$$\left. \begin{aligned} W_A &= \operatorname{Re}\{\mathbf{V}_{AB} \mathbf{I}_A^*\} \\ \mathbf{I}_A &= \mathbf{I}_{AB} + \mathbf{I}_{AC} \end{aligned} \right\}$$

$$\rightarrow W_A = \operatorname{Re}\{\mathbf{V}_{AB} \mathbf{I}_{AB}^*\} + \operatorname{Re}\{\mathbf{V}_{AB} \mathbf{I}_{AC}^*\}$$
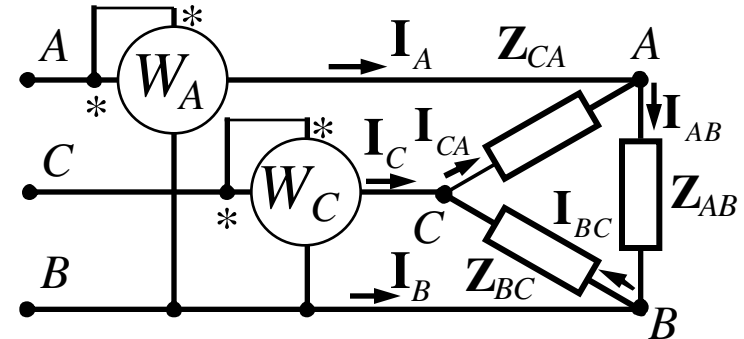
$$\left. \begin{aligned} \operatorname{Re}\{\mathbf{V}_{AB} \mathbf{I}_{AB}^*\} &= P_{AB} \end{aligned} \right\} \rightarrow W_A = P_{AB} + \operatorname{Re}\{\mathbf{V}_{AB} \mathbf{I}_{AC}^*\}$$



$$\left. \begin{aligned} W_C &= \operatorname{Re}\{\mathbf{V}_{CB} \mathbf{I}_C^*\} \\ \mathbf{I}_C &= \mathbf{I}_{CA} + \mathbf{I}_{CB} \end{aligned} \right\} \rightarrow W_C = \operatorname{Re}\{\mathbf{V}_{CB} \mathbf{I}_{CA}^*\} + \operatorname{Re}\{\mathbf{V}_{CB} \mathbf{I}_{CB}^*\}$$

$$\left. \begin{aligned} \operatorname{Re}\{\mathbf{V}_{CB} \mathbf{I}_{CB}^*\} &= P_{CB} \end{aligned} \right\} \rightarrow W_C = \operatorname{Re}\{\mathbf{V}_{CB} \mathbf{I}_{CA}^*\} + P_{CB}$$


$$\rightarrow W_A + W_C = P_{AB} + \operatorname{Re}\{(\mathbf{V}_{AB} - \mathbf{V}_{CB}) \mathbf{I}_{AC}^*\} + P_{CB}$$

$$\left. \begin{aligned} \mathbf{V}_{AB} - \mathbf{V}_{CB} &= \mathbf{V}_{AC} \rightarrow \operatorname{Re}\{(\mathbf{V}_{AB} - \mathbf{V}_{CB}) \mathbf{I}_{AC}^*\} = P_{AC} \end{aligned} \right\} \rightarrow \boxed{W_A + W_C = P_{AB} + P_{AC} + P_{CB}}$$

Unbalanced Three-phase Circuits (2)

Ex.
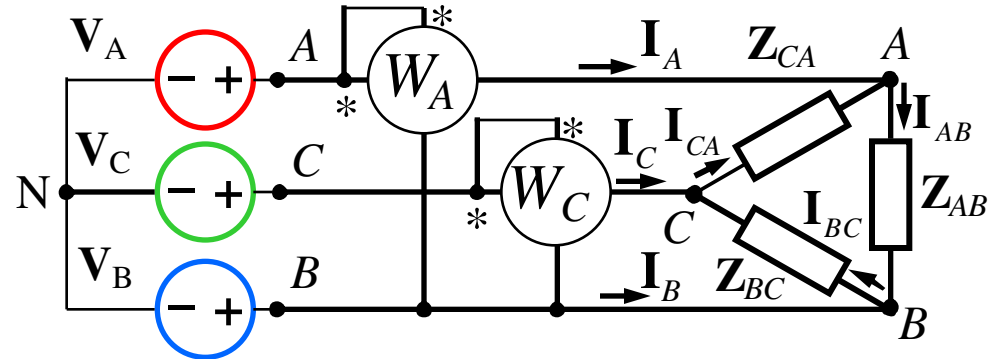
$$\begin{aligned} \mathbf{V}_A &= 220 \angle 0^\circ \text{ V}; \mathbf{V}_C = 220 \angle 120^\circ \text{ V} \\ \mathbf{V}_B &= 220 \angle -120^\circ \text{ V}; \mathbf{Z}_{AB} = 50 \Omega; \\ \mathbf{Z}_{BC} &= j75 \Omega; \mathbf{Z}_{CA} = -j100 \Omega. \end{aligned}$$



$$\mathbf{Z}_{AB} \mathbf{I}_{AB} = \mathbf{V}_A - \mathbf{V}_B \rightarrow \mathbf{I}_{AB} = \frac{\mathbf{V}_A - \mathbf{V}_B}{\mathbf{Z}_{AB}} = \frac{220 - 220 \angle -120^\circ}{50} = 6.60 + j3.81 \text{ A}$$

$$\mathbf{Z}_{BC} \mathbf{I}_{BC} = \mathbf{V}_B - \mathbf{V}_C \rightarrow \mathbf{I}_{BC} = \frac{\mathbf{V}_B - \mathbf{V}_C}{\mathbf{Z}_{BC}} = \frac{220 \angle -120^\circ - 220 \angle 120^\circ}{j75} = -5.08 \text{ A}$$

$$\mathbf{Z}_{CA} \mathbf{I}_{CA} = \mathbf{V}_C - \mathbf{V}_A \rightarrow \mathbf{I}_{CA} = \frac{\mathbf{V}_C - \mathbf{V}_A}{\mathbf{Z}_{CA}} = \frac{220 \angle 120^\circ - 220}{-j100} = -1.91 - j3.30 \text{ A}$$

$$\mathbf{I}_A + \mathbf{I}_{CA} - \mathbf{I}_{AB} = 0 \rightarrow \mathbf{I}_A = \mathbf{I}_{AB} - \mathbf{I}_{CA} = 6.60 + j3.81 - (-1.91 - j3.30) = 8.50 + j7.11 \text{ A}$$

$$\mathbf{I}_C + \mathbf{I}_{BC} - \mathbf{I}_{CA} = 0 \rightarrow \mathbf{I}_C = \mathbf{I}_{CA} - \mathbf{I}_{BC} = -1.91 - j3.30 - (-5.08) = 3.18 - j3.30 \text{ A}$$

Unbalanced Three-phase Circuits (3)

Ex.

$$\begin{aligned} \mathbf{V}_A &= 220 \angle 0^\circ \text{ V}; \mathbf{V}_C = 220 \angle 120^\circ \text{ V} \\ \mathbf{V}_B &= 220 \angle -120^\circ \text{ V}; \mathbf{Z}_{AB} = 50 \Omega; \\ \mathbf{Z}_{BC} &= j75 \Omega; \mathbf{Z}_{CA} = -j100 \Omega. \end{aligned}$$

$$\mathbf{I}_A = 8.50 + j7.11 \text{ A}; \mathbf{I}_C = 3.18 - j3.30 \text{ A}$$

$$\mathbf{I}_{AB} = 6.60 + j3.81 \text{ A}; \mathbf{I}_{BC} = -5.08 \text{ A}; \mathbf{I}_{CA} = -1.91 - j3.30 \text{ A}$$

$$W_A = \text{Re}\{\mathbf{V}_{AB} \mathbf{I}_A^*\} = \text{Re}\{(\mathbf{V}_A - \mathbf{V}_B) \mathbf{I}_A^*\}$$

$$= \text{Re}\{(220 - 220 \angle -120^\circ)(8.50 - j7.11)\} = 4161.5 \text{ W}$$

$$W_C = \text{Re}\{\mathbf{V}_{CB} \mathbf{I}_C^*\} = \text{Re}\{(\mathbf{V}_C - \mathbf{V}_B) \mathbf{I}_C^*\}$$

$$= \text{Re}\{(220 \angle 120^\circ - 220 \angle -120^\circ)(3.18 + j3.30)\} = -1257.5 \text{ W}$$

$$P_{\text{total}} = W_A + W_C = 4161.5 - 1257.5 = \boxed{2904.0 \text{ W}}$$

$$P_{\text{total}} = P_{AB} + P_{BC} + P_{CA} = R_{AB} I_{AB}^2 + 0 + 0 = 50(6.60^2 + 3.81^2) = \boxed{2903.8 \text{ W}}$$

