

Fundamentals of Electric Circuits

DC Circuits

Chapter 7. First Order Circuits

- 7.1. Introduction
- 7.2. The source-free RC/RL circuit
- 7.3. Singularity functions
- 7.4. Step response of an RC/RL circuit
- 7.5. First-order Op Amp circuit
- 7.6. Applications

First Order Circuits

7.1. Introduction

- + In this chapter: → study 2 types of circuits consisting storage elements : R-C, R-L
- + R-C, R-L circuits: → first-order differential equations of KCL, KVL
- + A **first-order circuit** → characterized by a first-order differential equation
- + To excite first order circuits:
 - *Source-free circuit*: Energy is initially stored in the capacitive or inductive element. The energy (*dependent source*) causes current to flow in the circuit and is dissipated in the resistors
 - *Independent source*: DC source (sinusoidal source, exponential source)
- + Applications of first order circuits: delay/relay circuit, photoflash unit, automobile ignition circuit,...

First Order Circuits


7.2. The source-free RC/RL circuit

7.2.1. R-C circuit

+ A source-free R-C circuit:

- Occurs when its DC source is suddenly disconnected
- Energy already stored in the capacitor is released to the resistors

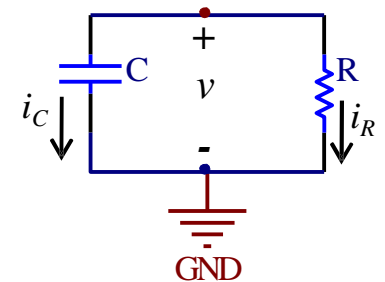+ Considered case: Series combination of a resistor and an initially charged capacitor with $V_0 \rightarrow$ determine the circuit response



Energy stored in the capacitor: $w = \frac{1}{2} CV_0^2$

KCL at the top node of the circuit: $i_C + i_R = 0 \rightarrow C \frac{dv}{dt} + \frac{v}{R} = 0 \rightarrow \frac{dv}{dt} + \frac{v}{RC} = 0$ (First-order differential equation)

$$\rightarrow \frac{dv}{v} = -\frac{1}{RC} dt \rightarrow \ln v = -\frac{t}{RC} + \ln A \rightarrow \ln \frac{v}{A} = -\frac{t}{RC} \rightarrow v(t) = Ae^{-\frac{t}{RC}}$$

$$A = v(0) = V_0 \rightarrow v(t) = V_0 \cdot e^{-\frac{t}{RC}}$$

7

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

First Order Circuits

7.2. The source-free RC/RL circuit

7.2.1. R-C circuit

+ **Circuit response** is: Natural response



→ Due to the initial energy stored and the physical characteristics of the circuit

→ Not due to external voltage or current sources

+ **The natural response** of a circuit → the behavior (in terms of voltages and currents) of the circuit itself, with no external sources of excitation

+ **The time constant** of a RC circuit: → the time required for the response to decay by a factor of 1/e or 36.8% of its initial value
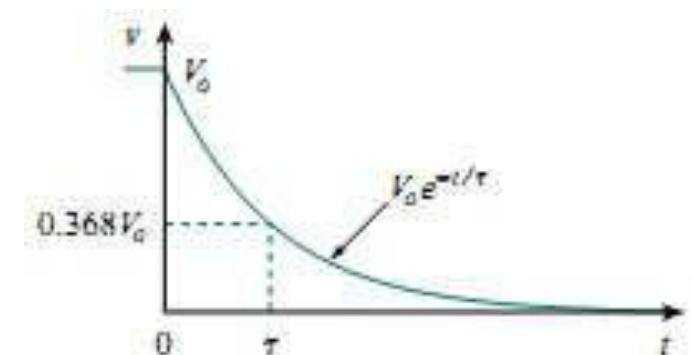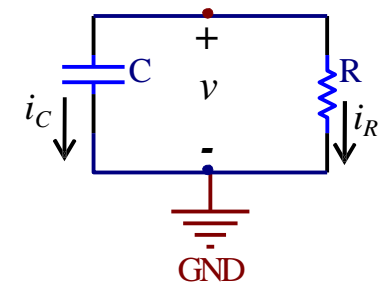
$$\tau = RC \rightarrow v(t) = V_0 \cdot e^{-\frac{t}{\tau}}$$



7

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

First Order Circuits

7.2. The source-free RC/RL circuit



7.2.1. R-C circuit

+ After 5τ :

→ the voltage $v(t)$ is less than 1% of V_0 → the capacitor is fully discharged (or charged)

→ Circuit to reach its *final state (steady state)* when no changes take place with time

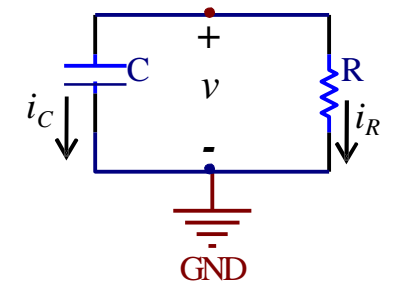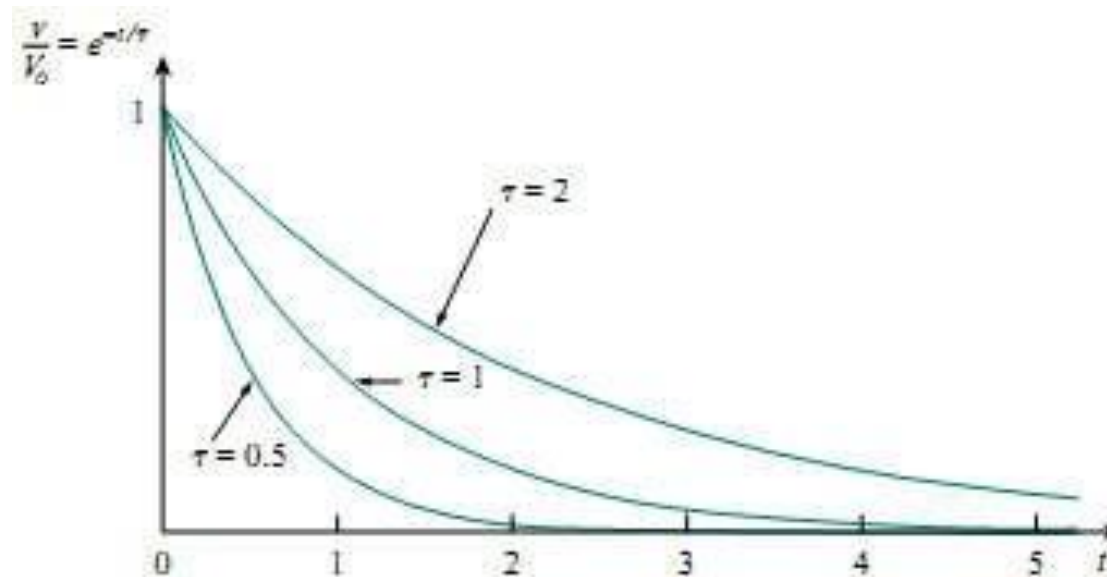+ The greater the time constant
→ the slower the response decay



$$v(t) = V_0 \cdot e^{-\frac{t}{\tau}}$$

t	$v(t) / V_0$
τ	0.36788
2τ	0.13534
3τ	0.04979
4τ	0.01832
5τ	0.00674

7

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

First Order Circuits

7.2. The source-free RC/RL circuit

7.2.1. R-C circuit

+ The **current** $i_R(t)$:

$$i_R(t) = \frac{v(t)}{R} = \boxed{\frac{V_0}{R} e^{-\frac{t}{\tau}}}$$


+ The **power** dissipated in the resistor:

$$p_R(t) = v(t)i_R(t) = \boxed{\frac{V_0^2}{R} e^{-\frac{2t}{\tau}}}$$

+ The **energy** absorbed by the resistor:

$$w_R(t) = \int_0^t p dt = \int_0^t \frac{V_0^2}{R} e^{-\frac{2t}{\tau}} dt = -\frac{\tau V_0^2}{2R} e^{-\frac{2t}{\tau}} \Big|_0^t = \boxed{\frac{1}{2} C V_0^2 \left(1 - e^{-\frac{2t}{\tau}} \right)}$$

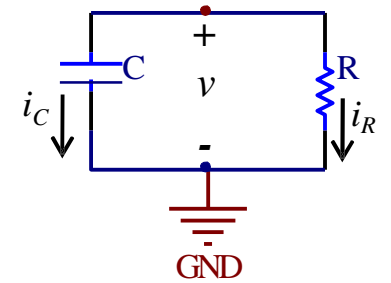+ **Note:** $t \rightarrow \infty \Rightarrow w_R(t) = \frac{1}{2} C V_0^2 = w_C(0)$ *(the energy initially stored in the capacitor)*



First Order Circuits

7.2. The source-free RC/RL circuit

7.2.1. R-C circuit

+ **Example 1**: Find v_C , v_x and i_x for $t > 0$ if $v_C(0) = 15V$



→ equivalent resistance: $R_{eq} = R_1 // (R_2 + R_3) = \frac{5 \cdot (8 + 12)}{5 + 8 + 12} = 4\Omega$

→ time constant: $\tau = R_{eq} C = 4 \cdot 0.1 = 0.4s$

$$\rightarrow v_C(t) = v_0 e^{-\frac{t}{\tau}} = 15e^{-\frac{t}{0.4}} = 15e^{-2.5t} V$$

$$\rightarrow v_x(t) = \frac{R_3}{R_2 + R_3} v_C(t) = \frac{12}{12 + 8} 15e^{-2.5t} = 9e^{-2.5t} V$$
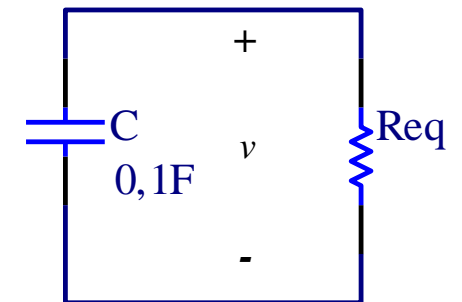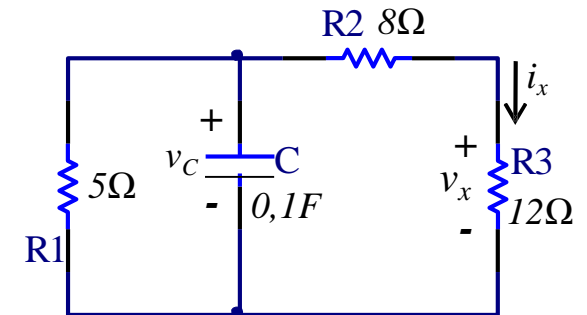
$$\rightarrow i_x(t) = \frac{v_x(t)}{R_3} = \frac{9e^{-2.5t}}{12} = 0.75e^{-2.5t} A$$




First Order Circuits

7.2. The source-free RC/RL circuit

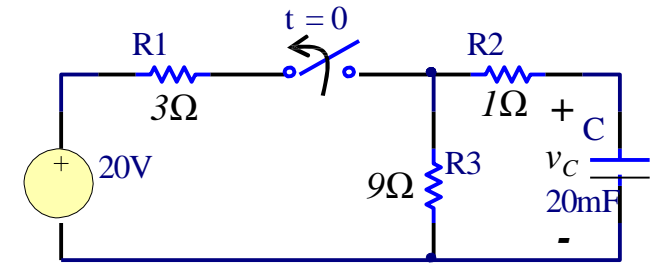7.2.1. R-C circuit

+ **Example 2:** The switch has been closed for a long time, it is opened at $t = 0$. Find $v_C(t)$ for $t \geq 0$. Calculate the initial energy stored in the capacitor



→ For $t < 0$, the switch is closed → C is open circuit to DC source

$$v_c(t) = \frac{v(t)}{R_1 + R_3} R_3 = \frac{20}{3 + 9} 9 = 15V \rightarrow v_c(0) = V_0 = 15V$$

→ For $t > 0$, time constant of the source free R-C circuit: $R_{eq} = R_2 + R_3 = 10\Omega \rightarrow \tau = R_{eq}C = 10 \cdot 20 \cdot 10^{-3} = 0.2s$

→ The voltage across the capacitor for $t \geq 0$: $v_c(t) = V_0 e^{-\frac{t}{\tau}} = 15e^{-5t}V$

→ The initial energy stored in the capacitor: $w_c(0) = \frac{1}{2} C V_0^2 = \frac{1}{2} 20 \cdot 10^{-3} \cdot 15^2 = 2.25J$

7

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

First Order Circuits

7.2. The source-free RC/RL circuit

7.2.2. R-L circuit

+ Consider case: $i_L(0) = I_0 \neq 0$



→ Energy stored in the inductor as: $w_L(0) = \frac{1}{2} LI_0^2$

+ Current through the resistor: $v_L(t) + v_R(t) = 0 \rightarrow L \frac{di}{dt} + Ri = 0 \rightarrow \int_{I_0}^{i(t)} \frac{di}{i} = - \int_0^t \frac{R}{L} dt$

$$\rightarrow \ln \frac{i(t)}{I_0} = -\frac{R}{L} t \rightarrow i(t) = I_0 e^{-\frac{R}{L} t} = I_0 e^{-\frac{t}{\tau}} \quad \tau = \frac{L}{R}$$

+ Energy absorbed by the resistor:
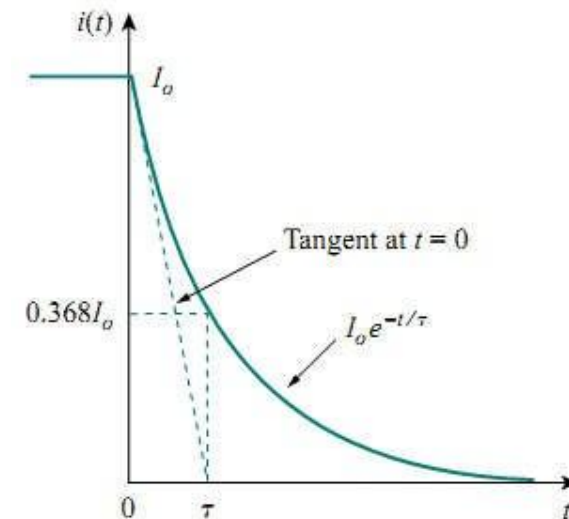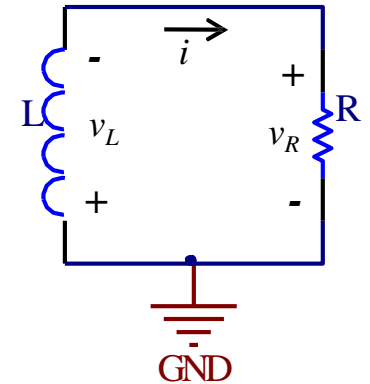
$$w_R(t) = \int_0^t p dt = \int_0^t RI_0^2 e^{-\frac{2t}{\tau}} dt = \frac{1}{2} LI_0^2 \left(1 - e^{-\frac{2t}{\tau}} \right) \quad t \rightarrow \infty : w_R(t) = \frac{1}{2} LI_0^2 = w_L(0)$$



First Order Circuits

7.2. The source-free RC/RL circuit

7.2.2. R-L circuit

+ **Example 3:** Assuming that $i(0) = 10A$, calculate $i(t)$ and $i_x(t)$

Solution 1: Apply the Thevenin's law

→ Connect $V_0 = 1V$ to the gate then apply loop current method to calculate i_0



$$\begin{cases} R_2(i_1 - i_2) + V_0 = 0 \\ (R_1 + R_2)i_2 - R_2i_1 - 3i_1 = 0 \end{cases} \rightarrow \begin{cases} i_1 - i_2 = -\frac{1}{2} \\ -5i_1 + 6i_2 = 0 \end{cases} \rightarrow \begin{cases} i_1 = -3A \\ i_0 = -i_1 = 3A \end{cases}$$

→ Hence: $R_{th} = \frac{V_0}{i_0} = \frac{1}{3}\Omega$ → Obtained an **equivalent RL circuit**

→ Time constant of the RL circuit: $\tau = \frac{L}{R_{th}} = \frac{3}{2} = 1.5s$

→ The current through the inductor is: $i(t) = i_0 e^{-\frac{t}{\tau}} = 10e^{-\frac{2}{3}t} A$

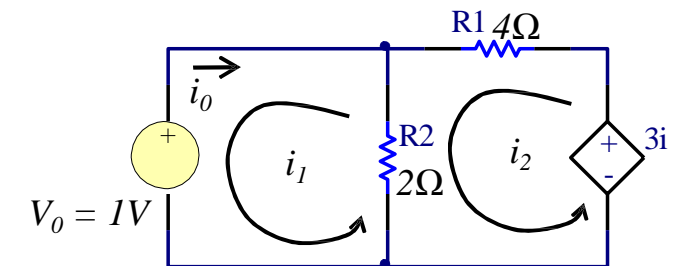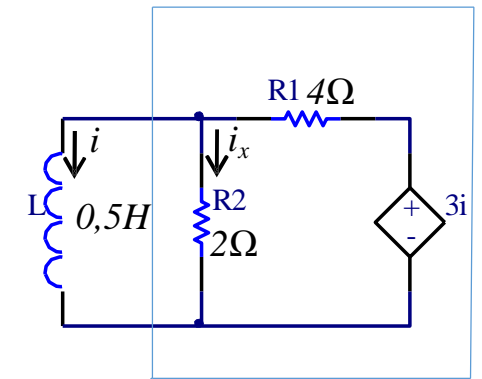→ The current through the resistor R_2 is: $i_x(t) = \frac{v_L(t)}{R_2} = \frac{L}{R_2} \frac{di}{dt} = -\frac{0.5}{2} \cdot 10 \cdot \frac{2}{3} e^{-\frac{2}{3}t} = -1.67e^{-\frac{2}{3}t} A$



First Order Circuits


7.2. The source-free RC/RL circuit

7.2.2. R-L circuit

+ **Example 3:** Assuming that $i(0) = 10\text{A}$, calculate $i(t)$ and $i_x(t)$

Solution 2: Apply directly the loop current method to the given circuit
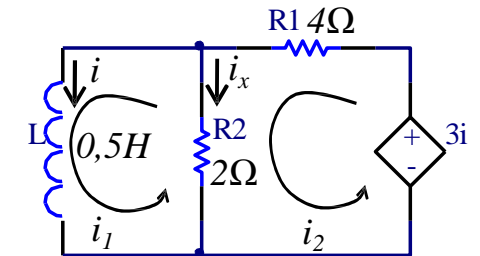
$$\begin{cases} L \frac{di_1}{dt} + R_2(i_1 - i_2) = 0 \\ (R_1 + R_2)i_2 - R_2i_1 - 3i_1 = 0 \end{cases} \rightarrow \begin{cases} \frac{di_1}{dt} + 4i_1 - 4i_2 = 0 \\ i_2 = \frac{5}{6}i_1 \end{cases}$$



The current through the inductor is:

$$\rightarrow \frac{di_1}{dt} + \frac{2}{3}i_1 = 0 \rightarrow i_1(t) = i(t) = i(0)e^{-\frac{2}{3}t} = 10e^{-\frac{2}{3}t} \text{ A}, t > 0$$

The current through the resistor R_2 is:


$$i_x(t) = \frac{v_L(t)}{R_2} = \frac{L}{R_2} \frac{di}{dt} = -\frac{0.5}{2} \cdot 10 \cdot \frac{2}{3} e^{-\frac{2}{3}t} = -1.67e^{-\frac{2}{3}t} \text{ A}$$

First Order Circuits

7.2. The source-free RC/RL circuit

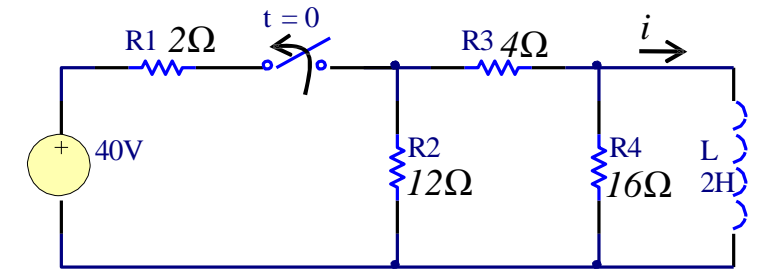7.2.2. R-L circuit

+ **Example 4:** The switch has been closed for a long time. At $t = 0$, the switch is opened. Calculate $i(t)$ for $t > 0$



t < 0: the inductor acts as a short circuit

$$i_{R1} = \frac{E}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} = \frac{40}{2 + \frac{12 \cdot 4}{12 + 4}} = 8A \rightarrow i_L = i_{R1} \frac{R_2}{R_2 + R_3} = 8 \cdot \frac{12}{12 + 4} = 6A \rightarrow i(0) = i_0 = 6A$$

t > 0: we have a R-L circuit

$$R_{eq} = \frac{R_4 (R_2 + R_3)}{R_4 + R_2 + R_3} = \frac{16(12 + 4)}{16 + 12 + 4} = 8\Omega \quad \rightarrow \text{time constant: } \tau = \frac{L}{R_{eq}} = \frac{2}{8} = 0.25s$$

The current through the inductor is: $i(t) = i_0 e^{-\frac{t}{\tau}} = 6e^{-4t} A$

7

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

First Order Circuits

7.2. The source-free RC/RL circuit

7.2.2. R-L circuit

+ **Example 5:** Calculate $i(t)$ for $t > 0$

t < 0: the inductor acts as a short circuit


$$5 = \frac{v}{R_1} + \frac{v}{R_3} = \frac{R_1 + R_3}{R_1 R_3} v \rightarrow v = \frac{R_1 R_3}{R_1 + R_3} 5 \rightarrow i(t) = \frac{v}{R_1} = \frac{R_3}{R_1 + R_3} 5 = 2A \rightarrow i(0) = i_0 = 2A$$

t > 0: we have a R-L circuit

$$R_{eq} = \frac{R_2(R_1 + R_3)}{R_2 + R_1 + R_3} = \frac{5(12 + 8)}{5 + 12 + 8} = 4\Omega$$

→ time constant: $\tau = \frac{L}{R_{eq}} = \frac{2}{4} = 0.5s$

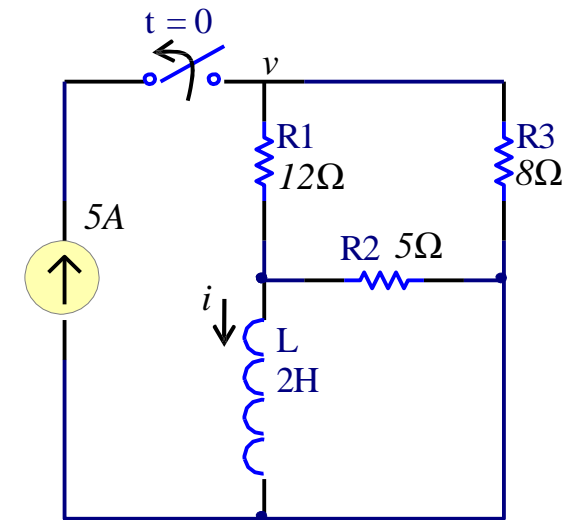Hence, the current through the inductor is: $i(t) = i_0 e^{-\frac{t}{\tau}} = 2e^{-2t} A$



7

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

First Order Circuits


7.2. The source-free RC/RL circuit

7.2.2. R-L circuit

+ **Example 6:** Find i_0 , v_0 and i for all time

$t < 0$: the inductor acts as a short circuit
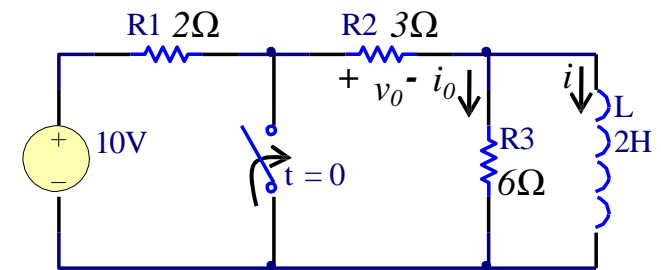
$$i(t) = \frac{E}{R_1 + R_2} = \frac{10}{2 + 3} = 2A, t < 0 \quad i_0(t) = 0A, t < 0 \quad v_0(t) = R_2 i(t) = 3 \cdot 2 = 6V, t < 0$$



$t > 0$: voltage source is disconnected to the right side, and we have a R-L circuit which consists of R_2 , R_3 , and L

$$R_{eq} = \frac{R_2 R_3}{R_2 + R_3} = \frac{3 \cdot 6}{3 + 6} = 2\Omega \quad \rightarrow \text{time constant: } \tau = \frac{L}{R_{eq}} = \frac{2}{2} = 1s \quad \rightarrow \text{current through L: } i(t) = i_0 e^{-\frac{t}{\tau}} = 2e^{-t} A$$

$$\rightarrow \text{voltage across } R_2: \quad v_0(t) = -v_L(t) = -L \frac{di}{dt} = -2 \cdot (-1)e^{-t} = 2e^{-t} V$$

$$\rightarrow \text{current through } R_3: \quad i_0(t) = \frac{v_L(t)}{R_3} = \frac{L}{R_3} \frac{di}{dt} = \frac{2}{6} \cdot (-1)e^{-t} = -\frac{1}{3}e^{-t} A$$

First Order Circuits

7.2. The source-free RC/RL circuit

7.2.2. R-L circuit

+ **Example 6:** Find i_o , v_o and i for all time



For all time:

$$i(t) = \begin{cases} 2A & t < 0 \\ 2e^{-t}A & t \geq 0 \end{cases} \quad i_o(t) = \begin{cases} 0A & t < 0 \\ -0.67e^{-t}A & t > 0 \end{cases}$$

$$v_o(t) = \begin{cases} 6V & t < 0 \\ 4e^{-t}V & t > 0 \end{cases}$$

Note:

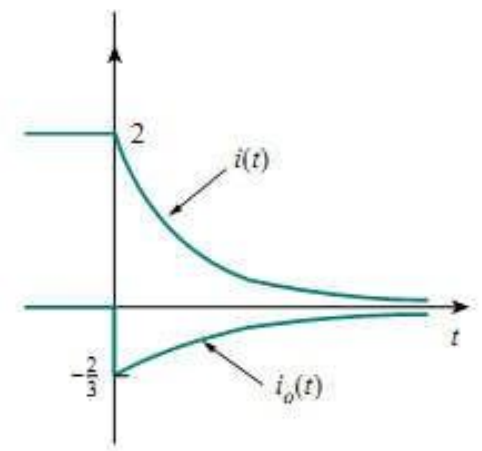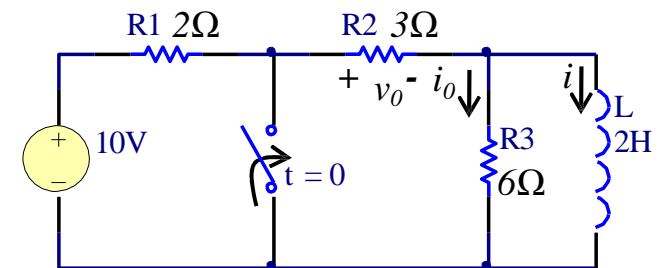- The current through inductor is continuous at $t = 0$
- $i_o(t)$ drops from 0 to $-2/3A$, and $v_o(t)$ drops from 6 to 4 at $t = 0$
- τ is the same regardless of what the output is defined to be



First Order Circuits

7.2. The source-free RC/RL circuit


7.2.2. R-L circuit

+ **Example 7:** Find i_0 , v_0 and i for all time

$t < 0$: the inductor acts as a short circuit

→ the current source and R_1 and R_3 are in parallel
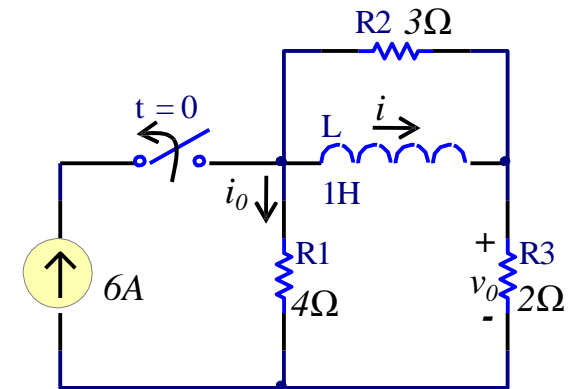
$$6 = \frac{v}{R_1} + \frac{v}{R_3} = \frac{R_1 + R_3}{R_1 R_3} v \rightarrow v = v_0(t) = \frac{R_1 R_3}{R_1 + R_3} 6 = 8V \rightarrow i(t) = \frac{v}{R_3} = 4A \rightarrow i_0(t) = 2A$$



$t > 0$: current source is disconnected, and we have a R-L circuit which consists of R_1 , R_2 , R_3 , and L

$$R_{eq} = \frac{R_2(R_1 + R_3)}{R_2 + R_1 + R_3} = \frac{3 \cdot 6}{3 + 6} = 2\Omega \quad \tau = \frac{L}{R_{eq}} = \frac{1}{2} = 0.5s \quad i(t) = i(0)e^{-\frac{t}{\tau}} = 4e^{-2t} A$$

$$i_2(t) = \frac{v_L(t)}{R_2} = \frac{L}{R_2} \frac{di}{dt} = \frac{1}{3} \cdot 4 \cdot (-2)e^{-2t} = -\frac{8}{3}e^{-2t} A \rightarrow i_0(t) = -(i + i_2) = -\left(4e^{-2t} - \frac{8}{3}e^{-2t}\right) = -\frac{4}{3}e^{-2t} = -1.33e^{-2t} A$$

$$v_0(t) = -R_3 i_0(t) = 2.67e^{-2t} V$$

For all time: → easy to find

First Order Circuits

7.3. Singularity functions

+ Singularity function (*switching function*):



- functions that either are discontinuous or have discontinuous derivatives
- Useful in circuit analysis: Serve as good approximations to the switching signals

+ Widely used singularity functions: *unit step, unit impulse, unit ramp*

+ Unit step function $u(t)$: equals to 0 for negative values of t and 1 for positive values of t

$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \\ \text{undefined}, & t = 0 \end{cases}$$
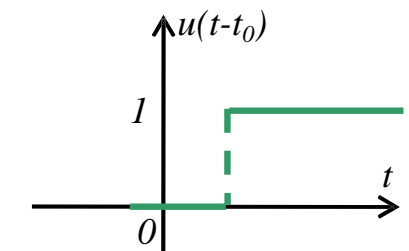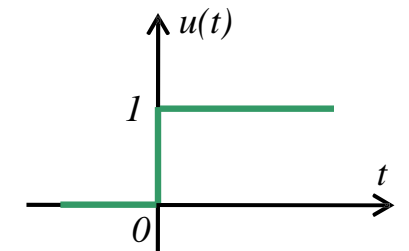
$$u(t - t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \\ \text{undefined}, & t = t_0 \end{cases}$$







First Order Circuits

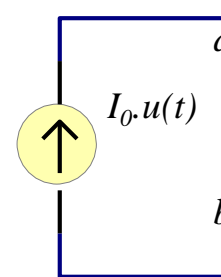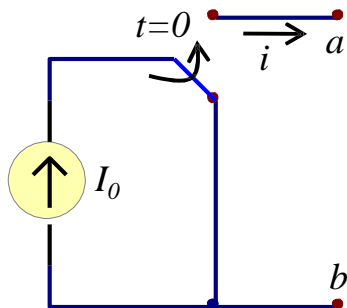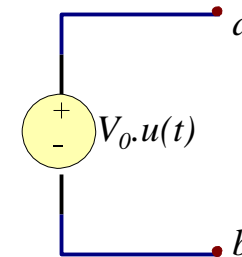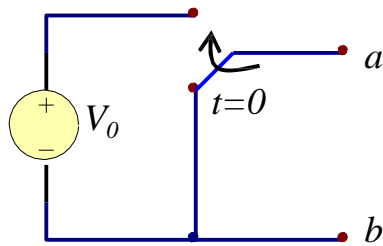7.3. Singularity functions

+ **Step function:** → can be used to represent an abrupt change in voltage or current

$$v(t) = \begin{cases} 0, & t < t_0 \\ V_0, & t > t_0 \\ \text{undefined}, & t = t_0 \end{cases} \rightarrow v(t) = V_0 \cdot u(t - t_0)$$




First Order Circuits

7.3. Singularity functions

+ **Unit impulse function $\delta(t)$** (*delta function*): derivative of the unit step function $u(t)$

$$\delta(t) = \begin{cases} 0, & t < 0 \\ 0, & t > 0 \\ \text{undefined}, & t = 0 \end{cases}$$
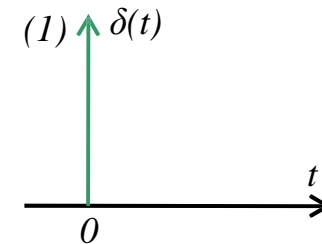
$$\int_{-0}^{+0} \delta(t) dt = 1 \rightarrow \int_{-\infty}^{+\infty} \delta(t) dt = 1$$




→ **Unit impulse function $\delta(t)$** is zero everywhere except at $t = 0$, where it is undefined

+ **Impulsive currents and voltages**: occur in electric circuits as a result of switching operations of impulsive sources

→ **Not** physically realizable, but useful mathematical tool

$$\int_a^b f(t) \delta(t) dt = f(0)$$
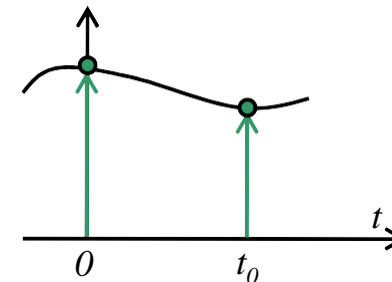
$$\int_a^b f(t) \delta(t - t_0) dt = f(t_0)$$




First Order Circuits

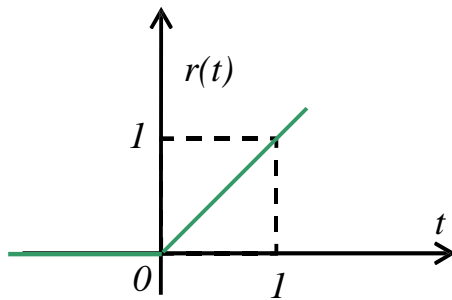
7.3. Singularity functions

+ **Unit ramp function:** zero for negative values of t and has a unit slope for positive values of t


$$r(t) = \int_{-\infty}^t u(t) dt = t \cdot u(t)$$


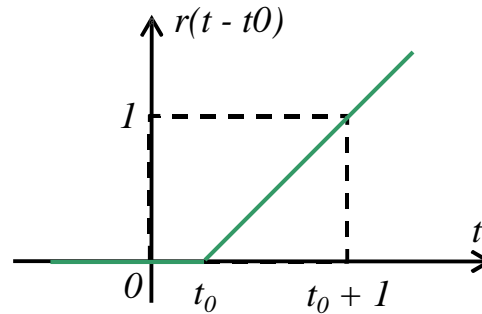
$$r(t) = \begin{cases} 0, & t \leq 0 \\ t, & t \geq 0 \end{cases}$$


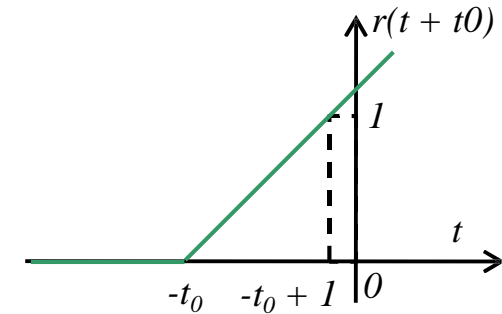
$$r(t - t_0) = \begin{cases} 0, & t \leq t_0 \\ t - t_0, & t \geq t_0 \end{cases}$$



$$r(t + t_0) = \begin{cases} 0, & t \leq -t_0 \\ t - t_0, & t \geq -t_0 \end{cases}$$

First Order Circuits

7.3. Singularity functions

+ **Example 8:** Express the given voltage pulse (*gate function*) in terms of the unit step. Calculate its derivative and sketch it




The given function may be regarded as a step function which:

- Switch on at one value of t ($t = 2s$)
- Switch off at another value of t ($t = 5s$)

$$v(t) = v_1(t) + v_2(t) = 10u(t-2) - 10u(t-5)V$$

Then, the derivative of the gate function:
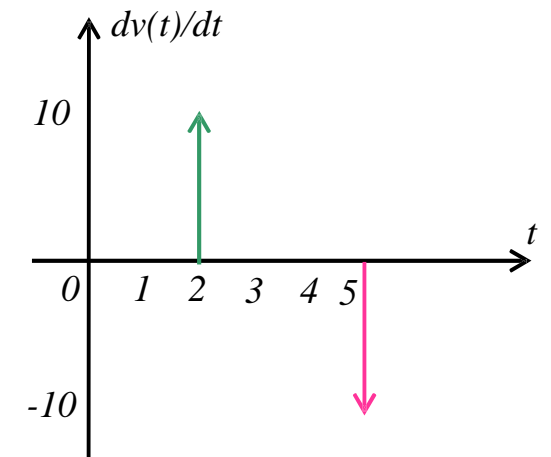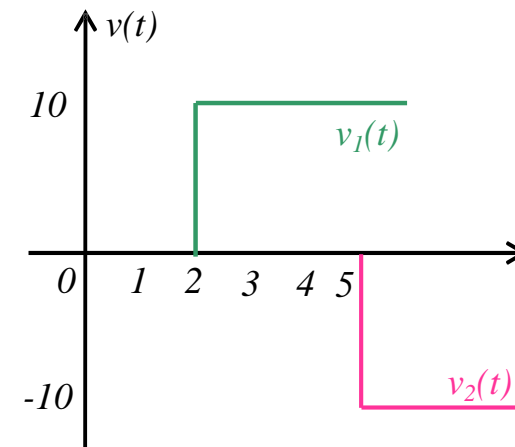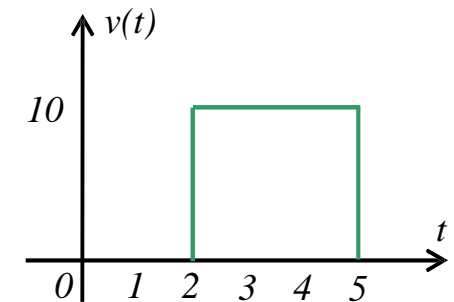
$$\frac{d}{dt}v(t) = 10\delta(t-2) - 10\delta(t-5)$$



First Order Circuits

7.3. Singularity functions

+ **Example 9:** Express the current pulse in terms of the unit step. Find its integral and sketch it

The given current pulse may be regarded as:




$$i(t) = i_1(t) + i_2(t) + i_3(t) = 10u(t) - 20u(t-2) + 10u(t-4)A$$

The integral of the current pulse:

$$\int_{-\infty}^t i(t)dt = \int_{-\infty}^t 10[u(t) - 2u(t-2) + u(t-4)]dt$$

$$\rightarrow \int_{-\infty}^t i(t)dt = 10[t.u(t) - 2t.u(t-2) + t.u(t-4)]$$
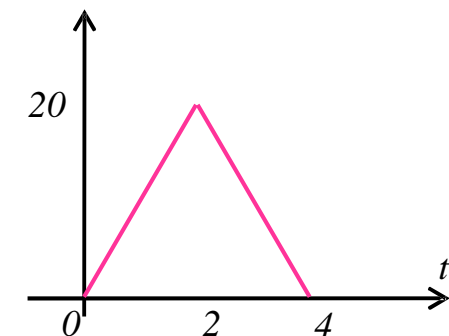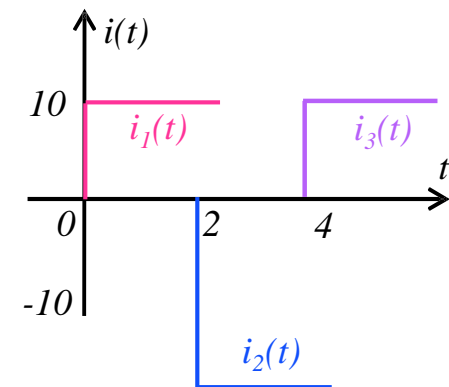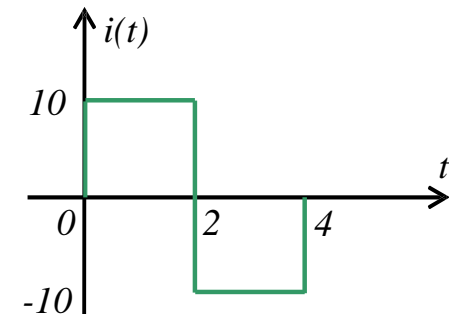
$$\rightarrow \int_{-\infty}^t i(t)dt = 10[r(t) - 2r(t-2) + r(t-4)]$$




First Order Circuits

7.3. Singularity functions




+ **Example 10:** Express the given *saw tooth* in terms of singularity functions

Solution 1: The saw tooth is expressed as a combination of unit functions

$$v(t) = 5t.u(t) - 5t.u(t-2) = 5t[u(t) - u(t-2)]$$

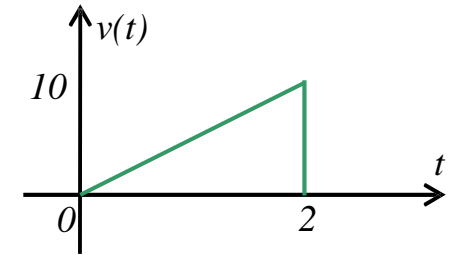

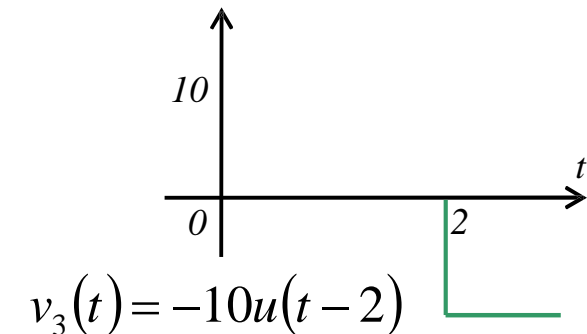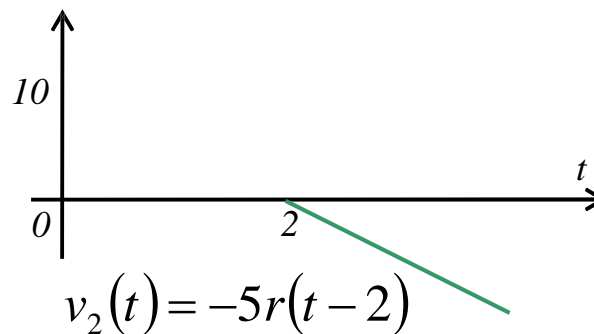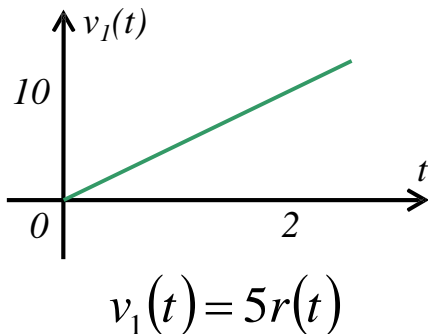Solution 2: The saw tooth is expressed as a combination of 2 functions: $u(t)$ & $r(t)$



$$v(t) = 5t.u(t) - 5t.u(t-2) = 5t.u(t) - 5(t-2+2).u(t-2) = 5t.u(t) - 5(t-2).u(t-2) - 5.2.u(t-2)$$

$$\rightarrow v(t) = 5r(t) - 5r(t-2) - 10.u(t-2)$$

First Order Circuits

7.3. Singularity functions

+ **Example 11:** Express $g(t)$ in terms of step and ramp functions

$$g(t) = \begin{cases} 3 & t < 0 \\ -2 & 0 < t < 1 \\ 2t - 4 & t > 1 \end{cases}$$

The signal $g(t)$ can be expressed as the sum of three function specified within the three intervals: $g_1(t)$, $g_2(t)$, $g_3(t)$

with $t < 0$: $g_1(t) = 3u(-t)$

with $0 < t < 1$: $g_2(t) = -2[u(t) - u(t-1)]$

with $t > 1$: $g_3(t) = (2t - 4)[u(t-1)]$

So:

$$g(t) = 3u(-t) - 2[u(t) - u(t-1)] + (2t - 4)[u(t-1)] = 3u(-t) - 2u(t) + (2t - 2)u(t-1)$$

$$g(t) = 3u(-t) - 2u(t) + 2r(t-1) = 3[1 - u(t)] - 2u(t) + 2r(t-1)$$

$$\rightarrow g(t) = 3 - 5u(t) + 2r(t-1)$$

First Order Circuits

7.4. Step response of a RC/RL circuit

7.4.1. Step response of a RC circuit

+ When the **DC source** of a RC circuit is **suddenly applied**:

→ **voltage or current source** can be modeled as a **step function**

→ the response of circuit is known as a **step response**

+ **Step response** of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source

+ **Example**: Consider the **RC** circuit, assume an initial voltage V_0 on the capacitor

$$V(-0) = V(+0) = V_0$$

$V(-0)$: Voltage across C just before switching


$V(+0)$: Voltage across C immediately after switching

Apply KVL to the loop:

$$Ri(t) + v(t) = V_s u(t) \rightarrow RC \frac{dv}{dt} + v(t) = V_s u(t)$$

With $t > 0$, we obtain:
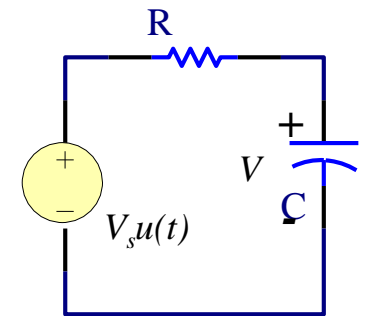
$$\frac{dv}{dt} + \frac{1}{RC} v(t) = \frac{1}{RC} V_s$$



First Order Circuits

7.4. Step response of a RC/RL circuit

7.4.1. Step response of a RC circuit

$$\frac{dv}{dt} + \frac{1}{RC}(v - V_s) = 0 \rightarrow \frac{dv}{v - V_s} = -\frac{dt}{RC} \rightarrow \ln(v - V_s) \Big|_{V_0}^{v(t)} = -\frac{t}{RC} \Big|_0^t$$



$$\rightarrow \ln[v(t) - V_s] - \ln(V_0 - V_s) = -\frac{t}{RC}$$

$$\rightarrow \ln \frac{v - V_s}{V_0 - V_s} = -\frac{t}{RC} \rightarrow \frac{v - V_s}{V_0 - V_s} = e^{-\frac{t}{\tau}} \rightarrow v(t) = \begin{cases} V_0 & t < 0 \\ V_s + (V_0 - V_s)e^{-\frac{t}{\tau}} & t > 0 \end{cases}$$

+ If C is uncharged initially: $V_0 = 0$

$$v(t) = V_s \left(1 - e^{-\frac{t}{\tau}} \right) u(t)$$
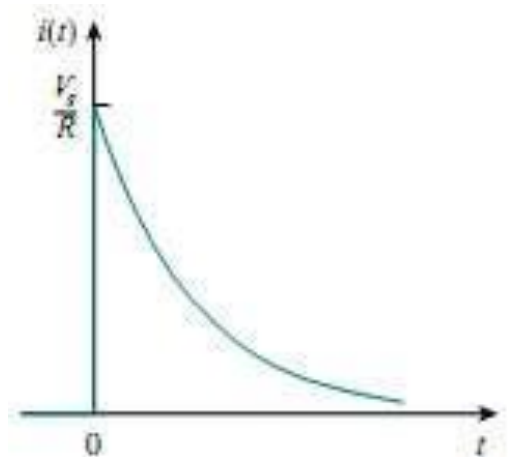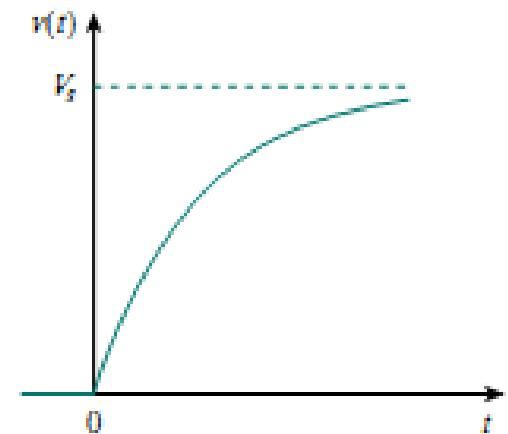
$$i(t) = C \frac{dv}{dt} = \frac{V_s}{R} e^{-\frac{t}{\tau}} u(t)$$



First Order Circuits

7.4. Step response of a RC/RL circuit

7.4.1. Step response of a RC circuit

+ In general, for $t > 0$:

$$v(t) = V_s + (V_0 - V_s)e^{-\frac{t}{\tau}} = v_n + v_f \quad \begin{cases} v_n = (V_0 - V_s)e^{-\frac{t}{\tau}} \\ v_f = V_s \end{cases}$$

- v_n : Natural response (*not remained by excitation source*) of circuit, will decay to zero after five time constants
- v_f : Forced response (*remained by excitation source*) of circuit, will represents what the circuit is forced to do by the input excitation, and remains a long time

+ Thus, to find the step response of an RC circuit requires 3 things:

$$v(t) = v(0)e^{-\frac{t}{\tau}} + v(\infty)\left(1 - e^{-\frac{t}{\tau}}\right)$$

$v(0)$ is the initial voltage at $t = +0$.

$v(\infty)$ is the final or steady state value


τ is the time constant of the circuit

First Order Circuits

7.4. Step response of a RC/RL circuit

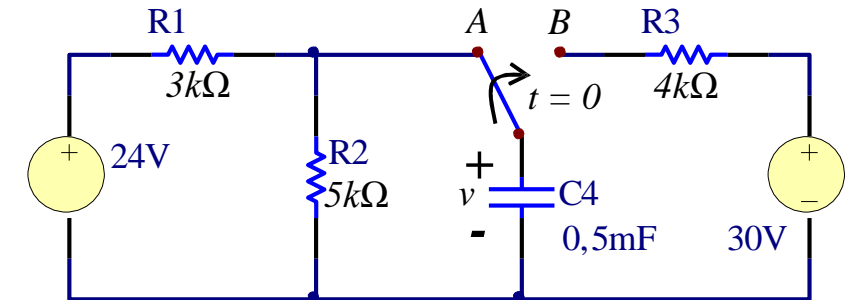7.4.1. Step response of a RC circuit

+ **Example 12:** The switch has been in position A for a long time. At $t = 0$, the switch moves to B. Determine $v(t)$ for $t > 0$ and calculate its value at $t = 1s$ and $4s$



The voltage across the capacitor at $t = -0$: $v(-0) = \frac{24}{R_1 + R_2} R_2 = 15V$

From charge conservation law at node A: $v(+0) = v(-0) = 15V$

For $t > 0$, the time constant is: $\tau = R_3 C_4 = 4 \cdot 10^3 \cdot 0.5 \cdot 10^{-3} = 2s$

Since the capacitor acts like an open circuit to DC at steady state: $v(\infty) = E_2 = 30V$

The voltage across C_4 is: $v(t) = v(+0)e^{-\frac{t}{\tau}} + v(\infty)\left(1 - e^{-\frac{t}{\tau}}\right) = 15e^{-0.5t} + 30(1 - e^{-0.5t}) = 30 - 15e^{-0.5t}V$

$$\text{At } t = 1s: \quad v(1s) = 30 - 15e^{-0.5 \cdot 1} = 20.902V$$

$$\text{At } t = 4s: \quad v(4s) = 30 - 15e^{-0.5 \cdot 4} = 27.970V$$

First Order Circuits

7.4. Step response of a RC/RL circuit

7.4.1. Step response of a RC circuit

+ Example 13: The switch has been closed for a long time and is opened at $t = 0$. Find i , v for all time




$$\text{For } t < 0: \quad v(0) = v(-0) = 10V \quad i = -\frac{v}{R_1} = -1A$$

$$\text{For } t > 0: \quad v(\infty) = \frac{30}{R_1 + R_2} R_2 = 20V$$

$$\tau = R_{eq} C_4 = \frac{R_1 R_2}{R_1 + R_2} \cdot C_4 = \frac{10 \cdot 20}{10 + 20} \cdot 0.25 = \frac{5}{3} s$$

$$\rightarrow v(t) = v(0)e^{-\frac{t}{\tau}} + v(\infty)\left(1 - e^{-\frac{t}{\tau}}\right) = 10e^{-0.6t} + 20(1 - e^{-0.6t}) = 20 - 10e^{-0.6t} V$$
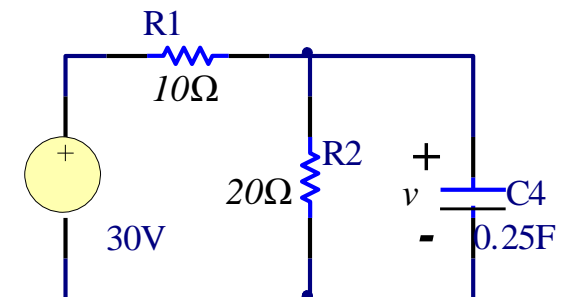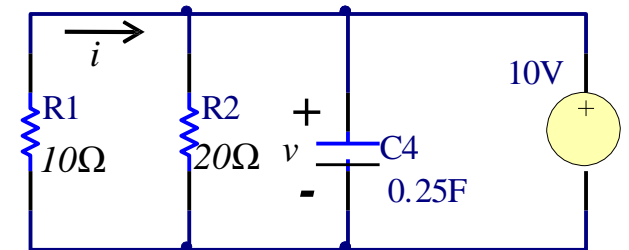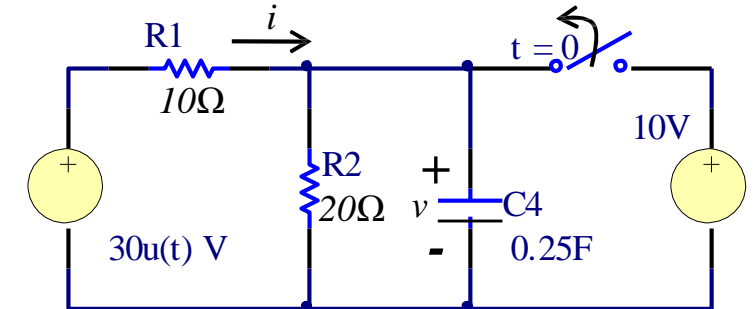
$$\rightarrow i(t) = \frac{v}{R_2} + C \frac{dv}{dt} = 1 - 0.5e^{-0.6t} + 0.25 \cdot (-10) \left(-\frac{3}{5}\right) e^{-0.6t} = 1 + e^{-0.6t} A$$



First Order Circuits

7.4. Step response of a RC/RL circuit

7.4.2. Step response of a RL circuit

+ Connect a R - L circuit to a DC source \rightarrow find i as the circuit response right after the connection

$\rightarrow i$ be the sum of the natural response and the forced response $i = i_n + i_f$



The natural response $i_n = Ae^{-\frac{R}{L}t}, \tau = \frac{L}{R}$

The steady-state response: $i_f = \frac{V_s}{R}$

At $t = 0$: $i(0) = i(-0) = I_0 \rightarrow A = I_0 - \frac{V_s}{R}$

Thus: $i(t) = Ae^{-\frac{t}{\tau}} + \frac{V_s}{R} = \left(I_0 - \frac{V_s}{R}\right)e^{-\frac{t}{\tau}} + \frac{V_s}{R}$
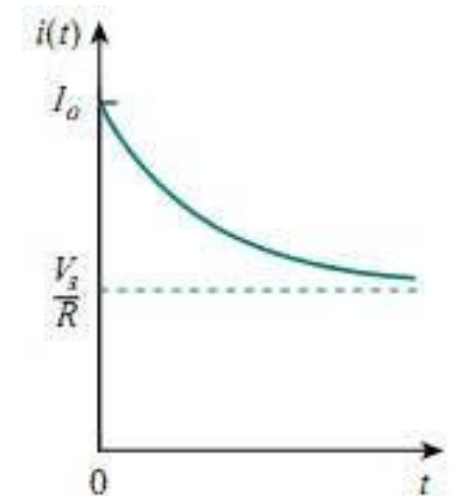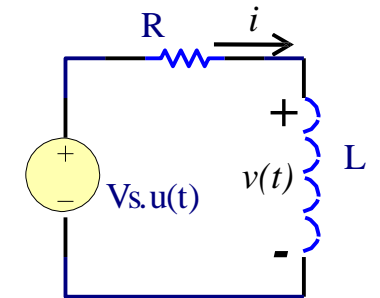
$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R}\right)e^{-\frac{t}{\tau}} = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}}$$



First Order Circuits

7.4. Step response of a RC/RL circuit

7.4.2. Step response of a RL circuit


+ **Example 14:** Find $i(t)$ for $t > 0$. Assume that the switch has been closed for a long time

$$\text{For } t < 0: i(-0) = \frac{E}{R_1} = \frac{10}{2} = 5A \rightarrow i(0) = i(-0) = 5A$$

$$\text{For } t > 0: i(\infty) = \frac{E}{R_1 + R_2} = \frac{10}{2+3} = 2A$$

$$\tau = \frac{L}{R_1 + R_2} = \frac{1}{3(2+3)} = \frac{1}{15} s$$

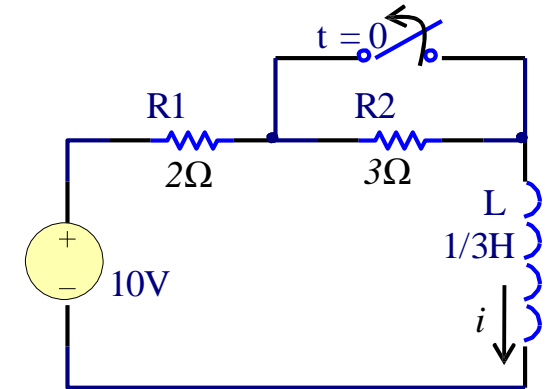Thus, the current through inductor L is: $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}} = 2 + (5 - 2)e^{-15t} = 2 + 3e^{-15t} A$



First Order Circuits

7.4. Step response of a RC/RL circuit

7.4.2. Step response of a RL circuit

+ **Example 15:** At $t = 0$, switch 1 is closed, and switch 2 is closed 4s later. Find $i(t)$ for $t > 0$. Calculate i for $t = 2s$ and $t = 5s$


For $t < 0$: Two switches are open $i(-0) = i(0) = 0A$

For $0 \leq t \leq 4$: The switch S_1 is closed, S_2 is open

$$i(\infty) = \frac{E_1}{R_1 + R_3} = \frac{40}{4 + 6} = 4A$$

$$\tau_1 = \frac{L}{R_{eq1}} = \frac{5}{4 + 6} = 0.5s$$
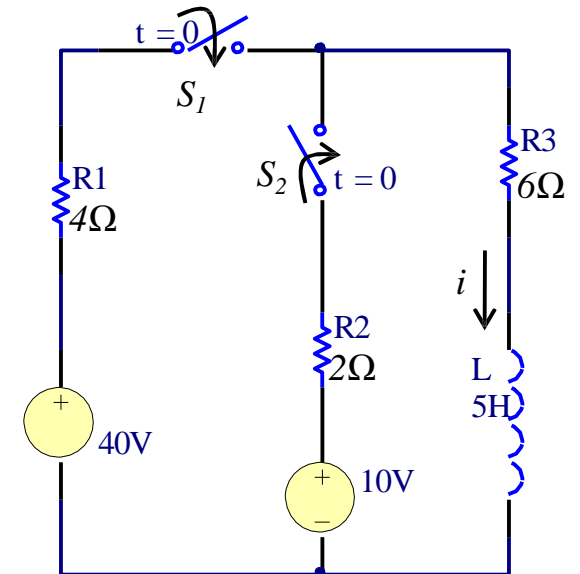
$$\rightarrow i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau_1}} = 4 - 4e^{-2t} A$$



First Order Circuits

7.4. Step response of a RC/RL circuit

7.4.2. Step response of a RL circuit

+ **Example 15:** At $t = 0$, switch 1 is closed, and switch 2 is closed 4s later. Find $i(t)$ for $t > 0$. Calculate i for $t = 2s$ and $t = 5s$

For $t > 4$: The switch S2 is closed


$$i(4) = 4 - 4e^{-2.4} \approx 4A$$

Using nodal analysis to find I in steady state

$$\frac{40 - v}{R_1} + \frac{10 - v}{R_2} = \frac{v}{R_3} \rightarrow v = \frac{180}{11} V \rightarrow i(\infty) = \frac{v}{R_3} = 2.72A$$

$$\tau = \frac{L}{R_{eq}} = \frac{L}{R_3 + \frac{R_1 R_2}{R_1 + R_2}} = \frac{15}{22} s$$
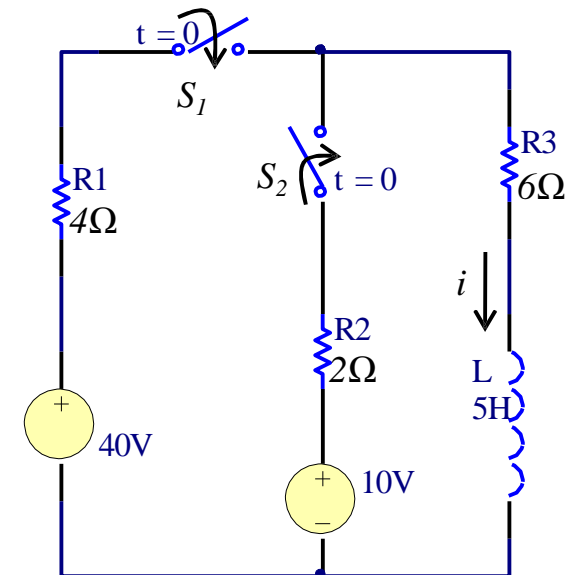
$$\rightarrow i(t) = i(\infty) + [i(4) - i(\infty)]e^{-\frac{t-4}{\tau}} = 2.72 + 1.28e^{-1.467(t-4)} A$$



First Order Circuits

7.4. Step response of a RC/RL circuit

7.4.2. Step response of a RL circuit

+ **Example 15:** At $t = 0$, switch 1 is closed, and switch 2 is closed 4s later. Find $i(t)$ for $t > 0$. Calculate i for $t = 2s$ and $t = 5s$

For all time, we have:


$$i(t) = \begin{cases} 0 & t \leq 0 \\ 4(1 - e^{-2t}) & 0 \leq t \leq 4 \\ 2.72 + 1.28e^{-1.467(t-4)} & t \geq 4 \end{cases}$$

At $t = 2s$:

$$i(2) = 4(1 - e^{-2 \cdot 2}) = 3.93A$$

At $t = 5s$:
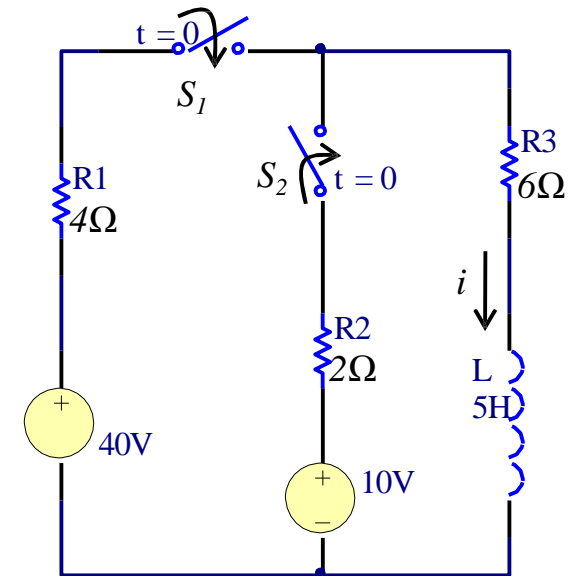
$$i(5) = 2.72 + 1.28e^{-1.467(5-4)} = 3.02A$$



First Order Circuits

7.5. First order op-amp circuits

- + Op amp circuit containing a storage element: → exhibit first-order behaviors
- + Examples of first-order op amp circuits: differentiators and integrators (in chapter 5)
- + For practical reasons, inductors are hardly ever used in op amp circuits → the op amp circuits considered here are of the RC type
- + Methods to analyze op amp circuits:
 - Using nodal analysis
 - Using the Thevenin equivalent circuit to simplify the op amp circuit

First Order Circuits

7.5. First order op-amp circuits

+ **Example 16:** Find v_o for $t > 0$, give that $v(0) = 3V$

Solution 1:

We have: $-\frac{v_1}{R_i} = C \frac{dv}{dt}$


Potentials at node 3 and node 4 are equal to zero:

$$v_1 - 0 = V \rightarrow v_1 = V \rightarrow \frac{dv}{dt} + \frac{v}{R_i C} = 0$$

$$\rightarrow v(t) = V_0 e^{-\frac{t}{\tau}}, \tau = R_i C \rightarrow v(t) = 3e^{-10t} V$$

At $t > 0$, applying KCL at node 3 gives:
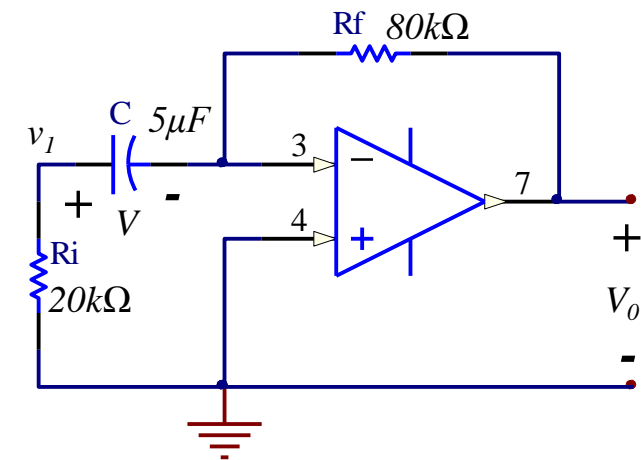
$$C \frac{dv}{dt} = \frac{-V_0}{R_f} \rightarrow V_0 = -R_f C \frac{dv}{dt} = -80 \cdot 10^3 \cdot 5 \cdot 10^{-6} (-30e^{-10t}) = 12e^{-10t} V$$



First Order Circuits

7.5. First order op-amp circuits

+ **Example 16:** Find v_o for $t > 0$, give that $v(0) = 3V$

Solution 2:

Voltage across the capacitor C : $v(+0) = v(-0) = 3V$

Apply KCL at node 3: $\frac{3}{R_i} + \frac{-V_o(+0)}{R_f} = 0 \rightarrow V_o(+0) = 12V$

The circuit is source free: $V_o(\infty) = 0V$



To find τ , need calculate R_{eq} across C :

→ Replace C by a 1-A current source

→ Applying KVL to the input loop:

$$R_i i_s - v = 0 \rightarrow 20 \cdot 10^3 \cdot 1 - v = 0 \rightarrow v = 20kV \rightarrow R_{eq} = \frac{v}{i_s} = 20k\Omega$$
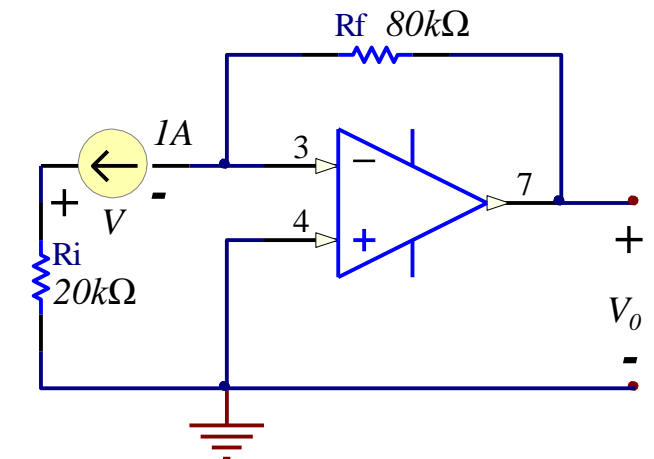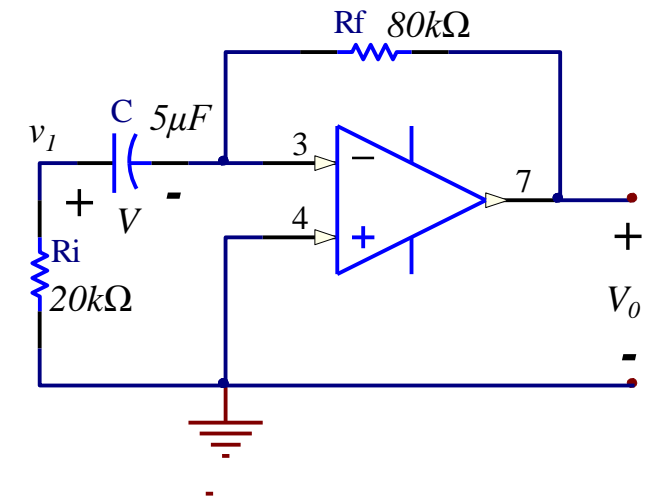
$$\rightarrow \tau = R_{eq} C = 0.1s \rightarrow V_o = V_o(\infty) + [V_o(0) - V_o(\infty)]e^{-\frac{t}{\tau}} = 12e^{-10t}V, t > 0$$



First Order Circuits

7.5. First order op-amp circuits

+ **Example 17:** Determine $v(t)$ and $v_o(t)$

$V(t)$ is the step response:

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-\frac{t}{\tau}}, t > 0$$

No current enters the op amp \rightarrow the elements on the feedback loop constitute an RC circuit

$$\tau = R_4 C = 50 \cdot 10^3 \cdot 10^{-6} = 0.05s$$


For $t < 0$: The switch is opened $V_o(0) = 0V$

$$\text{For } t > 0: V_1 = \frac{R_2}{R_1 + R_2} E = 2V$$

At steady state: C acts like an open circuit \rightarrow op amp is a non-inverting amplifier

$$V_o(\infty) = \left(1 + \frac{R_4}{R_3}\right) v_1 = 3.5 \times 2 = 7V \quad V_1(\infty) = v(\infty) + V_o(\infty) \rightarrow v(\infty) = V_1(\infty) - V_o(\infty) = 2 - 7 = -5V$$
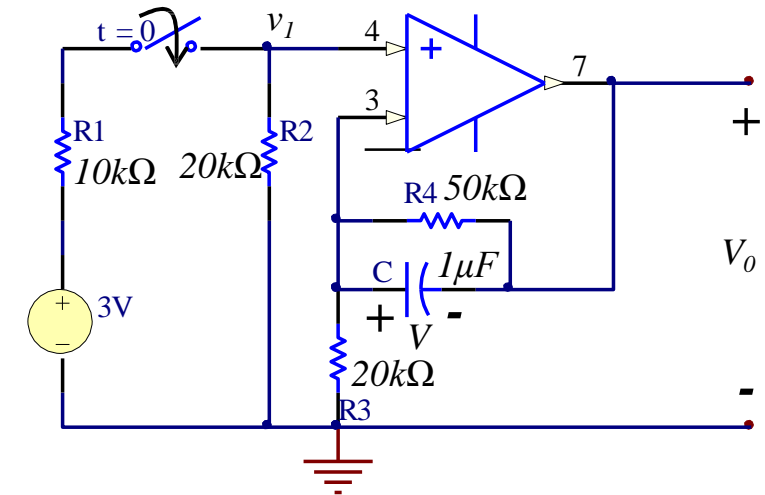
$$\rightarrow v(t) = v(\infty) + [v(0) - v(\infty)]e^{-\frac{t}{\tau}} = -5 + 5e^{-20t} \quad \rightarrow V_o(t) = V_1(t) - v(t) = 2 - 2e^{-20t} - (-5 + 5e^{-20t}) = 7 - 7e^{-20t}V, t > 0$$



First Order Circuits

7.5. First order op-amp circuits

+ **Example 18:** Determine *step response* $v_o(t)$

Remove C, and find the Thevenin equivalent at its terminal

Open voltage at the terminal:

$$V_{ab} = -\frac{R_f}{R_i} V_i \rightarrow V_{th} = \frac{R_3}{R_2 + R_3} V_{ab} = -\frac{R_3}{R_2 + R_3} \frac{R_f}{R_i} V_i = -2.5u(t)$$



Equivalent resistor at the terminal:

$$R_{th} = R_3 // (R_0 + R_2) \rightarrow R_{th} = \frac{(R_0 + R_2)R_3}{R_0 + R_2 + R_3} = \frac{R_2 R_3}{R_2 + R_3} = 5k\Omega$$

We obtain the Thevenin equivalent circuit:

$$V_o(t) = -2.5 \left(1 - e^{-\frac{t}{\tau}} \right) u(t), \tau = R_{th} C = 5 \cdot 10^3 \cdot 2 \cdot 10^{-6} = 0.01s$$
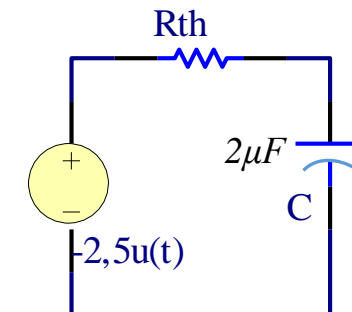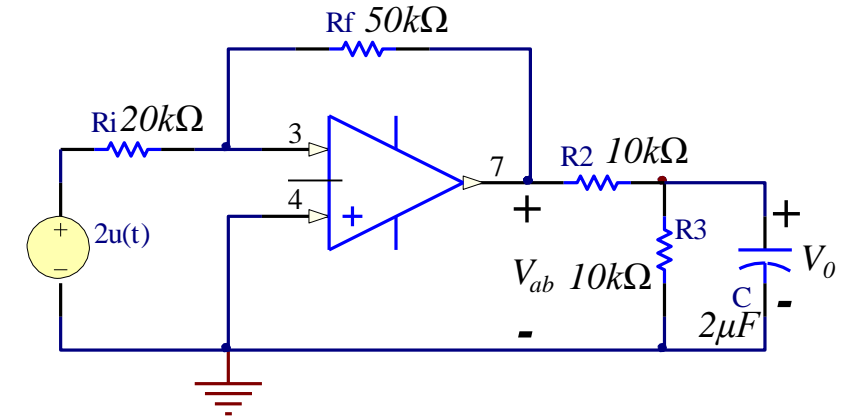
$$\rightarrow V_o(t) = -2.5(1 - e^{-100t})u(t)V, t > 0$$



First Order Circuits

7.6. Applications

7.6.1. Delay circuits

+ As an example → consider an RC circuit:

→ Capacitor connected in parallel with a neon lamp

→ Voltage source can provide enough voltage to fire the lamp


+ Close the switch: V_C increases to 110V with the time constant $(R_1 + R_2)C$

→ The lamp will act as an open-circuit and not emit light until the voltage across it exceeds a particular level (70V)

→ When V_C reaches, the lamp fires and the capacitor discharges through it → V_C drops and the lamp turn off

→ The lamp acts again as an open-circuit and C recharges

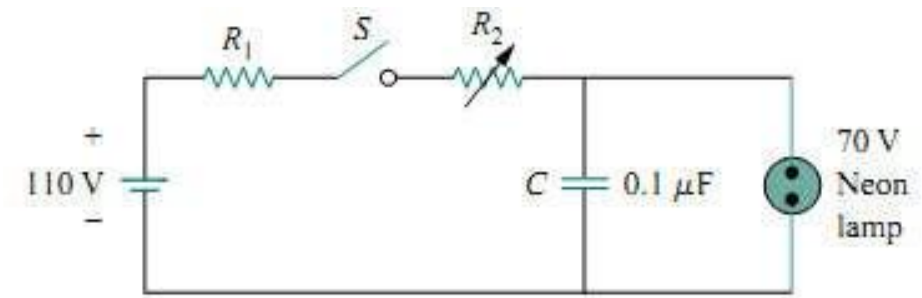→ Adjusting R_2 , we can introduce either short or long time delays



First Order Circuits

7.6. Applications

7.6.2. Photoflash unit

+ This application exploits the ability of the capacitor to oppose any abrupt change in voltage

+ Principle:

Switch is in 1: C charges slowly due to the large time constant $\tau = R_1 C$

→ V_C rises gradually from zero to V_S




→ I_C decreases from I_1 to 0

Switch is in 2: C discharges

→ Low resistance R_2 of the photo-lamp permits a high discharge current with peak I_2 in a short duration

$$t_{\text{discharge}} = 5R_2 C$$

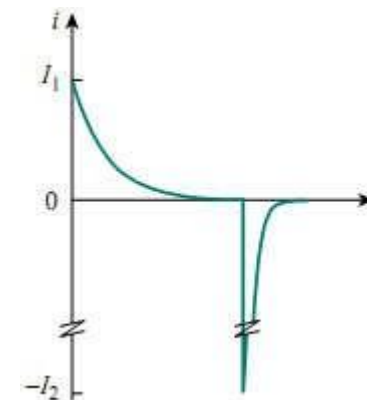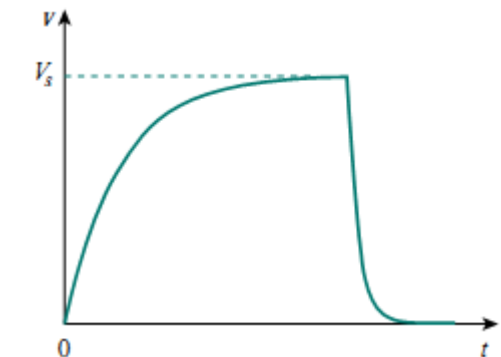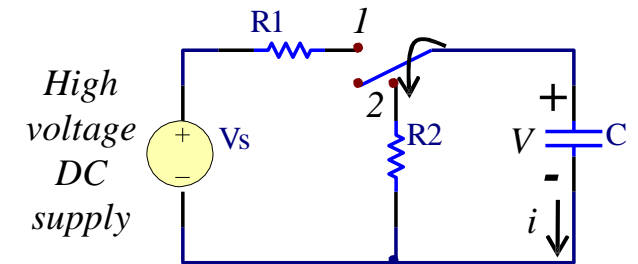→ The circuit provides a short-duration, high current pulse



First Order Circuits

7.6. Applications

7.6.2. Photoflash unit

+ **Example 19:** An **electronic flashgun** has a **current limiting** $R_1 = 6k\Omega$, and $C = 2000\mu F$ charged to 240V. If the **lamp resistance** R_2 is 12Ω , we have:

→ *Peak charging current:*
$$I_1 = \frac{V_s}{R_1} = \frac{240}{6 \cdot 10^3} = 40mA$$


→ *Time required for the C to fully charge:*
$$t_{charge} = 5R_1C = 5 \cdot 6 \cdot 10^3 \cdot 2000 \cdot 10^{-6} = 60s$$

→ *Peak discharging current:*
$$I_1 = \frac{V_s}{R_2} = \frac{240}{12} = 20A$$

→ *Energy stored:*
$$w = \frac{1}{2}CV_s^2 = \frac{1}{2}2000 \cdot 10^{-6} \cdot 240^2 = 57.6J$$

→ *Energy stored in C is dissipated across the lamp during the discharging period:*
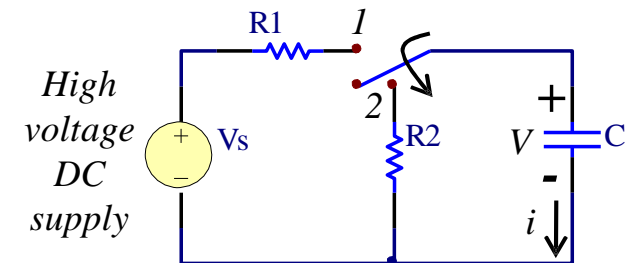
$$t_{discharge} = 5R_2C = 5 \cdot 12 \cdot 2000 \cdot 10^{-6} = 0.12s \rightarrow p = \frac{w}{t_{discharge}} = \frac{57.6}{0.12} = 480W$$



First Order Circuits

7.6. Applications

7.6.3. Relay circuit

+ **Relay:** → an electromagnetic device used to open or close a switch that controls another circuit



+ **Operation principle** of a relay: *RL* circuit

When S_1 is closed → i_L increases, produces a magnetic field

The magnetic field → pull the movable contact in the other circuit and close switch S_2

+ **Relay delay time:** time interval t_d between the closure of switches S_1 and S_2

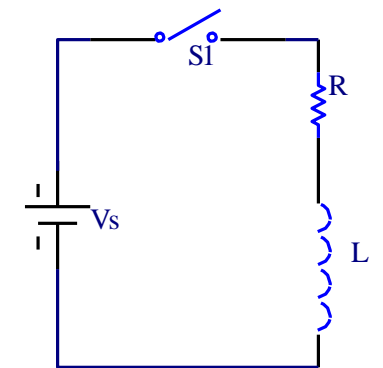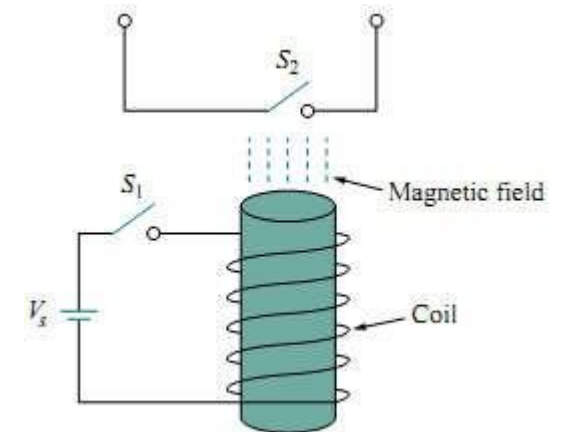+ **Application of Relays:** in the earliest *digital circuits* and are still used for *switching high power circuits*



First Order Circuits

7.6. Applications

7.6.3. Relay circuit

+ **Example 20:** The coil of a certain relay is operated by a 12V battery. If the coil has a resistance of 150Ω and an inductance of 30mH and the current needed to pull in is 50mA . Calculate the relay delay time

The current through the coil: $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{R}{L}t}$

$$i(0) = 0, i(\infty) = \frac{v_s}{R} = \frac{12}{150} = 80\text{mA}, \tau = \frac{L}{R} = \frac{30 \cdot 10^{-3}}{150} = 0.2\text{ms}$$

Thus: $i(t) = 80 - 80e^{-\frac{t}{\tau}}\text{mA}$

At t_d : $i(t_d) = 80 - 80e^{-\frac{t_d}{\tau}} = 50 \rightarrow e^{-\frac{t_d}{\tau}} = \frac{3}{8} \rightarrow t_d = \tau \ln \frac{8}{3} = 0.2 \ln \frac{8}{3} = 0.1962\text{ms}$