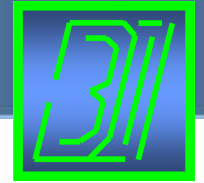




TRƯỜNG ĐẠI HỌC
BÁCH KHOA HÀ NỘI

Nguyễn Công Phương



Electric Circuit Theory

Sinusoidal Steady-State Analysis

Contents

- I. Basic Elements Of Electrical Circuits
- II. Basic Laws
- III. Electrical Circuit Analysis
- IV. Circuit Theorems
- V. Active Circuits
- VI. Capacitor And Inductor
- VII. First Order Circuits
- VIII. Second Order Circuits
- IX. Sinusoid and Phasors
- X. Sinusoidal Steady State Analysis**
- XI. AC Power Analysis
- XII. Three-phase Circuits
- XIII. Magnetically Coupled Circuits
- XIV. Frequency Response
- XV. The Laplace Transform
- XVI. Two-port Networks




Sinusoidal Steady-State Analysis

1. Sinusoidal Steady-State Analysis
2. Ohm's Law
3. Kirchhoff's Laws
4. Impedance Combinations
5. Branch Current Method
6. Node Voltage Method
7. Mesh Current Method
8. Superposition Theorem
9. Source Transformation
10. Thévenin & Norton Equivalent Circuits
11. Op Amp AC Circuits



Sinusoidal Steady-State Analysis (1)

Ex. 1

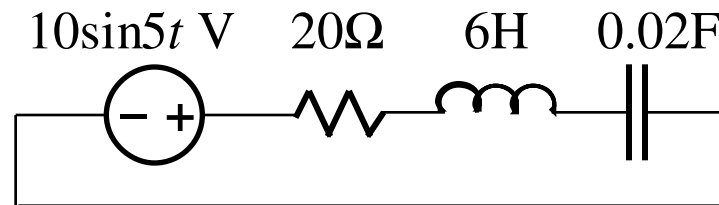

$$20i + 6 \frac{di}{dt} + \frac{1}{0.02} \int i dt = 10 \sin 5t$$


$$\rightarrow \left. \begin{aligned} 20 \frac{di}{dt} + 6 \frac{d^2 i}{dt^2} + \frac{i}{0.02} &= 50 \cos 5t \\ i &= I_m \sin(5t + \phi) \end{aligned} \right\}$$

$$\rightarrow 100I_m \cos(5t + \phi) - 150I_m \sin(5t + \phi) + 50I_m \sin(5t + \phi) = 50 \cos 5t$$

$$\rightarrow 2\sqrt{2}I_m \sin(5t + \phi + 135^\circ) = \sin(5t + 90^\circ)$$

$$\rightarrow \begin{cases} 2\sqrt{2}I_m = 1 \\ \phi + 135^\circ = 90^\circ \end{cases} \rightarrow \begin{cases} I_m = 0.35 \\ \phi = -45^\circ \end{cases}$$
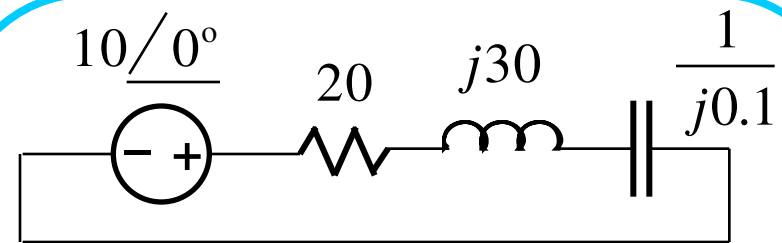
$$\rightarrow \boxed{i = 0.35 \sin(5t - 45^\circ) \text{ A}}$$




$$\mathbf{I} = \frac{10 \angle 0^\circ}{20 + j30 + \frac{1}{j0.1}} = 0.35 \angle -45^\circ \text{ A}$$

$$\rightarrow \boxed{i = 0.35 \sin(5t - 45^\circ) \text{ A}}$$

Sinusoidal Steady-State Analysis (2)


Ex. 1

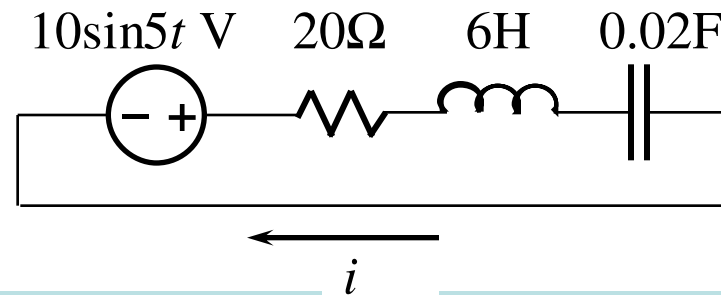

1. Transform to phasor domain

2. Solve the problem using dc circuit analysis

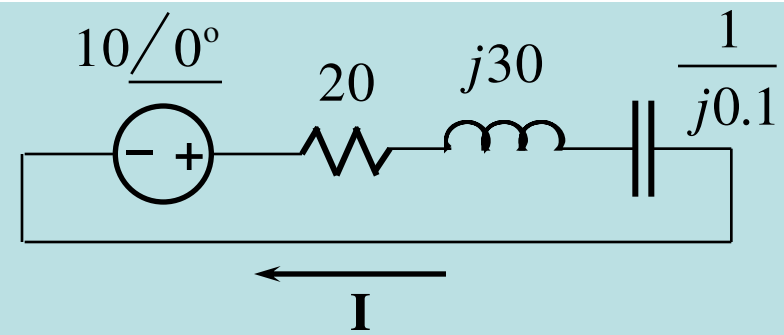3. Transform the resulting phasor to the time-domain.



$$\mathbf{I} = \frac{10\angle 0^\circ}{20 + j30 + \frac{1}{j0.1}} = 0.35\angle -45^\circ \text{ A}$$

$$\rightarrow i = 0.35 \sin(5t - 45^\circ) \text{ A}$$

Ex. 2 Sinusoidal Steady-State Analysis (3)

Given $i(t) = 2\sin(50t)$. Find $v(t)$?




$$I = 2A$$

$$V_R = RI = 100 \times 2 = 200 \text{ V}$$

$$V_L = Z_L I = j100 \times 2 = j200 \text{ V}$$

$$\begin{aligned} V &= V_R + V_L = 200 + j200 \\ &= 200\sqrt{2} \angle 45^\circ \text{ V} \end{aligned}$$
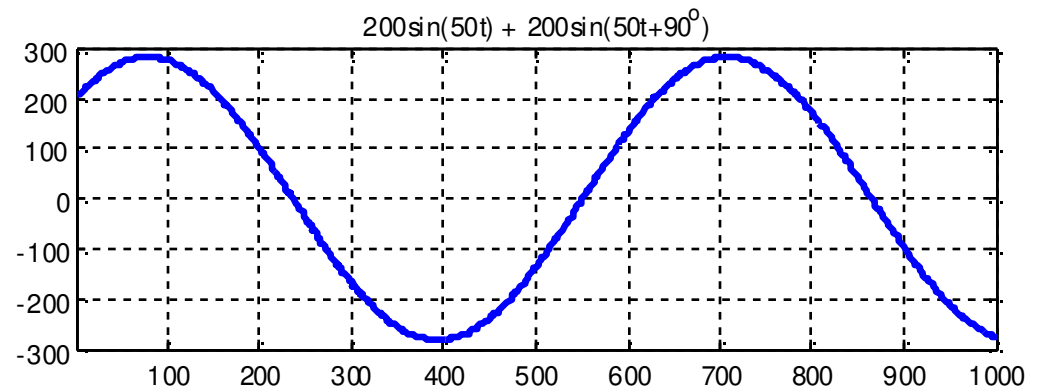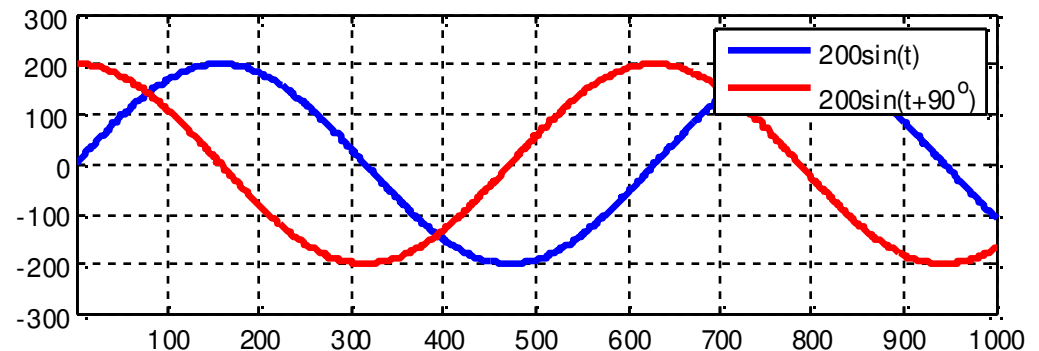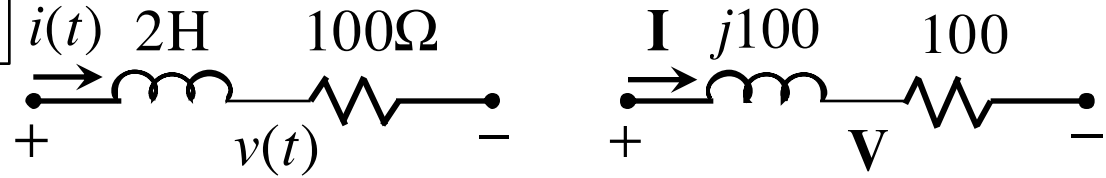
$$\rightarrow v(t) = 200\sqrt{2} \sin(50t + 45^\circ) \text{ V}$$



$$V_R = 100 \times 2 = 200V$$

$$V_L = 100 \times 2 = 200V$$

$$V = 200 + 200 = 400V$$

Sinusoidal Steady-State Analysis

1. Sinusoidal Steady-State Analysis
2. **Ohm's Law**
3. Kirchhoff's Laws
4. Impedance Combinations
5. Branch Current Method
6. Node Voltage Method
7. Mesh Current Method
8. Superposition Theorem
9. Source Transformation
10. Thévenin & Norton Equivalent Circuits
11. Op Amp AC Circuits



Ohm's Law (1)

$$\begin{array}{l} \mathbf{V}_R = R\mathbf{I} \quad \rightarrow \quad \frac{\mathbf{V}_R}{\mathbf{I}} = R \\ \mathbf{V}_L = j\omega L\mathbf{I} \quad \rightarrow \quad \frac{\mathbf{V}_L}{\mathbf{I}} = j\omega L \\ \mathbf{V}_C = \frac{\mathbf{I}}{j\omega C} \quad \rightarrow \quad \frac{\mathbf{V}_C}{\mathbf{I}} = \frac{1}{j\omega C} \end{array} \left. \vphantom{\begin{array}{l} \mathbf{V}_R = R\mathbf{I} \\ \mathbf{V}_L = j\omega L\mathbf{I} \\ \mathbf{V}_C = \frac{\mathbf{I}}{j\omega C} \end{array}} \right\} \rightarrow \boxed{\frac{\mathbf{V}}{\mathbf{I}} = \mathbf{Z}} \rightarrow \mathbf{V} = \mathbf{Z}\mathbf{I}$$

\mathbf{Z} : impedance (Ω)

$$\text{Admittance (S): } \mathbf{Y} = \frac{1}{\mathbf{Z}}$$

Ohm's Law (2)

$$\boxed{\frac{\mathbf{V}}{\mathbf{I}} = \mathbf{Z}}$$

$$\frac{\mathbf{V}_R}{\mathbf{I}} = R \rightarrow \mathbf{Z}_R = R$$

$$\mathbf{Y}_R = \frac{1}{R}$$

$$\frac{\mathbf{V}_L}{\mathbf{I}} = j\omega L \rightarrow \mathbf{Z}_L = j\omega L$$

$$\mathbf{Y}_L = \frac{1}{j\omega L} = \frac{-j}{\omega L}$$


$$\frac{\mathbf{V}_C}{\mathbf{I}} = \frac{1}{j\omega C} \rightarrow \mathbf{Z}_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

$$\mathbf{Y}_C = j\omega C$$

Ohm's Law (3)

	$\mathbf{Z}_L = j\omega L$	$\mathbf{Z}_C = \frac{-j}{\omega C}$
$\omega = 0$	$\mathbf{Z}_L = 0$ Short circuit	$\mathbf{Z}_C \rightarrow \infty$ Open circuit
$\omega \rightarrow \infty$	$\mathbf{Z}_L \rightarrow \infty$ Open circuit	$\mathbf{Z}_C = 0$ Short circuit


Ohm's Law (4)

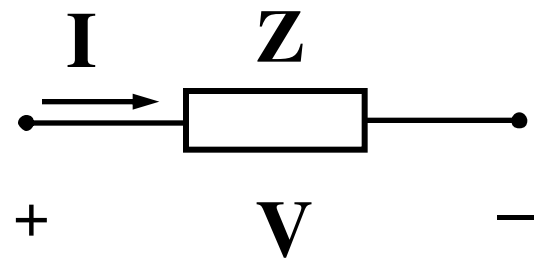
$$V = ZI$$


$$Z = R + jX$$

R : resistance

X : reactance

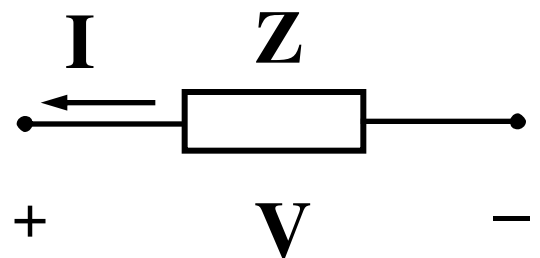

$$V = -ZI$$

Ohm's Law (5)

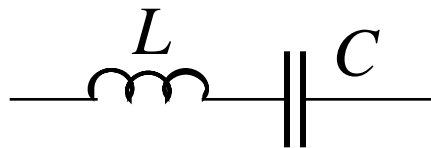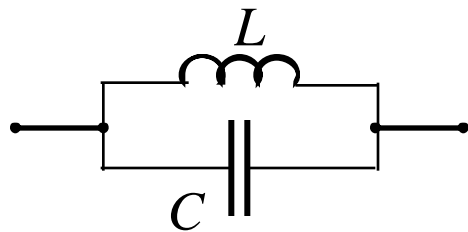

$$Z = j\omega L + \frac{1}{j\omega C}$$

$$\text{If } j\omega L + \frac{1}{j\omega C} = 0 \rightarrow \frac{-\omega^2 LC + 1}{j\omega C} = 0 \rightarrow \omega = \frac{1}{\sqrt{LC}} \left. \vphantom{\frac{-\omega^2 LC + 1}{j\omega C}} \right\} \rightarrow Z = 0$$



$$Z = \frac{j\omega L \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = \frac{L/C}{j\omega L + \frac{1}{j\omega C}}$$

$$\text{If } j\omega L + \frac{1}{j\omega C} = 0 \rightarrow \frac{-\omega^2 LC + 1}{j\omega C} = 0 \rightarrow \omega = \frac{1}{\sqrt{LC}} \left. \vphantom{\frac{-\omega^2 LC + 1}{j\omega C}} \right\} \rightarrow Z = \infty$$

Sinusoidal Steady-State Analysis

1. Sinusoidal Steady-State Analysis
2. Ohm's Law
- 3. Kirchhoff's Laws**
4. Impedance Combinations
5. Branch Current Method
6. Node Voltage Method
7. Mesh Current Method
8. Superposition Theorem
9. Source Transformation
10. Thévenin & Norton Equivalent Circuits
11. Op Amp AC Circuits



Kirchhoff's Law (1)

$$v_1 + v_2 + \dots + v_n = 0$$

$$\rightarrow V_{m1} \sin(\omega t + \phi_1) + V_{m2} \sin(\omega t + \phi_2) + \dots + V_{mn} \sin(\omega t + \phi_n) = 0$$

$$\rightarrow \boxed{\mathbf{V}_1 + \mathbf{V}_2 + \dots + \mathbf{V}_n = 0}$$



Kirchhoff's Law (2)

$$i_1 + i_2 + \dots + i_n = 0$$

$$\rightarrow I_{m1} \sin(\omega t + \phi_1) + I_{m2} \sin(\omega t + \phi_2) + \dots + I_{mn} \sin(\omega t + \phi_n) = 0$$

$$\rightarrow \boxed{\mathbf{I}_1 + \mathbf{I}_2 + \dots + \mathbf{I}_n = 0}$$





Sinusoidal Steady-State Analysis

1. Sinusoidal Steady-State Analysis
2. Ohm's Law
3. Kirchhoff's Laws
- 4. Impedance Combinations**
5. Branch Current Method
6. Node Voltage Method
7. Mesh Current Method
8. Superposition Theorem
9. Source Transformation
10. Thévenin & Norton Equivalent Circuits
11. Op Amp AC Circuits





Impedance Combinations (1)

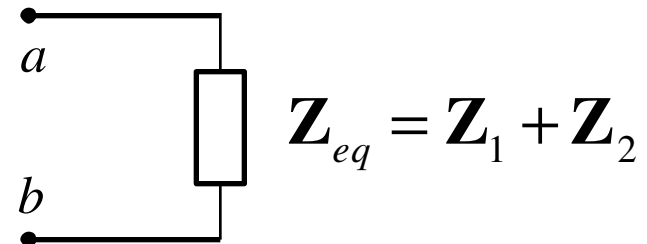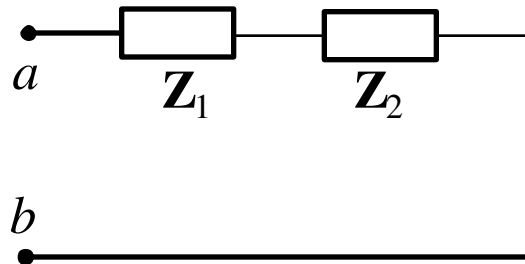

$$V_1 = \frac{Z_1}{Z_1 + Z_2} V_{ab}$$

$$Z_{eq} = Z_1 + Z_2 + \dots + Z_n$$

Impedance Combinations (2)

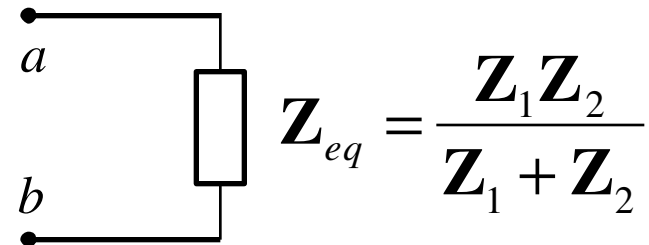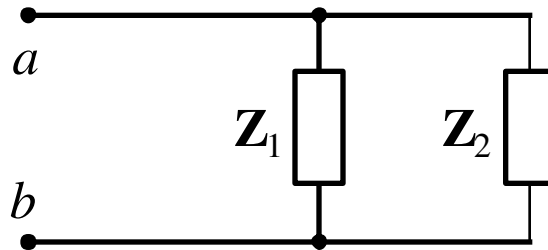

$$\mathbf{I}_1 = \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{I}_{ab}$$

$$\frac{1}{\mathbf{Z}_{eq}} = \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \dots + \frac{1}{\mathbf{Z}_n}$$

Ex. 1 Impedance Combinations (3)

$e = 10\sin 10t$ V; $L = 1$ H; $R_1 = 1 \Omega$; $R_2 = 5 \Omega$;
 $C = 0.01$ F; find i_C , i_{R2} , i_{R1} , & v_{R1} ?

$$\mathbf{Z}_{R2,C} = \frac{5(-j10)}{5 - j10} = 4 - j2 \Omega$$



$$\mathbf{Z}_t = j10 + 1 + \mathbf{Z}_{R2,C} = j10 + 1 + 4 - j2 = 5 + j8 \Omega$$

$$\mathbf{I}_{R1} = \frac{\mathbf{E}}{\mathbf{Z}_t} = \frac{10}{5 + j8} = 1.06 \angle -58^\circ \text{ A}$$


$$\mathbf{V}_{R1} = R_1 \mathbf{I}_{R1} = 1 \times 1.06 \angle -58^\circ = 1.06 \angle -58^\circ \text{ V}$$

$$\mathbf{I}_{R2} = \frac{\mathbf{I}_{R1}(-j10)}{5 - j10} = \frac{(1.06 \angle -58^\circ)(-j10)}{5 - j10} = 0.95 \angle -84.6^\circ \text{ A}$$
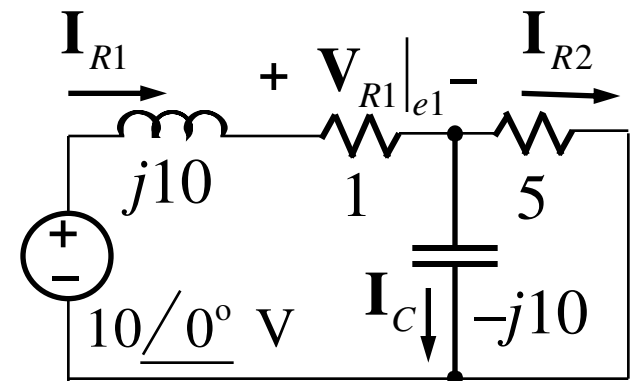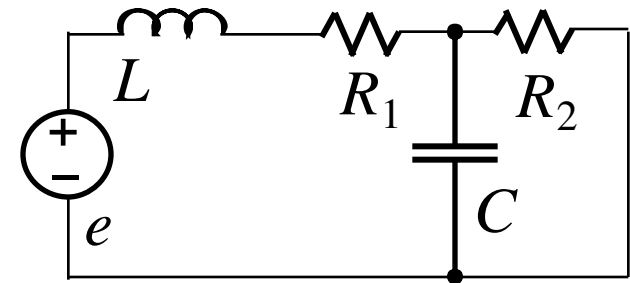
$$\mathbf{I}_C = \mathbf{I}_{R1} - \mathbf{I}_{R2} = 1.06 \angle -58^\circ - 0.95 \angle -84.6^\circ = 0.47 \angle 5.4^\circ \text{ A}$$



Impedance Combinations (4)

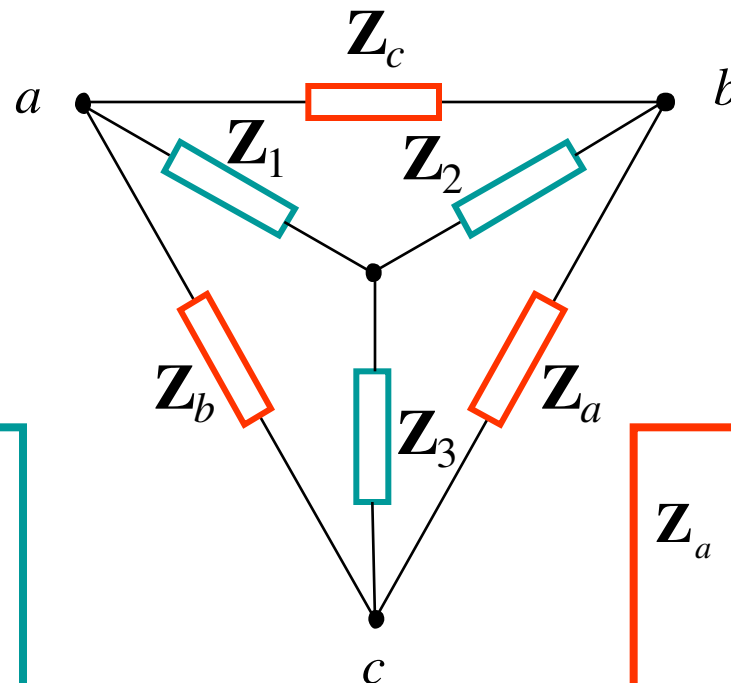

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$





$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

Ex. 2 Impedance Combination (5)

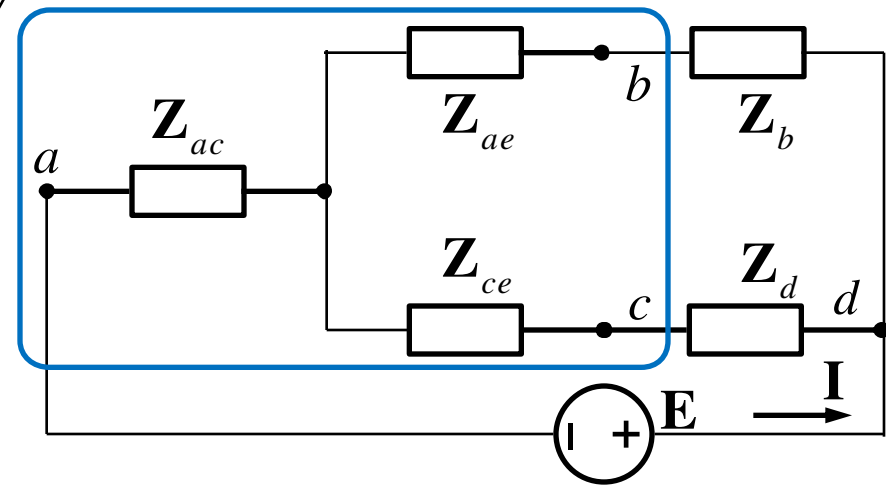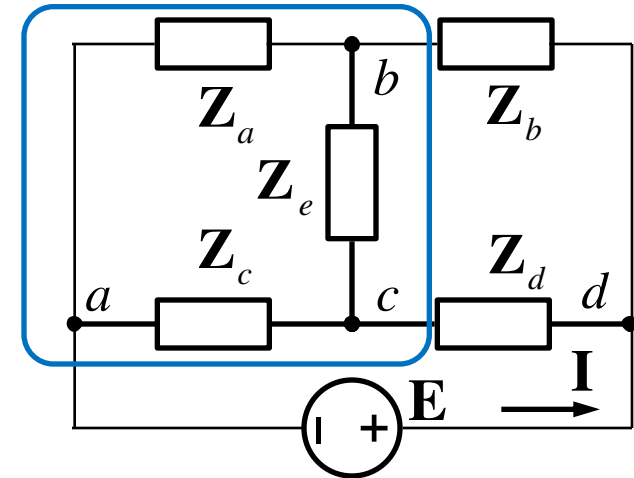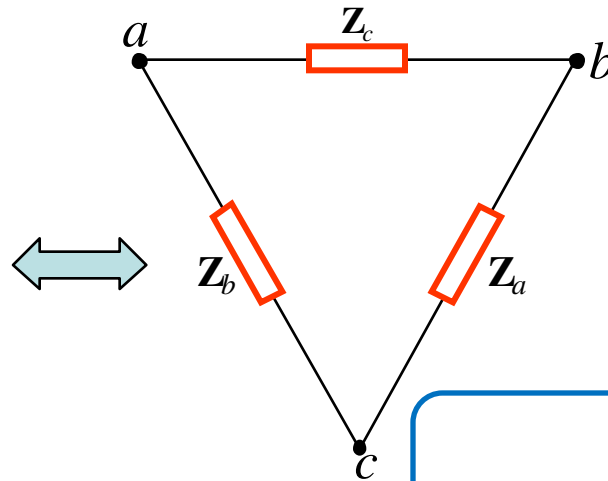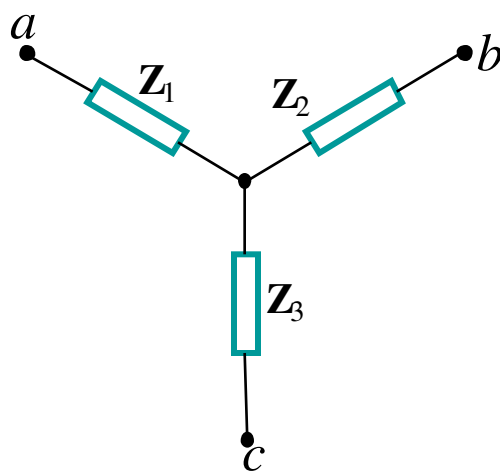$e = 100\sin 20t$ V; $Z_a = 20 \Omega$; $Z_b = 5 - j10 \Omega$;
 $Z_c = j25 \Omega$; $Z_d = 15 + j15 \Omega$; $Z_e = -j8 \Omega$. find i ?



Ex. 2 Impedance Combination (6)

$e = 100\sin 20t$ V; $Z_a = 20 \Omega$; $Z_b = 5 - j10 \Omega$;
 $Z_c = j25 \Omega$; $Z_d = 15 + j15 \Omega$; $Z_e = -j8 \Omega$. find i ?



$$Z_{ac} = \frac{Z_a Z_c}{Z_a + Z_c + Z_e} = \frac{20(j25)}{20 + j25 - j8} = 12.33 + j14.51 \Omega$$

$$Z_{ae} = \frac{Z_a Z_e}{Z_a + Z_c + Z_e} = \frac{20(-j8)}{20 + j25 - j8} = -3.95 - j4.64 \Omega$$

$$Z_{ce} = \frac{Z_c Z_e}{Z_a + Z_c + Z_e} = \frac{j25(-j8)}{20 + j25 - j8} = 5.81 - j4.93 \Omega$$




$$Z_t = Z_{ac} + [(Z_{ae} + Z_b) \parallel (Z_{ce} + Z_d)] = 22.46 + j3.18 \Omega$$
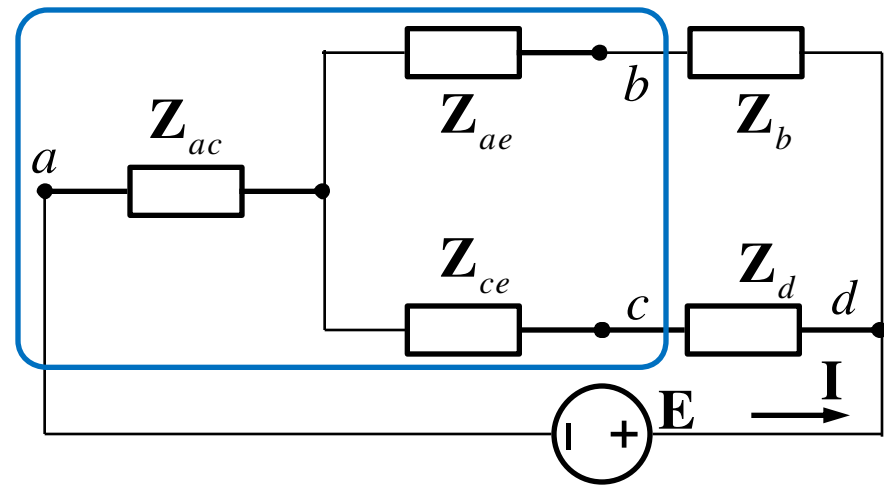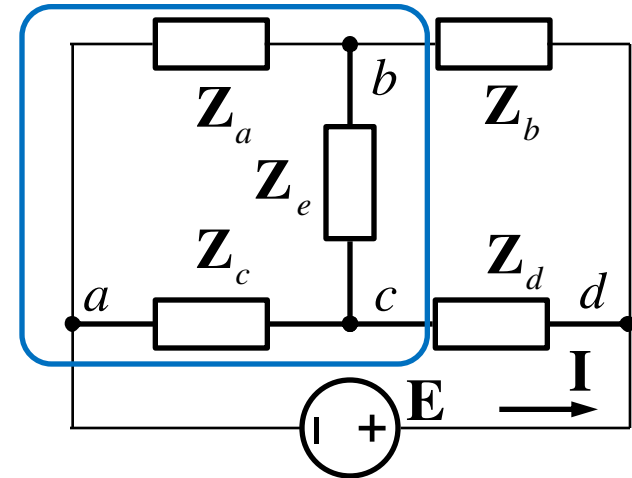
$$I = \frac{E}{Z_t} = \frac{100}{22.46 + j3.18} = 4.37 - j0.62 \text{ A}$$



Ex. 2 Impedance Combination (7)

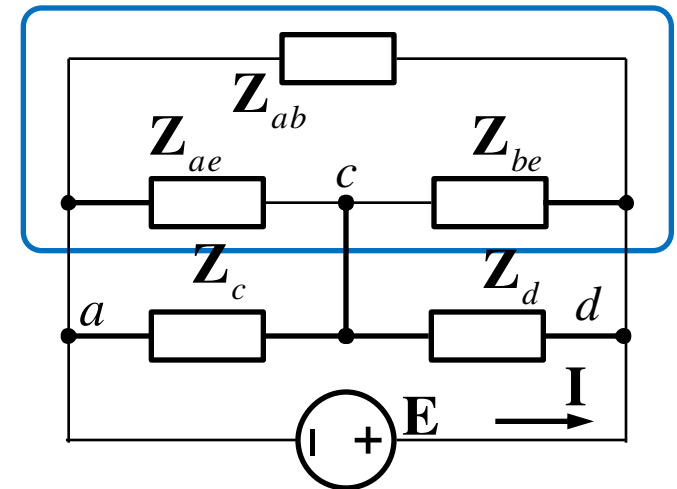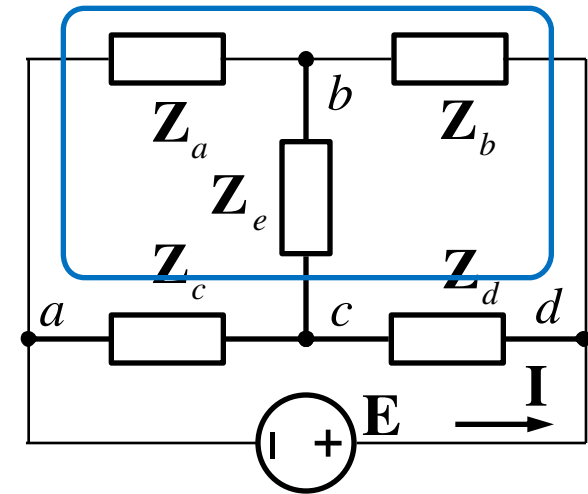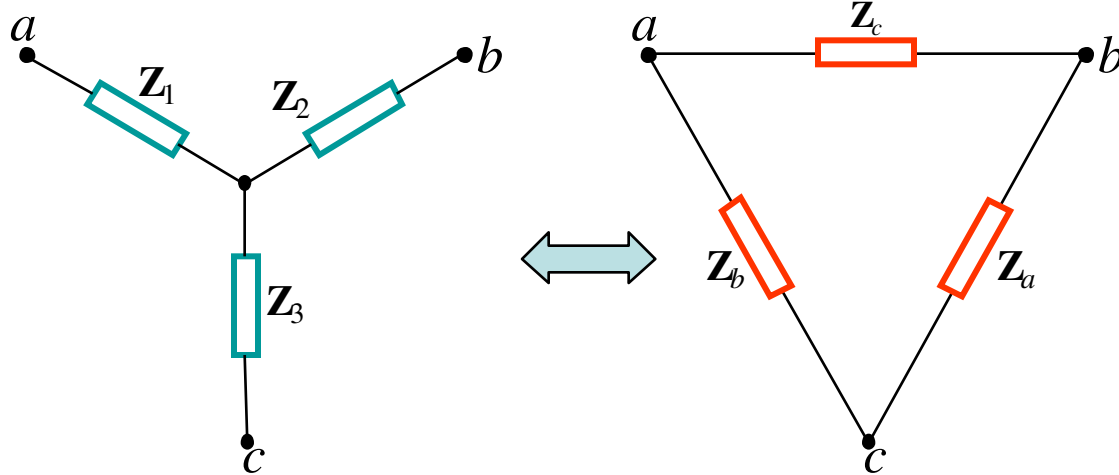$e = 100\sin 20t$ V; $Z_a = 20 \Omega$; $Z_b = 5 - j10 \Omega$;
 $Z_c = j25 \Omega$; $Z_d = 15 + j15 \Omega$; $Z_e = -j8 \Omega$. find i ?



Ex. 2 Impedance Combination (8)

$e = 100\sin 20t$ V; $Z_a = 20 \Omega$; $Z_b = 5 - j10 \Omega$;
 $Z_c = j25 \Omega$; $Z_d = 15 + j15 \Omega$; $Z_e = -j8 \Omega$. find i ?

$$Z_{ab} = \frac{Z_a Z_b + Z_b Z_e + Z_e Z_a}{Z_e} = 50 + j2.50 \Omega$$



$$Z_{ae} = \frac{Z_a Z_b + Z_b Z_e + Z_e Z_a}{Z_b} = 32.80 - j14.40 \Omega$$

$$Z_{be} = \frac{Z_a Z_b + Z_b Z_e + Z_e Z_a}{Z_a} = 1.00 - j20 \Omega$$

$$Z_t = Z_{ab} // [(Z_{ae} // Z_c) + (Z_{be} + Z_d)]$$

$$= 22.46 + j3.18 \Omega$$
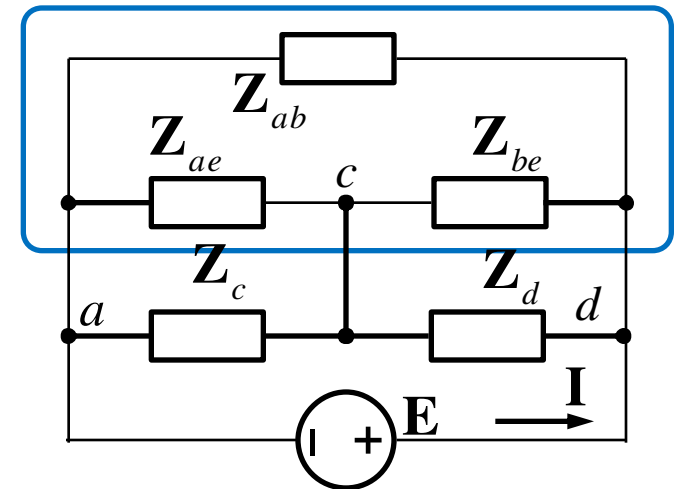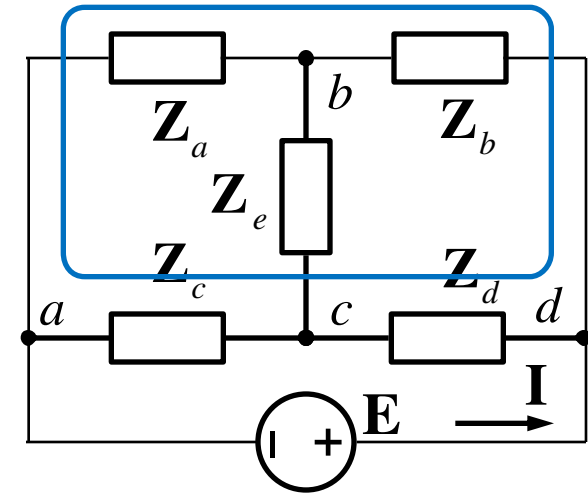
$$I = \frac{E}{Z_t} = \frac{100}{22.46 + j3.18} = \boxed{4.37 - j0.62 \text{ A}}$$




Sinusoidal Steady-State Analysis

1. Sinusoidal Steady-State Analysis
2. Ohm's Law
3. Kirchhoff's Laws
4. Impedance Combinations
- 5. Branch Current Method**
6. Node Voltage Method
7. Mesh Current Method
8. Superposition Theorem
9. Source Transformation
10. Thévenin & Norton Equivalent Circuits
11. Op Amp AC Circuits



Branch Current Method (1)

Ex. 1

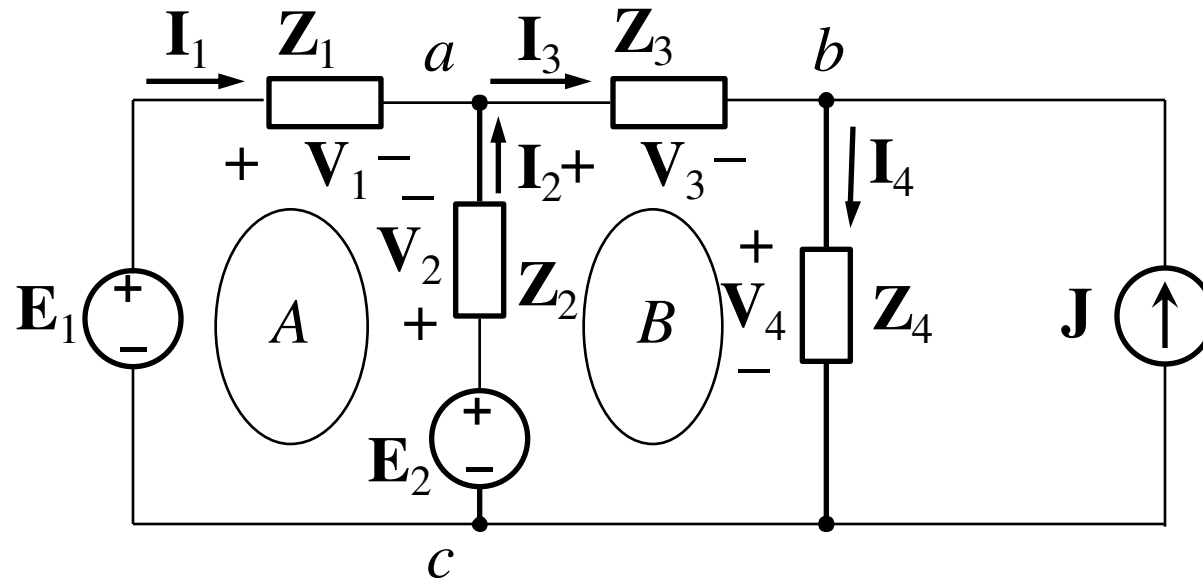


1. Find:
 $n_{KCL} = n - 1$, and
 $n_{KVL} = b - n + 1$
2. Apply KCL at n_{KCL} nodes
3. Apply KVL at n_{KVL} loops
4. Solve simultaneous equations

$$\begin{cases} \mathbf{I}_1 + \mathbf{I}_2 - \mathbf{I}_3 = 0 \\ \mathbf{I}_3 - \mathbf{I}_4 = -\mathbf{J} \\ \mathbf{Z}_1 \mathbf{I}_1 - \mathbf{Z}_2 \mathbf{I}_2 = \mathbf{E}_1 - \mathbf{E}_2 \\ \mathbf{Z}_2 \mathbf{I}_2 + \mathbf{Z}_3 \mathbf{I}_3 + \mathbf{Z}_4 \mathbf{I}_4 = \mathbf{E}_2 \end{cases}$$

Branch Current Method (2)

Ex. 2

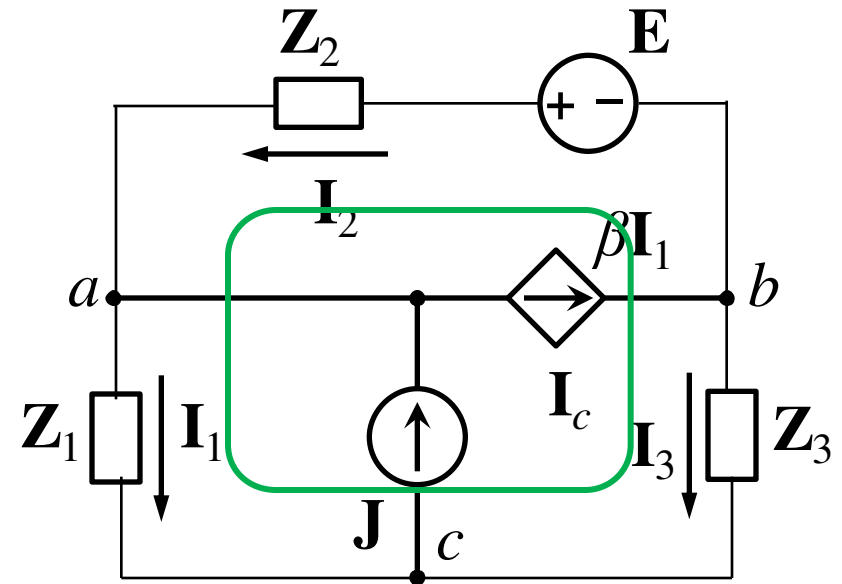
$$\left\{ \begin{array}{l} b : \mathbf{I}_c - \mathbf{I}_2 - \mathbf{I}_3 = 0 \\ c : \mathbf{I}_1 + \mathbf{I}_3 - \mathbf{J} = 0 \\ A : \mathbf{Z}_1 \mathbf{I}_1 - \mathbf{Z}_3 \mathbf{I}_3 + \mathbf{Z}_2 \mathbf{I}_2 - \mathbf{E} = 0 \\ \mathbf{I}_c = \beta \mathbf{I}_1 \end{array} \right.$$



$$\rightarrow \left\{ \begin{array}{l} \beta \mathbf{I}_1 - \mathbf{I}_2 - \mathbf{I}_3 = 0 \\ \mathbf{I}_1 + \mathbf{I}_3 - \mathbf{J} = 0 \\ \mathbf{Z}_1 \mathbf{I}_1 - \mathbf{Z}_3 \mathbf{I}_3 + \mathbf{Z}_2 \mathbf{I}_2 - \mathbf{E} = 0 \end{array} \right.$$

Ex. 3 Branch Current Method (3)

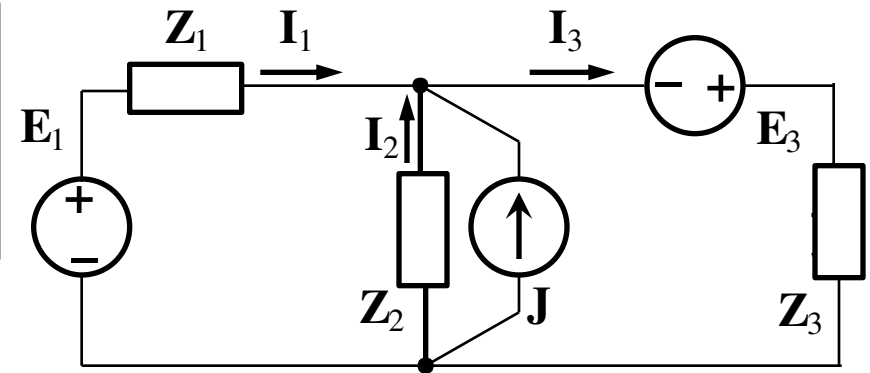$Z_1 = 10\Omega$; $Z_2 = j20\Omega$; $Z_3 = 5 - j10\Omega$;
 $E_1 = 30\text{ V}$; $E_3 = 45\angle 15^\circ\text{ V}$; $J = 2\angle -30^\circ\text{ A}$;
 Find currents?




$$\begin{cases}
 \mathbf{I}_1 + \mathbf{I}_2 - \mathbf{I}_3 + \mathbf{J} = 0 \\
 \mathbf{Z}_1 \mathbf{I}_1 - \mathbf{Z}_2 \mathbf{I}_2 = \mathbf{E}_1 \\
 \mathbf{Z}_2 \mathbf{I}_2 + \mathbf{Z}_3 \mathbf{I}_3 = \mathbf{E}_3
 \end{cases}$$

$$\rightarrow \begin{cases}
 \mathbf{I}_1 + \mathbf{I}_2 - \mathbf{I}_3 = -2\angle -30^\circ \\
 10\mathbf{I}_1 - j20\mathbf{I}_2 = 30 \\
 j20\mathbf{I}_2 + (5 - j10)\mathbf{I}_3 = 45\angle 15^\circ
 \end{cases}$$

$$\mathbf{I}_1 = \frac{\Delta_1}{\Delta}; \quad \mathbf{I}_2 = \frac{\Delta_2}{\Delta}; \quad \mathbf{I}_3 = \frac{\Delta_3}{\Delta}$$

Ex. 3 Branch Current Method (4)

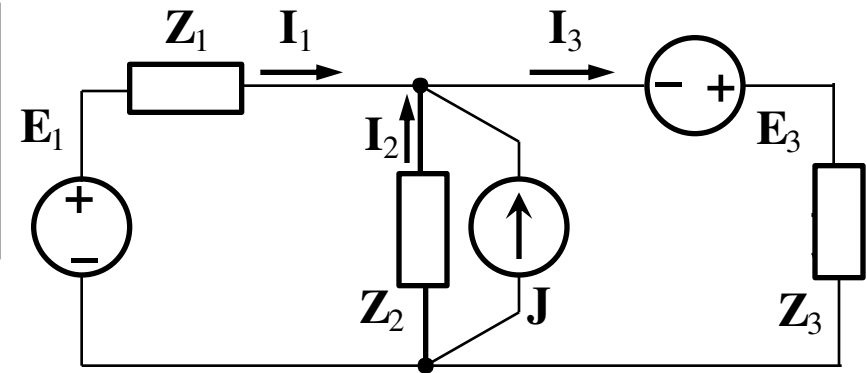$Z_1 = 10\Omega$; $Z_2 = j20\Omega$; $Z_3 = 5 - j10\Omega$;
 $E_1 = 30\text{ V}$; $E_3 = 45\angle 15^\circ\text{ V}$; $J = 2\angle -30^\circ\text{ A}$;
 Find currents?



$$\begin{cases}
 I_1 + I_2 - I_3 = -2\angle -30^\circ \\
 10I_1 - j20I_2 = 30 \\
 j20I_2 + (5 - j10)I_3 = 45\angle 15^\circ
 \end{cases}$$


$$I_1 = \frac{\Delta_1}{\Delta}; \quad I_2 = \frac{\Delta_2}{\Delta}; \quad I_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta = \begin{vmatrix} 1 & 1 & -1 \\ 10 & -j20 & 0 \\ 0 & j20 & 5 - j10 \end{vmatrix} = 1 \begin{vmatrix} -j20 & 0 \\ j20 & 5 - j10 \end{vmatrix} - 10 \begin{vmatrix} 1 & -1 \\ j20 & 5 - j10 \end{vmatrix} + 0 \begin{vmatrix} 1 & -1 \\ -j20 & 0 \end{vmatrix}$$

$$= -250 - j200$$

Ex. 3 Branch Current Method (5)

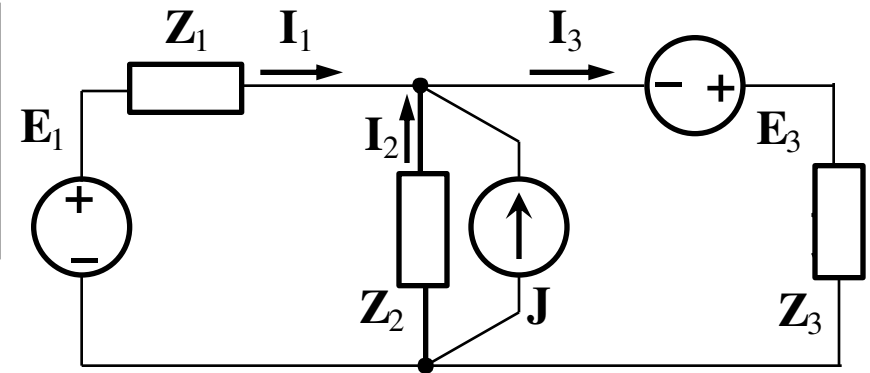$Z_1 = 10\Omega$; $Z_2 = j20\Omega$; $Z_3 = 5 - j10\Omega$;
 $E_1 = 30\text{ V}$; $E_3 = 45\angle 15^\circ\text{ V}$; $J = 2\angle -30^\circ\text{ A}$;
 Find currents?



$$\begin{cases}
 I_1 + I_2 - I_3 = -2\angle -30^\circ \\
 10I_1 - j20I_2 = 30 \\
 j20I_2 + (5 - j10)I_3 = 45\angle 15^\circ
 \end{cases}$$

$$I_1 = \frac{\Delta_1}{\Delta}; \quad I_2 = \frac{\Delta_2}{\Delta}; \quad I_3 = \frac{\Delta_3}{\Delta}$$


$$I_1 = \frac{\begin{vmatrix} -2\angle -30^\circ & 1 & -1 \\ 30 & -j20 & 0 \\ 45\angle 15^\circ & j20 & 5 - j10 \end{vmatrix}}{-250 - j200} = 1.04 + j3.95 = 4.09\angle 75.2^\circ\text{ A}$$

$$\rightarrow i_1 = 4.09 \sin(\omega t + 75.2^\circ)\text{ A}$$

Ex. 3

Branch Current Method (6)

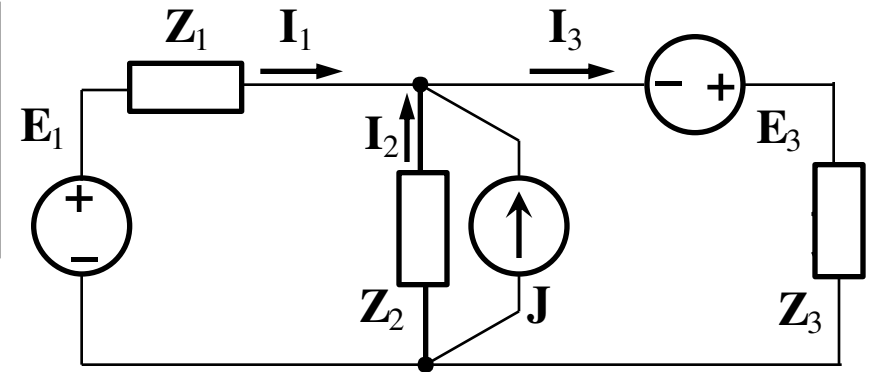$Z_1 = 10\Omega$; $Z_2 = j20\Omega$; $Z_3 = 5 - j10\Omega$;
 $E_1 = 30\text{ V}$; $E_3 = 45\angle 15^\circ\text{ V}$; $J = 2\angle -30^\circ\text{ A}$;
 Find currents?



$$\begin{cases} I_1 + I_2 - I_3 = -2\angle -30^\circ \\ 10I_1 - j20I_2 = 30 \\ j20I_2 + (5 - j10)I_3 = 45\angle 15^\circ \end{cases}$$


$$I_1 = \frac{\Delta_1}{\Delta}; \quad I_2 = \frac{\Delta_2}{\Delta}; \quad I_3 = \frac{\Delta_3}{\Delta}$$

$$I_2 = \frac{\begin{vmatrix} 1 & -2\angle -30^\circ & -1 \\ 10 & 30 & 0 \\ 0 & 45\angle 15^\circ & 5 - j10 \end{vmatrix}}{-250 - j200} = 1.98 + j0.98 = 2.20\angle 26.4^\circ\text{ A}$$

$$\rightarrow i_2 = 2.20 \sin(\omega t + 26.4^\circ)\text{ A}$$

Ex. 3 Branch Current Method (7)

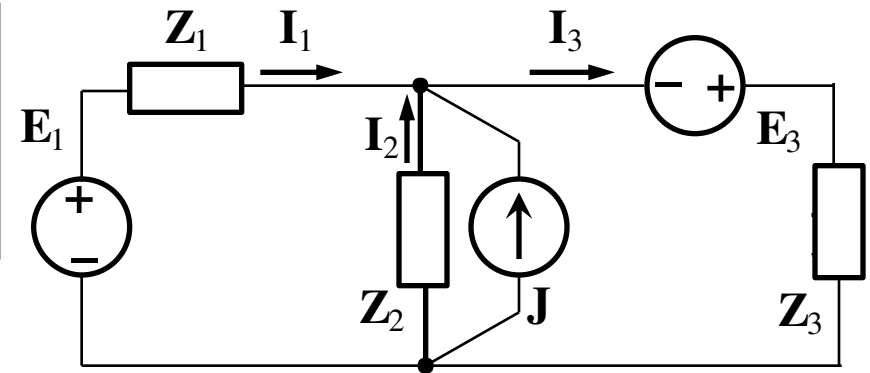$Z_1 = 10\Omega$; $Z_2 = j20\Omega$; $Z_3 = 5 - j10\Omega$;
 $E_1 = 30\text{ V}$; $E_3 = 45\angle 15^\circ\text{ V}$; $J = 2\angle -30^\circ\text{ A}$;
 Find currents?



$$\begin{cases} \mathbf{I}_1 + \mathbf{I}_2 - \mathbf{I}_3 = -2\angle -30^\circ \\ 10\mathbf{I}_1 - j20\mathbf{I}_2 = 30 \\ j20\mathbf{I}_2 + (5 - j10)\mathbf{I}_3 = 45\angle 15^\circ \end{cases}$$

$$\mathbf{I}_1 = \frac{\Delta_1}{\Delta}; \quad \mathbf{I}_2 = \frac{\Delta_2}{\Delta}; \quad \mathbf{I}_3 = \frac{\Delta_3}{\Delta}$$

$$\mathbf{I}_3 = \frac{\begin{vmatrix} 1 & 1 & -2\angle -30^\circ \\ 10 & -j20 & 30 \\ 0 & j20 & 45\angle 15^\circ \end{vmatrix}}{-250 - j200} = 4.75 + j3.93 = 6.16\angle 39.6^\circ\text{ A}$$

$$\rightarrow i_3 = 6.16 \sin(\omega t + 39.6^\circ)\text{ A}$$

Sinusoidal Steady-State Analysis


1. Sinusoidal Steady-State Analysis
2. Ohm's Law
3. Kirchhoff's Laws
4. Impedance Combinations
5. Branch Current Method
- 6. Node Voltage Method**
7. Mesh Current Method
8. Superposition Theorem
9. Source Transformation
10. Thévenin & Norton Equivalent Circuits
11. Op Amp AC Circuits



Node Voltage Method (1)

Ex. 1

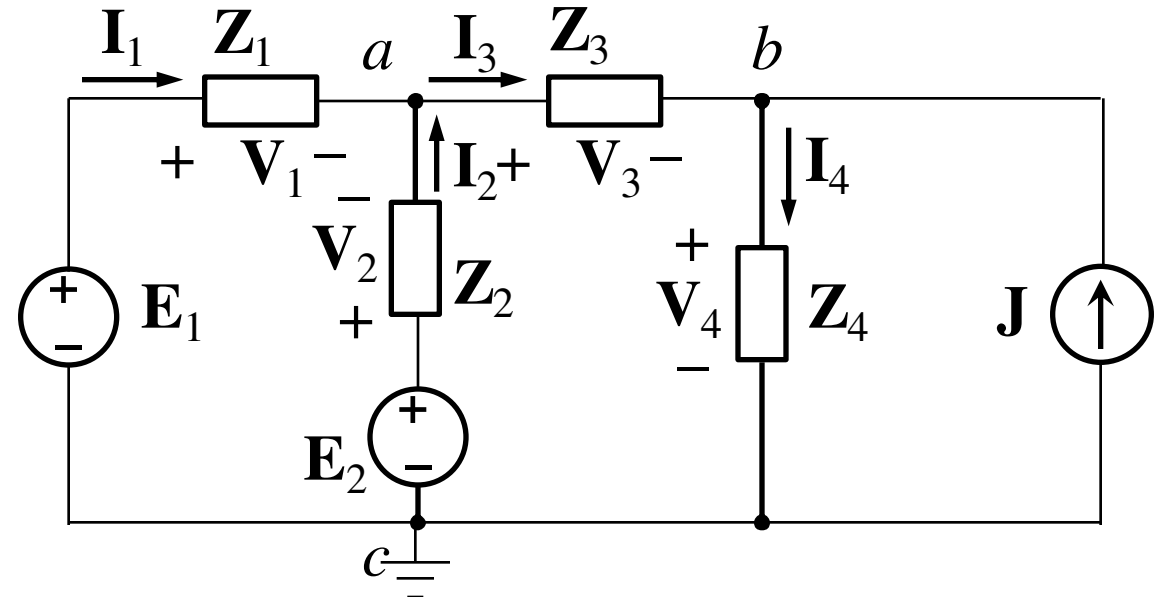1. the reference node
2. the sum of the reciprocals of all impedances connected to each node
3. the negative sum of the reciprocals of the impedances of all branches joining each pair of node
4. current source(s) for each node
5. node voltage equations
6. node voltages
7. branch currents




$$\begin{cases} \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \right) V_a - \left(\frac{1}{Z_3} \right) V_b = \frac{E_1}{Z_1} + \frac{E_2}{Z_2} \\ - \left(\frac{1}{Z_3} \right) V_a + \left(\frac{1}{Z_3} + \frac{1}{Z_4} \right) V_b = J \end{cases}$$

Node Voltage Method (2)

$$\left\{ \begin{array}{l} \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) V_a - \frac{1}{Z_2} V_b = J - I_c + \frac{E}{Z_2} \\ -\frac{1}{Z_2} V_a + \left(\frac{1}{Z_2} + \frac{1}{Z_3} \right) V_b = I_c - \frac{E}{Z_2} \end{array} \right.$$

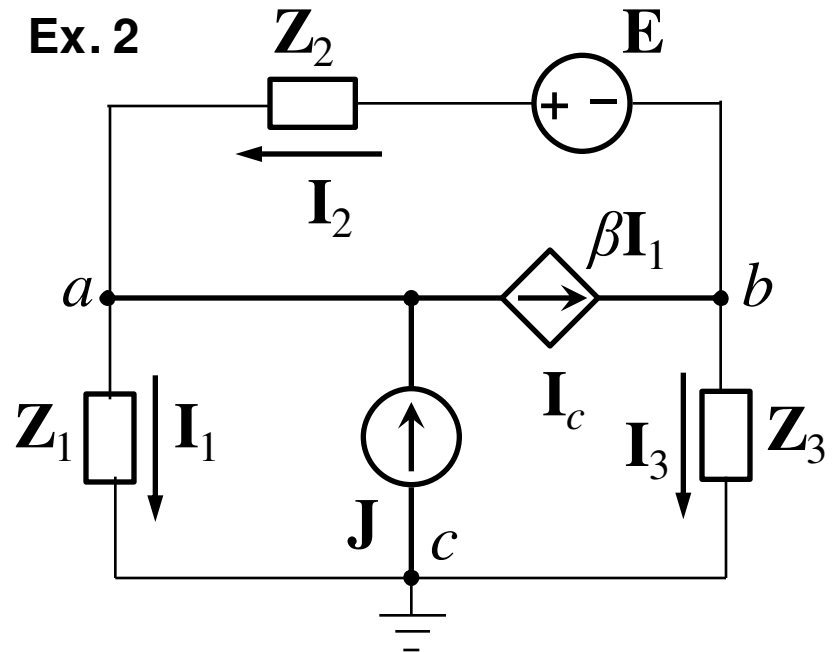
$$I_c = \beta I_1 = \beta \frac{V_a}{Z_1}$$



$$\rightarrow \left\{ \begin{array}{l} \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \beta \frac{1}{Z_1} \right) V_a - \frac{1}{Z_2} V_b = J + \frac{E}{Z_2} \\ -\left(\frac{1}{Z_2} + \beta \frac{1}{Z_1} \right) V_a + \left(\frac{1}{Z_2} + \frac{1}{Z_3} \right) V_b = -\frac{E}{Z_2} \end{array} \right.$$

Ex. 3 Node Voltage Method (3)

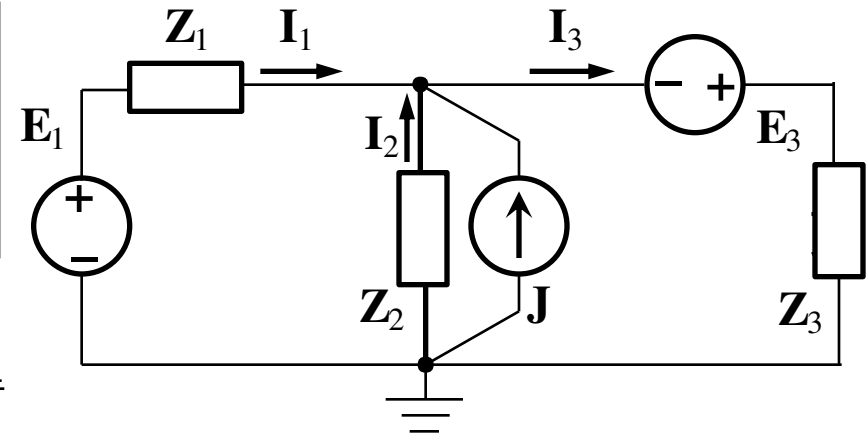$Z_1 = 10\Omega$; $Z_2 = j20\Omega$; $Z_3 = 5 - j10\Omega$;
 $E_1 = 30\text{ V}$; $E_3 = 45\angle 15^\circ\text{ V}$; $J = 2\angle -30^\circ\text{ A}$;
 Find currents?



$$\left(\frac{1}{10} + \frac{1}{j20} + \frac{1}{5 - j10} \right) \mathbf{V}_a = \frac{30}{10} + 2\angle -30^\circ - \frac{45\angle 15^\circ}{5 - j10}$$

$$\rightarrow \mathbf{V}_a = 19.57 - j39.50\text{ V}$$

$$\rightarrow \begin{cases} \mathbf{I}_1 = \frac{30 - (19.57 - j39.50)}{10} = 1.04 + j3.95 = 4.09\angle 75.2^\circ\text{ A} \\ \mathbf{I}_2 = \frac{-(19.57 - j39.50)}{j20} = 1.98 + j0.98 = 2.20\angle 26.4^\circ\text{ A} \\ \mathbf{I}_3 = \frac{45\angle 15^\circ + (19.57 - j39.50)}{5 - j10} = 4.75 + j3.93 = 6.16\angle 39.6^\circ\text{ A} \end{cases}$$

$$\rightarrow \begin{cases} i_1 = 4.09 \sin(\omega t + 75.2^\circ)\text{ A} \\ i_2 = 2.20 \sin(\omega t + 26.4^\circ)\text{ A} \\ i_3 = 6.16 \sin(\omega t + 39.6^\circ)\text{ A} \end{cases}$$


Sinusoidal Steady-State Analysis

1. Sinusoidal Steady-State Analysis
2. Ohm's Law
3. Kirchhoff's Laws
4. Impedance Combinations
5. Branch Current Method
6. Node Voltage Method
- 7. Mesh Current Method**
8. Superposition Theorem
9. Source Transformation
10. Thévenin & Norton Equivalent Circuits
11. Op Amp AC Circuits



Mesh Current Method (1)


Ex. 1

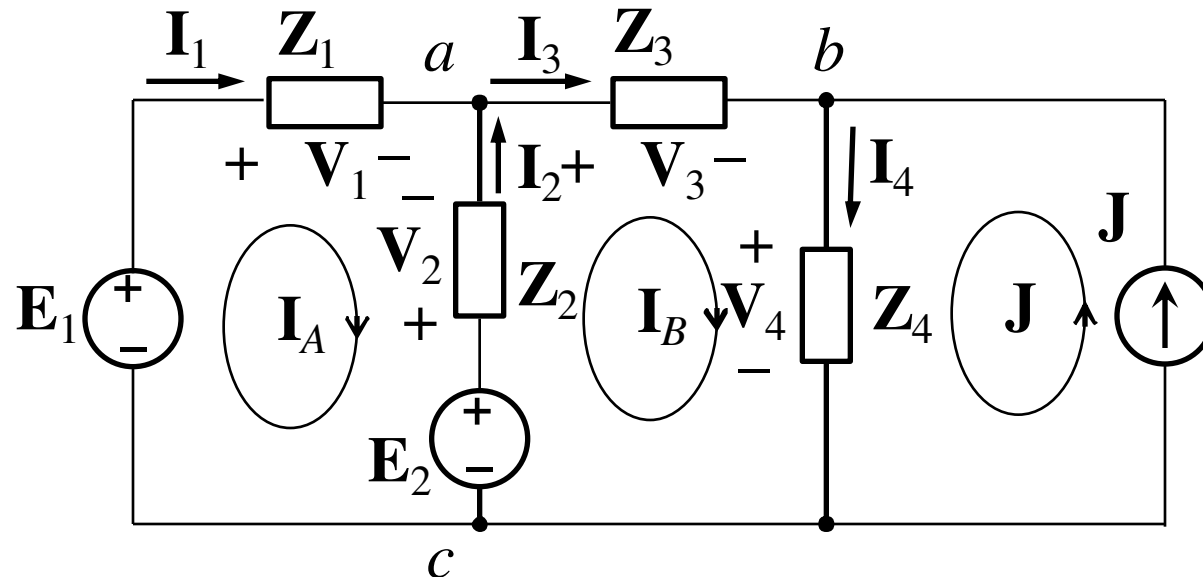

$$\left\{ \begin{array}{l} \mathbf{Z}_1 \mathbf{I}_1 - \mathbf{Z}_2 \mathbf{I}_2 = \mathbf{E}_1 - \mathbf{E}_2 \\ \mathbf{Z}_2 \mathbf{I}_2 + \mathbf{Z}_3 \mathbf{I}_3 + \mathbf{Z}_4 \mathbf{I}_4 = \mathbf{E}_2 \\ \mathbf{I}_1 = \mathbf{I}_A, \mathbf{I}_2 = \mathbf{I}_B - \mathbf{I}_A, \mathbf{I}_3 = \mathbf{I}_B, \mathbf{I}_4 = \mathbf{I}_B + \mathbf{J} \end{array} \right\} \rightarrow \left\{ \begin{array}{l} \mathbf{Z}_1 \mathbf{I}_A - \mathbf{Z}_2 (\mathbf{I}_B - \mathbf{I}_A) = \mathbf{E}_1 - \mathbf{E}_2 \\ \mathbf{Z}_2 (\mathbf{I}_B - \mathbf{I}_A) + \mathbf{Z}_3 \mathbf{I}_B + \mathbf{Z}_4 (\mathbf{I}_B + \mathbf{J}) = \mathbf{E}_2 \end{array} \right.$$

Mesh Current Method (2)
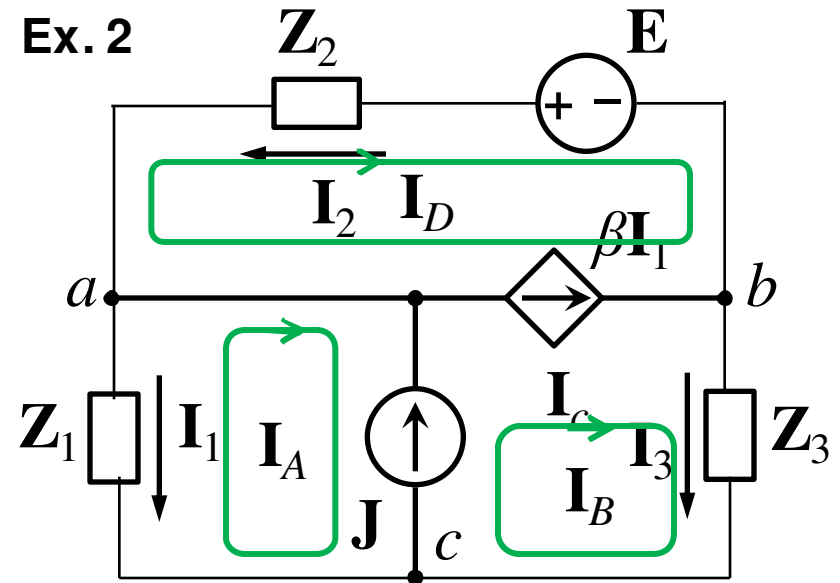
$$\left. \begin{aligned} \mathbf{Z}_1 \mathbf{I}_A + \mathbf{Z}_2 \mathbf{I}_D + \mathbf{Z}_3 \mathbf{I}_B + \mathbf{E} &= 0 \\ \mathbf{I}_B - \mathbf{I}_A &= \mathbf{J} \\ \mathbf{I}_B - \mathbf{I}_D &= \mathbf{I}_c \\ \mathbf{I}_c &= \beta \mathbf{I}_1 \end{aligned} \right\}$$




$$\left. \begin{aligned} \rightarrow (\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3) \mathbf{I}_A &= -\mathbf{E} - (\mathbf{Z}_2 + \mathbf{Z}_3) \mathbf{J} + \mathbf{Z}_2 \beta \mathbf{I}_1 \\ \mathbf{I}_A &= -\mathbf{I}_1 \end{aligned} \right\}$$

$$\rightarrow (\mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3 + \beta \mathbf{Z}_2) \mathbf{I}_A = \mathbf{E} + (\mathbf{Z}_2 + \mathbf{Z}_3) \mathbf{J}$$

Ex. 3 Mesh Current Method (3)

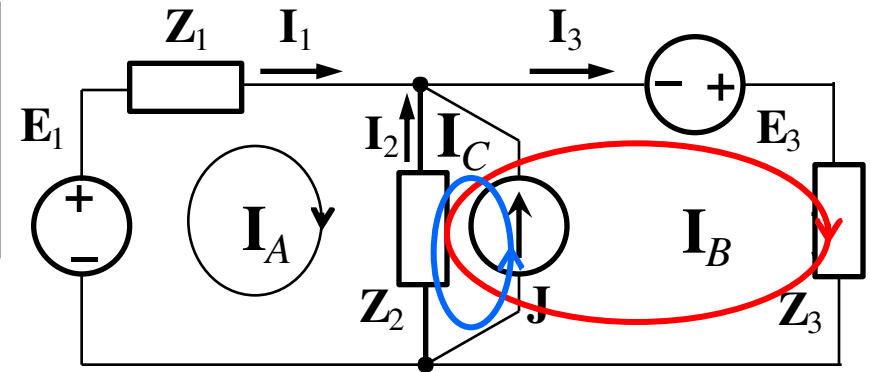$Z_1 = 10\Omega$; $Z_2 = j20\Omega$; $Z_3 = 5 - j10\Omega$;
 $E_1 = 30\text{ V}$; $E_3 = 45\angle 15^\circ\text{ V}$; $J = 2\angle -30^\circ\text{ A}$;
 Find currents?



$$\begin{cases} 10\mathbf{I}_A + j20(\mathbf{I}_A - \mathbf{I}_B + 2\angle -30^\circ) = 30 \\ j20(\mathbf{I}_B - \mathbf{I}_A - 2\angle -30^\circ) + (5 - j10)\mathbf{I}_B = 45\angle 15^\circ \end{cases}$$

$$\rightarrow \begin{cases} (10 + j20)\mathbf{I}_A - j20\mathbf{I}_B = 30 - j20 \times 2\angle -30^\circ \\ -j20\mathbf{I}_A + (5 + j20)\mathbf{I}_B = j20 \times 2\angle -30^\circ + 45\angle 15^\circ \end{cases} \rightarrow \begin{cases} \mathbf{I}_A = 1.04 + j3.95\text{ A} \\ \mathbf{I}_B = 4.75 + j3.93\text{ A} \end{cases}$$


$$\rightarrow \begin{cases} \mathbf{I}_1 = \mathbf{I}_A = 1.04 + j3.95 = 4.09\angle 75.2^\circ\text{ A} \\ \mathbf{I}_2 = -\mathbf{I}_A + \mathbf{I}_B - J = 2.20\angle 26.4^\circ\text{ A} \\ \mathbf{I}_3 = \mathbf{I}_B = 4.75 + j3.93 = 6.16\angle 39.6^\circ\text{ A} \end{cases} \rightarrow \begin{cases} i_1 = 4.09 \sin(\omega t + 75.2^\circ)\text{ A} \\ i_2 = 2.20 \sin(\omega t + 26.4^\circ)\text{ A} \\ i_3 = 6.16 \sin(\omega t + 39.6^\circ)\text{ A} \end{cases}$$

Sinusoidal Steady-State Analysis

1. Sinusoidal Steady-State Analysis
2. Ohm's Law
3. Kirchhoff's Laws
4. Impedance Combinations
5. Branch Current Method
6. Node Voltage Method
7. Mesh Current Method
- 8. Superposition Theorem**
9. Source Transformation
10. Thévenin & Norton Equivalent Circuits
11. Op Amp AC Circuits




Superposition Theorem (1)

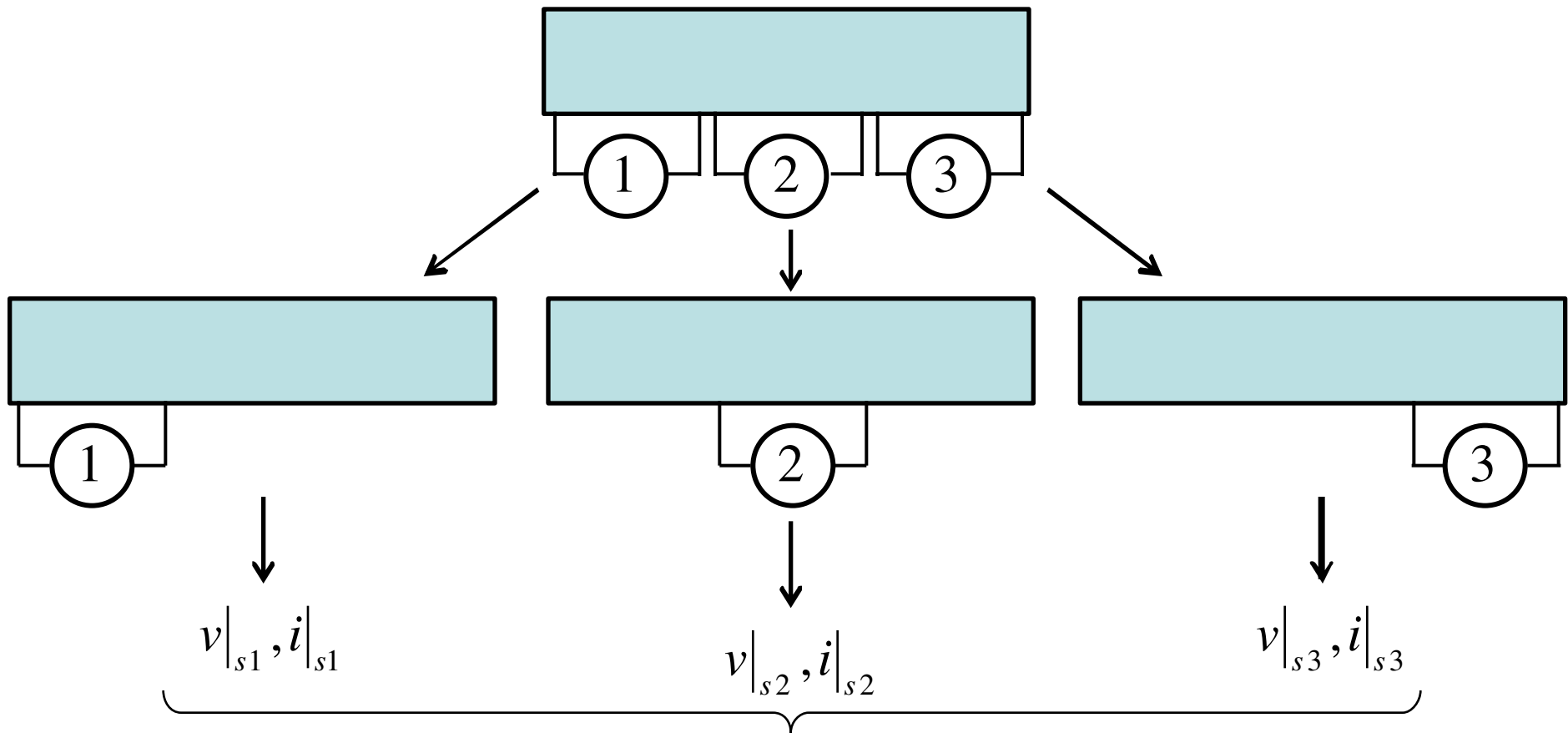

$$v = v|_{s1} + v|_{s2} + v|_{s3}; \quad i = i|_{s1} + i|_{s2} + i|_{s3}$$





Superposition Theorem (2)

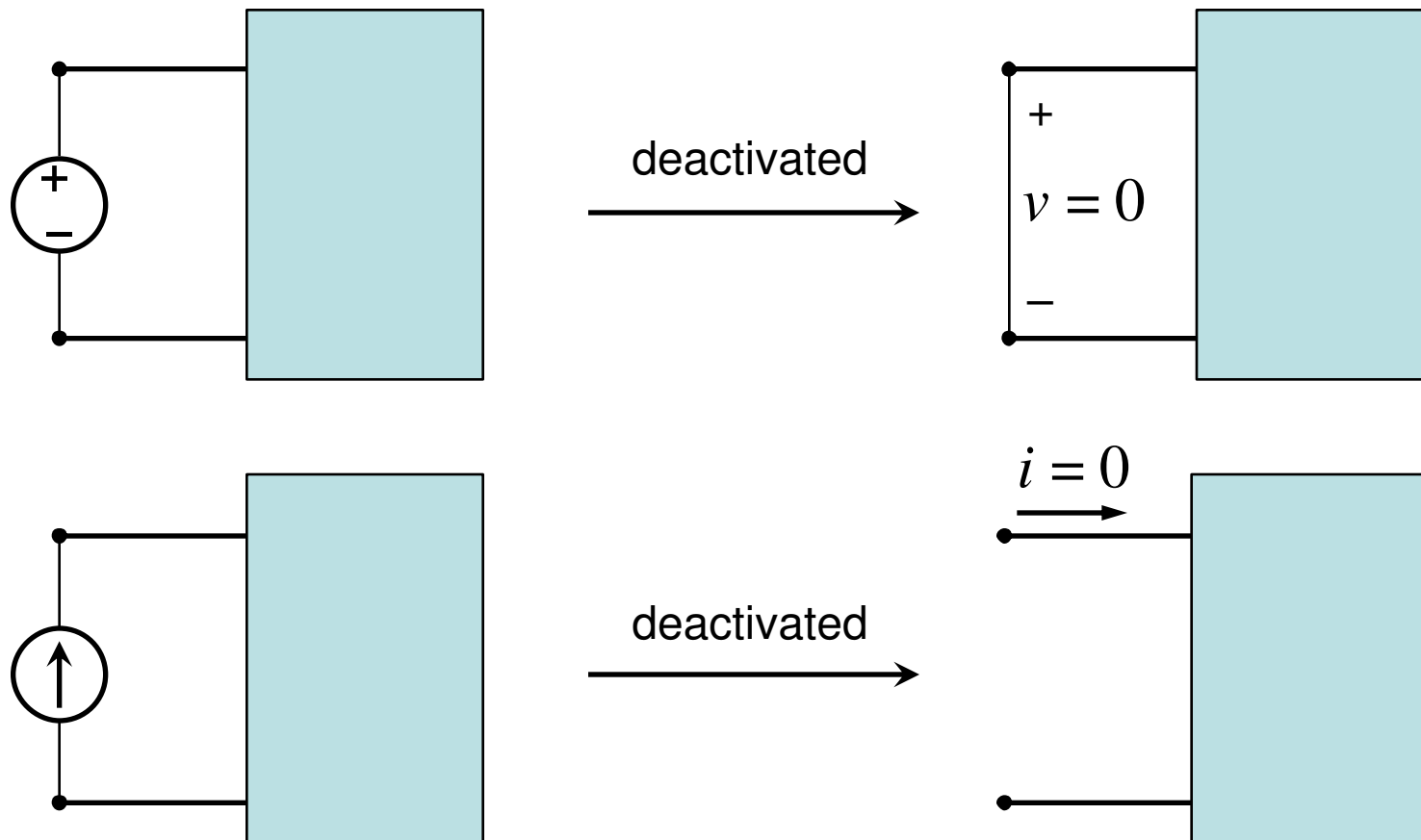

Superposition Theorem (3)

Ex. 1

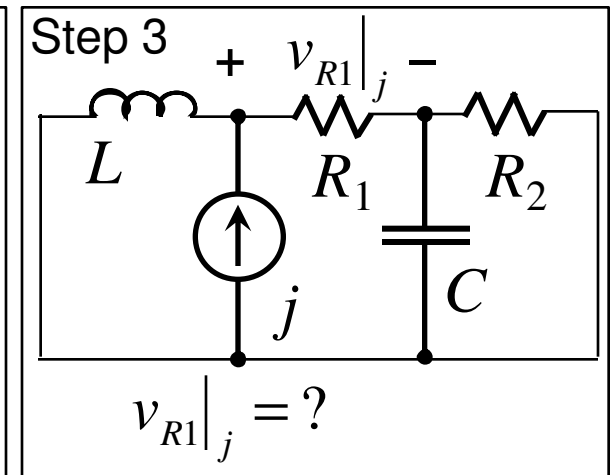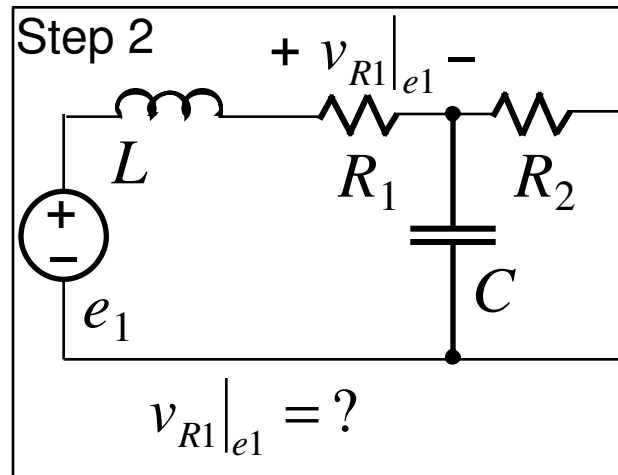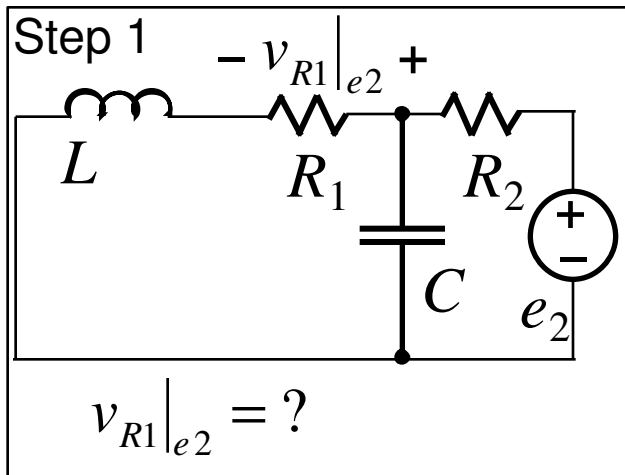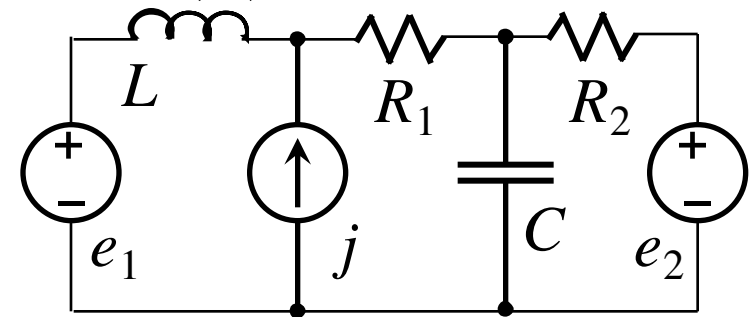$e_1 = 10\sin 10t$ V; $j = 4\sin(50t + 30^\circ)$ V; $e_2 = 6$ V (DC); $L = 1$ H; $R_1 = 1 \Omega$; $R_2 = 5 \Omega$; $C = 0.01$ F; $v_{R1} = ?$





Step 4: $v_{R1} = -v_{R1}|_{e2} + v_{R1}|_{e1} + v_{R1}|_j$

Superposition Theorem (4)

Ex. 1

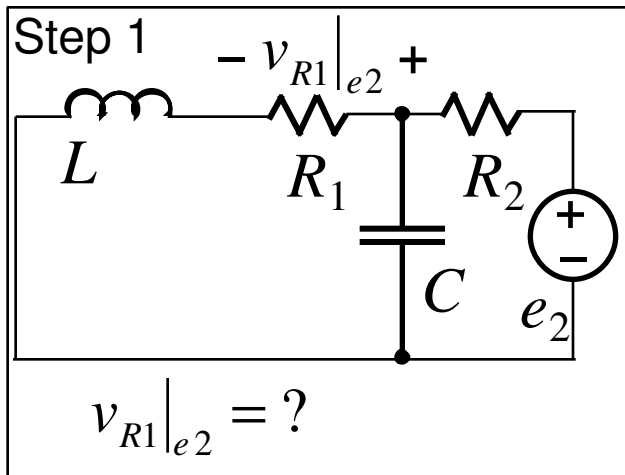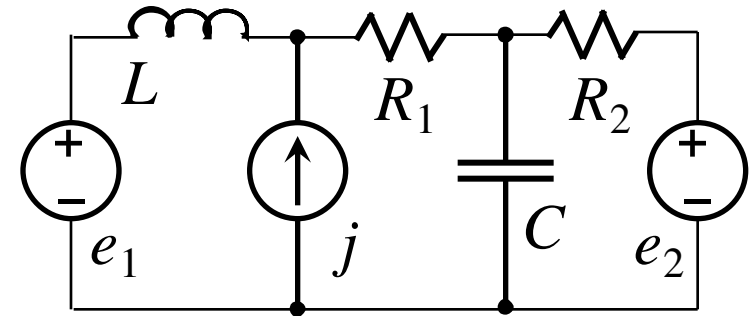$e_1 = 10\sin 10t$ V; $j = 4\sin(50t + 30^\circ)$ V; $e_2 = 6$ V (DC); $L = 1$ H; $R_1 = 1 \Omega$; $R_2 = 5 \Omega$; $C = 0.01$ F; $v_{R1} = ?$






$$i|_{e2} = \frac{6}{1+5} = 1\text{A}$$

$$v_{R1}|_{e2} = 1 \times 1 = \boxed{1\text{V}}$$

Superposition Theorem (5)

Ex. 1

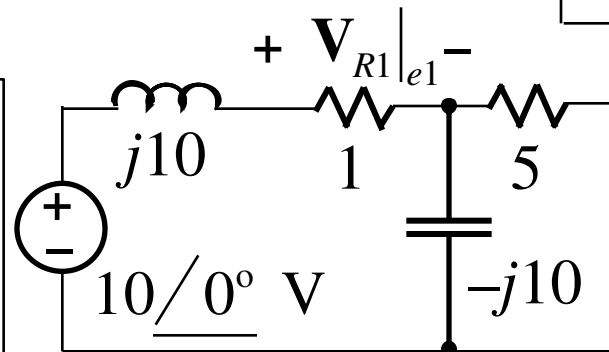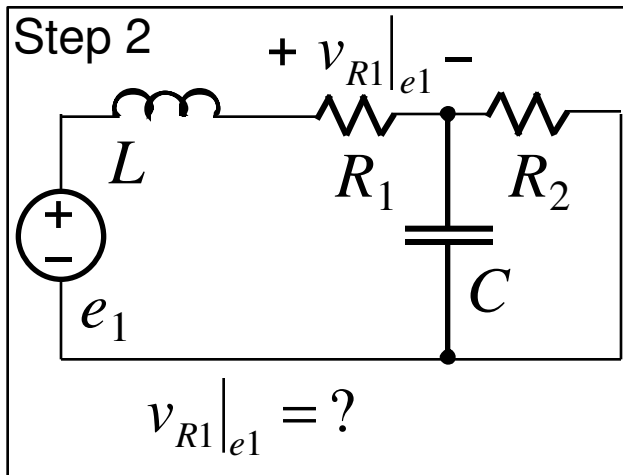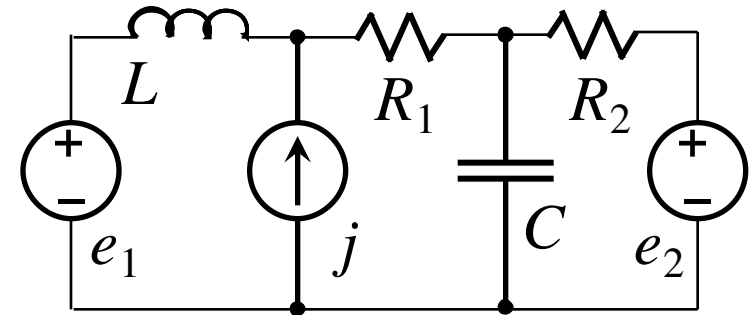$e_1 = 10\sin 10t$ V; $j = 4\sin(50t + 30^\circ)$ V; $e_2 = 6$ V (DC); $L = 1$ H; $R_1 = 1 \Omega$; $R_2 = 5 \Omega$; $C = 0.01$ F; $v_{R1} = ?$



$$\mathbf{Z} = j10 + 1 + \frac{5(-j10)}{5 - j10}$$

$$= 5 + j8 = 9.43 / 58^\circ \Omega$$

$$\mathbf{I}_{R1}|_{e1} = \frac{\mathbf{E}_1}{\mathbf{Z}} = \frac{10 / 0}{9.43 / 58^\circ} = 1.06 / -58^\circ \text{ A}$$





$$\mathbf{V}_{R1}|_{e1} = R_1 \mathbf{I}_{R1}|_{e1} = 1 \times 1.06 / -58^\circ = 1.06 / -58^\circ \text{ V}$$

$$\rightarrow v_{R2}|_{e1} = 1.06 \sin(10t - 58^\circ) \text{ V}$$

Superposition Theorem (6)

Ex. 1

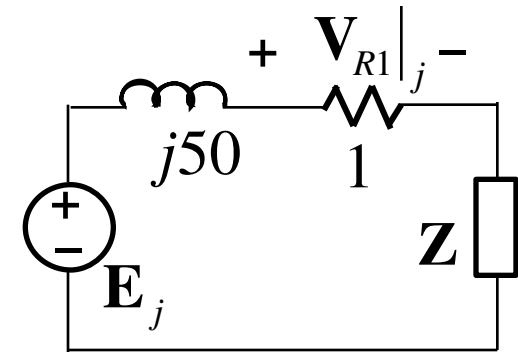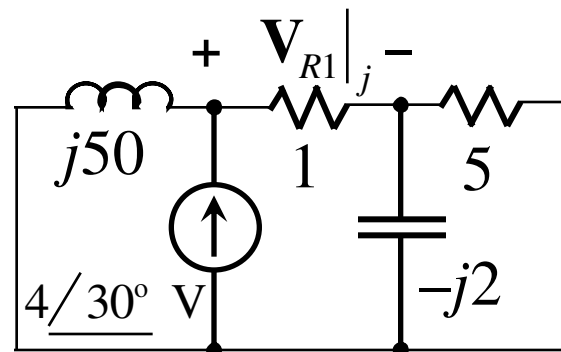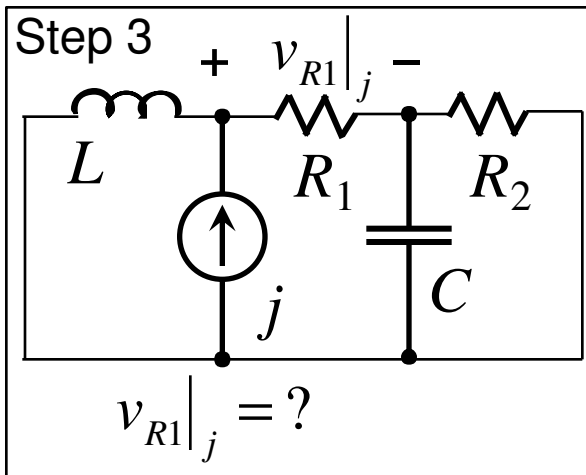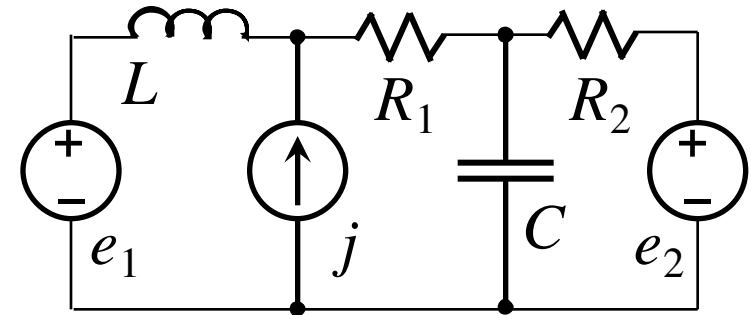$e_1 = 10\sin 10t$ V; $j = 4\sin(50t + 30^\circ)$ V; $e_2 = 6$ V (DC); $L = 1$ H; $R_1 = 1 \Omega$; $R_2 = 5 \Omega$; $C = 0.01$ F; $v_{R1} = ?$



$$\mathbf{I}_j = \frac{200/\underline{120^\circ}}{j50 + 1 + 0.69 - j1.72} = 4.14/\underline{32^\circ} \text{ A}$$

$$\mathbf{E}_j = (j50)(4/\underline{30^\circ}) = 200/\underline{120^\circ} \text{ V}$$

$$\mathbf{V}_{R1}|_j = 1 \times 4.14/\underline{32^\circ} = 4.14/\underline{32^\circ} \text{ V}$$





$$\mathbf{Z} = \frac{5(-j2)}{5 - j2} = 0.69 - j1.72 \Omega$$

$$\rightarrow v_{R1}|_j = \boxed{4.14 \sin(50t + 32^\circ) \text{ V}}$$

Ex. 1

Superposition Theorem (7)

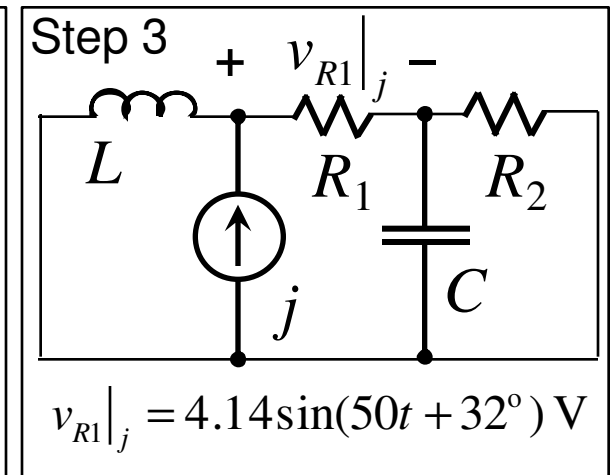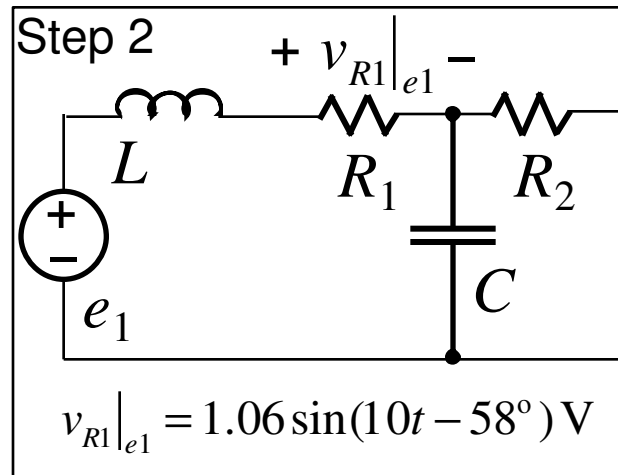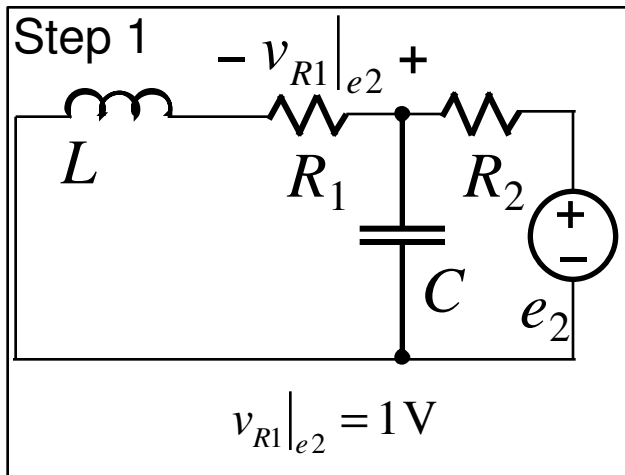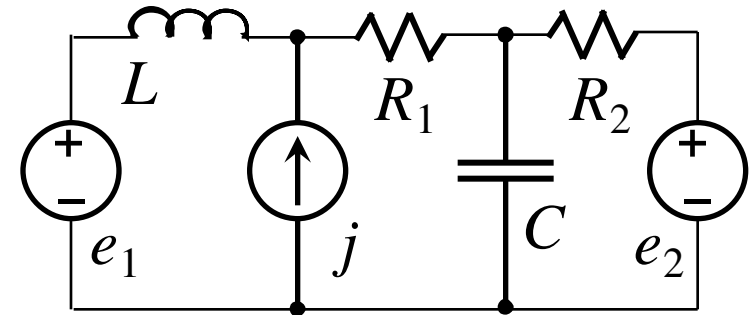$e_1 = 10\sin 10t$ V; $j = 4\sin(50t + 30^\circ)$ V; $e_2 = 6$ V
 (DC); $L = 1$ H; $R_1 = 1 \Omega$; $R_2 = 5 \Omega$; $C = 0.01$ F;
 $v_{R1} = ?$



$$v_{R1} = -v_{R1}|_{e2} + v_{R1}|_{e1} + v_{R1}|_j = -1 + 1.06 \sin(10t - 58^\circ) + 4.14 \sin(50t + 32^\circ) \text{ V}$$

Superposition Theorem (8)

$$v_{R1} = -v_{R1}|_{e2} + v_{R1}|_{e1} + v_{R1}|_j = \boxed{-1 + 1.06 \sin(10t - 58^\circ) + 4.14 \sin(50t + 32^\circ) \text{ V}}$$

$$v_{R1}|_{e2} = 1 \text{ V}$$

$$\mathbf{V}_{R1}|_{e1} = 1.06 \angle -58^\circ \text{ V}$$

$$\mathbf{V}_{R1}|_j = 4.14 \angle 32^\circ \text{ V}$$


$$\begin{aligned} \mathbf{V}_{R1} &= -1 + 1.06 \angle -58^\circ + 4.14 \angle 32^\circ \\ &= -1 + (0.56 - j0.90) + (3.51 + j2.19) \\ &= 3.07 + j1.29 = 3.33 \angle 22.8^\circ \text{ V} \end{aligned}$$

$$\rightarrow v_{R1} = 3.33 \sin(? + 22.8^\circ) \text{ V}$$


Superposition Theorem (9)

Ex. 2

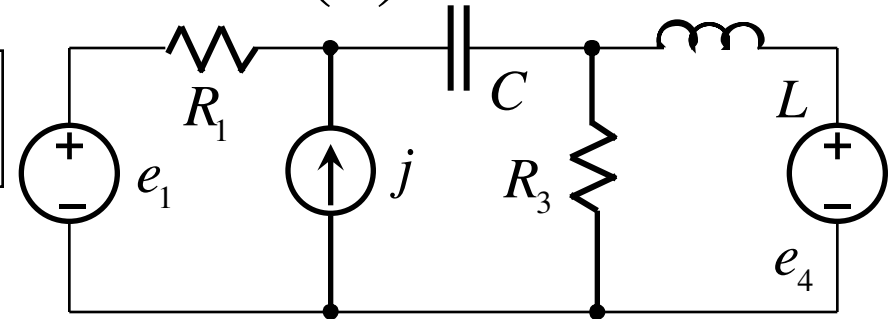
$e_1 = 45\text{V (DC)}$; $e_4 = 60\text{V (DC)}$; $j = 10\sin(100t)\text{ A}$;
 $R_1 = 5\Omega$; $R_3 = 10\Omega$; $C = 2\text{mF}$; $L = 0.1\text{H}$; $v_C = ?$



Step 1

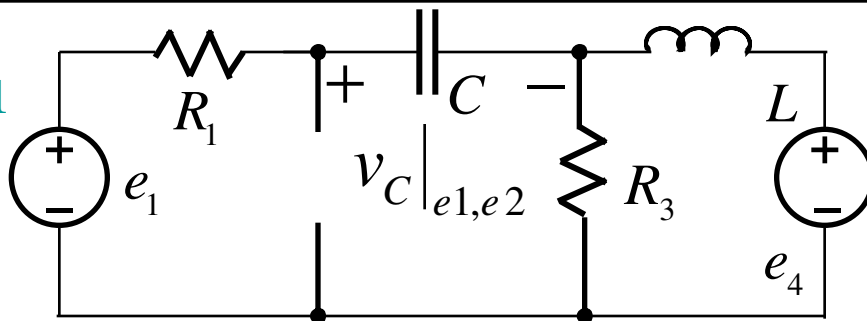

Step 2

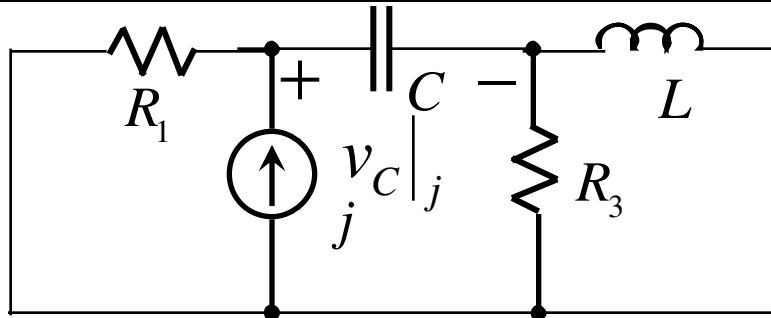



Step 3

$$v_C = v_C|_{e1,e2} + v_C|_j$$

Superposition Theorem (10)

Ex. 2

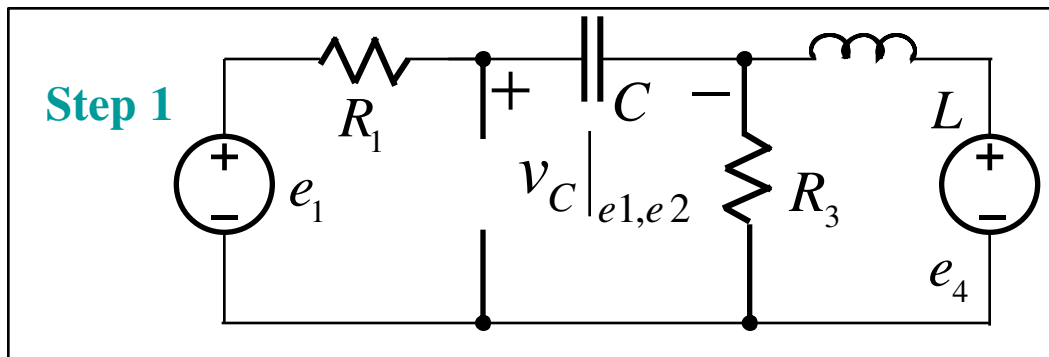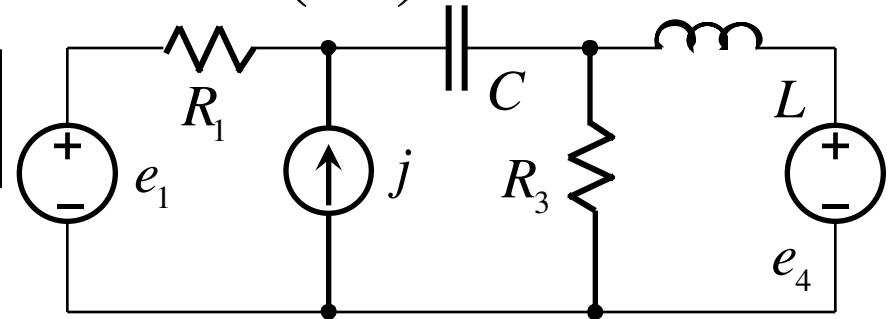$e_1 = 45\text{V}$ (DC); $e_4 = 60\text{V}$ (DC); $j = 10\sin(100t)$ A;
 $R_1 = 5\Omega$; $R_3 = 10\Omega$; $C = 2\text{mF}$; $L = 0.1\text{H}$; $v_C = ?$




$$v_C|_{e1,e2} = e_1 - e_4 = 45 - 60 = -15 \text{ V}$$

Superposition Theorem (11)

Ex. 2

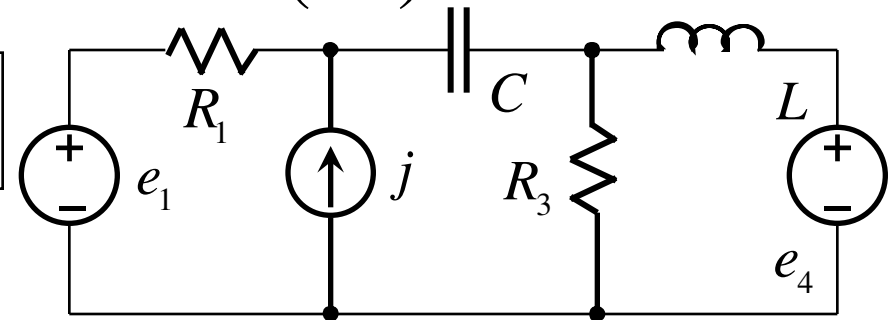
$e_1 = 45\text{V}$ (DC); $e_4 = 60\text{V}$ (DC); $j = 10\sin(100t)$ A;
 $R_1 = 5\Omega$; $R_3 = 10\Omega$; $C = 2\text{mF}$; $L = 0.1\text{H}$; $v_C = ?$



$$V_C|_j = \frac{R_1 \mathbf{J}}{R_1 + \frac{1}{j\omega C} + \frac{R_3(j\omega L)}{R_3 + j\omega L}} \times \frac{1}{j\omega C} = \frac{5 \times 10}{5 + \frac{1}{j100 \times 0.002} + \frac{10(j100 \times 0.1)}{10 + j100 \times 0.1}} \times \frac{1}{j100 \times 0.002}$$

$$= -j25.00 = 25.00 \angle -90^\circ \text{ V}$$


Step 2

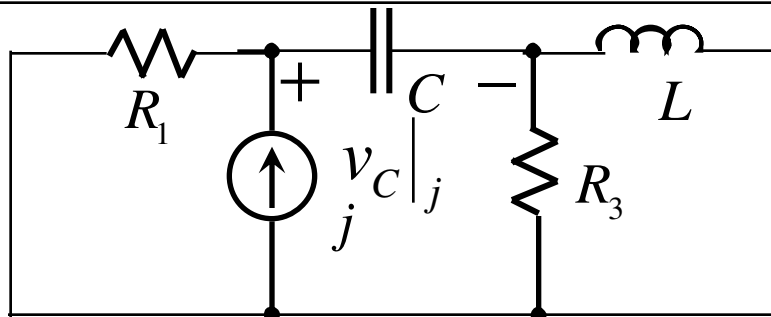



$$\rightarrow v_C|_j = 25\sin(100t - 90^\circ) \text{ V}$$

Ex. 2 Superposition Theorem (12)

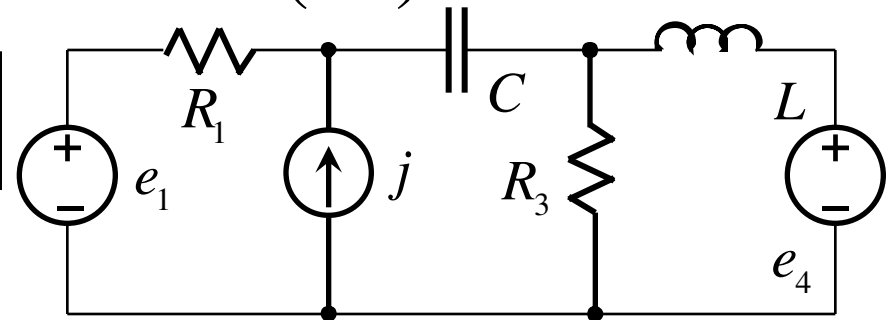$e_1 = 45\text{V (DC)}$; $e_4 = 60\text{V (DC)}$; $j = 10\sin(100t)\text{ A}$;
 $R_1 = 5\Omega$; $R_3 = 10\Omega$; $C = 2\text{mF}$; $L = 0.1\text{H}$; $v_C = ?$



$$v_C|_{e1,e2} = -15\text{ V}$$

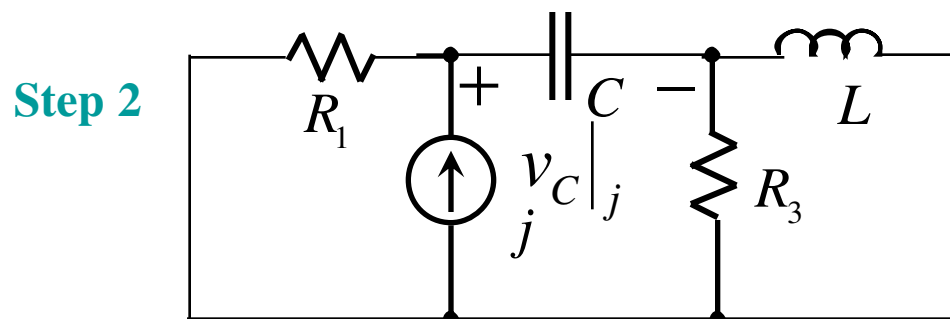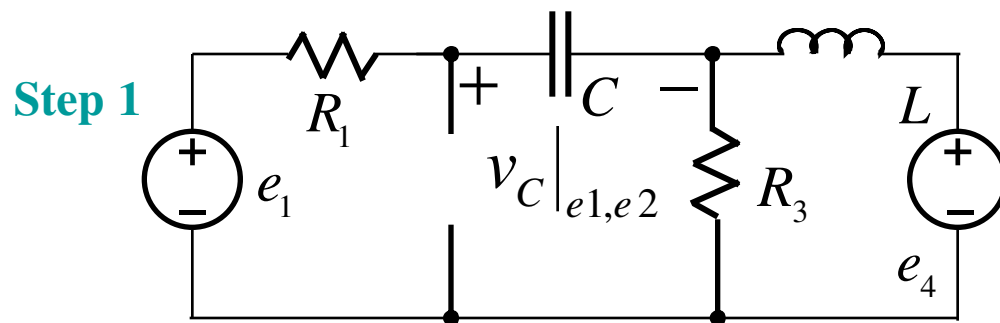

$$v_C|_j = 25\sin(100t - 90^\circ)\text{ V}$$

Step 3



$$v_C = v_C|_{e1,e2} + v_C|_j$$

$$= -15 + 25\sin(100t - 90^\circ)\text{ V}$$




Ex. 3 Superposition Theorem (13)

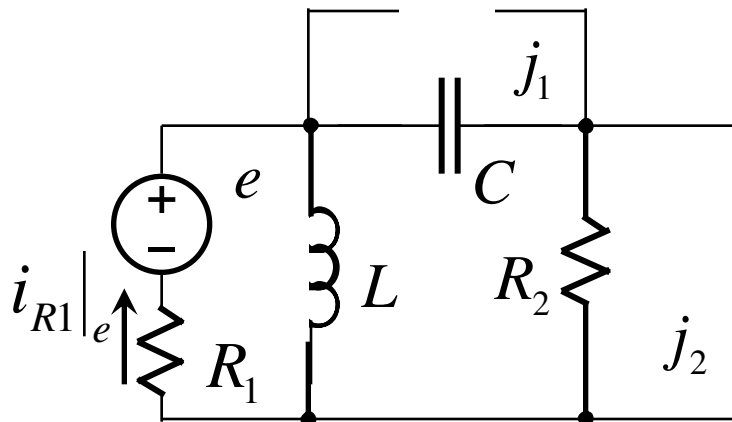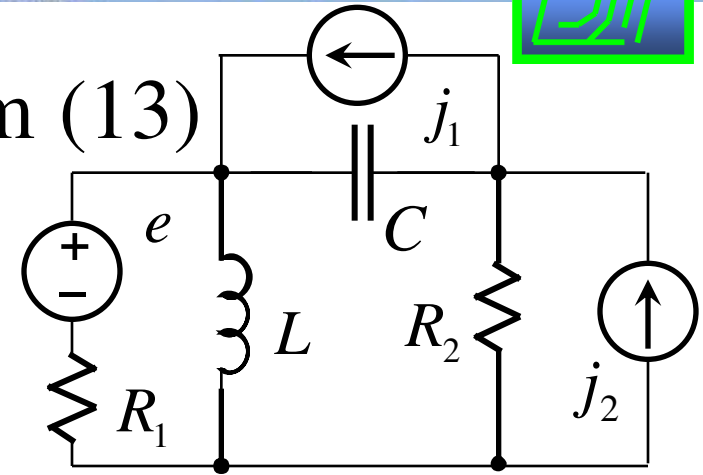$e = 45\text{V (DC)}$; $j_1 = 6\sin(100t + 15^\circ)\text{ A}$; $j_2 = 10\sin(100t)\text{ A}$;
 $R_1 = 5\Omega$; $R_2 = 10\Omega$; $C = 2\text{mF}$; $L = 0.1\text{H}$; $i_{R1} = ?$



$$i_{R1}|_e = \frac{e}{R_1} = \frac{45}{5} = 9\text{ A}$$

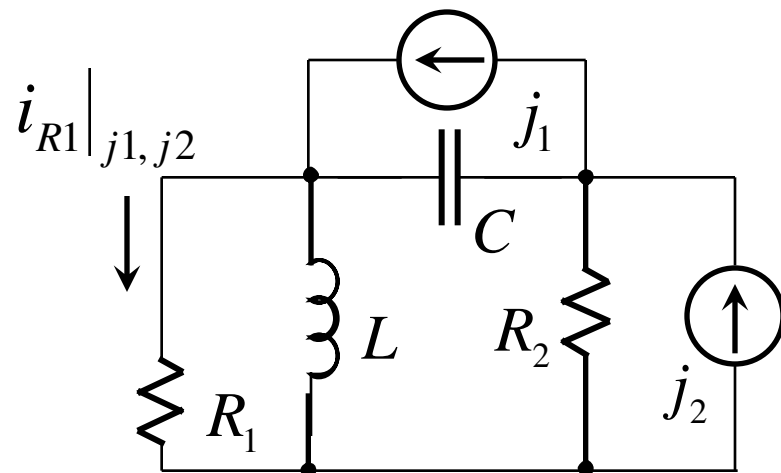

$$\begin{aligned} \mathbf{I}_{R1}|_{j1, j2} &= \frac{\frac{1}{j\omega C} \mathbf{J}_1 + R_2 \mathbf{J}_2}{R_2 + \frac{1}{j\omega C} + \frac{R_1(j\omega L)}{R_1 + j\omega L}} \times \frac{j\omega L}{R_1 + j\omega L} \\ &= 6.39 + j2.79 = 6.97 \angle 23.6^\circ \text{ A} \end{aligned}$$


$$\rightarrow i_{R1} = -9 + 6.97 \sin(100t + 23.6^\circ) \text{ A}$$

Sinusoidal Steady-State Analysis

1. Sinusoidal Steady-State Analysis
2. Ohm's Law
3. Kirchhoff's Laws
4. Impedance Combinations
5. Branch Current Method
6. Node Voltage Method
7. Mesh Current Method
8. Superposition Theorem
- 9. Source Transformation**
10. Thévenin & Norton Equivalent Circuits
11. Op Amp AC Circuits



Source Transformation (1)

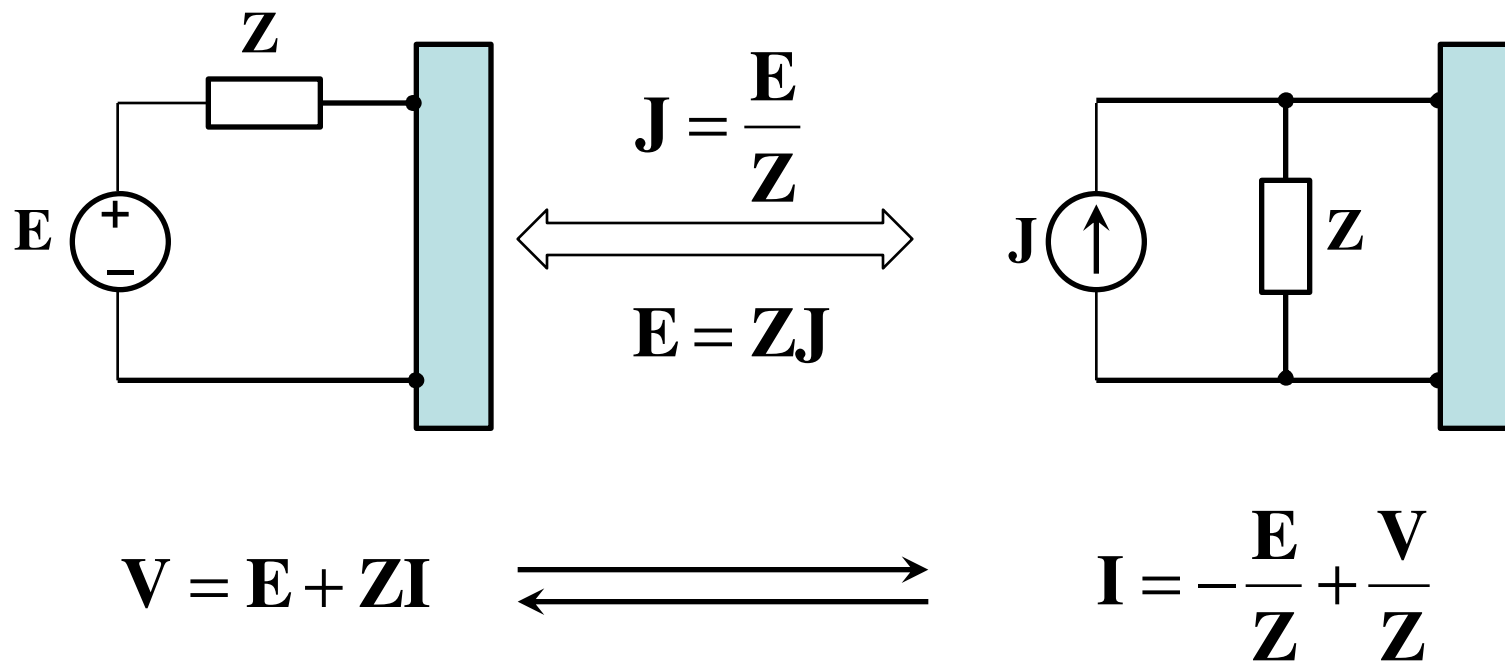

Source Transformation (2)



Ex. 1

$$\mathbf{E} = 20 \angle -45^\circ \text{ V}; \mathbf{J} = 5 \angle 60^\circ \text{ A};$$

$$\mathbf{Z}_1 = 12 \Omega; \mathbf{Z}_2 = j10 \Omega; \mathbf{Z}_3 = -j16 \Omega;$$

Find the current of \mathbf{Z}_2 ?
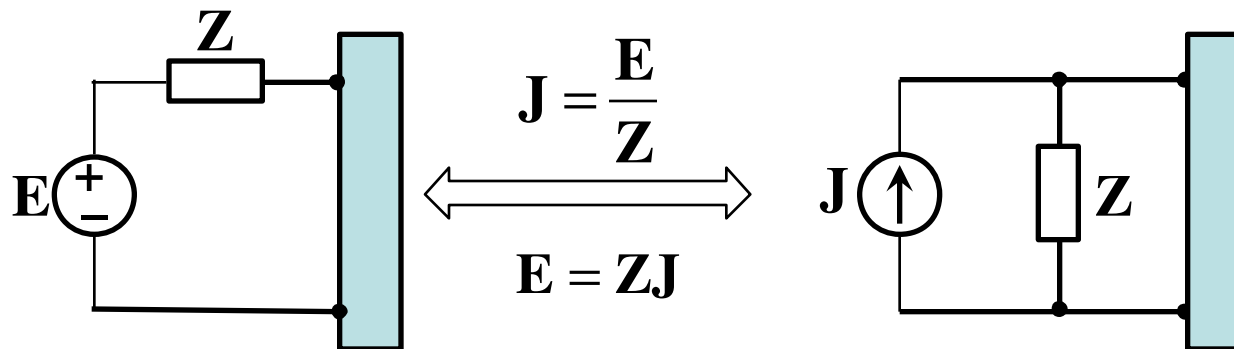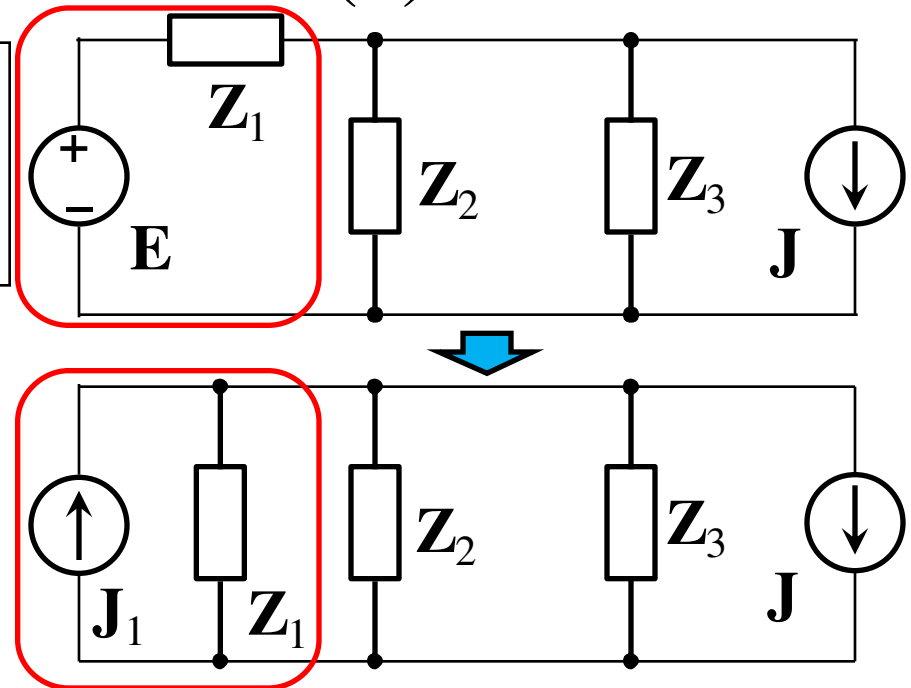
$$\mathbf{J}_1 = \frac{\mathbf{E}}{\mathbf{Z}_1} = \frac{20 \angle -45^\circ}{12} = 1.67 \angle -45^\circ \text{ A}$$



Source Transformation (3)

Ex. 1

$E = 20 \angle -45^\circ \text{ V}; J = 5 \angle 60^\circ \text{ A};$
 $Z_1 = 12 \Omega; Z_2 = j10 \Omega; Z_3 = -j16 \Omega;$
 Find the current of Z_2 ?




$$J_1 = \frac{E}{Z_1} = \frac{20 \angle -45^\circ}{12} = 1.67 \angle -45^\circ \text{ A}$$

$$Z_{13} = \frac{Z_1 Z_3}{Z_1 + Z_3} = \frac{12(-j16)}{12 - j16} = 7.68 - j5.76 \Omega$$

$$J_{eq} = J - J_1 = 5 \angle 60^\circ - 1.67 \angle -45^\circ = 1.32 + j5.51 \text{ A}$$

$$I_2 = J_{eq} \frac{Z_{13}}{Z_2 + Z_{13}} = (1.32 + j5.51) \frac{7.68 - j5.76}{j10 + 7.68 - j5.76}$$

$$= \boxed{6.09 + j1.16 \text{ A}}$$

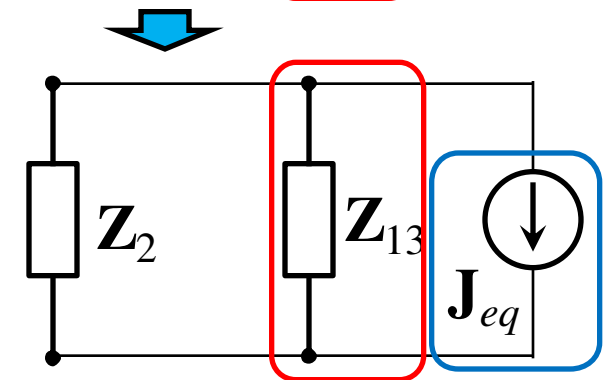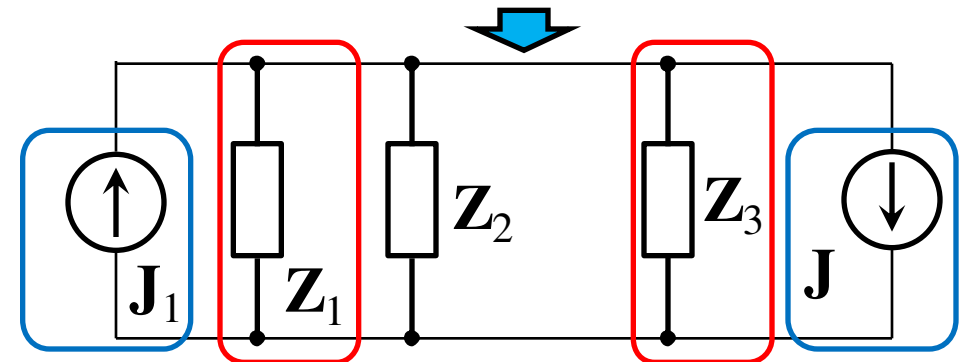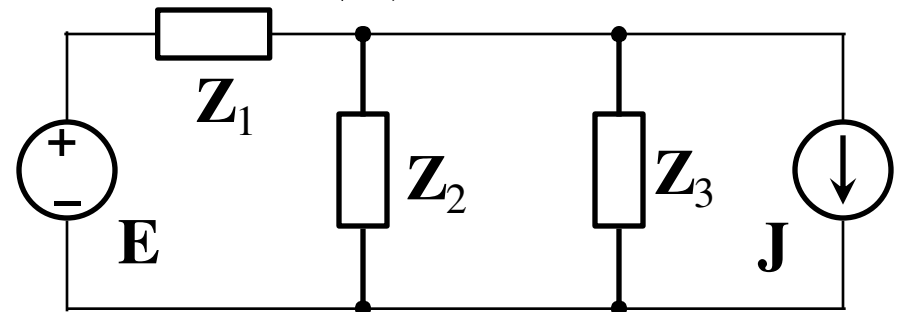

Source Transformation (3)

Ex. 2




$E_1 = 100 \angle 30^\circ \text{ V}; E_4 = 80 \angle -45^\circ \text{ V}; J = 5 \text{ A};$
 $Z_1 = 10 \Omega; Z_2 = 5 \Omega; Z_3 = j20 \Omega; Z_4 = -j25 \Omega;$
 Find the current of Z_2 ?

$$J_1 = \frac{E_1}{Z_1} = \frac{100 \angle 30^\circ}{10} = 10 \angle 30^\circ \text{ A}$$

$$J_4 = \frac{E_4}{Z_4} = \frac{80 \angle -45^\circ}{-j25} = 2.26 + j2.26 \text{ A}$$

$$J_{eq} = J_1 + J = 10 \angle 30^\circ + 5 = 13.66 + j5.00 \text{ A}$$

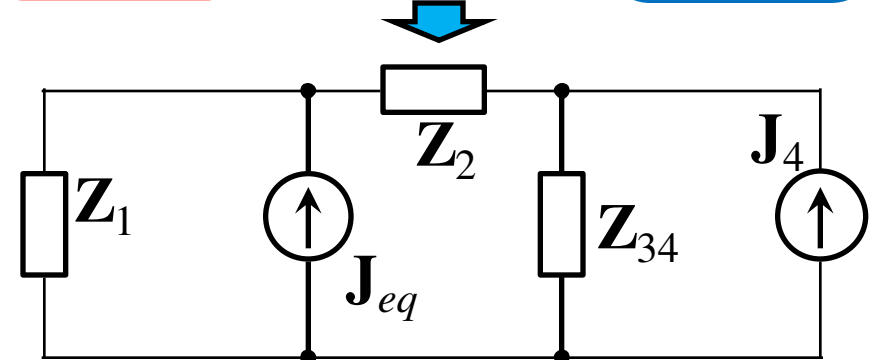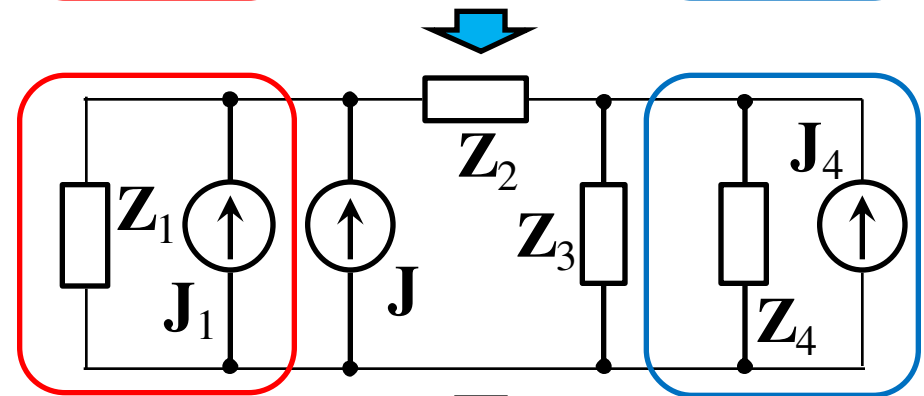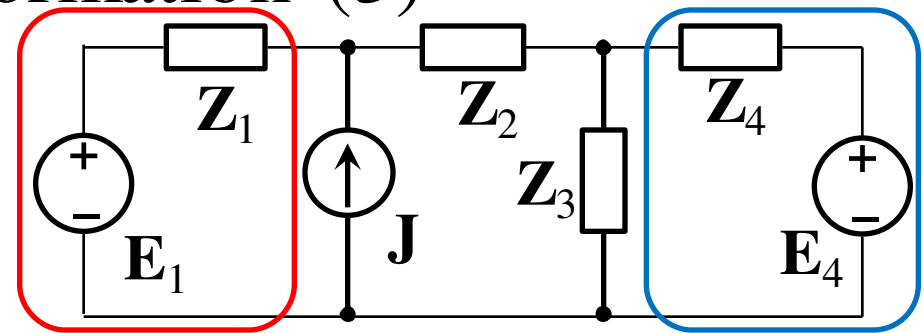
$$Z_{34} = \frac{Z_3 Z_4}{Z_3 + Z_4} = \frac{j20(-j25)}{j20 - j25} = j100 \Omega$$



Source Transformation (4)

Ex. 2

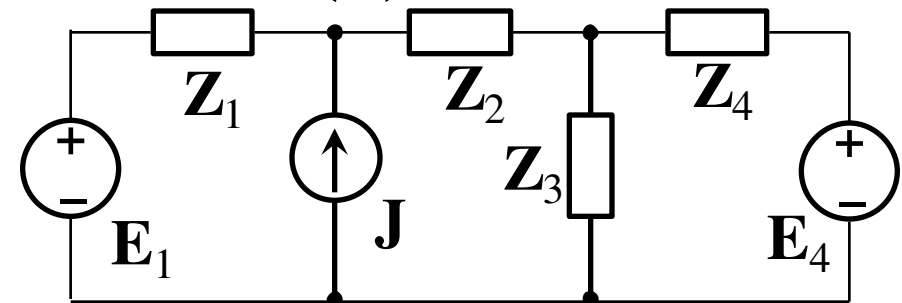
$E_1 = 100 \angle 30^\circ \text{ V}; E_4 = 80 \angle -45^\circ \text{ V}; J = 5 \text{ A};$
 $Z_1 = 10 \Omega; Z_2 = 5 \Omega; Z_3 = j20 \Omega; Z_4 = -j25 \Omega;$
 Find the current of Z_2 ?





$$J_{eq} = 13.66 + j5.00 \text{ A}; Z_{34} = j100 \Omega; J_4 = 2.26 + j2.26 \text{ A}$$

$$E_{eq} = Z_1 J_{eq} = 10(13.66 + j5.00) = 136.6 + j50 \text{ V}$$
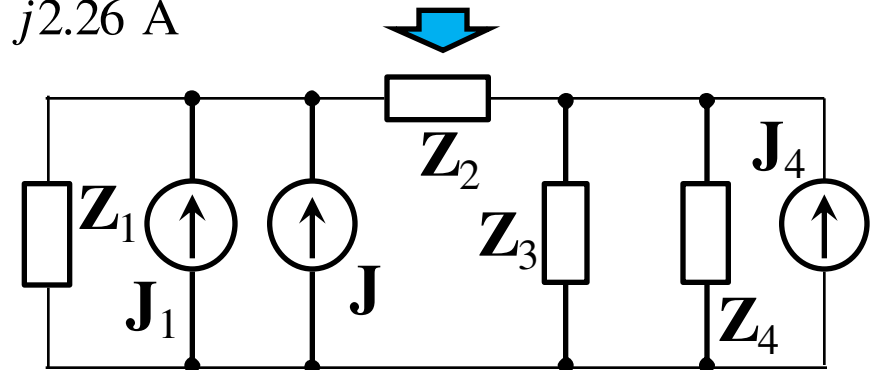
$$E_{34} = Z_{34} J_4 = -226 + j226 \text{ V}$$


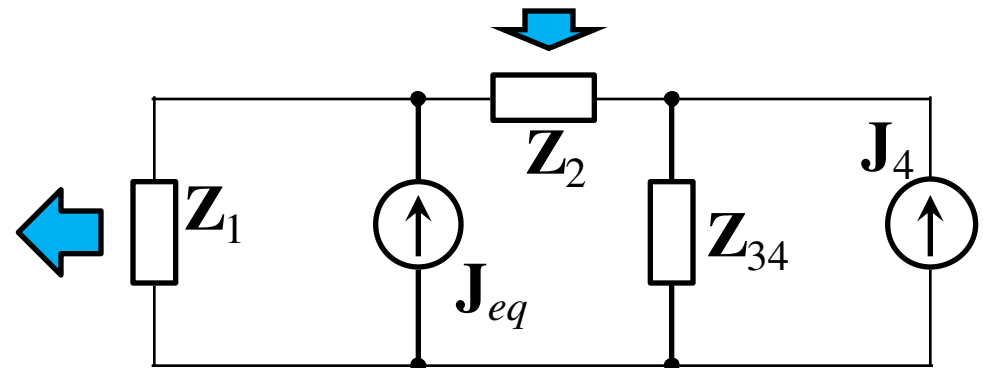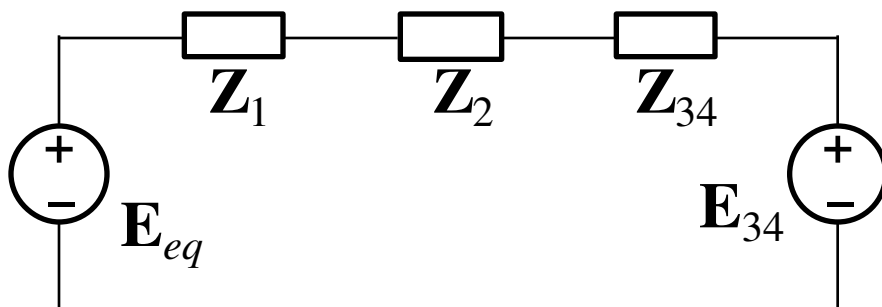
$$I_2 = \frac{E_{eq} - E_{34}}{Z_1 + Z_2 + Z_{34}} = \boxed{-1.19 - j3.81 \text{ A}}$$



Source Transformation (5)



Ex. 3

$E_1 = 100 \angle 30^\circ \text{ V}; J_3 = 5 \text{ A}; J_4 = 8 \angle -45^\circ \text{ A};$
 $Z_1 = 10 \Omega; Z_2 = 5 \Omega; Z_3 = j20 \Omega; Z_4 = -j25 \Omega;$
 Find the current of Z_3 ?

$$J_1 = \frac{E_1}{Z_1} = \frac{100 \angle 30^\circ}{10} = 10 \angle 30^\circ \text{ A} \quad Z_{12} = \frac{Z_1 Z_2}{Z_1 + Z_2} = 3.33 \Omega$$

$$Z_{12}(I - J_1) + Z_3(I + J_3) + Z_4(I + J_4) = 0 \rightarrow I = 7.68 + j28.94 \text{ A}$$
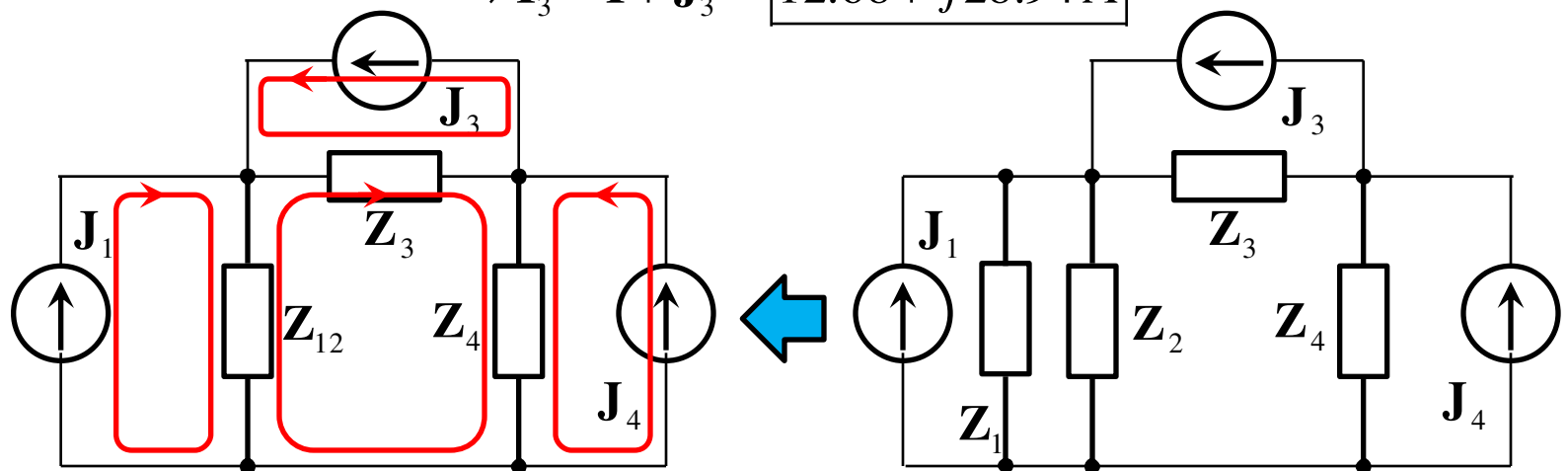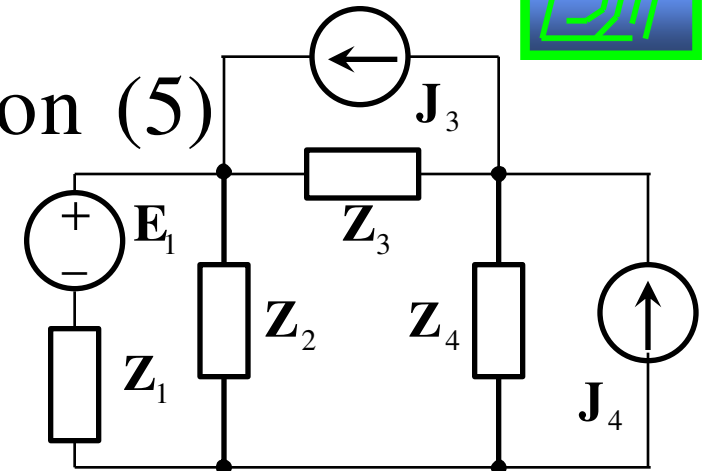
$$\rightarrow I_3 = I + J_3 = 12.68 + j28.94 \text{ A}$$





Sinusoidal Steady-State Analysis

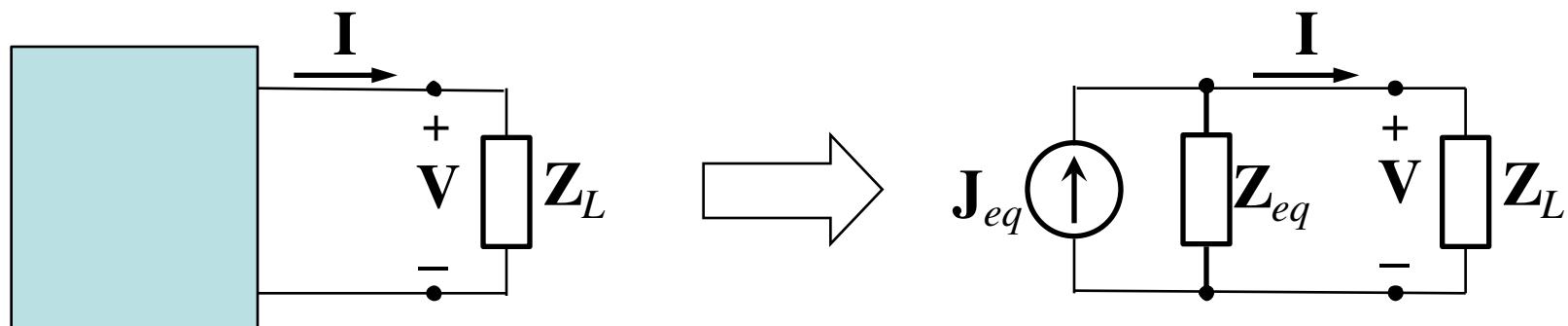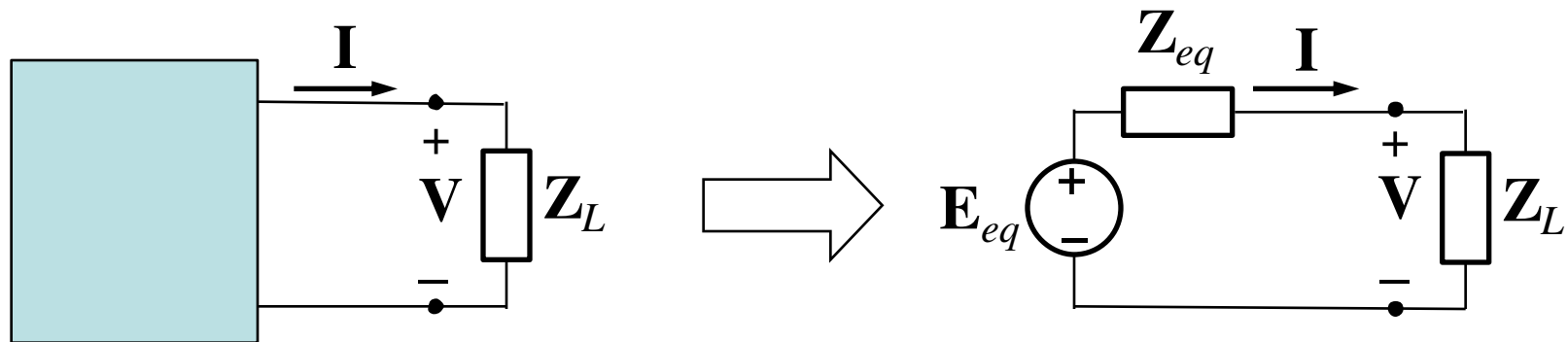
1. Sinusoidal Steady-State Analysis
2. Ohm's Law
3. Kirchhoff's Laws
4. Impedance Combinations
5. Branch Current Method
6. Node Voltage Method
7. Mesh Current Method
8. Superposition Theorem
9. Source Transformation
- 10. Thévenin & Norton Equivalent Circuits**
11. Op Amp AC Circuits



Thévenin & Norton Equivalent Circuits (1)



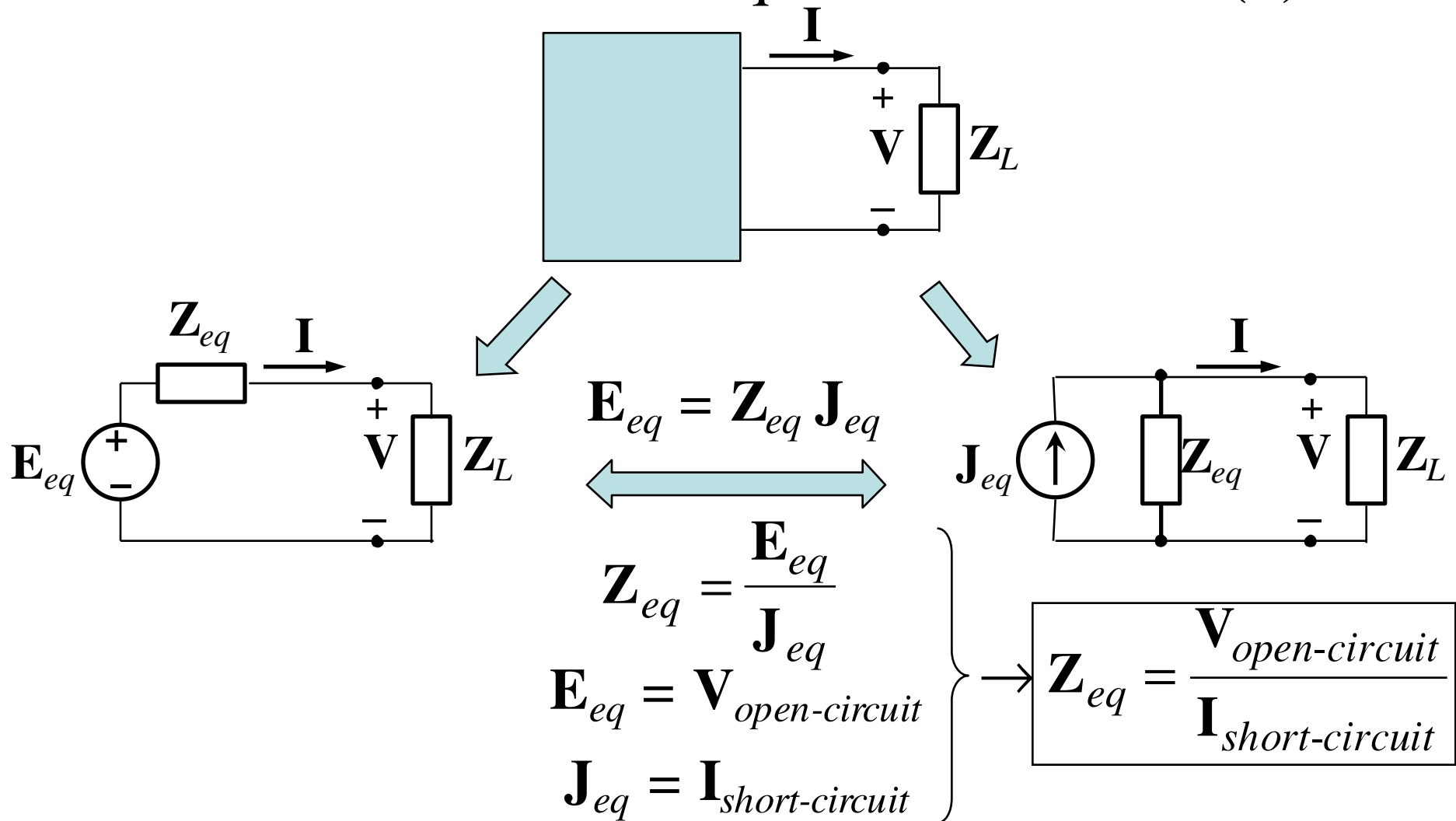Thévenin & Norton Equivalent Circuits (2)





Ex. 1 Thévenin & Norton Equivalent Circuits (3)


$$\mathbf{E} = 20 \angle -45^\circ \text{ V}; \mathbf{J} = 5 \angle 60^\circ \text{ A};$$

$$\mathbf{Z}_1 = 12 \Omega; \mathbf{Z}_2 = j10 \Omega; \mathbf{Z}_3 = -j16 \Omega;$$

Find the current of \mathbf{Z}_2 ?

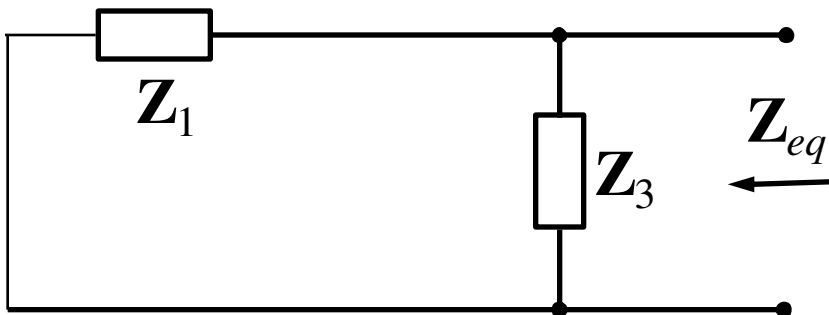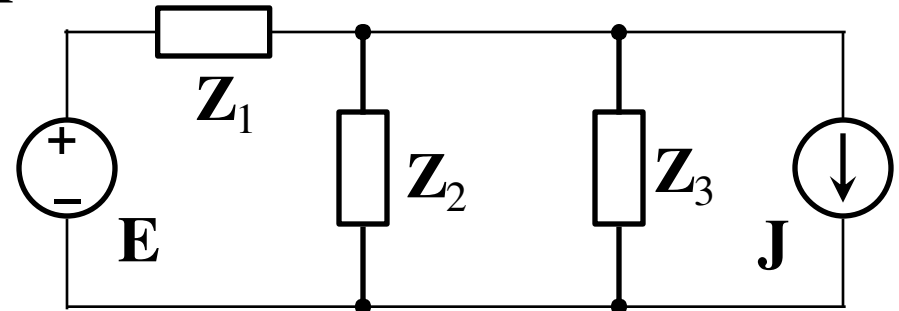
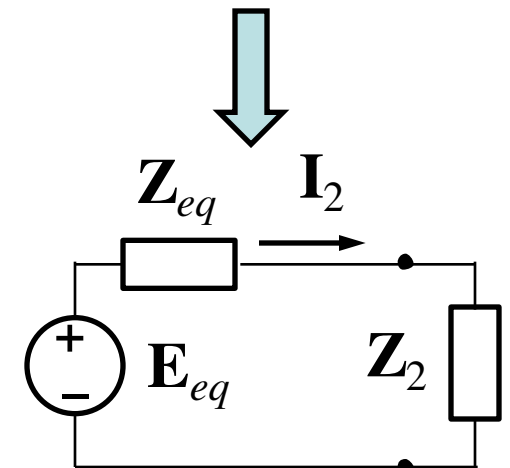
$$\mathbf{Z}_{eq} = \frac{\mathbf{Z}_1 \mathbf{Z}_3}{\mathbf{Z}_1 + \mathbf{Z}_3} = \frac{12(-j16)}{12 - j16} = \boxed{7.68 - j5.76 \Omega}$$






EX. 1 Thévenin & Norton Equivalent Circuits (4)

$$\mathbf{E} = 20 \angle -45^\circ \text{ V}; \mathbf{J} = 5 \angle 60^\circ \text{ A};$$

$$\mathbf{Z}_1 = 12 \Omega; \mathbf{Z}_2 = j10 \Omega; \mathbf{Z}_3 = -j16 \Omega;$$


Find the current of \mathbf{Z}_2 ?

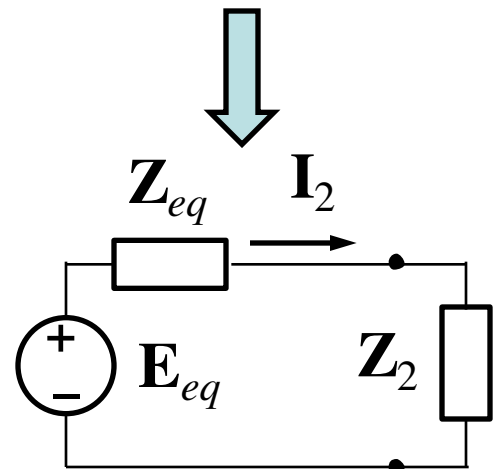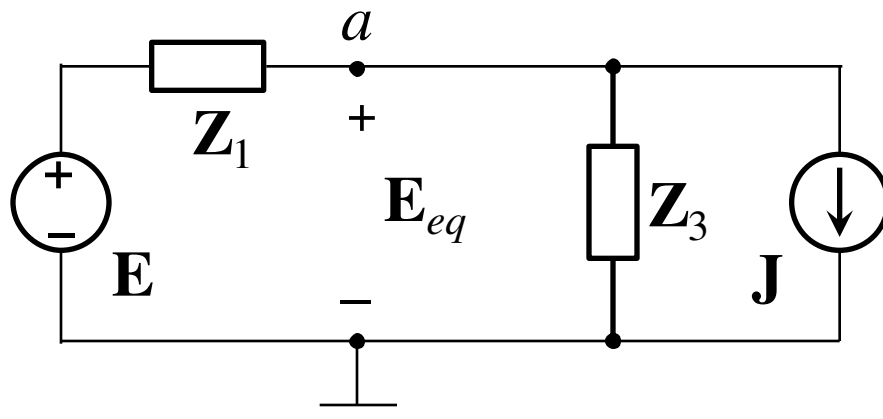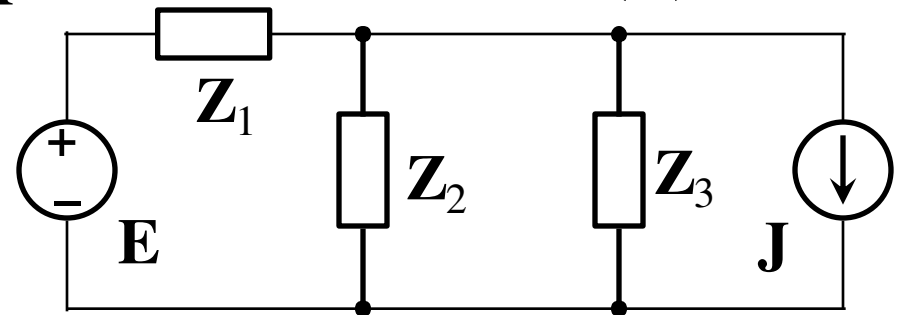

$$\mathbf{E}_{eq} = \mathbf{V}_a = \frac{\frac{\mathbf{E}}{\mathbf{Z}_1} - \mathbf{J}}{\frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_3}} = \frac{\frac{20 \angle -45^\circ}{12} - 5 \angle 60^\circ}{\frac{1}{12} + \frac{1}{-j16}} = \boxed{54.38 \angle -140.4^\circ \text{ V}}$$


Ex. 1 Thévenin & Norton Equivalent Circuits (5)

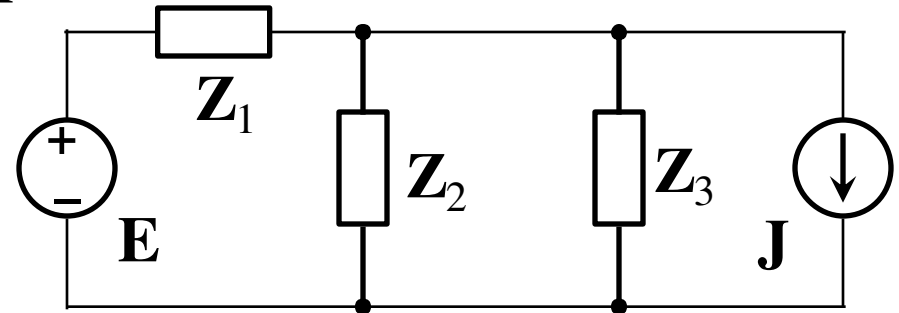$E = 20 \angle -45^\circ \text{ V}$; $J = 5 \angle 60^\circ \text{ A}$;
 $Z_1 = 12 \Omega$; $Z_2 = j10 \Omega$; $Z_3 = -j16 \Omega$;
 Find the current of Z_2 ?



$$Z_{eq} = 7.68 - j5.76 \Omega$$


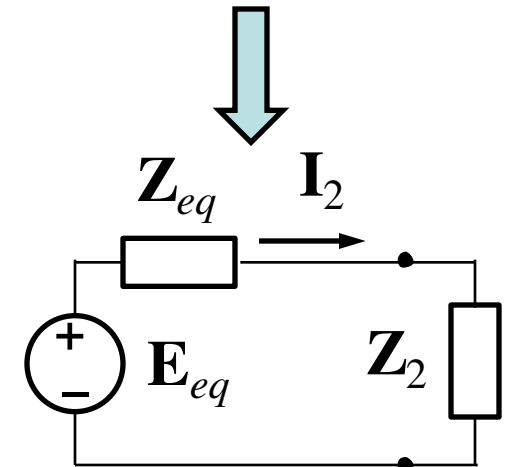
$$E_{eq} = 54.38 \angle -140.4^\circ \text{ V}$$



$$\rightarrow I_2 = \frac{E_{eq}}{Z_{eq} + Z_2} = \frac{54.38 \angle -140.4^\circ}{7.68 - j5.76 + j10} = \boxed{6.20 \angle -169.3^\circ \text{ A}}$$

EX. 2 Thévenin & Norton Equivalent Circuits (6)

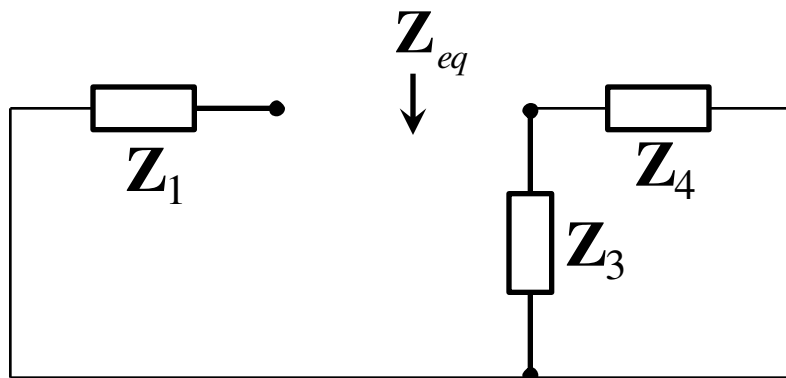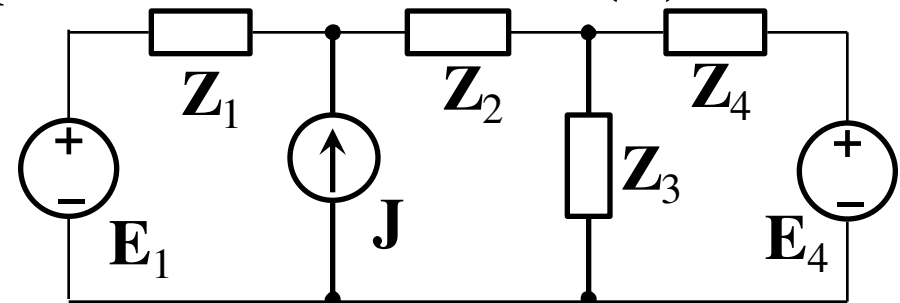
$E_1 = 100 \angle 30^\circ \text{ V}; E_4 = 80 \angle -45^\circ \text{ V}; J = 5 \text{ A};$
 $Z_1 = 10 \Omega; Z_2 = 5 \Omega; Z_3 = j20 \Omega; Z_4 = -j25 \Omega;$
 Find the current of Z_2 ?



$$Z_{eq} = Z_1 + \frac{Z_3 Z_4}{Z_3 + Z_4} = 10 + \frac{j20(-j25)}{j20 - j25} = 10 + j100 \Omega$$

$$E_{eq} = v_a - v_b$$
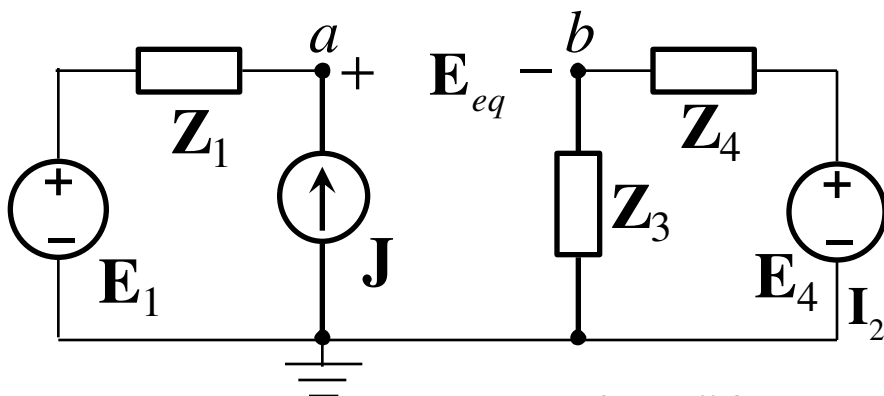
$$-Z_1 J + v_a = E_1 \rightarrow v_a = E_1 + Z_1 J = 137 + j50 \text{ V}$$





$$v_b = Z_3 I_3 = Z_3 \frac{E_4}{Z_3 + Z_4} = -226 + j226 \text{ V}$$

$$E_{eq} = v_a - v_b = 363 - j176 \text{ V}$$

$$I_2 = \frac{E_{eq}}{Z_{eq} + Z_2} = \frac{363 - j176}{10 + j100 + 5} = \boxed{-1.19 - j3.81 \text{ A}}$$

Ex. 3 Thévenin & Norton Equivalent Circuits (7)

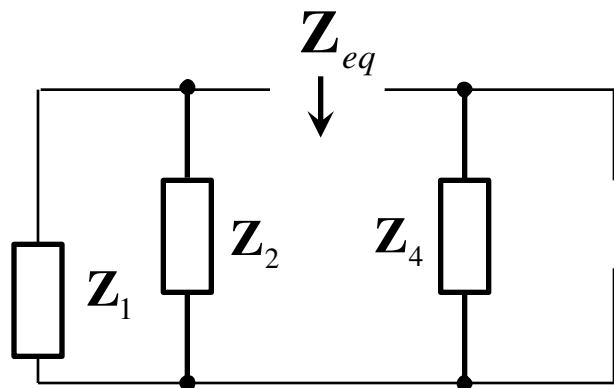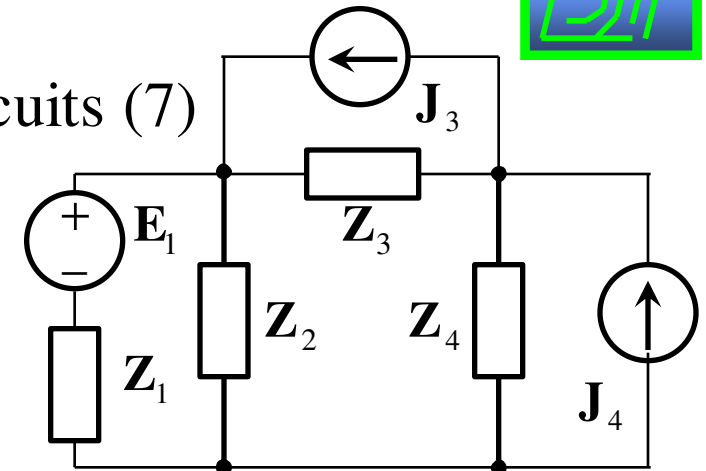$E_1 = 100 \angle 30^\circ \text{ V}; J_3 = 5 \text{ A}; J_4 = 8 \angle -45^\circ \text{ A};$
 $Z_1 = 10 \Omega; Z_2 = 5 \Omega; Z_3 = j20 \Omega; Z_4 = -j25 \Omega;$
 Find the current of Z_3 ?




$$E_{eq} = v_a - v_b$$

$$\begin{cases} \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) v_a = \frac{E_1}{Z_1} + J_3 \\ \frac{1}{Z_4} v_b = -J_3 + J_4 \end{cases}$$

$$Z_{eq} = Z_4 + \frac{Z_1 Z_2}{Z_1 + Z_2} = -j25 + \frac{10 \times 5}{10 + 5} = 3.33 - j25 \Omega$$


$$I_3 = \frac{E_{eq}}{Z_{eq} + Z_3} = 12.68 + j28.94 \text{ A}$$
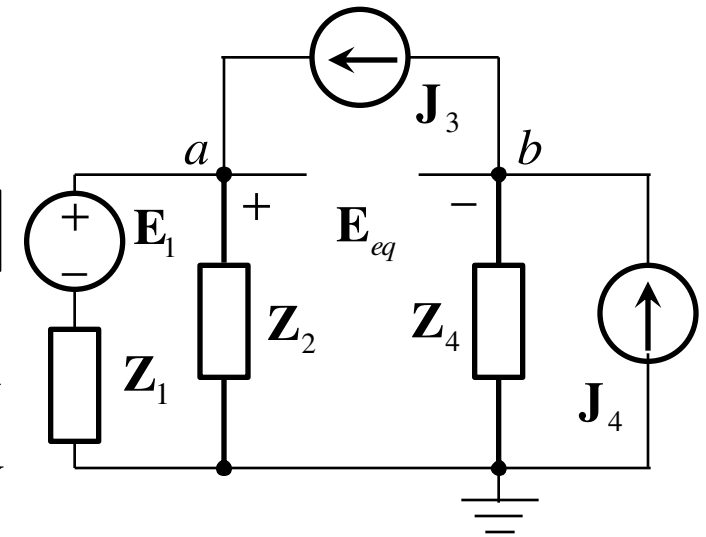
$$\rightarrow \begin{cases} v_a = 45.53 + j16.67 \text{ V} \\ v_b = -141.4 - j16.4 \text{ V} \end{cases}$$




EX. 4 Thévenin & Norton Equivalent Circuits (8)


$E_1 = 100 \angle 30^\circ \text{ V}; E_4 = 80 \angle -45^\circ \text{ V}; J = 5 \text{ A};$
 $Z_1 = 10\Omega; Z_2 = 5\Omega; Z_3 = j20\Omega; Z_4 = -j25\Omega;$
 Find Z_{ab} ?

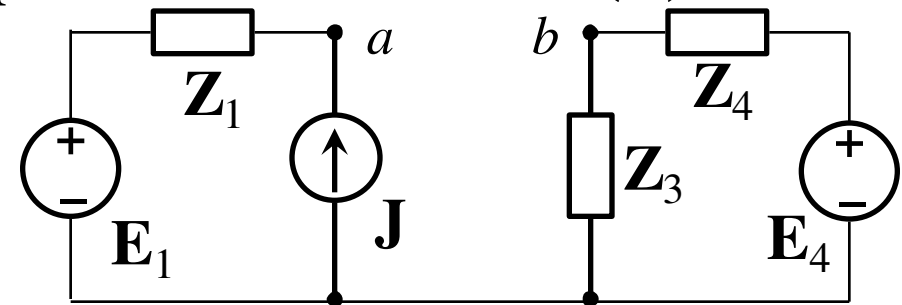

Method 1


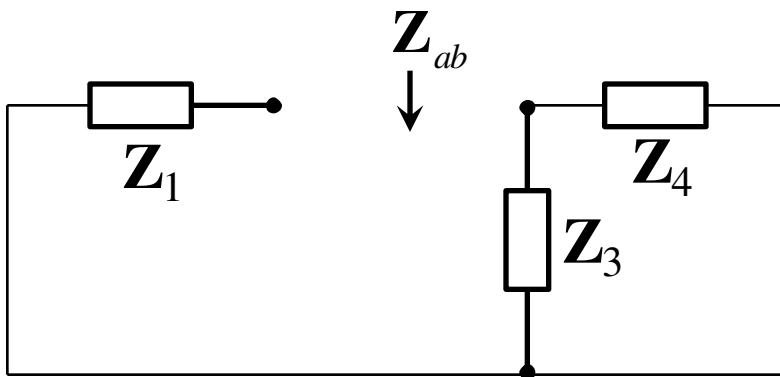

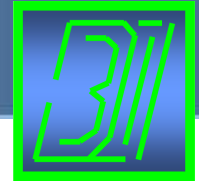
$$Z_{ab} = Z_1 + \frac{Z_3 Z_4}{Z_3 + Z_4} = 10 + \frac{j20(-j25)}{j20 - j25} = \boxed{10 + j100\Omega}$$



EX. 4 Thévenin & Norton Equivalent Circuits (9)

$E_1 = 100 \angle 30^\circ \text{ V}; E_4 = 80 \angle -45^\circ \text{ V}; J = 5 \text{ A};$
 $Z_1 = 10 \Omega; Z_2 = 5 \Omega; Z_3 = j20 \Omega; Z_4 = -j25 \Omega;$
 Find Z_{ab} ?

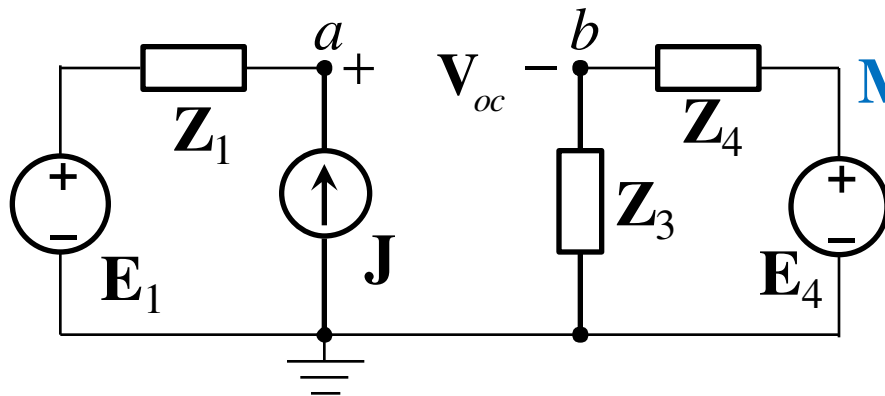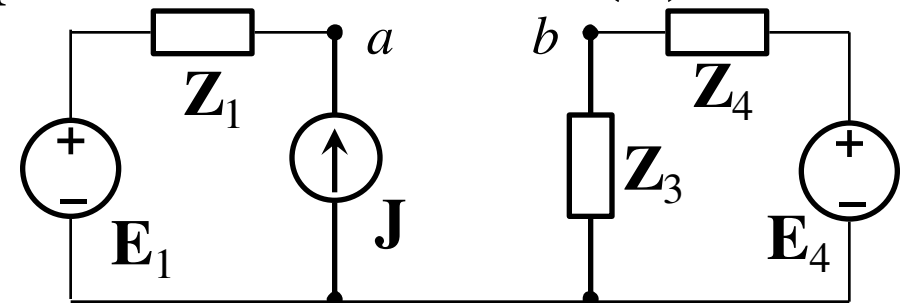

Method 2

$$Z_{ab} = \frac{V_{open-circuit}}{I_{short-circuit}}$$


$$V_{oc} = 363 - j176 \text{ V}$$

$$I_{sc} = I_1 + J = -1,39 - j3,77 \text{ A}$$

$$v_a = \frac{E_1 / Z_1 + J + E_4 / Z_4}{1/Z_1 + 1/Z_3 + 1/Z_4} = 150 + j88 \text{ V}$$


$$I_1 = (E_1 - v_a) / Z_1 = -6.39 - j3.77 \text{ A}$$
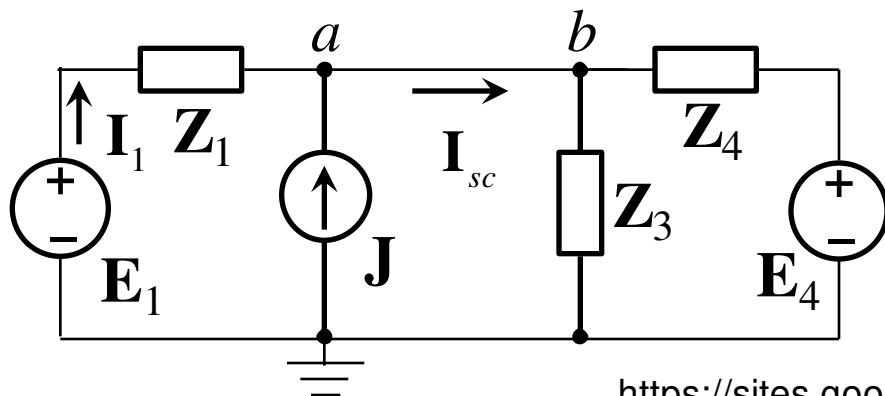
$$\rightarrow \boxed{Z_{ab} = 10 + j100 \Omega}$$



EX. 4 Thévenin & Norton Equivalent Circuits (10)


$E_1 = 100 \angle 30^\circ \text{ V}; E_4 = 80 \angle -45^\circ \text{ V}; J = 5 \text{ A};$
 $Z_1 = 10 \Omega; Z_2 = 5 \Omega; Z_3 = j20 \Omega; Z_4 = -j25 \Omega;$
 Find Z_{ab} ?

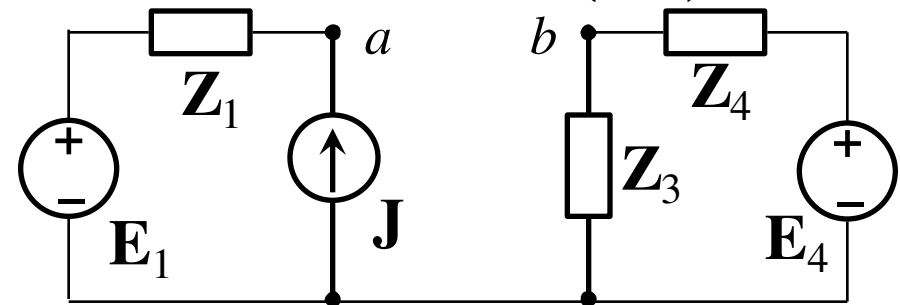

Method 3

$$Z_{ab} = \frac{E_{in}}{I_{in}}$$

$$E_{in} = 100 \text{ V}$$

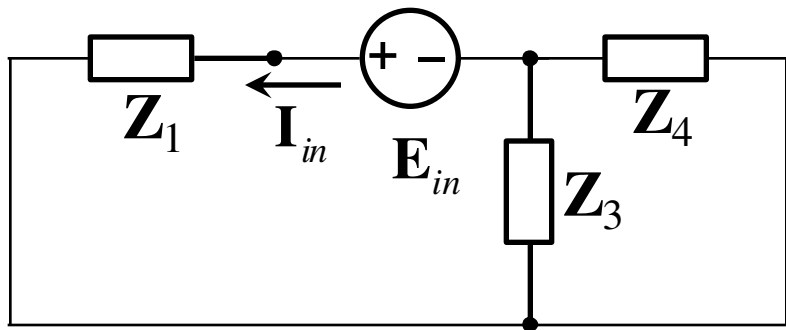

$$I_{in} = \frac{100}{Z_1 + \frac{Z_3 Z_4}{Z_3 + Z_4}} = \frac{100}{10 + \frac{j20(-j25)}{j20 - j25}} = 0.099 - j0.099 \text{ A}$$

$$\rightarrow Z_{ab} = \frac{100}{0.099 - j0.099} = \boxed{10 + j100 \Omega}$$

Thévenin & Norton Equivalent Circuits (11)


Ex. 5

Find Z_{eq} ? $Z_{eq} = \frac{V_{open-circuit}}{I_{short-circuit}}$

$$\left. \begin{aligned} (V_c - V_b) - 16 + j6I_2 + 4I_1 &= 0 \\ V_{oc} &= V_b - V_c \end{aligned} \right\}$$

$$\left. \begin{aligned} \rightarrow V_{oc} &= -16 + j6I_2 + 4I_1 \\ I_1 &= 2/30^\circ \\ I_2 = I_c &= 2I_1 = 2 \times 2/30^\circ \end{aligned} \right\}$$
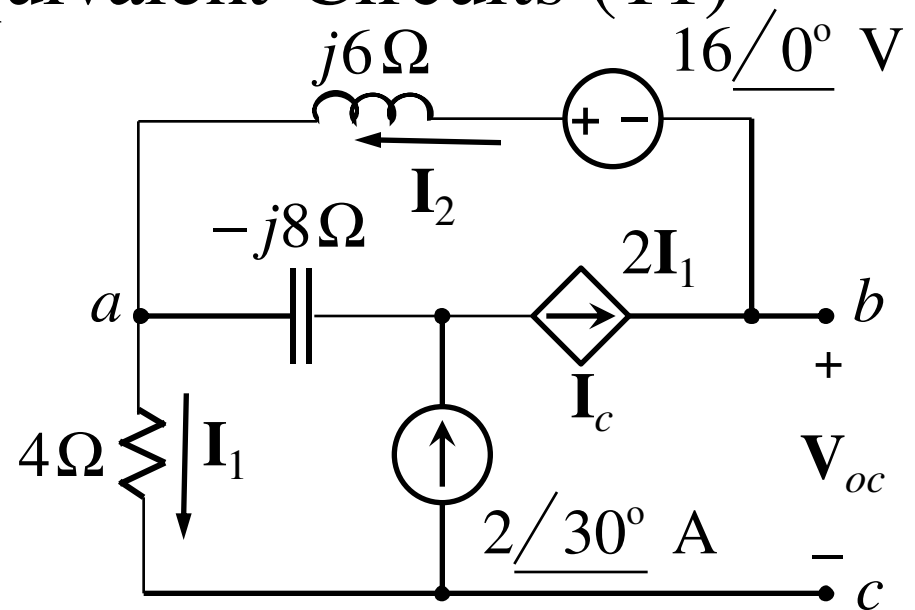
$$\rightarrow V_{oc} = -16 + j6 \times 2 \times 2/30^\circ + 4 \times 2/30^\circ = -21.07 + j24.78 \text{ V}$$



Thévenin & Norton Equivalent Circuits (12)

Ex. 5

Find Z_{eq} ? $Z_{eq} = \frac{V_{open-circuit}}{I_{short-circuit}}$

$$I_1 - 2\angle 30^\circ + I_{sc} = 0$$

$$\rightarrow I_{sc} = 2\angle 30^\circ - I_1$$

$$j6I_2 + 4I_1 = 16\angle 0^\circ$$


$$I_2 - I_1 + 2\angle 30^\circ - I_c = 0$$

$$\rightarrow I_2 - I_1 + 2\angle 30^\circ - 2I_1 = 0$$

$$\rightarrow 3I_1 - I_2 = 2\angle 30^\circ$$


$$\rightarrow I_1 = 0.67 - j0.41 \text{ A}$$
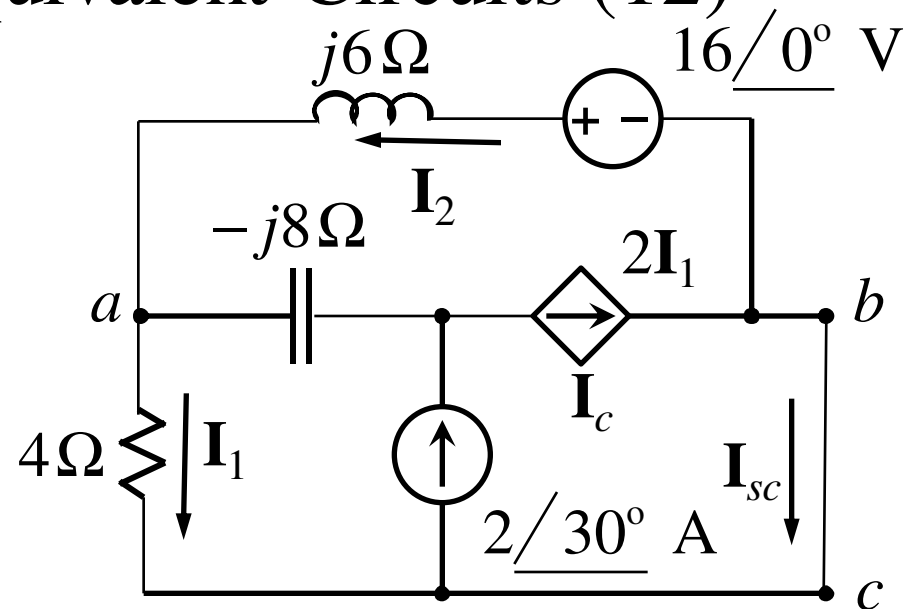
$$\begin{aligned} \rightarrow I_{sc} &= 2\angle 30^\circ - (0.67 - j0.41) \\ &= 1.06 + j1.41 \text{ A} \end{aligned}$$



Ex. 5 Thévenin & Norton Equivalent Circuits (13)

Find Z_{eq} ? **Method 1**

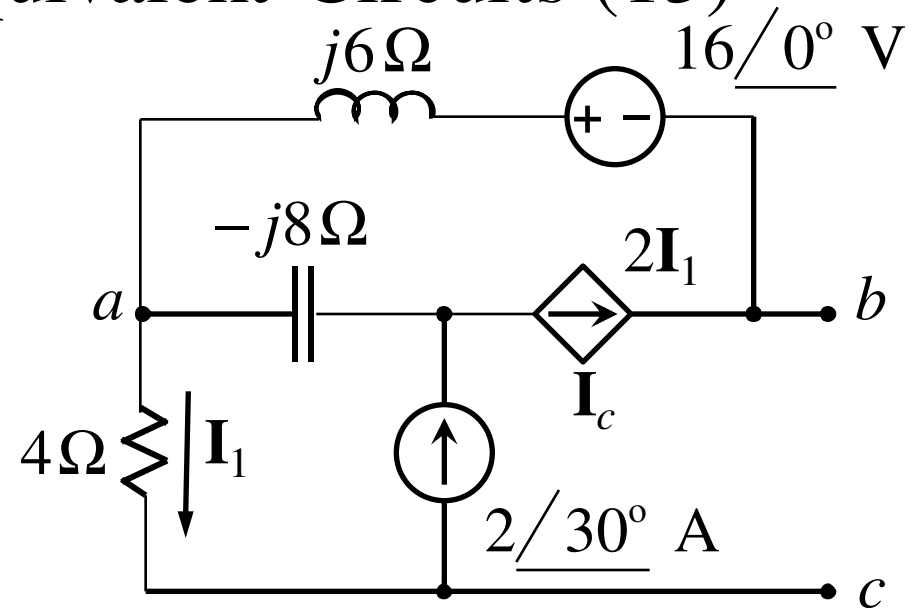

$$Z_{eq} = \frac{V_{open-circuit}}{I_{short-circuit}}$$

$$\left. \begin{array}{l} V_{oc} = -21.07 + j24.78 \text{ V} \\ I_{sc} = 1.06 + j1.41 \text{ A} \end{array} \right\} \rightarrow Z_{eq} = \frac{-21.07 + j24.78}{1.06 + j1.41} = \boxed{4.00 + j18.00 \Omega}$$



Thévenin & Norton Equivalent Circuits (14)

Ex. 5

Find Z_{eq} ?

Method 2

$$Z_{eq} = \frac{100}{I_{in}}$$

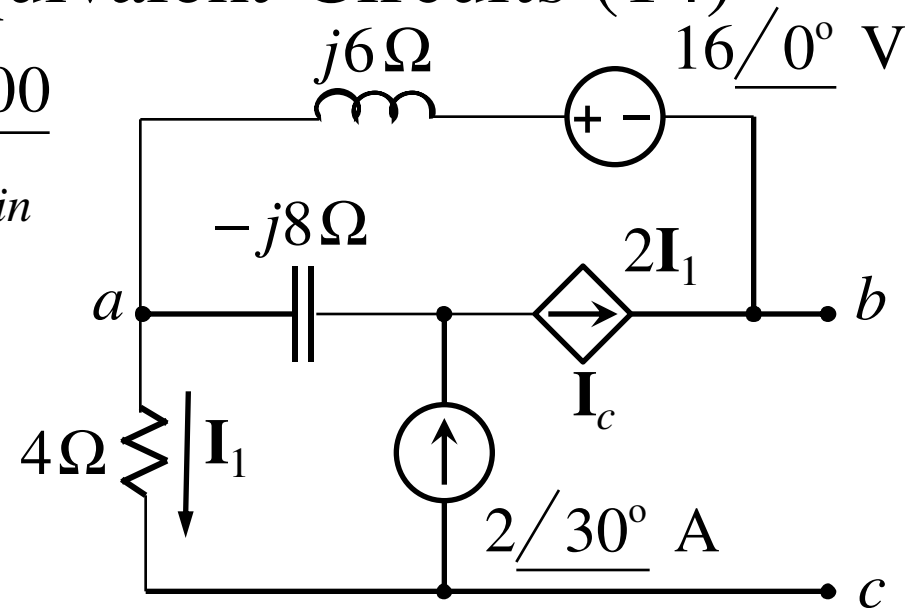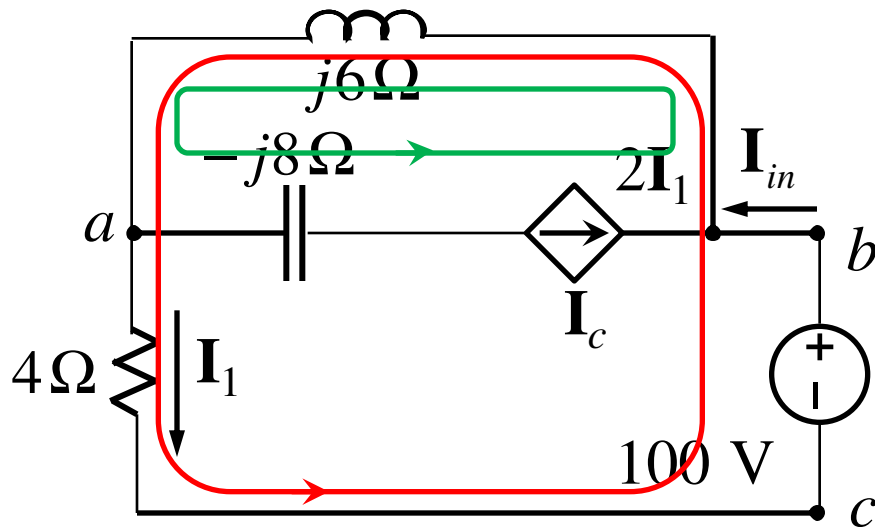


$$\left. \begin{aligned} j6(I_r + I_g) + 4I_r &= 100 \\ I_g &= 2I_1 = 2I_r \end{aligned} \right\} \rightarrow I_r = 1.18 - j5.29 \text{ A} = I_{in}$$

$$\rightarrow Z_{eq} = \frac{100}{1.18 - j5.29} = \boxed{4.00 + j18.00 \Omega}$$

Ex. 6 Thévenin & Norton Equivalent Circuits (15)

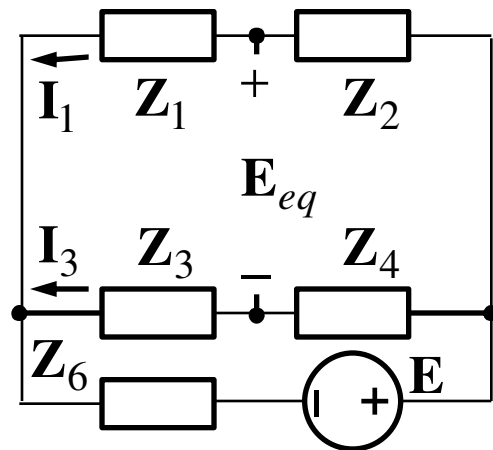$E = 100V$; $Z_1 = j10$; $Z_2 = 5 - j10$; $Z_3 = 10 + j5$; $Z_4 = 20$;
 $Z_5 = -j20$; $Z_6 = 5 + j5$; find the current flowing through Z_5 ?




$$E_{eq} + Z_3 I_3 - Z_1 I_1 = 0$$

$$I_6 = \frac{E}{\frac{(Z_1 + Z_2)(Z_3 + Z_4)}{Z_1 + Z_2 + Z_3 + Z_4} + Z_6} = 8.27 - j4.53 \text{ A}$$

$$I_1 = \frac{(Z_3 + Z_4)I_6}{Z_1 + Z_2 + Z_3 + Z_4} = 7.20 - j3.73 \text{ A}$$


$$I_3 = I_6 - I_1 = 1.07 - j0.80 \text{ A}$$
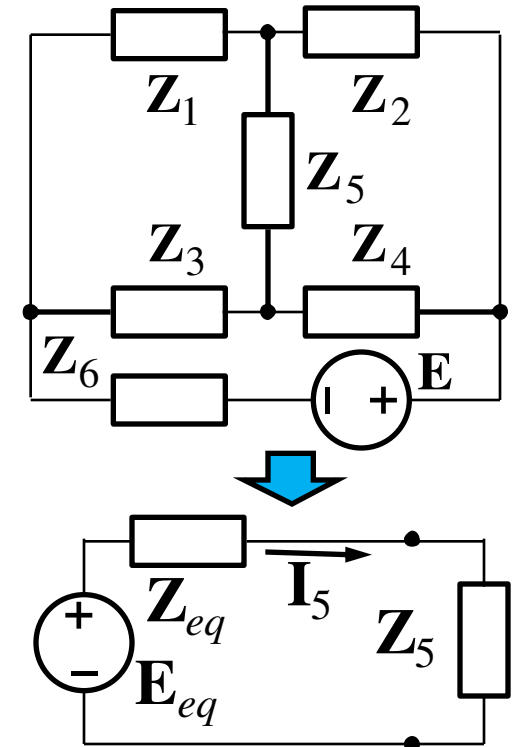
$$\rightarrow E_{eq} = -6.67 + j13.33 \text{ V}$$




Ex. 6 Thévenin & Norton Equivalent Circuits (16)

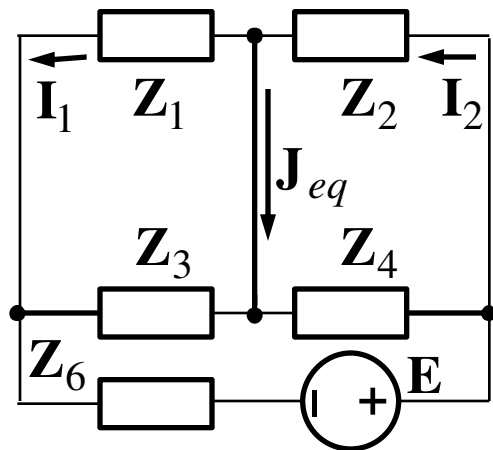$E = 100V$; $Z_1 = j10$; $Z_2 = 5 - j10$; $Z_3 = 10 + j5$; $Z_4 = 20$;
 $Z_5 = -j20$; $Z_6 = 5 + j5$; find the current flowing through Z_5 ?



$$\left. \begin{aligned} I_2 - I_1 - J_{eq} &= 0 \\ I_6 &= \frac{E}{\frac{Z_1 Z_3}{Z_1 + Z_3} + \frac{Z_2 Z_4}{Z_2 + Z_4} + Z_6} \\ &= 6.27 - j2.14 \text{ A} \\ I_1 &= \frac{Z_3 I_6}{Z_1 + Z_3} = 2.72 - j3.08 \text{ A} \\ I_2 &= \frac{Z_4 I_6}{Z_2 + Z_4} = 4.92 + j0.26 \text{ A} \end{aligned} \right\}$$
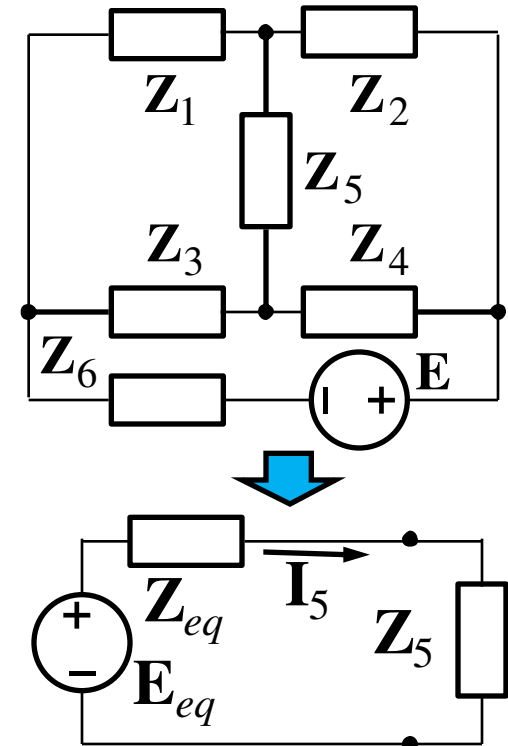
$$\rightarrow J_{eq} = 2.20 + j3.34 \text{ A} \rightarrow I_5 = \frac{E_{eq}}{Z_5 + \frac{E_{eq}}{J_{eq}}} = \boxed{-0.83 - j0.31 \text{ A}}$$



$$E_{eq} = -6.67 + j13.33 \text{ V}$$

Sinusoidal Steady-State Analysis

1. Sinusoidal Steady-State Analysis
2. Ohm's Law
3. Kirchhoff's Laws
4. Impedance Combinations
5. Branch Current Method
6. Node Voltage Method
7. Mesh Current Method
8. Superposition Theorem
9. Source Transformation
10. Thévenin & Norton Equivalent Circuits
- 11. Op Amp AC Circuits**




Op Amp AC Circuits (1)

Ex. 1

Find V_o ?
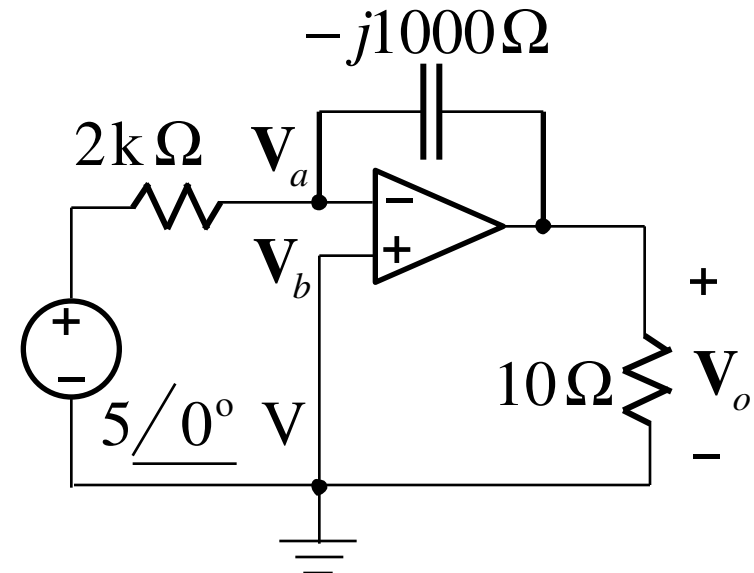
$$\frac{5/0^\circ}{2000} + \frac{V_o}{-j1000} = 0$$




$$\rightarrow V_o = j1000 \frac{5/0^\circ}{2000} = j2.5/0^\circ = \boxed{2.5/90^\circ \text{ V}}$$

Op Amp AC Circuits (2)

Ex. 2

Find v_o ?
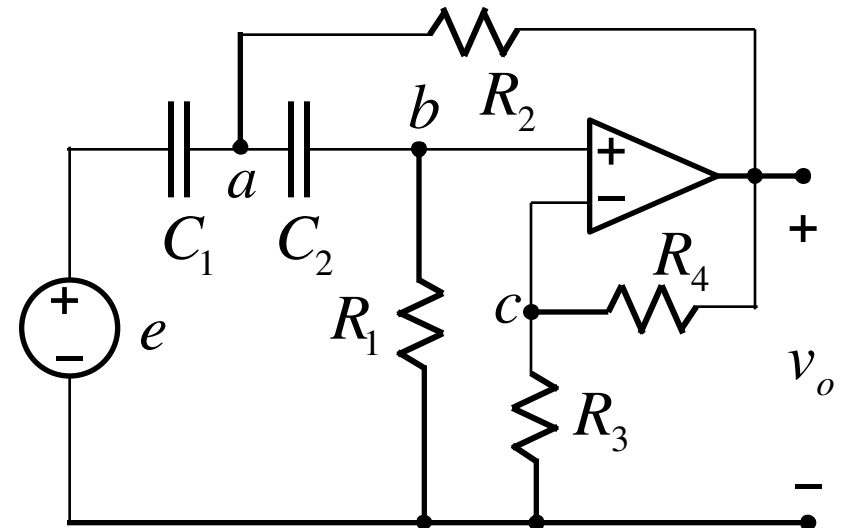
$$\left. \begin{aligned} a: \quad \frac{\mathbf{E} - \mathbf{V}_a}{\mathbf{Z}_{C1}} &= \frac{\mathbf{V}_a - \mathbf{V}_o}{R_2} + \frac{\mathbf{V}_a - \mathbf{V}_b}{\mathbf{Z}_{C2}} \\ b: \quad \frac{\mathbf{V}_a - \mathbf{V}_b}{\mathbf{Z}_{C2}} &= \frac{\mathbf{V}_b}{R_1} \\ c: \quad \mathbf{V}_c &= \frac{R_3}{R_3 + R_4} \mathbf{V}_o = \mathbf{V}_b \end{aligned} \right\}$$



$$\rightarrow \mathbf{V}_o = f(\mathbf{E}, R_1, R_2, R_3, R_4, \mathbf{Z}_{C1}, \mathbf{Z}_{C2})$$