



TRƯỜNG ĐẠI HỌC
BÁCH KHOA HÀ NỘI

Nguyễn Công Phương



Electric Circuit Theory


The Laplace Transform

Contents

- I. Basic Elements Of Electrical Circuits
- II. Basic Laws
- III. Electrical Circuit Analysis
- IV. Circuit Theorems
- V. Active Circuits
- VI. Capacitor And Inductor
- VII. First Order Circuits
- VIII. Second Order Circuits
- IX. Sinusoidal Steady State Analysis
- X. AC Power Analysis
- XI. Three-phase Circuits
- XII. Magnetically Coupled Circuits
- XIII. Frequency Response
- XIV. The Laplace Transform**
- XV. Two-port Networks



The Laplace Transform

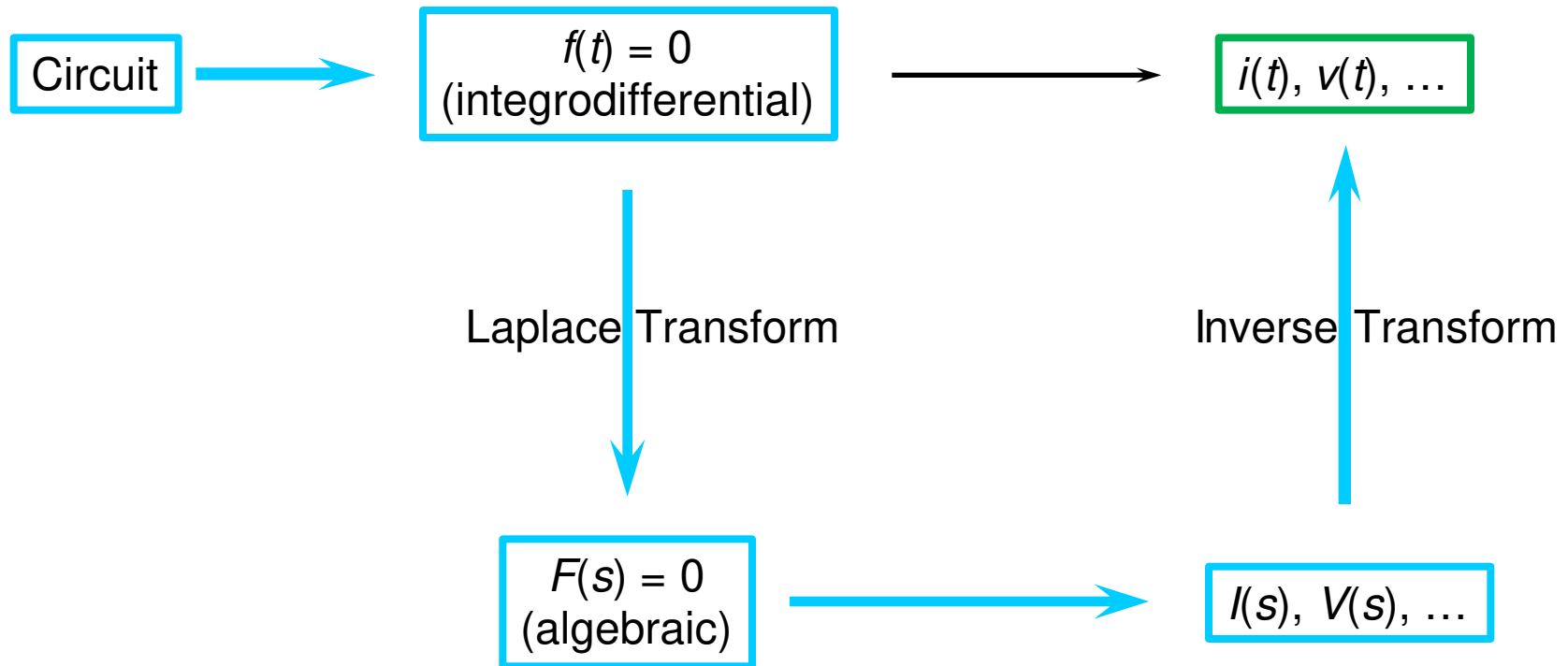


The Laplace Transform

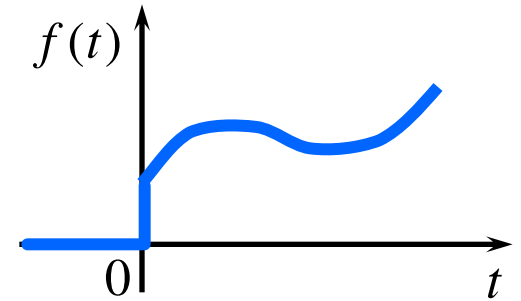1. Definition
2. Two Important Singularity Functions
3. Transform Pairs
4. Properties of the Transform
5. Inverse Transform
6. Initial-Value & Final-Value Theorems
7. Laplace Circuit Solutions
8. Circuit Element Models
9. Analysis Techniques
10. Convolution Integral
11. Transfer Function

Definition

$$F(s) = L[f(t)] = \int_0^{\infty} f(t)e^{-st} dt$$



$$s = \sigma + j\omega$$

$$\int_0^{\infty} |f(t)| e^{-\sigma t} dt < \infty$$

$$f(t) = L^{-1}[F(s)] = \frac{1}{2\pi j} \int_{\sigma_1 - j\infty}^{\sigma_1 + j\infty} F(s)e^{st} ds$$


The Laplace Transform

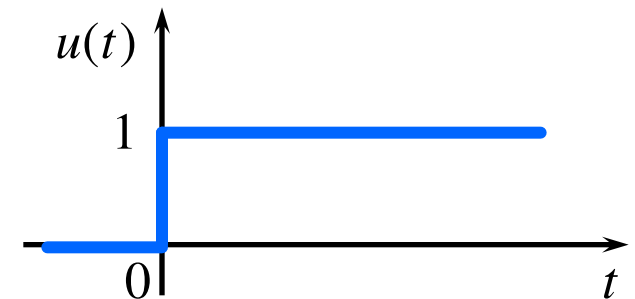1. Definition
- 2. Two Important Singularity Functions**
3. Transform Pairs
4. Properties of the Transform
5. Inverse Transform
6. Initial-Value & Final-Value Theorems
7. Laplace Circuit Solutions
8. Circuit Element Models
9. Analysis Techniques
10. Convolution Integral
11. Transfer Function




Two Important Singularity Functions (1)

$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$


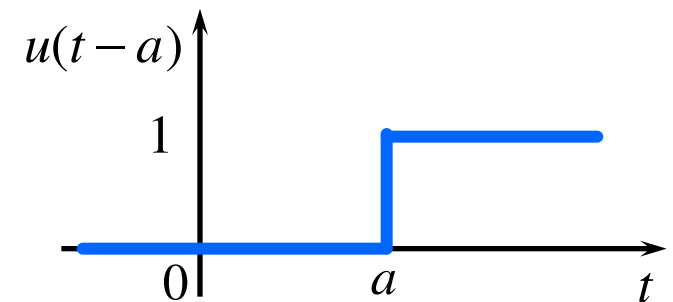
$$u(t - a) = \begin{cases} 0 & t < a \\ 1 & t > a \end{cases}$$



Ex. 1 Two Important Singularity Functions (2)


Determine the Laplace transform for the waveform?

$$F(s) = \int_0^{\infty} u(t) e^{-st} dt$$

$$= \int_0^{\infty} 1 e^{-st} dt$$

$$= -\frac{1}{s} e^{-st} \Big|_0^{\infty}$$


$$= \boxed{\frac{1}{s}}$$

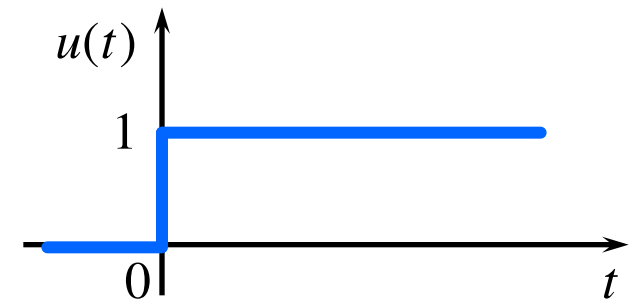

Ex. 2 Two Important Singularity Functions (3)

Determine the Laplace transform for the waveform?

$$\begin{aligned} F(s) &= \int_0^{\infty} u(t-a)e^{-st} dt \\ &= \int_0^a 0 dt + \int_a^{\infty} 1e^{-st} dt \\ &= -\frac{1}{s} e^{-st} \Big|_a^{\infty} \\ &= \boxed{\frac{e^{-as}}{s}} \end{aligned}$$

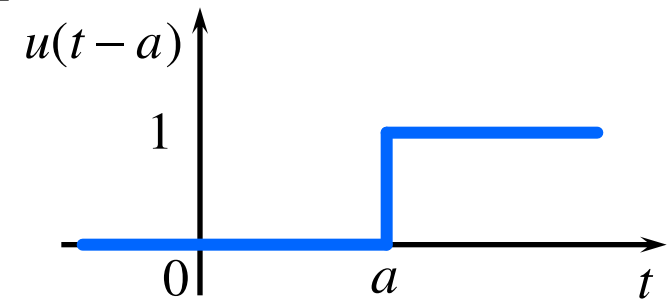




Ex. 3 Two Important Singularity Functions (4)

Determine the Laplace transform for the waveform?

$$F(s) = \int_0^{\infty} [u(t) - u(t-a)]e^{-st} dt$$

$$\left. \begin{aligned} \int_0^{\infty} u(t)e^{-st} dt &= \frac{1}{s} \\ \int_0^{\infty} u(t-a)e^{-st} dt &= \frac{e^{-as}}{s} \end{aligned} \right\}$$

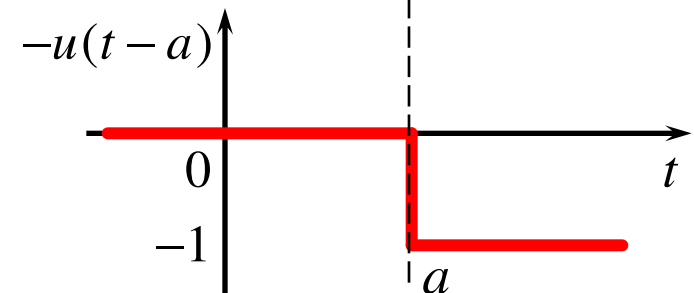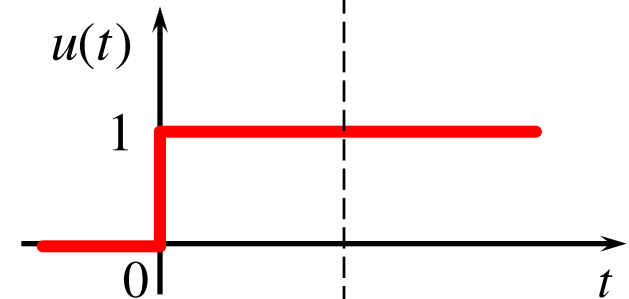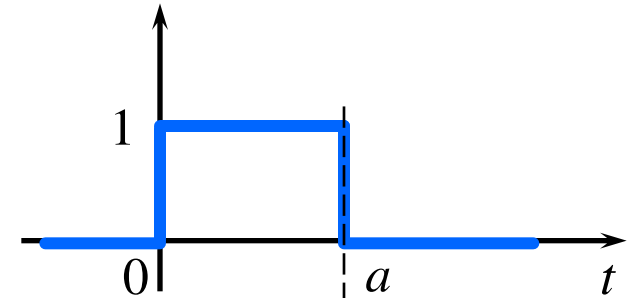
$$\rightarrow F(s) = \frac{1}{s} - \frac{e^{-as}}{s} = \boxed{\frac{1 - e^{-as}}{s}}$$



Two Important Singularity Functions (5)


$$\delta(t) = 0 \quad t \neq 0$$
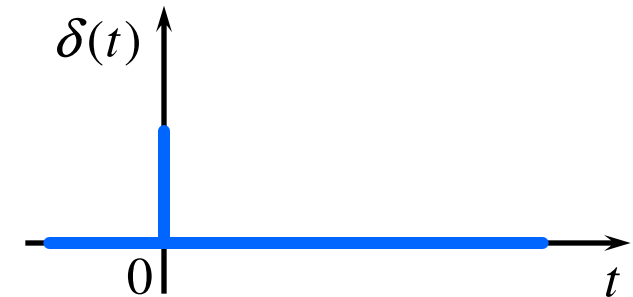
$$\int_{-\varepsilon}^{\varepsilon} \delta(t) dt = 1 \quad \varepsilon > 0$$



$$\delta(t - a) = 0 \quad t \neq a$$
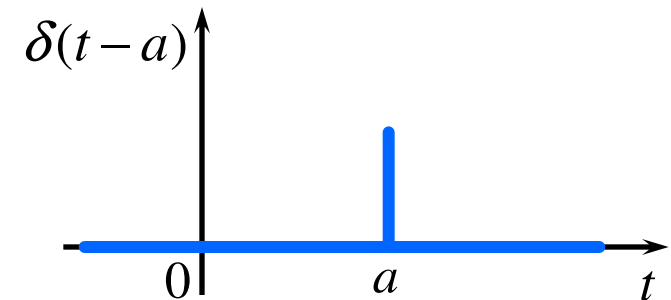
$$\int_{a-\varepsilon}^{a+\varepsilon} \delta(t - a) dt = 1 \quad \varepsilon > 0$$



$$\int_{t_1}^{t_2} f(t) \delta(t - a) dt = \begin{cases} f(a) & t_1 < a < t_2 \\ 0 & a < t_1, a > t_2 \end{cases}$$

Ex. 4 Two Important Singularity Functions (6)

Determine the Laplace transform of an impulse function?

$$\left. \begin{aligned} F(s) &= \int_0^{\infty} \delta(t-a)e^{-st} dt \\ \int_{t_1}^{t_2} f(t)\delta(t-a)dt &= \begin{cases} f(a) & t_1 < a < t_2 \\ 0 & a < t_1, a > t_2 \end{cases} \end{aligned} \right\} \rightarrow F(s) = e^{-as}$$

The Laplace Transform

1. Definition
2. Two Important Singularity Functions
- 3. Transform Pairs**
4. Properties of the Transform
5. Inverse Transform
6. Initial-Value & Final-Value Theorems
7. Laplace Circuit Solutions
8. Circuit Element Models
9. Analysis Techniques
10. Convolution Integral
11. Transfer Function



Ex. 1 Transform Pairs (1)

Find the Laplace transform of $f(t) = t$?

$$F(s) = \int_0^{\infty} t e^{-st} dt$$

$$\text{Let } u = t \text{ \& } dv = e^{-st} dt \rightarrow du = dt \text{ \& } v = \int e^{-st} dt = -\frac{1}{s} e^{-st}$$

$$\rightarrow F(s) = -\frac{t}{s} e^{-st} \Big|_0^{\infty} + \int_0^{\infty} \frac{e^{-st}}{s} dt = 0 - \frac{e^{-st}}{s} \Big|_0^{\infty} = \boxed{\frac{1}{s^2}}$$

Ex. 2

Transform Pairs (2)

Find the Laplace transform of $f(t) = \cos \omega t$?

$$\begin{aligned} F(s) &= \int_0^{\infty} \cos(\omega t) e^{-st} dt \\ &= \int_0^{\infty} \frac{e^{j\omega t} + e^{-j\omega t}}{2} e^{-st} dt \\ &= \int_0^{\infty} \frac{e^{-(s-j\omega)t} + e^{-(s+j\omega)t}}{2} dt \\ &= \frac{1}{2} \left(\frac{1}{s-j\omega} + \frac{1}{s+j\omega} \right) \\ &= \boxed{\frac{s}{s^2 + \omega^2}} \end{aligned}$$



Ex. 3 Transform Pairs (3)

Find the Laplace transform of $f(t) = \sin \omega t$?

Transform Pairs (4)

$f(t)$	$\delta(t)$	$u(t)$	e^{-at}	t	te^{-at}	$\sin at$	$\cos at$
$F(s)$	1	$\frac{1}{s}$	$\frac{1}{s+a}$	$\frac{1}{s^2}$	$\frac{1}{(s+a)^2}$	$\frac{a}{s^2+a^2}$	$\frac{s}{s^2+a^2}$

The Laplace Transform

1. Definition
2. Two Important Singularity Functions
3. Transform Pairs
- 4. Properties of the Transform**
5. Inverse Transform
6. Initial-Value & Final-Value Theorems
7. Laplace Circuit Solutions
8. Circuit Element Models
9. Analysis Techniques
10. Convolution Integral
11. Transfer Function

Properties of the Transform (1)

Property	$f(t)$	$F(s)$
1. Magnitude scaling	$Af(t)$	$AF(s)$
2. Addition/subtraction	$f_1(t) \pm f_2(t)$	$F_1(s) \pm F_2(s)$
3. Time scaling	$f(at)$	$\frac{1}{a} F\left(\frac{s}{a}\right)$
4. Time shifting	$f(t-a)u(t-a), a \geq 0$ $f(t)u(t-a), a \geq 0$	$e^{-as}F(s)$ $e^{-as}L[f(t+a)]$
5. Frequency shifting	$e^{-at}f(t)$	$F(s+a)$
6. Differentiation	$d^n f(t)/dt^n$	$s^n F(s) - s^{n-1}f(0) - s^{n-2}f'(0) \dots - s^0 f^{n-1}(0)$
7. Multiplication by t	$t^n f(t)$	$(-1)^n d^n F(s)/ds^n$
8. Division by t	$f(t)/t$	$\int_s^\infty F(\lambda)d\lambda$
9. Integration	$\int_0^t f(\lambda)d\lambda$	$F(s)/s$
10. Convolution	$f_1(t) * f_2(t) = \int_0^t f_1(\lambda)f_2(t-\lambda)d\lambda$	$F_1(s)F_2(s)$

Ex. 1 Properties of the Transform (2)

Find the Laplace transform of $f(t) = 5 + e^{-10t} - \cos 20t$?

$$f_1(t) \pm f_2(t) \rightarrow F_1(s) \pm F_2(s)$$

$$\rightarrow F(s) = L[5] + L[e^{-10t}] - L[\cos 20t]$$

$$Af(t) \rightarrow AF(s)$$

$$\rightarrow L[5] = 5L[1] \rightarrow L[5] = \frac{5}{s}$$

$$L[1] = \frac{1}{s}$$

$$L[e^{-10t}] = \frac{1}{s+10}$$

$$L[\cos 20t] = \frac{s}{s^2 + 20^2} = \frac{s}{s^2 + 400}$$


$$\rightarrow F(s) = \frac{5}{s} + \frac{1}{s+10} - \frac{s}{s^2 + 400} = \frac{5s^3 + 2400s + 4000}{s(s+10)(s^2 + 400)}$$

Ex. 2 Properties of the Transform (3)

Find the Laplace transform of the waveform?

$$f(t) = 5u(t-1) - 5u(t-2)$$

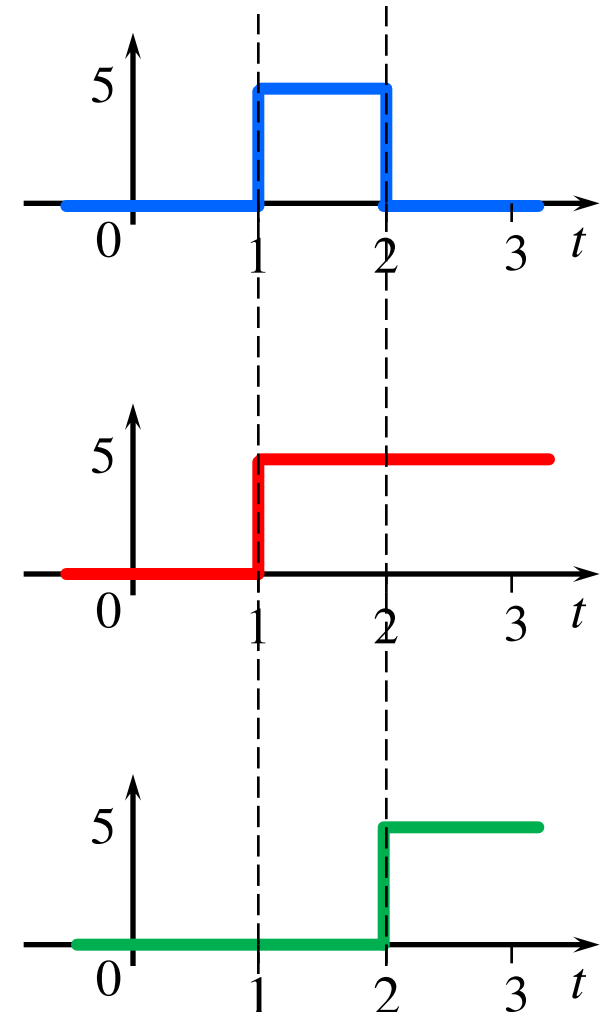
$$\rightarrow F(s) = 5\frac{e^{-s}}{s} - 5\frac{e^{-2s}}{s} = \frac{5}{s}(e^{-s} - e^{-2s})$$



Ex. 3 Properties of the Transform (4)

Find the Laplace transform of the waveform?


$$\begin{aligned}
 f(t) &= (-5t + 10)[u(t - 1) - u(t - 2)] \\
 &= -5tu(t - 1) + 10u(t - 1) + \\
 &\quad + 5tu(t - 2) - 10u(t - 2) \\
 -5tu(t - 1) &= -5(t - 1 + 1)u(t - 1) \\
 &= -5(t - 1)u(t - 1) - 5u(t - 1) \\
 5tu(t - 2) &= 5(t - 2 + 2)u(t - 2) \\
 &= 5(t - 2)u(t - 2) + 10u(t - 2) \\
 \rightarrow f(t) &= -5(t - 1)u(t - 1) - 5u(t - 1) + \\
 &\quad + 10u(t - 1) \\
 &\quad + 5(t - 2)u(t - 2) + 10u(t - 2) \\
 &\quad - 10u(t - 2)
 \end{aligned}$$

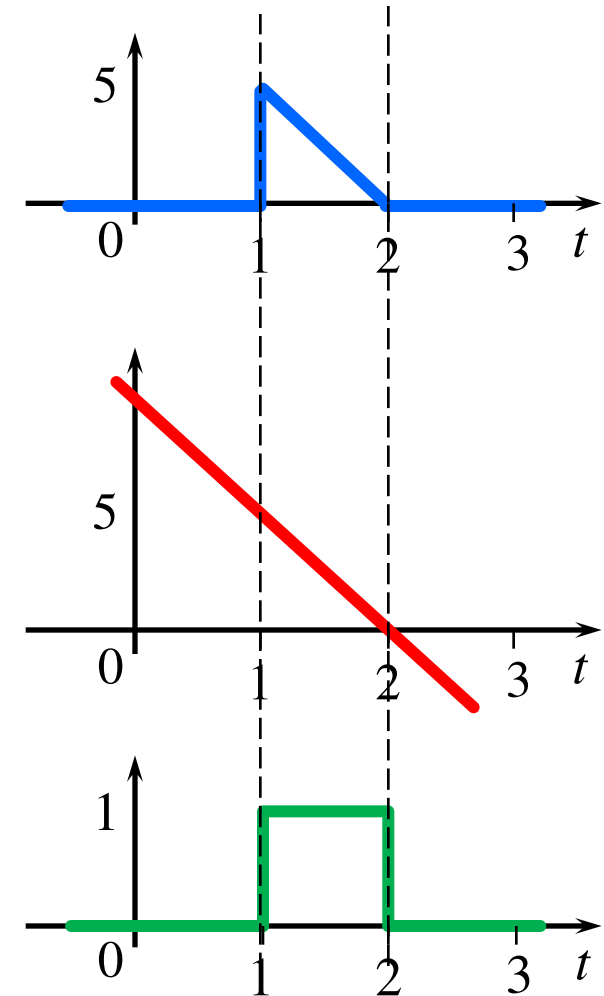

Ex. 3 Properties of the Transform (5)


Find the Laplace transform of the waveform?

$$\begin{aligned}
 f(t) &= (-5t + 10)[u(t - 1) - u(t - 2)] \\
 &= -5(t - 1)u(t - 1) - 5u(t - 1) + \\
 &\quad + 10u(t - 1) \\
 &\quad + 5(t - 2)u(t - 2) + 10u(t - 2) \\
 &\quad - 10u(t - 2) \\
 &= -5(t - 1)u(t - 1) + 5u(t - 1) + \\
 &\quad + 5(t - 2)u(t - 2) \\
 \rightarrow F(s) &= -5 \frac{e^{-s}}{s^2} + \frac{5}{s} e^{-s} + 5 \frac{e^{-2s}}{s^2} \\
 &= -\frac{5e^{-s}}{s^2} (1 - s - e^{-s})
 \end{aligned}$$

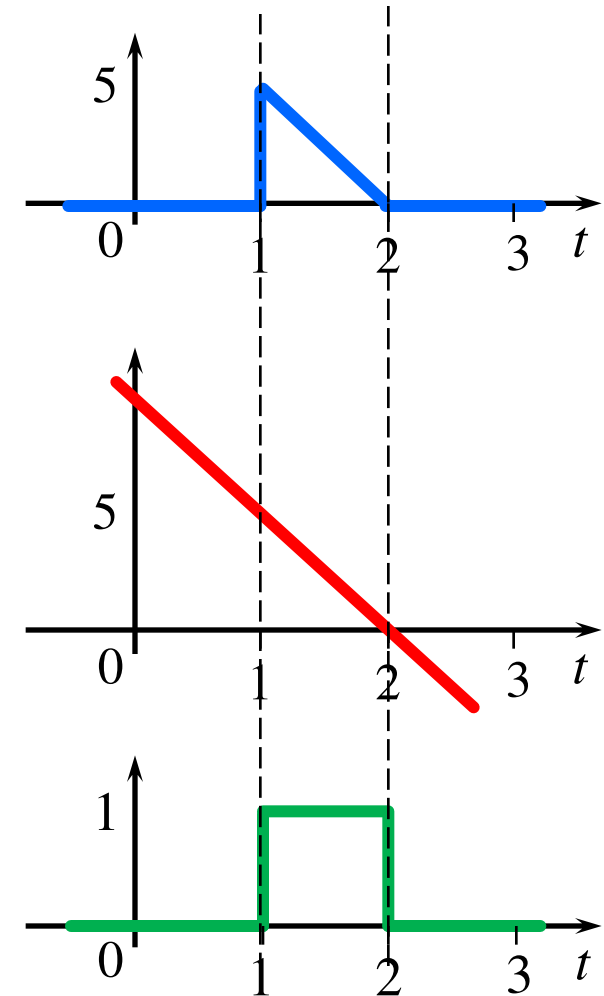

Ex. 4 Properties of the Transform (6)

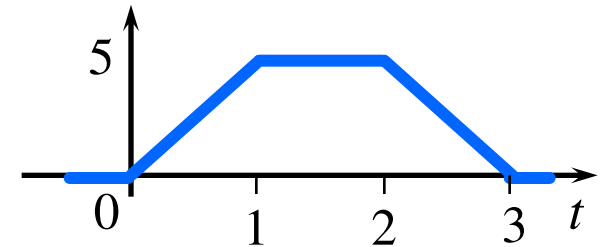Find the Laplace transform of the waveform?




The Laplace Transform

1. Definition
2. Two Important Singularity Functions
3. Transform Pairs
4. Properties of the Transform
- 5. Inverse Transform**
6. Initial-Value & Final-Value Theorems
7. Laplace Circuit Solutions
8. Circuit Element Models
9. Analysis Techniques
10. Convolution Integral
11. Transfer Function



The Laplace Transform

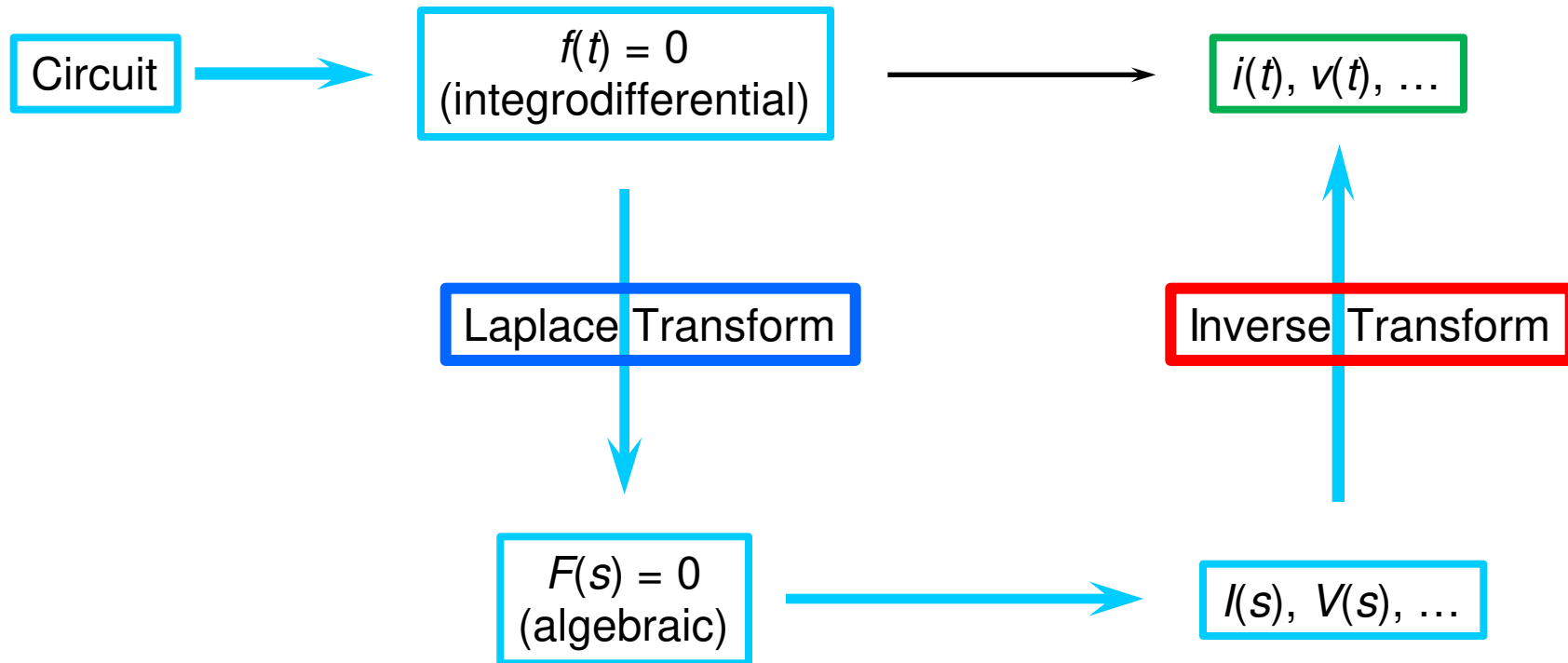

Inverse Transform (1)

$$F(s) = \frac{P(s)}{Q(s)} = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0}$$

Simple poles :
$$F(s) = \frac{K_1}{s + p_1} + \frac{K_2}{s + p_2} + \dots + \frac{K_n}{s + p_n}$$

Complex-conjugate poles :
$$F(s) = \frac{P_1(s)}{Q_1(s)(s + \alpha - j\beta)(s + \alpha + j\beta)}$$
$$= \frac{K_1}{s + \alpha - j\beta} + \frac{K_1^*}{s + \alpha + j\beta} + \dots$$

Multiple poles :
$$F(s) = \frac{P_1(s)}{Q_1(s)(s + p_1)^n}$$
$$= \frac{K_{11}}{(s + p_1)} + \frac{K_{12}}{(s + p_1)^2} + \dots + \frac{K_{1n}}{(s + p_1)^n} + \dots$$

Inverse Transform (2)

Simple poles : $F(s) = \frac{P(s)}{Q(s)} = \frac{K_1}{s + p_1} + \frac{K_2}{s + p_2} + \dots + \frac{K_n}{s + p_n}$

$$(s + p_i) \frac{P(s)}{Q(s)} \Big|_{s=-p_i} = 0 + \dots + 0 + K_i + 0 + \dots + 0$$

$$L^{-1} \left[\frac{K_i}{s + p_i} \right] = K_i e^{-p_i t}$$

$$f(t) = K_1 e^{-p_1 t} + K_2 e^{-p_2 t} + \dots + K_n e^{-p_n t}$$



Ex. 1 Inverse Transform (3)

Find the inverse Laplace transform of $F(s) = \frac{25s^2 + 300s + 640}{s(s+4)(s+8)}$

$$F(s) = \frac{K_1}{s} + \frac{K_2}{s+4} + \frac{K_3}{s+8}; \quad (s+p_i) \frac{P(s)}{Q(s)} \Big|_{s=p_i} = 0 + \dots + 0 + K_i + 0 + \dots + 0$$

$$K_1 = sF(s) \Big|_{s=0} = s \frac{25s^2 + 300s + 640}{s(s+4)(s+8)} \Big|_{s=0} = \frac{25s^2 + 300s + 640}{(s+4)(s+8)} \Big|_{s=0} = \frac{640}{4 \times 8} = 20$$

$$\begin{aligned} K_2 &= (s+4)F(s) \Big|_{s=-4} = (s+4) \frac{25s^2 + 300s + 640}{s(s+4)(s+8)} \Big|_{s=-4} = \frac{25s^2 + 300s + 640}{s(s+8)} \Big|_{s=-4} = \\ &= \frac{25(-4)^2 + 300(-4) + 640}{(-4)(-4+8)} = 10 \end{aligned}$$

**Ex. 1****Inverse Transform (4)**

Find the inverse Laplace transform of $F(s) = \frac{25s^2 + 300s + 640}{s(s+4)(s+8)}$

$$F(s) = \frac{K_1}{s} + \frac{K_2}{s+4} + \frac{K_3}{s+8}; \quad (s+p_i) \frac{P(s)}{Q(s)} \Big|_{s=p_i} = 0 + \dots + 0 + K_i + 0 + \dots + 0$$

$$K_1 = 20; \quad K_2 = 10$$

$$\begin{aligned} K_3 &= (s+8)F(s) \Big|_{s=-8} = (s+8) \frac{25s^2 + 300s + 640}{s(s+4)(s+8)} \Big|_{s=-8} = \frac{25s^2 + 300s + 640}{s(s+4)} \Big|_{s=-8} = \\ &= \frac{25(-8)^2 + 300(-8) + 640}{(-8)(-8+4)} = -5 \end{aligned}$$

$$\rightarrow F(s) = \frac{20}{s} + \frac{10}{s+4} - \frac{5}{s+8} \quad \rightarrow \boxed{f(t) = 20 + 10e^{-4t} - 5e^{-8t}}$$

Ex. 1

Inverse Transform (5)

Find the inverse Laplace transform of $F(s) = \frac{25s^2 + 300s + 640}{s(s+4)(s+8)}$

$$F(s) = \frac{K_1}{s} + \frac{K_2}{s+4} + \frac{K_3}{s+8}$$

$$K_1 = \frac{25s^2 + 300s + 640}{\cancel{s}(s+4)(s+8)} \Big|_{s=0} = \frac{25s^2 + 300s + 640}{(s+4)(s+8)} \Big|_{s=0} = \frac{640}{4 \times 8} = 20$$

$$K_2 = \frac{25s^2 + 300s + 640}{s \cancel{(s+4)}(s+8)} \Big|_{s=-4} = \frac{25s^2 + 300s + 640}{s(s+8)} \Big|_{s=-4} = 10$$

$$K_3 = \frac{25s^2 + 300s + 640}{s(s+4) \cancel{(s+8)}} \Big|_{s=-8} = \frac{25s^2 + 300s + 640}{s(s+4)} \Big|_{s=-8} = -5$$

$$\rightarrow F(s) = \frac{20}{s} + \frac{10}{s+4} - \frac{5}{s+8} \quad \rightarrow \boxed{f(t) = 20 + 10e^{-4t} - 5e^{-8t}}$$

Ex. 2 Inverse Transform (6)

Find the inverse Laplace transform of $F(s) = \frac{100(s+6)}{(s+1)(s+3)}$

Inverse Transform (7)

Complex-conjugate poles : $F(s) = \frac{P_1(s)}{Q_1(s)(s + \alpha - j\beta)(s + \alpha + j\beta)} = \frac{K_1}{s + \alpha - j\beta} + \frac{K_1^*}{s + \alpha + j\beta} + \dots$

$$(s + \alpha - j\beta) \left. \frac{P(s)}{Q(s)} \right|_{s = -\alpha + j\beta} = K_1 = |K_1| \angle \theta$$

$$K_1^* = |K_1| \angle -\theta$$

$$\rightarrow F(s) = \frac{|K_1| \angle \theta}{s + \alpha - j\beta} + \frac{|K_1| \angle -\theta}{s + \alpha + j\beta} + \dots = \frac{|K_1| e^{j\theta}}{s + \alpha - j\beta} + \frac{|K_1| e^{-j\theta}}{s + \alpha + j\beta} + \dots$$

$$\rightarrow f(t) = |K_1| e^{j\theta} e^{-(\alpha - j\beta)t} + |K_1| e^{-j\theta} e^{-(\alpha + j\beta)t} + \dots = |K_1| e^{-\alpha t} \left[e^{j(\beta t + \theta)} + e^{-j(\beta t + \theta)} \right] + \dots \left. \begin{array}{l} \\ e^{j\phi} = \cos \phi + j \sin \phi \end{array} \right\}$$

$$\rightarrow f(t) = |K_1| e^{-\alpha t} [\cos(\beta t + \theta) + j \sin(\beta t + \theta) + \cos(-\beta t - \theta) + j \sin(-\beta t - \theta)] + \dots$$

$$= \boxed{2|K_1| e^{-\alpha t} \cos(\beta t + \theta) + \dots}$$

Ex. 3 Inverse Transform (8)

Find the inverse Laplace transform of $F(s) = \frac{4s^2 + 76s}{(s+2)(s^2 + 6s + 25)}$

$$F(s) = \frac{K_1}{s+3-j4} + \frac{K_2}{s+3+j4} + \frac{K_3}{s+2}$$

$$K_1 = (s + \alpha - j\beta) \frac{P(s)}{Q(s)} \Big|_{s=-\alpha+j\beta} ; f(t) = 2|K_1|e^{-\alpha t} \cos(\beta t + \theta) + \dots$$

$$K_3 = (s+2) \left(\frac{4s^2 + 76s}{(s+2)(s^2 + 6s + 25)} \right) \Big|_{s=-2} = \frac{4s^2 + 76s}{s^2 + 6s + 25} \Big|_{s=-2} = -8$$

$$K_1 = (s+3-j4) \frac{4s^2 + 76s}{(s+2)(s^2 + 6s + 25)} \Big|_{s=-3+j4} = 6 - j8 = 10 \angle -53.1^\circ$$

$$\rightarrow f(t) = 2 \times 10 e^{-3t} \cos(4t - 53.1^\circ) - 8e^{-2t} = \boxed{20e^{-3t} \cos(4t - 53.1^\circ) - 8e^{-2t}}$$

Ex. 3

Inverse Transform (9)

Find the inverse Laplace transform of $F(s) = \frac{4s^2 + 76s}{(s+2)(s^2 + 6s + 25)}$

$$F(s) = \frac{K_1}{s+3-j4} + \frac{K_2}{s+3+j4} + \frac{K_3}{s+2}$$

$$K_3 = \frac{4s^2 + 76s}{\cancel{(s+2)}(s^2 + 6s + 25)} \Big|_{s=-2} = \frac{4s^2 + 76s}{s^2 + 6s + 25} \Big|_{s=-2} = -8$$

$$K_1 = \frac{4s^2 + 76s}{(s+2)\cancel{(s+3-j4)}\cancel{(s+3+j4)}} \Big|_{s=-3+j4} = 6 - j8 = 10 \angle -53.1^\circ$$

$$\rightarrow f(t) = 2 \times 10 e^{-3t} \cos(4t - 53.1^\circ) - 8e^{-2t} = \boxed{20e^{-3t} \cos(4t - 53.1^\circ) - 8e^{-2t}}$$

Ex. 4 Inverse Transform (10)

Find the inverse Laplace transform of $F(s) = \frac{5(s+2)}{s(s^2+4s+5)}$



Inverse Transform (11)

Multiple poles: $F(s) = \frac{P_1(s)}{Q_1(s)(s + p_1)^n} = \frac{K_{11}}{(s + p_1)} + \frac{K_{12}}{(s + p_1)^2} + \dots + \frac{K_{1n}}{(s + p_1)^n} + \dots$

$$(s + p_1)^n F(s) \Big|_{s=-p_1} = K_{1n}$$

$$\frac{d}{ds} [(s + p_1)^n F(s)] \Big|_{s=-p_1} = K_{1n-1}$$

$$\frac{d^2}{ds^2} [(s + p_1)^n F(s)] \Big|_{s=-p_1} = (2!) K_{1n-2}$$

$$K_{1j} = \frac{1}{(n-j)!} \frac{d^{n-j}}{ds^{n-j}} [(s + p_1)^n F(s)] \Big|_{s=-p_1}$$

Ex. 5

Inverse Transform (12)

Find the inverse Laplace transform of $F(s) = \frac{10s^2 + 34s + 27}{s(s+3)^2}$

$$F(s) = \frac{K_{11}}{s+3} + \frac{K_{12}}{(s+3)^2} + \frac{K_2}{s}; \quad K_{1j} = \frac{1}{(n-j)!} \frac{d^{n-j}}{ds^{n-j}} [(s+p_1)^n F(s)] \Big|_{s=-p_1}$$

$$K_{12} = (s+3)^2 F(s) \Big|_{s=-3} = (s+3)^2 \frac{10s^2 + 34s + 27}{s(s+3)^2} \Big|_{s=-3} = \frac{10s^2 + 34s + 27}{s} \Big|_{s=-3} = -5$$

$$K_{11} = \frac{d}{ds} [(s+3)^2 F(s)] \Big|_{s=-3} = \frac{d}{ds} \left(\frac{10s^2 + 34s + 27}{s} \right) \Big|_{s=-3} = \frac{s(20s + 34) - (10s^2 + 34s + 27)}{s^2} \Big|_{s=-3} = 7$$

$$K_2 = sF(s) \Big|_{s=0} = s \frac{10s^2 + 34s + 27}{s(s+3)^2} \Big|_{s=0} = 3$$

Ex. 5 Inverse Transform (13)

Find the inverse Laplace transform of $F(s) = \frac{10s^2 + 34s + 27}{s(s+3)^2}$

$$F(s) = \frac{K_{11}}{s+3} + \frac{K_{12}}{(s+3)^2} + \frac{K_2}{s}; \quad K_{1j} = \frac{1}{(n-j)!} \frac{d^{n-j}}{ds^{n-j}} [(s+p_1)^n F(s)] \Big|_{s=-p_1}$$

$$K_{11} = 7; K_{12} = -5; K_2 = 3$$

$$\rightarrow F(s) = \frac{7}{s+3} - \frac{5}{(s+3)^2} + \frac{3}{s}$$

$$\rightarrow \boxed{f(t) = 7e^{-3t} - 5te^{-3t} + 3}$$

Ex. 5 Inverse Transform (14)

Find the inverse Laplace transform of $F(s) = \frac{10s^2 + 34s + 27}{s(s+3)^2}$

$$F(s) = \frac{K_{11}}{s+3} + \frac{K_{12}}{(s+3)^2} + \frac{K_2}{s} = \frac{7}{s+3} - \frac{5}{(s+3)^2} + \frac{3}{s} \rightarrow f(t) = 7e^{-3t} - 5te^{-3t} + 3$$

$$K_2 = \frac{10s^2 + 34s + 27}{\cancel{s}(s+3)^2} \Big|_{s=0} = \frac{10s^2 + 34s + 27}{(s+3)^2} \Big|_{s=0} = 3$$

$$K_{12} = \frac{10s^2 + 34s + 27}{s \cancel{(s+3)^2}} \Big|_{s=-3} = \frac{10s^2 + 34s + 27}{s} \Big|_{s=-3} = -5$$

$$K_{11} = \left[\frac{d}{ds} \left(\frac{10s^2 + 34s + 27}{\cancel{(s+3)^2} s} \right) \right] \Big|_{s=-3} = \left[\frac{d}{ds} \left(\frac{10s^2 + 34s + 27}{s} \right) \right] \Big|_{s=-3}$$

$$= \frac{s(20s + 34) - (10s^2 + 34s + 27)}{s^2} \Big|_{s=-3} = 7$$

Ex. 6 Inverse Transform (15)

Find the inverse Laplace transform of $F(s) = \frac{5(s+3)}{(s+1)(s+2)^2}$

The Laplace Transform

1. Definition
2. Two Important Singularity Functions
3. Transform Pairs
4. Properties of the Transform
5. Inverse Transform
- 6. Initial-Value & Final-Value Theorems**
7. Laplace Circuit Solutions
8. Circuit Element Models
9. Analysis Techniques
10. Convolution Integral
11. Transfer Function



Initial-Value & Final-Value Theorems (1)

Initial– value theorem : $\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} sF(s)$

Final– value theorem : $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$



Ex. Initial-Value & Final-Value Theorems (2)

Find the initial and final values of $F(s) = \frac{5(s+1)}{s(s^2+2s+2)}$

$$f(0) = \lim_{s \rightarrow \infty} sF(s) = \lim_{s \rightarrow \infty} \frac{5(s+1)}{s^2+2s+2} = 0$$

$$f(\infty) = \lim_{s \rightarrow 0} sF(s) = \lim_{s \rightarrow 0} \frac{5(s+1)}{s^2+2s+2} = 2.5$$


The Laplace Transform

1. Definition
2. Two Important Singularity Functions
3. Transform Pairs
4. Properties of the Transform
5. Inverse Transform
6. Initial-Value & Final-Value Theorems
- 7. Laplace Circuit Solutions**
8. Circuit Element Models
9. Analysis Techniques
10. Convolution Integral
11. Transfer Function



Ex.

Laplace Circuit Solutions (1)

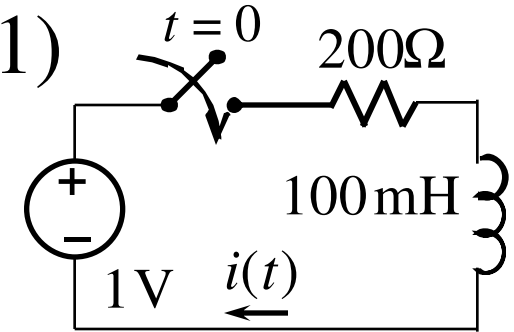

Find the current $i(t)$?

Method 1

$$v_L + v_R = e \rightarrow L \frac{di}{dt} + Ri = 1$$

$$L \frac{di_n}{dt} + Ri_n = 0 \rightarrow i_n = Ke^{-\alpha t} \rightarrow -LK\alpha e^{-\alpha t} + RKe^{-\alpha t} = 0 \rightarrow -L\alpha + R = 0$$

$$\rightarrow \alpha = \frac{R}{L} = \frac{200}{100 \times 10^{-3}} = 2000 \rightarrow i_n = Ke^{-2000t}$$


$$i_f = \frac{e}{R} = \frac{1}{200} = 0.005 \text{ A}$$

$$i = i_f + i_n = 0.005 + Ke^{-2000t}$$

$$i(0) = 0.005 + Ke^{-2000 \times 0} = 0.005 + K = 0 \rightarrow K = -0.005$$


$$\rightarrow i(t) = 0.005(1 - e^{-2000t}) \text{ A}$$

Laplace Circuit Solutions (2)

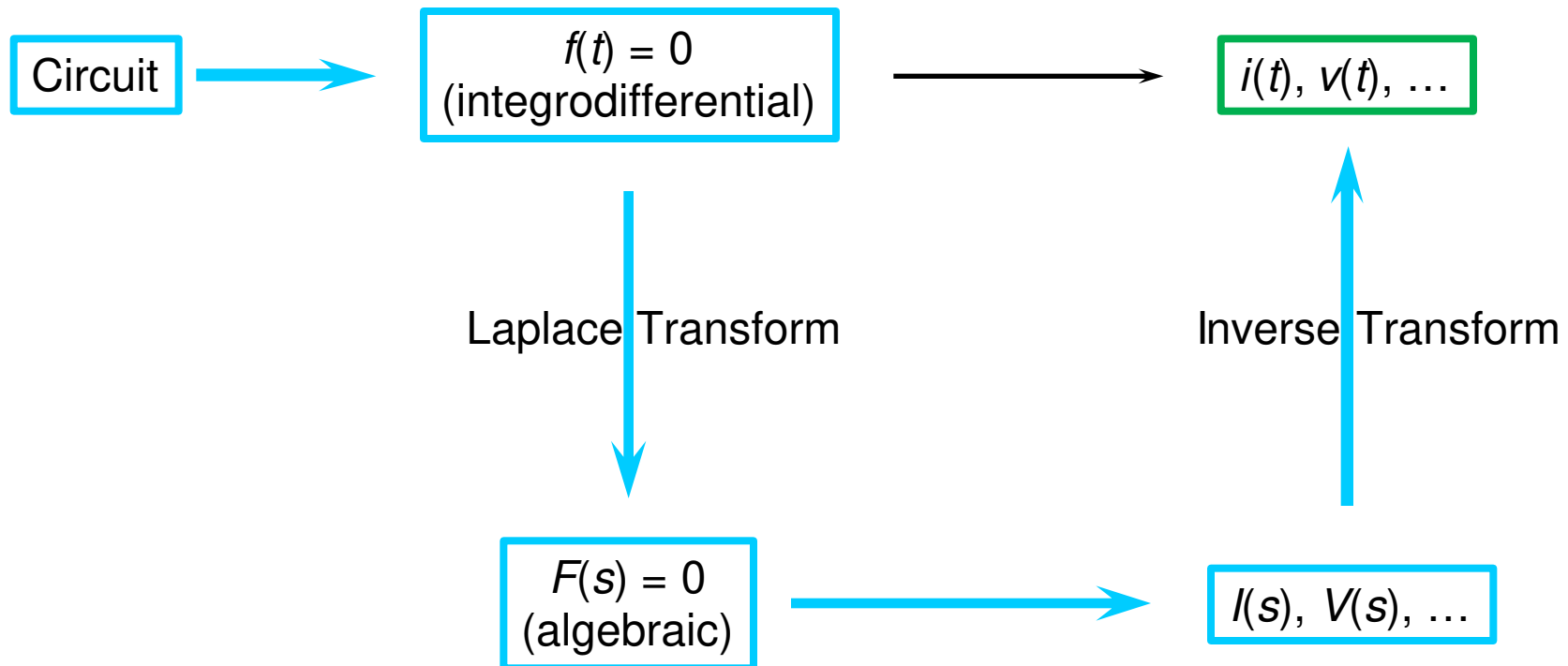

Ex.

Laplace Circuit Solutions (3)

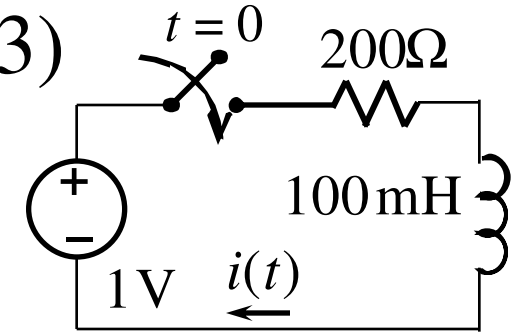

Find the current $i(t)$?

Method 2

$$v_L + v_R = e \rightarrow 0.1 \frac{di}{dt} + 200i = 1$$

$$L\left[0.1 \frac{di}{dt} + 200i\right] = L[1] = L\left[0.1 \frac{di}{dt}\right] + L[200i]$$

$$L[1] = \frac{1}{s}$$

$$L[200i] = 200I(s)$$


$$\frac{d^n f(t)}{dt^n} \rightarrow s^n F(s) - s^{n-1} f(0) - s^{n-2} f'(0) \dots - s^0 f^{n-1}(0)$$

$$\rightarrow L\left[0.1 \frac{di}{dt}\right] = 0.1[sI(s) - i(0)] = 0.1sI(s)$$

$$\rightarrow 0.1sI(s) + 200I(s) = \frac{1}{s}$$

Ex.

Laplace Circuit Solutions (4)

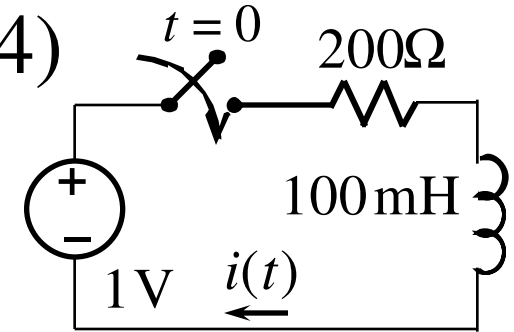

Find the current $i(t)$? **Method 2**

$$v_L + v_R = e \rightarrow 0.1 \frac{di}{dt} + 200i = 1$$


$$\rightarrow 0.1sI(s) + 200I(s) = \frac{1}{s}$$

$$\rightarrow I(s) = \frac{1}{s(0.1s + 200)} = \frac{10}{s(s + 2000)} = \frac{K_1}{s} + \frac{K_2}{s + 2000}$$

$$K_1 = \left. \frac{10}{s + 2000} \right|_{s=0} = 0.005$$

$$K_2 = \left. \frac{10}{s} \right|_{s=-2000} = -0.005$$
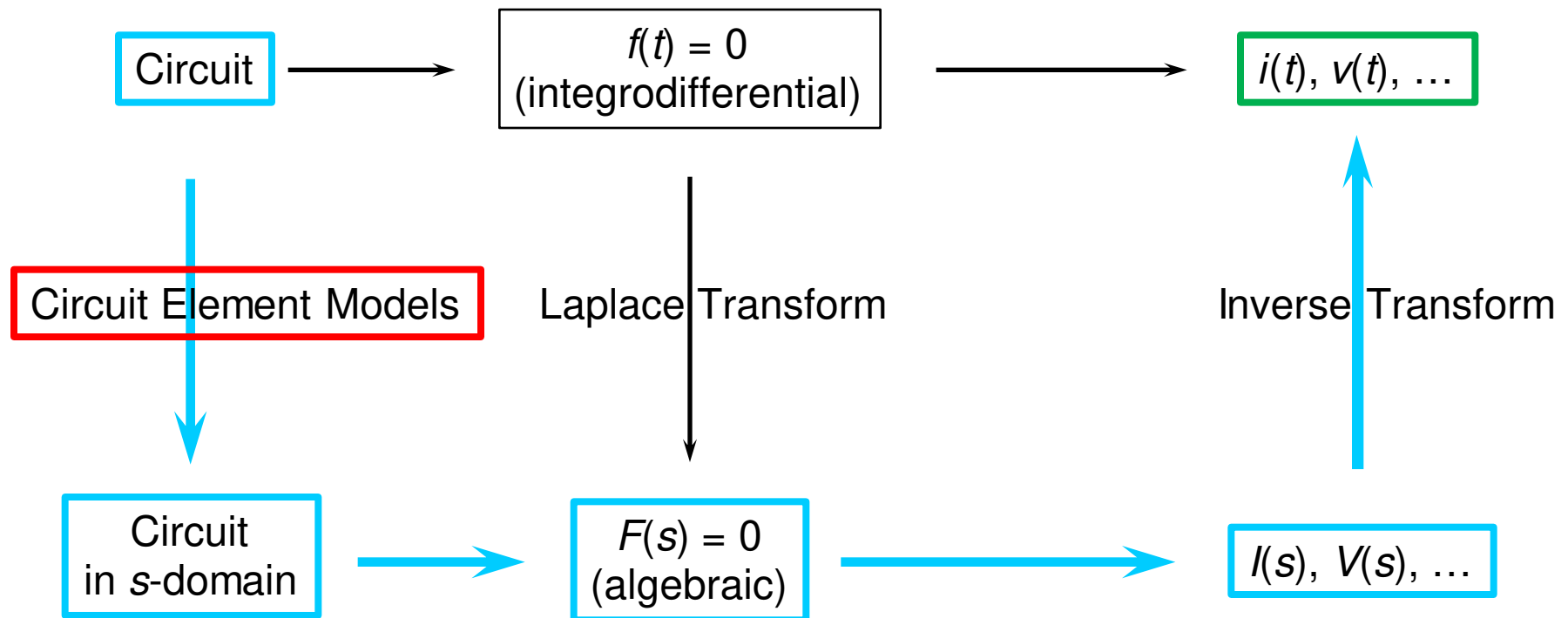
$$\rightarrow I(s) = \frac{0.005}{s} - \frac{0.005}{s + 2000} \rightarrow i(t) = 0.005(1 - e^{-2000t}) \text{ A}$$




The Laplace Transform

1. Definition
2. Two Important Singularity Functions
3. Transform Pairs
4. Properties of the Transform
5. Inverse Transform
6. Initial-Value & Final-Value Theorems
7. Laplace Circuit Solutions
- 8. Circuit Element Models**
9. Analysis Techniques
10. Convolution Integral
11. Transfer Function




Circuit Element Models (1)

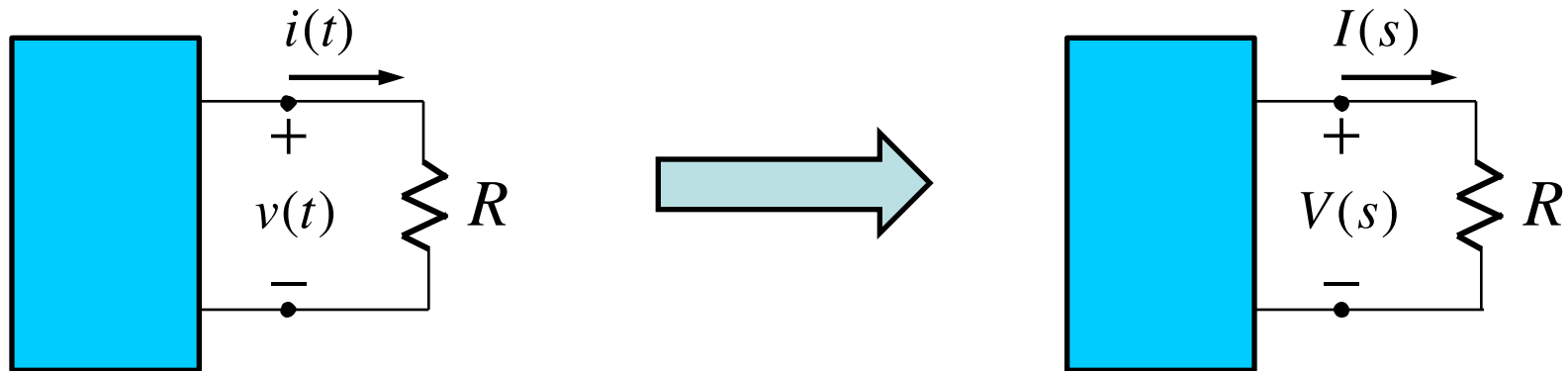

$$\left. \begin{array}{l} v = Ri \\ Af(t) \rightarrow AF(s) \end{array} \right\}$$


$$\rightarrow V(s) = RI(s)$$

Circuit Element Models (2)

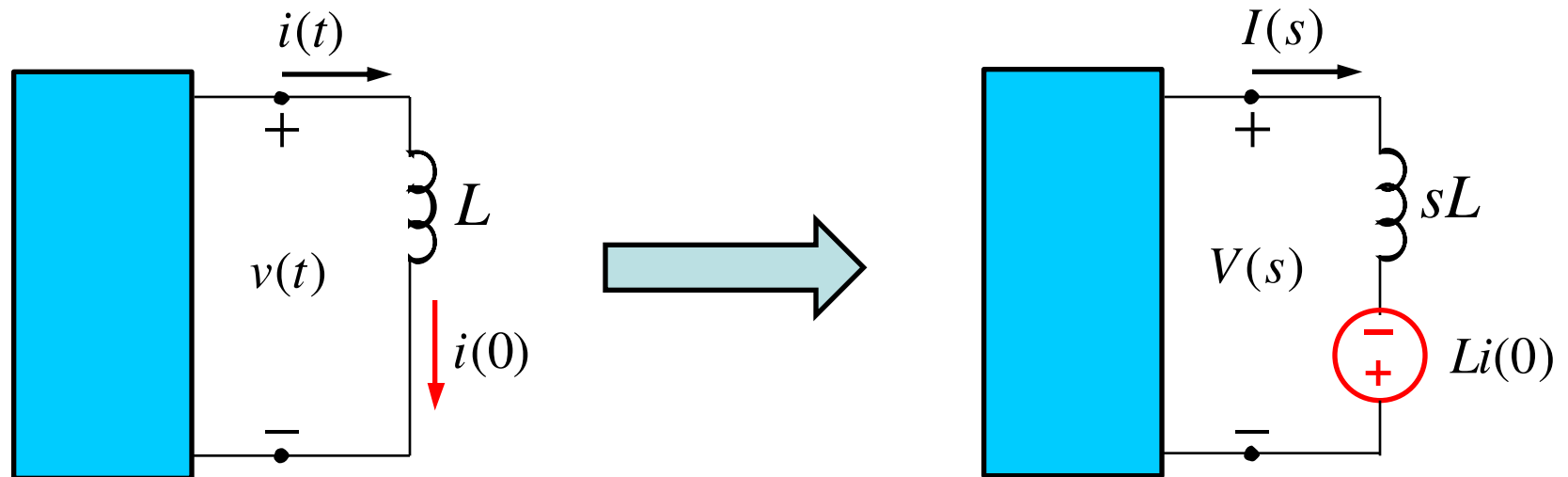

$$\left. \begin{aligned} v &= L \frac{di}{dt} \\ A \frac{df(t)}{dt} &\rightarrow A[sF(s) - f(0)] \end{aligned} \right\} \rightarrow \begin{aligned} V(s) &= L[sI(s) - i(0)] \\ &= sLI(s) - Li(0) \end{aligned}$$


Circuit Element Models (3)

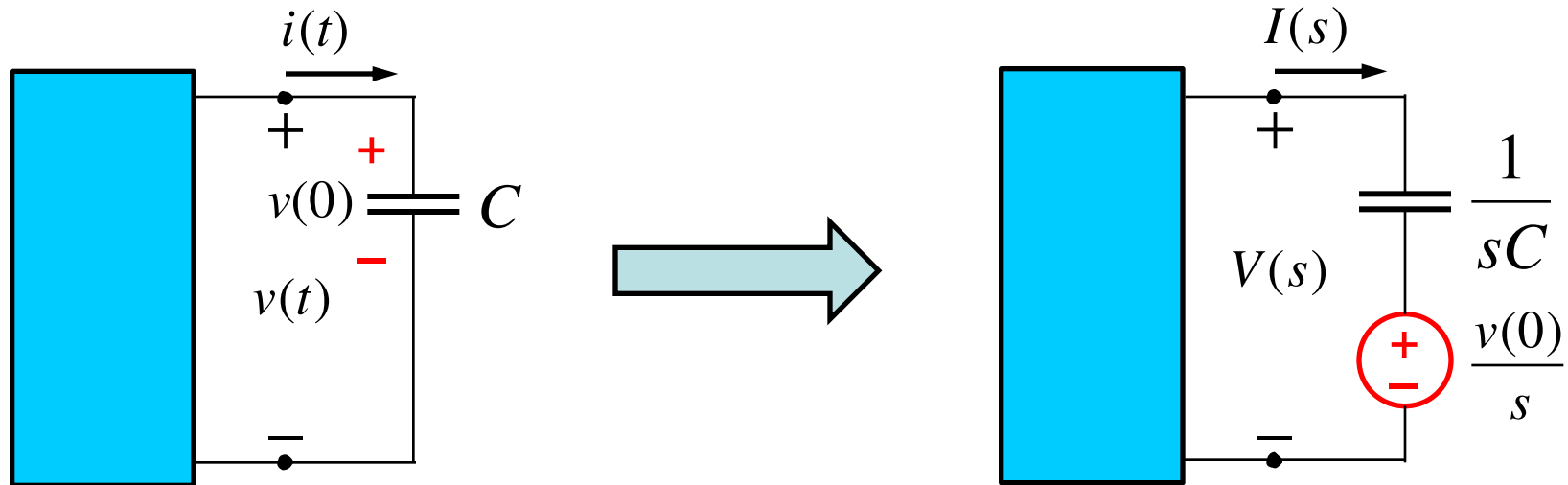

$$\left. \begin{aligned} v &= \frac{1}{C} \int_0^t i(x) dx + v(0) \\ \int_0^t f(\lambda) d\lambda &\rightarrow \frac{F(s)}{s} \\ v(0) &\rightarrow \frac{v(0)}{s} \end{aligned} \right\}$$

$$\rightarrow V(s) = \frac{1}{sC} I(s) + \frac{v(0)}{s}$$


Circuit Element Models (4)

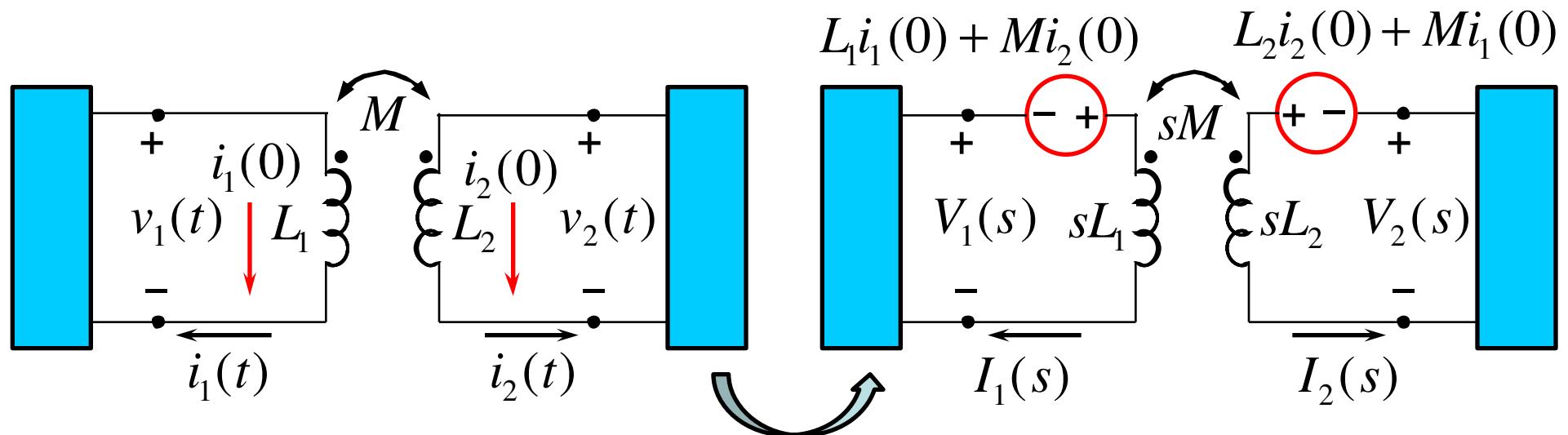

$$v_1(t) = L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt} \quad \rightarrow \quad V_1(s) = sL_1 I_1(s) - L_1 i_1(0) + sM I_2(s) - M i_2(0)$$



$$v_2(t) = L_2 \frac{di_2(t)}{dt} + M \frac{di_1(t)}{dt} \quad \rightarrow \quad V_2(s) = sL_2 I_2(s) - L_2 i_2(0) + sM I_1(s) - M i_1(0)$$

Circuit Element Models (5)


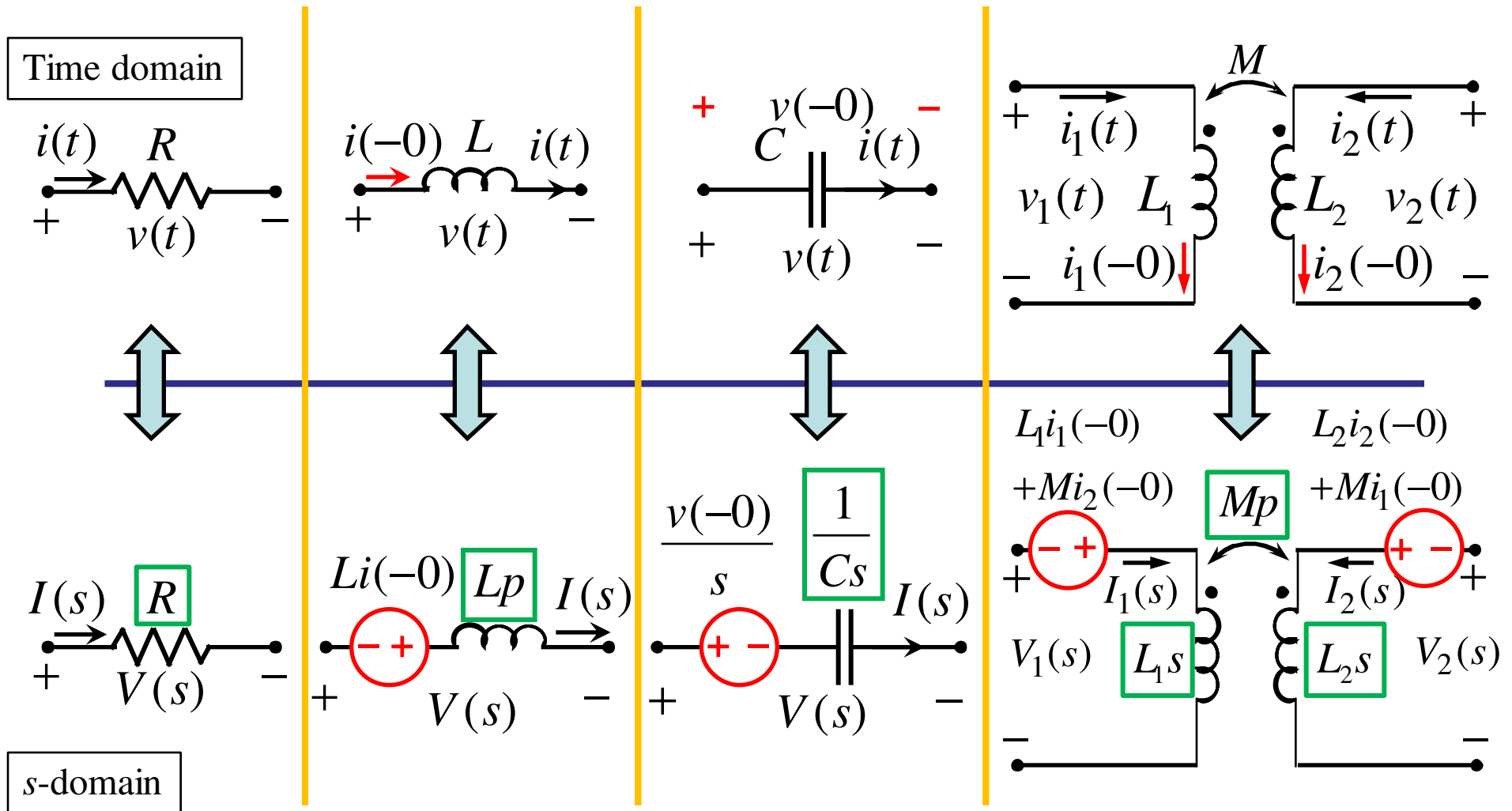


Circuit Element Models (6)



Ex. 1

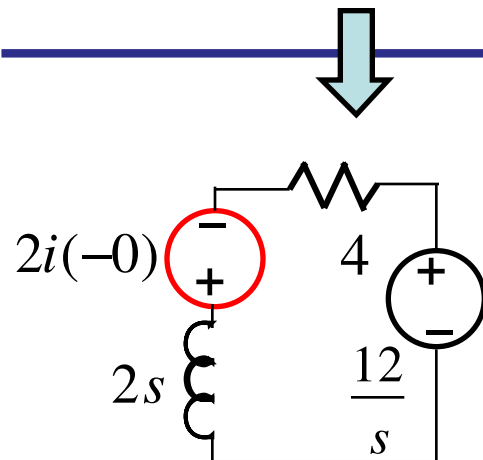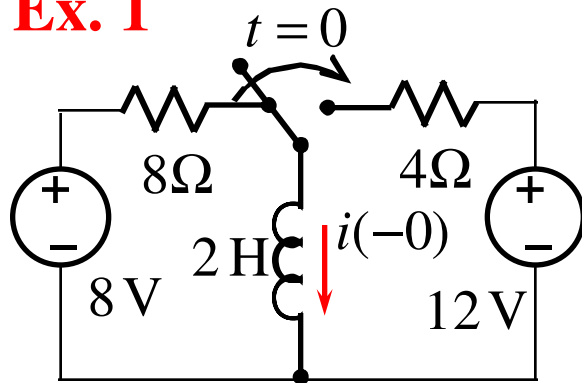

Ex. 2

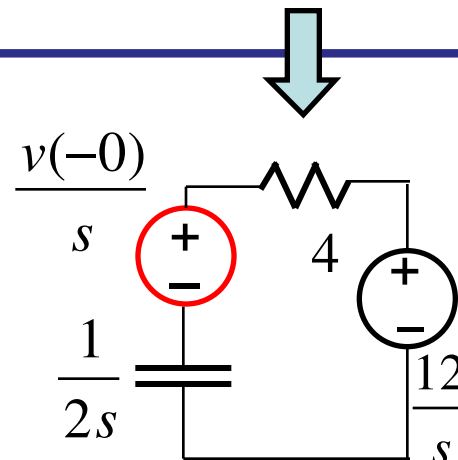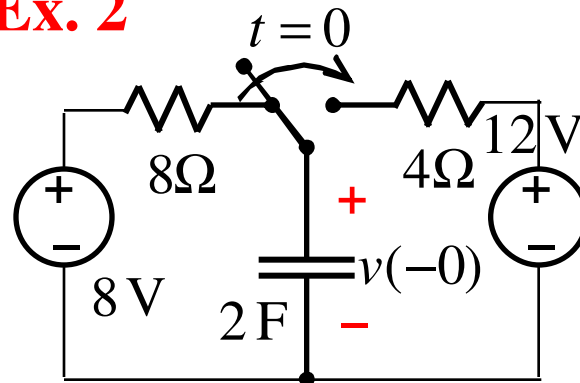


Ex. 3

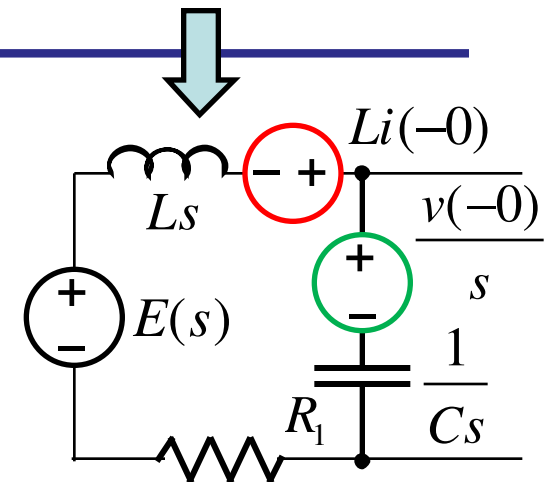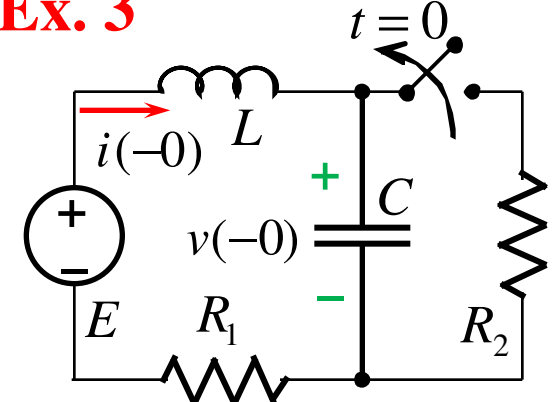

Ex. 4

Circuit Element Models (7)

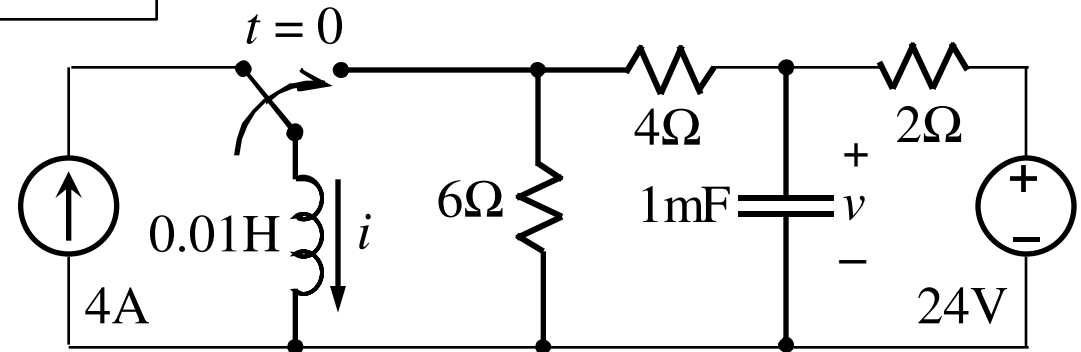Transfer the circuit into Laplace domain?



The Laplace Transform

1. Definition
2. Two Important Singularity Functions
3. Transform Pairs
4. Properties of the Transform
5. Inverse Transform
6. Initial-Value & Final-Value Theorems
7. Laplace Circuit Solutions
8. Circuit Element Models
- 9. Analysis Techniques**
10. Convolution Integral
11. Transfer Function




Analysis Techniques (1)

$$\text{KVL/KCL: } x_1(t) + x_2(t) + \dots + x_n(t) = 0$$





$$\text{KVL/KCL: } X_1(s) + X_2(s) + \dots + X_n(s) = 0$$

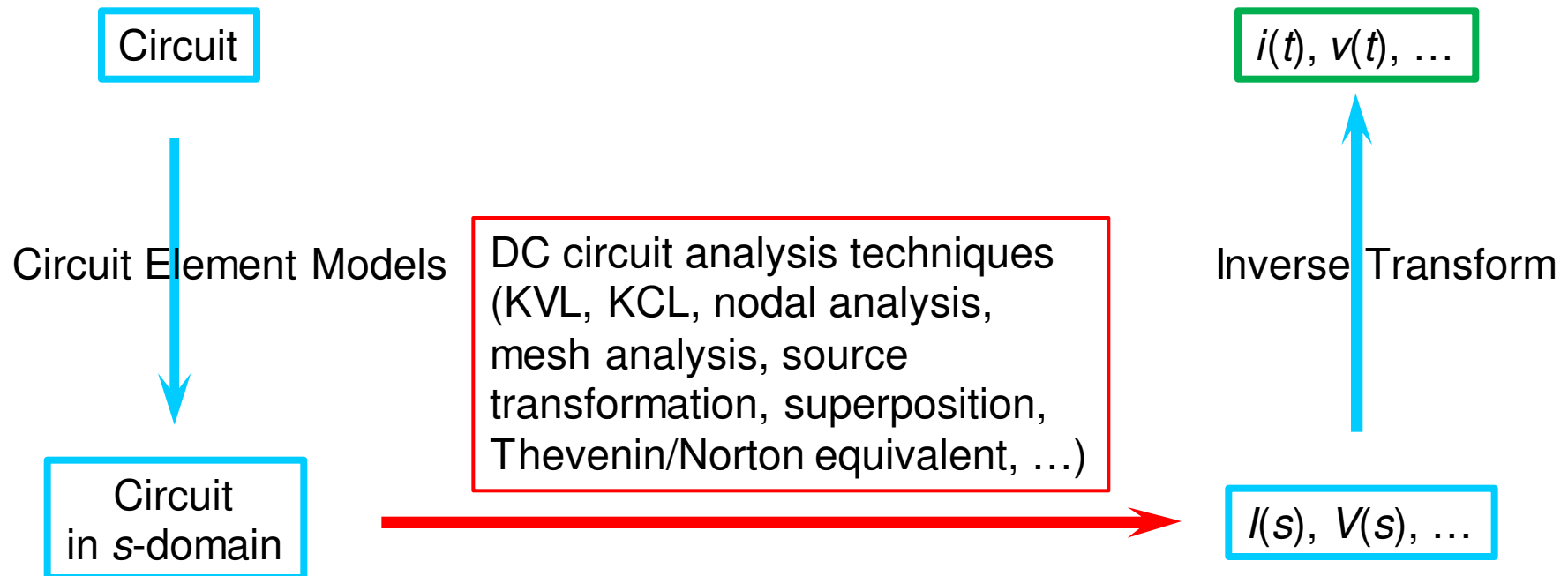

Ex. 1

Analysis Techniques (2)

Find the current $i(t)$?

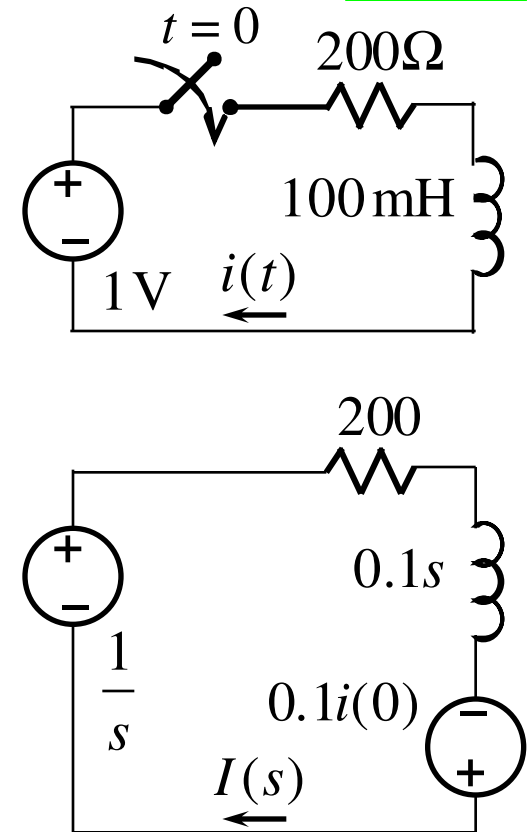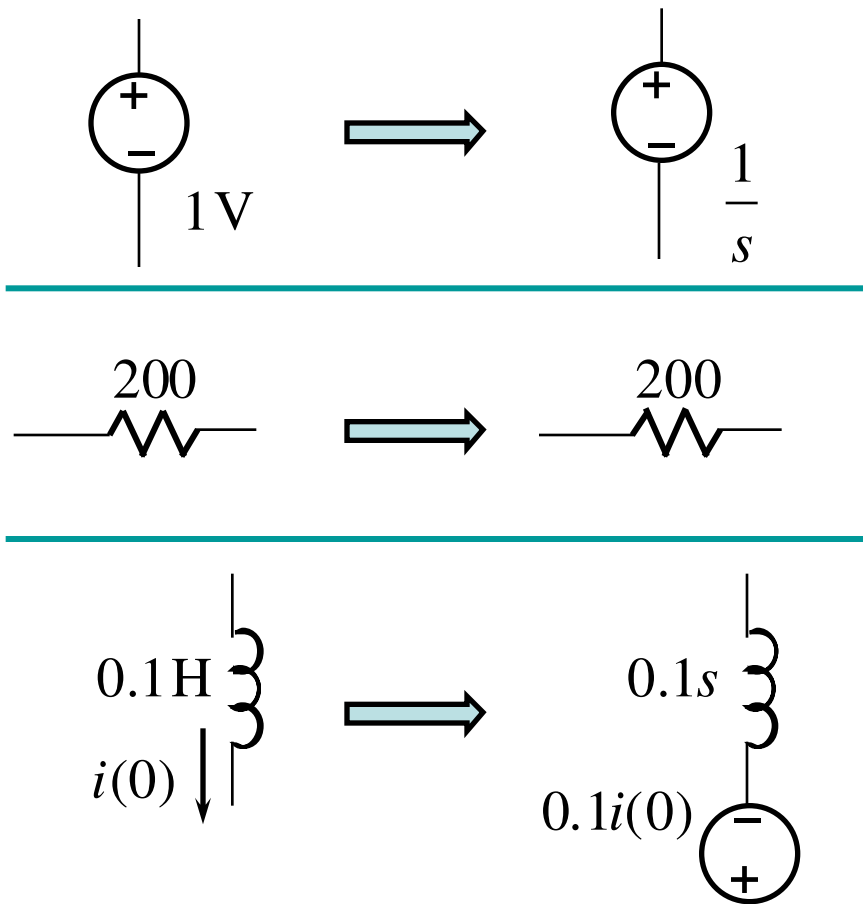

Ex. 1

Analysis Techniques (3)

Find the current $i(t)$?

$$i(0) = 0$$



$$200I(s) + 0.1sI(s) - 0.1i(0) = \frac{1}{s} = 200I(s) + 0.1sI(s)$$

$$\rightarrow I(s) = \frac{1}{s(0.1s + 200)} = \frac{10}{s(s + 2000)} = \frac{K_1}{s} + \frac{K_2}{s + 2000}$$

$$K_1 = \frac{10}{s + 2000} \Big|_{s=0} = 0.005$$

$$K_2 = \frac{10}{s} \Big|_{s=-2000} = -0.005$$


$$\rightarrow I(s) = \frac{0.005}{s} - \frac{0.005}{s + 2000} \rightarrow \boxed{i(t) = 0.005(1 - e^{-2000t}) \text{ A}}$$

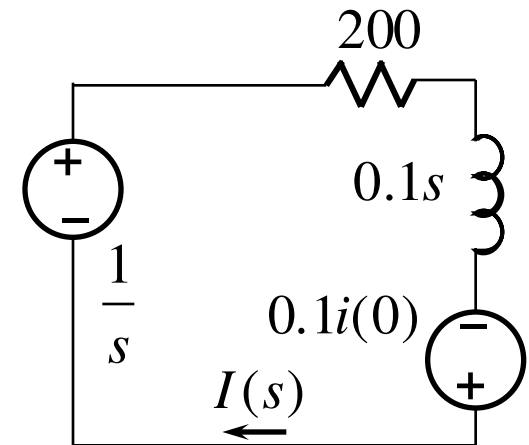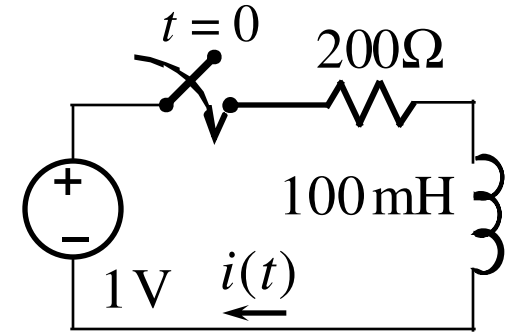

Ex. 1


Analysis Techniques (4)

Find the current $i(t)$?

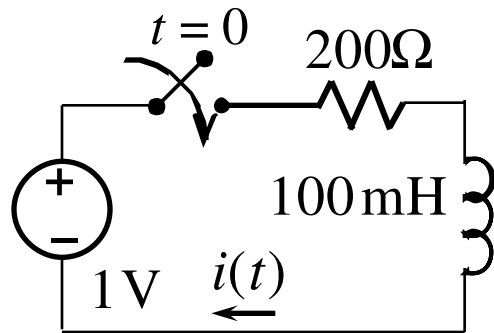

$$i(0) = 0$$

Circuit Element Models

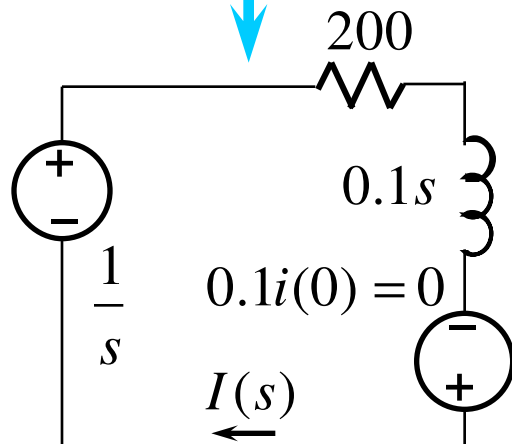

1. Solve for initial capacitor voltages & inductor currents
2. Draw an s -domain circuit
3. Use one of DC circuit analysis techniques to solve for voltages or/and currents in s -domain
4. Find the inverse Laplace transform to convert them back to the time domain

$$i(t) = 0.005(1 - e^{-2000t}) \text{ A}$$

Inverse Transform

$$200I(s) + 0.1sI(s) = \frac{1}{s} \rightarrow I(s) = \frac{10}{s(s + 2000)}$$

Ex. 2

Analysis Techniques (5)

Find the voltage $v(t)$?

$$v(0) = 0$$


$$V(s) = \left[R // \frac{1}{sC} \right] J(s) = \frac{10^4 \frac{1}{25 \times 10^{-6} s}}{10^4 + \frac{1}{25 \times 10^{-6} s}} \times \frac{5}{s+2}$$

$$= \frac{4 \times 10^4}{(s+2)(s+4)} = \frac{K_1}{s+2} + \frac{K_2}{s+4}$$

$$K_1 = \frac{4 \times 10^4}{s+4} \Big|_{s=-2} = 2 \times 10^4$$

$$K_2 = \frac{4 \times 10^4}{s+2} \Big|_{s=-4} = -2 \times 10^4$$
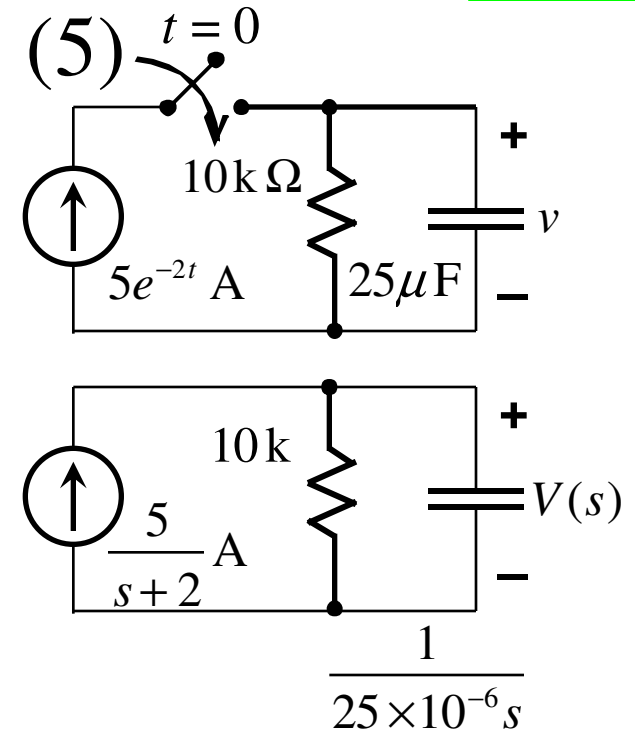
$$\rightarrow v(t) = 2 \times 10^4 (e^{-2t} - e^{-4t}) \text{ V}$$





1. ✓ Solve for initial capacitor voltages & inductor currents
2. ✓ Draw an s -domain circuit
3. ✓ Use one of DC circuit analysis techniques to solve for voltages or/and currents in s -domain
4. ✓ Find the inverse Laplace transform to convert them back to the time domain

Ex. 2

Analysis Techniques (6)

Find the voltage $v(t)$?

$$v(t) = 2 \times 10^4 (e^{-2t} - e^{-4t}) \text{ V}$$

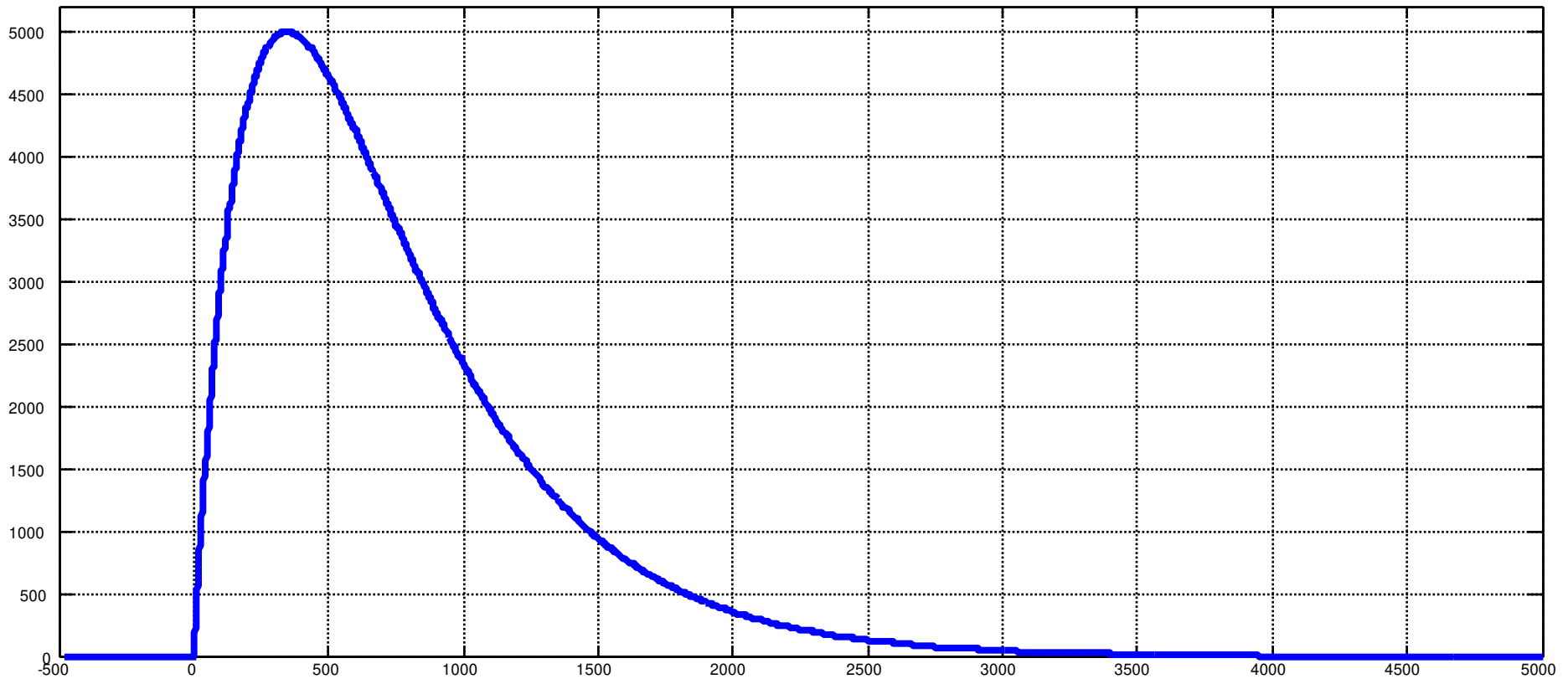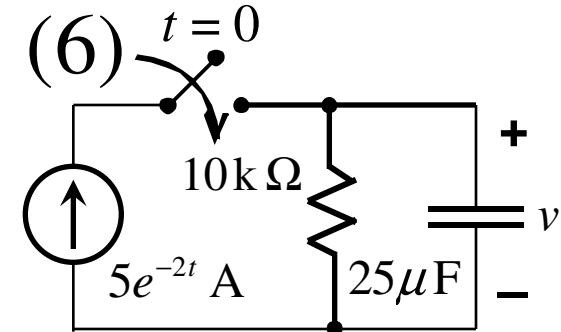

Ex. 3

Find the current $i(t)$?





$$i(0) = \frac{8}{8} = 1 \text{ A}$$

$$I(s) = \frac{2 + \frac{12}{s}}{2s + 4}$$

$$= \frac{s + 6}{s(s + 2)} = \frac{K_1}{s} + \frac{K_2}{s + 2}$$

$$K_1 = \left. \frac{s + 6}{s + 2} \right|_{s=0} = 3$$

$$K_2 = \left. \frac{s + 6}{s} \right|_{s=-2} = -2$$

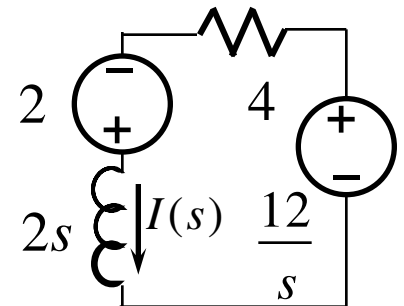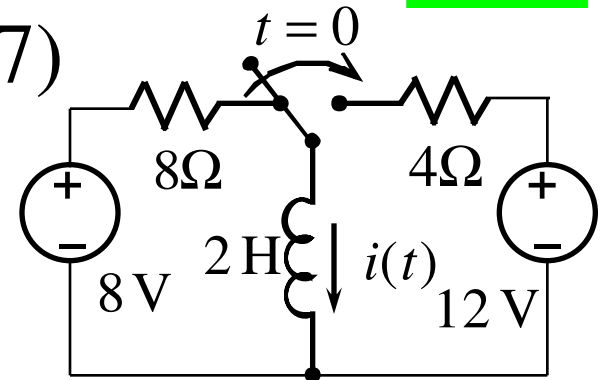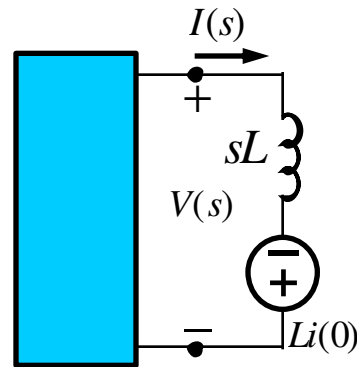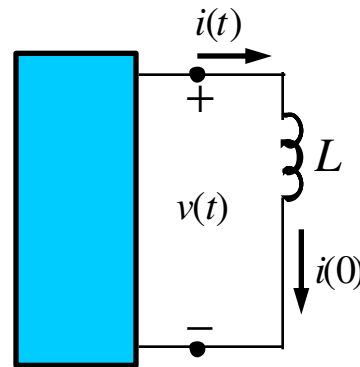

$$\rightarrow i(t) = 3 - 2e^{-2t} \text{ A}$$



1. ✓ Solve for initial capacitor voltages & inductor currents
2. ✓ Draw an s -domain circuit
3. ✓ Use one of DC circuit analysis techniques to solve for voltages or/and currents in s -domain
4. ✓ Find the inverse Laplace transform to convert them back to the time domain

Ex. 3

Find the current $i(t)$?

Analysis Techniques (8)

$$i(t) = 3 - 2e^{-2t} \text{ A}$$

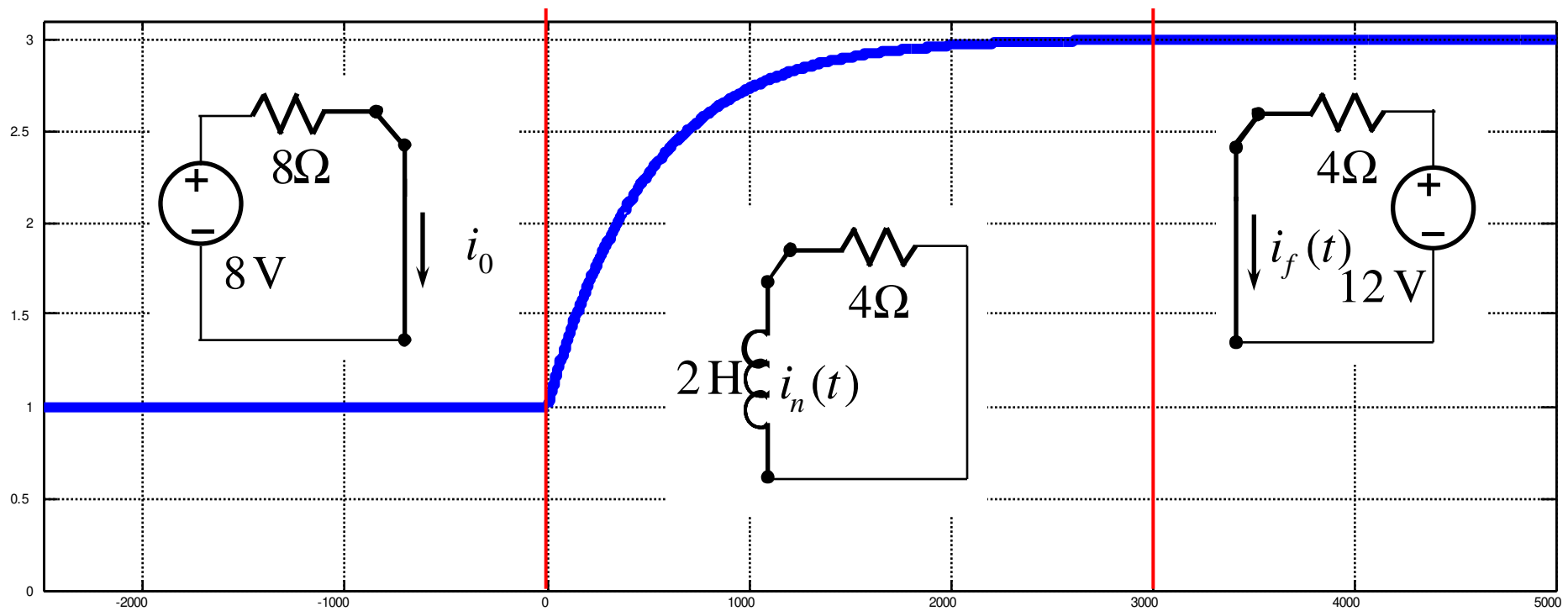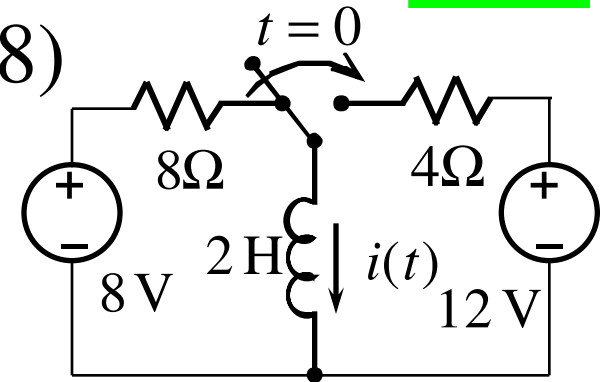

Ex. 4

Analysis Techniques (9)

Find the voltage $v(t)$?

$$v(0) = 8 \text{ V}$$




$$V(s) = \frac{1}{2s} \times \frac{\frac{12}{s} - \frac{8}{s}}{4 + \frac{1}{2s}} + \frac{8}{s}$$

$$= \frac{8s + 1.5}{s(s + 0.125)} = \frac{K_1}{s} + \frac{K_2}{s + 0.125}$$

$$K_1 = \frac{8s + 1.5}{s + 0.125} \Big|_{s=0} = 12$$

$$K_2 = \frac{0.5}{s} \Big|_{s=-0.125} = -4$$
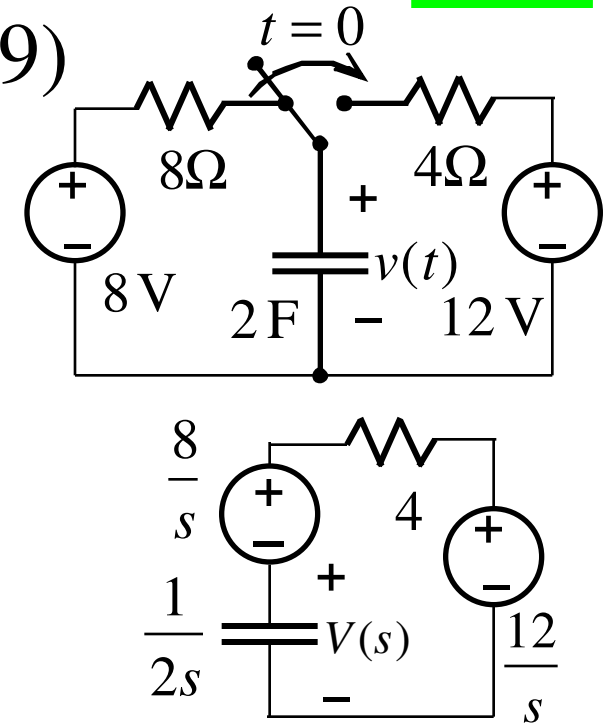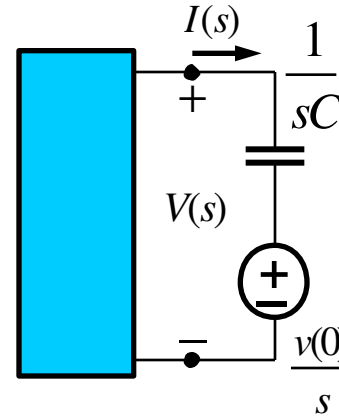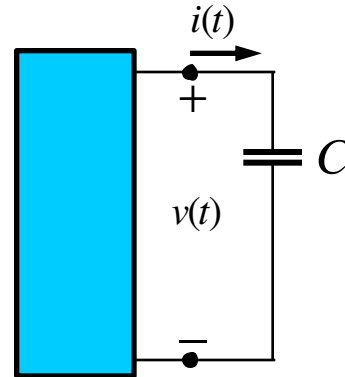
$$\rightarrow v(t) = 12 - 4e^{-0.125t} \text{ V}$$





1. ✓ Solve for initial capacitor voltages & inductor currents
2. ✓ Draw an s -domain circuit
3. ✓ Use one of DC circuit analysis techniques to solve for voltages or/and currents in s -domain
4. ✓ Find the inverse Laplace transform to convert them back to the time domain

Ex. 4

Find the voltage $v(t)$?

Analysis Techniques (10)




$$v(t) = 12 - 4e^{-0.125t} \text{ V}$$

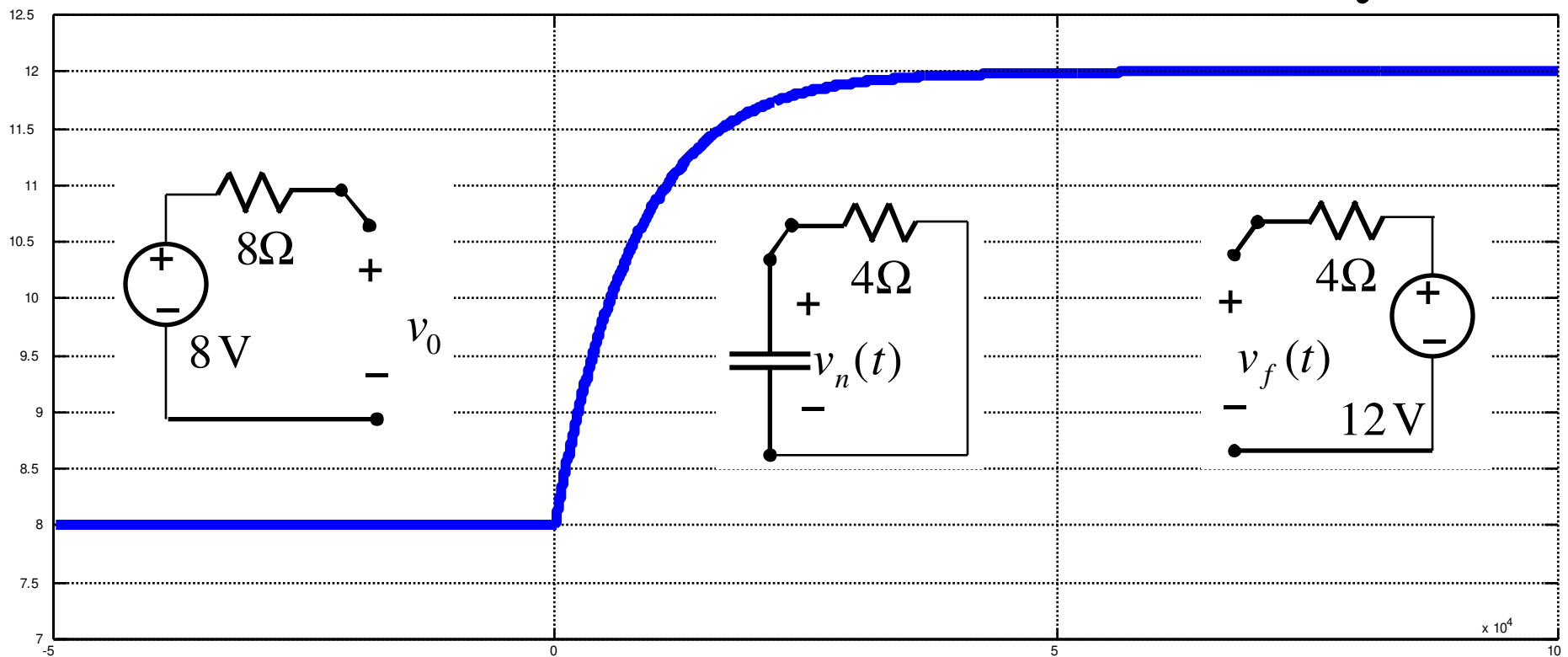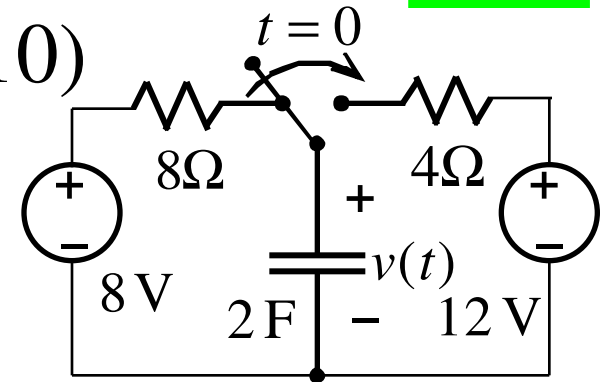

Ex. 5

Analysis Techniques (11)

Write the mesh equations in the s -domain?

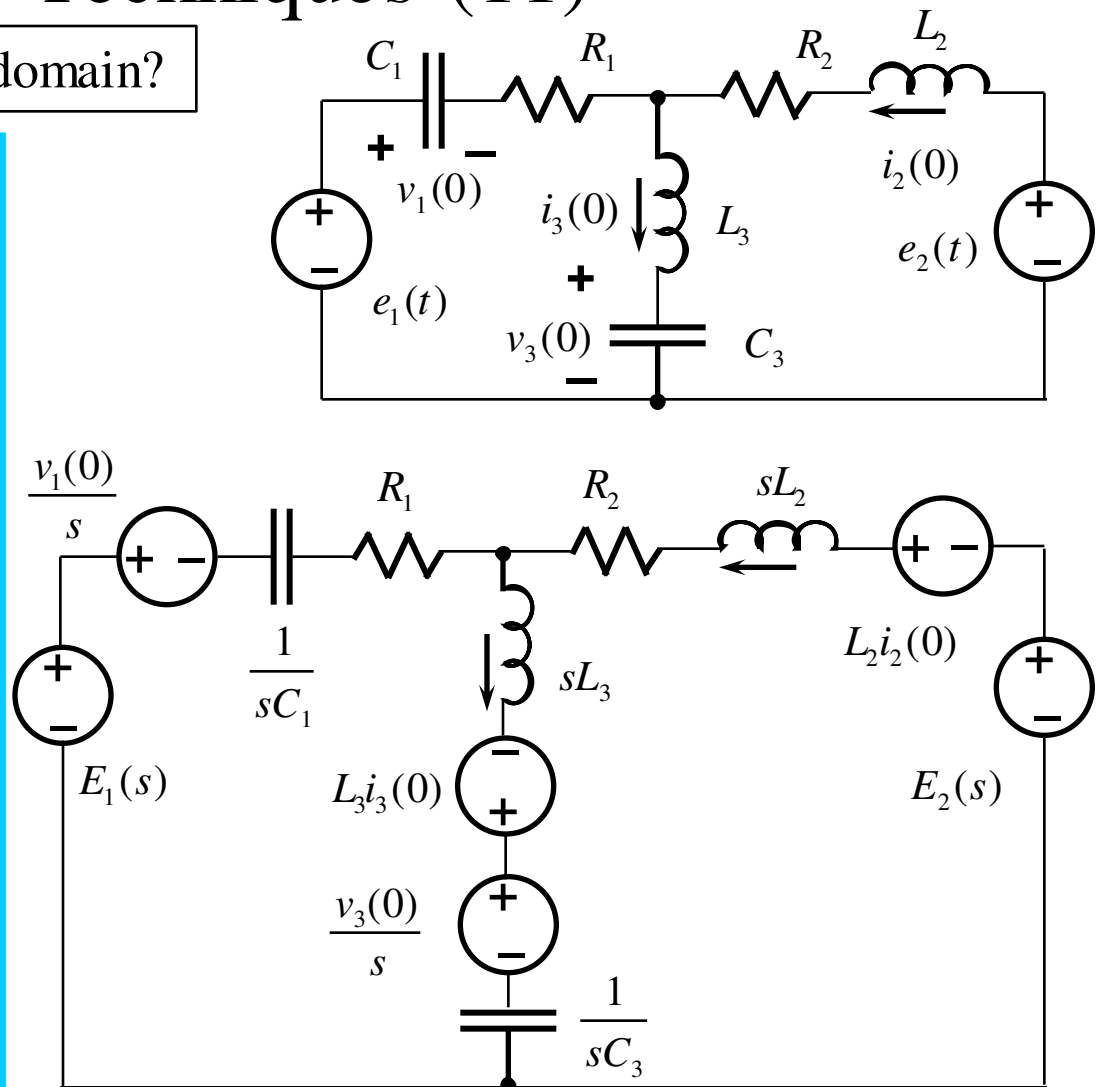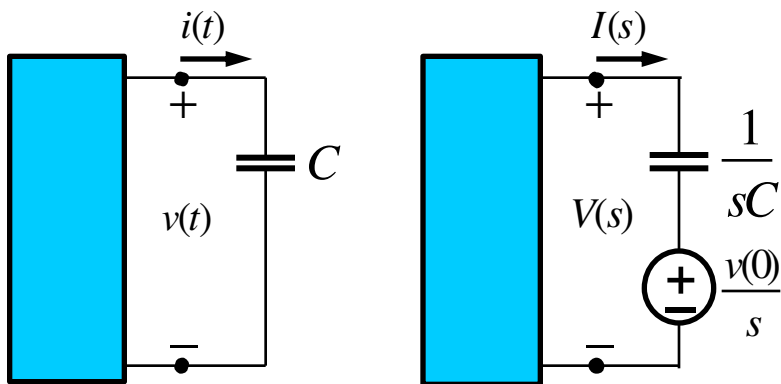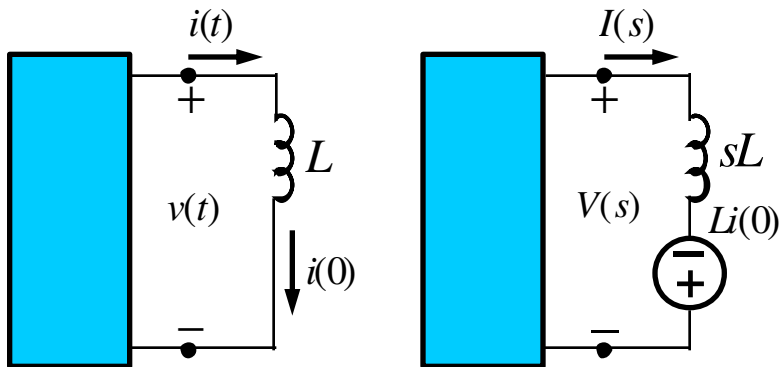



Ex. 5

Analysis Techniques (12)

Write the mesh equations in the s -domain?

$$A: \left(R_1 + \frac{1}{sC_1} \right) I_A(s) + \left(sL_3 + \frac{1}{sC_3} \right) [I_A(s) - I_B(s)] = E_1(s) - \frac{v_1(0)}{s} + L_3 i_3(0) - \frac{v_3(0)}{s}$$


$$B: (R_2 + sL_2) I_B(s) + \left(sL_3 + \frac{1}{sC_3} \right) [I_B(s) - I_A(s)] = \frac{v_3(0)}{s} - L_3 i_3(0) - L_2 i_2(0) - E_2(s)$$

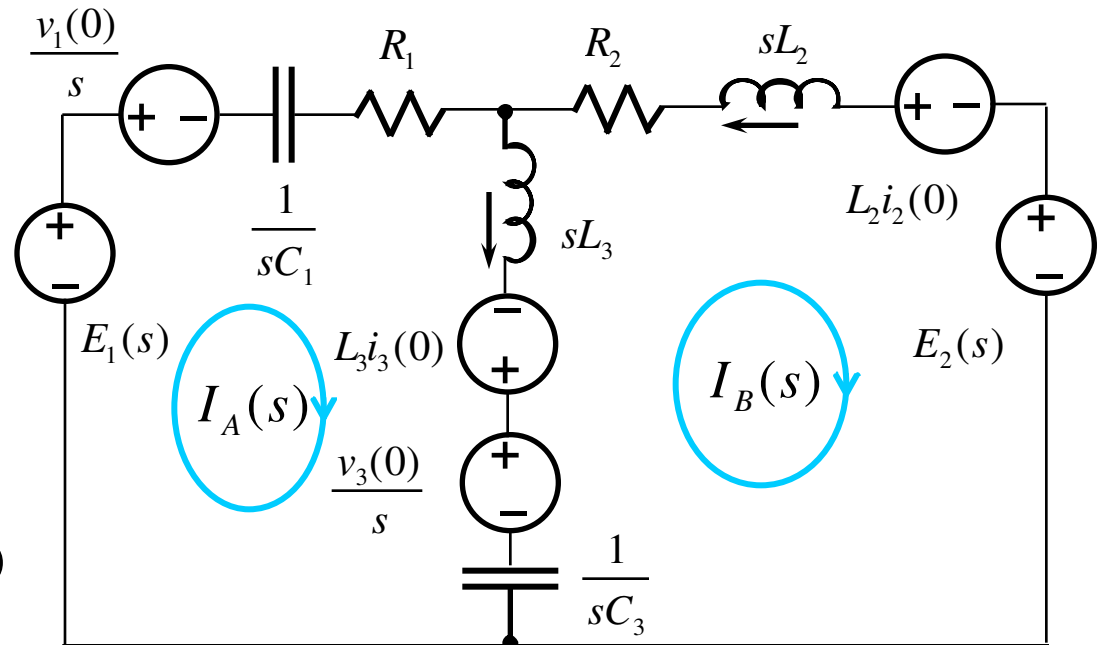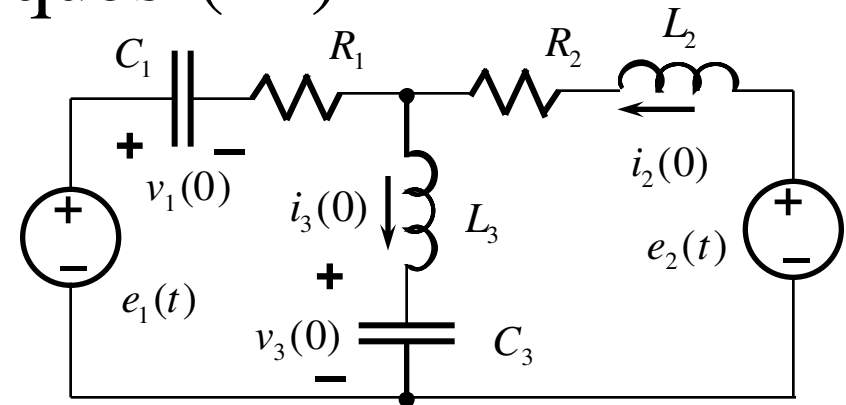

Ex. 6

Analysis Techniques (13)

Write the node equations in the s -domain?

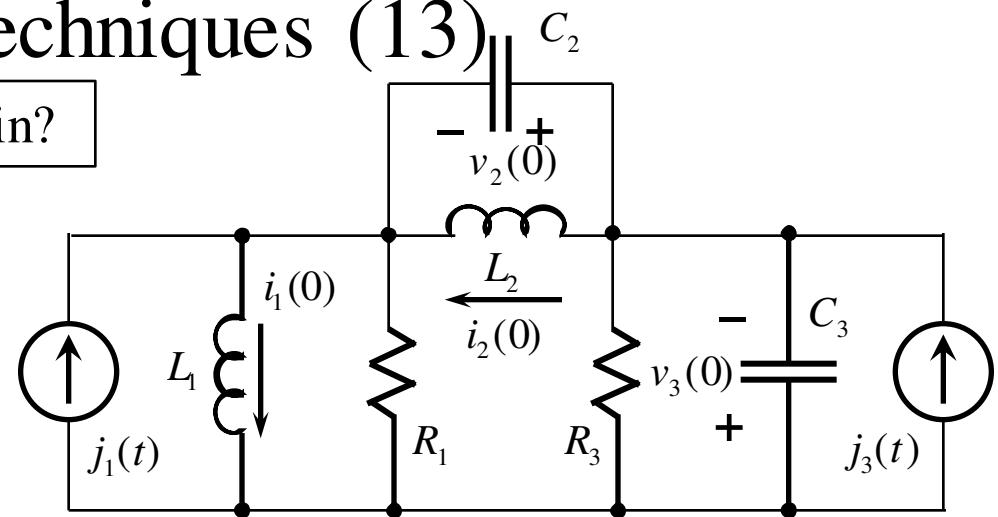

Ex. 7

Analysis Techniques (14)



Solve for $v(t)$? $i_L(0) = 0$; $v_C(0) = 0$;

$$a: \frac{5}{s} + \frac{\frac{15}{s} - V_a(s)}{s} - \frac{V_a(s)}{2 + \frac{1}{s}} = 0$$

$$\rightarrow V_a(s) = \frac{10s^2 + 35s + 15}{s^3 + 2s^2 + s}$$

$$\rightarrow V(s) = 2 \frac{V_a(s)}{2 + \frac{1}{s}} = 2 \frac{10s^2 + 35s + 15}{s^3 + 2s^2 + s} \times \frac{s}{2s + 1}$$

$$= \frac{10(s+3)}{(s+1)^2} = \frac{K_{11}}{s+1} + \frac{K_{12}}{(s+1)^2}$$

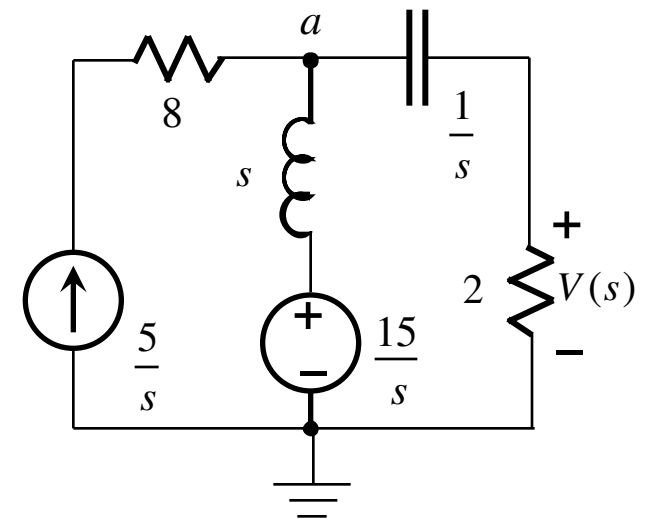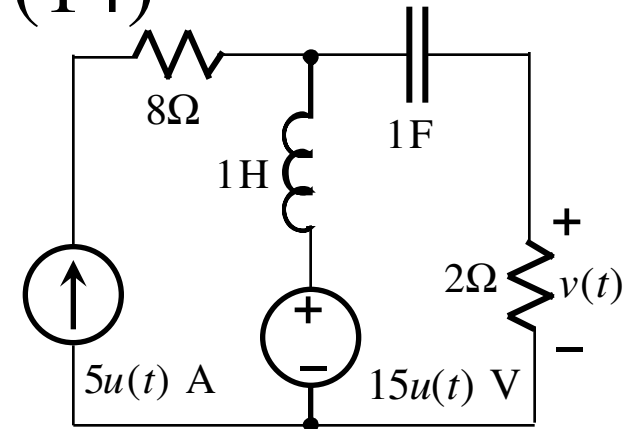

Ex. 7

Analysis Techniques (15)

Solve for $v(t)$?


Method 1

$$V(s) = \frac{10(s+3)}{(s+1)^2} = \frac{K_{11}}{s+1} + \frac{K_{12}}{(s+1)^2}$$

$$K_{12} = (s+1)^2 \frac{10(s+3)}{(s+1)^2} \Big|_{s=-1} = 10(s+3) \Big|_{s=-1} = 20$$

$$K_{11} = \frac{d}{ds} \left[(s+1)^2 \frac{10(s+3)}{(s+1)^2} \right] \Big|_{s=-1} = \frac{d}{ds} 10(s+3) \Big|_{s=-1} = 10$$

$$\rightarrow V(s) = \frac{10}{s+1} + \frac{20}{(s+1)^2} \rightarrow v(t) = \boxed{10(2t+1)e^{-t} \text{ V}}$$

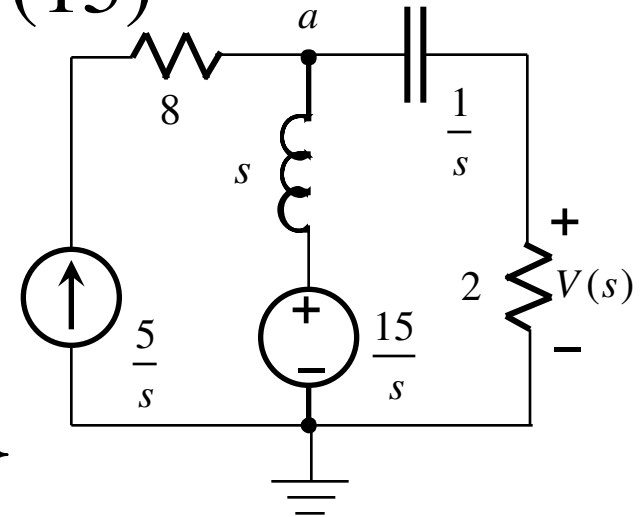


Ex. 7

Analysis Techniques (16)

Solve for $v(t)$?

Method 2

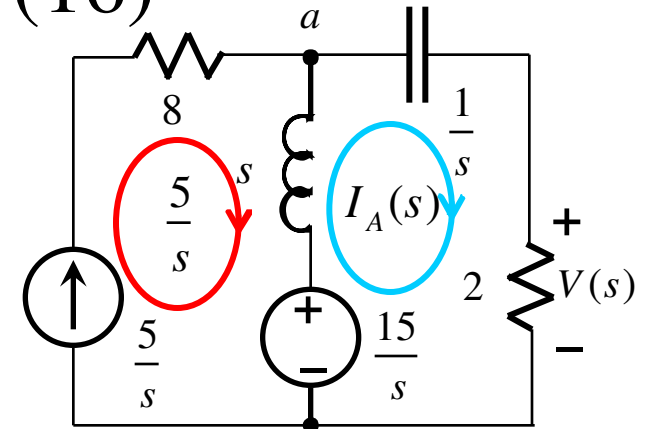

$$s \left[I_A(s) - \frac{5}{s} \right] + \left(2 + \frac{1}{s} \right) I_A(s) = \frac{15}{s}$$

$$\rightarrow I_A(s) = 5 \frac{s+3}{(s+1)^2}$$

$$\rightarrow V(s) = 10 \frac{s+3}{(s+1)^2}$$

Ex. 7



Analysis Techniques (17)

Solve for $v(t)$?

Method 3

$$V_{ab}(s) \Big|_{\frac{5}{s}} = \frac{s \left(2 + \frac{1}{s} \right)}{s + 2 + \frac{1}{s}} \times \frac{5}{s} = \frac{10(s + 0.5)}{(s + 1)^2}$$

$$\rightarrow V(s) \Big|_{\frac{5}{s}} = \frac{10(s + 0.5)}{(s + 1)^2} \times \frac{2}{2 + \frac{1}{s}} = \frac{10s}{(s + 1)^2}$$

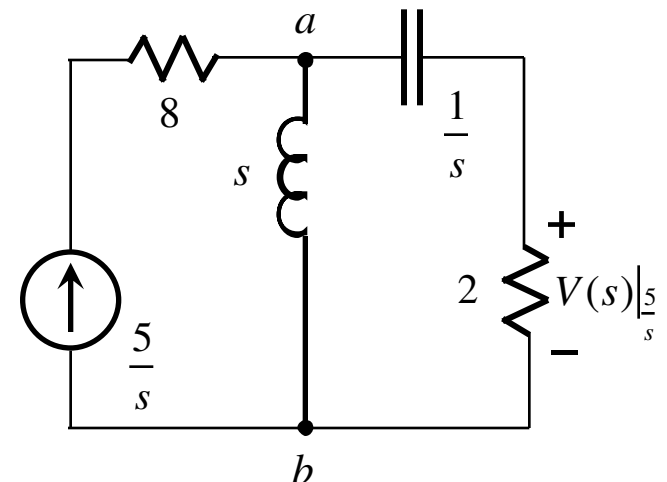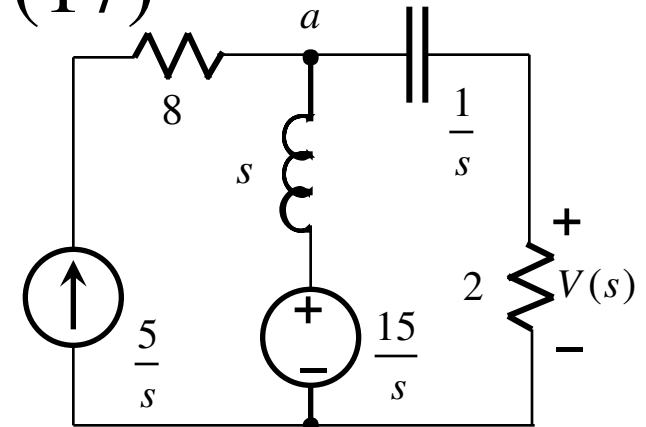

Ex. 7



Analysis Techniques (18)

Solve for $v(t)$?

Method 3

$$I_C(s) \Big|_{\frac{15}{s}} = \frac{\frac{15}{s}}{s + \frac{1}{s} + 2} = \frac{15}{(s+1)^2}$$

$$\rightarrow V(s) \Big|_{\frac{15}{s}} = 2 \frac{15}{(s+1)^2}$$

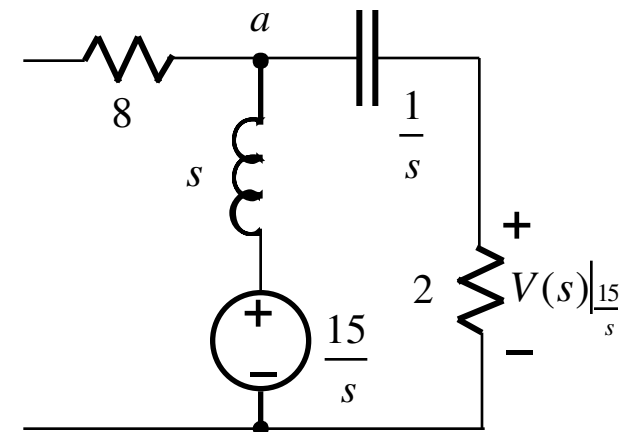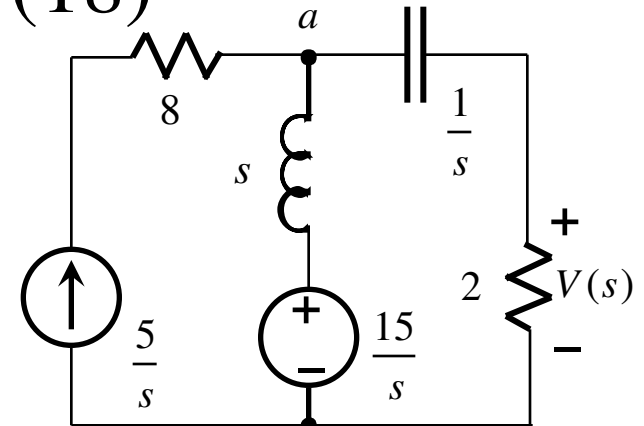


Ex. 7


Analysis Techniques (19)

Solve for $v(t)$?


Method 3

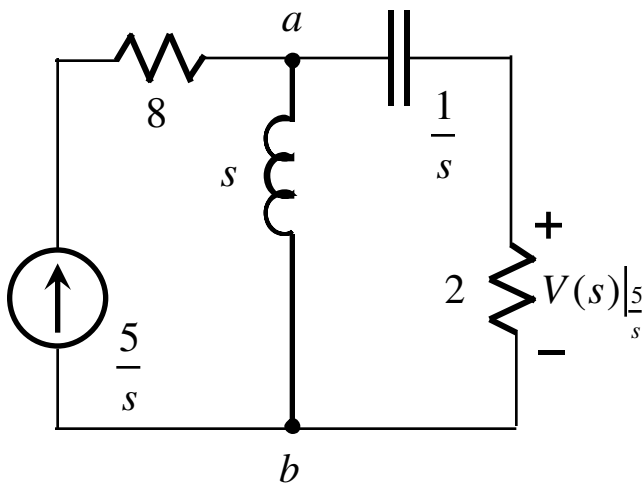

$$\rightarrow V(s)|_{\frac{5}{s}} = \frac{10s}{(s+1)^2}$$

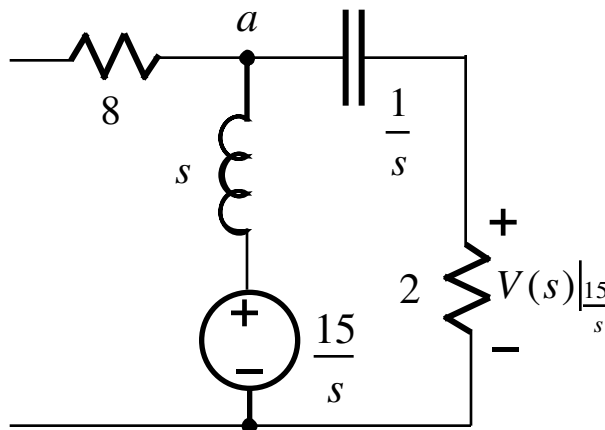

$$\rightarrow V(s)|_{\frac{15}{s}} = 2 \frac{15}{(s+1)^2}$$

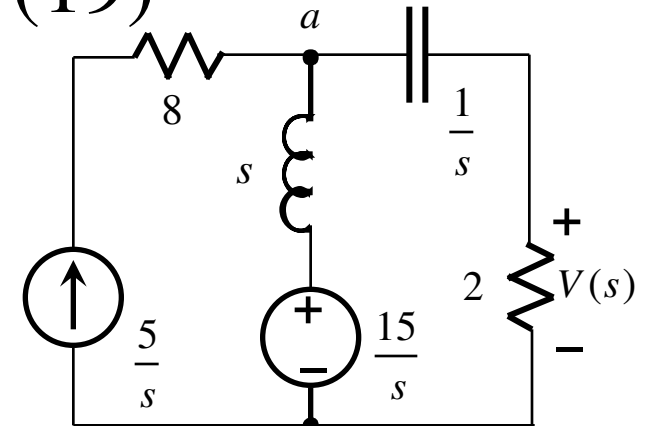

$$\begin{aligned}
 \rightarrow V(s) &= V(s)|_{\frac{5}{s}} + V(s)|_{\frac{15}{s}} \\
 &= \frac{10s}{(s+1)^2} + \frac{30}{(s+1)^2} \\
 &= \boxed{\frac{10(s+3)}{(s+1)^2}}
 \end{aligned}$$

Ex. 7

Analysis Techniques (20)

Solve for $v(t)$?



Method 4

$$Z(s) = s$$

$$E(s) = \left(\frac{5}{s} + \frac{15}{s^2} \right) s = 5 \frac{s+3}{s}$$

$$I(s) = \frac{5 \frac{s+3}{s}}{s + \frac{1}{s} + 2} = 5 \frac{s+3}{(s+1)^2}$$

$$V(s) = 2 \times 5 \frac{s+3}{(s+1)^2} = \boxed{10 \frac{s+3}{(s+1)^2}}$$

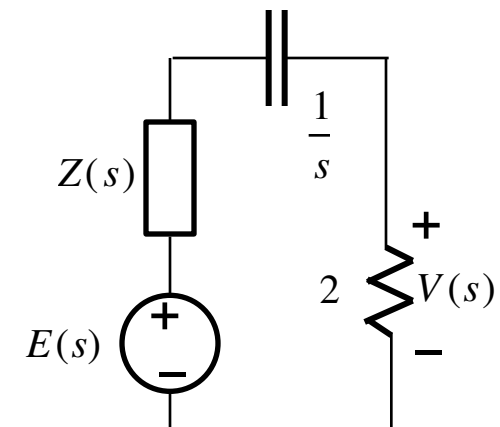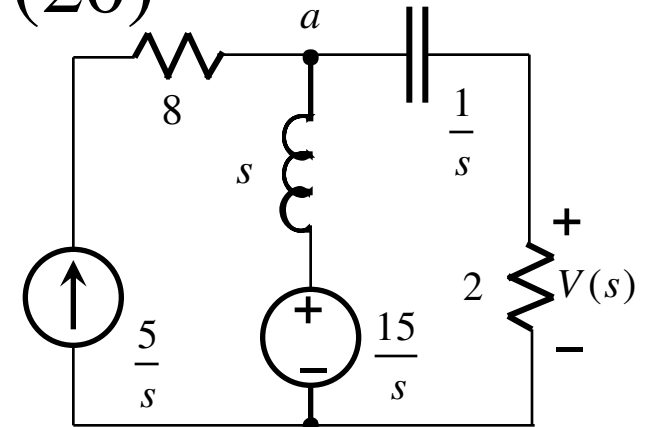


Ex. 7

Analysis Techniques (21)

Solve for $v(t)$?


Method 5

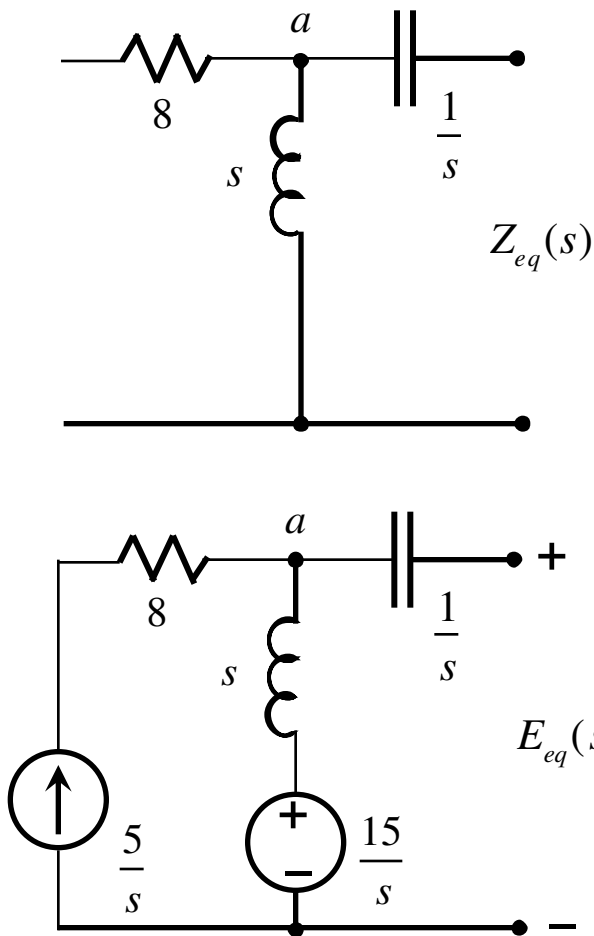

$$Z_{eq}(s) = s + \frac{1}{s}$$

$$E_{eq}(s) - s \frac{5}{s} = \frac{15}{s}$$
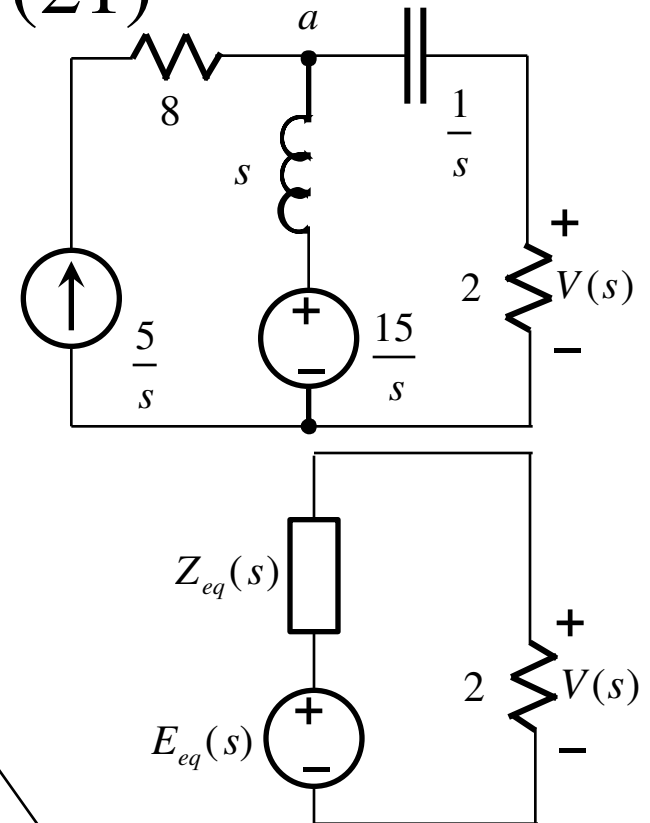
$$\rightarrow E_{eq}(s) = 5 \frac{s+3}{s}$$



$$V(s) = 2 \frac{E_{eq}(s)}{2 + Z_{eq}(s)}$$

$$= 10 \frac{s+3}{(s+1)^2}$$

Ex. 8

Analysis Techniques (22)




Solve for $i(t)$?

$$i(0) = 4A$$

$$v(0) = \frac{24}{6+4+2}(6+4) = 20V$$

$$Z_{eq}(s) = \frac{2 \frac{1000}{s}}{2 + \frac{1000}{s}} = \frac{1000}{s+500} \Omega$$

$$E_{eq}(s) = \frac{\frac{20/s}{1000/s} + \frac{24/s}{2}}{\frac{1}{1000/s} + \frac{1}{2}} = \frac{20s+12000}{s(s+500)} V$$

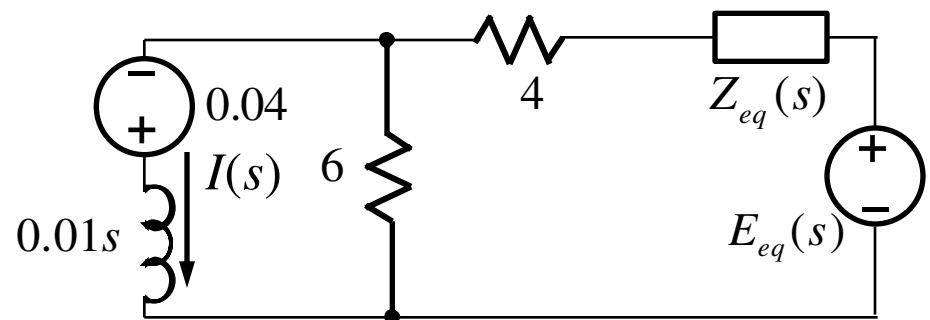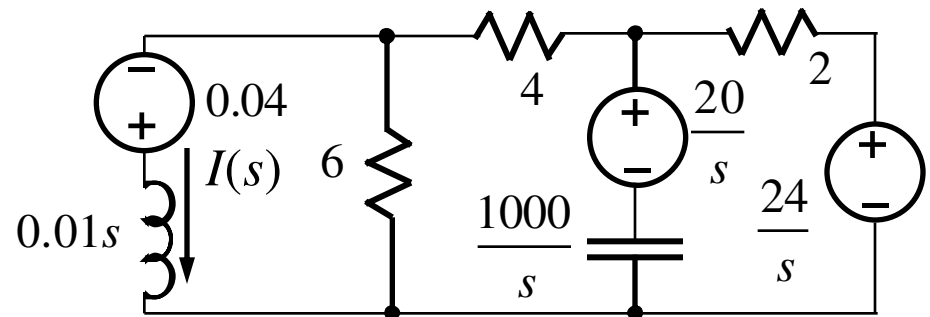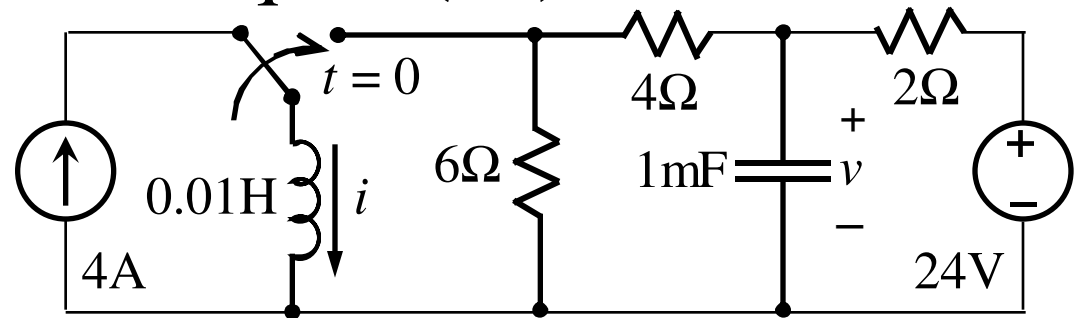

Ex. 8

Analysis Techniques (23)



Solve for $i(t)$?

$$V(s) = \frac{-\frac{0.04}{0.01s} + \frac{E_{eq}(s)}{4 + Z_{eq}(s)}}{\frac{1}{0.01s} + \frac{1}{6} + \frac{1}{4 + Z_{eq}(s)}}$$

$$= \frac{12s}{5s^2 + 4200s + 9 \times 10^5} \text{ V}$$

$$I(s) = \frac{0.04 + V(s)}{0.01s} = \frac{4s^2 + 3600s + 720000}{s(s^2 + 840s + 180000)} \text{ A}$$

$$i(t) = 4 + 4e^{-420t} \sin(60t) \text{ A}$$

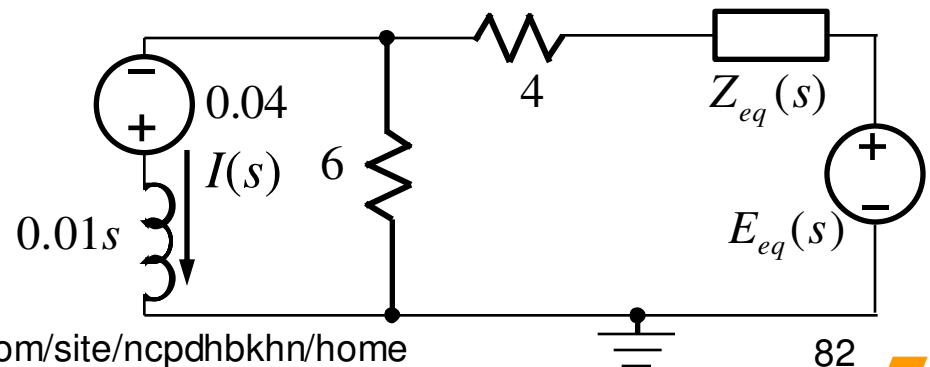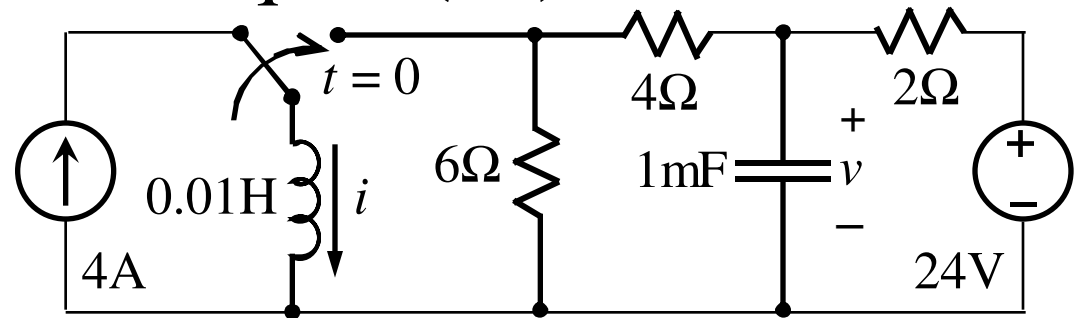

Ex. 9

Analysis Techniques (24)

Find the current $i(t)$?

$$i(0) = \frac{8}{8} = 1 \text{ A}$$



$$I(s) = \frac{2 + \frac{15}{s^2 + 9}}{2s + 4} = \frac{s^2 + 16.5}{(s + 2)(s^2 + 9)}$$

$$= \frac{K_1}{s + 2} + \frac{K_2}{s - j3} + \frac{K_2^*}{s + j3}$$

$$K_1 = \left. \frac{s^2 + 16.5}{s^2 + 9} \right|_{s=-2} = 1.58$$

$$K_2 = \left. \frac{s^2 + 16.5}{(s + 2)(s + j3)} \right|_{s=j3} = 0.35 \angle -146.3^\circ$$

$$\rightarrow i(t) = 1.58e^{-2t} + 0.70\cos(3t - 146.3^\circ) \text{ A}$$

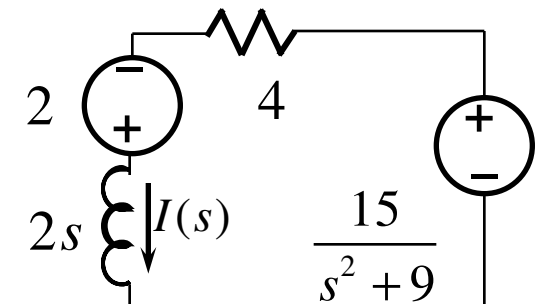
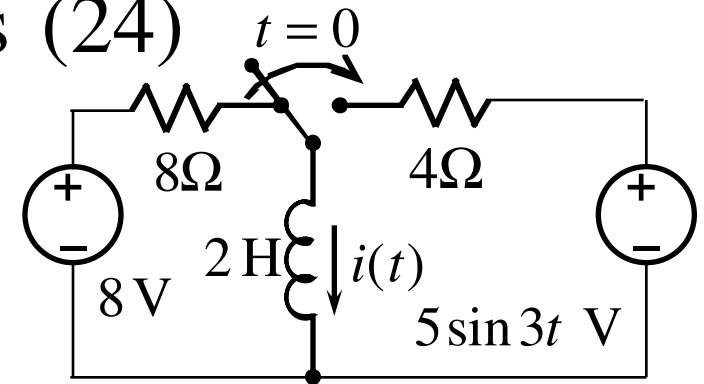


Ex. 9

Analysis Techniques (25)

Find the current $i(t)$?

$$i(t) = 1.58e^{-2t} + 0.70\cos(3t - 146.3^\circ) \text{ A}$$

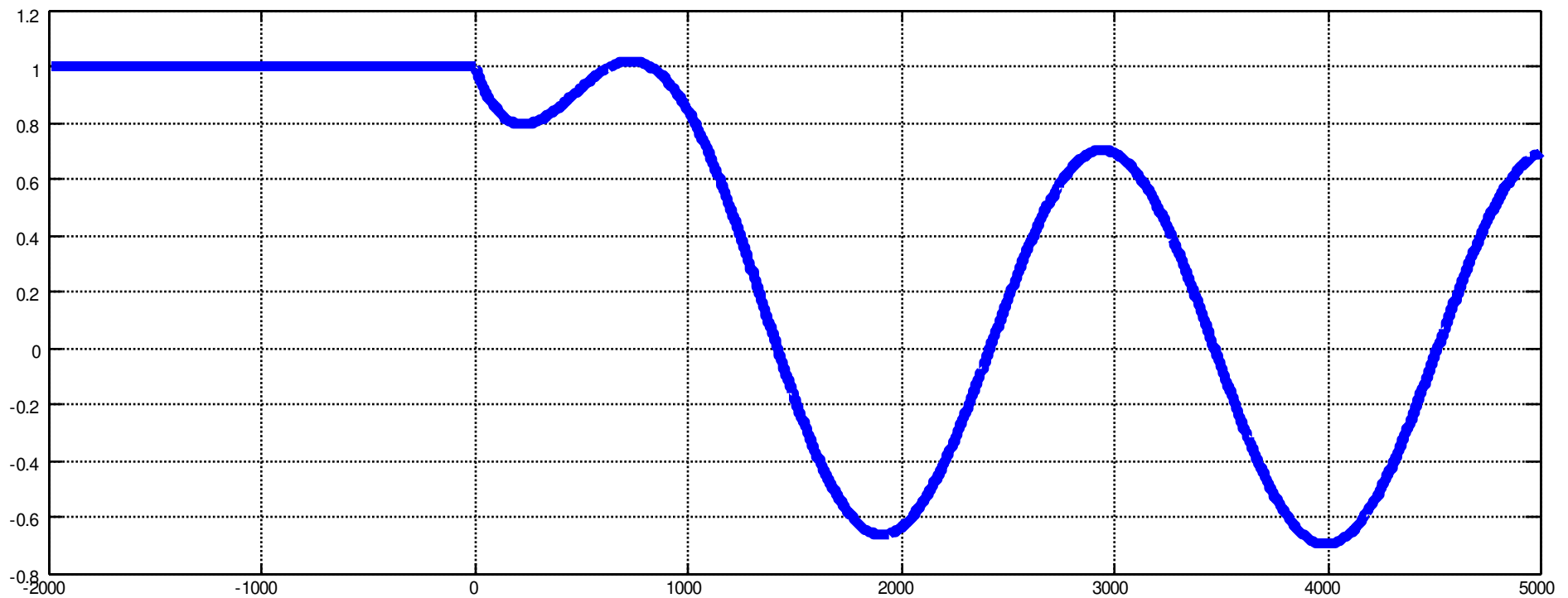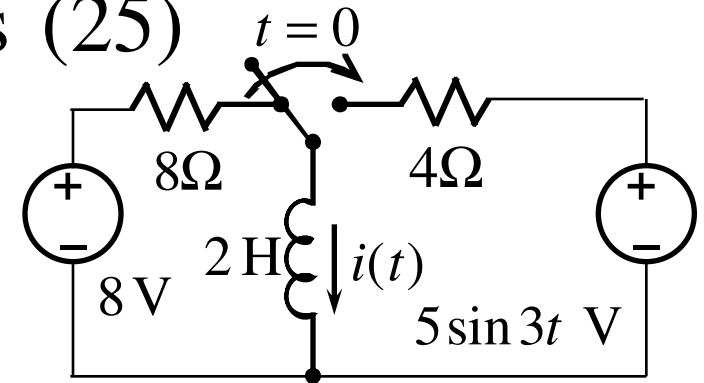

Ex. 10

Analysis Techniques (26)

Find the current $i(t)$?

$$I_0 = \frac{20}{8 + j6} = 2 \angle -36,9^\circ \text{ A}$$




$$\rightarrow i_0(t) = 2 \sin(3t - 36,9^\circ) \text{ A}$$

$$\rightarrow i(0) = 2 \sin(-36,9^\circ) = -1.20 \text{ A}$$

$$I(s) = \frac{-2.40 + \frac{8}{s}}{2s + 4} = \frac{-1.2s + 4}{s(s + 2)} \text{ A} = \frac{K_1}{s} + \frac{K_2}{s + 2}$$

$$K_1 = \left. \frac{-1.2s + 4}{s + 2} \right|_{s=0} = 2; \quad K_2 = \left. \frac{-1.2s + 4}{s} \right|_{s=-2} = -3.2$$

$$\rightarrow i(t) = 2 - 3.2e^{-2t} \text{ A}$$

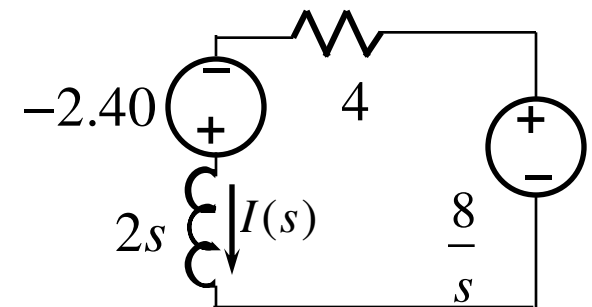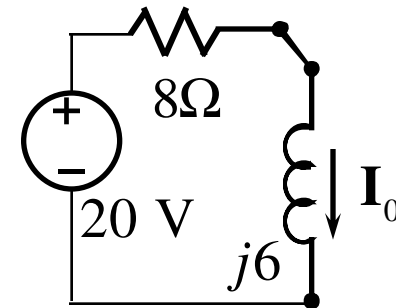
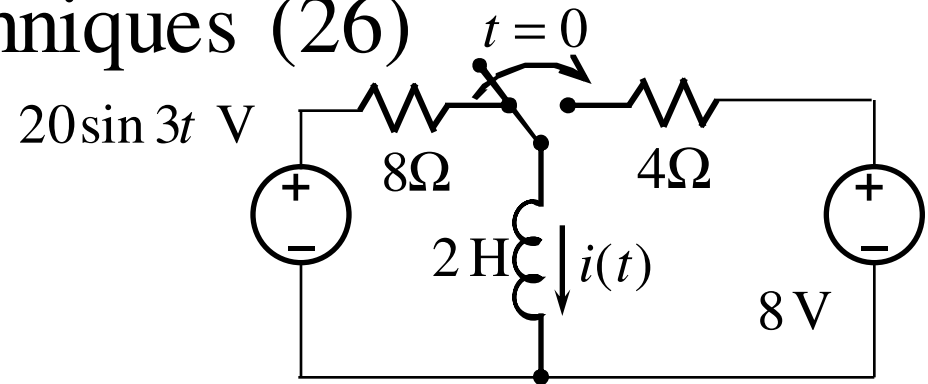


Ex. 10

Analysis Techniques (27)

Find the current $i(t)$?

$$i(t) = 2 - 3.2e^{-2t} \text{ A}$$

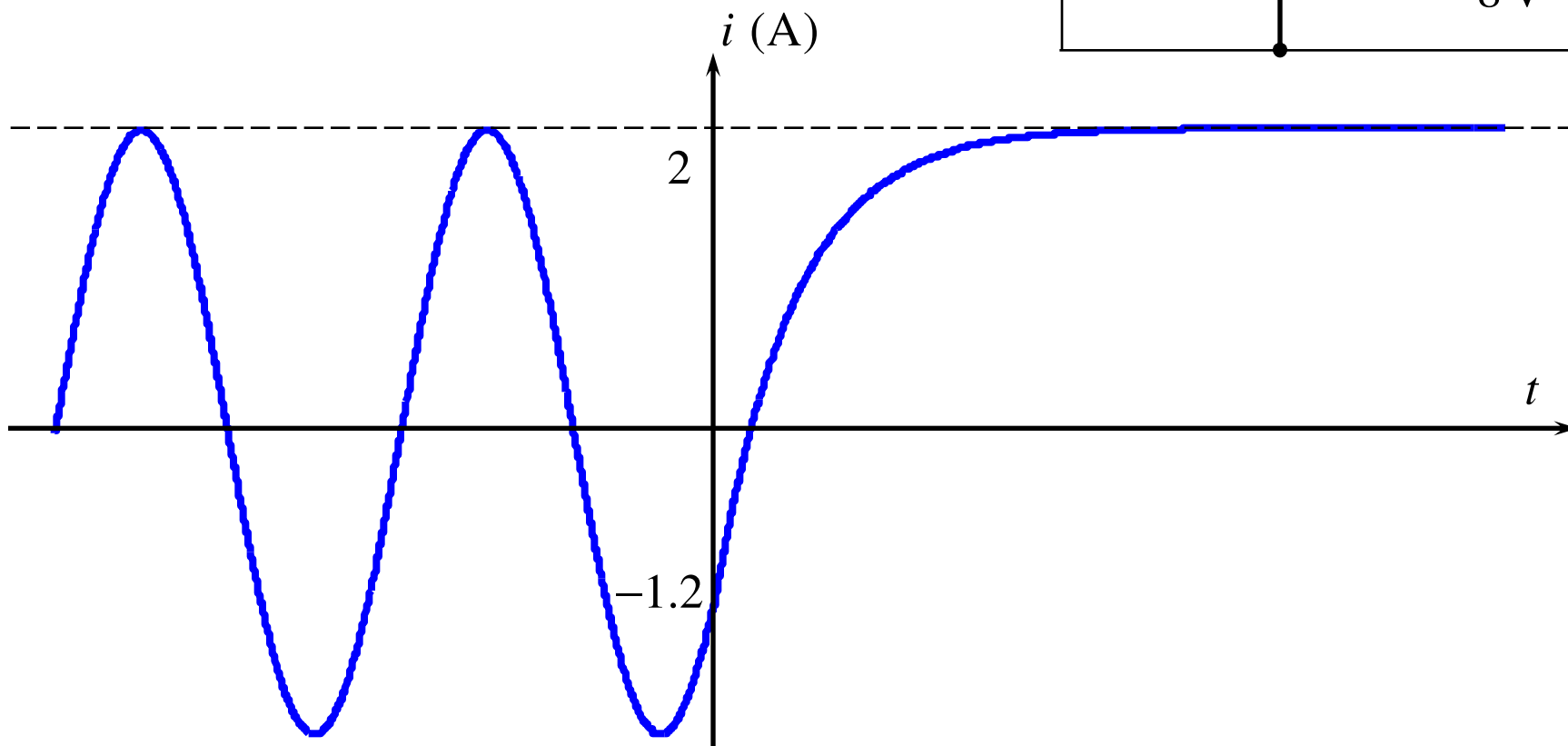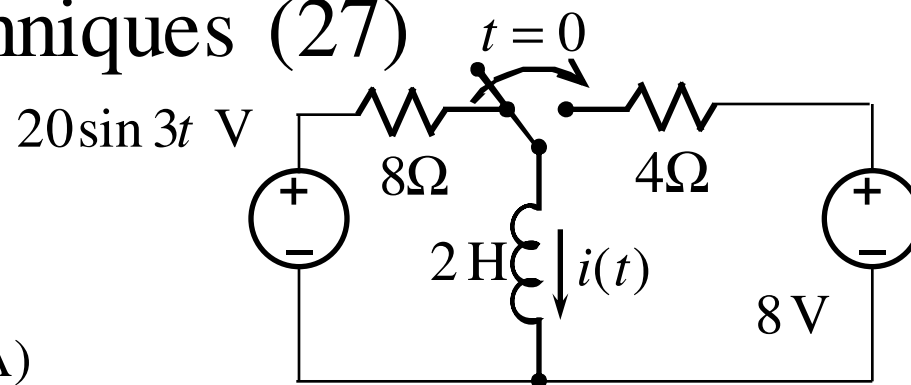


Ex. 11

Analysis Techniques (28)

Find the current $i_2(t)$?

$$i_1(0) = \frac{60}{12} = 5\text{A}; \quad i_2(0) = 0$$

$$v_{1M} = 2i_2'; \quad v_{2M} = 2i_1'$$

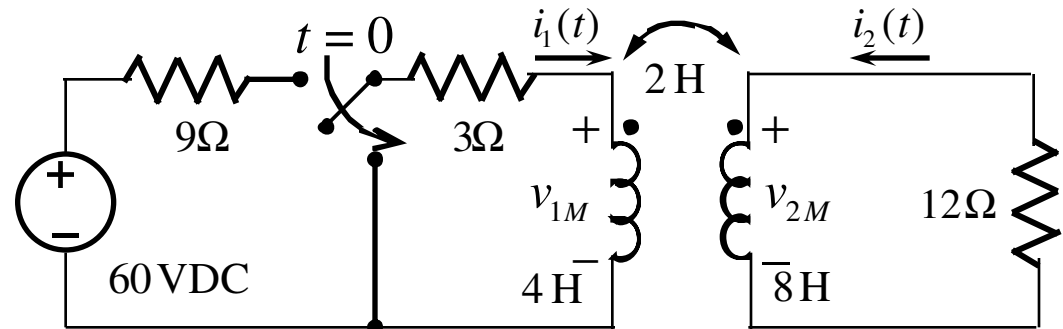

$$\begin{cases} 3i_1 + 4i_1' + 2i_2' = 0 \\ 12i_2 + 8i_2' + 2i_1' = 0 \end{cases}$$

$$kx(t) \rightarrow kX(s)$$

$$x'(t) \rightarrow sX(s) - x(-0)$$

$$\begin{cases} 3I_1(s) + 4[sI_1(s) - i_1(0)] + 2[sI_2(s) - i_2(0)] = 0 \\ 2[sI_1(s) - i_1(0)] + 12I_2(s) + 8[sI_2(s) - i_2(0)] = 0 \end{cases}$$

$$\rightarrow I_2(s) = \frac{15}{2(7s^2 + 18s + 9)} \text{ A}$$

$$\rightarrow i_2(t) = 0.8838(e^{-0.6796t} - e^{-1.8918t}) \text{ A}$$



Ex. 12

Analysis Techniques (29)

The switch has been at A for a long time, and it moves to B at $t = 0$; find i_L for $t \geq 0$?



$$i = \frac{24}{4} = 6 \text{ A}$$

$$6i_L(0) = 4i + 24$$

$$\rightarrow i_L(0) = \frac{4i + 24}{6} = \frac{4 \times 6 + 24}{6} = 8 \text{ A}$$

$$\left\{ \begin{aligned} \left(\frac{1}{12} + \frac{1}{4} + \frac{1}{4s+6} \right) V(s) &= \frac{36/s}{12} - \frac{4I(s) + 32}{4s+6} \\ V(s) &= 4I(s) \end{aligned} \right.$$

$$\rightarrow V(s) = -\frac{30s - 27}{2s(s+3)} \text{ V}$$

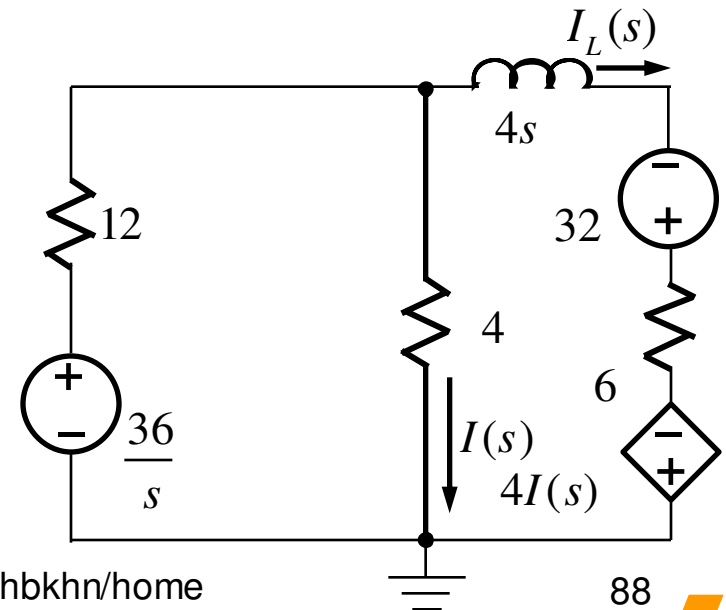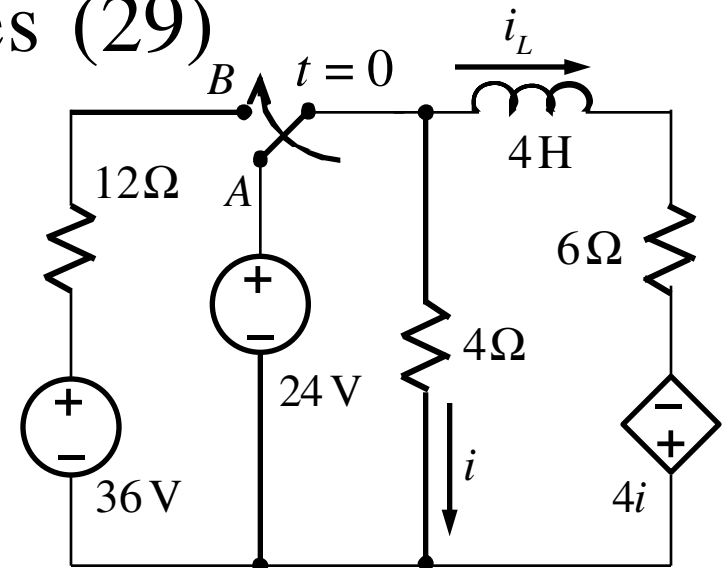

Ex. 12


Analysis Techniques (30)

The switch has been at A for a long time, and it moves to B at $t = 0$; find i_L for $t \geq 0$?

$$V(s) = -\frac{30s - 27}{2s(s + 3)} \text{ V}$$

$$\left. \begin{aligned} \rightarrow I_L(s) &= \frac{32 + 4I(s) + V(s)}{4s + 6} \\ V(s) &= 4I(s) \end{aligned} \right\}$$

$$\begin{aligned} \rightarrow I_L(s) &= \frac{32 + 2V(s)}{4s + 6} \\ &= \frac{16s + 9}{2s(s + 3)} \text{ A} \end{aligned}$$

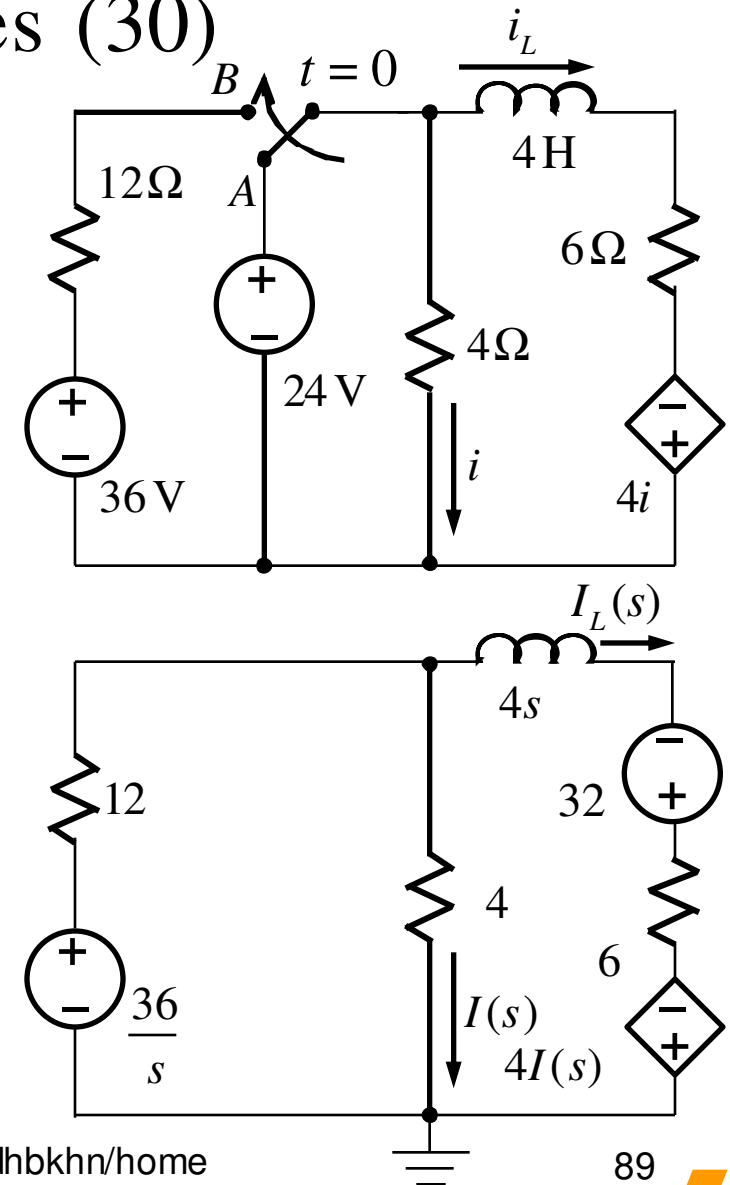

Ex. 12

Analysis Techniques (31)

The switch has been at A for a long time, and it moves to B at $t = 0$; find i_L for $t \geq 0$?


$$I_L(s) = \frac{16s + 9}{2s(s + 3)} = \frac{8s + 4.5}{s(s + 3)} \text{ A}$$

$$= \frac{K_1}{s} + \frac{K_2}{s + 3}$$

$$K_1 = \left. \frac{8s + 4.5}{s + 3} \right|_{s=0} = 1.5$$

$$K_2 = \left. \frac{8s + 4.5}{s} \right|_{s=-3} = 6.5$$

$$\rightarrow i_L(t) = 1.5 + 6.5e^{-3t} \text{ A}$$

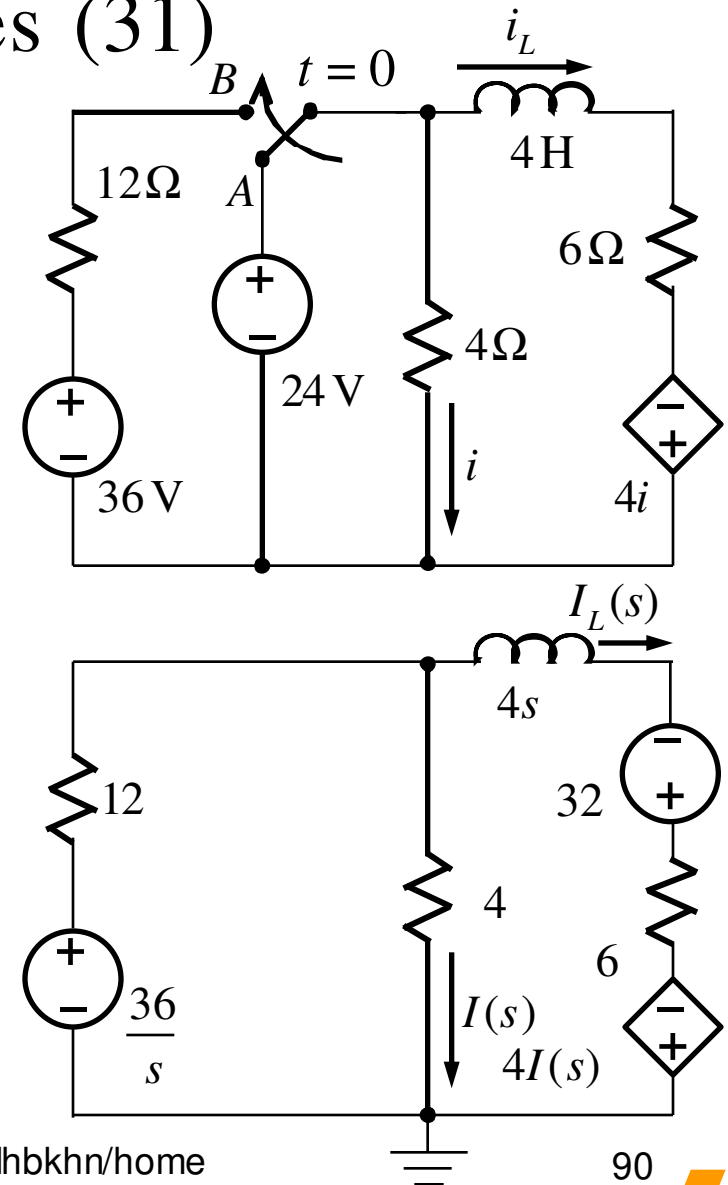

Ex. 13

Solve for $i(t)$?

$$v_C(0) = 0; \quad i_L(0) = 0$$

$$-V_x(s) + \left(2 + \frac{6}{s}\right)[I_A(s) - I_c(s)] + (s+2)I_A(s) = 0$$



$$\rightarrow -V_x(s) + \left(2 + \frac{6}{s}\right)[I_A(s) - 0.5V_x(s)] + (s+2)I_A(s) = 0$$

$$V_x(s) = 2 \left[\frac{2}{s} - I_A(s) \right] = \frac{4}{s} - 2I_A(s)$$

$$\rightarrow -\left[\frac{4}{s} - 2I_A(s) \right] + \left(2 + \frac{6}{s}\right) \left\{ I_A(s) - 0.5 \left[\frac{4}{s} - 2I_A(s) \right] \right\} + (s+2)I_A(s) = 0$$

$$\rightarrow I_A(s) = \frac{8s+12}{s(s+2)(s+6)} = I(s)$$

Analysis Techniques (32)

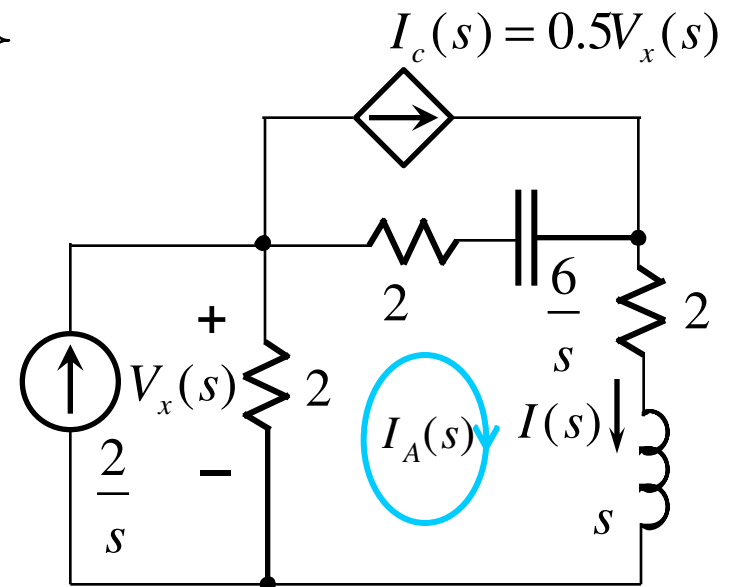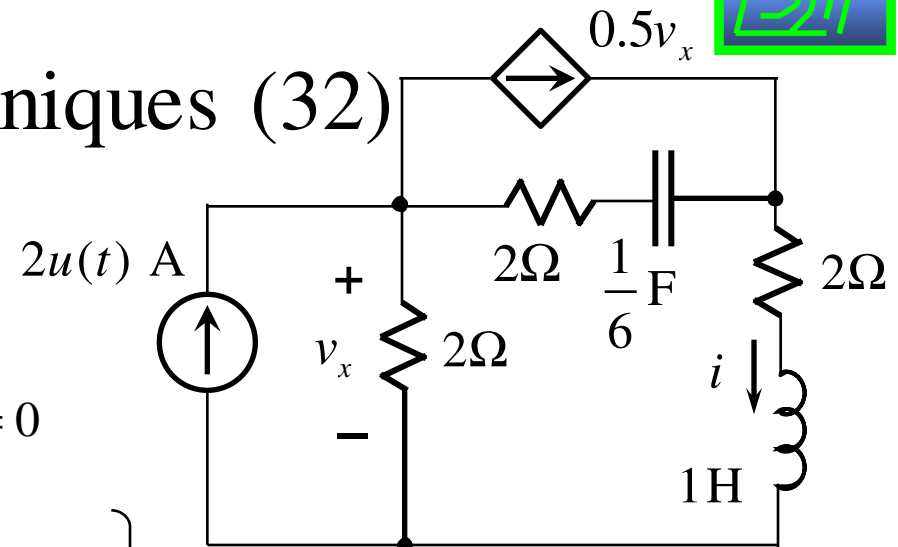

Ex. 13

Analysis Techniques (33)

Solve for $i(t)$?



$$I(s) = \frac{8s + 12}{s(s + 2)(s + 6)} = \frac{K_1}{s} + \frac{K_2}{s + 2} + \frac{K_3}{s + 6}$$

$$K_1 = \left. \frac{8s + 12}{(s + 2)(s + 6)} \right|_{s=0} = 1$$


$$K_2 = \left. \frac{8s + 12}{s(s + 6)} \right|_{s=-2} = 0.5$$

$$K_3 = \left. \frac{8s + 12}{s(s + 2)} \right|_{s=-6} = -1.5$$
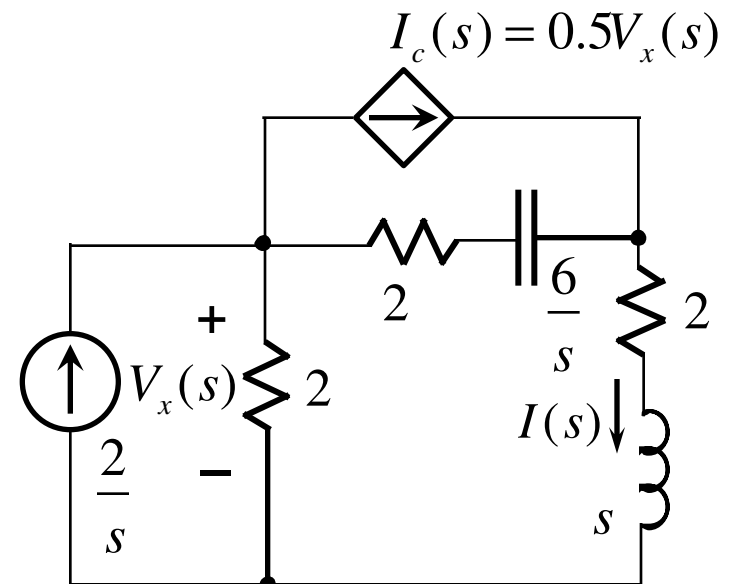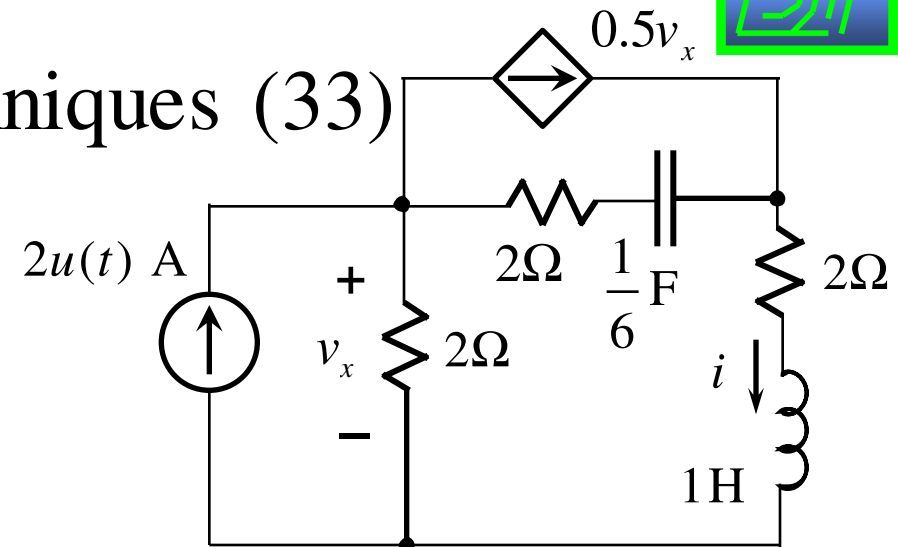
$$\rightarrow i(t) = \boxed{1 + 0.5e^{-2t} - 1.5e^{-6t} \text{ A}}$$



Analysis Techniques (34)

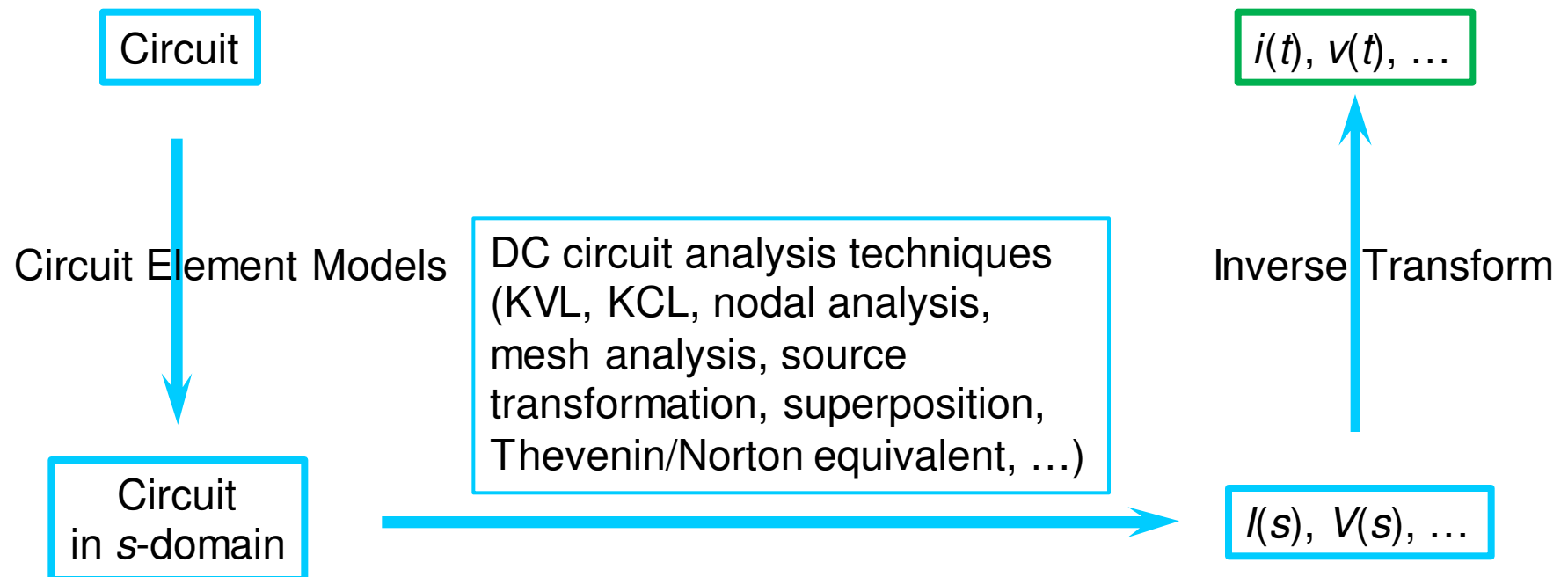





The Laplace Transform

1. Definition
2. Two Important Singularity Functions
3. Transform Pairs
4. Properties of the Transform
5. Inverse Transform
6. Initial-Value & Final-Value Theorems
7. Laplace Circuit Solutions
8. Circuit Element Models
9. Analysis Techniques
- 10. Convolution Integral**
11. Transfer Function



Convolution Integral (1)

$$f(t) = f_1(t) * f_2(t) = \int_0^t f_1(t - \lambda) f_2(\lambda) d\lambda = \int_0^t f_1(\lambda) f_2(t - \lambda) d\lambda$$

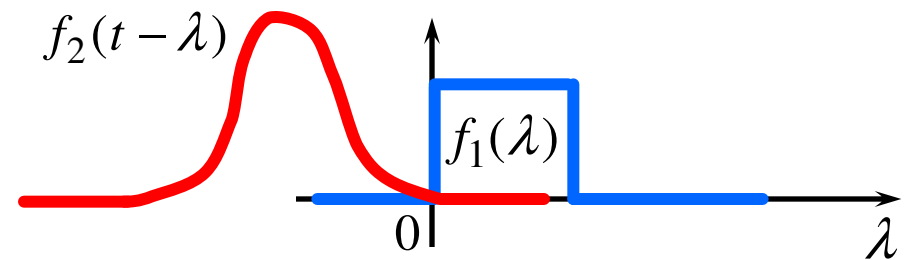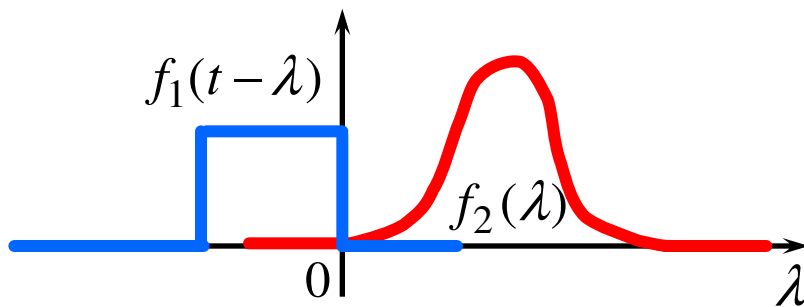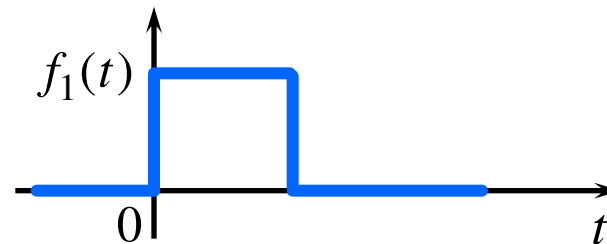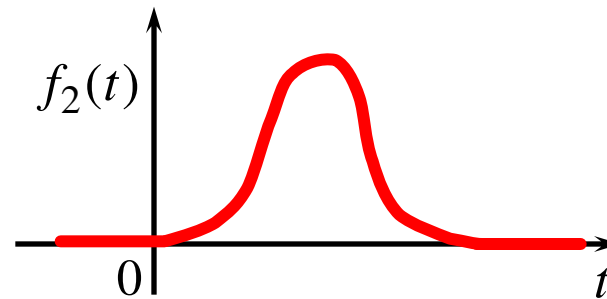


Ex. 1

Convolution Integral (2)




Find the convolution of the two signals?
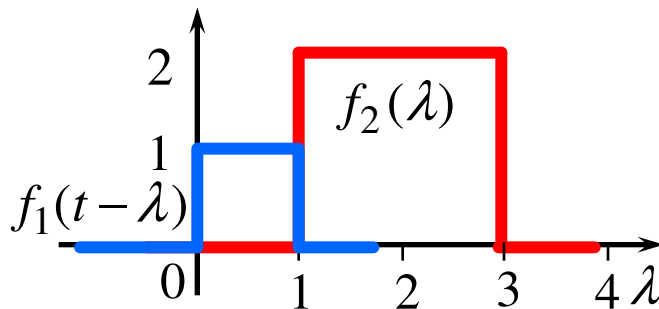
$$f(t) = f_1(t) * f_2(t) = \int_0^t f_1(t-\lambda) f_2(\lambda) d\lambda = \int_0^t f_1(\lambda) f_2(t-\lambda) d\lambda$$



$$0 < t < 1: f_1 = 1; f_2 = 0$$

$$f_1(t) * f_2(t) = 0$$

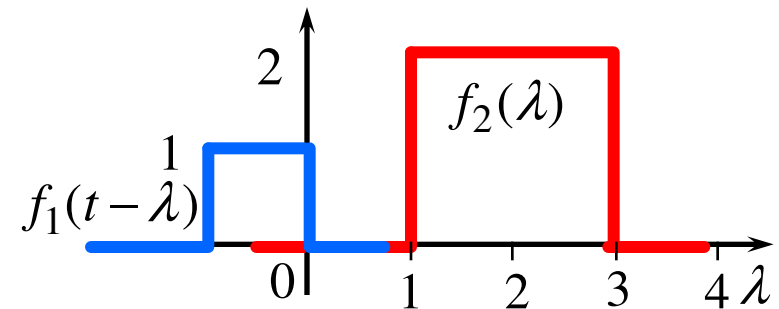
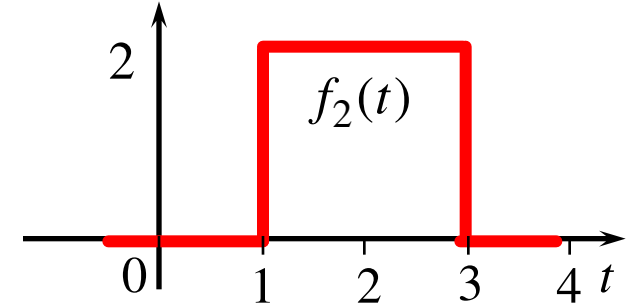
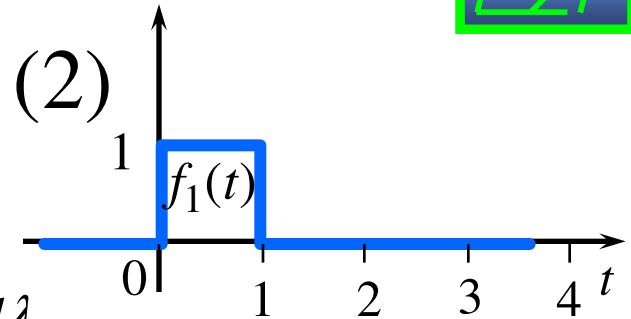


Ex. 1

Convolution Integral (3)

Find the convolution of the two signals?
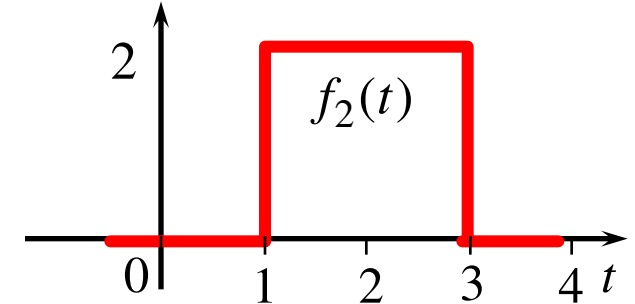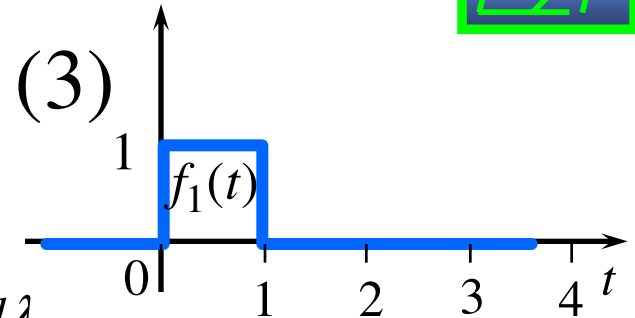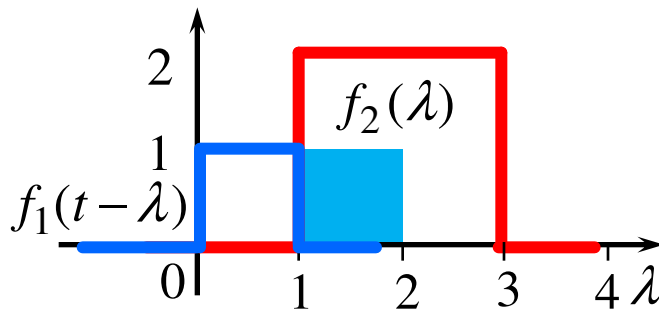
$$f(t) = f_1(t) * f_2(t) = \int_0^t f_1(t-\lambda) f_2(\lambda) d\lambda = \int_0^t f_1(\lambda) f_2(t-\lambda) d\lambda$$



$$0 < t < 1: \quad f_1(t) * f_2(t) = 0$$

$$1 < t < 2: \quad f_1 = 1; \quad f_2 = 2$$




$$f_1(t) * f_2(t) = \int_1^t f_1(t-\lambda) f_2(\lambda) d\lambda = \int_1^t 1 \times 2 d\lambda = 2\lambda \Big|_{\lambda=1}^t = 2(t-1)$$

Ex. 1

Convolution Integral (4)

Find the convolution of the two signals?
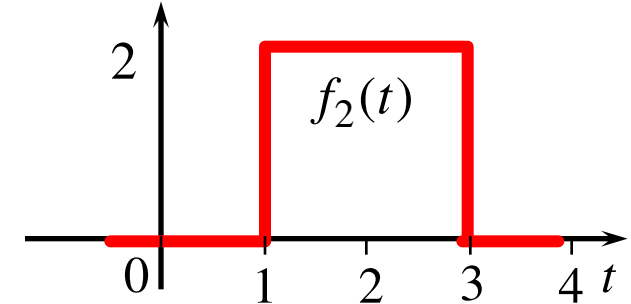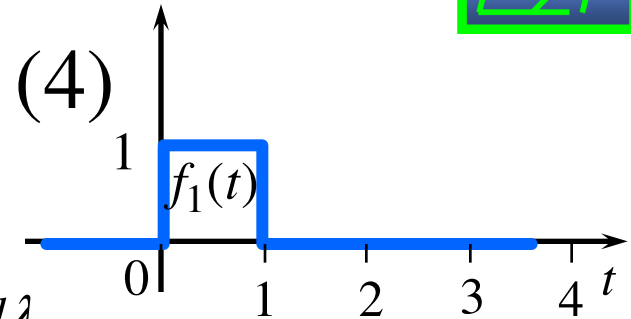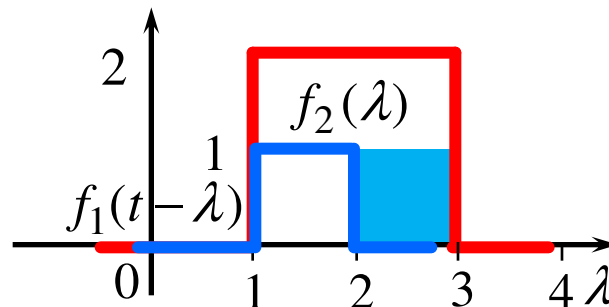
$$f(t) = f_1(t) * f_2(t) = \int_0^t f_1(t-\lambda) f_2(\lambda) d\lambda = \int_0^t f_1(\lambda) f_2(t-\lambda) d\lambda$$



$$0 < t < 1: f_1(t) * f_2(t) = 0$$

$$1 < t < 2: f_1(t) * f_2(t) = 2(t-1)$$

$$2 < t < 3: f_1 = 1; f_2 = 2$$




$$f_1(t) * f_2(t) = \int_{t-1}^t f_1(t-\lambda) f_2(\lambda) d\lambda = \int_{t-1}^t 1 \times 2 d\lambda = 2\lambda \Big|_{\lambda=t-1}^t = 2$$

Ex. 1

Convolution Integral (5)

Find the convolution of the two signals?
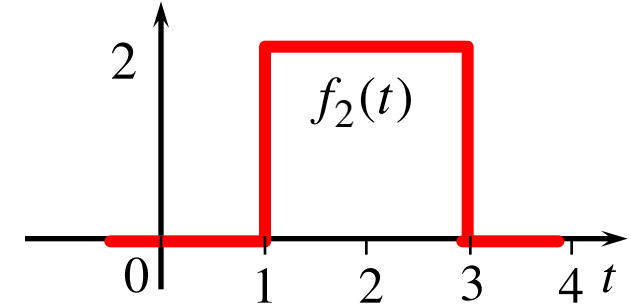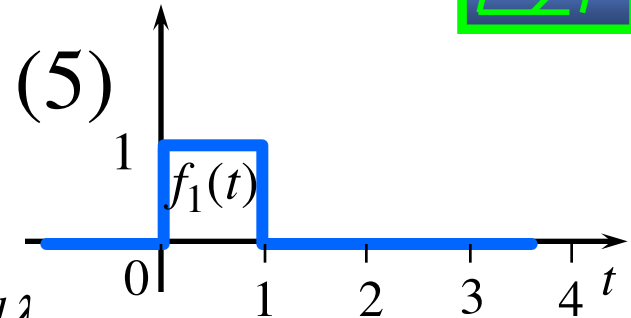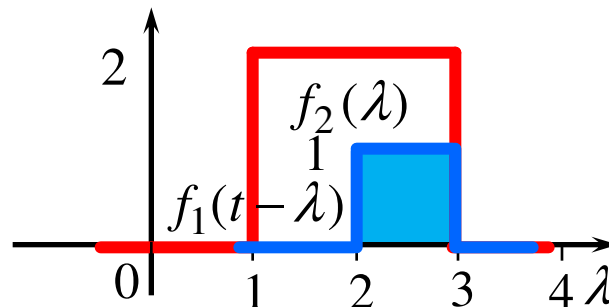
$$f(t) = f_1(t) * f_2(t) = \int_0^t f_1(t-\lambda) f_2(\lambda) d\lambda = \int_0^t f_1(\lambda) f_2(t-\lambda) d\lambda$$



$$3 < t < 4: f_1 = 1; f_2 = 2$$

$$0 < t < 1: f_1(t) * f_2(t) = 0$$

$$1 < t < 2: f_1(t) * f_2(t) = 2(t-1)$$

$$2 < t < 3: f_1(t) * f_2(t) = 2$$


$$f_1(t) * f_2(t) = \int_{t-1}^3 f_1(t-\lambda) f_2(\lambda) d\lambda = \int_{t-1}^3 1 \times 2 d\lambda = 2\lambda \Big|_{\lambda=t-1}^3 = 8 - 2t$$

Ex. 1



Convolution Integral (6)

Find the convolution of the two signals?
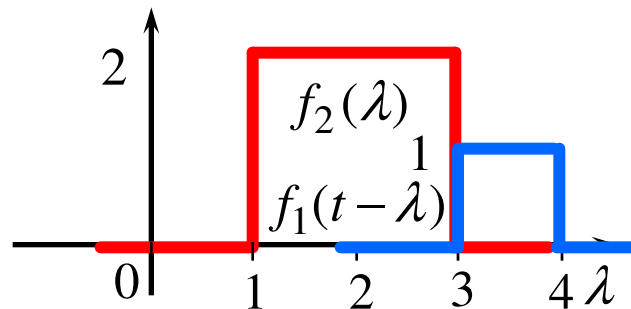
$$f(t) = f_1(t) * f_2(t) = \int_0^t f_1(t-\lambda) f_2(\lambda) d\lambda = \int_0^t f_1(\lambda) f_2(t-\lambda) d\lambda$$



$$t > 4: f_1 = 1; f_2 = 0$$

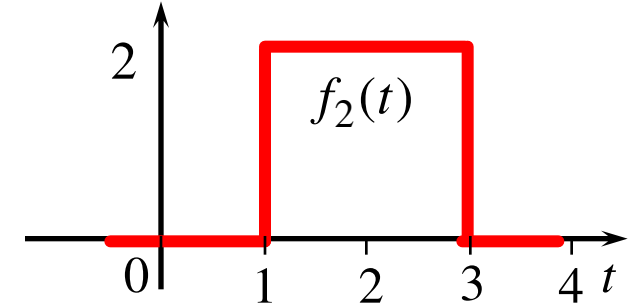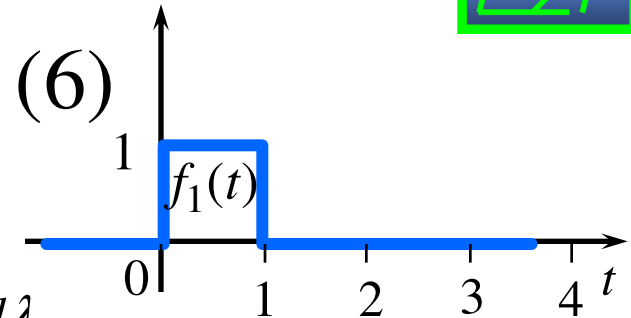

$$0 < t < 1: f_1(t) * f_2(t) = 0$$

$$1 < t < 2: f_1(t) * f_2(t) = 2(t-1)$$

$$2 < t < 3: f_1(t) * f_2(t) = 2$$

$$3 < t < 4: f_1(t) * f_2(t) = 8 - 2t$$



$$f_1(t) * f_2(t) = 0$$

Ex. 1

Convolution Integral (7)

Find the convolution of the two signals?
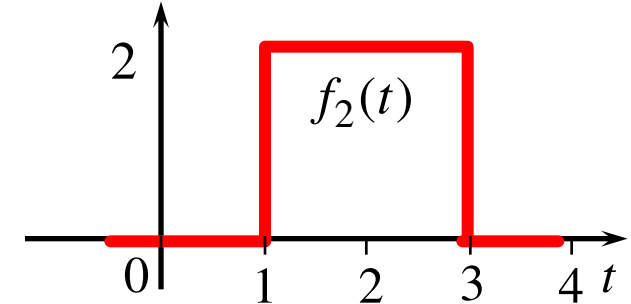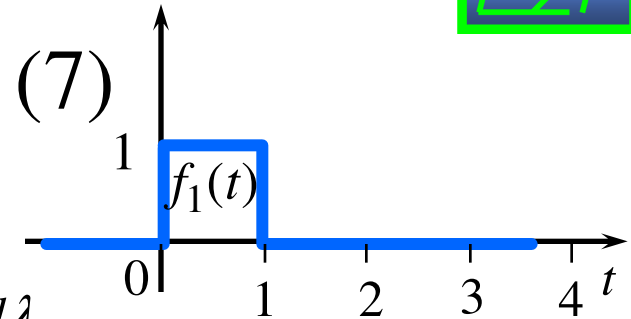
$$f(t) = f_1(t) * f_2(t) = \int_0^t f_1(t-\lambda) f_2(\lambda) d\lambda = \int_0^t f_1(\lambda) f_2(t-\lambda) d\lambda$$




$$0 < t < 1: \quad f_1(t) * f_2(t) = 0$$

$$1 < t < 2: \quad f_1(t) * f_2(t) = 2(t-1)$$

$$2 < t < 3: \quad f_1(t) * f_2(t) = 2$$

$$3 < t < 4: \quad f_1(t) * f_2(t) = 8 - 2t$$


$$t > 4: \quad f_1(t) * f_2(t) = 0$$

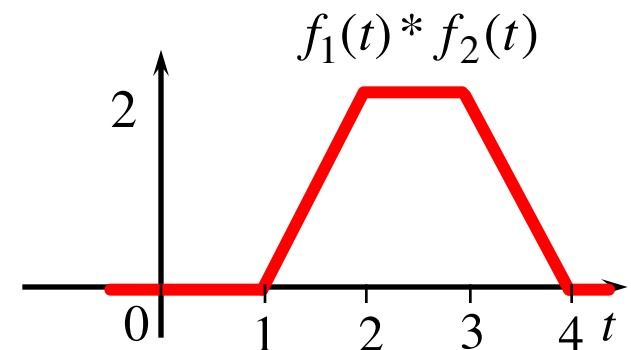

Ex. 2



Convolution Integral (8)

Find the convolution of the two signals?

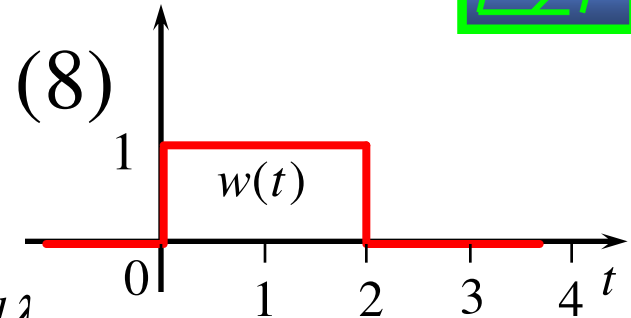


$$f(t) = f_1(t) * f_2(t) = \int_0^t f_1(t-\lambda) f_2(\lambda) d\lambda = \int_0^t f_1(\lambda) f_2(t-\lambda) d\lambda$$

Method 1

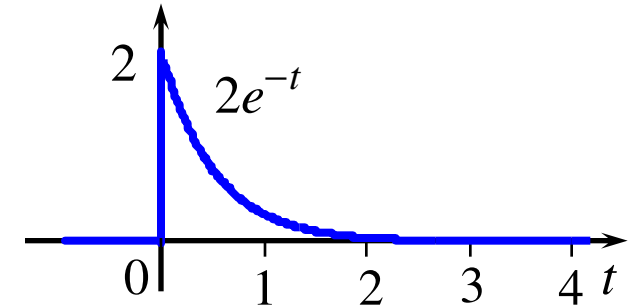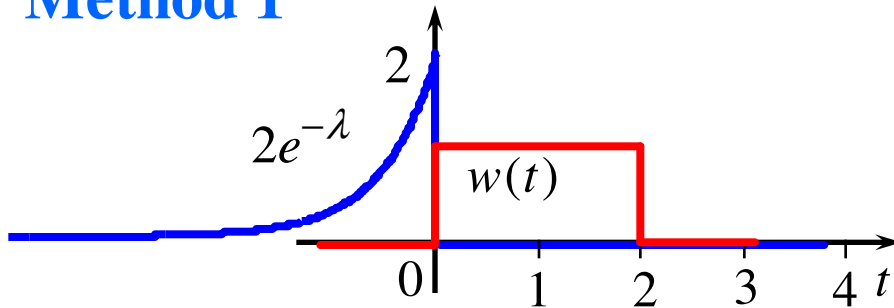

$$0 < t < 2: f(t) = \int_0^t 2e^{-(t-\lambda)} \times 1 d\lambda = 2e^{\lambda-t} \Big|_{\lambda=0}^{\lambda=t} = 2(1 - e^{-t})$$


$$t > 2: f(t) = \int_0^2 2e^{-(t-\lambda)} \times 1 d\lambda = 2e^{\lambda-t} \Big|_{\lambda=0}^{\lambda=2} = 2(e^2 - 1)e^{-t}$$

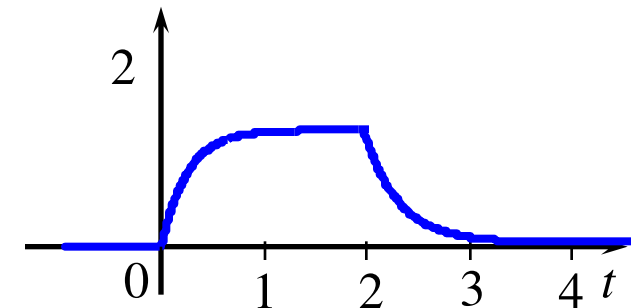

Ex. 2



Convolution Integral (9)

Find the convolution of the two signals?

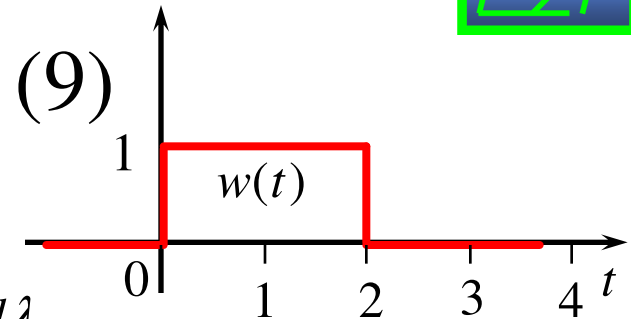


$$f(t) = f_1(t) * f_2(t) = \int_0^t f_1(t-\lambda) f_2(\lambda) d\lambda = \int_0^t f_1(\lambda) f_2(t-\lambda) d\lambda$$

Method 2

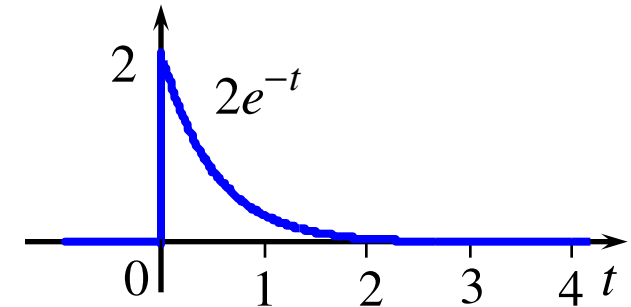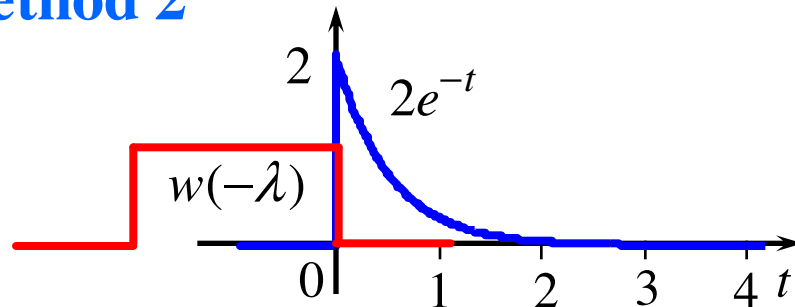

$$0 < t < 2: f(t) = \int_0^t 1 \times 2e^{-\lambda} d\lambda = -2e^{-\lambda} \Big|_{\lambda=0}^{\lambda=t} = 2(1 - e^{-t})$$

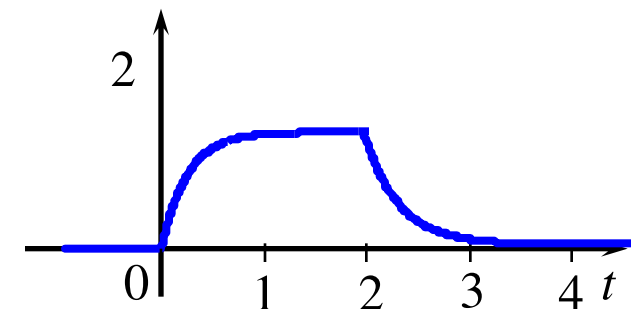

$$t > 2: f(t) = \int_{t-2}^t 1 \times 2e^{-\lambda} d\lambda = -2e^{-\lambda} \Big|_{\lambda=t-2}^{\lambda=t} = 2(e^2 - 1)e^{-t}$$



Convolution Integral (10)

Property	$f(t)$	$F(s)$
1. Magnitude scaling	$Af(t)$	$AF(s)$
2. Addition/subtraction	$f_1(t) \pm f_2(t)$	$F_1(s) \pm F_2(s)$
3. Time scaling	$f(at)$	$\frac{1}{a}F\left(\frac{s}{a}\right)$
4. Time shifting	$f(t-a)u(t-a), a \geq 0$ $f(t)u(t-a), a \geq 0$	$e^{-as}F(s)$ $e^{-as}L[f(t+a)]$
5. Frequency shifting	$e^{-at}f(t)$	$F(s+a)$
6. Differentiation	$d^n f(t)/dt^n$	$s^n F(s) - s^{n-1}f(0) - s^{n-2}f'(0) \dots - s^2 f^{n-1}(0)$
7. Multiplication by t	$t^n f(t)$	$(-1)^n d^n F(s)/ds^n$
8. Division by t	$f(t)/t$	$\int_s^\infty F(\lambda)d\lambda$
9. Integration	$\int_0^t f(\lambda)d\lambda$	$F(s)/s$
10. Convolution	$f_1(t) * f_2(t) = \int_0^t f_1(\lambda)f_2(t-\lambda)d\lambda$	$F_1(s)F_2(s)$

Ex. 3

Convolution Integral (11)

Find $v_o(t)$?

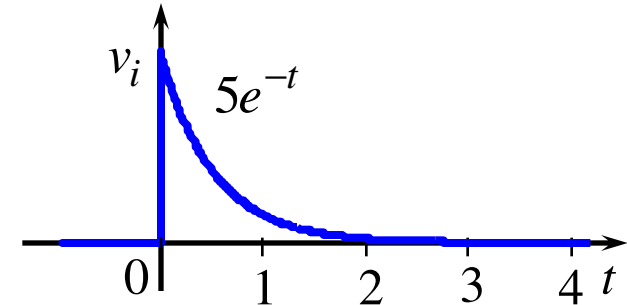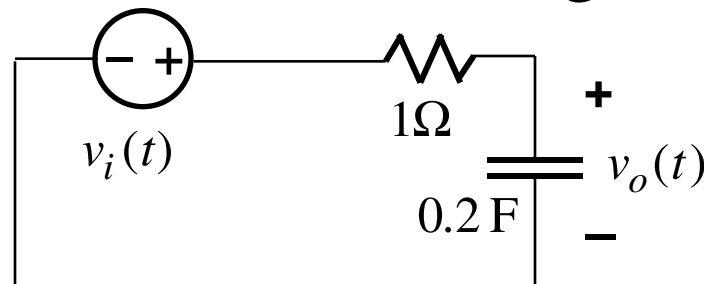

$$V_o(s) = \frac{Z_C(s)}{R + Z_C(s)} V_i(s) = \frac{\frac{0.2s}{1 + \frac{1}{0.2s}}}{s + 1} \times \frac{5}{s + 1} = \frac{5}{s + 5} \times \frac{5}{s + 1}$$

Method 1: $V_o(s) \rightarrow v_o(t) = \boxed{6.25(e^{-t} - e^{-5t}) \text{ V}}$

Method 2: $V_o(s) = H(s)V_i(s) \rightarrow v_o(t) = h(t) * v_i(t)$

$$H(s) = \frac{5}{s + 5} \rightarrow h(t) = 5e^{-5t}$$


$$v_o(t) = \int_0^t h(t - \lambda) v_i(\lambda) d\lambda = \int_0^t 5e^{-5(t-\lambda)} 5e^{-\lambda} d\lambda = 25 \int_0^t e^{-5t+4\lambda} d\lambda = 6.25e^{-5t+4\lambda} \Big|_{\lambda=0}^{\lambda=t}$$

$$= \boxed{6.25(e^{-t} - e^{-5t}) \text{ V}}$$

The Laplace Transform

1. Definition
2. Two Important Singularity Functions
3. Transform Pairs
4. Properties of the Transform
5. Inverse Transform
6. Initial-Value & Final-Value Theorems
7. Laplace Circuit Solutions
8. Circuit Element Models
9. Analysis Techniques
10. Convolution Integral
- 11. Transfer Function**

Transfer Function (1)

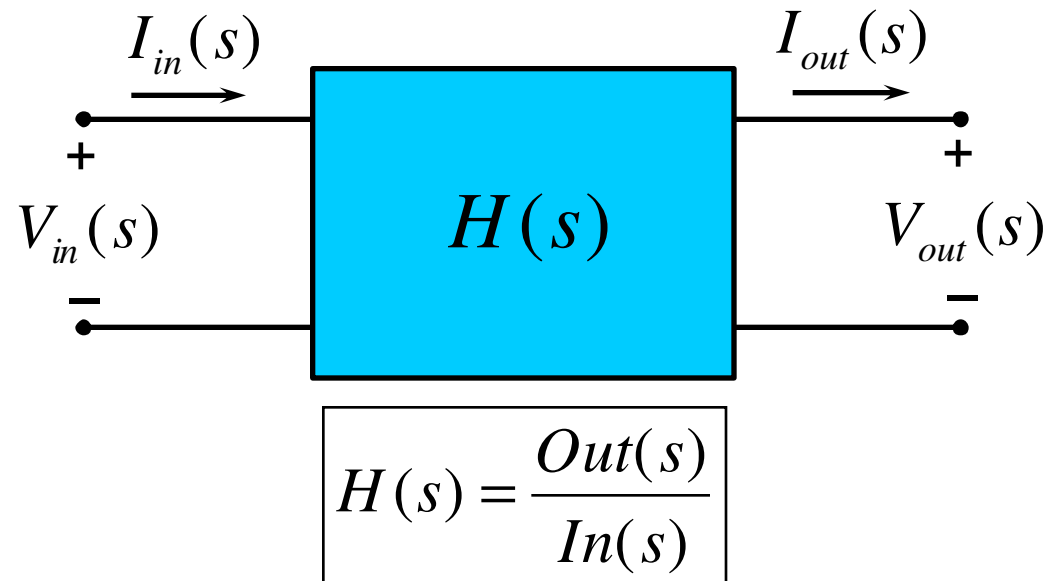

If $in(t) = \delta(t) \rightarrow In(s) = 1 \rightarrow H(s) = Out(s)$

Ex. 1

Transfer Function (2)

Find the transfer function $h(t)$ of the filter?



$$v_i(t) = 10u(t)$$

$$V_o(s) = H(s)V_i(s) = H(s)\frac{10}{s}$$


$$\rightarrow H(s) = \frac{1}{10}sV_o(s)$$

$$\rightarrow h(t) = \frac{1}{10} \frac{dv_o(t)}{dt}$$

Ex. 2

Transfer Function (3)

Find the transfer function $H(s)$?

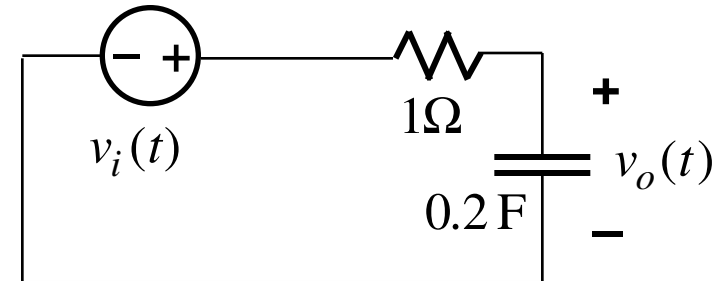

$$V_o(s) = \frac{Z_C(s)}{R + Z_C(s)} V_i(s) = \frac{\frac{1}{0.2s}}{1 + \frac{1}{0.2s}} V_i(s) = \frac{5}{s + 5} V_i(s) = H(s) V_i(s)$$



$$\rightarrow H(s) = \frac{V_o(s)}{V_i(s)} = \frac{5}{s + 5}$$

Ex. 3

Transfer Function (4)

Given the transfer function $H(s) = \frac{5}{s+5}$

Find C ?

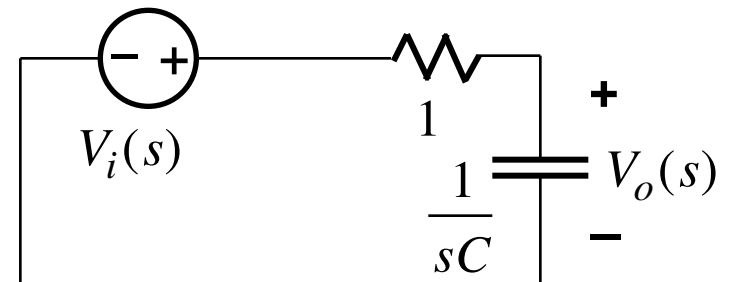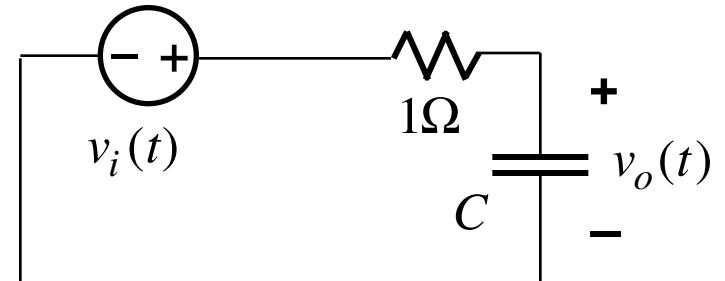

$$V_o(s) = \frac{Z_C(s)}{R + Z_C(s)} V_i(s) = \frac{\frac{1}{sC}}{1 + \frac{1}{sC}} V_i(s) = \frac{1}{Cs + 1} V_i(s)$$

$$\rightarrow H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{Cs + 1} = \frac{5}{5Cs + 5}$$


$$\rightarrow 5C = 1$$

$$\rightarrow \boxed{C = 0.2 \text{ F}}$$

Ex. 4

Transfer Function (5)

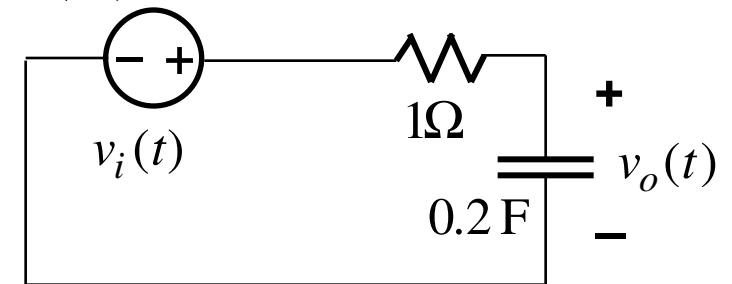Find $v_o(t)$ in two cases: $v_i = 10\text{VDC}$;
and $v_i(t) = 10\cos 2t \text{ V}$?



$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{5}{s+5}$$

$$V_{o1}(s) = V_{i1}(s)H(s) = \frac{10}{s} \cdot \frac{5}{s+5}$$

$$\rightarrow v_{o1}(t) = 10(1 - e^{-5t}) \text{ V}$$

$$V_{o2}(s) = V_{i2}(s)H(s) = \frac{10s}{s^2 + 4} \cdot \frac{5}{s+5}$$

$$\rightarrow v_{o2}(t) = -8.62e^{-5t} + 9.28\cos(2t + 21.8^\circ) \text{ V}$$

Ex. 5 Transfer Function (6)

Find the step responses of $H_1(s) = \frac{1}{s+1}$, $H_2(s) = \frac{4}{s^2+4}$, $H_3(s) = \frac{3}{s-3}$.

$$Y_1(s) = X(s)H_1(s) = \frac{1}{s} \cdot \frac{1}{s+1} \quad \rightarrow y_1(t) = 1 - e^{-t}$$


$$Y_2(s) = X(s)H_2(s) = \frac{1}{s} \cdot \frac{4}{s^2+4} \quad \rightarrow y_2(t) = 1 - \cos 2t$$

$$Y_3(s) = X(s)H_3(s) = \frac{1}{s} \cdot \frac{3}{s-3} \quad \rightarrow y_1(t) = -1 + e^{3t}$$

Transfer Function (7)


$$H(s) = \frac{1}{s+1}$$

$$y(t) = 1 - e^{-t}$$

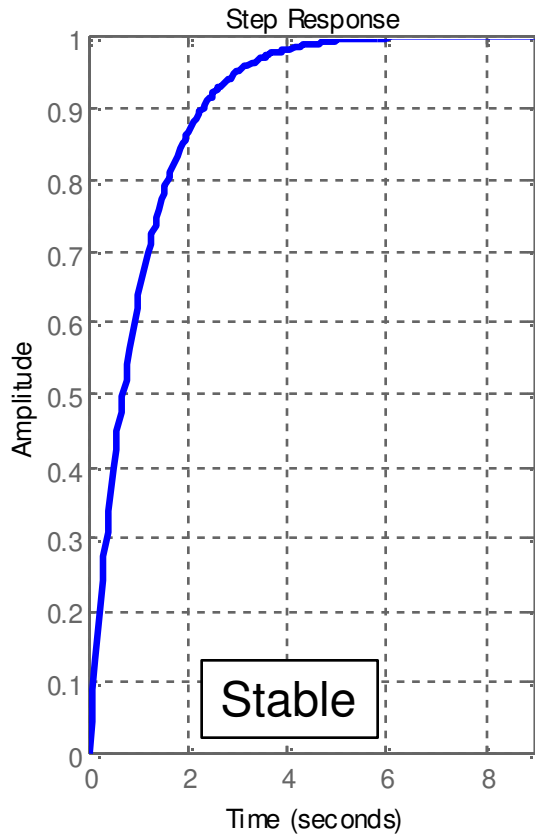


$$H(s) = \frac{4}{s^2 + 4}$$

$$y(t) = 1 - \cos 2t$$

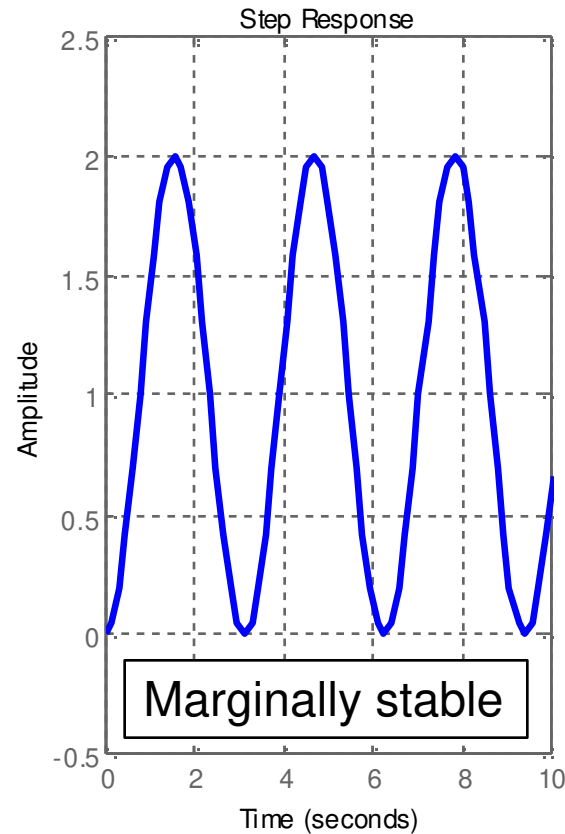

$$H(s) = \frac{3}{s-3}$$

$$y(t) = -1 + e^{3t}$$

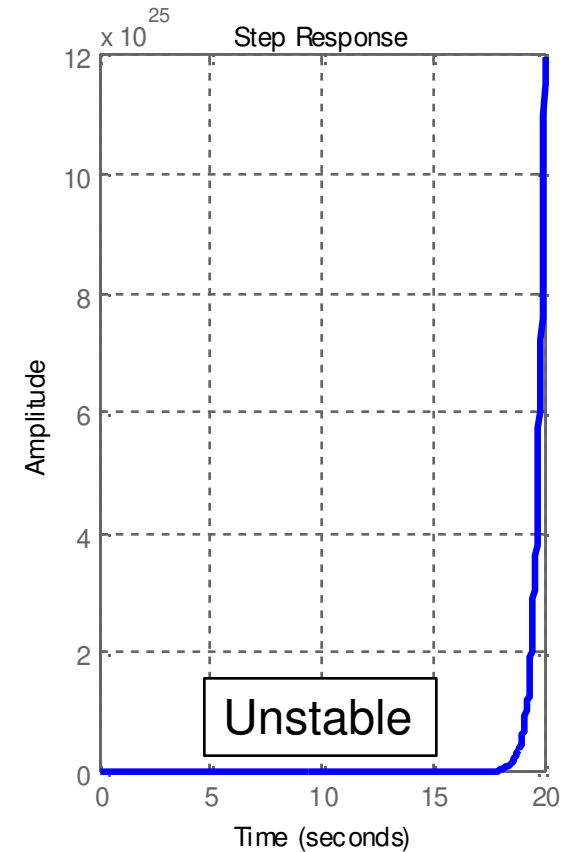


Transfer Function (8)

A circuit is stable if : $\lim_{t \rightarrow \infty} |h(t)| = \text{finite}$

$$H(s) = \frac{N(s)}{(s + p_1)(s + p_2) \dots (s + p_n)}$$
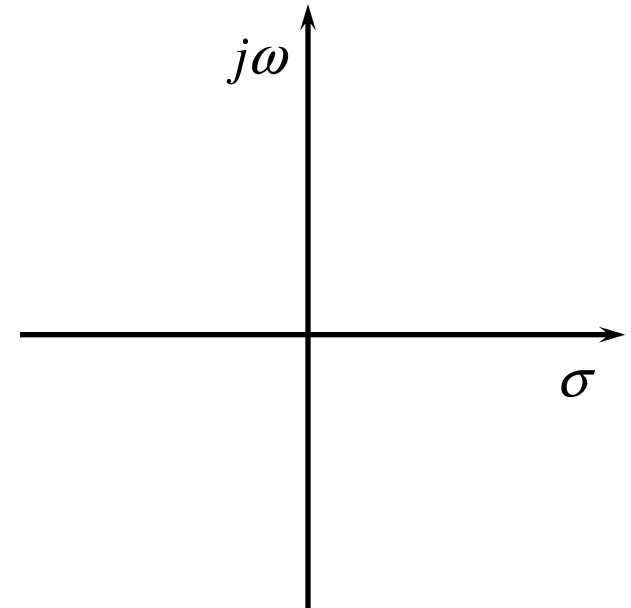
$$\rightarrow h(t) = (k_1 e^{-p_1 t} + k_2 e^{-p_2 t} + \dots + k_n e^{-p_n t}) u(t)$$



A circuit is stable when all the poles of its transfer function $H(s)$ lie in the left half of the s -plane

Ex. 6 Transfer Function (9)

An active filter has the transfer function $H(s) = \frac{k}{s^2 + (4-k)s + 1}$


For what values of k is the filter stable?

A circuit is stable when all the poles of its transfer function $H(s)$ lie in the left half of the s -plane

$$p_{1,2} = \frac{-(4-k) \pm \sqrt{(4-k)^2 - 4}}{2}$$

$$\rightarrow 4 - k > 0$$

$$\rightarrow \boxed{k < 4}$$

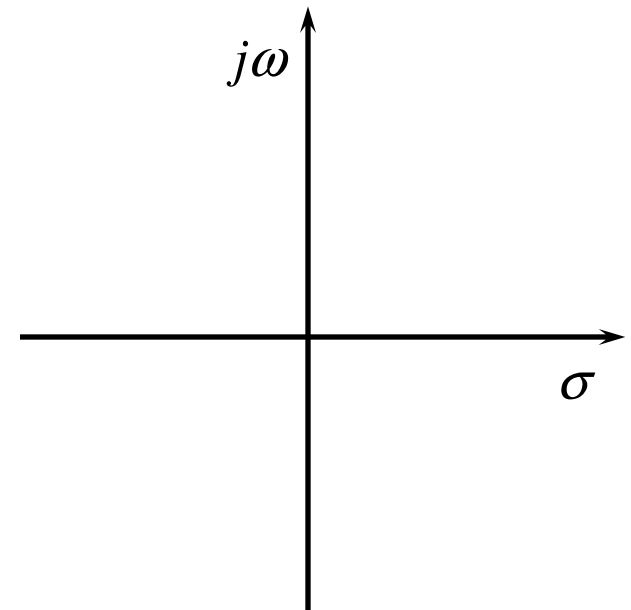

Ex. 7

Transfer Function (10)

Find the frequency responses of the system $H(s) = \frac{1}{s+1}$.

$$\mathbf{H}(j\omega) = H(s)\big|_{s=j\omega} = \frac{1}{j\omega+1} = \frac{j\omega-1}{(j\omega)^2-1^2} = \frac{1}{1+\omega^2} - j\frac{\omega}{1+\omega^2}$$

$$|\mathbf{H}| = \sqrt{\left(\frac{1}{1+\omega^2}\right)^2 + \left(\frac{\omega}{1+\omega^2}\right)^2}$$

$$\angle \mathbf{H} = \text{atan} \left(\frac{\frac{\omega}{1+\omega^2}}{\frac{1}{1+\omega^2}} \right)$$

