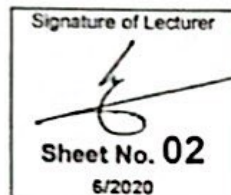


(Documents are allowed to use. Return the question sheet)



Student's name: _____ Student's Code: _____

Question 1 (2 pts)

Given a circuit as in the figure 1.

Write the system of equations for the given circuit using both KCL and KVL (branch current method)?

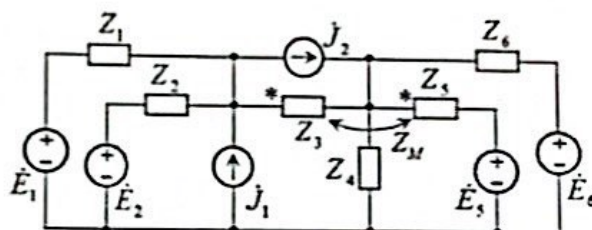


Figure 1

Question 2 (4 pts)

Given a circuit as in the figure 2, where: $Z_1 = 25 + j25\Omega$,

$Z_2 = 20 + j20\Omega$, $Z_3 = 40 + j40\Omega$, $Z_4 = 50 + j50\Omega$,

$\dot{E}_1 = 50\angle 0^\circ V$ (RMS), $\dot{E}_2 = 80\angle 30^\circ V$ (RMS), $Z_M = j5\Omega$,

$\dot{J}_1 = 0.5\angle 0^\circ A$ (RMS), $\dot{J}_2 = 1\angle 45^\circ A$ (RMS)

a) Calculate the effective power delivered by \dot{E}_1 and \dot{J}_2 ?

b) Find the value of Z_1 to obtain the maximum effective power on it, then calculate that maximum power?

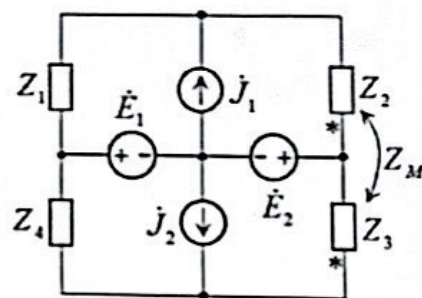


Figure 2

Question 3 (3 pts)

Given a circuit as in the figure 3,

where: $R_1 = 50\Omega$, $R_2 = 20\Omega$,

$C = 5 \cdot 10^{-4} F$, $E_1 = 150V$ (DC),

$E_2 = 35V$ (DC), two pure resistive

two-port networks have the impedance parameters

$$Z = \begin{bmatrix} 100 & -50 \\ 50 & -100 \end{bmatrix} \Omega, \text{ and the}$$

transmission parameters

$$A = \begin{bmatrix} 2 & 50 \\ 0.02 & 1 \end{bmatrix}.$$

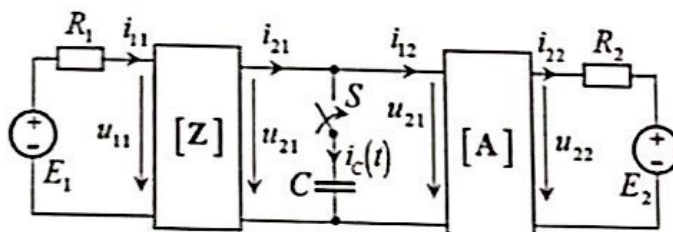


Figure 3

Find the step response $i_c(t)$ when the switch S is closed at the time $t = 0$? (Note that, for $t < 0$, the given circuit was being in steady state)

Note:

Good presentation: 1 pt