

Fundamentals of Electric Circuits

DC Circuits

Chapter 2. Basic Laws

- 2.1. Introduction
- 2.2. Ohm's law
- 2.3. Nodes, branches, and loops
- 2.4. Kirchhoff's laws
- 2.5. Series resistors and voltage division
- 2.6. Parallel resistors and current division
- 2.7. Wye-delta transformations

Basic Laws

2.1. Introduction

+ Understand some fundamental laws:

→ First important steps to determine the values of current, voltage, and power in an electric circuit

+ In this chapter:

→ Ohm's law, Kirchhoff's laws

→ Some common techniques applied in circuit design and analysis

Combining resistors in series and parallel

Voltage division

Current division

Wye – Delta transformations

Basic Laws

2.2. Ohm's law



- + Resisting the flow of electric charge: behavior of materials, in general
- + The ability to resist electric current → **Resistance** (R)

$$R = \rho \frac{l}{A}$$

ρ : **resistivity** of the material [Ωm]

l : **length** of material [m]

A : **cross sectional** area [m^2]

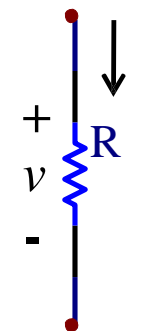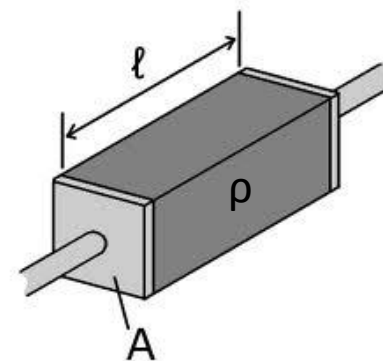

- + **Ohm's law:** *The voltage v across a resistor is directly proportional to the current i flowing through the resistor*

$$v = Ri$$

- + The resistance R of an element: → its ability to resist the flow of electric current, **measured in Ohms** [Ω]

$$R = \frac{v}{i} \rightarrow 1\Omega = 1 \frac{\text{V}}{\text{A}}$$


Basic Laws

2.2. Ohm's law

+ A circuit element with resistance approaching zero:

→ *Short circuit* (current could be anything)


$$R = 0 \rightarrow v = iR = 0$$

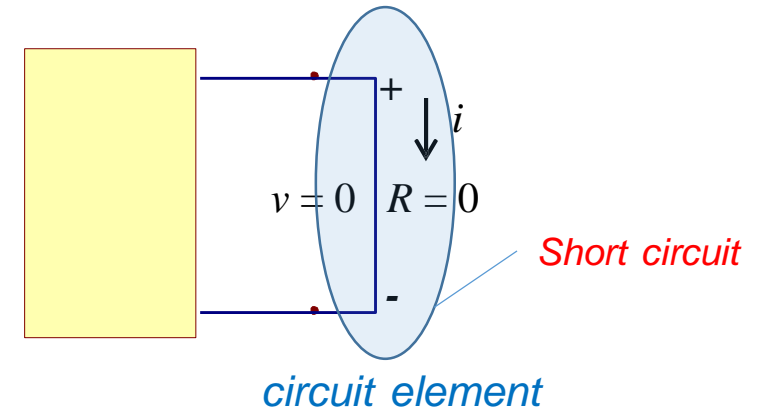

+ A circuit element with resistance approaching infinity:

→ *Open circuit* (voltage could be anything)
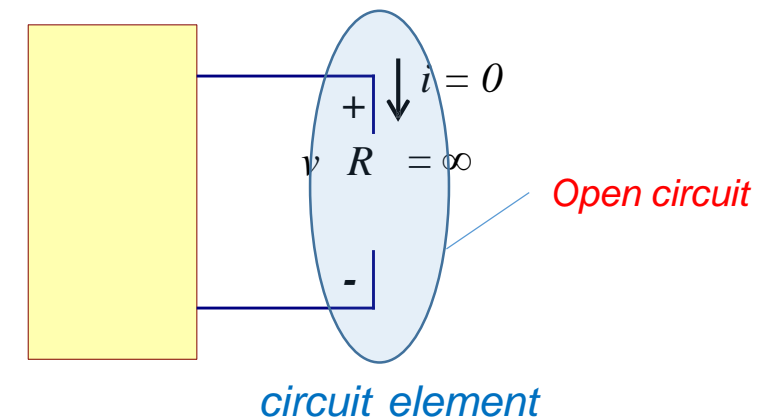
$$i = \lim_{R \rightarrow \infty} \frac{v}{R} = 0$$



2

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Basic Laws

2.2. Ohm's law

+ Resistor classification

→ Fixed resistors



fixed value



Wire wound (small resistance)



Composition (large resistance)

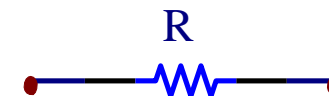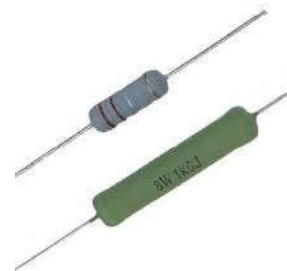

Symbol for fixed resistor

→ Variable resistors

variable value



Two kinds of VR





Symbol for variable resistor

→ Linear and nonlinear resistors

Linear resistor: linear relationship between v and $i \rightarrow R$ is constant

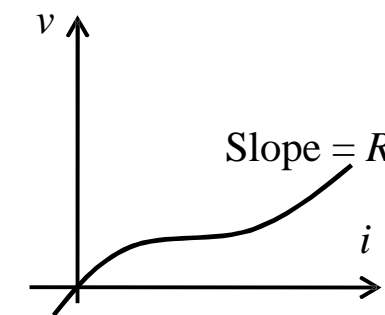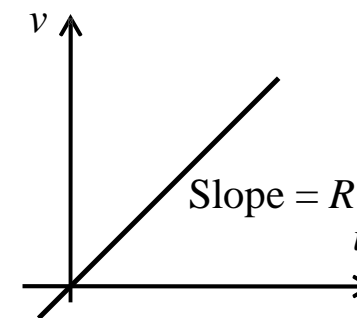Nonlinear resistor: nonlinear relationship between v and $i \rightarrow R$ is not constant (not be considered)



Basic Laws

2.2. Ohm's law

+ The **ability** of an element to **conduct electric current**: **Conductance** (measured in Siemens [S])

$$G = \frac{1}{R} = \frac{i}{v} \quad 1\text{S} = 1\frac{\text{A}}{\text{V}}$$

+ **Power dissipated by a resistor** (conductance)

$$p = vi = i^2 R = \frac{v^2}{R}$$

$$p = vi = v^2 G = \frac{i^2}{G}$$

→ a resistor always absorbs power from the circuit

Basic Laws

2.3. Nodes, branches, and loops

+ **Nodes, branches, loops**: basic concepts of network (**circuit**) topology

a **network** → an interconnection of elements or devices

a **circuit** → a network providing one or more closed paths

+ **Nodes, branches, loops**

Giving information of

→ *geometric configuration of the network/circuit*

→ *properties relating to the placement of elements* in the network

2

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Basic Laws

2.3. Nodes, branches, and loops

+ **A branch** (b): represents a single element (any two terminal element) in a network

Ex: Given circuit has five branches: the 5-V voltage source, the 1-A current source, and three resistors


+ **A node** (n): → the point of connection between two or more branches

Ex: The given circuit has three nodes: a , b , and c

+ **A loop**: → any closed path in a circuit, formed by starting at a node, passing through a set of nodes, and returning to the starting node without passing through any node more than once

Ex: $abca$ is a loop, containing the $R1$, $R2$ and voltage source, or containing the $R1$, $R3$ and voltage source

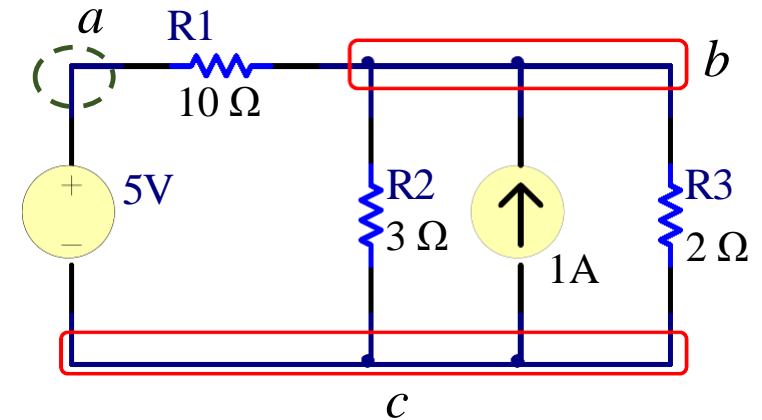→ **Important note**: different definition of node, branch, and loop



2

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Basic Laws


2.3. Nodes, branches, and loops

+ An **independent loop**: → contains a branch which is not in any other loop

Ex: The given circuit → six loops, three of them are independent

+ A network with **b branches**, **n nodes**, and **l independent loops**, has an equation

$$b = l + n - 1$$

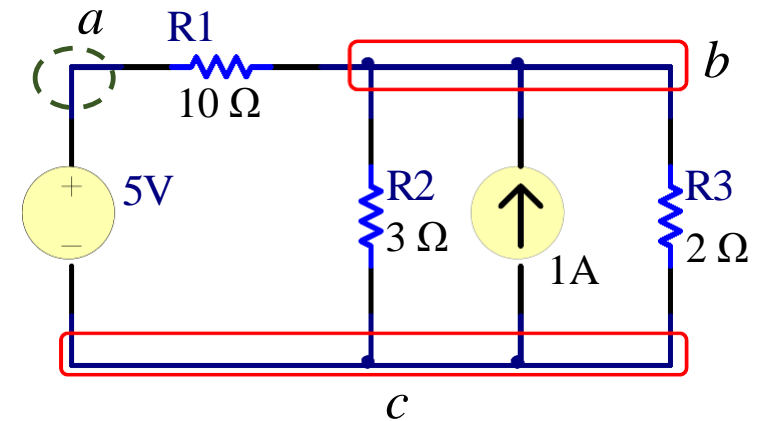

+ Two or more elements are in **series**: → they are cascaded or **connected sequentially** and consequently carry the same current

+ Two or more elements are in **parallel**: → they are **connected to the same two nodes** and sequentially have the **same voltage across them**

Basic Laws

2.4. Kirchhoff's laws



+ **Kirchhoff's current law (KCL):** the algebraic sum of currents entering a node (or a closed boundary) is zero

$$\sum_{n=1}^N i_n = 0$$

Common Convention:

- ❖ Current **entering** a node → regarded as **positive**
- ❖ Current **leaving** the node → taken as **negative**

For example:

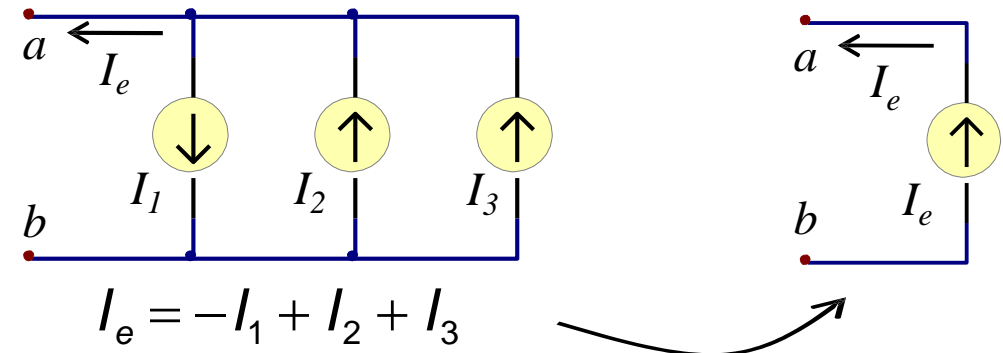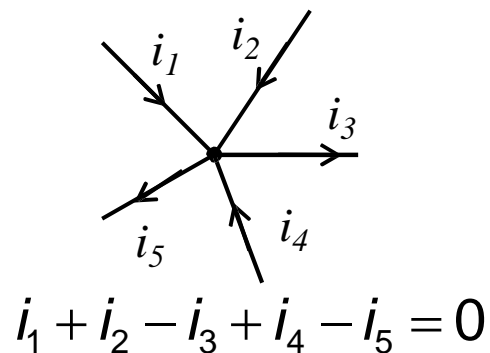

(KCL applied to current sources which connected in parallel)

2

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Basic Laws

2.4. Kirchhoff's laws

+ **Kirchhoff's voltage law (KVL):** the algebraic sum of all voltages around a closed path (or loop) is zero

$$\sum_{m=1}^M v_m = 0$$


For example:

$$-v_1 + v_2 + v_3 + v_4 + v_5 = 0$$




$$v_2 + v_3 + v_5 = v_1 - v_4$$

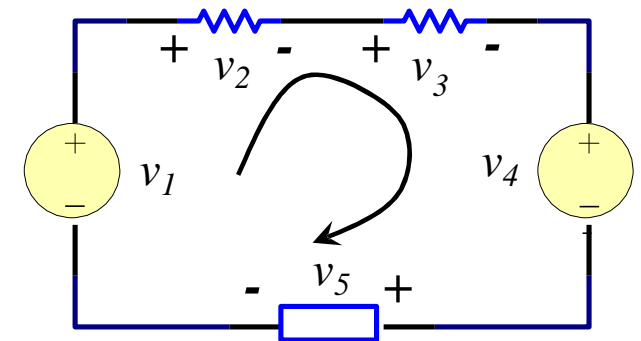(go around the loop either clockwise or counterclockwise)



$$V_{ab} = V_1 + V_2 - V_3$$

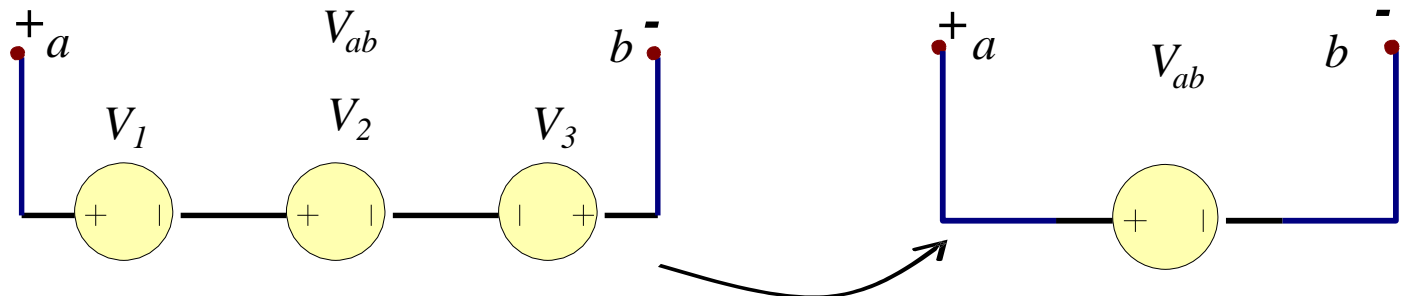(KVL applied to voltage sources which connected in series)



Basic Laws

2.4. Kirchhoff's laws

+ Kirchhoff's laws, coupled with Ohm's law \rightarrow a sufficient and powerful set of tools for analyzing electric circuits

Example 1: find v_1 and v_2 in the given circuit

From Ohm's law: $v_1 = 4i$; $v_2 = -2i$


Applying KVL around the loop gives: $v_1 - v_2 = 10 + 8 = 18$

Substituting i in Ohm's law to KVL: $6i = 18 \rightarrow i = 3A$

So we have:

$$v_1 = 4i = 12V$$

$$v_2 = -2i = -6V$$

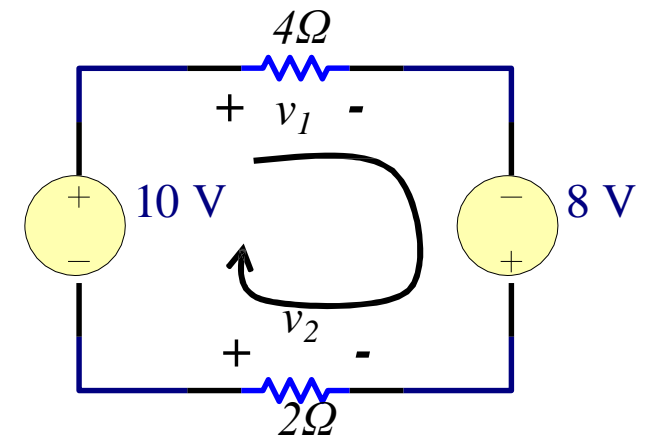

2

FUNDAMENTALS OF ELECTRIC CIRCUITS – DC Circuits

Basic Laws

2.4. Kirchhoff's laws

Example 2: find the currents and voltages in the given circuit

From Ohm's law $v_1 = 2i_1$ $v_2 = 8i_2$ $v_3 = 4i_3$


At node a, applying KCL gives $i_1 - i_2 - i_3 = 0$

Applying KVL to loop 1 and loop 2

$$\begin{cases} v_1 + v_2 = 5 \\ -v_2 + v_3 = 3 \end{cases} \rightarrow \begin{cases} 2i_1 + 8i_2 = 5 \\ -8i_2 + 4i_3 = 3 \end{cases}$$

So we have
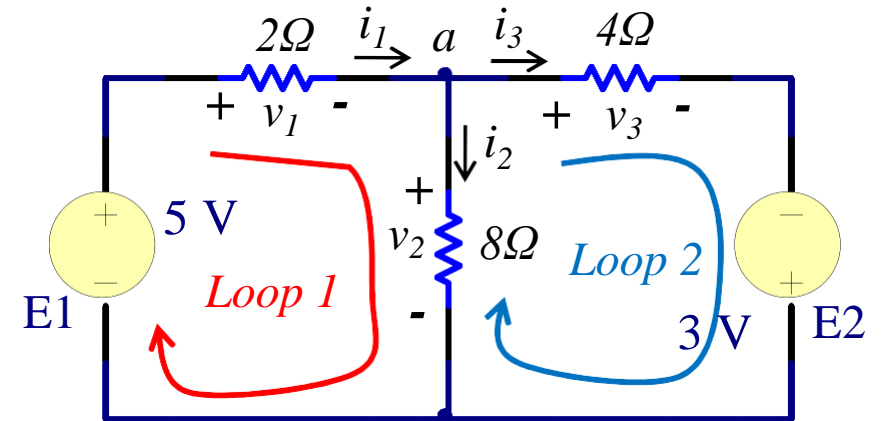
$$\begin{cases} i_1 - i_2 - i_3 = 0 \\ 2i_1 + 8i_2 = 5 \\ -8i_2 + 4i_3 = 3 \end{cases} \rightarrow \begin{cases} i_1 = 1.5A \\ i_2 = 0.25A \\ i_3 = 1.25A \end{cases} \rightarrow \begin{cases} v_1 = 3V \\ v_2 = 2V \\ v_3 = 5V \end{cases}$$



Basic Laws

2.5. Series resistors and voltage division

+ **Equivalent resistance** of any number of resistors connected in series: → the sum of the individual resistances

$$R_{eq} = R_1 + R_2 + \dots + R_N = \sum_{n=1}^N R_n$$

+ **Voltage division**: The voltage v is divided among the resistors in **direct proportion** to their resistances, the larger the resistance, the larger the voltage drop

$$V_n = \frac{R_n}{R_1 + R_2 + \dots + R_N} V$$

Basic Laws

2.6. Parallel resistors and current division

+ **Equivalent resistance** of two parallel resistors: → equal to the product of their resistances divided by their sum

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

(case N parallel resistors)

+ **Equivalent conductance** of resistors connected in parallel: → the sum of their individual conductance

$$G_{eq} = G_1 + G_2 + \dots + G_N = \sum_{n=1}^N G_n$$


+ **Current division**

$$i_n = \frac{G_n}{G_1 + G_2 + \dots + G_N} i$$


Basic Laws

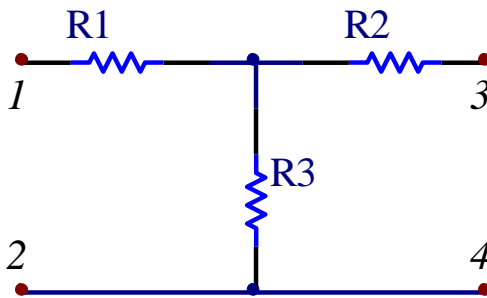2.7. Wye-delta transformations


+ Resistors are neither in series nor in parallel



Wye (Y) or T network

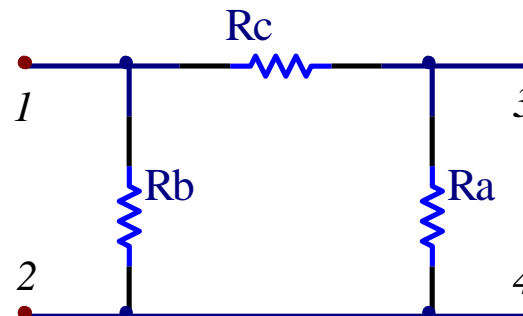

Delta (Δ) or Π network

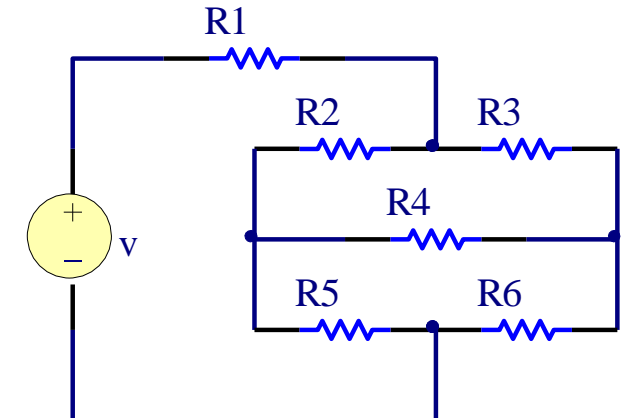



Bridge circuit

+ Delta to Wye conversion

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} ; R_2 = \frac{R_c R_a}{R_a + R_b + R_c} ; R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

Basic Laws

2.7. Wye-delta transformations

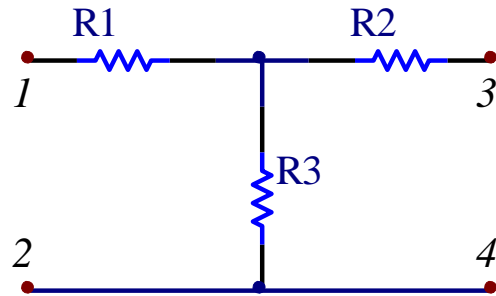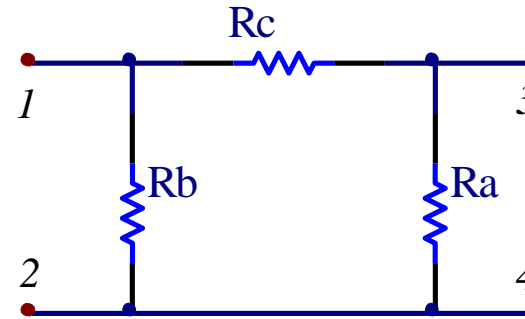*Wye (Y) or T network**Delta (Δ) or Π network*

+ *Wye to Delta conversion*

$$R_a = R_2 + R_3 + \frac{R_2 R_3}{R_1} ; R_b = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$

$$R_c = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

Basic Laws

2.7. Wye-delta transformations

For example: Given a bridge circuit as beside figure, find R_{eq} and i

Having two Y networks: (R_2, R_4, R_6) and (R_3, R_5, R_6)
 → transforming just one of them to simplify the circuit

Applying the Y to Δ transformation:

$$R_a = R_3 + R_5 + \frac{R_3 R_5}{R_6} = 85\Omega \quad R_b = R_5 + R_6 + \frac{R_5 R_6}{R_3} = 170\Omega$$

$$R_c = R_3 + R_6 + \frac{R_3 R_6}{R_5} = 34\Omega$$

The equivalent resistor:

$$R_{eq} = R_1 + \left\{ \left[(R_2 \parallel R_c) + (R_4 \parallel R_b) \right] \parallel R_a \right\} \Rightarrow R_{eq} = 40\Omega$$

The current needed to find:

$$i = \frac{U_{ab}}{R_{eq}} = \frac{100}{40} = 2.5A$$

